 


Analog Fundamentals

A SYSTEMS APPROACH

THOMAS L. FLOYD

DAVID M. BUCHLA



ANALOG FUNDAMENTALS

A SYSTEMS APPROACH

THOMAS L. FLOYD
DAVID M. BUCHLA

PEARSON

Boston Columbus Indianapolis New York San Francisco Upper Saddle River
Amsterdam Cape Town Dubai London Madrid Milan Munich Paris Montreal Toronto
Delhi Mexico City São Paulo Sydney Hong Kong Seoul Singapore Taipei Tokyo

Editorial Director: Vernon R. Anthony
Senior Acquisitions Editor: Lindsey Prudhomme
Development Editor: Dan Trudden
Editorial Assistant: Yvette Schlarman
Director of Marketing: David Gesell
Marketing Manager: Harper Coles
Senior Marketing Coordinator: Alicia Wozniak
Marketing Assistant: Les Roberts
Senior Managing Editor: JoEllen Gohr
Senior Project Manager: Rex Davidson
Senior Operations Supervisor: Pat Tonneman
Creative Director: Andrea Nix
Art Director: Diane Y. Ernsberger
Text and Cover Designer: Candace Rowley
Cover Image: stoupa/Shutterstock.com
Media Project Manager: Karen Bretz
Full-Service Project Management: Penny Walker/Aptara[®], Inc.
Composition: Aptara[®], Inc.
Printer/Binder: R. R. Donnelley & Sons
Cover Printer: Lehigh/Phoenix Color Hagerstown
Text Font: Times Roman

Credits and acknowledgments for materials borrowed from other sources and reproduced, with permission, in this textbook appear on the appropriate page within text.

Copyright © 2013 by Pearson Education, Inc. All rights reserved. Manufactured in the United States of America. This publication is protected by Copyright, and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. To obtain permission(s) to use material from this work, please submit a written request to Pearson Education, Inc., Permissions Department, One Lake Street, Upper Saddle River, New Jersey 07458, or you may fax your request to 201-236-3290.

Many of the designations by manufacturers and sellers to distinguish their products are claimed as trademarks. Where those designations appear in this book, and the publisher was aware of a trademark claim, the designations have been printed in initial caps or all caps.

Library of Congress Cataloging-in-Publication Data

Floyd, Thomas L.
Analog fundamentals : a systems approach / Thomas L. Floyd,
David M. Buchla.
p. cm.
Includes index.
ISBN-13: 978-0-13-293394-0
ISBN-10: 0-13-293394-2
1. Electronic circuits. 2. Electronic apparatus and appliances.
I. Buchla, David M. II. Title.
TK7867.F578 2013
621.3815'3—dc23

2012020324

10 9 8 7 6 5 4 3 2 1

PEARSON

ISBN 10: 0-13-293394-2
ISBN 13: 978-0-13-293394-0

CONTENTS

1	BASIC ANALOG CONCEPTS	1
1-1	Analog Electronics	2
1-2	Analog Signals	5
1-3	Signal Sources	14
1-4	Amplifiers	20
1-5	Troubleshooting	29
2	DIODES AND APPLICATIONS	42
2-1	The Atomic Structure of Semiconductors	43
2-2	The <i>PN</i> Junction	46
2-3	Biasing the Semiconductor Diode	48
2-4	Diode Characteristics	50
2-5	Rectifiers	57
2-6	Rectifier Filters and IC Regulators	63
2-7	Diode Limiting and Clamping Circuits	72
2-8	Special-Purpose Diodes	78
2-9	The Diode Data Sheet	91
2-10	Troubleshooting	95
3	BIPOLAR JUNCTION TRANSISTORS (BJTs)	111
3-1	Structure of Bipolar Junction Transistors	112
3-2	BJT Bias Circuits	121
3-3	Data Sheet Parameters and AC Considerations	131
3-4	Common-Emitter Amplifiers	136
3-5	Common-Collector Amplifiers	143
3-6	Common-Base Amplifiers	147
3-7	The Bipolar Transistor as a Switch	152
3-8	Transistor Packages and Terminal Identification	157
3-9	Troubleshooting	160
4	FIELD-EFFECT TRANSISTORS (FETs)	177
4-1	Structure of Field-Effect Transistors	178
4-2	JFET Characteristics	179
4-3	JFET Biasing	186
4-4	MOSFET Characteristics	194
4-5	MOSFET Biasing	202

- 4-6 FET Linear Amplifiers 205
- 4-7 MOSFET Switching Circuits 216
- 4-8 A System 224

5 MULTISTAGE, RF, AND POWER AMPLIFIERS 239

- 5-1 Capacitively Coupled Amplifiers 240
- 5-2 RF Amplifiers 247
- 5-3 Transformer-Coupled Amplifiers 252
- 5-4 Direct-Coupled Amplifiers 259
- 5-5 Class A Power Amplifiers 265
- 5-6 Class B Power Amplifiers 272
- 5-7 Class C and Class D Power Amplifiers 283
- 5-8 IC Power Amplifiers 293

6 OPERATIONAL AMPLIFIERS 307

- 6-1 Introduction to Operational Amplifiers 308
- 6-2 The Differential Amplifier 310
- 6-3 Op-Amp Data Sheet Parameters 317
- 6-4 Negative Feedback 323
- 6-5 Op-Amp Configurations with Negative Feedback 325
- 6-6 Op-Amp Impedances and Noise 331
- 6-7 Troubleshooting 340

7 OP-AMP RESPONSES 354

- 7-1 Basic Concepts 355
- 7-2 Op-Amp Open-Loop Response 361
- 7-3 Op-Amp Closed-Loop Response 363
- 7-4 Positive Feedback and Stability 366
- 7-5 Op-Amp Compensation 371

8 BASIC OP-AMP CIRCUITS 385

- 8-1 Comparators 386
- 8-2 Summing Amplifiers 396
- 8-3 Integrators and Differentiators 403
- 8-4 Converters and Other Op-Amp Circuits 409
- 8-5 Troubleshooting 411

9 ACTIVE FILTERS 425

- 9-1 Basic Filter Responses 426
- 9-2 Filter Response Characteristics 431

- 9-3 Active Low-Pass Filters 434
- 9-4 Active High-Pass Filters 439
- 9-5 Active Band-Pass Filters 442
- 9-6 Active Band-Stop Filters 448
- 9-7 Filter Response Measurements 450

10 OSCILLATORS AND TIMERS 462

- 10-1 The Oscillator 463
- 10-2 Feedback Oscillator Principles 464
- 10-3 Sinusoidal Oscillators with *RC* Feedback Circuits 466
- 10-4 Oscillators with *LC* Feedback Circuits 475
- 10-5 Relaxation Oscillator Principles 482
- 10-6 The 555 Timer as an Oscillator 488
- 10-7 The 555 Timer as a One-Shot 493

11 VOLTAGE REGULATORS 506

- 11-1 Voltage Regulation 507
- 11-2 Basic Series Regulators 510
- 11-3 Basic Shunt Regulators 516
- 11-4 Basic Switching Regulators 519
- 11-5 Integrated Circuit Voltage Regulators 525
- 11-6 Applications of IC Voltage Regulators 532

12 SPECIAL-PURPOSE AMPLIFIERS 547

- 12-1 Instrumentation Amplifiers 548
- 12-2 Isolation Amplifiers 555
- 12-3 Operational Transconductance Amplifiers (OTAs) 561
- 12-4 Log and Antilog Amplifiers 569

13 COMMUNICATIONS CIRCUITS 585

- 13-1 Basic Receivers 586
- 13-2 The Linear Multiplier 590
- 13-3 Amplitude Modulation 694
- 13-4 The Mixer 600
- 13-5 AM Demodulation 602
- 13-6 IF and Audio Amplifiers 604
- 13-7 Frequency Modulation 607
- 13-8 The Phase-Locked Loop (PLL) 610
- 13-9 Fiber Optics 618

14 DATA CONVERSION 631

- 14-1 Analog Switches 632
- 14-2 Sample-and-Hold Amplifiers 638
- 14-3 Interfacing the Analog and Digital Worlds 643
- 14-4 Digital-to-Analog (D/A) Conversion 646
- 14-5 Basic Concepts of Analog-to-Digital (A/D) Conversion 651
- 14-6 Analog-to-Digital (A/D) Conversion Methods 655
- 14-7 Voltage-to-Frequency (V/F) and Frequency-to-Voltage (F/V) Converters 665
- 14-8 Troubleshooting 674

15 MEASUREMENT AND CONTROL 691

- 15-1 RMS-to-DC Converters 692
- 15-2 Angle Measurement 697
- 15-3 Temperature Measurement 703
- 15-4 Strain Measurement, Pressure Measurement, and Motion Measurement 713
- 15-5 Power Control 720

APPENDIX

Derivations of Selected Equations 733

ANSWERS TO ODD-NUMBERED PROBLEMS 739

GLOSSARY 749

INDEX 755

PREFACE

This first edition of *Analog Fundamentals: A Systems Approach* provides unique coverage of analog devices and circuits with a systems emphasis. Discrete linear devices, operational amplifiers, and important analog integrated circuits are covered with examples of how these devices and circuits are used in electronic systems. Important analog integrated circuits include instrumentation amplifiers, isolation amplifiers, operational transconductance amplifiers, phase-locked loops, and analog-to-digital conversion circuits. Analog devices are still of fundamental importance, even within many “digital” systems. Consequently, many of the system examples focus on these mixed systems. Coverage of analog devices used in switching applications is also included. The text wraps up with a chapter entitled “Measurement and Control,” which includes discussions on transducers and interfacing methods.

As electronics has evolved, the need to understand the relationship among system blocks, interfaces, and input/output signals has increased. We have addressed these changes by including system examples (many with block diagrams) and descriptions in every chapter. The system examples and system notes complement and illustrate the analog concepts covered in the chapter and section in which they appear. Many chapters also include a troubleshooting section that emphasizes the testing and measurements necessary at a system level. Multisim examples and troubleshooting simulations are also included in many of the examples.

The text emphasizes operation and application rather than analysis and design. Both discrete and integrated analog devices are presented from a practical view. Mathematical topics are limited to only essential coverage that a technician or technologist will need to understand the basic concepts. This includes a basic understanding of algebra and trigonometric functions; higher-level mathematics, such as calculus, is not required.

A mix of analog and digital components is very common in real-world applications and systems. Both technologies have their strengths for specific systems. Examples of mixed systems are provided at selected points in the text to illustrate how the two technologies are used together to produce a specific result.

Features

- Systems are emphasized in every chapter with System Examples that are coordinated to the section.
- System Notes throughout the text highlight important ideas or system-related issues such as electronic noise.
- Multisim is used in selected examples, figures, and problems to provide practice in simulating circuits and systems and in troubleshooting.
- Worked examples help to illustrate the function and application of both discrete and integrated analog devices. Practice exercises in each worked example to provide additional practice.
- Each chapter begins with a chapter outline, chapter objectives, key terms list, introduction, and website reference.
- Each section within a chapter begins with an introduction and section objectives.
- Links to manufacturers’ online data sheets are provided for most of the devices covered in each chapter.
- Each section concludes with a set of Checkup questions, which review the main concepts in the section.
- Each chapter ends with a summary, glossary, key formulas list, self-test, troubleshooting quiz, and sectionalized problem set.

- Answers to section checkups, related problems for examples, self-test, and troubleshooting quiz are at the end of each chapter.
- A comprehensive glossary is provided at the end of the text. Key terms are highlighted in bold color and defined at the end of each chapter as well as at the end of the book. Other glossary terms are bold black when first used.
- Answers to odd-numbered problems are provided at the end of the textbook.
- The website includes Multisim files for selected examples, figures, and Multisim troubleshooting practice are in the website (www.pearsonhighered.com).

Student Resources

- *Experiments in Analog Fundamentals: A Systems Approach* (ISBN 0132988674) by David Buchla. Lab exercises are coordinated with the text and solutions are provided in the Instructor's Resource Manual.
- *Multisim Experiments for the DC/AC, Digital, and Devices Courses* (ISBN 0132113880) by Gary Snyder and David Buchla. Students take data, analyze results, and write a conclusion to simulate an actual laboratory experience.
- **Multisim Files Available on the Website** Circuit files coordinated with this text in Versions 11 and 12 of Multisim are located on the website at www.pearsonhighered.com/floyd. Circuit files with prefix F are figure circuits; files with prefix P are Multisim Troubleshooting circuits; and files with prefix SE are System Example circuits.

In order to use the Multisim circuit files, you must have Multisim software installed on your computer. Multisim software is available at www.ni.com/Multisim. Although the Multisim circuit files are intended to complement classroom, textbook, and laboratory study, these files are not essential to successfully using this text.

Instructor Resources

Instructor resources are available from Pearson's **Instructor's Resource Center**.

- PowerPoint® slides (ISBN 0132987708) support the topics in each chapter.
- Instructor's Resource Manual (ISBN 0132988593) contains the solutions to the text problems and the solutions to the lab manual.
- TestGen (ISBN 0132989883) This electronic bank of test questions can be used to develop customized quizzes, tests, and/or exams.

To access supplementary materials online, instructors need to request an instructor access code. Go to www.pearsonhighered.com/irc, where you can register for an instructor access code. Within 48 hours after registering, you will receive a confirming e-mail, including an instructor access code. Once you have received your code, go to the site and log on for full instructions on downloading the materials you wish to use.

Illustrations of Textbook Features

Chapter Opener A typical chapter opener is shown in Figure P-1.

Worked Example, Practice Exercise and Multisim Exercise A typical worked example with Practice Exercise, and Multisim exercise are shown in Figure P-2.

Section Opener A typical section opener and section objectives are shown in Figure P-3.

Section Checkup A typical section checkup is shown in Figure P-3.

System Note A typical system note is shown in Figure P-3.

CHAPTER 5

MULTISTAGE, RF, AND POWER AMPLIFIERS

OUTLINE

- 5-1 Capacitively Coupled Amplifiers
- 5-2 RF Amplifiers
- 5-3 Transformer-Coupled Amplifiers
- 5-4 Direct-Coupled Amplifiers
- 5-5 Class A Power Amplifiers
- 5-6 Class B Power Amplifiers
- 5-7 Class C and Class D Power Amplifiers
- 5-8 IC Power Amplifiers

OBJECTIVES

- Determine the ac parameters for a capacitively coupled multistage amplifier
- Describe the characteristics of high-frequency amplifiers and give practical considerations for implementing high-frequency circuits
- Describe the characteristics of transformer-coupled amplifiers, tuned amplifiers, and mixers
- Determine basic dc and ac parameters for direct-coupled amplifiers and describe how negative feedback can stabilize the gain of an amplifier
- Compute key ac and dc parameters for class A power amplifiers and discuss operation along the ac load line
- Compute key ac and dc parameters for class B power amplifiers including bipolar and FET types
- Describe the characteristics of class C and class D power amplifiers

- Give principal features and describe applications for IC power amplifiers
- Show systems using components and circuits discussed in this chapter

KEY TERMS

Quality factor (Q)	Class B
Intermediate frequency	Push-pull
Mixer	Class AB
Open-loop voltage gain	Current mirror
Closed-loop voltage gain	Class C
Class A	Class D
Power gain	Pulse-width modulation (PWM)
Efficiency	

INTRODUCTION

The previous two chapters have introduced single-stage amplifiers whose primary function was to increase the voltage of a signal. You should be familiar with the biasing and ac parameters for both BJTs and FETs. When very small signals must be amplified, such as from an antenna, variations about the Q-point are relatively small. Amplifiers designed to amplify these signals are called small-signal amplifiers. They may also be designed specifically for high frequencies. Frequently, it is useful to have additional stages of gain; this is particularly true in

VISIT THE WEBSITE
Study aids for this chapter are available at <http://pearsonhighered.com/boyd>

FIGURE P-1 Chapter opener.

EXAMPLE 8-2

Determine the upper and lower trigger points and the hysteresis for the comparator circuit in Figure 8-9. Assume that $+V_{out(max)} = +5\text{ V}$ and $-V_{out(max)} = -5\text{ V}$.

 


FIGURE 8-9

SOLUTION

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)}) = 0.5(5\text{ V}) = +2.5\text{ V}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)}) = 0.5(-5\text{ V}) = -2.5\text{ V}$$

$$V_{HYS} = V_{UTP} - V_{LTP} = 2.5\text{ V} - (-2.5\text{ V}) = 5\text{ V}$$

PRACTICE EXERCISE

Determine the upper and lower trigger points and the hysteresis in Figure 8-9 for $R_1 = 68\text{ k}\Omega$ and $R_2 = 82\text{ k}\Omega$. The maximum output voltage levels are $\pm 7\text{ V}$.

MULTISIM

Open file F08-09 found on the companion website. This simulation demonstrates the operation of a comparator with hysteresis.

Output Bounding

In some applications, it is necessary to limit the output voltage levels of a comparator to a value less than that provided by the saturated op-amp. A single zener diode can be used as shown in Figure 8-10 to limit the output voltage to the zener voltage in one direction and to the forward diode drop in the other. This process of limiting the output range is called **bounding**.

 


FIGURE 8-10 Comparator with output bounding.

The operation is as follows. Since the anode of the zener is connected to the inverting (−) input, it is at virtual ground (0 V) when it has a conducting path. Therefore, when the output voltage reaches a positive value equal to the zener voltage, it limits at that value, as illustrated in Figure 8-11. When the output switches negative, the zener acts as a regular diode and becomes forward-biased at 0.7 V, limiting the negative output voltage to this value, as shown. Turning the zener around limits the output voltage in the opposite direction.

FIGURE P-2 Worked example with Practice Exercise and Multisim exercise.

FIGURE P-3 Section opener, Section Checkup and System note.

7-5 OP-AMP COMPENSATION 371

Noise in Systems

Many systems share power supplies between various assemblies. The longer runs of power supply cables are vulnerable to noise pickup and are conductive paths for noise. As mentioned in this section, power supply leads should have 0.1 to 1 μF tantalum capacitors installed at every circuit board and assembly at the entry point. On circuit boards, every 3 or 4 ICs should also have bypass capacitors on the supply lines. In some systems, the designer will install a separate regulator circuit in each board, to help isolate the main power supply. This is a simple modification but can cure conductive noise problems.

Systems such as radar systems have high power in the same system as sensitive receiver circuits. To avoid noise problems in these systems, it is important to isolate high power signals and utility cables from low-level signal lines. Covers and shields should be checked and kept in place, both for safety and to avoid radiated noise. In many systems, electromagnetic shielding gaskets are used on doors and enclosures to block a path for electromagnetic interference (EMI). These shields are useless if a door or enclosure is left ajar, so it is important to maintain good housekeeping practices.



FIGURE SN7-1 Radio-frequency gasket material for EMI protection. (Courtesy of Leader Tech, Tampa, FL.)



SYSTEM NOTE

SECTION 7-4 CHECKUP

1. Under what feedback condition can an amplifier oscillate?
2. How much can the phase shift of an amplifier's internal RC network be before instability occurs? What is the phase margin at the point where instability begins?

3. What is the maximum roll-off rate of the open-loop gain of an op-amp for which the device will still be stable?

7-5 OP-AMP COMPENSATION

The last section demonstrated that instability can occur when an op-amp's response has roll-off rates exceeding -20 dB/decade and the op-amp is operated in a closed-loop configuration having a gain curve that intersects a higher roll-off rate portion of the open-loop response. In situations like those examined in the last section, the closed-loop voltage gain is restricted to very high values. In many applications, lower values of closed-loop gain are necessary or desirable. To allow op-amps to be operated at low closed-loop gains, phase lag compensation is required. This section may be treated as optional.

After completing this section, you should be able to

- Explain op-amp phase compensation
- Describe phase-lag compensation
- Explain a compensating circuit
- Apply single-capacitor compensation
- Apply feedforward compensation

System Example A typical system example is shown in Figure P-4.

Troubleshooting Section A portion of a typical troubleshooting section is shown in Figure P-5.

FIGURE P-4 System Example.

568 CHAPTER 12 • SPECIAL-PURPOSE AMPLIFIERS

SYSTEM EXAMPLE 12-3

SYNTHESIZED SINE-WAVE GENERATOR

A synthesized sine-wave generator is shown in block diagram form in SE12-5. A synthesized sine-wave generator is a test instrument that can generate a sine wave with a very accurate frequency for testing circuit responses. To generate the sine wave, the user enters the desired parameters into a digital controller. The controller stores the information and passes along data to a sequence generator. This portion of the circuit generates numbers representing amplitude values along the wave at the desired interval and stores the values in a read-only memory. The memory is clocked at a certain interval that depends on the desired frequency and the digital steps are converted to a sine wave by the digital-to-analog converter (covered in Chapter 14). The conversion process produces unwanted higher frequencies components, which are removed with a low-pass filter that is set to pass the desired sine wave but not the higher harmonics. Here is where a transconductance amplifier (OTA) is very useful—the transconductance amplifier can be configured as a voltage-controlled variable cutoff low-pass filter. If the user decides to change frequencies, the low-pass filter is reconfigured by the controller to a new cutoff frequency by sending a certain voltage to it. Voltage-controlled low-pass circuits have other applications (electronic music for example). The circuit description for a variable low-pass filter is available in the manufacturer's specification sheet (see www.national.com for the LM13700 for example).

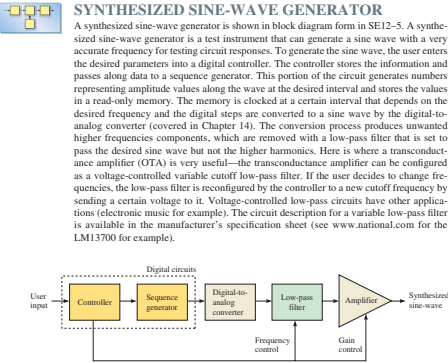


FIGURE SE 12-5 A synthesized sine-wave generator

SECTION 12-3 CHECKUP

1. What does OTA stand for?
2. If the bias current in an OTA is increased, does the transconductance increase or decrease?
3. What happens to the voltage gain if the OTA is connected as a fixed-voltage amplifier and the supply voltages are increased?

4. What happens to the voltage gain if the OTA is connected as a variable-gain voltage amplifier and the voltage at the bias terminal is decreased?

14-8 TROUBLESHOOTING 677

FIGURE 14-56 A method for testing ADCs.

MISSING CODE The staircase output in Figure 14-57(a) indicates that the binary code 1001 does not appear on the output of the ADC. Notice that the 1000 value stays for two intervals and then the output jumps to the 1010 value. In a flash ADC, for example, a failure of one of the comparators can cause a missing-code error.

FIGURE 14-57 Illustrations of A/D conversion errors.

INCORRECT CODES The staircase output in Figure 14-57(b) indicates that several of the binary code words coming out of the ADC are incorrect. Analysis indicates that the 2³-bit line is stuck in the low state in this particular case.

OFFSET Offset conditions are shown in 14-57(c). In this situation, the ADC interprets the analog input voltage as greater than its actual value. This error is probably due to a faulty comparator circuit.

EXAMPLE 14-9

A 4-bit flash ADC is shown in Figure 14-58(a). It is tested with a setup like the one in Figure 14-56. The resulting reconstructed analog output is shown in Figure 14-58(b). Identify the problem and the most probable fault.

FIGURE P-5 Troubleshooting section.

Other Features

End of Chapter The following features are at the end of each chapter.

- Summary
- Glossary
- Key Formulas
- Self-test
- Troubleshooting quiz
- Sectionalized and categorized problem set
- Answers to section checkups, related problems for examples, troubleshooting quiz, and self-test

End of Book The following features are at the end of book.

- Derivations of selected equations
- Answers to odd-numbered problems
- Comprehensive glossary
- Index

To the Student

Any career training requires effort, and the electronics field is no exception. The best way for you to learn new material is by reading, thinking, and doing. This text is designed to help you along the way and to illustrate how discrete and integrated analog devices are used in systems, both large and small.

Read each section of the text carefully and think about what you have read. Sometimes you may need to read the section more than once. Work through each example problem step-by-step before you try the related problem that goes with the example. After each

section, answer the checkup questions. Answers to the related problems and the section checkup questions are at the end of each chapter.

Review the chapter summary, the key term definitions, and the formula list. Review system examples and notes. Multisim examples are a good way to see circuits in action and answer “what-if?” questions you may have. Take the multiple-choice self-test, and the troubleshooting quiz. Check your answers against those at the end of the chapter. Finally, work the problems and compare your answers to the odd-numbered problems with those provided at the end of the book.

The importance of obtaining a thorough understanding of the concepts contained in this text cannot be overemphasized. These will prove to be invaluable when you are dealing with complex analog circuits and systems. If you have a good training in these concepts, an employer will train you in the specifics of the job to which you are assigned.

Acknowledgments

The concept of this series of systems-oriented textbooks is credited to suggestions and discussions with senior instructional staff at ITT Schools and Vern Anthony at Pearson Education. The staff and others at Pearson Education, by their hard work and dedication, have helped make the textbook a reality. Rex Davidson skillfully guided the work through its many detailed phases of production to create the end product that you are now looking at. Dan Trudden, the development editor, has provided effective overall guidance for this project. We also thank acquisitions editor Lindsey Prudhomme.

In addition to the hard work from the staff at Pearson, we appreciate the contributions and many suggestions for system notes and examples from Toby Boydell. In addition to many excellent suggestions, Toby did a complete review of the manuscript. We also thank Gary Snyder for his support in developing the final Multisim exercises throughout the book and his contribution of the Multisim tutorial. Finally, we offer thanks to our wives for the sacrifices made while we worked on the manuscript.

TOM FLOYD
DAVID BUCHLA

CHAPTER 1

BASIC ANALOG CONCEPTS

OUTLINE

- 1-1 Analog Electronics
- 1-2 Analog Signals
- 1-3 Signal Sources
- 1-4 Amplifiers
- 1-5 Troubleshooting

OBJECTIVES

- Discuss the basic characteristics of analog electronics
- Describe analog signals
- Analyze signal sources
- Explain the characteristics of an amplifier
- Describe the process for troubleshooting a circuit

KEY TERMS

Characteristic curve	Thevenin's theorem
Analog signal	Load line
Digital signal	Transducer
Period (T)	Amplifier
Cycle	Gain
Phase angle	Decibel (dB)
Frequency	Attenuation

INTRODUCTION

With the influence of computers and other digital devices, it's easy to overlook the fact that virtually all natural phenomena that we measure (for example, pressure, flow rate, and temperature) originate as analog signals. In electronics, transducers are used to convert these analog quantities into voltage or current. Usually amplification or other processing is required for these signals. Depending on the application, either digital or analog techniques may be more efficient for processing. Analog circuits are found in nearly all power supplies, in many "real-time" applications (such as motor-speed controls), and in high-frequency communication systems. Digital processing is more effective when mathematical operations must be performed and has major advantages in reducing the noise inherent in processing analog signals. In short, the two sides of electronics (analog and digital) complement each other, and the competent technician needs to be knowledgeable of both.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

1-1 ANALOG ELECTRONICS

The field of electronics can be subdivided into various categories for study. The most basic division is to categorize signals between those that are represented by binary numbers (digital) and those that are represented by continuously variable quantities (analog). Digital electronics includes all arithmetic and logic operations such as performed in computers and calculators. Analog electronics includes virtually all other (nondigital) signals. Analog electronics includes signal-processing functions such as amplification, differentiation, and integration. It is true that today almost all information—audio, video, and data—is digitized for transmission, and some types of signal processing. But it is also true that we cannot interact directly with the digital world. We are analog machines, and analog devices continue to play an important role in modern electronics.

After completing this section, you should be able to

- Discuss the basic characteristics of analog electronics
- Contrast the characteristic curve for a linear component with that of a nonlinear component
- Explain what is meant by a characteristic curve
- Compare dc and ac resistance and explain how they differ
- Explain the difference between conventional current and electron flow

Modern electronics had its beginnings in 1907 when Lee deForest first inserted a metallic grid in a vacuum tube and was able to control the current in a circuit. Today, electronic systems still control voltages and currents but use solid-state devices. Basic electronic components, such as resistors or diodes, can be represented with graphs that show their characteristics in a more intuitive manner than mathematical equations. In this section, you will examine graphs representing resistors and diodes. In Chapter 3, you will see how the addition of a control element (like deForest's grid) can also be illustrated with graphs to provide a graphical picture of circuit operation.

Linear Equations

In basic algebra, a linear equation is one that plots a straight line between the variables and is usually written in the following form:

$$y = mx + b$$

where y = the dependent variable

x = the independent variable

m = the slope

b = the y -axis intercept

If the plot of the equation goes through the origin, then the y -axis intercept is zero, and the equation reduces to

$$y = mx$$

which has the same form as Ohm's law.

$$I = \frac{V}{R} \quad (1-1)$$

As written here, the dependent variable in Ohm's law is current (I), the independent variable is voltage (V), and the slope is the reciprocal of resistance ($1/R$). Recall from your dc/ac course that this is simply the conductance, (G). By substitution, the linear form of Ohm's law is more obvious; that is,

$$I = GV$$

A **linear component** is one in which an increase in current is proportional to the applied voltage as given by Ohm's law. In general, a plot that shows the relationship

between two variable properties of a device defines a **characteristic curve**. For most electronic devices, a characteristic curve refers to a plot of the current, I , plotted as a function of voltage, V . For example, resistors have an IV characteristic described by the straight lines given in Figure 1-1. Notice that current is plotted on the y -axis because it is the dependent variable.

 


FIGURE 1-1 IV characteristic curve for two resistors.

EXAMPLE 1-1

Figure 1-1 shows the IV characteristic curve for two resistors. What are the conductance and resistance of R_1 ?

SOLUTION

Find the conductance, G_1 , by measuring the slope of the IV characteristic curve for R_1 . The slope is the change in the y variable (written Δy) divided by the corresponding change in the x variable (written Δx).

$$\text{slope} = \frac{\Delta y}{\Delta x}$$

Choosing the point ($x = 8 \text{ V}$, $y = 10 \text{ mA}$) from Figure 1-1 and the origin, ($x = 0 \text{ V}$, $y = 0 \text{ mA}$), you can find the slope and therefore the conductance as

$$G_1 = \frac{10 \text{ mA} - 0 \text{ mA}}{8.0 \text{ V} - 0 \text{ V}} = \mathbf{1.25 \text{ mS}}$$

For a straight line, the slope is constant so you can use any two points to determine the conductance. The resistance is the reciprocal of the conductance.

$$R_1 = \frac{1}{G_1} = \frac{1}{1.25 \text{ mS}} = \mathbf{0.8 \text{ k}\Omega}$$

PRACTICE EXERCISE*

Find the conductance and resistance of R_2 .

*Answers are at the end of the chapter.

AC Resistance

As you have seen, the graph of the characteristic curve for a resistor is a straight line that passes through the origin. The slope of the line is constant and represents the conductance of the resistor; the reciprocal of the slope represents resistance. The ratio of voltage at

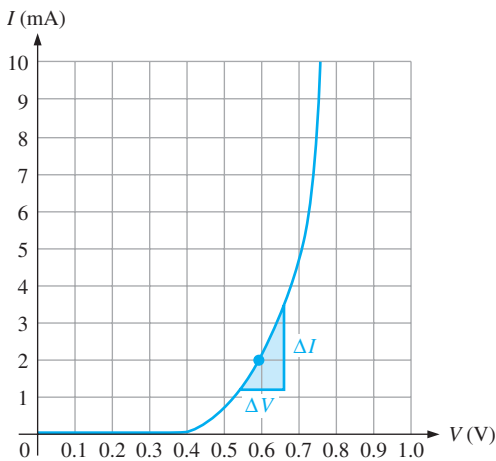


FIGURE 1-2 An *IV* characteristic curve for a diode.

some point to the corresponding current at that point is referred to as *dc resistance*. DC resistance is defined by Ohm's law, $R = V/I$.

Many devices studied in analog electronics have a characteristic curve for which the current is not proportional to the voltage. These devices are nonlinear by nature but are included in the study of analog electronics because they take on a continuous range of input signals.

Figure 1-2 shows an *IV* characteristic curve for a diode, a nonlinear analog device. (Diodes are discussed in Chapter 2.) Generally, it is more useful to define the resistance of a nonlinear analog device as a small *change* in voltage divided by the corresponding *change* in current, that is, $\Delta V/\Delta I$. The ratio of a small change in voltage divided by the corresponding small change in current is defined as the **ac resistance** of an analog device.

$$r_{ac} = \frac{\Delta V}{\Delta I}$$

This internal resistance (indicated with a lowercase italic *r*) is also called the *dynamic*, *small signal*, or *bulk resistance* of the device. The ac resistance depends on the particular point on the *IV* characteristic curve where the measurement is made.

For the diode in Figure 1-2, the slope varies dramatically; the point where the ac resistance is measured needs to be specified with any measurement. For example, the slope at the point $x = 0.6 \text{ V}$, $y = 2 \text{ mA}$ is found by computing the ratio of the change in current to the change in voltage as defined by the small triangle shown in the figure. The change in current, ΔI , is $3.4 \text{ mA} - 1.2 \text{ mA} = 2.2 \text{ mA}$ and the change in voltage, ΔV , is $0.66 \text{ V} - 0.54 \text{ V} = 0.12 \text{ V}$. The ratio of $\Delta I/\Delta V$ is $2.2 \text{ mA}/0.12 \text{ V} = 18.3 \text{ mS}$. This represents the conductance, *g*, at the specified point. The internal ac resistance is the reciprocal of this value:

$$r = \frac{1}{g} = \frac{1}{18.3 \text{ mS}} = 54.5 \Omega$$

Conventional Current Versus Electron Flow

From your dc/ac circuits course, you know that current is the rate of flow of charge. The original definition of current was based on Benjamin Franklin's belief that electricity was an unseen substance that moved from positive to negative. *Conventional current* assumes for analysis purposes that current is out of the positive terminal of a voltage source, through the circuit, and into the negative terminal of the source. Engineers use this definition and many textbooks show current with arrows drawn with this viewpoint.

Today, it is known that in solid metallic conductors, the moving charge is actually negatively charged electrons. Electrons move from the negative to the positive point, opposite to the defined direction of conventional current. The movement of electrons in a conductor is called *electron flow*. Many schools and textbooks show electron flow with current arrows drawn out of the negative terminal of a voltage source.

Unfortunately, the controversy between whether it is better to show conventional current or electron flow in representing circuit behavior has continued for many years and does not appear to be subsiding. It is not important which direction you use to form a mental picture of current. In practice, there is only one correct direction to connect a dc ammeter to make current measurements. Throughout this text, the proper polarity for dc meters is shown when appropriate. Current paths are indicated with special bar meter symbols. In a given circuit, larger or smaller currents are indicated by the relative number of bars shown on a bar graph meter.

SECTION 1-1 CHECKUP*

1. What is a characteristic curve for a component?
2. How does the characteristic curve for a large resistor compare to the curve for a smaller resistor?
3. What is the difference between dc resistance and ac resistance?

1-2 ANALOG SIGNALS

A signal is any physical quantity that carries information. It can be an audible, visual, or other indication of information. In electronics, the term *signal* refers to the information that is carried by electrical waves, either in a conductor or as an electromagnetic field.

After completing this section, you should be able to

- Describe analog signals
- Compare an analog signal with a digital signal
- Define *sampling* and *quantizing*
- Apply the equation for a sinusoidal wave to find the instantaneous value of a voltage or current
- Find the peak, rms, or average value, given the equation for a sinusoidal wave
- Explain the difference between the time-domain signal and the frequency-domain signal

Analog and Digital Signals

Signals can be classified as either continuous or discrete. A continuous signal changes smoothly, without interruption. A discrete signal can have only certain values. The terms *continuous* and *discrete* can be applied either to the amplitude or to the time characteristic of a signal.

In nature, most signals take on a continuous range of values within limits; such signals are referred to as **analog signals**. For example, consider a potentiometer that is used as a shaft encoder as shown in Figure 1-3(a). The output voltage can be continuously varied within the limit of the supply voltage, resulting in an analog signal that is related to the angular position of the shaft.



An analog quantity, such as voltage, that is repetitive or varies in a certain manner is an analog signal. An analog signal can be a repetitive waveform, such as the sine wave in Figure SN1-1(a), or a continuously varying audio signal that carries information (music, the spoken word, or other sounds), as shown in part (b). Other examples of analog signals are amplitude-modulated signals (AM) and frequency-modulated signals (FM), as illustrated in parts (c) and (d). In AM, a lower-frequency information signal, such as voice, varies the amplitude of a high-frequency sine wave. In FM, the information signal varies the frequency of the sine wave.

 


FIGURE SN1-1

On the other hand, another type of encoder has a certain number of steps that can be selected as shown in Figure 1–3(b). When numbers are assigned to these steps, the result is called a **digital signal**.

 


FIGURE 1–3 Analog and digital shaft encoders.

Analog circuits are generally simple, have high speed and low cost, and can readily simulate natural phenomena. They are often used for operations such as performing linearizing functions, waveshaping, transforming voltage to current or current to voltage, multiplying, and mixing. By contrast, digital circuits have high noise immunity, no drift, and the ability to process data rapidly and to perform various calculations. In many electronic systems, a mix of analog and digital signals are required to optimize the overall system's performance or cost.

Many signals have their origin in a natural phenomenon such as a measurement of pressure or temperature. Transducer outputs are typically analog in nature; a microphone, for example, provides an analog signal to an amplifier. Frequently, the analog signal is converted to digital form for storing, processing, or transmitting.

Conversion from analog to digital form is accomplished by a two-step process: sampling and quantizing. **Sampling** is the process of breaking the analog waveform into time "slices" that approximate the original wave. This process always loses some information; however, the advantages of digital systems (noise reduction, digital storage, and processing) outweigh the disadvantages. After sampling, the time slices are assigned a numeric value. This process, called **quantizing**, produces numbers that can be processed by digital computers or other digital circuits. Figure 1–4 illustrates the sampling and quantizing process.

 



FIGURE 1–4 Digitizing an analog waveform.

Frequently, digital signals need to be converted back to their original analog form to be useful in their final application. For instance, the digitized sound on a CD must be converted to an analog signal and eventually back to sound by a loudspeaker.

A cellular phone is a common example of a system that employs both analog and digital signals. The microphone captures voice data which is an *analog* signal. The analog voice data is converted into a *digital* signal and then modulated on an *analog* RF carrier signal. It is then transmitted via the antenna to a cell tower.

In the same way, the incoming signal from the cell tower is received as *digital* intelligence modulated on an *analog* carrier. It is amplified by a low-noise amplifier (LNA) and down-converted using an *analog* carrier frequency. The *digital* voice data is then converted back to *analog* and sent to the audio power amp and finally the speaker.

SYSTEM NOTE

 

Periodic Signals

To carry information, some property such as the voltage or frequency of an electrical wave needs to vary. Frequently, an electrical signal repeats at a regular interval of time. Repeating waveforms are said to be **periodic**. The **period** (T) represents the time for a periodic wave to complete one cycle. A **cycle** is the complete sequence of values that a waveform exhibits before another identical pattern occurs. The period can be measured between any two corresponding points on successive cycles.

Periodic waveshapes are used extensively in electronics. Many practical electronic circuits such as oscillators generate periodic waves. Most oscillators are designed to produce a particular shaped waveform—either a sinusoidal wave or nonsinusoidal waves such as the square, rectangular, triangle, and sawtooth waves.

The most basic and important periodic waveform is the sinusoidal wave. Both the trigonometric sine and cosine functions have the shape of a sinusoidal wave. The term *sine wave* usually implies the trigonometric function, whereas the term *sinusoidal wave* means a waveform with the shape of a sine wave. A sinusoidal waveform is generated as the natural waveform from many ac generators and in radio waves. Sinusoidal waves are also present in physical phenomena from the generation of laser light, the vibration of a tuning fork, or the motion of ocean waves.

A **vector** is any quantity that has both magnitude and direction. A sinusoidal curve can be generated by plotting the projection of the end point of a rotating vector that is turning with uniform circular motion, as illustrated in Figure 1-5. Successive revolutions of the point generate a periodic curve which can be expressed mathematically as

 


FIGURE 1-5 Generation of a sinusoidal waveform from the projection of a rotating vector.

$$y(t) = A \sin(\omega t \pm \phi) \quad (1-2)$$

where $y(t)$ = vertical displacement of a point on the curve from the horizontal axis. The bracketed quantity (t) is an optional indicator, called *functional notation*, to emphasize that the signals vary with time. Functional notation is frequently omitted when it isn't important to emphasize the time relationship but is introduced to familiarize you with the concept when it is shown.

A = amplitude. This is the maximum displacement from the horizontal axis.

ω = angular frequency of the rotating vector in radians per second.

t = time in seconds to a point on the curve.

ϕ = phase angle in radians. The **phase angle** is simply a fraction of a cycle that a waveform is shifted from a reference waveform of the same frequency. It is positive if the curve begins before $t = 0$ and is negative if the curve starts after $t = 0$.

Equation (1-2) illustrates that the sinusoidal wave can be defined in terms of three basic parameters. These are the frequency, amplitude, and phase angle.

FREQUENCY AND PERIOD When the rotating vector has made one complete cycle, it has rotated through 2π radians. The number of complete cycles generated per second is called the **frequency**. Dividing the angular frequency (ω , in rad/s) of the rotating vector by the number of radians in one cycle (2π rad/cycle) gives the frequency in hertz.¹

$$f(\text{Hz}) = \frac{\omega \text{ (rad/s)}}{2\pi \text{ (rad/cycle)}} \quad (1-3)$$

One cycle per second is equal to 1 Hz. The frequency (f) of a periodic wave is the number of cycles in one second and the period (T) is the time for one cycle, so it is logical that the reciprocal of the frequency is the period and the reciprocal of the period is the frequency.

$$T = \frac{1}{f} \quad (1-4)$$

and

$$f = \frac{1}{T} \quad (1-5)$$

For example, if a signal repeats every 10 ms, then its period is 10 ms and its frequency is

$$f = \frac{1}{T} = \frac{1}{10 \text{ ms}} = 0.1 \text{ kHz}$$

INSTANTANEOUS VALUE OF A SINUSOIDAL WAVE If the sinusoidal waveform shown in Figure 1-5 represents a voltage, Equation (1-2) is written

$$v(t) = V_p \sin(\omega t \pm \phi)$$

In this equation, $v(t)$ is a variable that represents the voltage. Since it changes as a function of time, it is often referred to as the *instantaneous voltage*.

PEAK VALUE OF A SINUSOIDAL WAVE The amplitude of a sinusoidal wave is the maximum displacement from the horizontal axis as shown in Figure 1-5. For a voltage waveform, the amplitude is called the peak voltage, V_p . When making voltage measurements with an oscilloscope, it is often easier to measure the peak-to-peak voltage, V_{pp} . The peak-to-peak voltage is twice the peak value.

AVERAGE VALUE OF A SINUSOIDAL WAVE During one cycle, a sinusoidal waveform has equal positive and negative excursions. Therefore, the mathematical definition of the average value of a sinusoidal waveform must be zero. However, the term *average value* is generally used to mean the average over a cycle without regard to the sign. That is, the average is usually computed by converting all negative values to positive values, then averaging. The average voltage is defined in terms of the peak voltage by the following equation:

$$V_{avg} = \frac{2V_p}{\pi}$$

Simplifying,

$$V_{avg} = 0.637V_p \quad (1-6)$$

¹The unit of frequency was cycles per second (cps) prior to 1960 but was renamed the hertz (abbreviated Hz) in honor of Heinrich Hertz, a German physicist who demonstrated radio waves. The old unit designation was more descriptive of the definition of frequency.

The average value is useful in certain practical problems. For example, if a rectified sinusoidal waveform is used to deposit material in an electroplating operation, the quantity of material deposited is related to the average current:

$$I_{avg} = 0.637I_p$$

EFFECTIVE VALUE (rms VALUE) OF A SINUSOIDAL WAVE If you apply a dc voltage to a resistor, a steady amount of power is dissipated in the resistor and can be calculated using the following power law:

$$P = IV \quad (1-7)$$

where V = dc voltage across the resistor (volts)

I = dc current in the resistor (amperes)

P = power dissipated (watts)

A sinusoidal waveform transfers maximum power at the peak excursions of the curve and no power at all at the instant the voltage crosses zero. In order to compare ac and dc voltages and currents, ac voltages and currents are defined in terms of the equivalent heating value of dc. This equivalent heating value is computed with calculus, and the result is called the rms (for *root-mean-square*) voltage or current. The rms voltage is related to the peak voltage by the following equation:

$$V_{rms} = 0.707V_p \quad (1-8)$$

Likewise, the effective or rms current is

$$I_{rms} = 0.707I_p$$

EXAMPLE 1-2

A certain voltage waveform is described by the following equation:

$$v(t) = 15 \text{ V} \sin(600t)$$

- (a) From this equation, determine the peak voltage and the average voltage. Give the angular frequency in rad/s.
- (b) Find the instantaneous voltage at a time of 10 ms.

SOLUTION

- (a) The form of the equation is

$$y(t) = A \sin(\omega t)$$

The peak voltage is the same as the amplitude (A).

$$V_p = 15 \text{ V}$$

The average voltage is related to the peak voltage.

$$V_{avg} = 0.637V_p = 0.637(15 \text{ V}) = 9.56 \text{ V}$$

The angular frequency, ω , is **600 rad/s**.

- (b) The instantaneous voltage at a time of 10 ms is

$$v(t) = 15 \text{ V} \sin(600t) = 15 \text{ V} \sin(600)(10 \text{ ms}) = -4.19 \text{ V}$$

Note the negative value indicates that the waveform is below the axis at this point.

PRACTICE EXERCISE

Find the rms voltage, the frequency in hertz, and the period of the waveform described in the example.

Time-Domain Signals

Thus far, the signals you have looked at vary with time, and it is natural to associate time as the independent variable. Some instruments, such as the oscilloscope, are designed to record signals as a function of time. Time is therefore the independent variable. The values assigned to the independent variable are called the **domain**. Signals that have voltage, current, resistance, or other quantity vary as a function of time are called *time-domain* signals.

Frequency-Domain Signals

Sometimes it is useful to view a signal where frequency is represented on the horizontal axis and the signal amplitude (usually in logarithmic form) is plotted along the vertical axis. Since frequency is the independent variable, the instrument works in the *frequency domain*, and the plot of amplitude versus frequency is called a **spectrum**. The spectrum analyzer is an instrument used to view the spectrum of a signal. These instruments are extremely useful in radio frequency (RF) measurements for analyzing the frequency response of a circuit, testing for harmonic distortion, checking the percent modulation from transmitters, and many other applications.

You have seen how the sinusoidal wave can be defined in terms of three basic parameters. These are the amplitude, frequency, and phase angle. A continuous sinusoidal wave can be shown as a time-varying signal defined by these three parameters. The same sinusoidal wave can also be shown as a single line on a frequency spectrum. The frequency-domain representation gives information about the amplitude and frequency, but it does not show the phase angle. These two representations of a sinusoidal wave are compared in Figure 1-6. The height of the line on the spectrum is the amplitude of the sinusoidal wave.

 


FIGURE 1-6 Time-domain and frequency-domain representations of a sinusoidal wave.

HARMONICS A nonsinusoidal repetitive waveform is composed of a fundamental frequency and harmonic frequencies. The fundamental frequency is the basic repetition rate of the waveform, and the **harmonics** are higher-frequency sinusoidal waves that are multiples of the fundamental. Interestingly, these multiples are all related to the fundamental by integers (whole numbers).

Odd harmonics are frequencies that are odd multiples of the fundamental frequency of a waveform. For example, a 1 kHz square wave consists of a fundamental of 1 kHz and odd harmonics of 3 kHz, 5 kHz, 7 kHz, and so on. The 3 kHz frequency in this case is called the third harmonic, the 5 kHz frequency is called the fifth harmonic, and so on.

Even harmonics are frequencies that are even multiples of the fundamental frequency. For example, if a certain wave has a fundamental of 200 Hz, the second harmonic is 400 Hz, the fourth harmonic is 800 Hz, and the sixth harmonic is 1200 Hz.

Any variation from a pure sinusoidal wave produces harmonics. A nonsinusoidal wave is a composite of the fundamental and certain harmonics. Some types of waveforms have only odd harmonics, some have only even harmonics, and some contain both. The shape of the wave is determined by its harmonic content. Generally, only the fundamental and the

MULTISIM



Open file F01-07 found on the companion website. This simulation illustrates the difference between time-domain and frequency-domain measurements. It also demonstrates how the odd-order harmonics of a fundamental sine wave combine to produce a square wave.

first few harmonics are important in determining the waveshape. For example, a square wave is formed from the fundamental and odd harmonics, as illustrated in Figure 1-7.


 


FIGURE 1-7 Odd harmonics combine to produce a square wave.

Signal distortion is always a concern in any system. One source of distortion is the *harmonic distortion* produced by nonlinear devices. A nonlinear device is one in which the output current is not proportional to changes in the applied voltage. Overdriving an amplifier is one common cause.

Nonlinear devices can also produce another type of distortion called *intermodulation distortion* (IMD). If two or more frequencies are processed by a nonlinear device, intermodulation products that are the sum and difference of the fundamentals and the integer multiples (harmonics) are produced. This is a much less desirable type of distortion.

SYSTEM NOTE

 


FOURIER SERIES All periodic waves except the sinusoidal wave itself are complex waveforms composed of a series of sinusoidal waves. Jean Fourier, a French mathematician interested in problems of heat conduction, formed a mathematical series of trigonometry terms to describe periodic waves. This series is appropriately called the Fourier series.² With the Fourier series, one can mathematically determine the amplitude of each of the sinusoidal waves that compose a complex waveform.


The frequency spectrum developed by Fourier is often shown as an amplitude spectrum with units of voltage or power on the y -axis plotted against Hz on the x -axis. Figure 1-8(a) illustrates the amplitude spectrum for several different periodic waveforms. Notice that all spectrums for periodic waves are depicted as lines located at harmonics of the fundamental frequency. These individual frequencies can be measured with a spectrum analyzer.

Nonperiodic signals such as speech, or other transient waveforms, can also be represented by a spectrum; however, the spectrum is no longer a series of lines as in the case of repetitive waves. Transient waveforms are computed by another method called the *Fourier transform*. The spectrum of a transient waveform contains a continuum of frequencies rather than just harmonically related components. A representative Fourier pair of signals for a nonrepetitive pulse are shown in Figure 1-8(b).

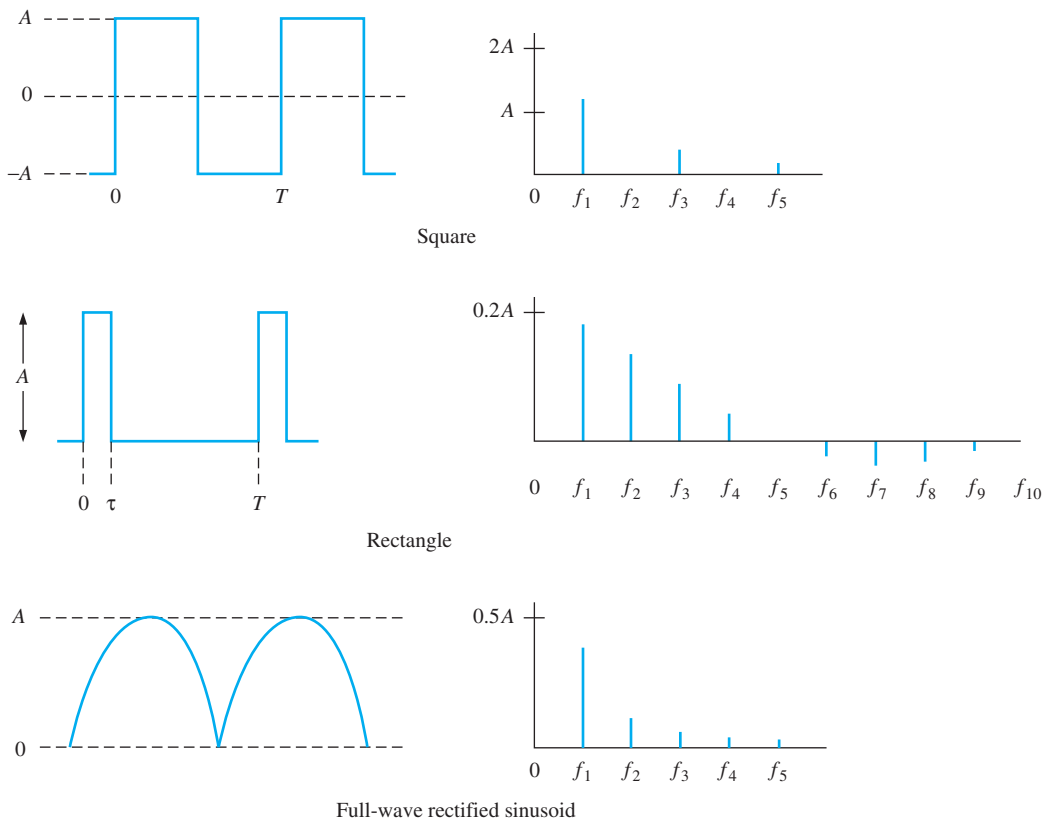²Although Fourier's work was significant and he was awarded a prize, his colleagues were uneasy about it. The famous mathematician, Lagrange, argued in the French Academy of Science that Fourier's claim was impossible. For further information, see *Scientific American*, June 1989, p. 86.



 
(a) Examples of time-domain and frequency-domain representations of repetitive waves



(b) Examples of the frequency spectrum of a nonrepetitive pulse waveform

FIGURE 1-8 Comparison of the frequency spectrum of repetitive and nonrepetitive waves.

SYSTEM EXAMPLE 1-1

 

ANALOG SYSTEMS

An **analog system** is one that processes data in analog form only. One example is a public address system, used to amplify sound so that it can be heard by a large audience. The basic diagram in Figure SE1-1. illustrates that sound waves, which are analog in nature, are picked up by a microphone and converted to a small analog voltage called the audio signal. This voltage varies continuously as the volume and frequency of the sound changes and is applied to the input of a linear amplifier. The output of the amplifier, which is an increased reproduction of input voltage, goes to the speaker(s). The speaker changes the amplified audio signal back to sound waves that have a much greater volume than the original sound waves picked up by the microphone.

 


FIGURE SE1-1 A basic audio public address system.

Another example of an analog system is the FM receiver. The system processes the incoming frequency-modulated carrier signal, extracts the audio signal for amplification, and produces audible sound waves. A block diagram is shown in Figure SE1-2 with a representative signal shown at each point in the system.

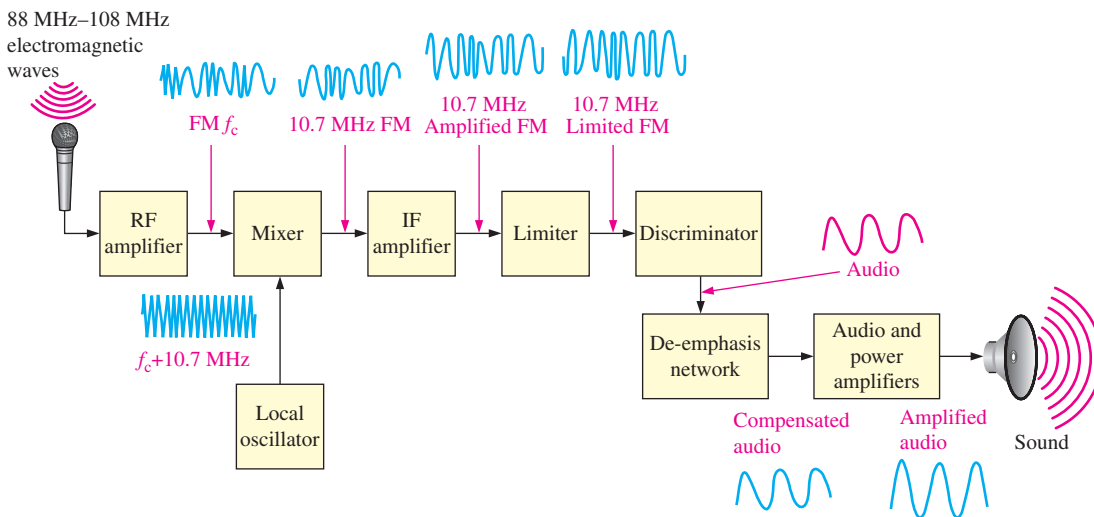


FIGURE SE1-2 Block diagram of superheterodyne FM receiver.

SECTION 1-2 CHECKUP

1. What is the difference between an analog signal and a digital signal?
2. Describe the spectrum for a square wave.
3. How does the spectrum for a repetitive waveform differ from that of a nonrepetitive waveform?

1–3 SIGNAL SOURCES

You may recall from basic electronics that Thevenin’s theorem allows you to replace a complicated linear circuit with a single voltage source and a series resistance. The circuit is viewed from the standpoint of two output terminals. Likewise, Norton’s theorem allows you to replace a complicated two-terminal, linear circuit with a single current source and a parallel resistance. These important theorems are useful for simplifying the analysis of a wide variety of circuits and should be thoroughly understood.

After completing this section, you should be able to

- Analyze signal sources
- Define two types of independent sources
- Draw a Thevenin or Norton equivalent circuit for a dc resistive circuit
- Show how to draw a load line for a Thevenin circuit
- Explain the meaning of Q-point
- Explain how a passive transducer can be modeled with a Thevenin equivalent circuit

Independent Sources

Signal sources can be defined in terms of either voltage or current and may be defined for either dc or ac. An ideal independent voltage source generates a voltage which does not depend on the load current. An ideal independent current source produces a current in the load which does not depend on the voltage across the load.

The value of an ideal independent source can be specified without regard to any other circuit parameter. Although a truly ideal source cannot be realized, in some cases, (such as a regulated power supply), it can be closely approximated. Actual sources can be modeled as consisting of an ideal source and a resistor (or other passive component for ac sources).

Thevenin’s Theorem

Thevenin’s theorem allows you to replace a complicated, two-terminal linear circuit with an ideal independent voltage source and a series resistance as illustrated in Figure 1–9. The source can be either a dc or ac source (a dc source is shown). **Thevenin’s theorem** provides an equivalent circuit from the standpoint of the two output terminals. That is, the original circuit and the Thevenin circuit will produce exactly the same voltage and current in any load. Thevenin’s theorem is particularly useful for analysis of linear circuits such as amplifiers, a topic that will be covered in Section 1–4.


 


FIGURE 1–9 Thevenin’s equivalent for a dc circuit.


Only two quantities are needed to determine the equivalent Thevenin circuit—the Thevenin voltage and the Thevenin resistance. The Thevenin voltage, V_{TH} , is the open circuit (no load, NL) voltage from the original circuit. The Thevenin resistance, R_{TH} , is the resistance from the point of view of the output terminals with all voltage or current sources replaced by their internal resistance.

 EXAMPLE 1-3


Find the equivalent Thevenin circuit for the dc circuit shown in Figure 1-10(a). The output terminals are represented by the open circles.



 (a) Original circuit with load resistor, R_L



 (b) Original circuit with load resistor, R_L , removed



(c) Thevenin equivalent of original circuit

FIGURE 1-10 Simplifying a circuit with Thevenin's theorem.

SOLUTION

Find the Thevenin voltage by computing the voltage on the output terminals *as if the load were removed* as shown in Figure 1-10(b). With no load, there is no path for current through R_4 . Therefore, there is no current and no voltage drop will appear across it. The output (Thevenin) voltage must be the same as the drop across R_2 . Applying the voltage-divider rule for the equivalent series combination of R_1 , R_2 , and R_3 , the voltage across R_2 is

$$\begin{aligned} V_{\text{TH}} = V_2 &= V_S \left(\frac{R_2}{R_1 + R_2 + R_3} \right) \\ &= 12 \text{ V} \left(\frac{470 \Omega}{150 \Omega + 470 \Omega + 220 \Omega} \right) = \mathbf{6.71 \text{ V}} \end{aligned}$$

The Thevenin resistance is the resistance from the perspective of the output terminals with sources replaced with their internal resistance. The internal resistance of a voltage source is zero (ideally). Replacing the source with zero resistance places R_1 and R_3 in series and the combination in parallel with R_2 . The equivalent resistance of these three resistors is in series with R_4 . Thus, the Thevenin resistance for this circuit is

$$\begin{aligned} R_{\text{TH}} &= [(R_1 + R_3) \parallel R_2] + R_4 \\ &= [(150 \Omega + 220 \Omega) \parallel 470 \Omega] + 100 \Omega = \mathbf{307 \Omega} \end{aligned}$$

The Thevenin circuit is shown in Figure 1-10(c).

PRACTICE EXERCISE

Use the Thevenin circuit to find the voltage across the 330 Ω load resistor.

Thevenin's theorem is a useful way of combining linear circuit elements to form an equivalent circuit that can be used to answer questions with respect to various loads. The requirement that the Thevenin circuit elements are linear places some restrictions on the use of Thevenin's theorem. In spite of this, if the circuit to be replaced is approximately linear, Thevenin's theorem may produce useful results. This is the case for many amplifier circuits that we will investigate later.

 


FIGURE 1-11 Norton circuit. The arrow in the current source symbol always points to the positive side of the source.


Norton's Theorem

Norton's theorem provides another equivalent circuit similar to the Thevenin equivalent circuit. Norton's equivalent circuit can also replace any two-terminal linear circuit with a reduced equivalent. Instead of a voltage source, the Norton equivalent circuit uses a current source in parallel with a resistance, as illustrated in Figure 1-11.


The magnitude of the Norton current source is found by replacing the load with a short and determining the current in the load. The Norton resistance is the same as the Thevenin resistance.

 EXAMPLE 1-4


Find the equivalent Norton circuit for the dc circuit shown in Figure 1-12(a). The output terminals are represented by the open circles.




(a) Original circuit

 

(b) R_L replaced with a short

 

 (c) R_2 and R_4 form an equivalent parallel resistor.



(d) The current in the short is equal to the Norton current.

FIGURE 1-12 Simplifying a circuit with Norton's theorem.

SOLUTION

Find the Norton current by computing the current in the load *as if it were replaced by a short* as shown in Figure 1-12(b). The shorted load causes R_4 to appear in parallel with R_2 as shown in Figure 1-12(b). The total current in the equivalent circuit of Figure 1-12(c) can be found by applying Ohm's law to the total resistance.

$$I = \frac{V_S}{R_T} = \frac{12 \text{ V}}{R_1 + R_{2,4} + R_3} = \frac{12.0 \text{ V}}{452.5 \Omega} = 26.5 \text{ mA}$$

The current (I_{SL}) in the shorted load is found by applying the current-divider rule to the R_2 and R_4 junction in the circuit of Figure 1-12(b).

$$I_{SL} = I_T \left(\frac{R_2}{R_2 + R_4} \right) = 26.5 \text{ mA} \left(\frac{470 \Omega}{470 \Omega + 100 \Omega} \right) = \mathbf{21.9 \text{ mA}}$$

The current in the shorted load is the Norton current. The Norton resistance is equal to the Thevenin resistance, as found in Example 1-3. Notice that the Norton resistance is in parallel with the Norton current source. The equivalent circuit is shown in Figure 1-12(d).

PRACTICE EXERCISE

Use Norton's theorem to find the voltage across the 330Ω load resistor. Show that Norton's theorem gives the same result as Thevenin's theorem for this circuit (see Practice Exercise in Example 1-3).

Load Lines

An interesting way to obtain a “conceptual picture” of circuit operation is through the use of a load line for the circuit. Load lines are introduced here and will be explored further in Chapter 3.

Imagine a linear circuit that has an equivalent Thevenin circuit as shown in Figure 1-13. Let’s see what happens if various loads are placed across the output terminals. First, assume there is a short (zero resistance). In this case, the voltage across the load is zero and the current is given by Ohm’s law.

$$I_L = \frac{V_{TH}}{R_{TH}} = \frac{10 \text{ V}}{1.0 \text{ k}\Omega} = 10 \text{ mA}$$

Now assume the load is an open (infinite resistance). In this case, the load current is zero, and the voltage across the load is equal to the Thevenin voltage.

The two tested conditions represent the maximum and minimum current in the load. Table 1-1 shows the results of trying some more points to see what happens with different loads. Plotting the data as shown in Figure 1-14 establishes an IV curve for the Thevenin circuit. Because the circuit is a linear circuit, *any load that is placed across the output terminals falls onto the same straight line*. This line is called the **load line** for the circuit and describes the driving circuit (in this case, the Thevenin circuit), not the load itself. Since the load line is a straight line, the first two calculated conditions (a short and an open load) are all that are needed to establish it.

 


FIGURE 1-13

TABLE 1-1 • Various load conditions for the circuit in Figure 1-13.		
R_L	V_L	I_L
0 Ω	0.0 V	10.0 mA
250 Ω	2.00 V	8.00 mA
500 Ω	3.33 V	6.67 mA
750 Ω	4.29 V	5.72 mA
1.0 k Ω	5.00 V	5.00 mA
2.0 k Ω	6.67 V	3.33 mA
4.0 k Ω	8.00 V	2.00 mA
open	10.0 V	0.00 mA

 


FIGURE 1-14 Load line for the circuit in Figure 1-13.

Before we leave the topic of load lines, consider one more idea. Recall that a resistor (or any other device) has its own characteristic that can be described by its IV curve. The characteristic curve for a resistor represents all of the possible operating points for the device, whereas the load line represents all of the possible operating points for the circuit. Combining these ideas, you can superimpose the IV curve for a resistor on the plot of the load line for the Thevenin circuit. The intersection of these two lines gives the operating point for the combination.

Figure 1-15(a) shows an 800 Ω load resistor added to the Thevenin circuit from Figure 1-13. The load line for the Thevenin circuit and the characteristic curve for resistor R_1 from Figure 1-1 are shown in Figure 1-15(b). R_1 now serves as a load resistor, R_L . The intersection of the two lines represents the operating point, or **quiescent point**, commonly referred to as the Q-point. Note that the load voltage (4.4 V) and load current (5.6 mA) can be read directly from the graph. In Chapter 3, you will see that this idea can be extended to transistors and other devices to give a graphical tool for understanding circuit operation.

 


FIGURE 1-15 Load line and a resistor IV curve showing the Q-point.

Transducers

Analog circuits are frequently used in conjunction with a measurement that needs to be made. A **transducer** is a device that converts a physical quantity (such as position, pressure, or temperature) from one form to another; for electronic systems, input transducers convert a physical quantity to be measured into an electrical quantity (voltage, current, resistance). Transducers will be covered further in Chapter 15.

The signal from transducers is frequently very small, requiring amplification before being suitable for further processing. Passive transducers, such as strain gages, require a separate source of electrical power (called *excitation*) to perform their job. Others, such as thermocouples, are active transducers; they are self-generating devices that convert a small portion of the quantity to be measured into an electrical signal. Both passive and active transducers are often simplified to a Thevenin or Norton equivalent circuit for analysis.

In order to choose an appropriate amplifier, it is necessary to consider both the size of the source voltage and the size of the equivalent Thevenin or Norton resistance. When the equivalent resistance is very small, Thevenin's equivalent circuit is generally more useful because the circuit approximates an ideal voltage source. When the equivalent resistance is large, Norton's theorem is generally more useful because the circuit approximates an ideal current source. When the source resistance is very high, such as the case with a pH meter, a very high input impedance amplifier must be used. Other considerations, such as the frequency response of the system or the presence of noise, affect the choice of amplifier.

EXAMPLE 1-5

A piezoelectric crystal is used in a vibration monitor. Assume the output of the transducer should be a 60 mV rms sine wave with no load. When a technician connects an oscilloscope with a 10 MΩ input impedance across the output, the voltage is observed to be only 40 mV rms. Based on these observations, draw the Thevenin equivalent circuit for this transducer.

SOLUTION

The open circuit ac voltage is the Thevenin voltage; thus, $V_{th} = 60 \text{ mV}$. The Thevenin resistance can be found indirectly using the voltage-divider rule. The oscilloscope input impedance is considered the load resistance, R_L , in this case. The voltage across the load is

$$V_{R_L} = V_{th} \left(\frac{R_L}{R_L + R_{th}} \right)$$

Rearranging terms,

$$\frac{R_L + R_{th}}{R_L} = \frac{V_{th}}{V_{R_L}}$$

Now solving for R_{th} and substituting the given values,

$$R_{th} = R_L \left(\frac{V_{th}}{V_{R_L}} - 1 \right) = 10 \text{ M}\Omega \left(\frac{60 \text{ mV}}{40 \text{ mV}} - 1 \right) = 5.0 \text{ M}\Omega$$

The equivalent transducer circuit is shown in Figure 1-16.

 


FIGURE 1-16

PRACTICE EXERCISE

Draw the Norton's equivalent circuit for the same transducer.

As you know, an analog quantity is one with continuous values and most quantities in nature are analog. If you graphed the temperature in a typical summer day, you would have a smooth curve of values. A transducer converts the temperature into an electrical quantity (usually a voltage). This voltage is then used as the analog input to a system; a weather station may have several types of transducers each with its own input but all with an electrical output that is then fed to a weather monitoring system.


 


FIGURE SN1-2 Graph of an analog quantity (temperature versus time).

SYSTEM NOTE

 

SECTION 1-3 CHECKUP

1. What is an independent source?
2. What is the difference between a Thevenin and a Norton circuit?
3. What is the difference between a passive and an active transducer?

1-4 AMPLIFIERS

Before processing, most signals require amplification. Amplification is simply increasing the magnitude of a signal (either voltage, current, or both) and is one of the most important operations in electronics. Other operations in the field of linear electronics include signal generation (oscillators), waveshaping, frequency conversion, modulation, and many other processes. In addition to strictly linear or strictly digital circuits, many electronic circuits involve a combination of digital and linear electronics. These include an important class of interfacing circuits that convert analog-to-digital and digital-to-analog. These circuits will be considered in Chapter 14.

After completing this section, you should be able to

- Explain the characteristics of an amplifier
- Write the equations for voltage gain and power gain
- Draw the transfer curve for an amplifier
- Show how an amplifier can be modeled as Thevenin or Norton equivalent circuits to represent the input circuit and the output circuit
- Describe how an amplifier can be formed by cascading stages
- Determine the loading effect of one amplifier stage on another
- Use a calculator to find the logarithm or antilog of a given number
- Compute decibel voltage and power gain for an amplifier or circuit

Linear Amplifiers

The previous discussion on linear circuits can be extended to **amplifiers**. Linear amplifiers produce a magnified replica (**amplification**) of the input signal in order to produce a useful outcome (such as driving a loudspeaker). The concept of an *ideal amplifier* means that the amplifier introduces no noise or distortion to the signal; the output varies in time and replicates the input exactly.

Amplifiers are designed primarily to amplify either voltage or power. For a voltage amplifier, the output signal, $V_{out}(t)$, is proportional to the input signal, $V_{in}(t)$, and the ratio of output voltage to input voltage is voltage **gain**. To simplify the gain equation, you can omit the functional notation, (t) , and simply show the ratio of the output signal voltage to the input signal voltage as

$$A_v = \frac{V_{out}}{V_{in}} \quad (1-9)$$

where A_v = voltage gain

V_{out} = output signal voltage

V_{in} = input signal voltage

A useful way of looking at any circuit is to show the output for a given input. This plot, called a **transfer curve**, shows the response of the circuit. An ideal amplifier is characterized by a straight line that goes to infinity. For an actual linear amplifier, the transfer curve is a straight line until saturation is reached as shown in Figure 1-17. From this plot, the output voltage can be read for a given input voltage.

All amplifiers have certain limits, beyond which they no longer act as ideal. The output of the amplifier illustrated in Figure 1-17 eventually cannot follow the input; at this point the amplifier is no longer linear. Additionally, all amplifiers must operate from a source of energy, usually in the form of a dc power supply. Essentially, amplifiers convert some of this dc energy from the power supply into signal power. Thus, the output signal has larger power than the input signal. Frequently, block diagrams and other circuit representations omit the power supply, but it is understood to be present.

 


FIGURE 1-17 Transfer curve for a linear amplifier.

The Nonlinear Amplifier

Amplifiers are frequently used in situations where the output is not intended to be a replica of the input. These amplifiers form an important part of the field of analog electronics. They include two main categories: waveshaping and switching. A *waveshaping amplifier* is used to change the shape of a waveform. A *switching amplifier* produces a rectangular output from some other waveform. The input can be any waveform, for example, sinusoidal, triangle, or sawtooth. The rectangular output wave is often used as a control signal for some digital applications.

EXAMPLE 1-6

The input and output signals for a linear amplifier are shown in Figure 1-18 and represent an oscilloscope display. What is the voltage gain of the amplifier?

 


FIGURE 1-18 Oscilloscope display.

SOLUTION

The input signal is 2.0 divisions from peak to peak.

$$V_{in} = 2.0 \text{ div} \times 0.2 \text{ V/div} = 0.4 \text{ V}$$

The output signal is 3.2 divisions from peak to peak.

$$V_{out} = 3.2 \text{ div} \times 5.0 \text{ V/div} = 16 \text{ V}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{16 \text{ V}}{0.4 \text{ V}} = \mathbf{40}$$

Note that voltage gain is a ratio of voltages and therefore has no units. The answer is the same if rms or peak values had been used for both the input and output voltages.

PRACTICE EXERCISE

The input to an amplifier is 20 mV. If the voltage gain is 300, what is the output signal?

Another gain parameter is power gain, A_p , defined as the ratio of the signal power out to the signal power in. Power is generally calculated using rms values of voltage or current; however, power gain is a ratio so you can use any consistent units. Power gain, shown as a function of time, is given by the following equation:

$$A_p = \frac{P_{out}}{P_{in}} \quad (1-10)$$

where A_p = power gain

P_{out} = power out

P_{in} = power in

Power can be expressed by any of the standard power relationships studied in basic electronics. For instance, given the voltage and current of the input and output signals, the power gain can be written

$$A_p = \frac{I_{out}V_{out}}{I_{in}V_{in}}$$

where I_{out} = output signal current to the load

I_{in} = input signal current

Power gain can also be expressed by substituting $P = V^2/R$ for the input and output power.

$$A_p = \left(\frac{V_{out}^2/R_L}{V_{in}^2/R_{in}} \right)$$

where R_L = load resistor


R_{in} = input resistance of the amplifier

The particular equation you choose depends on what information is given.


Amplifier Model

An amplifier is a device that increases the magnitude of a signal for use by a load. Although amplifiers are complicated arrangements of transistors, resistors, and other components, a simplified description is all that is necessary when the requirement is to analyze the source and load behavior. The amplifier can be thought of as the interface between the source and load, as shown in Figure 1-19(a) and 1-19(b). You can apply the concept of equivalent circuits, learned in basic electronics courses, to the more complicated case of an amplifier. By drawing an amplifier as an equivalent circuit, you can simplify equations related to its performance.

The input signal from a source is applied to the input terminals of the amplifier, and the output is taken from a second set of terminals. (Terminals are represented by open circles on a schematic.) The amplifier's input terminals present an input resistance, R_{in} , to the source. This input resistance affects the input voltage to the amplifier because it forms a voltage divider with the source resistance.

 

(a) Thevenin output circuit

 

(b) Norton output circuit

FIGURE 1-19 Basic amplifier models showing the equivalent input resistance and dependent output circuits.

The output of the amplifier can be drawn as either a Thevenin or Norton source, as shown in Figure 1-19. The magnitude of this source is dependent on the unloaded gain (A_v) and the input voltage; thus, the amplifier's output circuit (drawn as a Thevenin or Norton equivalent) is said to contain a *dependent* source. The value of a dependent source always depends on voltage or current elsewhere in the circuit.³ The voltage or current values for the Thevenin and Norton cases are shown in Figure 1-19.

Cascaded Stages

The Thevenin and Norton models reduce an amplifier to its “bare-bones” for analysis purposes. In addition to considering the simplified model for source and load effects, the simplified model is also useful to analyze the internal loading when two or more stages are cascaded to form a single amplifier. Consider two stages cascaded as shown in Figure 1-20. The overall gain is affected by loading effects from each of the three loops. The loops are simple series circuits, so voltages can easily be calculated with the voltage-divider rule.

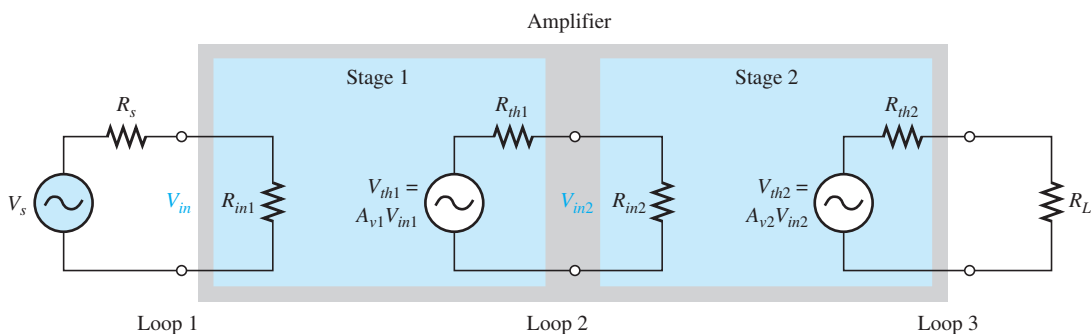


FIGURE 1-20 Cascaded stages in an amplifier.

³The relationship between the dependent source and its reference cannot be broken. The superposition theorem, which allows sources to be treated separately, does not apply to dependent sources.

EXAMPLE 1-7

Assume a transducer with a Thevenin (unloaded) source, V_s , of 10 mV and a Thevenin source resistance, R_s , of 50 k Ω is connected to a two-stage cascaded amplifier, as shown in Figure 1-21. Compute the voltage across a 1.0 k Ω load.

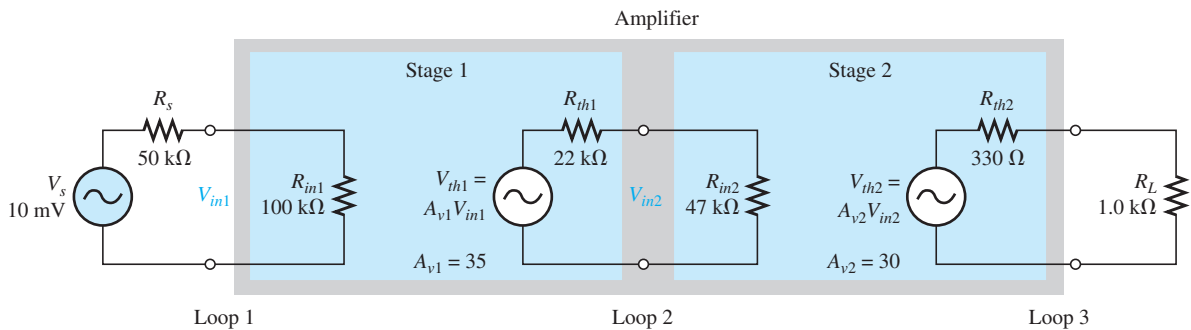


FIGURE 1-21 Two-stage cascaded amplifier.

SOLUTION

Compute the input voltage to stage 1 from the voltage-divider rule applied to loop 1.

$$V_{in1} = V_s \left(\frac{R_{in1}}{R_{in1} + R_s} \right) = 10 \text{ mV} \left(\frac{100 \text{ k}\Omega}{100 \text{ k}\Omega + 50 \text{ k}\Omega} \right) = 6.67 \text{ mV}$$

The Thevenin voltage for stage 1 is

$$V_{th1} = A_{v1} V_{in1} = (35)(6.67 \text{ mV}) = 233 \text{ mV}$$

Compute the input voltage to stage 2 again from the voltage-divider rule, this time applied to loop 2.

$$V_{in2} = V_{th1} \left(\frac{R_{in2}}{R_{in2} + R_{th1}} \right) = 233 \text{ mV} \left(\frac{47 \text{ k}\Omega}{47 \text{ k}\Omega + 22 \text{ k}\Omega} \right) = 159 \text{ mV}$$

The Thevenin voltage for stage 2 is

$$V_{th2} = A_{v2} V_{in2} = (30)(159 \text{ mV}) = 4.77 \text{ V}$$

Apply the voltage-divider rule one more time to loop 3. The voltage across the 1.0 k Ω load is

$$V_{R_L} = V_{th2} \left(\frac{R_L}{R_L + R_{th2}} \right) = 4.77 \text{ V} \left(\frac{1.0 \text{ k}\Omega}{1.0 \text{ k}\Omega + 330 \Omega} \right) = 3.59 \text{ V}$$

PRACTICE EXERCISE

Assume a transducer with a Thevenin source voltage of 5.0 mV and a source resistance of 100 k Ω is connected to the same amplifier. Compute the voltage across the 1.0 k Ω load.

MULTISIM



Open file F01-21 found on the companion website. This circuit is designed to simulate the circuit in Example 1-7 and demonstrate loading effects in cascaded amplifiers.

Logarithms

A widely used unit in electronics is the *decibel*, which is based on logarithms. Before defining the decibel, let's quickly review logarithms (sometimes called *logs*). A **logarithm** is simply an exponent. Consider the equation

$$y = b^x$$

The value of y is determined by the exponent of the base (b). The exponent, x , is said to be the logarithm of the number represented by the letter y .

Two bases are in common use—base ten and base e (discussed in mathematics courses). To distinguish the two, the abbreviation “log” is written to mean base ten, and the

letters “ln” are written to mean base e . Base ten is standard for work with decibels. Thus, for base ten,

$$y = 10^x$$

Solving for x ,

$$x = \log_{10}y$$

The subscript 10 can be omitted because it is implied by the abbreviation “log.”

Logarithms are useful when you multiply or divide very large or small numbers. When two numbers written with exponents are multiplied, the exponents are simply added. That is,

$$10^x \times 10^y = 10^{x+y}$$

This is equivalent to writing

$$\log xy = \log x + \log y$$

This concept will be applied to problems involving multiple stages of amplification or attenuation.

EXAMPLE 1-8

- (a) Determine the logarithm (base ten) for the numbers 2, 20, 200, and 2000.
 (b) Find the numbers whose logarithms are 0.5, 1.5, and 2.5.

SOLUTION

- (a) Determine the logarithms by entering each number in a calculator and pressing the $\boxed{\log}$ key. The results are

$$\begin{array}{ll} \log 2 = \mathbf{0.30103} & \log 20 = \mathbf{1.30103} \\ \log 200 = \mathbf{2.30103} & \log 2000 = \mathbf{3.30103} \end{array}$$

Notice that each factor-of-ten increase in y is an increase of 1.0 in the log.

- (b) Find the number whose logarithm is a given value by entering the given value in a calculator and pressing the $\boxed{10^x}$ function (or $\boxed{\text{INV}} \boxed{\log}$). The results are

$$10^{0.5} = \mathbf{3.16228} \quad 10^{1.5} = \mathbf{31.6228} \quad 10^{2.5} = \mathbf{316.228}$$

Notice that each increase of 1 in x (the logarithm) is a factor-of-10 increase in the number.

PRACTICE EXERCISE

- (a) Find the logarithms for the numbers 0.04, 0.4, 4, and 40.
 (b) What number has a logarithm of 4.8?

Decibel Power Ratios

Power ratios are often very large numbers. Early in the development of telephone communication systems, engineers devised the decibel as a means of describing large ratios of gain or attenuation (a signal reduction). The **decibel (dB)** is defined as 10 multiplied by the logarithmic ratio of the power gain.

$$\text{dB} = 10 \log \left(\frac{P_2}{P_1} \right) \quad (1-11)$$

where P_1 and P_2 are the two power levels being compared.

Previously, power gain was introduced and defined as the ratio of power delivered from an amplifier to the power supplied to the amplifier. To show power gain, A_p , as a decibel ratio, we use a prime in the abbreviation.

$$A'_p = 10 \log\left(\frac{P_{out}}{P_{in}}\right) \quad (1-12)$$

where A'_p = power gain expressed as a decibel ratio

P_{out} = power delivered to a load

P_{in} = power delivered to the amplifier

The decibel (dB) is a dimensionless quantity because it is a ratio. Any two power measurements with the same ratio are the same number of decibels. For example, the power ratio between 500 W and 1 W is 500:1, and the number of decibels this ratio represents is 27 dB. There is exactly the same number of decibels between 100 mW and 0.2 mW (500:1) or 27 dB. When the power ratio is less than 1, there is a power loss or **attenuation**. The decibel ratio is *positive* for power gain and *negative* for power loss.

One important power ratio is 2:1. This ratio is the defining power ratio for specifying the cutoff frequency of instruments, amplifiers, filters, and the like. By substituting into Equation (1-11), the dB equivalent of a 2:1 power ratio is

$$\text{dB} = 10 \log\left(\frac{P_2}{P_1}\right) = 10 \log\left(\frac{2}{1}\right) = 3.01 \text{ dB}$$

This result is usually rounded to 3 dB.

Since 3 dB represents a doubling of power, 6 dB represents another doubling of the original power (a power ratio of 4:1). Nine decibels represents an 8:1 ratio of power and so forth. If the ratio is the same, but P_2 is smaller than P_1 , the decibel result remains the same except for the sign.

$$\text{dB} = 10 \log\left(\frac{P_2}{P_1}\right) = 10 \log\left(\frac{1}{2}\right) = -3.01 \text{ dB}$$

The negative result indicates that P_2 is less than P_1 .

Another useful ratio is 10:1. Since the log of 10 is 1, 10 dB equals a power ratio of 10:1. With this in mind, you can quickly estimate the overall gain (or attenuation) in certain situations. For example, if a signal is attenuated by 23 dB, it can be represented by two 10 dB attenuators and a 3 dB attenuator. Two 10 dB attenuators are a factor of 100 and another 3 dB represents another factor of 2 for an overall attenuation ratio of 1:200.

EXAMPLE 1-9

Compute the overall power gain of the amplifier in Example 1-7. Express the answer as both power gain and decibel power gain.

SOLUTION

The power delivered to the amplifier is

$$P_{in1} = \frac{V_{in1}^2}{R_{in1}} = \frac{(6.67 \text{ mV})^2}{100 \text{ k}\Omega} = 445 \text{ pW}$$

The power delivered to the load is

$$P_{out} = \frac{V_{RL}^2}{R_L} = \frac{(3.59 \text{ V})^2}{1.0 \text{ k}\Omega} = 12.9 \text{ mW}$$

The power gain, A_p , is the ratio of P_{out}/P_{in1} .

$$A_p = \frac{P_{out}}{P_{in1}} = \frac{12.9 \text{ mW}}{445 \text{ pW}} = 29.0 \times 10^6$$

Expressed in dB,

$$A'_p = 10 \log 29.0 \times 10^6 = \mathbf{74.6 \text{ dB}}$$

PRACTICE EXERCISE

Compute the power gain (in dB) for an amplifier with an input power of $50 \mu\text{W}$ and a power delivered to the load of 4 W .

It is common in certain applications of electronics (microwave transmitters, for example) to combine several stages of gain or attenuation. When working with several stages of gain or attenuation, the total voltage gain is the product of the gains in absolute form.

$$A_{v(\text{tot})} = A_{v1} \times A_{v2} \times \cdots \times A_{vn}$$

Decibel units are useful when combining these gains or losses because they involve just addition or subtraction. The algebraic addition of decibel quantities is equivalent to multiplication of the gains in absolute form.

$$A'_{v(\text{tot})} = A'_{v1} + A'_{v2} + \cdots + A'_{vn}$$

EXAMPLE 1-10

Assume the transmitted power from a radar is 10 kW . A directional coupler (a device that samples the transmitted signal) has an output that represents -40 dB of attenuation. Two 3 dB attenuators are connected in series to this output, and the attenuated signal is terminated with a 50Ω terminator (load resistor). What is the power dissipated in the terminator?

SOLUTION

$$\text{dB} = 10 \log \left(\frac{P_2}{P_1} \right)$$

The transmitted power is attenuated by 46 dB (sum of the attenuators). Substituting,

$$-46 \text{ dB} = 10 \log \left(\frac{P_2}{10 \text{ kW}} \right)$$

Divide both sides by 10 and remove the log function.

$$10^{-4.6} = \frac{P_2}{10 \text{ kW}}$$

Therefore,

$$P_2 = \mathbf{251 \text{ mW}}$$

PRACTICE EXERCISE

Assume one of the 3 dB attenuators is removed.

- What is the total attenuation?
- What is the new power dissipated in the terminator?

Although decibel power ratios are generally used to compare two power levels, they are occasionally used for absolute measurements when the reference power level is understood. Although different standard references are used depending on the application, the

most common absolute measurement is the dBm. A **dBm** is the power level when the reference is understood to be 1 mW developed in some assumed load impedance. For radio frequency systems, this is commonly 50 Ω ; for audio systems, it is generally 600 Ω . The dBm is defined as

$$\text{dBm} = 10 \log\left(\frac{P_2}{1 \text{ mW}}\right)$$

The dBm is commonly used to specify the output level of signal generators and is used in telecommunication systems to simplify the computation of power levels.

Decibel Voltage Ratios

Since power is given by the ratio of V^2/R , the decibel power ratio can be written as

$$\text{dB} = 10 \log\left(\frac{V_2^2/R_2}{V_1^2/R_1}\right)$$

where R_1, R_2 = resistances in which P_1 and P_2 are developed

V_1, V_2 = voltages across the resistances R_1 and R_2

If the resistances are equal, they cancel.

$$\text{dB} = 10 \log\left(\frac{V_2^2}{V_1^2}\right)$$

A property of logarithms is

$$\log x^2 = 2 \log x$$

Thus, the decimal voltage ratio is

$$\text{dB} = 20 \log\left(\frac{V_2}{V_1}\right)$$

When V_2 is the output voltage (V_{out}) and V_1 is the input voltage (V_{in}) for an amplifier, the equation defines the decibel voltage gain. By substitution,

$$A'_v = 20 \log\left(\frac{V_{out}}{V_{in}}\right) \quad (1-13)$$

where A'_v = voltage gain expressed as a decibel ratio

V_{out} = voltage delivered to a load

V_{in} = voltage delivered to the amplifier

Equation (1-13) gives the decibel voltage gain, a logarithmic ratio of amplitudes. The equation was originally derived from the decibel power equation when both the input and load resistances are the same (as in telephone systems).

Both the decibel voltage gain equation and decibel power gain equation give the same ratio if the input and load resistances are the same. However, it has become common practice to apply the decibel voltage equation to cases where the resistances are *not* the same. When the resistances are not equal, the two equations do not give the same result.

In the case of decibel voltage gain, note that if the amplitudes have a ratio of 2:1, the decibel voltage ratio is very close to 6 dB (since $20 \log 2 = 6$). If the signal is attenuated by a factor of 2 (ratio = 1:2), the decibel voltage ratio is -6 (since $20 \log 1/2 = -6$). Another useful ratio is when the amplitudes have a 10:1 ratio; in this case, the decibel voltage ratio is 20 dB (since $20 \log 10 = 20$).

EXAMPLE 1-11

An amplifier with an input resistance of 200 k Ω drives a load resistance of 16 Ω . If the input voltage is 100 μV and the output voltage is 18 V, calculate the decibel power gain and the decibel voltage gain.

SOLUTION

The power delivered to the amplifier is

$$P_{in} = \frac{V_{in}^2}{R_{in}} = \frac{(100 \mu\text{V})^2}{200 \text{ k}\Omega} = 5 \times 10^{-14} \text{ W}$$

The output power (delivered to the load) is

$$P_{out} = \frac{V_{out}^2}{R_L} = \frac{(18 \text{ V})^2}{16 \Omega} = 20.25 \text{ W}$$

The decibel power gain is

$$A'_p = 10 \log\left(\frac{P_{out}}{P_{in}}\right) = 10 \log\left(\frac{20.25 \text{ W}}{5 \times 10^{-14} \text{ W}}\right) = \mathbf{146 \text{ dB}}$$

The decibel voltage gain is

$$A'_v = 20 \log\left(\frac{V_{out}}{V_{in}}\right) = 20 \log\left(\frac{18 \text{ V}}{100 \mu\text{V}}\right) = \mathbf{105 \text{ dB}}$$

PRACTICE EXERCISE

A video amplifier with an input resistance of 75 Ω drives a load of 75 Ω .

- How do the power gain and voltage gains compare?
- If the input voltage is 20 mV and the output voltage is 1.0 V, what is the decibel voltage gain?

SECTION 1-4 CHECKUP


- What is an ideal amplifier?
- What is a dependent source?
- What is a decibel?

1-5 TROUBLESHOOTING

Technicians must diagnose and repair malfunctioning circuits or systems. Troubleshooting is the application of logical thinking to correct the malfunctioning circuit or system. Troubleshooting skills will be emphasized throughout the text.

After completing this section, you should be able to

 - Describe the process for troubleshooting a circuit
- Explain what is meant by *half-splitting*
- Cite basic rules for replacing a part in a printed circuit (PC) board
- Describe basic bench test equipment for troubleshooting



Analysis, Planning, and Measuring

When troubleshooting any circuit, the first step is to analyze the clues (symptoms) of a failure. The analysis can begin by determining the answer to several questions: Has the circuit ever worked? If so, under what conditions did it fail? What are the symptoms of a failure? What are possible causes of this failure? The process of asking these questions is part of the analysis of a problem.

After analyzing the clues, the second step in the troubleshooting process is forming a logical plan for troubleshooting. A lot of time can be saved by planning the process. As part of this plan, you must have a working understanding of the circuit you are troubleshooting. Take the time to review schematics, operating instructions, or other pertinent information if you are not certain how the circuit should operate. It may turn out that the failure was that of the operator, not the circuit! A schematic with proper voltages or waveforms marked at various test points is particularly useful for troubleshooting.

Logical thinking is the most important tool of troubleshooting but rarely can solve the problem by itself. The third step is to narrow the possible failures by making carefully thought-out measurements. These measurements usually confirm the direction you are taking in solving the problem or point to a new direction. Occasionally, you may find a totally unexpected result!

The thinking process that is part of analysis, planning, and measuring is best illustrated with an example. Suppose you have a string of 16 decorative lamps connected in series to a 120 V source as shown in Figure 1–22. Assume that this circuit worked at one time and stopped after being moved to a new location. When plugged in, the lamps fail to turn on. How would you go about finding the trouble?

 


FIGURE 1–22 A series of lights. Is one of them open?

You might think like this: Since the circuit worked before it was moved, the problem could be that there is no voltage at this location. Or perhaps the wiring was loose and pulled apart when moved. It's possible a bulb burned out or became loose. This reasoning has considered possible causes and failures that could have occurred. The fact that the circuit was once working eliminates the possibility that the original circuit may have been incorrectly wired. In a series circuit, the possibility of two open paths occurring together is unlikely. You have analyzed the problem and now you are ready to plan the troubleshooting approach.

The first part of your plan is to measure (or test) for voltage at the new location. If voltage is present, then the problem is in the light string. If voltage is not present, check the circuit breakers at the input panel to the house. Before resetting breakers, you should think about why a breaker may be tripped.

The second part of your plan assumes voltage is present and the string is bad. You can disconnect power from the string and make resistance checks to begin isolating the problem. Alternatively, you could apply power to the string and measure voltage at various points. The decision whether to measure resistance or voltage is a toss-up and can be made based on the ease of making the test. Seldom is a troubleshooting plan

developed so completely that all possible contingencies are included. The troubleshooter will frequently need to modify the plan as tests are made. You are ready to make measurements.

Suppose you have a digital multimeter (DMM) handy. You check the voltage at the source and find 120 V present. Now you have eliminated one possibility (no voltage). You know the problem is in the string, so you proceed with the second part of your plan. You might think: Since I have voltage across the entire string, and apparently no current in the circuit (since no bulb is on), there is almost certainly an open in the path—either a bulb or a connection. To eliminate testing each bulb, you decide to break the circuit in the middle and to check the *resistance* of each half of the circuit.

Now you are using logical thinking to reduce the effort needed. The technique you are using is a common troubleshooting procedure called *half-splitting*. By measuring the resistance of half the bulbs at once, you can reduce the effort required to find the open. Continuing along these lines, by half-splitting again, will lead to the solution in a few tests.

Unfortunately, most troubleshooting is more difficult than this example. However, analysis and planning are important for effective troubleshooting. As measurements are made, the plan is modified; the experienced troubleshooter narrows the search by fitting the symptoms and measurements into a possible cause.

Soldering

When repairing circuit boards, sooner or later the technician will need to replace a soldered part. When you replace any part, it is important to be able to remove the old part without damaging the board by excessive force or heat. Transfer of heat for removal of a part is facilitated with a chisel tip (as opposed to a conical tip) on the soldering iron.

Before installing a new part, the area must be clean. Old solder should be completely removed without exposing adjacent devices to excess heat. A degreasing cleaner or alcohol is suggested for cleaning (remember—solder won't stick to a dirty board!). Solder must be a resin core type (acid solder is never used in electronic circuits and shouldn't even be on your workbench!). Solder is applied to the joint (not to the iron). As the solder cools, it must be kept still. A good solder connection is a smooth, shiny one and the solder *flows* into the printed circuit trace. A poor solder connection looks dull. During repair, it is possible for excessive solder to short together two parts or two pins on an integrated circuit (this rarely happens when boards are machine soldered). This is called a solder bridge, and the technician must be alert for this type of error when repairing boards. After the repair is completed, any flux must be removed from the board with alcohol or other cleaner.

Basic Test Equipment

The ability to troubleshoot effectively requires the technician to have a set of test equipment available and to be familiar with the operation of the instruments. An oscilloscope, DMM, and power supply are basic instruments for troubleshooting. These instruments are shown in Figure 1-23. No one instrument is best for all situations, so it is important to understand the limitations of the test equipment at hand. All electronic measuring instruments become part of the circuit they are measuring and thus affect the measurement itself (an effect called *instrument loading*). In addition, instruments are specified for a range of frequencies and must be properly calibrated if readings are to be trusted. An expert troubleshooter must consider these effects when making electronic measurements.

For general-purpose troubleshooting of analog circuits, all technicians need access to an oscilloscope and a DMM. The oscilloscope needs to be a good two-channel scope, fast enough to spot noise or ringing when it occurs. A set of switchable probes, with the ability to switch between $\times 1$ and $\times 10$, is useful for looking at large or small signals. (Note that in the $\times 1$ position, the scope loses bandwidth.)

The DMM is a general-purpose meter that has the advantage of very high input impedance but may yield errors if used in circuits with frequencies above a few kilohertz.



(a) Oscilloscope



(b) Digital multimeter



(c) Power supply

FIGURE 1-23 Test instruments. (Copyright © Tektronix, Inc. Reprinted by permission.)

Many new DMMs offer special features, such as continuity testing and diode checking, and may include capacitance and frequency measurements. While DMMs are excellent test instruments, the VOM (volt-ohm-milliammeter) has some advantages (for example, spotting trends faster than a digital meter). Although generally not as accurate as a DMM, a VOM has very small capacitance to ground, and it is isolated from the line voltage. Also, because a VOM is a passive device, it will not tend to inject noise into a circuit under test.

Many times the circuit under test needs to have a test signal injected to simulate operation in a system. The circuit's response is then observed with a scope or other instrument. This type of testing is called *stimulus-response testing* and is commonly used when a portion of a complete system is tested. For general-purpose troubleshooting, the function generator is used as the stimulus instrument. All function generators have a sine wave, square wave, and triangle wave output; the frequency range varies widely, from a low frequency of 1 μHz to a high of 50 MHz (or more) depending on the generator. Higher-quality function generators offer the user a choice of other waveforms (pulses and ramps, for example) and may have triggered or gated outputs as well as other features.

The basic function generator waveforms (sine, square, and triangle) are used in many tests of electronic circuits and equipment. A common application of a function generator is to inject a sine wave into a circuit to check the circuit's response. The signal is capacitively coupled to the circuit to avoid upsetting the bias network; the response is observed on an oscilloscope. With a sine wave, it is easy to ascertain if the circuit is operating properly by checking the amplitude and shape of the sine wave at various points or to look for possible troubles such as high-frequency oscillation.

A common test for wide-band amplifiers is to inject a square wave into a circuit to test the frequency response. Recall that a square wave consists of the fundamental frequency and an infinite number of odd harmonics (as discussed in Section 1-2). The square wave is applied to the input of the test circuit and the output is monitored. The

shape of the output square wave indicates if specific frequencies are selectively attenuated.

Figure 1-24 illustrates square wave distortions due to selective attenuation of low or high frequencies. A good amplifier should show a high-quality replica of the input. If the square wave sags, as in Figure 1-24(b), low frequencies are not being passed properly by the circuit. The rising edge contains mostly higher-frequency harmonics. If the square wave rolls over before reaching the peak, as in Figure 1-24(c), high frequencies are being attenuated. The rise time of the square wave is an indirect measurement of the bandwidth of the circuit.

For testing dc voltages or providing power to a circuit under test, a multiple output power supply, with both positive and negative outputs, is necessary. The outputs should be variable from 0 to 15 V. A separate low voltage supply is also handy for powering logic circuits or as a dc source for analog circuits.

For certain situations and applications, there are specialized measuring instruments designed for the application. Some of this specialized equipment is designed for a specific frequency range or for a specific application, so they won't be discussed here. The digital storage oscilloscope (DSO) has mostly replaced the analog CRT-based scope. It has some particular advantages for troubleshooting because it can be used to store and compare waveforms from a known good unit or to capture a failure that occurs intermittently. It also has the ability to display events that occur before and after the trigger event, a feature that is invaluable with intermittent problems.

A complete list of “nice to have” accessories could be quite long indeed, but another handy set of instruments is a pulser and pulse tracer. These tools are useful for tracing a short such as one from the power supply to ground. The pulser stimulates the circuit with a series of very short pulses. The current tracer can follow the path of the current and lead right to the short. These tools are useful for both digital and analog circuits.

Other Troubleshooting Materials

In general, some materials that are useful for general-purpose troubleshooting that fall under the “must have” category include the following:

- A basic set of hand tools for electronics, including long-nose pliers, diagonal wire cutters, wire strippers, screwdrivers (especially jeweler's screwdrivers), and a small flashlight.
- Soldering and desoldering tools, including solder wick and a magnifying glass for inspecting work or looking for hairline cracks, solder splashes, or other problems.
- A collection of spare parts (resistors, capacitors, transistors, diodes, switches, ICs). In this category, you will also need extra clip leads, cables with various connectors, banana to alligator converters, heat shrink, and the like.
- A capacitor and a resistor substitution box. This is a useful tool for various tests such as changing the time constant in a circuit under test.
- A hair dryer and freeze spray for testing thermal effects of a circuit.
- A static safe wrist strap (and static-free work station, if possible) to prevent damaging static-sensitive circuits.

SYSTEM EXAMPLE 1-2

THERMOGRAPHY FOR DIAGNOSING SYSTEM FAULTS

All electronic systems, and all the components within that system, dissipate power in one form or another. Discrete components, integrated circuits, and even the wires or circuit board traces that connect components, dissipate some amount of power. The most


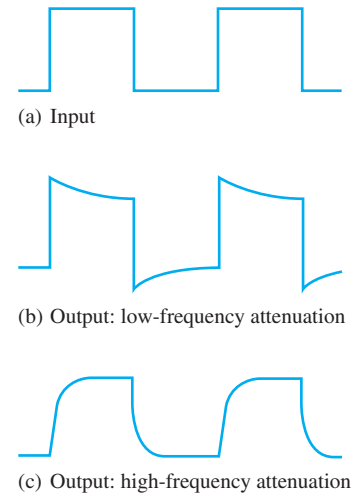


FIGURE 1-24 Square-wave response of wide-band amplifiers.

 

common byproduct of power dissipation is heat. Power amplifiers, by their very nature, tend to produce more heat than small-signal amplifiers. Monitoring the amount of heat that a system produces can be a strong indicator of whether a circuit or sub circuit within a given system is operating within expected parameters. We will begin this topic with a brief discussion of radiant energy.

Figure SE1–3 shows the electromagnetic spectrum. Electromagnetic energy is a continuous band of frequencies that includes visible light, but this is only a small fraction of the electromagnetic spectrum. At longer wavelengths than the visible region there is infrared radiation. The infrared region is subdivided into the *near-infrared*, *mid-infrared*, and the *far-infrared*. It is this far-infrared region that temperature-sensitive nerve endings in our skin sense as thermal energy, as when we are in direct sunlight or stand next to a heat source such as a hot stove. Below the far-infrared are microwave frequencies and radio waves. Above the visible light region are the ultraviolet and x-ray regions.

 


FIGURE SE1–3 The Electromagnetic spectrum

The surfaces of all bodies radiate some electromagnetic energy. You might wonder why if all bodies emit energy all of the time, why don't they eventually radiate all of their energy and cool to absolute zero? The reason is that they also continuously absorb energy from their surroundings. If the amount of energy they absorb is greater than what is radiated, the temperature of the body rises; if it is less, its temperature falls. The wavelength that is emitted depends on the temperature of the body. If a body is hot enough, it radiates energy in the visible spectrum; if it is cooler the radiated energy is primarily in the infrared region.

Although our skin is very sensitive to heat, we have physical limitations in our ability to detect the location and the amount of heat being produced. Thermal imaging instruments provide a radiometric image of any target system that enhances our ability to locate and quantize the amount of heat being produced by the components within the system.

A **radiometric image** is a thermal image that contains temperature measurement calculations for various points within the image. The image is displayed on a screen where colors correspond to the amount of infrared radiation emitted by the components within the target system—the more infrared energy emitted, the more heat being produced.

Figure SE1–4 shows a thermal imager being used to evaluate a piece of electronic equipment. The imager generates a false-color picture of the infrared energy emitted by (and thus the temperature of) the components within the circuit under test. This makes the thermal imager a valuable tool, both in development and testing, as well as in troubleshooting. Note that the thermal imager is not connected to the system and does not impact on its performance in any way.

All electronic systems have a recognizable thermal signature when they are operating correctly. Any variation to this reference thermal signature indicates an abnormal condition which is easily detected, even when a visual inspection shows little indication of a failure. An incorrect thermal signature often precedes a catastrophic failure. Thermal imaging can indicate a poor design before it goes into production, or diagnose a problem before the system fails.



FIGURE SE1-4 Thermal imager showing the temperature profile of the target system (Photo provided courtesy of Fluke Corporation.)

SECTION 1-5 CHECKUP

1. What is the first step in troubleshooting a circuit?
2. What is meant by half-splitting?
3. What is meant by instrument loading?

SUMMARY

- A linear component is one in which an increase in current is proportional to the applied voltage.
- An analog signal takes on a continuous range of values within limits. A digital signal is a discrete signal that can have only certain values. Many circuits use a combination of analog and digital circuits.
- Waveforms that repeat in a certain interval of time are said to be periodic. A cycle is the complete sequence of values that a waveform exhibits before an identical pattern occurs. The period is the time interval for one cycle.
- Signals that have voltage, current, resistance, or other quantity vary as a function of time are called time-domain signals. When the frequency is made the independent variable, the result is a frequency-domain signal. Any signal can be observed in either the time domain or the frequency domain.
- Thevenin's theorem replaces a complicated, two-terminal, linear circuit with an ideal independent voltage source and a series resistance. The Thevenin circuit is equivalent to the original circuit for any load that is connected to the output terminals.
- Norton's theorem replaces a complicated, two-terminal, linear circuit with an ideal independent current source and a parallel resistance. The Norton circuit is equivalent to the original circuit for any load that is connected to the output terminals.
- A transducer is a device that converts a physical quantity from one form to another; for electronic systems, input transducers convert a physical quantity to an electrical quantity (voltage, current, resistance).
- An ideal amplifier increases the magnitude of an input signal in order to produce a useful outcome. For a voltage amplifier, the output signal, $v_{out}(t)$, is proportional to the input signal, $v_{in}(t)$. The ratio of the output voltage to the input voltage is called the voltage gain, A_v .

- The decibel is a dimensionless number that is ten times the logarithmic ratio of two powers. Decibel gains and losses are combined by algebraic addition.
- Troubleshooting begins with analyzing the symptoms of a failure; then forming a logical plan. Carefully thought-out measurements are made to narrow the search for the cause of the failure. These measurements may modify or change the plan.
- For general-purpose troubleshooting, a reasonable fast, two-channel oscilloscope and a DMM are the principal measuring instruments. The most common stimulus instruments are a function generator and a regulated power supply.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Amplifier An electronic circuit having the capability of amplification and designed specifically for that purpose.

Analog signal A signal that can take on a continuous range of values within certain limits.

Attenuation The reduction in the level of power, current, or voltage.

Characteristic curve A plot which shows the relationship between two variable properties of a device. For most electronic devices, a characteristic curve refers to a plot of the current, I , plotted as a function of voltage, V .

Cycle The complete sequence of values that a waveform exhibits before another identical pattern occurs.

Decibel A dimensionless quantity that is 10 times the logarithm of a power ratio or 20 times the logarithm of a voltage ratio.

Digital signal A noncontinuous signal that has discrete numerical values assigned to specific steps.

Frequency The number of repetitions per unit of time for a periodic waveform.

Gain The amount of amplification. Gain is a ratio of an output quantity to an input quantity (e.g., voltage gain is the ratio of the output voltage to the input voltage).

Load line A straight line plotted on a current versus voltage plot that represents all possible operating points for an external circuit.

Period (T) The time for one cycle of a repeating wave.

Phase angle (in radians) The fraction of a cycle that a waveform is shifted from a reference waveform of the same frequency.

Thevenin's theorem An equivalent circuit that replaces a complicated two-terminal linear circuit with a single voltage source and a series resistance.

Transducer A device that converts a physical quantity from one form to another; for example, a microphone converts sound into voltage.

KEY FORMULAS

(1-1)	$I = \frac{V}{R}$	Ohm's law
(1-2)	$y(t) = A \sin(\omega t \pm \phi)$	Instantaneous value of a sinusoidal wave
(1-3)	$f(\text{Hz}) = \frac{\omega \text{ (rad/s)}}{2\pi \text{ (rad/cycle)}}$	Conversion from radian frequency (rad/s) to hertz (Hz)
(1-4)	$T = \frac{1}{f}$	Conversion from frequency to period
(1-5)	$f = \frac{1}{T}$	Conversion from period to frequency
(1-6)	$V_{avg} = 0.637V_p$	Conversion from peak voltage to average voltage for a sinusoidal wave
(1-7)	$P = IV$	Power law
(1-8)	$V_{rms} = 0.707V_p$	Conversion from peak voltage to rms voltage for a sinusoidal wave
(1-9)	$A_v = \frac{V_{out}}{V_{in}}$	Voltage gain


- (1-10) $A_p = \frac{P_{out}}{P_{in}}$ Power gain
- (1-11) $\text{dB} = 10 \log\left(\frac{P_2}{P_1}\right)$ Definition of the decibel
- (1-12) $A'_p = 10 \log\left(\frac{P_{out}}{P_{in}}\right)$ Decibel power gain
- (1-13) $A'_v = 20 \log\left(\frac{V_{out}}{V_{in}}\right)$ Decibel voltage gain

SELF-TEST

Answers are at the end of the chapter.

- The graph of a linear equation
 - always has a constant slope
 - always goes through the origin
 - must have a positive slope
 - answers (a), (b), and (c)
 - none of these answers
- AC resistance is defined as
 - voltage divided by current
 - a change in voltage divided by a corresponding change in current
 - current divided by voltage
 - a change in current divided by a corresponding change in voltage
- A discrete signal
 - changes smoothly
 - can take on any value
 - is the same thing as an analog signal
 - answers (a), (b), and (c)
 - none of these answers
- The process of assigning numeric values to a signal is called
 - sampling
 - multiplexing
 - quantizing
 - digitizing
- The reciprocal of the repetition time of a periodic signal is the
 - frequency
 - angular frequency
 - period
 - amplitude
- If a sinusoidal wave has a peak amplitude of 10 V, the rms voltage is
 - 0.707 V
 - 6.37 V
 - 7.07 V
 - 20 V
- If a sinusoidal wave has a peak-to-peak amplitude of 325 V, the rms voltage is
 - 103 V
 - 115 V
 - 162.5 V
 - 460 V
- Assume the equation for a sinusoidal wave is $v(t) = 200 \sin(500t)$. The peak voltage is
 - 100 V
 - 200 V
 - 400 V
 - 500 V
- A harmonic is
 - an integer multiple of a fundamental frequency
 - an unwanted signal that adds noise to a system
 - a transient signal
 - a pulse
- A Thevenin circuit consists of a
 - current source in parallel with a resistor
 - current source in series with a resistor
 - voltage source in parallel with a resistor
 - voltage source in series with a resistor
- A Norton circuit consists of a
 - current source in parallel with a resistor
 - current source in series with a resistor
 - voltage source in parallel with a resistor
 - voltage source in series with a resistor
- A load line is a plot that describes
 - the IV characteristic curve for a load resistor
 - a driving circuit
 - both (a) and (b)
 - neither (a) nor (b)

 13. The intersection of an IV curve with the load line is called the
 - (a) transfer curve
 - (b) transition point
 - (c) load point
 - (d) Q-point
14. Assume a certain amount of power is attenuated by 20 dB. This is a factor of
 - (a) 10
 - (b) 20
 - (c) 100
 - (d) 200
15. Assume an amplifier has a decibel voltage gain of 100 dB. The output will be larger than the input by a factor of
 - (a) 100
 - (b) 1000
 - (c) 10,000
 - (d) 100,000
16. An important rule for soldering is
 - (a) always use a good acid-based solder
 - (b) always apply solder directly to the iron, never to the parts being soldered
 - (c) wiggle the solder joint as it cools to strengthen it
 - (d) answers (a), (b), and (c)
 - (e) none of these answers



TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 1–22.

- Assume the circuit is plugged in and operating normally. If a bulb is then removed,
 1. The voltage across the socket of the removed bulb will
 - (a) increase
 - (b) decrease
 - (c) not change
 2. The voltage across all other bulbs will
 - (a) increase
 - (b) decrease
 - (c) not change
 3. The voltage to the circuit will
 - (a) increase
 - (b) decrease
 - (c) not change
- Assume one of the sockets in the circuit is shorted with the bulb out, but the other bulbs are on.
 4. As a result of the short, the voltage across each of the other bulbs will
 - (a) increase
 - (b) decrease
 - (c) not change
 5. The total voltage applied to the circuit will
 - (a) increase
 - (b) decrease
 - (c) not change
 6. The light output from the other bulbs will
 - (a) increase
 - (b) decrease
 - (c) not change
- Assume the circuit is disconnected from the source and the resistance is measured between the prongs.
 7. If one of the sockets is shorted, the total resistance will
 - (a) increase
 - (b) decrease
 - (c) not change
 8. If one of the bulbs is open, the total resistance will
 - (a) increase
 - (b) decrease
 - (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 1–1 Analog Electronics

1. What is the conductance of a 22 k Ω resistor?
2. How does the ac resistance of a diode change as the voltage increases?
3. Compute the ac resistance of the diode in Figure 1–2 at the point $V = 0.7$ V, $I = 5.0$ mA.
4. Sketch the shape of an IV curve for a device that has a decreasing ac resistance as voltage increases.

SECTION 1-2 Analog Signals

5. Assume a sinusoidal wave is described by the equation $v(t) = 100 \text{ V} \sin(200t + 0.52)$.
 - (a) From this expression, determine the peak voltage, the average voltage, and the angular frequency in rad/s.
 - (b) Find the instantaneous voltage at a time of 2.0 ms. (Reminder: the angles are in radians in this equation).
6. Determine the frequency (in Hz) and the period (in s) for the sinusoidal wave described in Problem 5.
7. An oscilloscope shows a wave repeating every $27 \mu\text{s}$. What is the frequency of the wave?
8. A DMM indicates the rms value of a sinusoidal wave. If a DMM indicates a sinusoidal wave is 3.5 V, what peak-to-peak voltage would you expect to observe on an oscilloscope?
9. The ratio of the rms voltage to the average voltage for any wave is called the *form factor* (used occasionally to convert meter readings). What is the form factor for a sinusoidal wave?
10. What is the fifth harmonic of a 500 Hz triangular wave?
11. What is the only type of harmonics found in a square wave?

SECTION 1-3 Signal Sources

12. Draw the Thevenin equivalent circuit for the circuit shown in Figure 1-25. Show values on your drawing.
13. Assume a $1.0 \text{ k}\Omega$, $2.7 \text{ k}\Omega$ and $3.6 \text{ k}\Omega$ load resistor are connected, one at a time, across the output terminals of the circuit in Figure 1-25. Determine the voltage across each load.
14. Draw the Norton equivalent circuit for the circuit shown in Figure 1-25. Show values on your drawing.
15. Draw a graph showing the load line for the Thevenin circuit shown in Figure 1-26. On the same graph, show the *IV* curve for a $150 \text{ k}\Omega$ resistor. Show the Q-point on your plot.

 


FIGURE 1-25

 


FIGURE 1-26

16. Assume the output of a transducer is a 10 mV ac signal with no load and drops to 5 mV when a $100 \text{ k}\Omega$ load is connected to the outputs. Based on these observations, draw the Thevenin equivalent circuit for this transducer.
17. Draw the Norton equivalent circuit for the transducer circuit described in Problem 16.

SECTION 1-4 Amplifiers

18. For the amplifier described by the transfer curve in Figure 1-17, what is the voltage gain in the linear region? What is the largest output voltage before saturation?
19. The input to an amplifier is $80 \mu\text{V}$. If the voltage gain of the amplifier is 50,000, what is the output signal?
20. Assume a transducer with a Thevenin (unloaded) voltage of 5.0 mV and a Thevenin resistance of $20 \text{ k}\Omega$ is connected to a two-stage cascaded amplifier with the following specifications:

$$R_{in1} = 50 \text{ k}\Omega$$

$$A_{v1} (\text{unloaded}) = 50$$

$$R_{ih1} = 5 \text{ k}\Omega$$

$$R_{in2} = 10 \text{ k}\Omega$$

$$A_{v2} (\text{unloaded}) = 40$$

$$R_{ih2} = 1.0 \text{ k}\Omega$$

Draw the amplifier model and compute the voltage across a $2.0 \text{ k}\Omega$ load.

21. Compute the decibel voltage gain for the amplifier in Problem 20.
22. Compute the decibel power gain for the amplifier in Problem 20.


23. Assume you want to attenuate the voltage from a signal generator by a factor of 1000. What is the decibel attenuation required?
24. (a) What is the power dissipated in a $50\ \Omega$ load resistor when 20 V is across the load?
(b) Express your answer in dBm.
25. A certain instrument is limited to 2 watts of input power dissipated in its internal $50\ \Omega$ input resistor.
(a) How much attenuation (in dB) is required in order to connect a 20 W source to the instrument?
(b) What is the maximum allowable voltage at the input?

SECTION 1-5 Troubleshooting

26. Figure 1-27 shows a small system consisting of four microphones connected to a two-channel amplifier through a selector switch (SW1). Either the *A* set or the *B* set of microphones is selected and amplified. The output of the amplifier is connected to two speakers. Power to the amplifier is supplied by a single power supply that furnishes dc voltages to the amplifier and two batteries that provide power to two each of the microphones as shown.

Assume no sound is heard when the system is plugged in and turned on. Outline a basic troubleshooting plan by indicating the tests you would make to isolate the trouble to either the power supply, amplifier, a microphone, microphone battery, switch, speaker, or other fault.

FIGURE 1-27 A small system consisting of a two-channel amplifier and four microphones.

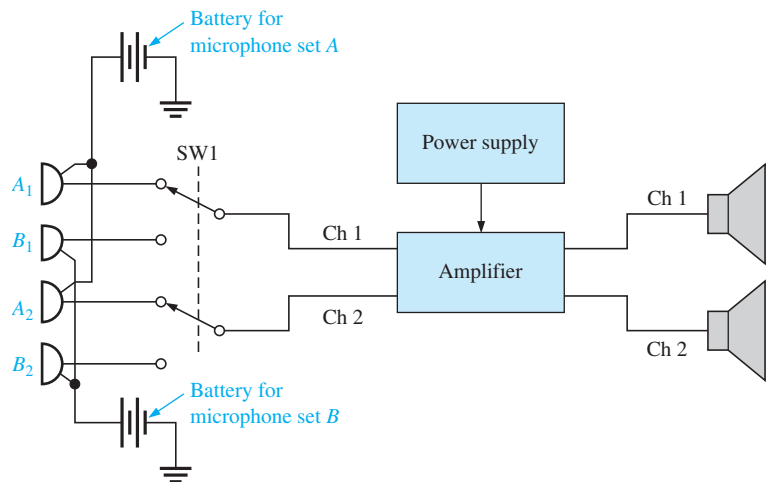

27. For the system described in Problem 26, outline a basic troubleshooting plan for the case where Channel 1 operates normally but no sound is heard from Channel 2. Indicate the tests you would make to isolate the trouble. (Can you think of a method to do half-splitting?)
28. What information is obtained when a square wave calibration signal is used as the input to an oscilloscope?
29. How can you protect a static-sensitive circuit from damage when you are working on it?
30. Cite two important advantages of a digital storage oscilloscope over an analog oscilloscope.

ANSWERS TO SECTION CHECKUPS

SECTION 1-1

1. A characteristic curve is a graph of the relationship between current and voltage for a component.
2. The slope of curve is lower for larger resistors.
3. DC resistance is the voltage divided by the current. AC resistance is the *change* in voltage divided by the *change* in current.

SECTION 1-2

1. An analog signal takes on a continuous range of values; a digital signal represents information that has a discrete number of codes.
2. The spectrum is a line spectrum with a single line at the fundamental and other lines at the odd harmonic frequencies. See Figure 1-8(a).

- The spectrum for the repetitive waveform is a line spectrum; the spectrum for the nonrepetitive waveform is a continuous spectrum.

SECTION 1-3

- An independent source is a voltage or current source that can be specified without regard to any other circuit parameter.
- A Thevenin circuit consists of a series voltage source and resistor that duplicates the performance of a more complicated circuit for any given load. A Norton circuit consists of a parallel current source and resistor that duplicates the performance of a more complicated circuit for any given load.
- Passive transducers require a separate source of electrical power; active transducers are self-generating devices.

SECTION 1-4

- An ideal amplifier is one that introduces no noise or distortion to the signal; the output varies in time and replicates the input exactly.
- A dependent source is one whose value depends on voltage or current elsewhere in the circuit.
- A decibel is a dimensionless number that is 10 multiplied by the logarithmic ratio of two powers.

SECTION 1-5

- Analyzing the symptoms of a failure by asking questions: Has the circuit ever worked? If so, under what conditions did it fail? What are the symptoms of a failure? What are possible causes of this failure?
- Half-splitting divides a troubleshooting problem into halves and determines which half of the circuit is likely to have the problem.
- Instrument loading is the effect of changing circuit voltages due to the process of connecting an instrument.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

1-1. $G_2 = 375 \mu\text{S}$, $R_2 = 2.67 \text{ k}\Omega$

1-2. $V_{rms} = 10.6 \text{ V}$, $f = 95 \text{ Hz}$, $T = 10.5 \text{ ms}$

1-3. $V_{RL} = 3.48 \text{ V}$

1-4. $V_{RL} = 3.48 \text{ V}$

1-5. See Figure 1-28.

1-6. 6 V

1-7. 1.34 V

1-8. (a) $\log 0.04 = -1.398$ (b) $10^{4.8} = 63,096$

$\log 0.4 = -0.398$

$\log 4.0 = 0.602$

$\log 40 = 1.602$

1-9. 49 dB

1-10. (a) -43 dB (b) 503 mW

1-11. (a) The decibel power gain is one-half the decibel voltage gain. (b) 34 dB

 


FIGURE 1-28

ANSWERS TO SELF-TEST

1. (a) 2. (b) 3. (e) 4. (c) 5. (a) 6. (c) 7. (b) 8. (b)
 9. (a) 10. (d) 11. (a) 12. (b) 13. (d) 14. (c) 15. (d) 16. (e)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. increase 2. decrease 3. not change 4. increase
 5. not change 6. increase 7. decrease 8. increase

CHAPTER 2

DIODES AND APPLICATIONS

OUTLINE

- 2-1 The Atomic Structure of Semiconductors
- 2-2 The *PN* Junction
- 2-3 Biasing the Semiconductor Diode
- 2-4 Diode Characteristics
- 2-5 Rectifiers
- 2-6 Rectifier Filters and IC Regulators
- 2-7 Diode Limiting and Clamping Circuits
- 2-8 Special-Purpose Diodes
- 2-9 The Diode Data Sheet
- 2-10 Troubleshooting

OBJECTIVES

- Discuss the basic atomic structure of semiconductors
- Describe the characteristics of a *pn* junction
- Explain how to bias a semiconductor diode
- Describe the basic diode characteristics
- Analyze the operation of three basic types of rectifiers
- Describe the operation of rectifier filters and IC regulators
- Analyze the operation of diode limiters and clampers
- Explain the characteristics of four different special-purpose diodes
- Interpret and use a diode data sheet
- Troubleshoot a power supply using accepted techniques

KEY TERMS

- | | |
|--------------------|--------------------|
| Energy | Reverse bias |
| Electron | Rectifier |
| Semiconductor | Filter |
| <i>PN</i> junction | Integrated circuit |
| Diode | Limiter |
| Bias | Clamper |
| Forward bias | |

INTRODUCTION

In this chapter, the basic materials used in manufacturing diodes, transistors, and integrated circuits are described. You will be introduced to *pn* junctions, an important concept essential for the understanding of diode and transistor operation. Diode characteristics are introduced, and you will learn how to use diodes in various applications. We discuss converting ac to dc by the process known as *rectification* and introduce the integrated circuit (IC) regulator. You will also learn about diode-limiting circuits and dc restoring (clamping) circuits.

In addition to rectifier diodes, you will be introduced to zener diodes, varactor diodes, light-emitting diodes, and photodiodes. Applications for these special-purpose diodes are discussed.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

2-1 THE ATOMIC STRUCTURE OF SEMICONDUCTORS

Electronic devices such as diodes and transistors are constructed from special materials called semiconductors. This section lays the foundation for understanding how semiconductor devices function.

After completing this section, you should be able to

- Discuss the basic atomic structure of semiconductors
- Describe the planetary model of the atom
- Discuss how silicon and germanium atoms bond together to form crystals
- Compare electron energy levels in a conductor, insulator, and a semiconductor

Electron Shells and Orbits

The electrical properties of materials are explained by their atomic structure. In the classic Bohr model of the atom, electrons orbit the nucleus only in certain discrete (separate and distinct) distances. The nucleus contains positively charged protons and uncharged neutrons. The orbiting electrons are negatively charged. Modern quantum mechanical models of the atom retain some of the ideas of the original Bohr model but have replaced the concept of electron “particles” with mathematical “matter waves”; however, the Bohr model provides a useful mental picture of the structure of an atom.

The distance from the nucleus determines the electron’s **energy**. Electrons near the nucleus have less energy than those in more distant orbits. These discrete orbits mean that only certain energy levels are permitted within the atom. These energy levels are known as **shells**. Each shell has a certain maximum permissible number of electrons. The differences in energy levels within a shell are much smaller than the difference in energy between shells. The shells are designated 1, 2, 3, 4, and so on, with 1 being closest to the nucleus. This concept is illustrated in Figure 2-1.

 


FIGURE 2-1 Energy levels increase as the distance from the nucleus of the atom increases. The ratio of the radii of electron orbits is proportional to the square of the shell number. A neutral silicon atom (with 14 electrons and 14 protons in the nucleus) is shown.

Valence Electrons, Conduction Electrons, and Ions

Electrons in orbits farther from the nucleus are less tightly bound to the atom than those closer to the nucleus.

This is because the force of attraction between the positively charged nucleus and the negatively charged electron decreases with increasing distance in accordance with Coulomb’s law. Outer-shell electrons are also shielded from the nuclear charge by the inner-shell electrons.

Electrons in the outermost shell, called **valence electrons**, have the highest energy and are relatively loosely bound to their parent atom. For the silicon atom in Figure 2-1, the third shell electrons are the valence electrons. Sometimes, a valence electron can acquire enough energy to break free of its parent atom. This free electron is called a **conduction electron** because it is not bound to any certain atom. When a negatively charged electron is freed from an atom, the rest of the atom is positively charged and is said to be a positive **ion**. In some chemical reactions, the freed electron attaches itself to a neutral atom (or group of atoms), forming a negative ion.

Metallic Bonds

Metals tend to be solids at room temperature. The nucleus and inner-shell electrons of metals occupy fixed lattice positions. The outer valence electrons are held loosely by all of the atoms of the crystal and are free to move about. This “sea” of negatively charged electrons holds the positive ions of the metal together, forming metallic bonding.

With the large number of atoms in the metallic crystal, the discrete energy level for the valence electrons is blurred into a band called the *valence band*. These valence electrons are mobile and account for the thermal and electrical conductivity of metals. In addition to the valence energy band, the next (normally occupied) level from the nucleus in the atom is also blurred into a band of energies called the *conduction band*.

Figure 2–2 compares the energy-level diagram for three types of solids. Notice that for conductors, shown in Figure 2–2(c), the bands are overlapping. Electrons can easily move between the valence and conduction bands by absorbing light. The movement, back and forth, of electrons between the valence band and conduction band accounts for the luster of metals.

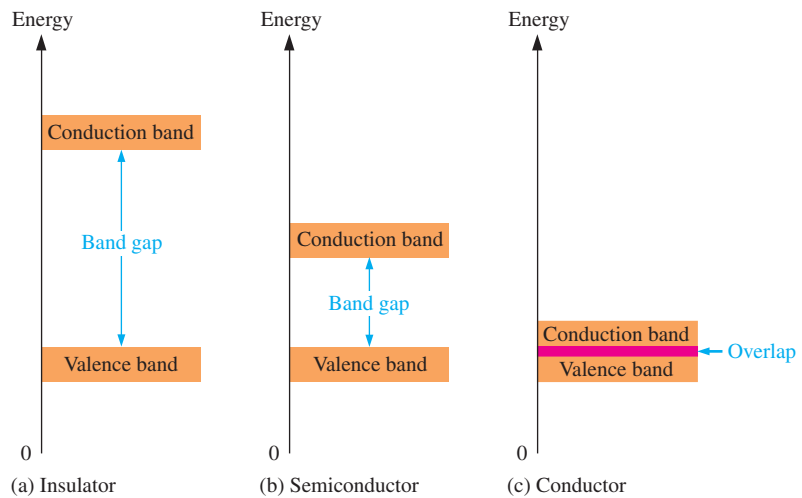


FIGURE 2–2 Energy diagrams for three categories of materials. The upper band is the conduction band; the lower band is the valence band.

Covalent Bonds

Atoms of some solid materials form **crystals**, which are three-dimensional structures held together by strong bonds between the atoms. In diamond, for example, four bonds are formed by the sharing of four valence electrons in each carbon atom with adjacent atoms. This effectively creates eight valence electrons for each atom and produces a state of chemical stability. This sharing of valence electrons produces strong **covalent bonds** that hold the atoms together.

The shared electrons are not mobile; each electron is associated by a covalent bond between the atoms of the crystal. Therefore, there is a large energy gap between the valence band and the conduction band. As a consequence, crystalline materials such as diamond are insulators, or nonconductors, of electricity. Figure 2–2(a) shows the energy bands for a solid insulator.

Electronic devices are constructed from materials called **semiconductors**. The most common semiconductive material is **silicon**; however, **germanium** is sometimes used. At room temperature, silicon forms a covalent crystal. The actual atomic structure is similar to diamond but the covalent bonds in silicon are not as strong as those in diamond. In silicon, each atom shares a valence electron with each of its four neighbors. As in the case of other crystalline materials, the discrete levels are blurred into a valence band and a conduction band, as shown in Figure 2–2(b).

The important difference between a conductor and a semiconductor is the gap that separates the bands. With semiconductors, the gap is narrow; electrons can easily be promoted to the conduction band with the addition of thermal energy. At absolute zero, the

electrons in a silicon crystal are all in the valence band, but at room temperature many electrons have sufficient energy to move to the conduction band. The conduction-band electrons are no longer bound to a parent atom within the crystal.

Electrons and Hole Current

When an electron jumps to the conduction band, a vacancy is left in the valence band. This vacancy is called a **hole**. For every electron raised to the conduction band by thermal or light energy, there is one hole left in the valence band, creating what is called an electron-hole pair. **Recombination** occurs when a conduction-band electron loses energy and falls back into a hole in the valence band.

A piece of **intrinsic** (pure) silicon at room temperature has, at any instant, a number of conduction-band (free) electrons that are unattached to any atom and are essentially drifting randomly throughout the material. Also, an equal number of holes are created in the valence band when these electrons jump into the conduction band.

When a voltage is applied across a piece of intrinsic silicon, as shown in Figure 2-3, the thermally generated free electrons in the conduction band are easily attracted toward the positive end. This movement of free electrons is one type of current in a semiconductor and is called *electron current*.


 


FIGURE 2-3 Electron current in intrinsic silicon is produced by thermally generated electrons.

Another type of current occurs at the valence level, where the holes created by the free electrons exist. Electrons remaining in the valence band are still attached to their atoms and are not free to move randomly in the crystal structure. However, a valence electron can move into a nearby hole, with little change in its energy level, thus leaving another hole where it came from. Effectively, the hole has moved from one place to another in the crystal structure, as illustrated in Figure 2-4. This current is called *hole current*.

 

When a valence electron moves left to right to fill a hole while leaving another hole behind, the hole has effectively moved from right to left. Gray arrows indicate effective movement of a hole.

FIGURE 2-4 Hole current in intrinsic silicon.

SECTION 2-1 CHECKUP*

1. In an intrinsic semiconductor, in which energy band do free electrons exist? In which band do holes exist?
2. How are holes created in an intrinsic semiconductor?
3. Why is current established more easily in a semiconductor than in an insulator?

*Answers are at the end of the chapter.

2-2 THE PN JUNCTION

Intrinsic silicon (or germanium) is not a good conductor. It must be modified by increasing either the free electrons or the holes to increase its conductivity. If a pentavalent impurity is added to pure silicon, an *n*-material is formed; if a trivalent impurity is added, a *p*-material is formed. During manufacture, these materials can be joined and form a boundary called the *pn* junction. Amazingly, it is the characteristics of the *pn* junction that allow diodes and transistors to work.

After completing this section, you should be able to

- Describe the characteristics of a *pn* junction
 - Compare *p*-type and *n*-type semiconductive materials
 - Give examples of donor and acceptor materials
 - Describe the formation of a *pn* junction

Doping

The conductivity of silicon (or germanium) can be drastically increased by the controlled addition of impurities to the pure (intrinsic) semiconductive material. This process, called **doping**, increases the number of current carriers (electrons or holes), thus increasing the conductivity and decreasing the resistivity. The two categories of doped intrinsic silicon are *n*-type and *p*-type.

To increase the number of conduction-band electrons in pure silicon, a controlled number of pentavalent impurity atoms called *donors* are added to the silicon crystal. These are atoms with five valence electrons, such as arsenic, phosphorus, and antimony. Each pentavalent atom forms covalent bonds with four adjacent silicon atoms, leaving one extra electron. This extra electron becomes a conduction (free) electron because it is not bonded to any atom in the crystal. The electrons in these *n* materials are called the *majority carriers*; the holes are called *minority carriers*.

To increase the number of holes in pure silicon, trivalent impurity atoms called *acceptors* are added. These are atoms with only three valence electrons, such as aluminum, boron, and gallium. Each trivalent atom forms covalent bonds with four adjacent silicon atoms. All three of the impurity atom's valence electrons are used in the covalent bonds. However, since four electrons are required in the crystal structure, a hole is formed with each trivalent atom added. With *p* materials, the acceptor causes extra holes in the valence band; the majority carrier in *p* materials is holes, the minority carrier is electrons.

It is important to note that the process of creating *n*-type or *p*-type materials retains the overall electrical neutrality. With *n*-type materials, the extra electron in the crystal is balanced by the additional positive charge of the donor's nucleus.

The PN Junction

When a piece of intrinsic silicon is doped so that half is n type and the other half is p type, a **pn junction** is formed between the two regions. The n region has many free electrons (majority carriers) and only a few thermally generated holes (minority carriers). The p region has many holes (majority carriers) and only a few thermally generated free electrons (minority carriers). The pn junction forms a basic diode and is fundamental to the operation of all solid-state devices. A **diode** is a device that allows current in only one direction.

THE DEPLETION REGION When the pn junction is formed, some of the conduction electrons near the junction drift across into the p region and recombine with holes near the junction as shown in Figure 2-5(a). For each electron that crosses the junction and recombines with a hole, a pentavalent atom is left with a net positive charge in the n region near the junction. Also, when the electron recombines with a hole in the p region, a trivalent atom acquires a net negative charge. As a result, positive ions are found on the n side of the junction and negative ions are found on the p side of the junction. The existence of the positive and negative ions on opposite sides of the junction creates a **barrier potential** (V_B) across the depletion region. The barrier potential depends on temperature, but it is approximately 0.7 V for silicon and 0.3 V for germanium at room temperature. Since germanium diodes are rarely used, 0.7 V is normally found in practice and will be assumed in this text.

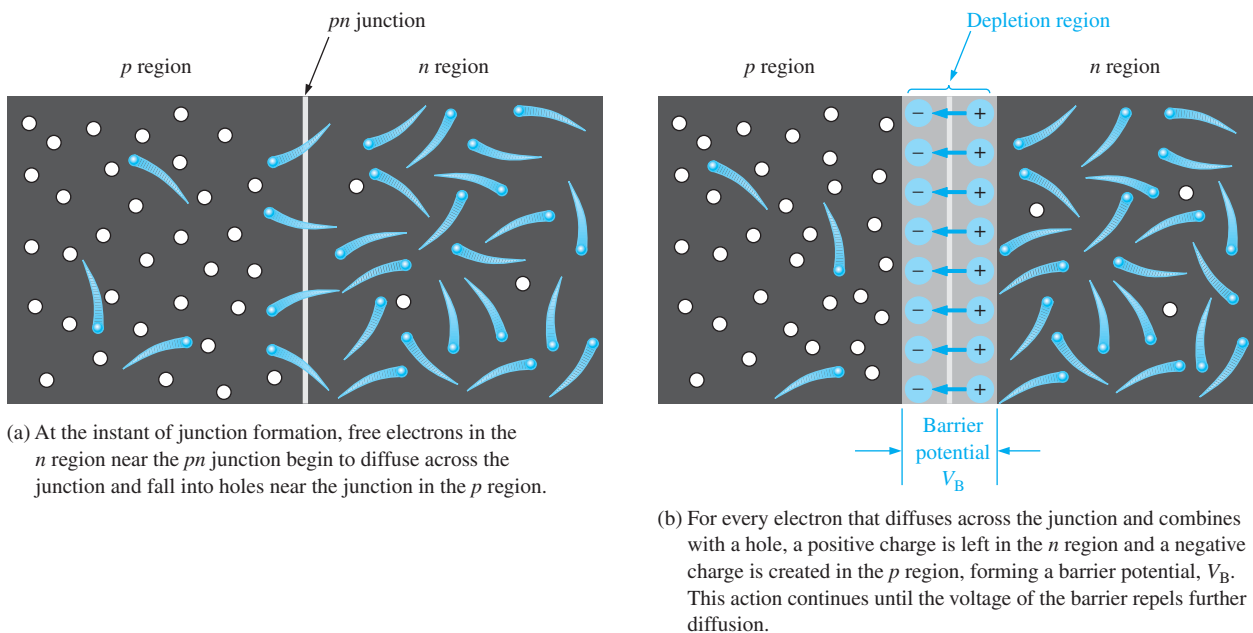


FIGURE 2-5 Formation of the pn junction.

Conduction electrons in the n region must overcome both the attraction of the positive ions and the repulsion of the negative ions in order to migrate into the p region. After the ion layers build up, the area on both sides of the junction becomes essentially depleted of any conduction electrons or holes and is known as the **depletion region**. This condition is illustrated in Figure 2-5(b). Any further movement of charge across the boundary requires that the barrier potential be overcome.

SECTION 2-2 CHECKUP

1. How is an n -type semiconductor formed?
2. How is a p -type semiconductor formed?
3. What is a pn junction?
4. What is the value of the barrier potential for silicon?

2-3 BIASING THE SEMICONDUCTOR DIODE

A single pn junction forms a semiconductor diode. There is no current across a pn junction at equilibrium. The primary usefulness of the semiconductor diode is its ability to allow current in only one direction as determined by the bias. There are two bias conditions for a pn junction—forward and reverse. Either of these conditions is created by connecting an external dc voltage in the proper direction across the pn junction.

After completing this section, you should be able to

- Explain how to bias a semiconductor diode
- Describe forward and reverse bias of a diode
- Describe avalanche breakdown

Forward Bias

The term **bias** in electronics refers to a fixed dc voltage that sets the operating conditions for a semiconductor device. **Forward bias** is the condition that permits current across a pn junction.

Figure 2-6 shows the polarity required from a dc source to forward-bias the semiconductor diode. The negative side of a source is connected to the n region (at the cathode terminal), and the positive side of a source is connected to the p region (at the anode terminal). When the semiconductor diode is forward-biased, the **anode** is the more positive terminal and the **cathode** is the more negative terminal.¹

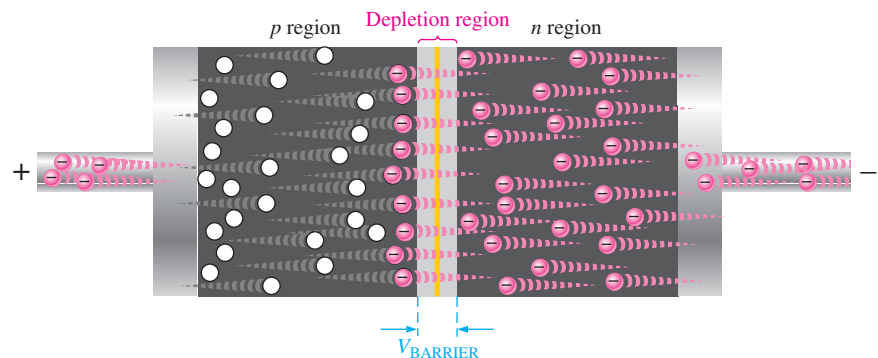



FIGURE 2-6 Electron flow in a forward-biased semiconductor diode.

This is how forward bias works: When a dc source is connected to forward-bias diode, the negative side of the source pushes the conduction electrons in the n region toward the junction because of electrostatic repulsion. The positive side pushes the holes in the p region also toward the junction. When the external bias voltage is sufficient to overcome the barrier potential, electrons have enough energy to penetrate the depletion region and cross the junction, where they combine with the p region holes. As electrons leave the n region, more electrons flow in from the negative side of the source. Thus, current through the n region is formed by the movement of conduction electrons (majority carriers) toward the junction. When the conduction electrons enter the p region and combine with holes, they become valence electrons. Then they move as valence electrons from hole to hole toward the positive anode connection. The movement of these valence electrons essentially creates a movement of holes in the opposite direction. Thus, current in the p region is formed by the movement of holes (majority carriers) toward the junction.


¹Chemists define anode and cathode in terms of the type of chemical reaction that occurs in electrochemical cells. For electrochemistry, the anode is the terminal that acts as an electron donor; the cathode is the terminal that acts as an electron acceptor.

Reverse Bias

Reverse bias is the bias condition that prevents current across the pn junction. Figure 2-7(a) shows the polarity required from a dc source to reverse-bias the semiconductor diode. Notice that the negative side of the source is connected to the p region, and the positive side to the n region. When the semiconductor diode is reverse-biased, the anode is the more negative terminal and the cathode is the more positive terminal.

 

 (a) Transient current at initial application of reverse bias



(b) Current ceases when the barrier potential equals the bias voltage.

FIGURE 2-7 Reverse bias.

This is how reverse bias works: The negative side of the source attracts holes in the p region away from the pn junction, while the positive side of the source attracts electrons away from the junction due to the attraction of opposite charges. As electrons and holes move away from the junction, the depletion region begins to widen; more positive ions are created in the n region, and more negative ions are created in the p region. The depletion region widens until the potential difference across it is equal to the external bias voltage, as shown in Figure 2-7(b). The depletion region effectively acts as an insulator between the layers of oppositely charged ions when the diode is reverse-biased.

PEAK INVERSE VOLTAGE (PIV) When a diode is reverse-biased, it must be able to withstand the maximum value of reverse voltage that is applied or it will break down. The maximum rated voltage for a diode is designated as *peak inverse voltage (PIV)*. The required PIV depends on the application; for most cases with ordinary diodes, the PIV rating should be higher than the reverse voltage.

REVERSE BREAKDOWN If the external reverse-bias voltage is increased to a large enough value, *avalanche breakdown* occurs. Here is what happens: Assume that one minority conduction-band electron acquires enough energy from the external source to accelerate it toward the positive end of the diode. During its travel, it collides with an atom and imparts enough energy to knock a valence electron into the conduction band. There are now two conduction-band electrons. Each will collide with an atom, knocking two more valence electrons into the conduction band. There are now four conduction-band electrons which, in turn, knock four more into the conduction band. This rapid multiplication of conduction-band electrons, known as an *avalanche effect*, results in a rapid buildup of reverse current.

Most diode circuits are not designed to operate in reverse breakdown, and the diode may be destroyed if it is. By itself, reverse breakdown will not harm a diode, but current limiting must be present to prevent excessive heating. One type of diode, the zener diode, is specially designed for reverse-breakdown operation if sufficient current limiting is provided. (Zeners are discussed in Section 2–8.)

SECTION 2–3 CHECKUP

1. What are the two bias conditions?
2. Which bias condition produces majority carrier current?
3. Which bias condition produces a widening of the depletion region?
4. What is avalanche breakdown?

2–4 DIODE CHARACTERISTICS

In this section, you will learn that the characteristic curve graphically shows the current-voltage relationship for a diode. Three diode models are discussed. Each model represents the diode at a different level of accuracy so that you can use the one most appropriate for a given situation. In some cases, the lowest level of accuracy is all that is needed and additional details only complicate the situation. In other cases, you need the highest level of accuracy so that all factors can be taken into account.

After completing this section, you should be able to

- Describe the basic diode characteristics
- Describe the diode characteristic IV curve
- Explain how to plot the diode characteristic IV curve on an oscilloscope
- Describe three models that are used to simplify diode circuits

Diode Symbol

Figure 2–8(a) shows the standard schematic symbol for a general-purpose diode. The two terminals of the diode are the anode and cathode, labeled A and K on the figure. The arrow always points toward the cathode.

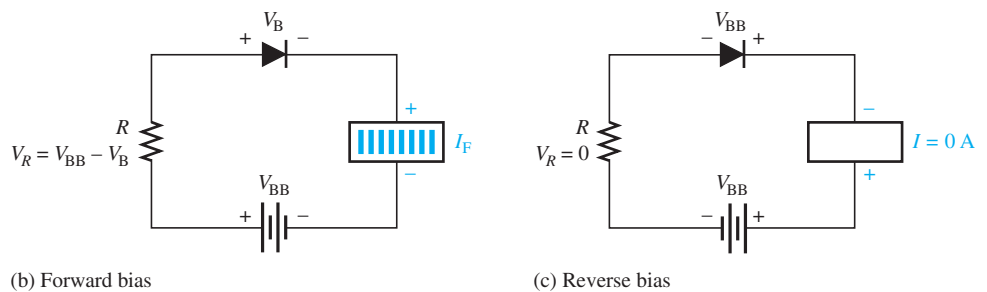
 


FIGURE 2–8 Diode schematic symbol and bias circuits. V_{BB} is the bias battery voltage, and V_B is the barrier potential. The resistor limits the forward current to a safe value.

Figure 2–8(b) shows a forward-biased diode connected to a source through a current-limiting resistor. The anode is positive with respect to the cathode, causing the diode to conduct as indicated by the ammeter symbol. Remember that when the diode is forward-biased, the barrier potential, V_B , always appears between the anode and cathode, as indicated. The voltage across the resistor, V_R , is V_{BB} less the barrier potential, V_B .

Figure 2-8(c) shows the diode with reverse bias. The anode is negative with respect to the cathode, and the diode does not conduct as indicated by the ammeter symbol. The entire bias voltage, V_{BB} , appears across the diode. There is no voltage across the resistor because there is no current in the circuit. Notice that the bias voltage, V_{BB} , is not the same as the barrier potential, V_B .

Some typical diodes are shown in Figure 2-9 to illustrate common packaging. The letter A is used to identify the anode; K is used to identify the cathode.

 


FIGURE 2-9 Typical diode packages and terminal identification.

Diode Characteristic Curve

Figure 2-10 is a graph of diode current versus voltage. The upper right quadrant of the graph represents the forward-biased condition. As you can see, there is essentially no forward current (I_F) for forward voltages (V_F) below the barrier potential. As the forward voltage approaches the value of the barrier potential (typically 0.7 V for silicon and 0.3 V for germanium), the current begins to increase. Once the forward voltage reaches the barrier potential, the current increases drastically and must be limited by a series resistor. The voltage across the forward-biased diode remains approximately equal to the barrier potential, but increases slightly with forward current. For a forward-biased diode, this barrier voltage is often referred to as a *diode drop*.

The lower left quadrant of the graph represents the reverse-biased condition. As the reverse voltage increases to the left, the current remains near zero until the breakdown voltage is reached. When breakdown occurs, there is a large reverse current which, if not limited, can destroy the diode.² Typically, the breakdown voltage is greater than 50 V for most rectifier diodes. Most applications for ordinary diodes do not include operation in the reverse-breakdown region.

PLOTTING THE CHARACTERISTIC CURVE ON AN OSCILLOSCOPE

You can plot the diode's forward characteristic on your oscilloscope by connecting the circuit shown in Figure 2-11. The signal is a 5 V peak-to-peak triangle that is centered about zero volts. This causes the diode to be alternately forward-biased and then reverse-biased. Channel 1 senses the voltage drop across the diode; channel 2 shows a signal that is proportional to the current. The scope is placed in the X-Y mode. The common lead on the signal generator *must not* be the same as the scope ground. Channel 2 must be inverted to display the signal in the proper orientation.

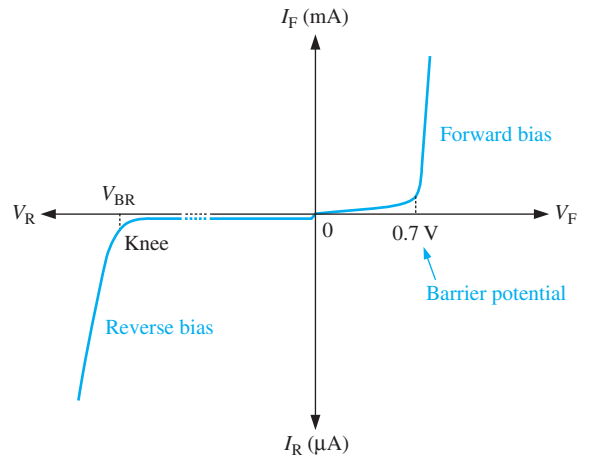


FIGURE 2-10 Diode characteristic curve.

²With proper current limiting, operation in the reverse-breakdown region does not harm the diode.

 


FIGURE 2-11 Plotting the *IV* curve for a diode on an oscilloscope. The oscilloscope is placed in the X-Y mode and the Y channel is inverted.

Testing Diodes with an Ohmmeter or a Multimeter

The internal battery in most analog ohmmeters can forward-bias or reverse-bias a diode, permitting a quick relative check of the diode. To check the diode with an analog ohmmeter, select the $R \times 100$ range (to limit current through the diode), connect the meter leads to the diode, then reverse the leads. The meter’s internal voltage source will tend to forward-bias the diode in one direction and reverse-bias it in the other. As a result, the resistance will read a lower value in one direction than the other. Look for a high ratio between the forward and reverse readings (typically 1000 or more). The actual reading depends on the internal voltage of the meter, the range selected, and the type of diode, so this is only a relative test.

Many digital multimeters have a diode test position that will indicate the forward diode voltage when a good diode is placed across the test leads. The meter will show an overload when the leads are reversed.

Diode Models

THE IDEAL MODEL The simplest way to visualize diode operation is to think of it as a switch. When forward-biased, the diode ideally acts as a closed (on) switch; and when reverse-biased, it acts as an open (off) switch, as shown in Figure 2–12. The characteristic curve for this model is also shown. Note that the forward voltage and the reverse current are always zero in the ideal case. This ideal model, of course, neglects the effect of the barrier potential, the internal resistance, and other effects. However, in many cases, it is accurate enough, particularly when the bias voltage is at least ten times greater than the barrier potential.

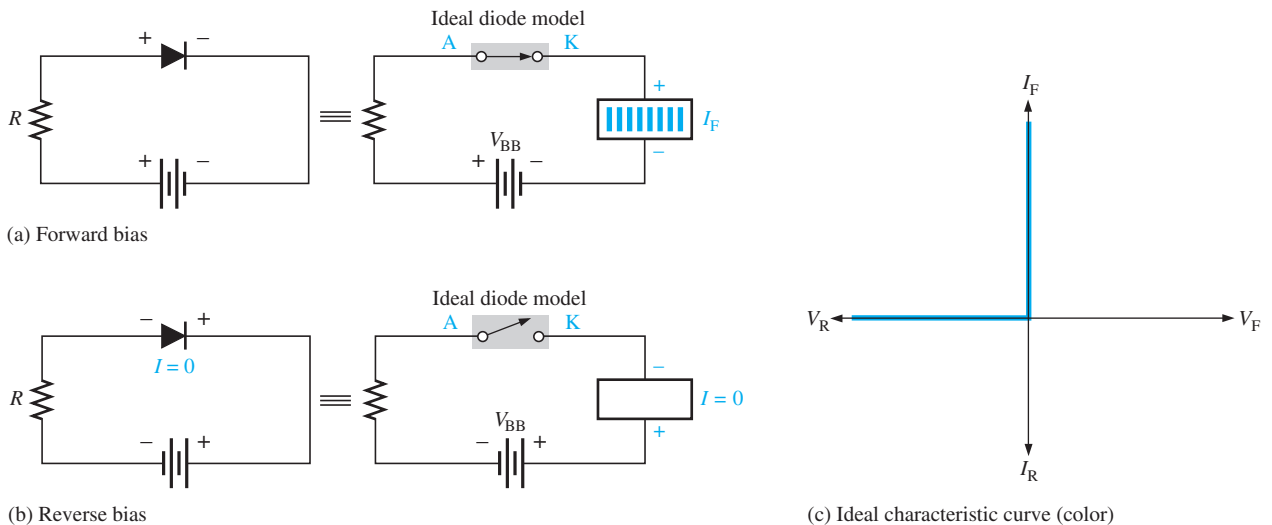


FIGURE 2-12 Ideal model of a diode as a switch.

THE OFFSET MODEL The next higher level of accuracy is the offset model. It includes the barrier potential of the diode. In this model, the forward-biased diode is represented as a closed switch in series with a small “battery” equal to the barrier potential V_B (0.7 V for Si), as shown in Figure 2-13(a). The positive end of the equivalent battery is toward the anode. Keep in mind that the barrier potential is *not* a voltage source and cannot be measured with a voltmeter; rather it only has the effect of an offsetting battery when forward bias is applied because the forward-bias voltage, V_{BB} , must overcome this barrier potential before the diode begins to conduct. The reverse-biased diode is represented by an open switch, as in the ideal case, because the barrier potential does not affect reverse bias, as shown in Figure 2-13(b). The characteristic curve for the offset model is shown in Figure 2-13(c). In this textbook, this model is used for analysis unless otherwise stated.

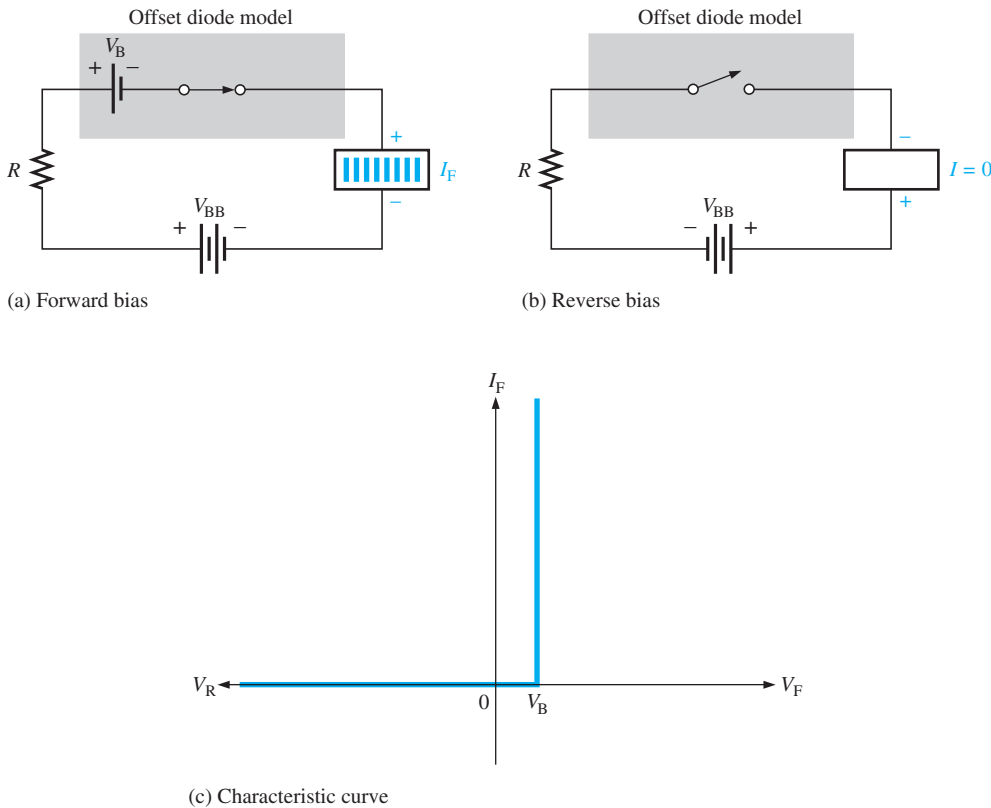


FIGURE 2-13 The offset model for a diode. The barrier potential is included in this model.

THE OFFSET-RESISTANCE MODEL Figure 2-14(a) shows the forward-biased diode model with both the barrier potential and the low forward (bulk) resistance. The forward resistance is actually an ac resistance (see Section 1-1). The forward resistance varies (depending on where it is measured) but is shown here with a straight-line approximation.


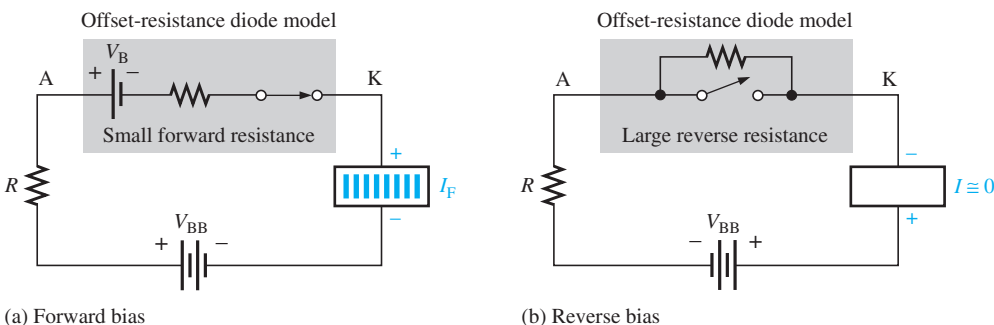


FIGURE 2-14 The offset-resistance model for a diode. The barrier potential and forward ac resistance is included in this model.

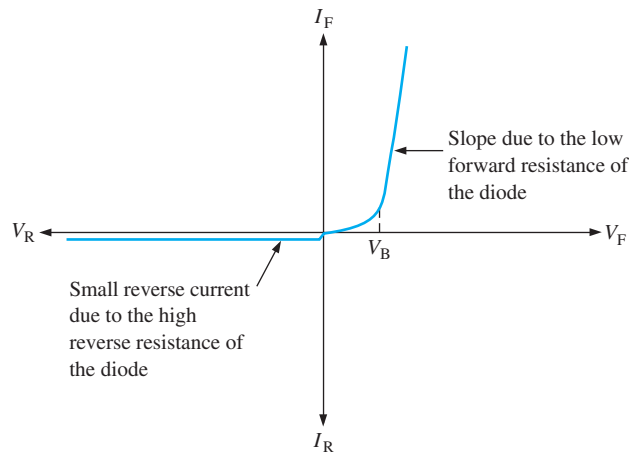


(c) Characteristic curve

FIGURE 2-14 (Continued)

The reversed-biased condition is represented in the offset-resistance model with a very high parallel resistance. This results in an extremely small reverse current. Figure 2-14(b) shows how the high reverse resistance affects the reverse-biased model. The characteristic curve is shown in Figure 2-14(c). There are other small-scale effects (such as junction capacitance) that are not included in this model. For these cases, computer modeling is normally done.

SYSTEM EXAMPLE 2-1

 

SOLAR POWER SYSTEMS

The pn junction is a key part of all diodes including photovoltaic (PV) cells (also called solar cells) used in solar power systems. The **photovoltaic effect** is the basic physical process by which a solar cell converts sunlight into electricity. Sunlight contains photons or “packets” of energy sufficient to create electron-hole pairs in the n and p regions. Electrons accumulate in the n -region and holes accumulate in the p region, producing a potential difference (voltage) across the cell. When an external load is connected, the electrons flow through the semiconductor material and provide current to the external load.

THE SOLAR CELL STRUCTURE Although there are other types of solar cells and continuing research promises new developments in the future, the crystalline silicon solar cell is by far the most widely used. A silicon solar cell consists of a thin layer or wafer of silicon that has been doped to create a pn junction. The depth and distribution of impurity atoms can be controlled very precisely during the doping process. The most commonly used process for creating a silicon ingot, from which a silicon wafer is cut, is called the *Czochralski method*. In this process, a seed crystal of silicon is dipped into melted polycrystalline silicon. As the seed crystal is withdrawn and rotated, a cylindrical ingot of silicon is formed.

Thin circular shaped-wafers are sliced from an ingot of ultra-pure silicon and then are polished and trimmed to an octagonal, hexagonal, or rectangular shape for maximum coverage when fitted into an array. The silicon wafer is doped so that the n region is much thinner than the p region to permit light penetration, as shown in Figure SE2-1(a).

A grid-work of very thin conductive contact strips are deposited on top of the wafer by methods such as photoresist or silk-screen, as shown in part (b). The contact grid must maximize the surface area of the silicon wafer that will be exposed to the sunlight in order to collect as much light energy as possible.

 


FIGURE SE2-1 Basic construction of a PV solar cell.

The conductive grid across the top of the cell is necessary so that the electrons have a shorter distance to travel through the silicon when an external load is connected. The farther electrons travel through the silicon material, the greater the energy loss due to resistance. A solid contact covering all of the bottom of the wafer is then added, as indicated in the figure. Thickness of the solar cell compared to the surface area is greatly exaggerated for purposes of illustration.

After the contacts are incorporated, an antireflective coating is placed on top the contact grid and n region, as shown in Figure SE2-1(c). This allows the solar cell to absorb as much of the sun's energy as possible by reducing the amount of light energy reflected away from the surface of the cell. Finally, a glass or transparent plastic layer is attached to the top of the cell with transparent adhesive to protect it from the weather. Figure SE2-2 shows a completed solar cell.

 


FIGURE SE2-2 A complete PV solar cell.

Solar Cell Panels

Currently, the problem is in harnessing solar energy in sufficient amounts and at a reasonable cost to meet our requirements. It takes approximately a square meter solar panel to produce 100 W in a sunny climate. Some energy can be harvested even if cloud cover exists, but no energy can be obtained during the night.

A single solar cell is impractical for most applications because it can produce only about 0.5 V to 0.6 V. To produce higher voltages, multiple solar cells are connected in series as shown in Figure SE2-3(a). For example, the six series cells will ideally produce

 


FIGURE SE2-3 Solar cells connected together to create an array called a solar panel.

$6(0.5 \text{ V}) = 3 \text{ V}$. Since they are connected in series, the six cells will produce the same current as a single cell. For increased current capacity, series cells are connected in parallel, as shown in part (b). Assuming a cell can produce 2 A, the series-parallel arrangement of twelve cells will produce 4 A at 3 V. Multiple cells connected to produce a specified power output are called *solar panels* or *solar modules*.

Solar panels are generally available in 12 V, 24 V, 36 V, and 48 V versions. Higher output solar panels are also available for special applications. In actuality, a 12 V solar panel produces more than 12 V (15 V to 20 V) in order to charge a 12 V battery and compensate for voltage drops in the series connection and other losses. Ideally, a panel with 24 individual solar cells is required to produce an output of 12 V, assuming each cell produces 0.5 V. In practice, more than thirty cells are typically used in a 12 V panel. Manufacturers usually specify the output of a solar panel in terms of power at a certain solar radiation called the *peak sun irradiance*, which is 1000 W/m^2 . For example, a 12 V solar panel that has a rated voltage of 17 V and produces a current of 3.5 A to a load at peak sun condition has a specified output power of

$$P = VI = (17 \text{ V})(3.5 \text{ A}) = 59.5 \text{ W}$$

Many solar panels can be interconnected to form large arrays for high power outputs, as illustrated in Figure SE2–4.

FIGURE SE2–4 Large array of solar panels. NREL.gov.




The Solar Power System

A basic solar power system that can supply power to ac loads generally consists of four components, as shown in the block diagram in Figure SE2–5. These components are the solar panel, the charge controller, the batteries, and the inverter. For supplying only dc loads, such as solar-powered instruments and dc lamps, the inverter is not needed. Some solar power systems do not include battery backup or the charge controller and are used to provide supplemental power only when the sun is shining.

Efficiency is an important characteristic of a solar power system. Energy loss due to voltage drops, the photovoltaic process, and other factors are inevitable, so minimizing losses is a critical consideration in solar power systems.

FIGURE SE2–5 Basic solar power system with battery backup.

 

SECTION 2-4 CHECKUP

1. What are the two conditions under which the diode is operated?
2. What region of the diode characteristic curve is not part of normal diode operation?
3. What is the simplest way to visualize a diode?
4. What two approximations are included in the offset-resistance model of a diode?

2-5 RECTIFIERS

Because of their ability to conduct current in one direction and block current in the other direction, diodes are used in circuits called rectifiers that convert ac voltage into dc voltage. Rectifiers are found in all dc power supplies that operate from an ac voltage source. Power supplies are an essential part of all electronic systems from the simplest to the most complex. In this section, you will study three basic types of rectifiers—the half-wave, center-tapped full wave, and full-wave bridge rectifiers.

After completing this section, you should be able to

- Analyze the operation of three basic types of rectifiers
- Recognize a half-wave rectifier and explain how it works
- Recognize a center-tapped full-wave rectifier and explain how it works
- Recognize a full-wave bridge rectifier and explain how it works

Half-Wave Rectifiers

A **rectifier** is an electronic circuit that converts ac into pulsating dc. Figure 2-15 illustrates the process called *half-wave rectification*. In a **half-wave rectifier**, shown in part (a), an ac source is connected in series with a diode and the load resistor. When the sinusoidal input voltage goes positive, the diode is forward-biased and conducts current to the load resistor, as shown in part (b). The output voltage is equal to the peak voltage less one diode drop.

$$V_{p(out)} = V_{p(in)} - 0.7 \text{ V} \quad (2-1)$$

The current produces a voltage across the load, which has the same shape as the positive half-cycle of the input voltage. When the input voltage goes negative during the second half of its cycle, the diode is reverse-biased. There is no current, so the voltage across the load resistor is zero, as shown in part (c). The net result is that only the positive half-cycles of the ac input voltage, less one diode drop, appear across the load, making the output a pulsating dc voltage, as shown in part (d). Notice that during the negative cycle, the diode must withstand the negative peak voltage from the source without breaking down.

In working with diode circuits, it is sometimes practical to neglect the diode drop when the peak value of the applied voltage is much greater than the barrier potential. This is equivalent to using the ideal model.

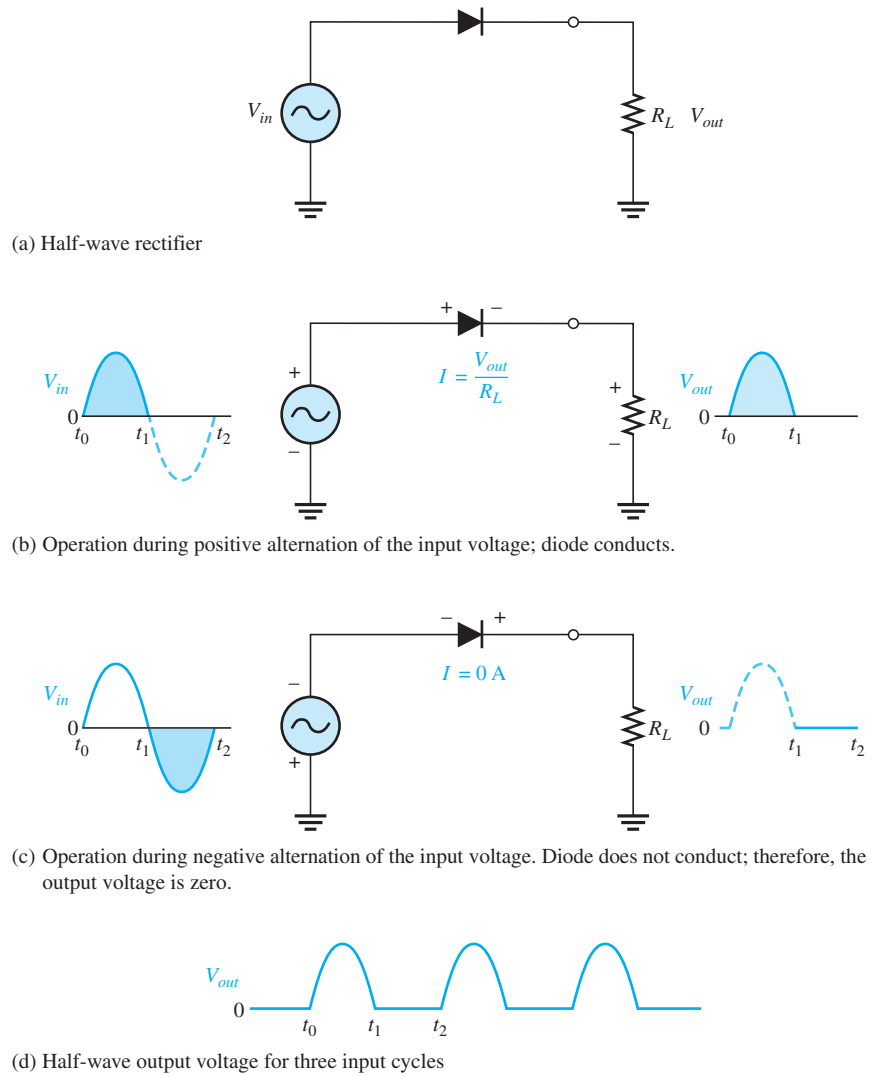


FIGURE 2-15 Operation of half-wave rectifier. The diode is considered ideal.

EXAMPLE 2-1

Determine the peak output voltage and the peak inverse voltage (PIV) of the rectifier in Figure 2-16 for the indicated input voltage. Sketch the waveforms you should observe across the diode and the load resistor.

 


FIGURE 2-16

SOLUTION

The peak half-wave output voltage is

$$V_p = 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}$$

The PIV is the maximum voltage across the diode when it is reverse-biased. The PIV is the maximum voltage during the negative half cycle.

$$\text{PIV} = V_p = 5 \text{ V}$$

Waveforms are shown in Figure 2-17. Notice that if you add the load resistor voltage to the diode voltage, you will obtain the input voltage.

 


FIGURE 2-17

PRACTICE EXERCISE*

Determine the peak output voltage and the PIV for the rectifier in Figure 2-16 if the peak input is 3 V.

* Answers are at the end of the chapter.

Full-Wave Rectifiers

The difference between full-wave and half-wave rectification is that a **full-wave rectifier** allows unidirectional current to the load during the entire input cycle, and the half-wave rectifier allows current only during one-half of the cycle. The result of full-wave rectification is a dc output voltage that pulsates every half-cycle of the input, as shown in Figure 2-18.

 


FIGURE 2-18 Full-wave rectification.

THE CENTER-TAPPED FULL-WAVE RECTIFIER The **center-tapped (CT)** full-wave rectifier uses two diodes connected to the secondary of a center-tapped transformer, as shown in Figure 2-19. The input signal is coupled through the transformer to the secondary. Half of the total secondary voltage appears between the center tap and each end of the secondary winding as shown.

For a positive half-cycle of the input voltage, the polarities of the secondary voltages are as shown in Figure 2-20(a). This condition forward-biases the upper diode D_1 and reverse-biases the lower diode D_2 . The current path is through D_1 and the load resistor, as indicated in color.

For a negative half-cycle of the input voltage, the voltage polarities on the secondary are as shown in Figure 2-20(b). This condition reverse-biases D_1 and forward-biases D_2 . The current path is through D_2 and the load resistor, as indicated in color.

MULTISIM



Open file F02-17 found on the companion website. This simulation illustrates the operation of a positive and negative half-wave rectifier.



 


FIGURE 2-19 A center-tapped (CT) full-wave rectifier.

 

 (a) During positive half-cycles, D_1 is forward-biased and D_2 is reverse-biased.



(b) During negative half-cycles, D_2 is forward-biased and D_1 is reverse-biased.

FIGURE 2-20 Conducting paths in the secondary are shown in color.

Because the current during both the positive and the negative portions of the input cycle is in the same direction through the load, the output voltage developed across the load is a full-wave rectified dc voltage.

EFFECT OF THE TURNS RATIO ON THE FULL-WAVE OUTPUT VOLTAGE If the turns ratio of a transformer is 1, the peak value of the rectified output voltage equals half the peak value of the primary input voltage less one diode drop. This value occurs because half of the input voltage appears across each half of the secondary winding.

In order to obtain a peak output voltage equal to the peak input voltage (less the barrier potential), you must use a step-up transformer with a turns ratio of 2 (1:2). In this case, the total secondary voltage is twice the primary voltage, so the voltage across each half of the secondary is equal to the input.

PEAK INVERSE VOLTAGE (PIV) Each diode in the full-wave rectifier is alternately forward-biased and then reverse-biased. The maximum reverse voltage that each diode must withstand is the peak value of the total secondary voltage (V_{sec}). The peak inverse voltage across either diode in the center-tapped full-wave rectifier is

$$PIV = V_{p(out)}$$

EXAMPLE 2-2

- (a) Show the voltage waveforms across the secondary winding and across R_L when a 25 V peak sine wave is applied to the primary winding in Figure 2-21.
- (b) What minimum PIV rating must the diodes have?

 


FIGURE 2-21

SOLUTION

- (a) The waveforms are shown in Figure 2-22.
- (b) The total peak secondary voltage is

$$V_{p(sec)} = \left(\frac{N_{sec}}{N_{pri}} \right) V_{p(in)} = 2(25) \text{ V} = 50 \text{ V}$$

There is a 25 V peak across each half of the secondary. Using the ideal model, one diode is a short while the other diode has the full secondary voltage across it. Each diode must have a minimum PIV rating of **50 V**.

 


FIGURE 2-22

PRACTICE EXERCISE

What diode PIV rating is required to handle a peak input of 160 V in Figure 2-21?


MULTISIM

Open file F02-21 found on the companion website. This simulation illustrates the operation of both a positive and negative center-tapped full-wave rectifier.


Bridge Rectifiers

The bridge rectifier uses four diodes, as shown in Figure 2-23 and is the most popular arrangement for power supplies because it does not require a center-tapped transformer. The four diodes are available in a single package, already wired in a bridge configuration. The bridge rectifier is a type of full-wave rectifier because each half of the sine wave contributes to the output.

This is how the bridge rectifier works: When the input cycle is positive as in Figure 2-23(a), diodes D_1 and D_2 are forward-biased and conduct current as shown by the colored path. A voltage is developed across R_L which looks like the positive half of the input cycle. During this time, diodes D_3 and D_4 are reverse-biased. When the input cycle is negative, as in Figure 2-23(b), diodes D_3 and D_4 are forward-biased and conduct as shown by the

 

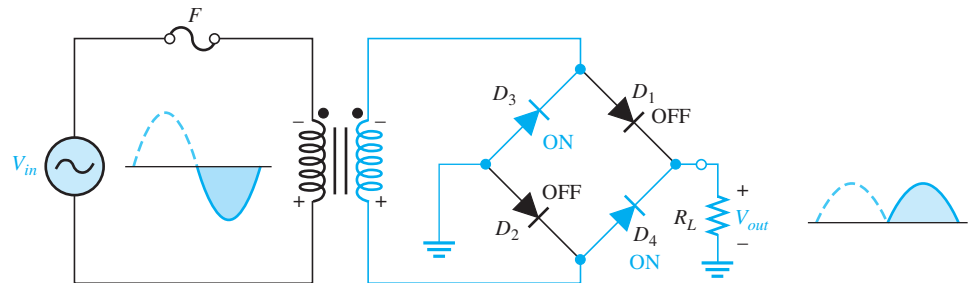(a) During positive half-cycle of the input, D_1 and D_2 are forward-biased and conduct current. D_3 and D_4 are reverse-biased.



(b) During negative half-cycle of the input, D_3 and D_4 are forward-biased and conduct current. D_1 and D_2 are reverse-biased.

FIGURE 2–23 Operation of the full-wave rectifier. Conducting paths in the secondary are shown in color.

colored path. A voltage is again developed across R_L in the same direction as during the positive half-cycle. During the negative half-cycle, D_1 and D_2 are reverse-biased. A full-wave rectified output voltage appears across R_L as a result of this action.

BRIDGE OUTPUT VOLTAGE Neglecting the diode drops, the total secondary voltage, V_{sec} , appears across the load resistor. Thus,

$$V_{out} = V_{sec}$$

As you can see in Figure 2–23, two diodes are always in series with the load resistor during both the positive and the negative half-cycles. If these diode drops are taken into account, the output voltage (with silicon diodes) is

$$V_{out} = V_{sec} - 1.4 \text{ V} \quad (2-2)$$

PEAK INVERSE VOLTAGE When D_1 and D_2 are forward-biased, the reverse voltage is across D_3 and D_4 . Visualizing D_1 and D_2 as shorts (ideally), the peak inverse voltage is equal to the peak secondary voltage.

$$\text{PIV} = V_{p(out)}$$

SECTION 2–5 CHECKUP

- Which type of rectifier (half-wave, full-wave, or bridge) has the greatest output voltage for the same input voltage and transformer turns ratio?
- For a given output voltage, is the PIV for bridge rectifier diodes less than, the same as, or greater than the PIV for center-tapped rectifier diodes?
- At what point on the input cycle does the PIV occur in a half-wave rectifier that has a positive output?
- For a half-wave rectifier, there is current through the load for approximately what percentage of the input cycle?

2-6 RECTIFIER FILTERS AND IC REGULATORS

A power supply filter greatly reduces the fluctuations in the output voltage of a rectifier and produces a nearly constant-level dc voltage. The reason for filtering is that electronic circuits require a constant source of dc voltage and current to provide power and biasing for proper operation. Filtering is generally done using large capacitors. To improve the filtering action even more, the capacitor-input filter is followed by a regulator. Today, inexpensive but effective regulators are available as integrated circuits (ICs). IC regulators are introduced here and will be covered in more detail in Chapter 11.

After completing this section, you should be able to

- Describe the operation of rectifier filters and IC regulators
 - Give examples of IC regulators and show how they are connected to the output of a rectifier
 - Compute the ripple from an IC regulator given the ripple rejection and the input ripple
 - Compute the load regulation given the loaded and unloaded output voltage
 - Compute the line regulation given the change in output voltage for a given change in the input voltage
-

In most power supply applications, the standard 60 Hz ac power line voltage must be converted to a nearly constant dc voltage. The 60 Hz pulsating dc output of a half-wave rectifier or the 120 Hz pulsating output of a full-wave or bridge rectifier must be filtered to reduce the large voltage variations. Filtering can be accomplished by a capacitor, an inductor, or a combination of these. The capacitor-input **filter** is the least expensive and most widely used type, by far.

Capacitor-Input Filter


A half-wave rectifier with a capacitor-input filter is shown in Figure 2-24. We will use the half-wave rectifier to illustrate the filtering principle and then expand the concept to the full-wave rectifier.

During the positive first quarter-cycle of the input, the diode is forward-biased, allowing the capacitor to charge to within a diode drop of the input peak, as illustrated in Figure 2-24(a). When the input begins to decrease below its peak, as shown in Figure 2-24(b), the capacitor retains its charge and the diode becomes reverse-biased. During the remaining part of the cycle and the beginning of the next cycle, the capacitor can discharge only through the load resistance at a rate determined by the RC time constant. The larger the time constant, the less the capacitor will discharge.


During the peak of the next cycle, as illustrated in Figure 2-24(c), the diode again will become forward-biased when the input voltage exceeds the capacitor voltage by approximately a diode drop.

RIPPLE VOLTAGE As you have seen, the capacitor quickly charges at the beginning of a cycle and slowly discharges through R_L after the positive peak (when the diode is reverse-biased). The variation in the capacitor voltage due to the charging and discharging is called the **ripple voltage**. The smaller the ripple voltage, the better the filtering action.


For a given input frequency, the output frequency of a full-wave rectifier is twice that of a half-wave rectifier. As a result, a full-wave rectifier is easier to filter because of the shorter time between peaks. When filtered, the full-wave rectified voltage has less ripple voltage than does a half-wave voltage for the same load resistance and filter capacitor values. Less ripple voltage occurs because the capacitor discharges less during the shorter interval between full-wave pulses, as shown in Figure 2-25.

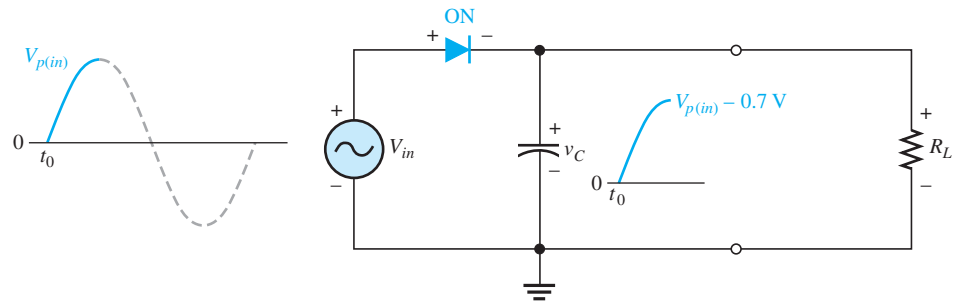

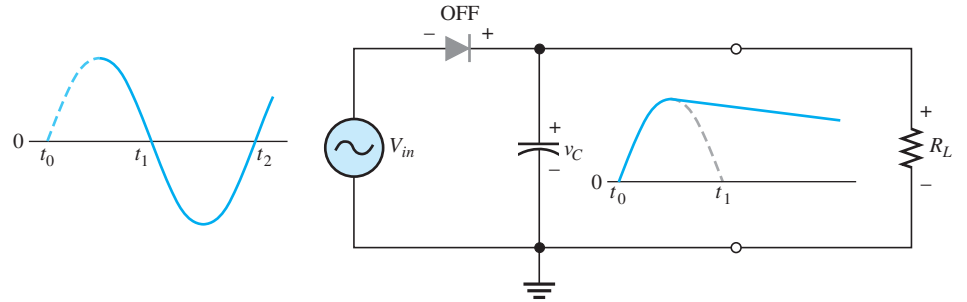(a) Initial charging of capacitor (diode is forward-biased) happens only once when power is turned on.



 (b) The capacitor discharges through R_L after peak of positive alternation when the diode is reverse-biased. This discharging occurs during the portion of the input voltage indicated by the solid colored curve.



(c) The capacitor charges back to peak of input when the diode becomes forward-biased. This charging occurs during the portion of the input voltage indicated by the solid colored curve. Notice that the diode is not forward-biased on the second cycle until the capacitor voltage is overcome.

FIGURE 2-24 Operation of a half-wave rectifier with a capacitor-input filter.

 


FIGURE 2-25 Comparison of ripple voltages for half-wave and full-wave rectifier outputs with the same filter capacitor and derived from the same sinusoidal input.

SURGE CURRENT IN THE CAPACITOR-INPUT FILTER When the power is first applied to a power supply, the filter capacitor is uncharged. At the instant the switch is closed, voltage is connected to the rectifier and the uncharged capacitor appears as a short. This case is illustrated for a bridge circuit in Figure 2-26(a). An initial surge of current (sometimes called inrush current) is produced through the forward-biased diodes. The worst-case situation occurs when the switch is closed at a peak of the secondary voltage and a maximum surge current is produced.

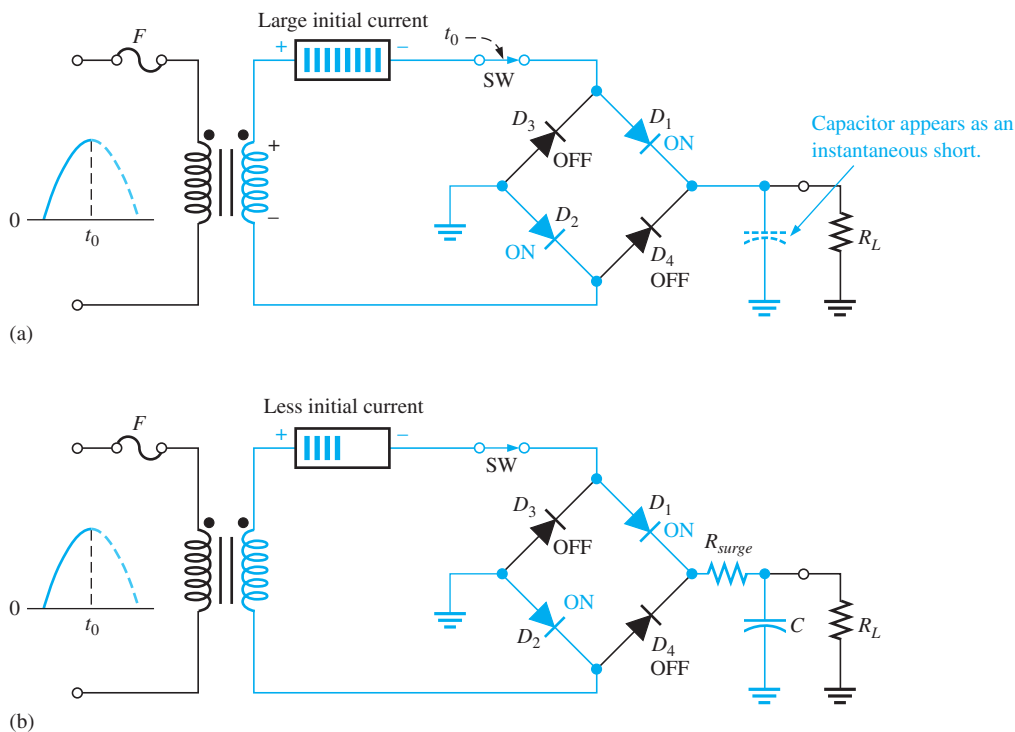



FIGURE 2-26 Surge current in a capacitor-input filter follows the path drawn in color.

It is possible that the surge (inrush) current could destroy the diodes, and for this reason a surge-limiting resistor, R_{surge} , is sometimes connected, as shown in Figure 2-26(b). The value of this resistor must be small to avoid a significant voltage drop across it. Also, the diodes must have a forward current rating such that they can withstand the momentary surge of current.

Thermistors are widely used in systems where temperature measurement is required. Surge current is usually controlled with an NTC (negative temperature coefficient) thermistor. A *thermistor* is a resistor whose resistance changes significantly, and predictably, as its temperature changes. Thermistors are covered in more detail in Chapter 15. A cold NTC thermistor has high resistance. Surge current heats the thermistor and its resistance decreases to a level where the voltage drop across the thermistor is insignificant.

Surge current limiting NTC thermistors have initial resistance values from as low as $0.2\ \Omega$ up to about $220\ \Omega$. What initial resistance value is chosen will be determined by system requirements. Thermistors require a cool-down or recovery time after a system is powered down to allow their resistance to increase sufficiently to control the next surge current. Typical recovery times are about 1 minute, depending on device ratings and heat sinking. For systems that may be turned off and on within a short period of time, some form of active current limiting may be required.

SYSTEM NOTE

 


IC Regulators

While filters can reduce the ripple from power supplies to a low value, the most effective filter is a combination of a capacitor-input filter used with an IC regulator. In general, an IC (**integrated circuit**) is a complete functional circuit constructed on a single, tiny chip of silicon. An integrated circuit **regulator** is an IC that is connected to the output of a rectifier and maintains a constant output voltage (or current) despite changes in the input, the load current, or the temperature. The capacitor filter reduces the input ripple to the regulator to an acceptable level. The combination of a large capacitor and an IC regulator is inexpensive and helps produce an excellent small power supply.

The most popular IC regulators have three terminals—an input terminal, an output terminal, and a reference (or adjust) terminal. The input to the regulator is first filtered with a capacitor to reduce the ripple to $<10\%$. The regulator reduces the ripple to a negligible amount. In addition, most regulators have an internal voltage reference, short-circuit protection, and thermal shutdown circuitry. They are available in a variety of voltages, including positive and negative outputs, and can be designed for variable outputs with a minimum of external components. Typically, IC regulators can furnish a constant output of one or more amps of current with high ripple rejection. IC regulators are available that can supply load currents of over 5 A.


Three-terminal regulators designed for a fixed output voltage require only external capacitors to complete the regulation portion of the power supply, as shown in Figure 2–27. Filtering is accomplished by a large-value capacitor between the input voltage and ground. Sometimes a second smaller-value input capacitor is connected in parallel, especially if the filter capacitor is not close to the IC regulator, to prevent oscillation. This capacitor needs to be located close to the IC regulator. Finally, an output capacitor (typically $0.1\ \mu\text{F}$ to $1.0\ \mu\text{F}$) is placed in parallel with the output to improve the transient response.

 

(a) Standard configuration

Type number	Output voltage
7805	+5.0 V
7806	+6.0 V
7808	+8.0 V
7809	+9.0 V
7812	+12.0 V
7815	+15.0 V
7818	+18.0 V
7824	+24.0 V

(b) The 7800 series

 

(c) Typical metal and plastic packages

FIGURE 2–27 The 7800 series three-terminal fixed positive voltage regulators.

Examples of fixed three-terminal regulators are the 78XX and 79XX series of regulators that are available with various output voltages and can supply up to 1 A of load current (with adequate heat sinking). The last two digits of the number stand for the output voltage; thus, the 7812 has a +12 V output. The negative output versions of the same regulator are numbered as the 79XX series; the 7912 has a -12 V output. The output voltage from these regulators is between 1.5% and 4% of the nominal value but will hold a nearly constant output despite changes in the input voltage or output load. A basic fixed +5 V power supply with a 7805 regulator is shown in Figure 2-28. Data sheets for the 78XX and 79XX series of regulators can be found at www.onsemi.com.

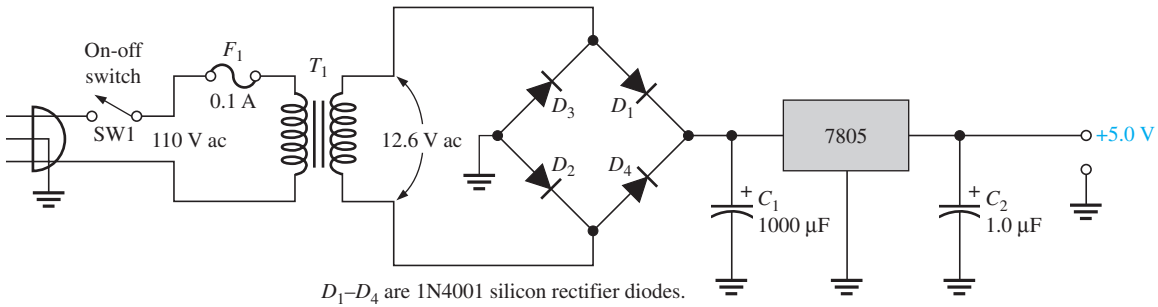



FIGURE 2-28 A basic +5.0 V power supply.

As an example of the reduction in ripple that can be obtained from a 7812 regulator, note the typical ripple rejection specification, RR , in the data sheet. For the 7812, the typical ripple rejection is 60 dB (refer to Section 1-4 for a review of decibels). This means that the output ripple is 60 dB less than the input ripple, a very significant reduction as illustrated in the next example.

All of the power supply designs covered in this chapter are linear power supplies. Many systems today use switch-mode power supplies (SMPSs). Switch-mode power supplies use switching voltage regulators (covered in Chapter 11) rather than the IC voltage regulators covered in this section. SMPSs offer several advantages and disadvantages compared to linear power supplies. They are lighter and more efficient, but they are more complex, and harder to troubleshoot. They can also produce significant amounts of EMI as a result of the high-speed switching action of the regulator, usually between 50 kHz and 1 MHz.

Switch mode power supplies can also result in poor power factor and high harmonic content in the power distribution grid. This is a growing problem since almost all computers use SMPSs. In some jurisdictions, especially in Europe, SMPSs are required to include power factor correction circuitry. Despite these drawbacks, SMPSs are becoming more common than linear power supplies in many systems. To alleviate problems with switching noise, often designers will add an IC regulator to the output of a switching regulator.

SYSTEM NOTE

 

EXAMPLE 2-3

Assume the input ripple to an MC7812B regulator is 100 mV. What is the typical output ripple? From the data sheet, the typical ripple rejection is 60 dB.

SOLUTION

The decibel voltage ratio is

$$\text{dB} = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$$

Since 60 dB is an attenuation, it is shown with a negative sign.

$$-60 \text{ dB} = 20 \log \left(\frac{V_{out}}{V_{in}} \right)$$

Dividing by 20,

$$-3.0 = \log\left(\frac{V_{out}}{100 \text{ mV}}\right)$$

and eliminating the log results in

$$10^{-3.0} = \frac{V_{out}}{100 \text{ mV}}$$

$$V_{out} = (100 \text{ mV})1.0 \times 10^{-3} = \mathbf{100 \mu\text{V}}$$

PRACTICE EXERCISE

Find the output ripple for an MC7805B, using the typical value specified on the data sheet found at www.onsemi.com.

Another type of three-terminal regulator is an adjustable regulator. Figure 2–29 shows a power supply circuit with an adjustable output, controlled by the variable resistor, R_2 . Note that R_2 is adjustable from zero to 1.0 k Ω . The LM317 regulator keeps a constant 1.25 V between the output and adjust terminals. This produces a constant current in R_1 of $1.25 \text{ V}/240 \Omega = 52 \text{ mA}$. If we neglect the very small current through the adjust terminal, the current in R_2 is the same as the current in R_1 . The output is taken across both R_1 and R_2 and is found from the equation,

$$V_{out} = 1.25 \text{ V} \left(\frac{R_1 + R_2}{R_1} \right)$$

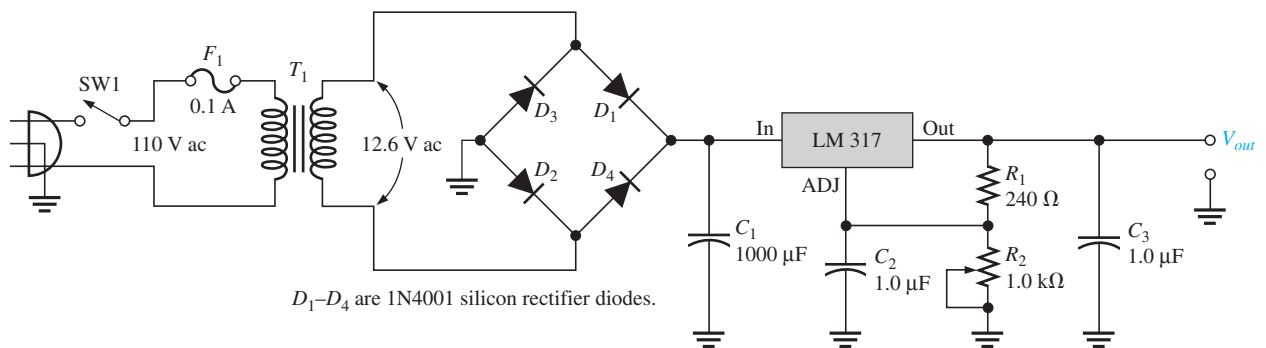


FIGURE 2–29 A basic power supply with a variable output voltage (from 1.25 V to 6.5 V).

MULTISIM



Open file F02-29 found on the companion website. This simulation illustrates the operation of the LM 317 adjustable voltage regulator.

Notice that the output voltage from the power supply is the regulator's 1.25 V multiplied by a ratio of resistances. For the case shown in Figure 2–29, when R_2 is set to the minimum (zero) resistance, the output is 1.25 V. When R_2 is set to the maximum, the output is nearly 6.5 V.

Percent Regulation

The regulation expressed as a percentage is a figure of merit used to specify the performance of a voltage regulator. It can be in terms of input (line) regulation or load regulation. **Line regulation** specifies how much change occurs in the output voltage for a given change in the input voltage. It is typically defined as a ratio of a change in output voltage for a corresponding change in the input voltage expressed as a percentage.

$$\text{Line regulation} = \left(\frac{\Delta V_{OUT}}{\Delta V_{IN}} \right) 100\%$$

(2–3)

Load regulation specifies how much change occurs in the output voltage over a certain range of load current values, usually from minimum current (no load, NL) to maximum current (full load, FL). It is normally expressed as a percentage and can be calculated with the following formula:

$$\text{Load regulation} = \left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) 100\% \quad (2-4)$$

where V_{NL} is the output voltage with no load and V_{FL} is the output voltage with full (maximum) load. Line and load regulation are discussed further in Section 11-1.

EXAMPLE 2-4

Assume a certain MC7805B regulator has a measured no-load output voltage of 5.185 V and a full-load output of 5.152 V. What is the load regulation expressed as a percentage? Is this within the manufacturer's specification?

SOLUTION

$$\text{Load regulation} = \left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) = \left(\frac{5.185 \text{ V} - 5.152 \text{ V}}{5.152 \text{ V}} \right) 100\% = \mathbf{0.64\%}$$

The data sheet for the MC7805B indicates a maximum variation of the output voltage (with a load current from 5 mA to 1.0 A) of 100 mV. This represents a maximum load regulation of 2% (typical is 0.4%). The measured percent regulation is within specifications.

PRACTICE EXERCISE

If the no-load output voltage of a regulator is 24.8 V and the full-load output is 23.9 V, what is the load regulation expressed as a percentage?


The preceding discussion concentrated on the popular three-terminal regulators. Three-terminal regulators can be adapted to a number of specialized applications or requirements such as current sources or automatic shutdown, current limiting, and the like. For certain other applications (high current, high efficiency, high voltage), more complicated regulators are constructed from integrated circuits and discrete transistors. Chapter 11 discusses some of these applications in more detail.

SYSTEM EXAMPLE 2-2

A LINEAR POWER SUPPLY

The power supply is an important part of most electronic systems because it supplies the dc voltage and current necessary for all the other circuits in the system to operate. A typical power supply converts ac power into a constant dc voltage. In this system example we will look at some of the design criteria that must be considered, even in a simple system like a basic linear power supply. This system will be illustrated in two stages. In the first stage, we will calculate the required components for an unregulated 16 V output. In the second stage, we will reduce the output voltage to a regulated +12 V. A schematic of the initial design is shown in Figure SE2-6. Assume that the initial design criteria are as follows:

- Input voltage is 120 V @ 60 Hz
- DC output voltage should be +16 V \pm 10% for stage 1.
- Load current: 250 mA (max)

 

 


FIGURE SE2-6 Linear power supply with filter capacitor

- Ripple factor: 0.03 (max)
- Fusing should be done on the primary side of the transformer
- Costs should be kept as low as possible

THE TRANSFORMER: The dc output voltage from the bridge must be $16\text{ V} \pm 10\%$. Therefore the peak transformer secondary voltage must be $\pm 16\text{ V}$ plus the bridge diode drops. Transformers are rated in rms voltages, so the rms secondary voltage must be calculated. Several considerations come into play in choosing the transformer. It must have the necessary turns ratio and be able to handle the maximum load current. It should also be an “off-the-shelf” component if possible to keep costs down.

THE FUSE: The fuse must be chosen based upon several factors. It must have a high enough current rating so that it doesn’t blow during maximum load current, or during any surge current when the capacitor is charging. It must have a low enough current rating so the transformer, bridge, and load, are protected if an over-current event occurs. Since the fuse is installed on the primary side of the transformer, all calculations must be based on primary current.

THE RECTIFIER BRIDGE: The bridge is comprised of four separate rectifier diodes or a single IC package. The IC bridge is the best choice as only a single part must be kept in stock and assembly costs will be lower with a single component. Maximum forward current and PIV must be determined when choosing the IC bridge.

THE FILTER CAPACITOR: The filter capacitor and the load resistance determine the ripple voltage. In order to determine the minimum acceptable value of the filter capacitor for a 0.03 ripple factor, some calculations are required.

Ripple factor (r) is found as

$$r = \frac{V_{r(pp)}}{V_{DC}}$$

where: $V_{r(pp)}$ is the peak-to-peak ripple voltage

$V_{r(pp)}$ can be approximated as

$$V_{r(pp)} = \left(\frac{1}{fR_L C} \right) V_{P(rect)}$$

where: f = the frequency of the pulsating dc voltage from the rectifier

$V_{P(rect)}$ = peak unfiltered output voltage from the rectifier.

Transposing the $V_{r(pp)}$ equation we solve for the minimum value of C and find that a $4700\ \mu\text{F}$ capacitor will allow us to meet our ripple factor specifications. The voltage rating of the capacitor must also be taken into account. Note that the value of R_L is determined by the dc output voltage and the maximum load current.

Regulated DC Power Supply

The second stage of this circuit design is to add voltage regulation and an LED indicator to show when the circuit is powered. The power supply should provide a fixed output voltage of $+12\ \text{V}_{dc}$. Maximum load current is to remain the same. The schematic for this circuit is illustrated in Figure SE2-7.

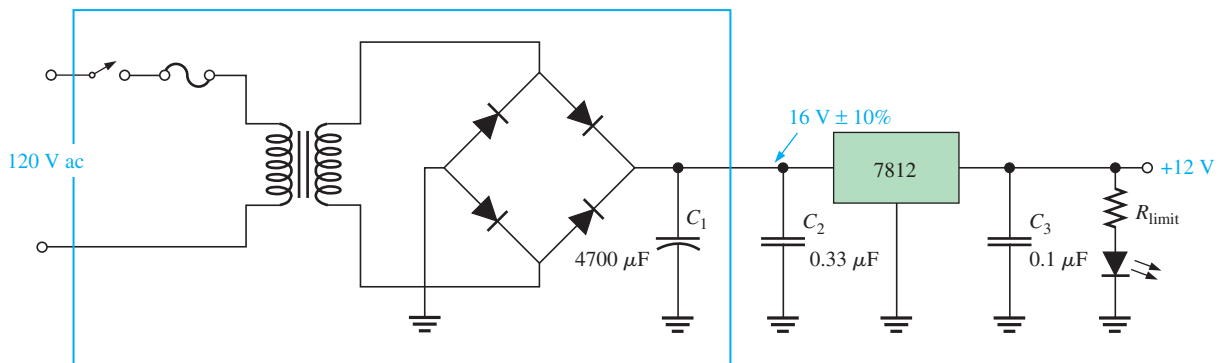


FIGURE SE2-7 Regulated linear power supply

THE REGULATOR: A simple 78XX series linear voltage regulator is a good choice for this circuit. Since the last two digits of the 78XX series indicate the output voltage, an MC7812 is chosen. Whenever possible, heat sinking is a good idea. The cost is small and it will increase the stability and life expectancy of the regulator.

Note from the 78XX spec sheet that the manufacturer recommends that a $0.33\ \mu\text{F}$ capacitor be connected from the input terminal to ground. It also suggests another capacitor may be connected from the output terminal to ground to improve transient response. The input capacitor helps eliminate high-frequency oscillations. You may wonder why a small capacitor is connected in parallel with the large filter capacitor. The reason is that large electrolytic capacitors have internal equivalent series resistance, and some inductance, which can affect the high frequency response of the circuit. Again, make sure that the capacitors have the proper voltage rating.

THE LED CIRCUIT: The LED requires a current limiting resistor. A red LED is commonly chosen as an “ON” indicator. The value of the current limiting resistor is calculated based upon the test current range in the spec sheet. You must also determine the power rating of the resistor.

CIRCUIT SIMULATION: It would be wise to simulate the circuit prior to construction using Multisim or other simulation software.

PROTOTYPING AND TESTING: Once the simulation tests are complete, the circuit can be built and tested. A PCB must be designed and the board populated. A possible circuit board layout is shown in Figure SE2-8. Finally, the circuit is evaluated to make certain that it meets all circuit design parameters, and final production costs can be calculated. As you can see, there are a number of decisions, calculations, and measurements that must be made even for a relatively simple circuit such as this.

MULTISIM



Open file SE02-08 found on the companion website. This simulation will be used to determine if all design criteria for this power supply design have been met.

 


FIGURE SE2-8 Regulated 12 V power supply on a printed circuit board.

SECTION 2-6 CHECKUP

1. What causes the ripple voltage on the output of a capacitor-input filter?
2. The load resistance of a capacitor-filtered full-wave rectifier is reduced. What effect does this reduction have on the ripple voltage?
3. What advantages are offered by a three-terminal regulator?
4. What is the difference between input (line) regulation and load regulation?

2-7 DIODE LIMITING AND CLAMPING CIRCUITS


Diode circuits, called limiters or clippers, are sometimes used to clip off portions of signal voltages above or below certain levels. Another type of diode circuit, called a clamper, is used to restore a dc level to an electrical signal.

After completing this section, you should be able to


- Analyze the operation of diode limiters and clippers
- Explain how a diode limiter works and determine the clipping level for a given circuit
- Explain how a diode clamping circuit works
- Cite applications for diode limiting and clamping circuits

Diode Limiters

Figure 2-30(a) shows a diode circuit called a **limiter** (also called a clipper) that limits or clips off the positive part of the input signal. As the input signal goes positive, the diode becomes forward-biased. Because the cathode is at ground potential (0 V), the anode cannot exceed 0.7 V (assuming a silicon diode). Thus, point A is clipped at +0.7 V when the input exceeds this value.

 

 (a) Limiting of the positive alternation; diode conducts on positive alternation.



(b) Limiting of the negative alternation; diode conducts on negative alternation.

FIGURE 2-30 Diode limiting (clipping circuits).

Whenever the input is below 0.7 V, the diode is reverse-biased and appears as an open. The output voltage looks like the negative part of the input, but with a magnitude determined by the voltage divider formed by R_1 and R_L , as follows:

$$V_{out} = \left(\frac{R_L}{R_1 + R_L} \right) V_{in}$$

If R_1 is small compared to R_L , then $V_{out} \cong V_{in}$.

Turn the diode around, as in Figure 2-30(b), and the negative part of the input is clipped off. When the diode is forward-biased during the negative part of the input, point A is held at -0.7 V by the diode drop. When the input goes above -0.7 V, the diode is no longer forward-biased; and a voltage appears across R_L proportional to the input.

A LIMITER APPLICATION Figure 2-31 shows an application of a limiter. Suppose you wanted to use the power line to synchronize a computer operation to the ac line. In the case shown, a half-wave rectifier is connected to a 6.3 V output from a transformer. The peak signal from the rectifier is approximately 9 V, too large for a computer input. Computers and other logic circuits are designed for a specific voltage maximum (typically +5.0 V) that cannot be exceeded without risking serious damage to the computer. The limiter shown in the figure prevents the signal to the computer from exceeding 4.7 V.

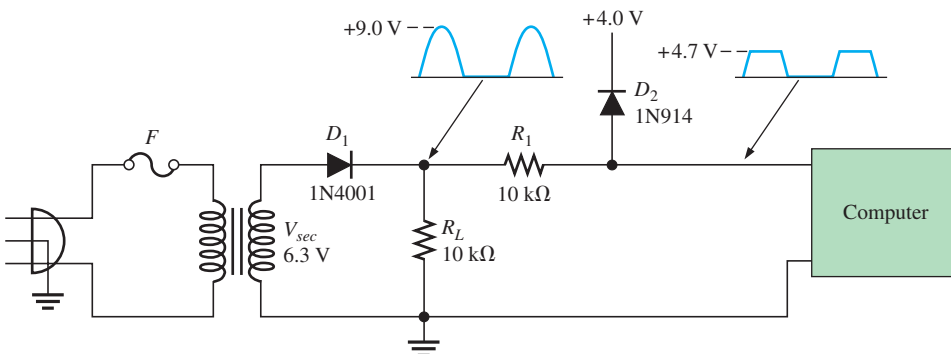


FIGURE 2-31 Limiting the signal into a computer.

EXAMPLE 2-5

What would you expect to see displayed on an oscilloscope connected as shown in Figure 2-32? The time base on the scope is set to show one and one-half cycles.

 


FIGURE 2-32

SOLUTION

The diode is forward-biased and conducts when the input voltage goes below -0.7 V. Thus, a negative limiter with a peak output voltage across R_L can be determined by the following equation:

$$V_{p(out)} = \left(\frac{R_L}{R_1 + R_L} \right) V_{p(in)} = \left(\frac{1.0 \text{ k}\Omega}{1.1 \text{ k}\Omega} \right) 10 \text{ V} = \mathbf{9.1 \text{ V}}$$

The scope will display an output waveform as shown in Figure 2-33.

 


FIGURE 2-33 Waveforms for Figure 2-32.

PRACTICE EXERCISE

Describe the output waveform for Figure 2-32 if R_L is changed to 680Ω .

ADJUSTMENT OF THE LIMITING LEVEL To adjust the level at which a signal voltage is limited, a bias voltage can be added in series with the diode, as shown in Figure 2-34. The voltage at point A must equal $V_{BB} + 0.7$ V before the diode will become forward-biased and conduct. Once the diode begins to conduct, the voltage at point A is limited to $V_{BB} + 0.7$ V so that all input voltage above this level is clipped off, as shown in the figure.

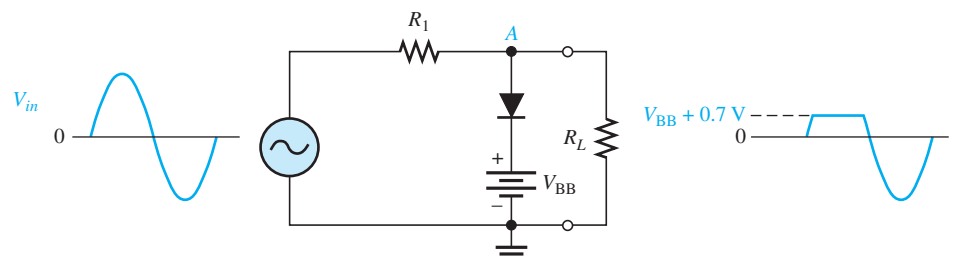


FIGURE 2-34 A positive limiter with positive bias.

If the bias voltage is varied up or down, the clipping level changes correspondingly, as shown in Figure 2-35. If the polarity of the bias voltage is reversed, as in Figure 2-36, voltages above $-V_{BB} + 0.7\text{ V}$ are clipped, resulting in an output waveform as shown. The diode is reverse-biased only when the voltage at point A goes below $-V_{BB} + 0.7\text{ V}$.

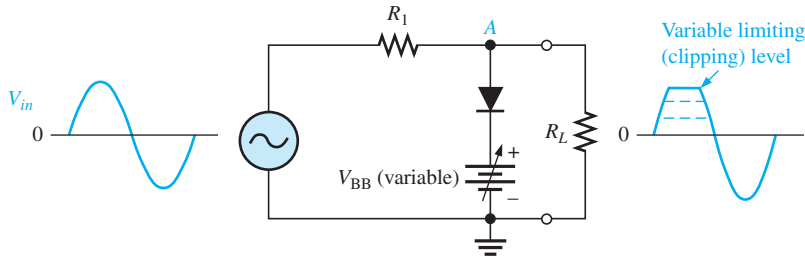


FIGURE 2-35 A positive limiter with variable positive bias.

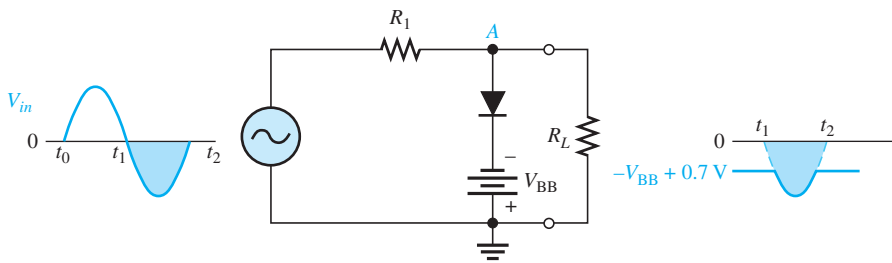


FIGURE 2-36 A positive limiter with negative bias. Notice that the positive side of the waveform is limited above $-V_{BB} + 0.7\text{ V}$.

If it is necessary to clip the voltage below a specified negative level, then the diode and bias voltage must be connected as in Figure 2-37. In this case, the voltage at point A must go below $-V_{BB} - 0.7\text{ V}$ to forward-bias the diode and initiate clipping action, as shown.

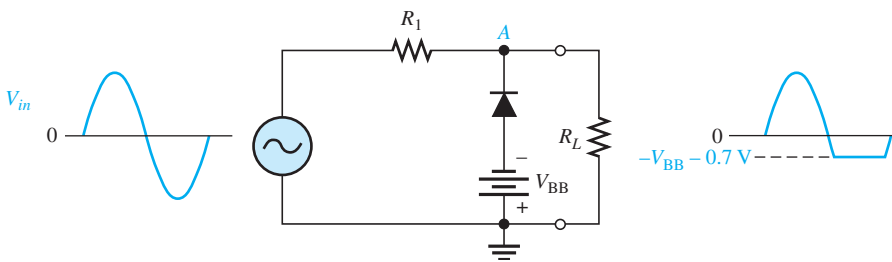


FIGURE 2-37 A negative limiter with negative bias.

EXAMPLE 2-6

Figure 2-38 shows a circuit combining a positive-biased limiter with a negative-biased limiter. Determine the output waveform.

 
 


FIGURE 2-38

SOLUTION

When the voltage at point *A* reaches +7.7 V, diode D_1 conducts and limits the waveform at +7.7 V. Diode D_2 does not conduct until the voltage reaches -7.7 V. Therefore, positive voltages above +7.7 V and negative voltages below -7.7 V are clipped. The resulting output waveform is shown in Figure 2-39.

FIGURE 2-39 Output waveform for Figure 2-38.

**PRACTICE EXERCISE**

Determine the output waveform in Figure 2-38 if both dc sources are 10 V and the input has a peak value of 20 V.

Diode Clampers

A diode **clammer** adds a dc level to an ac signal. Clampers are sometimes known as *dc restorers*. Figure 2-40 shows a diode clamper that inserts a positive dc level in the output waveform. To understand the operation of this circuit, consider the first negative half-cycle of the input voltage. When the input initially goes negative, the diode is forward-biased, allowing the capacitor to charge to near the peak of the input ($V_{p(in)} - 0.7$ V), as shown in Figure 2-40(a). Just past the negative peak, the diode becomes reverse-biased. This is because the cathode is held near $V_{p(in)}$ by the charge on the capacitor.

The capacitor can discharge only through the high resistance of R_L . Thus, from the peak of one negative half-cycle to the next, the capacitor discharges very little. The amount that is discharged, of course, depends on the value of R_L . For good clamping action, the RC time constant should be at least ten times the period of the input signal.

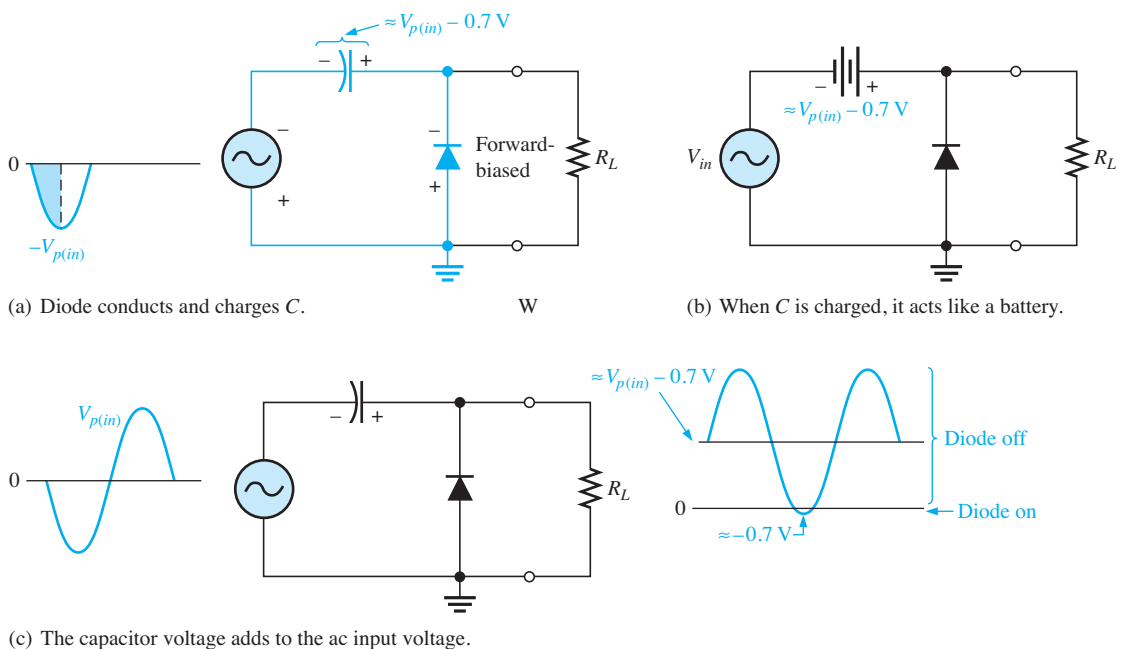


FIGURE 2-40 Positive clamping. The diode allows the capacitor to charge rapidly. The capacitor can discharge only through R_L .

The net effect of the clamping action is that the capacitor retains a charge approximately equal to the peak value of the input less the diode drop. The capacitor voltage acts essentially as a battery in series with the input signal, as shown in Figure 2-40(b). The dc voltage of the capacitor adds to the ac input voltage by superposition, as shown in Figure 2-40(c).

If the diode is turned around, a negative dc voltage is added to the input signal to produce the output signal, as shown in Figure 2-41. If necessary, the diode can be biased to adjust the clamping level.

 


FIGURE 2-41 Negative clamping.

EXAMPLE 2-7

What is the output voltage that you would expect to observe across R_L in the clamping circuit of Figure 2-42? Assume that RC is large enough to prevent significant capacitor discharge.

 


FIGURE 2-42

SOLUTION

Ideally, a negative dc value equal to the input peak less the diode drop is inserted by the clamping circuit.

$$V_{DC} \cong -(V_{p(in)} - 0.7 \text{ V}) = -(24 \text{ V} - 0.7 \text{ V}) = -23.3 \text{ V}$$

Actually, the capacitor will discharge slightly between peaks, and, as a result, the output voltage will have an average value of slightly less than that calculated previously. The output waveform goes to approximately 0.7 V above ground, as shown in Figure 2-43.

 


FIGURE 2-43 Output waveform for Figure 2-42.

PRACTICE EXERCISE

What output voltage would you observe across R_L in Figure 2-42 if the polarity of the diode and the polarity of the capacitor were reversed?

SECTION 2-7 CHECKUP

1. Discuss how diode limiters and diode clampers differ in terms of their function.
2. What happens if the diode is reversed in a limiter?
3. To limit the output of a positive limiter to +5 V when a +10 V peak input is applied, what value must the bias voltage be?
4. What component in a clamper circuit effectively acts as a battery?

2-8 SPECIAL-PURPOSE DIODES

The preceding discussion of diodes has focused on applications that exploit the fact that a diode is a one-way conductor. A number of diodes are designed for other applications. In this section, several special-purpose diodes, namely the zener diode, the varactor diode, the photodiode, and the light-emitting diode will be considered.

After completing this section, you should be able to

- Explain the characteristics of four different special-purpose diodes
- Describe the characteristic curve for a zener diode
- Show how a zener diode can be used as a basic regulator
- Explain how a varactor diode is used as a variable capacitor
- Discuss the basic principles of light-emitting diodes (LEDs) and photodiodes

Zener Diodes



FIGURE 2-44 Zener symbol.

Figure 2-44 shows the schematic symbol for a **zener diode**. The zener diode is a silicon *pn* junction device that differs from the rectifier diode in that it is designed for operation in the reverse-breakdown region. Zeners with breakdown voltages of 1.8 V to 200 V are commercially available. The breakdown voltage is set by carefully controlling the doping level during manufacture. From the discussion of the diode characteristic curve in Section 2-4, recall that when a diode reaches reverse breakdown, its voltage remains almost constant even though the current may change drastically. This volt-ampere characteristic is shown again in Figure 2-45.

 


FIGURE 2-45 Diode IV characteristic curve.

The principal applications of zener diodes are as a voltage reference and for voltage regulators in low-current applications. As a regulator, zeners have limitations: they do not

have the high ripple rejection of integrated circuit regulators (discussed in Section 2-6) and they can't handle large load current changes. By combining a zener diode with a transistor or op-amp, better regulators can be constructed.

Figure 2-46 shows the reverse portion of the characteristic curve of a zener diode. Notice that as the reverse voltage (V_R) is increased, the reverse current (I_R) remains extremely small up to the knee of the curve. At this point, the breakdown effect begins; the internal zener ac resistance begins to decrease as the reverse current increases rapidly. This resistance is generally shown on a data sheet as impedance, Z_Z . From the bottom of the knee, the zener breakdown voltage (V_Z) remains essentially constant although, it increases slightly as I_Z increases. This constant voltage region of the characteristic curve accounts for the zener's ability to regulate.

A minimum value of reverse current, I_{ZK} , must be maintained in order to keep the diode in regulation. You can see on the curve in Figure 2-46 that when the reverse current is reduced below the knee of the curve, the voltage decreases drastically and regulation is lost. Also, there is a maximum current, I_{ZM} , above which the diode may be damaged. Thus, basically, the zener diode maintains a nearly constant voltage across its terminals for values of reverse current ranging from I_{ZK} to I_{ZM} . A nominal zener voltage, V_{ZT} , is usually specified on a data sheet at a value of reverse current called the *zener test current*, I_{ZT} .

 


FIGURE 2-46 Reverse characteristic of a zener diode. V_Z is usually specified at the test current, I_{ZT} , and is designated V_{ZT} .

ZENER EQUIVALENT CIRCUIT Figure 2-47(a) shows the ideal approximation of a zener diode in reverse breakdown. It acts simply as a battery having a value equal to the nominal zener voltage. Figure 2-47(b) represents the practical equivalent of a zener, where the zener impedance (Z_Z) is included. Since the actual voltage curve is not ideally vertical, a change in zener current (ΔI_Z) produces a small change in zener voltage (ΔV_Z), as illustrated in Figure 2-47(c).

By Ohm's law, the ratio of ΔV_Z to ΔI_Z is the zener impedance, as expressed in the following equation:

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} \tag{2-5}$$

Normally, Z_Z is specified at I_{ZT} , the zener test current. In most cases, you can assume that Z_Z is constant over the full linear range of zener current values.

 


FIGURE 2-47 Zener diode equivalent circuits and the characteristic curve illustrating Z_Z .

EXAMPLE 2–8

A certain zener diode exhibits a 50 mV change in V_Z for a 2 mA change in I_Z on the linear portion of the characteristic curve between I_{ZK} and I_{ZM} . What is the zener impedance?


SOLUTION

$$Z_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{50 \text{ mV}}{2 \text{ mA}} = 25 \Omega$$


PRACTICE EXERCISE

Calculate the zener impedance if the zener voltage changes 120 mV for a 15 mA change in zener current.

 ZENER VOLTAGE REGULATION As mentioned, zener diodes can be used for **voltage regulation** in noncritical applications. Figure 2–48 illustrates how a zener diode can be used to regulate a varying dc input voltage to keep it at a constant level. As you learned earlier, this process is called line regulation. (See Section 2–6.)



 (a) As the input voltage increases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).



(b) As the input voltage decreases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).

FIGURE 2–48 Zener regulation of a varying input voltage.

As the input voltage varies (within limits), the zener diode maintains a nearly constant voltage across the output terminals. However, as V_{IN} changes, I_Z will change proportionally, and therefore the limitations on the input variation are set by the minimum and

maximum current values (I_{ZK} and I_{ZM}) with which the zener can operate and on the condition that $V_{IN} > V_Z$. R is the series current-limiting resistor. The bar graph on the DMM symbols indicates the relative values and trends. Many DMMs provide analog bar graph displays in addition to the digital readout.

EXAMPLE 2-9

Figure 2-49 shows a zener diode regulator designed to hold 10 V at the output. Assume the zener impedance is zero and the zener current ranges from 4 mA minimum (I_{ZK}) to 40 mA maximum (I_{ZM}). What are the minimum and maximum input voltages for these currents?

 


FIGURE 2-49

SOLUTION

For the minimum current, the voltage across the 1.0 kΩ resistor is

$$V_R = I_{ZK}R = (4 \text{ mA})(1.0 \text{ k}\Omega) = 4 \text{ V}$$

Since $V_R = V_{IN} - V_Z$,

$$V_{IN} = V_R + V_Z = 4 \text{ V} + 10 \text{ V} = \mathbf{14 \text{ V}}$$

For the maximum zener current, the voltage across the 1.0 kΩ resistor is

$$V_R = (40 \text{ mA})(1.0 \text{ k}\Omega) = 40 \text{ V}$$

Therefore,

$$V_{IN} = 40 \text{ V} + 10 \text{ V} = \mathbf{50 \text{ V}}$$

As you can see, this zener diode can provide line regulation for an input voltage that varies from 14 V to 50 V and maintain approximately a 10 V output. The output will vary slightly from this value because of the zener's impedance.

PRACTICE EXERCISE

Determine the minimum and maximum input voltages that can be regulated by the zener in Figure 2-50 if the minimum current (I_{ZK}) is 2.5 mA and the maximum (I_{ZM}) is 35 mA.

 


FIGURE 2-50

Varactor Diodes

 


FIGURE 2-51 The reverse-biased varactor diode acts as a variable capacitor.

Varactor diodes are also known as variable-capacitance diodes because the junction capacitance varies with the amount of reverse-bias voltage. Varactors are specifically designed to take advantage of this variable-capacitance characteristic. The capacitance can be changed by changing the reverse voltage. These devices are commonly used in electronic tuning circuits used in communications systems.

A **varactor** is basically a reverse-biased *pn* junction that utilizes the inherent capacitance of the depletion region. The depletion region, created by the reverse bias, acts as a capacitor dielectric because of its nonconductive characteristic. The *p* and *n* regions are conductive and act as the capacitor plates, as illustrated in Figure 2-51.

Recall that capacitance is determined by the plate area (*A*), dielectric constant (ϵ), and dielectric thickness (*d*), as expressed in the following formula:

$$C = \frac{A\epsilon}{d}$$

As the reverse-bias voltage increases, the depletion region widens, effectively increasing the dielectric thickness and thus decreasing the capacitance. When the reverse-bias voltage decreases, the depletion region narrows, thus increasing the capacitance. This action is shown in Figure 2-52(a) and (b). A general curve of capacitance versus voltage is shown in Figure 2-52(c).


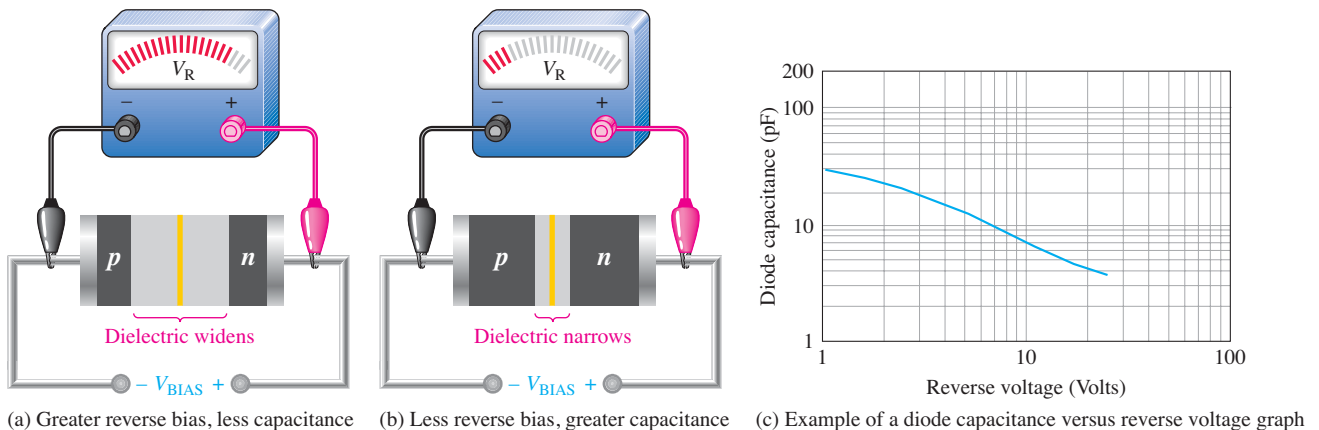


FIGURE 2-52 Varactor diode capacitance varies with reverse voltage.

In a varactor diode, the capacitance parameters are controlled by the method of doping in the depletion region and the size and geometry of the diode’s construction. Varactor capacitances typically range from a few picofarads to a few hundred picofarads.

Figure 2-53(a) shows a common symbol for a varactor, and Figure 2-53(b) shows a simplified equivalent circuit. The internal reverse series resistance is labeled r_s , and the variable capacitance is labeled C_V .

FIGURE 2-53 Varactor diode.

 

A major application of varactors is in tuning circuits used in many communications systems. For example, electronic tuners in TV and other commercial receivers utilize varactors as one of their elements. When used in a resonant circuit, the varactor acts as a variable capacitor, thus allowing the resonant frequency to be adjusted by a variable voltage level, as illustrated in Figure SN2-1 where two varactor diodes provide the total variable capacitance in a parallel resonant (tank) circuit. V_C is a variable dc voltage that controls the reverse bias and therefore the capacitance of the diodes.

Recall that the resonant frequency of the tank circuit is

$$f_r \cong \frac{1}{2\pi\sqrt{LC}}$$

 


FIGURE SN2-1 Varactors in a resonant circuit.

This approximation is valid for $Q > 10$.

SYSTEM NOTE



EXAMPLE 2-10

The capacitance of a certain varactor can be varied from 5 pF to 50 pF. The diode is used in a tuned circuit similar to that shown in Figure SN2-1. Determine the tuning range for the circuit if $L = 10$ mH.

SOLUTION

The equivalent circuit is shown in Figure 2-54. Notice that the varactor capacitances are in series; the total *minimum* capacitance is the product-over-sum of the individual capacitor's minimum value.

$$C_{T(\min)} = \frac{C_{1(\min)}C_{2(\min)}}{C_{1(\min)} + C_{2(\min)}} = \frac{(5 \text{ pF})(5 \text{ pF})}{5 \text{ pF} + 5 \text{ pF}} = 2.5 \text{ pF}$$

The maximum resonant frequency, therefore, is

$$f_{r(\max)} = \frac{1}{2\pi\sqrt{LC_{T(\min)}}} = \frac{1}{2\pi\sqrt{(10 \text{ mH})(2.5 \text{ pF})}} \cong 1 \text{ MHz}$$

 


FIGURE 2-54

The maximum total capacitance is

$$C_{T(\max)} = \frac{C_{1(\max)}C_{2(\max)}}{C_{1(\max)} + C_{2(\max)}} = \frac{(50 \text{ pF})(50 \text{ pF})}{50 \text{ pF} + 50 \text{ pF}} = 25 \text{ pF}$$

The minimum resonant frequency, therefore, is

$$f_{r(\min)} = \frac{1}{2\pi\sqrt{LC_{T(\max)}}} = \frac{1}{2\pi\sqrt{(10 \text{ mH})(25 \text{ pF})}} \cong 318 \text{ kHz}$$

PRACTICE EXERCISE

Determine the tuning range for Figure 2–54 if $L = 2.7 \text{ mH}$.

Light-Emitting Diodes (LEDs)

As the name implies, the **light-emitting diode** is a light emitter; LEDs are used as indicators (such as in logic probes), in displays such as the familiar seven-segment displays used in many digital clocks, and as sources for optical fiber communication systems. IR-emitting diodes, related to LEDs, are used in optical coupling applications (such as isolating electrocardiogram sensors on a patient from the measuring instrument) and in remote control applications.

The basic operation of the light-emitting diode (LED) is as follows: When the device is forward-biased, electrons cross the pn junction from the n region and recombine with holes in the p region. These free electrons are in the conduction band and are at a higher energy level than the holes in the valence band. When recombination takes place, the recombining electrons release energy in the form of heat and light. A large exposed surface area on one layer of the semiconductive material permits the photons to be emitted as visible light. Figure 2–55 illustrates this process which is called **electroluminescence**.

FIGURE 2–55 Electroluminescence in an LED.

 


FIGURE 2–56 LED schematic symbol.

The semiconductive materials used in LEDs are gallium arsenide (GaAs), gallium arsenide phosphide (GaAsP), and gallium phosphide (GaP). Silicon and germanium are not used because they are essentially heat-producing materials and are very poor at producing light. GaAs LEDs emit infrared (IR) radiation, which is invisible. GaAsP produces either red or yellow visible light, and GaP emits red or green visible light. LEDs that emit blue light are also available. The schematic symbol for an LED is shown in Figure 2–56.

The LED emits light in response to a sufficient forward current (I_F), as shown in Figure 2-57(a). The amount of power output translated into light is directly proportional to the forward current, as indicated in Figure 2-57(b). Typical LEDs are shown in Figures 2-57(c) and 2-57(d).



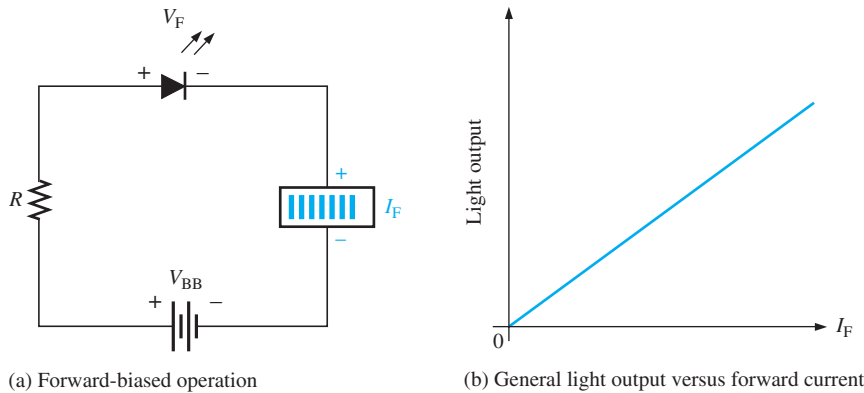


FIGURE 2-57 Operation of an LED.

 

(c) Typical small LEDs for indicators

 

(d) Typical LEDs for lighting applications


LED Applications

Standard LEDs are used for indicator lamps and readout displays on a wide variety of instruments, ranging from consumer appliances to scientific apparatus. A common type of display device using LEDs is the seven-segment display. Combinations of the segments form the ten decimal digits as illustrated in Figure 2-58. Each segment in the display is an LED. By forward-biasing selected combinations of segments, any decimal digit and a decimal point can be formed. Two types of LED circuit arrangements are the common anode and common cathode as shown.


One common application of an infrared LED is in remote control units for TV, DVD, gate openers, etc. The IR LED sends out a beam of invisible light that is sensed by the receiver in your TV, for example. For each button on the remote control unit, there is a unique code. When a specific button is pressed, a coded electrical signal is generated that goes to the LED, which converts the electrical signal to a coded infrared light signal. The TV receiver recognizes the code and takes appropriate action, such as changing the channel or increasing the volume.

Also, IR light-emitting diodes are used in optical coupling applications, often in conjunction with fiber optics. Areas of application include industrial processing and control, position encoders, bar graph readers, and optical switching.

FIGURE 2-58 The 7-segment LED display.

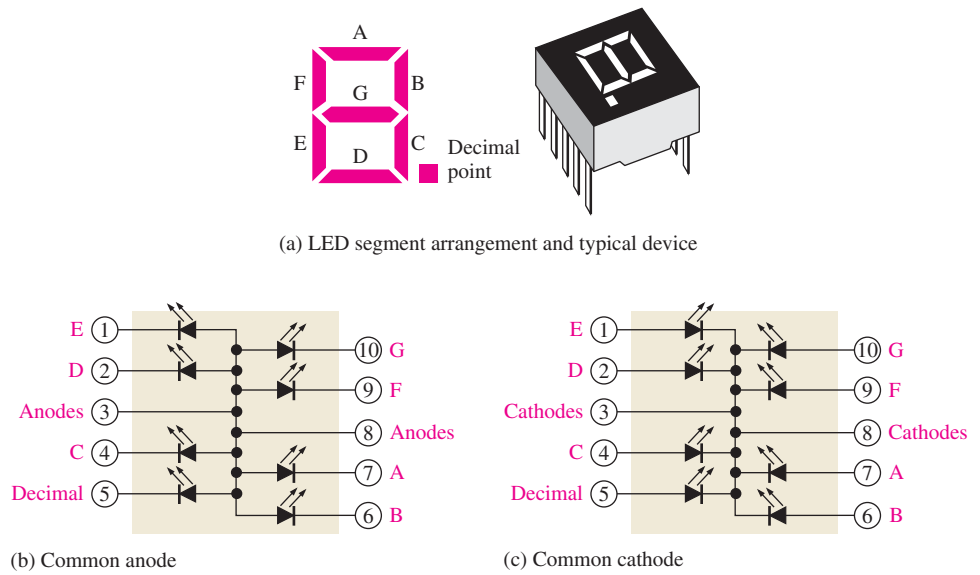

SYSTEM EXAMPLE 2-3

 

BASEBALL COUNTING SYSTEM

IR LEDs and detectors find many applications in systems for which there is a need to count items. Figure SE2-9 shows an example of a system for counting baseballs as they are fed down a chute into a box for shipping. As each ball passes through the chute, the IR beam emitted by the LED is interrupted. This is detected by the photodiode (discussed later) and the resulting change in current is sensed by a detector circuit. An electronic circuit counts each time that the beam is interrupted; and when a preset number of balls pass through the chute, the “stop” mechanism is activated to stop the flow of balls until the next empty box is automatically moved into place on the conveyor. When the next box is in place, the “stop” mechanism is deactivated and the balls begin to roll again. This idea can also be applied to inventory and packing control for many other types of products.

 


FIGURE SE2-9 Basic concept and block diagram of a counting and control system.

High-Intensity LEDs

LEDs that produce much greater light outputs than standard LEDs are found in many applications including traffic lights, automotive lighting, indoor and outdoor advertising and informational signs, and home lighting.

TRAFFIC LIGHTS LEDs are quickly replacing the traditional incandescent bulbs in traffic signal applications. Arrays of tiny LEDs form the red, yellow, and green lights in a traffic light unit. An LED array has three major advantages over the incandescent bulb: brighter light, longer lifetime (years vs. months), and less energy consumption (about 90% less).

LED traffic lights are constructed in arrays with lenses that optimize and direct the light output. Figure 2-59(a) illustrates the concept of a traffic light array using red LEDs. A relatively low density of LEDs is shown for illustration. The actual number and spacing of the LEDs in a traffic light unit depends on the diameter of the unit, the type of lens, the color, and the required light intensity. With an appropriate LED density and a lens, an 8- or 12-inch traffic light will appear essentially as a solid-color circle.

LEDs in an array are usually connected either in a series-parallel or a parallel arrangement. A series connection is not practical because if one LED fails open, then all the LEDs are disabled. For a parallel connection, each LED requires a limiting resistor. To reduce the number of limiting resistors, a series-parallel connection can be used, as shown in Figure 2-59(b).


 


FIGURE 2-59 LED traffic light.

 

Special application LEDs are also commonly used as transmitters in fiber optic telecommunication systems. They differ from conventional LEDs in a number of ways. They only emit light in the infrared rather than the visible spectrum and over a much narrower angle (emission pattern) for better coupling to the fiber optic cable. This is a result of the way that LEDs used in fiber optic systems emit light.

LEDs are divided into two types, based upon how they emit light. Conventional LEDs are *surface emitting*; they emit light from the top. The emitting area is large, and even though the output of this type of LED may be high, not as much of the light can be coupled into an optical fiber. *Edge-emitting* LEDs emit light from their edge and have a very small aperture, usually between 30 and 50 μm . This allows them to couple very well to a multimode fiber optic cable which has a diameter of between 50 and 62.5 μm . A new type of edge-emitting LED called a *superradiant* LED has a very narrow emission spectrum (1-2% of the central wavelength) and can provide power levels that rival laser diodes. A comparison of top and edge-emitting LEDs is shown in Figure SN2-2.

 


FIGURE SN2-2 Top and edge-emitting LEDs

LED DISPLAYS LEDs are widely used in large and small signs and message boards color, multicolor, or full-color. Full-color screens use a tiny grouping of high-intensity red, green, and blue LEDs to form a **pixel**. A typical screen is made of thousands of RGB pixels with the exact number determined by the sizes of the screen and the pixel.

Red, green, and blue (RGB) are primary colors and when mixed together in varying amounts, can be used to produce any color in the visible spectrum. A basic pixel formed by three LEDs is shown in Figure 2–60. The light emission from each of the three diodes can be varied independently by varying the amount of forward current. Yellow is added to the three primary colors (RGBY) in some TV screen applications.

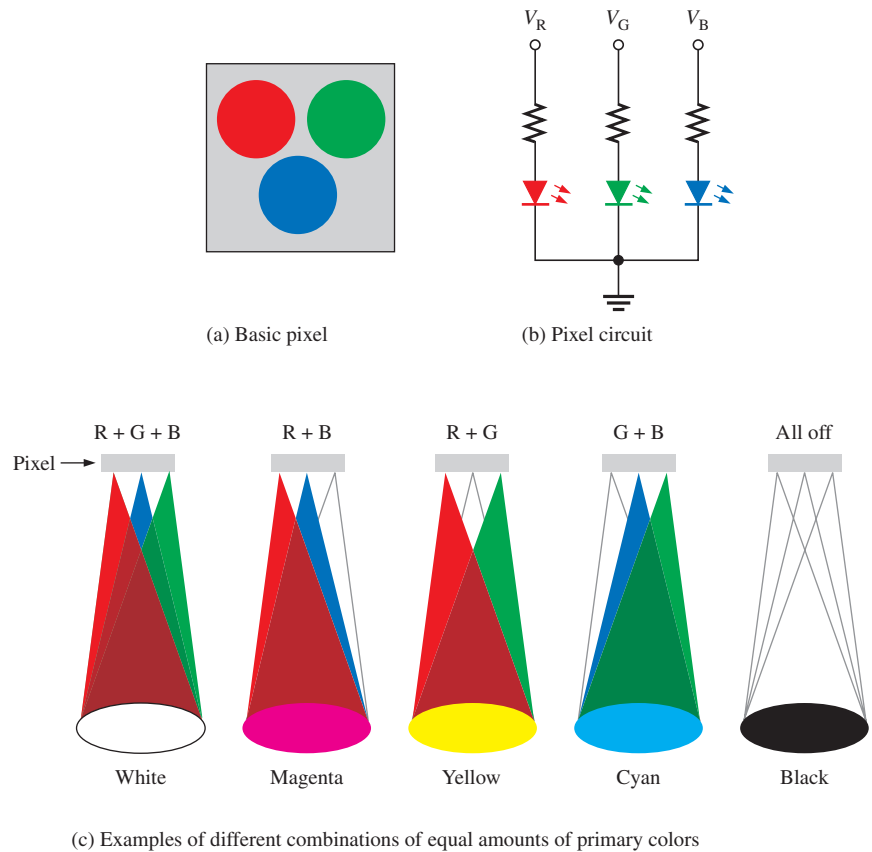


FIGURE 2–60 The concept of an RGB pixel used in LED display screens.

OTHER APPLICATIONS High-intensity LEDs are becoming more widely used in automotive lighting for taillights, brakelights, turn signals, back-up lights, and interior applications. LED arrays are expected to replace most incandescent bulbs in automotive lighting. Eventually, headlights may also be replaced by white LED arrays. LEDs can be seen better in poor weather and can last 100 times longer than an incandescent bulb.

LEDs are also finding their way into interior home and business lighting applications. Arrays of white LEDs may eventually replace incandescent light bulbs and fluorescent lighting in interior living and work areas. Most white LEDs use a blue GaN (gallium nitride) LED covered by a yellowish phosphor coating made of a certain type of crystals that have been powdered and bound in a type of viscous adhesive. Since yellow light stimulates the red and green receptors of the eye, the resulting mix of blue and yellow light gives the appearance of white.

The Organic LED (OLED)

An **OLED** is a device that consists of two or three layers of materials composed of organic molecules or polymers that emit light with the application of voltage. OLEDs produce light through the process of electrophosphorescence. The color of the light depends on the type of organic molecule in the emissive layer. The basic structure of a 2-layer OLED is shown in Figure 2-61.

 



FIGURE 2-61 Basic structure of a top-emitting 2-layer OLED.

Electrons are provided to the emissive layer and removed from the conductive layer when there is current between the cathode and anode. This removal of electrons from the conductive layer leaves holes. The electrons from the emissive layer recombine with the holes from the conductive layer near the junction of the two layers. When this recombination occurs, energy is released in the form of light that passes through the transparent cathode material. If the anode and substrate are also made from transparent materials, light is emitted in both directions, making the OLED useful in applications such as heads-up displays.

OLEDs can be sprayed onto substrates just like inks are sprayed onto paper during printing. Inkjet technology greatly reduces the cost of OLED manufacturing and allows OLEDs to be printed onto very large films for large displays like 80-inch TV screens or electronic billboards.

OLED technology was developed by Eastman Kodak. It is beginning to replace LCD (liquid crystal display) technology in handheld devices such as PDAs and cellular phones. OLEDs are brighter, thinner, faster, and lighter than conventional LEDs or LCDs. They also use less power and are cheaper to manufacture.

SYSTEM NOTE

 

The Photodiode

The **photodiode** is a *pn* junction device that operates in reverse bias, as shown in Figure 2-62, where I_λ is the reverse current. Note the schematic symbol for the photodiode. The photodiode has a small transparent window that allows light to strike the *pn* junction.

Recall that when reverse-biased, a rectifier diode has a very small reverse leakage current. The same is true for the photodiode. The reverse-biased current is produced by thermally generated electron-hole pairs in the depletion region, which are swept across the junction by the electric field created by the reverse voltage. In a rectifier diode, the reverse leakage current increases with temperature due to an increase in the number of electron-hole pairs.



 


FIGURE 2-62 Photodiode.

In a photodiode, the reverse current increases with the light intensity at the *pn* junction. When there is no incident light, the reverse current (I_λ) is almost negligible and is called the *dark current*. An increase in the amount of light energy (measured in lumens per square meter, lm/m^2) produces an increase in the reverse current, as shown by the graph in Figure 2–63(a). For a given value of reverse-bias voltage, Figure 2–63(b) shows a set of characteristic curves for a typical photodiode.

 

(a)

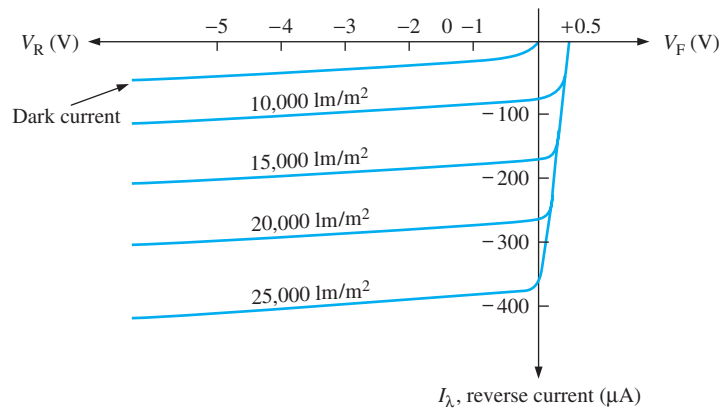

(b)

FIGURE 2–63 Typical photodiode characteristics.

From the characteristic curve in Figure 2–63(b), the dark current for this particular device is approximately 35 μA at a reverse-bias voltage of -3 V. Therefore, the reverse resistance of the device with no incident light is

$$R_R = \frac{V_R}{I_\lambda} = \frac{3 \text{ V}}{35 \mu\text{A}} = 86 \text{ k}\Omega$$

At 25,000 lm/m^2 , the current is approximately 400 μA at -3 V. The resistance under this condition is

$$R_R = \frac{V_R}{I_\lambda} = \frac{3 \text{ V}}{400 \mu\text{A}} = 7.5 \text{ k}\Omega$$

These calculations show that the photodiode can be used as a variable-resistance device controlled by light intensity.

Figure 2–64 illustrates that the photodiode allows essentially no reverse current (except for a very small dark current) when there is no incident light. When a light beam strikes the photodiode, it conducts an amount of reverse current that is proportional to the light intensity.

 


FIGURE 2-64 Operation of a photodiode.

SECTION 2-8 CHECKUP

1. How are zener diodes normally operated?
2. What does the parameter I_{ZM} refer to?
3. What is the purpose of a varactor diode?
4. Based on the general curve in Figure 2-53(c), what happens to the diode capacitance when the reverse voltage is increased?
5. List some semiconductive materials used for LEDs.
6. There is a small current in a photodiode under no-light conditions. What is this current called?

2-9 THE DIODE DATA SHEET

A manufacturer's data sheet gives detailed information on a device so that it can be used properly in a given application. A typical data sheet provides maximum ratings, electrical characteristics, mechanical data, and graphs of various parameters.

After completing this section, you should be able to

- Interpret and use a diode data sheet
 - Identify maximum voltage and current ratings
 - Determine the electrical characteristics of a diode
 - Analyze graphical data
 - Select an appropriate diode for a given set of specifications

Table 2-1 shows the maximum ratings for a certain series of rectifier diodes. The data sheet for the 1N4001 through 1N4007 series of diodes can be found at www.onsemi.com. These are the absolute maximum values under which the diode can be operated without damage to the device. For greatest reliability and longer life, the diode should always be operated well under these maximums. Generally, the maximum ratings are specified at 25°C and must be adjusted downward for greater temperatures.

An explanation of some of the parameters from Table 2-1 follows.

V_{RRM} The maximum reverse peak voltage that can be applied repetitively across the diode. Notice that in this case, it is 50 V for the 1N4001 and 1 kV for the 1N4007. This is the same as PIV rating.

TABLE 2-1

RATING	SYMBOL	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	UNIT
Peak repetitive reverse voltage	V_{RRM}								
Working peak reverse voltage	V_{RWM}	50	100	200	400	600	800	1000	V
DC blocking voltage	V_R								
Nonrepetitive peak reverse voltage	V_{RSM}	60	120	240	480	720	1000	1200	V
rms reverse voltage	$V_{R(rms)}$	35	70	140	280	420	560	700	V
Average rectified forward current (single-phase, resistive load, 60 Hz, $T_A = 75^\circ\text{C}$)	I_O	1.0							A
Nonrepetitive peak surge current (surge applied at rated load conditions)	I_{FSM}	30 (for 1 cycle)							A
Operating and storage junction temperature range	T_J, T_{stg}	-65 to +175							$^\circ\text{C}$

V_R The maximum reverse dc voltage that can be applied across the diode.

V_{RSM} The maximum reverse peak value of nonrepetitive (one-cycle) voltage that can be applied across the diode.

I_O The maximum average value of a 60 Hz rectified forward current.

I_{FSM} The maximum peak value of nonrepetitive (one-cycle) forward current. The graph in Figure 2-65 expands on this parameter to show values for more than one cycle at temperatures of 25°C and 175°C . The dashed lines represent values where typical failures occur. Notice what happens on the lower solid line when ten cycles of I_{FSM} are applied. The limit is 15 A rather than the one-cycle value of 30 A.

 


FIGURE 2-65 Nonrepetitive forward surge current capability.

Table 2-2 lists typical and maximum values of certain electrical characteristics for the 1N4001–1N4007 series. These items differ from the maximum ratings in that they are not selected by design but are the result of operating the diode under specified conditions. A brief explanation of these parameters follows.

- v_F The instantaneous voltage across the forward-biased diode when the forward current is 1 A at 25°C. Figure 2-66 shows how the forward voltages vary with forward current.
- $V_{F(av)}$ The maximum forward voltage drop averaged over a full cycle (also shown as V_F on some data sheets).
- I_R The maximum current when the diode is reverse-biased with a dc voltage.

TABLE 2-2 • Electrical characteristics.				
CHARACTERISTICS AND CONDITIONS	SYMBOL	TYPICAL	MAXIMUM	UNIT
Maximum instantaneous forward voltage drop ($I_F = 1\text{ A}$, $T_J = 25^\circ\text{C}$)	v_F	0.93	1.1	V
Maximum full-cycle average forward voltage drop ($I_O = 1\text{ A}$, $T_L = 75^\circ\text{C}$, 1 in. leads)	$V_{F(av)}$	—	0.8	V
Maximum reverse current (rated dc voltage) $T_J = 25^\circ\text{C}$ $T_J = 100^\circ\text{C}$	I_R	0.05 1.0	10.0 50.0	μA
Maximum full-cycle average reverse current ($I_O = 1\text{ A}$, $T_L = 75^\circ\text{C}$, 1 in. leads)	$I_{R(av)}$	—	30.0	μA

 








FIGURE 2-66 Forward voltage (V_F) versus forward current (I_F).

$I_{R(avg)}$ The maximum reverse current averaged over one cycle (when reverse-biased with an ac voltage).

T_L The lead temperature.

Figure 2–67 shows a selection of rectifier diodes arranged in order of increasing I_O , I_{FSM} , and V_{RRM} ratings.

V_{RRM} (Volts)	I_O , Average Rectified Forward Current (Amperes)					
	1.0	1.5	3.0		6.0	
	59-03 (DO-41) Plastic 	59-04 Plastic 	60-01 Metal 	267-03 Plastic 	267-02 Plastic 	194-04 Plastic 
50	1N4001	1N5391	1N4719	MR500	1N5400	MR750
100	1N4002	1N5392	1N4720	MR501	1N5401	MR751
200	1N4003	1N5393 MR5059	1N4721	MR502	1N5402	MR752
400	1N4004	1N5395 MR5060	1N4722	MR504	1N5404	MR754
600	1N4005	1N5397 MR5061	1N4723	MR506	1N5406	MR756
800	1N4006	1N5398	1N4724	MR508		MR758
1000	1N4007	1N5399	1N4725	MR510		MR760
I_{FSM} (Amps)	30	50	300	100	200	400
T_A @ Rated I_O (°C)	75	$T_L = 70$	75	95	$T_L = 105$	60
T_C @ Rated I_O (°C)						
T_J (Max) (°C)	175	175	175	175	175	175










V_{RRM} (Volts)	I_O , Average Rectified Forward Current (Amperes)										
	12	20	24	25	30		40	50	25	35	40
	245A-02 (DO-203AA) Metal 	339-02 Plastic 	193-04 Plastic 	193-04 Plastic 	43-02 (DO-21) Metal 		42A-01 (DO-203AB) Metal 	43-04 Metal 	309A-03 	309A-02 	
50	MR1120 1N1199,A,B	MR2000	MR2400	MR2500	1N3491	1N3659	1N1183A	MR5005	MDA2500	MDA3500	
100	MR1121 1N1200,A,B	MR2001	MR2401	MR2501	1N3492	1N3660	1N1184A	MR5010	MDA2501	MDA3501	
200	MR1122 1N1202,A,B	MR2002	MR2402	MR2502	1N3493	1N3661	1N1186A	MR5020	MDA2502	MDA3502	MDA4002
400	MR1124 1N1204,A,B	MR2004	MR2404	MR2504	1N3495	1N3663	1N1188A	MR5040	MDA2504	MDA3504	MDA4004
600	MR1126 1N1206,A,B	MR2006	MR2406	MR2506			1N1190A		MDA2506	MDA3506	MDA4006
800	MR1128	MR2008		MR2508					MDA2508	MDA3508	MDA4008
1000	MR1130	MR2010		MR2510					MDA2510	MDA3510	
I_{FSM} (Amps)	300	400	400	400	300	400	800	600	400	400	800
T_A @ Rated I_O (°C)											
T_C @ Rated I_O (°C)	150	150	125	150	130	100	150	150	55	55	35
T_J (Max) (°C)	190	175	175	175	175	175	190	195	175	175	175


FIGURE 2–67 A selection of rectifier diodes based on maximum ratings of I_O , I_{FSM} , and V_{RRM} .

SECTION 2-9 CHECKUP

- List the three rating categories typically given on all diode data sheets.
- Define each of the following parameters: V_F , I_R , and I_O .
- Define I_{FSM} , V_{RRM} , and V_{RSM} .
- From Figure 2-67, select a diode to meet the following specifications: $I_O = 3\text{ A}$, $I_{FSM} = 300\text{ A}$, and $V_{RRM} = 100\text{ V}$.

 2-10 TROUBLESHOOTING

The backbone for nearly all electronic circuits is the power supply. Several types of failures can occur in power supplies. In this section, we will expand on our earlier coverage of troubleshooting by looking at specific power supply failures and the effects they would have on the supply's operation. Then we'll look at one more example of how you might troubleshoot a regulated power supply.



After completing this section, you should be able to

- Troubleshoot a power supply using accepted techniques
 - Discuss the steps in forming a troubleshooting plan
 - Explain fault analysis
 - Describe symptoms that are likely for different failures

As discussed in Section 1-5, the first step in troubleshooting is to analyze the clues (symptoms) of a failure. These clues should lead to a logical plan for troubleshooting. The plan for a circuit that has never worked will be different than one that has been working. The history of past failures, or failures in a similar circuit, can also be a clue to a failure.

It is always useful to have a good understanding of the circuit you are troubleshooting and a schematic. There is no one plan that fits all situations; the one to use depends on the type and complexity of the circuit or system, the nature of the problem, and the preference of the individual technician.

A Troubleshooting Plan

Above all else, efficient troubleshooting requires logical thinking and a plan that will find the simple problems (such as a blown fuse) quickly. As an example, consider the following plan for troubleshooting a power supply that has failed in operation.

- Step 1:** Ask questions of the person reporting the trouble. When did it fail? (Right after it was plugged in? After running for 2 hours at maximum current out?) How do you know it failed? (Smoke? Low voltage?)
- Step 2:** Power check: Make sure the power cord is plugged in and the fuse is not burned out. Check that the controls are set for proper operation. Something this simple is often the cause of the problem. Perhaps the operator did not understand the correct settings required for controls.
- Step 3:** Sensory check: Beyond the power check, the simplest troubleshooting method relies on your senses of observation to check for obvious defects. Remove power, open the supply, and do a visual check for broken wires, poor solder connections, burned out fuses, and the like. Also, when certain types of components fail, you may be able to detect a smell of smoke if you happen to be there when it fails or shortly afterward. Since some failures are temperature dependent, you can sometimes use your sense of touch (carefully!) to detect an overheated component.

Step 4: Isolate the failure. Apply power to the supply while it is on the bench and trace the voltage. As described in Section 1–5, you can start in the middle of the circuit and do half-splitting or check the voltage at successive test points from the input side until you get an incorrect measurement. Some problems are more difficult than simply finding no voltage, but tracing should isolate the problem to an area or a component.

Having reviewed a plan for troubleshooting, let's turn to fault analysis. When you find a symptom, you next need to ask the question, *If component X fails in the circuit, what are the symptoms?* You will apply fault analysis when you find an incorrect voltage or waveform. For example, assume you observe high ripple at the input to a regulator. From your knowledge of circuit operation, you might reason that a defective or incorrect value capacitor could be the culprit. The following discussion describes four possible failures and gives more examples of fault analysis.

Open Fuse or Circuit Breaker

An overcurrent-protection device is essential to virtually all electronic equipment. These devices prevent damage to the equipment in case of a failure or an overload condition and reduce the probability of a violent failure. Overcurrent-protection devices include fuses, circuit breakers, solid-state current-limiting devices, and thermal overload devices. The circuit breakers for the ac line cannot be counted on to protect electronic devices as they only open when the current is 15 A or more in the ac line, far too high to offer protection to most electronic equipment.

If a single fuse is present, it is usually on the primary side of the transformer, and will be rated for 115 or 230 VAC at a current that is consistent with the maximum power rating of the supply. Frequently, protection devices may also be included on the secondary side, especially if a single transformer has multiple outputs. A fuse is designed to carry its rated current indefinitely (and will typically carry 120% of its rated current for several hours). Fuses are available in fast- and slow-blow versions. A fast-blow fuse opens in a few milliseconds when overloaded; a slow-blow fuse can survive transient overloads such as occurs when power is first applied. Most of the time, slow-blow fuses should be used on the input side of a power supply circuit.


Testing for an open fuse is relatively simple. Glass fuses can be checked by inspection or checked with an ohmmeter (be certain power is disconnected from the circuit). If power is still applied, a blown fuse will have voltage across it (provided there are no other opens in the path, such as a switch). Usually an open fuse is symptomatic of a short circuit or overload; however, fuses can have fatigue failure and may be the only problem in the circuit.

Before replacing a blown fuse, the technician should check for the cause. If the fuse simply opened, it may be a fatigue failure. If the fuse has blown violently (as evidenced by complete vaporization of the wire inside), it is most likely that it opened due to another problem. Look for a short circuit with an ohmmeter; it can be the load, the filter capacitor, or other component that has shorted. Look for any visible signs of an overheated or damaged component. If the fuse is replaced, it is important to replace it with the identical type and current rating as specified by the manufacturer. The wrong fuse can cause further damage and may be a safety hazard.


Open Diode

Consider the full-wave, center-tapped rectifier in Figure 2–68. Assume that diode D_1 has failed open. This causes diode D_2 to conduct on only the negative cycle. With an oscilloscope connected to the output, as shown in part (a), you would observe a larger-than-normal ripple voltage at a frequency of 60 Hz rather than 120 Hz. Disconnecting the filter capacitor, you would observe a half-wave rectified voltage, as in part (b).

 With the filter capacitor in the circuit, the half-wave signal will allow it to discharge more than it would with a normal full-wave signal, resulting in a larger ripple voltage. Basically, the same observations would be made for an open failure of diode D_2 .



 (a) Ripple should be less and have a frequency of 120 Hz. Instead it is greater in amplitude with a frequency of 60 Hz.



(b) With C removed, output should be a full-wave 120 Hz signal. Instead it is a 60 Hz, half-wave voltage.

FIGURE 2-68 Symptoms of an open diode in a full-wave, center-tapped rectifier.

An open diode in a bridge rectifier would create symptoms identical to those just discussed for the center-tapped rectifier. As illustrated in Figure 2-69, the open diode would prevent current through R_L during half of the input cycle (in this case, the negative half). As a result, there would be a half-wave output and an increased ripple voltage at 60 Hz, as discussed before.

 



FIGURE 2-69 Effect of an open diode in a bridge rectifier. A half-wave operation results in an increased ripple at 60 Hz.

Generally, the easiest test for an open diode in a full-wave power supply is to measure the ripple frequency. If the ripple frequency is the same as the input ac frequency, look for an open diode or a connection problem with a diode (such as a cracked trace).


Shorted Diode

A shorted diode is one that has failed such that it has a very low resistance in both directions. If a diode suddenly became shorted in a bridge rectifier, normally a fuse would blow or other circuit protection would be activated. If the supply was not protected by a fuse, the shorted diode will most likely cause the transformer to be damaged or cause the other diode in series to open, as illustrated in Figure 2-70.

FIGURE 2-70 Effect of shorted diode in a bridge rectifier. Conducting paths are shown in color.

 

 (a) Positive half-cycle: The shorted diode acts as a forward-biased diode, so the load current is normal. D_3 and D_4 are reverse-biased.




(b) Negative half-cycle: The shorted diode places forward-biased D_4 across the secondary. As a result D_1, D_4 , or the transformer secondary will probably burn open, or a fuse (not shown) will open.

In part (a) of Figure 2-70, current is supplied to the load through the shorted diode during the first positive half-cycle, just as though it were forward-biased. During the negative half-cycle, the current is shorted through D_1 and D_4 , as shown in part (b). It is this excessive current that leads to the second failure; hence, when a shorted diode is discovered, it is a good idea to check other components for a failure.

Shorted or Leaky Filter Capacitor

Electrolytic capacitors can appear shorted (or have high “leakage” current) when they fail. One cause of failure that produces symptoms of a short occurs when an electrolytic capacitor is put in backwards, an error that can happen with newly manufactured circuit boards. As in the case of a shorted diode, the normal symptom is a blown fuse due to excessive current. A leaky capacitor is a form of partial failure; it can be represented by a leakage resistance in parallel with the capacitor, as shown in Figure 2-71(a). The effect of the leakage resistance is to reduce the discharging time constant, causing an increase in ripple voltage on the output, as shown in Figure 2-71(b). A leaky capacitor may simply overheat; a capacitor should never show signs of overheating. For an unfused supply, a shorted capacitor would most likely cause one or more diodes or the transformer to open due to excessive current. In any event, there would be no dc voltage on the output.

FIGURE 2-71 Effect of a leaky filter capacitor on the output of a full-wave rectifier. The capacitor has a dc path simulating a parallel resistance to the load.

 

(a)

(b)

R_{leak} causes faster-than-normal discharge, producing increased ripple.

When a defective capacitor is replaced, it is important to observe the working voltage specification as well as the size of the capacitor. If the working voltage specification is exceeded, the replacement is likely to fail again. In addition, it is vitally important to observe the polarity of the capacitor. An electrolytic capacitor installed backwards can literally explode.

Troubleshooting a Regulated Power Supply

As indicated at the beginning of this section, the plan for repairing any electronic equipment depends on the observed symptoms. Let's assume you have a supply like the one shown previously in Figure 2–28 that has blown a fuse immediately after it was connected to a printed circuit card. Your thinking might go like this: “The power supply was working fine until I added the card; perhaps I exceeded the current limit of the supply.” Here you have considered the conditions and hypothesized a possible cause. The first step then is to remove the load and test the supply to see if this clears the problem. If so, then check the current requirement of the card that was added, or check to see if it is drawing too much current. If not, the problem is in the supply.

What if a power supply is completely dead but has a good fuse? In this case, start tracing the voltage to isolate the problem. For example, you could check for voltage on the primary of the transformer; if there is voltage, then test the secondary voltage. If the primary does not have voltage, check the path for the ac—the switch and connections to the transformer. If a single open is in series with the ac line, the full ac voltage will appear across that open.

Let's assume you have found that the transformer has ac on the primary but no voltage on the secondary. This indicates that the transformer is open, either the primary or the secondary winding. An ohmmeter should confirm this. Before replacing it, you should look to see why the failure occurred. Transformers seldom fail if they are operated properly. The likelihood is that another component shorted in the circuit. Look for a shorted diode or capacitor as an initial cause.

As previously stated, the exact strategy for troubleshooting depends on what is found at each step, the ease of making a particular test, and the likely cause of a failure. The key is that the technician use a series of logical tests to reduce the problem to the exact cause.


SECTION 2-10 CHECKUP

1. What would you expect to see if R_1 of the power supply in Figure 2–29 were open?
2. You are checking a 60 Hz full-wave bridge rectifier and observe that the output has a 60 Hz ripple. What failure(s) do you suspect?
3. You observe that the output ripple of a full-wave rectifier is much greater than normal but its frequency is still 120 Hz. What component do you suspect?

SUMMARY

- The Bohr model of an atom consists of a nucleus containing positively charged protons and uncharged neutrons orbited by negatively charged electrons.
- Atomic shells are energy bands. The outermost shell containing electrons is the valence shell.
- Silicon is the predominant semiconductive material.
- Atoms within a semiconductor crystal structure are held together with covalent bonds.
- Electron-hole pairs are thermally produced.
- A *p*-type semiconductor is made by adding trivalent impurity atoms to an intrinsic (pure) semiconductor.
- An *n*-type semiconductor is made by adding pentavalent impurity atoms to an intrinsic (pure) semiconductor.
- The depletion region is a region adjacent to the *pn* junction containing no majority carriers.

- Forward bias permits majority carrier current through the pn junction.
- Reverse bias prevents majority carrier current.
- A pn junction is called a diode.
- Reverse breakdown occurs when the reverse-biased voltage exceeds a specified value.
- Three types of rectifiers are the half-wave, the center-tapped full-wave, and the bridge. The center-tapped and the bridge are both types of full-wave rectifiers.
- The single diode in a half-wave rectifier conducts for half of the input cycle and has the entire output current in it. The output frequency equals the input frequency.
- Each diode in the center-tapped full-wave rectifier and the bridge rectifier conduct for one-half of the input cycle but share the total current. The output frequency of a full-wave rectifier is twice the input frequency.
- The PIV (peak inverse voltage) is the maximum voltage appearing across a reverse-biased diode.
- A capacitor-input filter provides a dc output approximately equal to the peak of the input.
- Ripple voltage is caused by the charging and discharging of the filter capacitor.
- Three-terminal integrated circuit regulators provide a nearly constant dc output from an unregulated dc input.
- Regulation of output voltage over a range of input voltages is called input or line regulation.
- Regulation of output voltage over a range of load currents is called load regulation.
- Diode limiters (clippers) cut off voltage above or below specified levels.
- Diode clammers add a dc level to an ac signal.
- The zener diode operates in reverse breakdown.
- A zener diode maintains an essentially constant voltage across its terminals over a specified range of zener currents.
- Zener diodes are used to establish a reference voltage and in basic regulator circuits.
- A varactor diode acts as a variable capacitor under reverse-biased conditions.
- The capacitance of a varactor varies inversely with reverse-biased voltage.

 

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Bias The application of dc voltage to a diode or other electronic device to produce a desired mode of operation.

Clamper A circuit that adds a dc level to an ac signal; also called a *dc restorer*.

Diode An electronic device that permits current in only one direction.

Electron The basic particle of negative electrical charge in matter.

Energy The ability to do work.

Filter A type of electrical circuit that passes certain frequencies and rejects all others.

Forward bias The condition in which a pn junction conducts current.

Integrated circuit (IC) A type of circuit in which all the components are constructed on a single tiny chip of silicon.

Limiter A circuit that removes part of a waveform above or below a specified level; also called a *clipper*.

PN junction The boundary between n -type and p -type materials.

Rectifier An electronic circuit that converts ac into pulsating dc.

Reverse bias The condition in which a pn junction blocks current.

Semiconductor A material that has a conductance value between that of a conductor and that of an insulator. Silicon and germanium are examples.

KEY FORMULAS

- (2-1) $V_{p(out)} = V_{p(in)} - 0.7\text{ V}$ Half-wave and full-wave rectifier peak output voltage
- (2-2) $V_{out} = V_{sec} - 1.4\text{ V}$ Bridge rectifier peak output voltage
- (2-3) **Line regulation** = $\left(\frac{\Delta V_{OUT}}{\Delta V_{IN}}\right)100\%$ Line regulation expressed as a percentage
- (2-4) **Load regulation** = $\left(\frac{V_{NL} - V_{FL}}{V_{FL}}\right)100\%$ Load regulation expressed as a percentage
- (2-5) $Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$ Zener impedance

SELF-TEST

Answers are at the end of the chapter.

- When a neutral atom loses or gains a valence electron, the atom becomes
 (a) covalent (b) a metal (c) a crystal (d) an ion
- Atoms within a semiconductor crystal are held together by
 (a) metallic bonds (b) subatomic particles
 (c) covalent bonds (d) the valence band
- Free electrons exist in the
 (a) valence band (b) conduction band
 (c) lowest band (d) recombination band
- A hole is a
 (a) vacancy in the valence band (b) vacancy in the conduction band
 (c) positive electron (d) conduction-band electron
- The widest energy gap between the valence band and the conduction band occurs in
 (a) semiconductors (b) insulators (c) conductors (d) a vacuum
- The process of adding impurity atoms to a pure semiconductive material is called
 (a) recombination (b) crystallization (c) bonding (d) doping
- In a semiconductor diode, the region near the *pn* junction consisting of positive and negative ions is called the
 (a) neutral zone (b) recombination region
 (c) depletion region (d) diffusion area
- In a semiconductor diode, the two bias conditions are
 (a) positive and negative (b) blocking and nonblocking
 (c) open and closed (d) forward and reverse
- The voltage across a forward-biased silicon diode is approximately
 (a) 0.7 V (b) 0.3 V (c) 0 V (d) dependent on the bias voltage
- In Figure 2-72, identify the forward-biased diode(s).
 (a) D_1 (b) D_2 (c) D_3 (d) D_1 and D_3


 


FIGURE 2-72

 11. When the positive lead of an ohmmeter is connected to the cathode of a diode and the negative lead is connected to the anode, the meter reads a(n)
 - (a) very low resistance
 - (b) infinitely high resistance
 - (c) high resistance initially, decreasing to about $100\ \Omega$
 - (d) gradually increasing resistance
12. The output frequency of a full-wave rectifier with a 60 Hz sinusoidal input is
 - (a) 30 Hz
 - (b) 60 Hz
 - (c) 120 Hz
 - (d) 0 Hz
13. If a single diode in a center-tapped full-wave rectifier opens, the output is
 - (a) 0 V
 - (b) half-wave rectified
 - (c) reduced in amplitude
 - (d) unaffected
14. During the positive half-cycle of the input voltage in a bridge rectifier,
 - (a) one diode is forward-biased
 - (b) all diodes are forward-biased
 - (c) all diodes are reverse-biased
 - (d) two diodes are forward-biased
15. The process of changing a half-wave or a full-wave rectified voltage to a constant dc voltage is called
 - (a) filtering
 - (b) ac to dc conversion
 - (c) damping
 - (d) ripple suppression
16. Assume a particular IC regulator attenuates the input ripple by 60 dB. The output ripple will be attenuated by a factor of
 - (a) 60
 - (b) 600
 - (c) 1000
 - (d) 1,000,000
17. The purpose of a small capacitor placed across the output of an IC regulator is to
 - (a) improve transient response
 - (b) couple the output signal to the load
 - (c) filter the ac
 - (d) protect the IC regulator
18. A diode limiting circuit
 - (a) removes part of a waveform
 - (b) inserts a dc level
 - (c) produces an output equal to the average value of the input
 - (d) increases the peak value of the input
19. A clamping circuit is also known as a(n)
 - (a) averaging circuit
 - (b) inverter
 - (c) dc restorer
 - (d) ac restorer
20. The zener diode is designed for operation in
 - (a) zener breakdown
 - (b) forward bias
 - (c) reverse bias
 - (d) avalanche breakdown
21. Zener diodes are widely used as
 - (a) current limiters
 - (b) power distributors
 - (c) voltage regulators
 - (d) variable resistors
22. Varactor diodes are used as
 - (a) variable resistors
 - (b) variable current sources
 - (c) variable inductors
 - (d) variable capacitors
23. LEDs are based on the principle of
 - (a) forward bias
 - (b) electroluminescence
 - (c) photon sensitivity
 - (d) electron-hole recombination
24. In a photodiode, light produces
 - (a) reverse current
 - (b) forward current
 - (c) electroluminescence
 - (d) dark current



TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 2-76(a).

- If the power supply voltage is set for 10 V instead of 12 V,
 1. The positive peak voltage of the output will
 - (a) increase
 - (b) decrease
 - (c) not change

2. The negative peak voltage of the output will
 (a) increase (b) decrease (c) not change
3. The voltage across the $2.2\text{ k}\Omega$ resistor will
 (a) increase (b) decrease (c) not change

Refer to Figure 2-77(a).

- If the diode is open,
 4. The peak-to-peak output voltage will
 (a) increase (b) decrease (c) not change
 5. The center of the output waveform will
 (a) increase (b) decrease (c) not change
- If the capacitor is shorted,
 6. The peak-to-peak output voltage will
 (a) increase (b) decrease (c) not change
 7. The center of the output waveform will
 (a) increase (b) decrease (c) not change

Refer to Figure 2-85.

- If the capacitor is smaller than $1000\ \mu\text{F}$,
 8. The ripple frequency will
 (a) increase (b) decrease (c) not change
 9. The amplitude of the ripple voltage will
 (a) increase (b) decrease (c) not change
- If the zener diode is open,
 10. The output voltage will
 (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 2-5 Rectifiers

1. Sketch the waveforms for the load current and voltage for Figure 2-73. Show the peak values.

 


FIGURE 2-73

2. Determine the peak voltage and the peak power delivered to R_L in Figure 2-74.

 


FIGURE 2-74

3. Consider the circuit in Figure 2–75.
 - (a) What type of circuit is this?
 - (b) What is the total peak secondary voltage?
 - (c) Find the peak voltage across each half of the secondary.
 - (d) Sketch the voltage waveform across R_L .
 - (e) What is the peak current through each diode?
 - (f) What is the PIV for each diode?

 


FIGURE 2-75

4. Show how to connect the diodes in a center-tapped rectifier in order to produce a negative-going full-wave voltage across the load resistor.
5. What PIV rating is required for the diodes in a bridge rectifier that produces an average output voltage of 50 V?

SECTION 2-6 Rectifier Filters and IC Regulators

6. The ideal dc output voltage of a capacitor-input filter is the (peak, average) value of the rectified input.
7. The minimum ripple rejection for a 7805 regulator is 68 dB. Compute the output ripple voltage for an input that has 150 mV of ripple.
8. If the no-load output voltage of a regulator is 15.5 V and the full-load output is 14.9 V, what is the percent load regulation?
9. Assume a regulator has a percent load regulation of 0.5%. What is output voltage at full-load if the unloaded output is 12.0 V?
10. For the variable output supply shown in Figure 2–29, what setting of R_2 would provide an output of 5.0 V?
11. For the variable output supply shown in Figure 2–29, what maximum output voltage could be obtained if R_2 were replaced with a 1.5 kΩ resistor?

SECTION 2-7 Diode Limiting and Clamping Circuits

12. Sketch the output waveforms for each circuit in Figure 2–76.

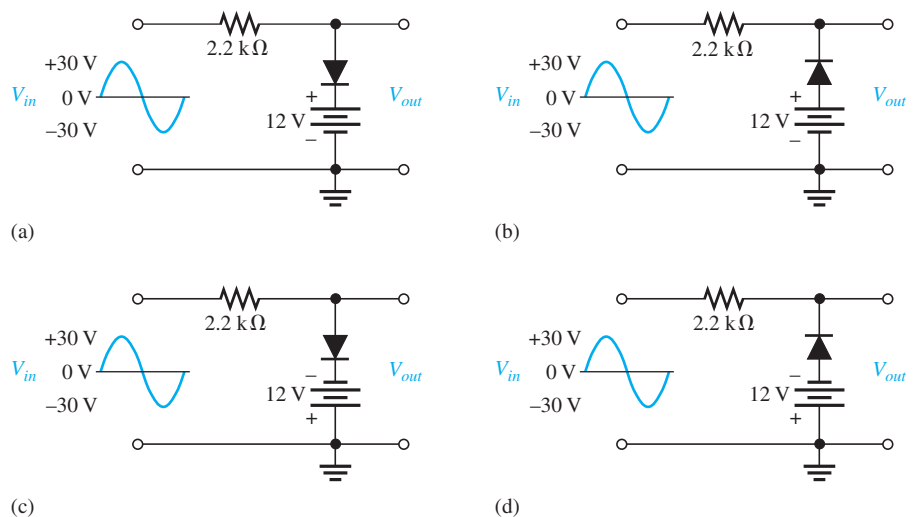


FIGURE 2-76

13. Describe the output waveform of each circuit in Figure 2-77. Assume that the RC time constant is much greater than the period of the input.

 


FIGURE 2-77

SECTION 2-8 Special-Purpose Diodes

14. Figure 2-78 shows a zener diode regulator designed to hold 5.0 V at the output. Assume the zener resistance is zero and the zener current ranges from 2 mA minimum (I_{ZK}) to 30 mA maximum (I_{ZM}). What are the minimum and maximum input source voltages for these currents?
15. A certain zener diode has a $V_Z = 7.5$ V and a $Z_Z = 5 \Omega$ at a certain current. Sketch the equivalent circuit.
16. To what value must R be adjusted in Figure 2-79 to make $I_Z = 40$ mA? Assume that $V_Z = 12$ V at 30 mA and $Z_Z = 30 \Omega$.

 


FIGURE 2-78

 


FIGURE 2-79

17. Assume the output of a zener regulator circuit drops from 8.0 V with no load to 7.8 V with a 500 Ω load. What is the percent load regulation?
18. Figure 2-80 is a curve of reverse voltage versus capacitance for a certain varactor. Determine the change in capacitance if V_R varies from 5 V to 20 V.
19. Refer to Figure 2-80 and determine the value of V_R that produces a capacitance of 25 pF.
20. What capacitance value is required for each of the varactors in Figure 2-81 to produce a resonant frequency of 1 MHz?

 


FIGURE 2-80

 


FIGURE 2-81

21. At what value must the control voltage be set in Problem 20 if the varactors have the characteristic curve in Figure 2–80?
22. When the switch in Figure 2–82 is closed, will the microammeter reading increase or decrease? Assume that D_1 and D_2 are optically coupled.
23. With no incident light, there is a certain amount of reverse current in a photodiode. What is this current called?

 


FIGURE 2–82

SECTION 2–9 The Diode Data Sheet

24. From the data sheet, determine how much peak inverse voltage that a 1N4933 diode can withstand. The data sheet can be found at www.onsemi.com.
25. Repeat Problem 24 for a 1N4936.
26. If the peak output voltage of a full-wave bridge rectifier is 50 V, determine the minimum value of the surge-limiting resistor required when 1N4933 diodes are used.

SECTION 2–10 Troubleshooting

27. From the meter readings in Figure 2–83, determine the most likely problem. State how you could quickly isolate the exact location of the problem.

 


FIGURE 2–83

28. Each part of Figure 2–84 shows oscilloscope displays of rectifier output voltages. In each case, determine whether or not the rectifier is functioning properly and, if it is not, what is (are) the most likely failure(s). Assume all displays are set for the same time per division.

 


FIGURE 2–84

29. For each set of measured voltages at the points 1, 2, and 3 indicated in Figure 2–85, determine if they are correct and if not identify the most likely fault(s). State what you would do to correct the problem once it is isolated. The specs for the 1N5349 can be found at www.onsemi.com.
- (a) $V_1 = 110\text{ V rms}$, $V_2 \cong 30\text{ V dc}$, $V_3 \cong 12\text{ V dc}$
 - (b) $V_1 = 110\text{ V rms}$, $V_2 \cong 30\text{ V dc}$, $V_3 \cong 30\text{ V dc}$
 - (c) $V_1 = 0\text{ V}$, $V_2 = 0\text{ V}$, $V_3 = 0\text{ V}$
 - (d) $V_1 = 110\text{ V rms}$, $V_2 \cong 30\text{ V peak full-wave } 120\text{ Hz voltage}$, $V_3 \cong 12\text{ V}$, $120\text{ Hz pulsating voltage}$
 - (e) $V_1 = 110\text{ V rms}$, $V_2 = 0\text{ V}$, $V_3 = 0\text{ V}$

 


FIGURE 2–85

30. Determine the most likely failure in the circuit board of Figure 2–86 for each of the following symptoms. State the corrective action you would take in each case. The normal output of the transformer is 12.6 V ac. The regulator (IC1) is a 7812.
- (a) No voltage between points 1 and 6.
 - (b) 110 V rms between points 1 and 6 but no voltage between points 2 and 5.
 - (c) 110 V rms between points 1 and 6 but 11.5 V rms between points 2 and 5.
 - (d) A pulsating full-wave rectified voltage with a peak of 19 V between point 3 and ground.
 - (e) Excessive 120 Hz ripple voltage between point 3 and ground.
 - (f) Ripple voltage has a frequency of 60 Hz between point 3 and ground.
 - (g) 17 V dc with 120 Hz ripple at point 3 but no dc voltage at point 4.

 


FIGURE 2–86

- 31. Draw the schematic for the circuit board in Figure 2–87 and determine what the correct output voltages should be.
- 32. The ac input of the circuit board in Figure 2–87 is connected to the secondary of a transformer with a turns ratio of 1 that is operating from the 110 V ac source. When you measure the output voltages, both are zero. What do you think has failed, and what is the reason for this failure?

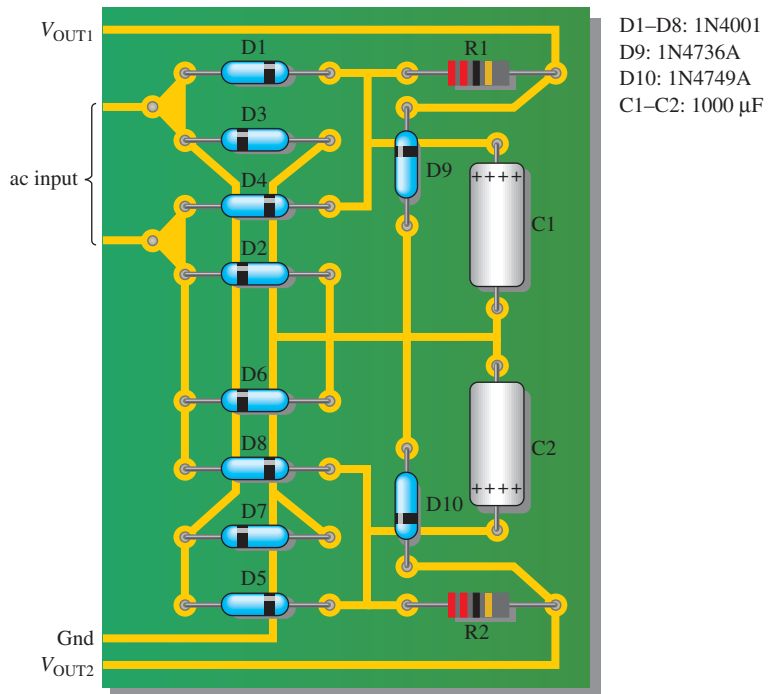


FIGURE 2-87

33. Select a transformer turns ratio that will provide the proper secondary voltage compatible with the circuit board in Figure 2-90.
34. In Figure 2-90, V_{OUT2} is zero and V_{OUT1} is correct. What are possible reasons for this?

MULTISIM



MULTISIM TROUBLESHOOTING PROBLEMS

35. Open file P02-35 and determine the fault.
36. Open file P02-36 and determine the fault.
37. Open file P02-37 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 2-1

1. Conduction band; valence band
2. An electron is thermally raised to the conduction band leaving a vacancy (hole) in the valence band.
3. The gap between the valence band and the conduction band is narrower in a semiconductor than in an insulator.

SECTION 2-2

1. By the addition of pentavalent impurities into the semiconductive material
2. By the addition of trivalent impurities into the semiconductive material
3. The boundary between p and n materials
4. 0.7 V

SECTION 2-3

1. Forward, reverse
2. Forward

- Reverse
- A rapid buildup of current when sufficient reverse bias is applied to the diode

SECTION 2-4

- Forward-bias and reverse-bias
- The reverse-breakdown region
- As a switch
- The barrier potential and the forward (bulk) resistance

SECTION 2-5

- Bridge
- Less
- The peak of the negative alteration
- 50% (with no filter)

SECTION 2-6

- The charging and discharging of the capacitor
- Increases ripple
- Much better ripple rejection, line and load regulation, thermal protection
- Line regulation:* Constant output voltage for varying input voltage
Load regulation: Constant output voltage for varying load current

SECTION 2-7

- Limiters clip off or remove portions of a waveform. Clampers insert a dc level.
- Reversing the diode causes the limiter to clip the other side of the waveform.
- The bias voltage must be $5\text{ V} - 0.7\text{ V} = 4.3\text{ V}$.
- The capacitor acts as a battery.

SECTION 2-8

- In breakdown
- The maximum current, above which the diode may be damaged
- It is a variable capacitor.
- The diode capacitance decreases.
- Gallium arsenide, gallium arsenide phosphide, gallium phosphide
- Dark current

SECTION 2-9

- The three rating categories on a diode data sheet are maximum ratings, electrical characteristics, and mechanical data.
- V_F is the maximum instantaneous forward voltage drop, I_R is reverse current, and I_O is peak average forward current.
- I_{FSM} is maximum forward surge current, V_{RRM} is maximum reverse peak repetitive voltage, and V_{RSM} is maximum reverse peak nonrepetitive voltage.
- The 1N4720 has an $I_O = 3.0\text{ A}$, $I_{FSM} = 300\text{ A}$, and $V_{RRM} = 100\text{ V}$.

SECTION 2-10

- The output would not change as the potentiometer was varied; it would be slightly more than 1.25 V.
- Open diode
- The filter capacitor

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 2-1 2.3 V, 3.0 V
2-2 320 V
2-3 $39.8 \mu\text{V}$
2-4 3.7%
2-5 The peak voltage drops to 8.7 V and -0.7 V.
2-6 The output is clipped at +10.7 V and -10.7 V.
2-7 The output would be a sinusoidal wave that goes from approximately -0.7 V to +47.3 V.
2-8 8Ω
2-9 6.8 V and 28.9 V
2-10 612 kHz to 1.94 MHz

ANSWERS TO SELF-TEST

1. (d) 2. (c) 3. (b) 4. (a) 5. (b) 6. (d) 7. (c) 8. (d)
9. (a) 10. (d) 11. (b) 12. (c) 13. (b) 14. (d) 15. (a) 16. (c)
17. (a) 18. (a) 19. (c) 20. (a) 21. (c) 22. (d) 23. (b) 24. (a)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. decrease 2. not change 3. increase 4. not change
5. increase 6. not change 7. increase 8. not change
9. increase 10. increase

CHAPTER 3

BIPOLAR JUNCTION TRANSISTORS (BJTs)

OUTLINE

- 3-1 Structure of Bipolar Junction Transistors
- 3-2 BJT Bias Circuits
- 3-3 Data Sheet Parameters and AC Considerations
- 3-4 Common-Emitter Amplifiers
- 3-5 Common-Collector Amplifiers
- 3-6 Common-Base Amplifiers
- 3-7 The Bipolar Transistor as a Switch
- 3-8 Transistor Packages and Terminal Identification
- 3-9 Troubleshooting

OBJECTIVES

- Describe the basic construction and operation of bipolar junction transistors (BJTs)
- Explain the operation of the four basic BJT bias circuits
- Discuss transistor parameters and characteristics and use them to analyze a transistor circuit
- Understand and analyze the operation of common-emitter amplifiers
- Understand and analyze the operation of common-collector amplifiers
- Understand and analyze the operation of common-base amplifiers

- Explain how a transistor can be used as a switch
- Identify various types of transistor package configurations
- Troubleshoot various faults in transistor circuits

KEY TERMS

Bipolar junction transistor (BJT)

Emitter

Base

Collector

dc beta (β_{DC})

Cutoff

Saturation

Negative feedback

ac beta (β_{AC})

Common-emitter (CE)

Common-collector (CC)

Common-base (CB)

INTRODUCTION

Two basic types of **transistors** are the bipolar junction transistor (BJT) and the field-effect transistor (FET). In this chapter, you will be introduced to the first of these types—the bipolar junction transistor. The chapter begins with a discussion of dc operation and bias circuits. You will see how these various bias circuits operate and how basic types of discrete amplifiers work in linear and switching applications. You will also learn to read manufacturer's data sheets.

VISIT THE WEBSITE

Study aids for this chapter are available at

<http://pearsonhighered.com/floyd>

3-1 STRUCTURE OF BIPOLAR JUNCTION TRANSISTORS

The basic structure of the bipolar junction transistor (BJT) determines its operating characteristics. In this section, you will see how semiconductive materials form a BJT, and you will learn the standard transistor symbols. You will see the application of a load line to a basic transistor circuit for setting up proper dc currents and voltages (bias) in a transistor circuit.

After completing this section, you should be able to

- Describe the basic construction and operation of bipolar junction transistors (BJTs)
- Distinguish between *npn* and *pnp* transistors
- Define BJT currents and explain how they are related
- Interpret the characteristic curves for a BJT
- Explain how a dc load line is constructed for a transistor circuit
- Define the terms *cutoff* and *saturation*

The **bipolar junction transistor (BJT)** is constructed with three doped semiconductor regions called **emitter**, **base**, and **collector**. These three regions are separated by two *pn* junctions. The two types of bipolar transistors are shown in Figure 3-1. One type consists of two *n* regions separated by a thin *p* region (*npn*), and the other type consists of two *p* regions separated by a thin *n* region (*pnp*). Both types are widely used; however, because the *npn* type is more prevalent, it will be used for most of the discussion which follows.


 


FIGURE 3-1 Construction of bipolar junction transistors.

The *pn* junction joining the base region and the emitter region is called the *base-emitter junction*. The *pn* junction joining the base region and the collector region is called the *base-collector junction*, as indicated in Figure 3-1(b). These junctions act just like the diode junctions discussed in Chapter 2 and are frequently referred to as the base-emitter diode and the base-collector diode. Each region is connected to a wire lead, labeled E, B, and C for emitter, base, and collector, respectively. Although the emitter and collector regions are made from the same type of material, the doping level and other characteristics are different.


Figure 3-2 shows the schematic symbols for the *npn* and *pnp* bipolar transistors. (Note that the arrow on an *npn* transistor is not pointing in.) The term **bipolar** refers to the use of both holes and electrons as carriers in the transistor structure.

FIGURE 3-2 Standard bipolar junction transistor symbols.

 

All industries are trying to lessen their environmental impact. In the semiconductor manufacturing industry one of the major concerns is the use of heavy metals, especially lead (Pb). Many companies are now producing Pb-free components. There are two primary requirements for a semiconductor device to gain a Pb-free designation. First, since lead-free solder has a higher melting temperature, Pb-free components must be able to withstand peak temperatures of 260°C. Second, a Pb-free designation requires that lead levels must not exceed 1,000 parts per million (ppm). Other heavy metals like mercury, cadmium, and chromium must also not exceed 1,000 ppm.

SYSTEM NOTE

 

Transistor Operation

In order for the transistor to operate properly, the two pn junctions must be supplied with external dc bias voltages to set the proper operating conditions. Figure 3-3 shows the proper bias arrangement for both npn and pnp transistors. In both cases, the base-emitter (BE) junction is forward-biased and the base-collector (BC) junction is reverse-biased. This is called *forward-reverse bias*. Both npn and pnp transistors normally use this forward-reverse bias, but the bias voltage polarities and the current directions are reversed between the two types.

 


FIGURE 3-3 Forward-reverse bias of a bipolar junction transistor.


To illustrate transistor action, let's examine what happens inside an npn transistor when the junctions are forward-reverse biased. (The same concepts can be applied to a pnp transistor by reversing the polarities.) The forward bias from base to emitter narrows the BE depletion region, and the reverse bias from base to collector widens the BC depletion region, as depicted in Figure 3-4. The heavily doped n -type emitter region is teeming with conduction-band (free) electrons that easily diffuse through the forward-biased BE junction into the p -type base region, just as in a forward-biased diode.

The base region is lightly doped and very narrow so that it has a very limited number of holes. Thus, only a small percentage of all the electrons flowing through the BE junction can combine with the available holes in the base. These relatively few recombined electrons flow out of the base lead as valence electrons, forming the small base current, as shown in Figure 3-4.

Most of the electrons flowing from the emitter into the narrow lightly doped base region do not recombine but diffuse into the BC depletion region. Once in the region, they are pulled through the reverse-biased BC junction by the electric field set up by the force of attraction between the positive and negative ions. Actually, you can think of the electrons as being pulled across the reverse-biased BC junction by the attraction of the collector supply voltage. The electrons now move through the collector region, out through the collector lead, and into the positive terminal of the external dc source, thereby forming the collector current, as shown. The amount of collector current depends directly on the amount of base current and is essentially independent of the dc collector voltage.

The bottom line is this: *A small base current can control a larger collector current.* Because the controlling element is base current and it controls a larger collector current, the bipolar transistor is essentially a current amplifier. This concept of a small control element for a large current is analogous to deForest's control grid mentioned in Section 1-1.

FIGURE 3-4 BJT operation showing electron flow.

 

Transistor Currents

Kirchhoff's current law (KCL) says the total current entering a junction must be equal to the total current leaving that junction. Applying this law to both the *nnp* and the *npn* transistors shows that the emitter current (I_E) is the sum of the collector current (I_C) and base current (I_B), expressed as follows:

$$I_E = I_C + I_B \quad (3-1)$$

The base current, I_B , is very small compared to I_E or I_C , which leads to the approximation $I_E \cong I_C$, a useful assumption for analyzing transistor circuits. Examples of an *nnp* and a *npn* small-signal transistor with representative currents are shown on the meters in Figures 3-5(a) and 3-5(b), respectively. Notice the polarity of the ammeters and supply voltages are reversed between the *nnp* and the *npn* transistors. The capital-letter subscripts indicate dc values.

DC Beta (β_{DC})

When a transistor is operated within certain limits, the collector current is proportional to the base current. The **dc beta** (β_{DC}), the current gain of a transistor, is the ratio of the dc collector current to the dc base current.

$$\beta_{DC} = \frac{I_C}{I_B} \quad (3-2)$$

The dc beta (β_{DC}) represents a constant of proportionality called the current gain and is usually designated as h_{FE} on transistor data sheets. It is valid as long as the transistor is operated within its linear range. For this case, the collector current is equal to β_{DC} multiplied by the base current. For the examples in Figure 3-5, $\beta_{DC} = 100$.

 


FIGURE 3-5 Currents in small-signal transistors.

The values for β_{DC} vary widely and depend on the type of transistor. They are typically from 20 (power transistors) to 200 (small-signal transistors). Even two transistors of the same type can have current gains that are quite different. Although the current gain is necessary for a transistor to be useful as an amplifier, good designs do not rely on a particular value of β_{DC} to operate properly.

Transistor Voltages

The three dc voltages for the biased transistor in Figure 3-6 are the emitter voltage (V_E), the collector voltage (V_C), and the base voltage (V_B). These single-subscript voltages mean that they are referenced to ground. The collector power supply voltage, V_{CC} , is shown with repeated subscript letters. Because the emitter is grounded, the collector voltage is equal to the dc supply voltage, V_{CC} , less the drop across R_C .

$$V_C = V_{CC} - I_C R_C$$

Kirchhoff's voltage law (KVL) says the sum of the voltage drops and rises around a closed path is zero. The previous equation is an application of this law.

As mentioned earlier, the base-emitter diode is forward-biased when the transistor is operating normally. The forward-biased base-emitter diode drop, V_{BE} , is approximately 0.7 V. This means that the base voltage is one diode drop larger than the emitter voltage. In equation form,

$$V_B = V_E + V_{BE} = V_E + 0.7 \text{ V}$$

In the configuration of Figure 3-6, the emitter is the reference terminal, so $V_E = 0 \text{ V}$ and $V_B = 0.7 \text{ V}$.

 


FIGURE 3-6 Bias voltages.

EXAMPLE 3-1

Determine I_B , I_C , I_E , V_B , and V_C in Figure 3-7, where β_{DC} is 50.

 


FIGURE 3-7

SOLUTION

Since V_E is ground, $V_B = 0.7 \text{ V}$. The drop across R_B is $V_{BB} - V_B$, so I_B is calculated as follows:

$$I_B = \frac{V_{BB} - V_B}{R_B} = \frac{3 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = \mathbf{0.23 \text{ mA}}$$

Now you can find I_C , I_E , and V_C .

$$I_C = \beta_{DC} I_B = 50(0.23 \text{ mA}) = \mathbf{11.5 \text{ mA}}$$

$$I_E = I_C + I_B = 11.5 \text{ mA} + 0.23 \text{ mA} = \mathbf{11.7 \text{ mA}}$$

$$V_C = V_{CC} - I_C R_C = 20 \text{ V} - (11.5 \text{ mA})(1.0 \text{ k}\Omega) = \mathbf{8.5 \text{ V}}$$

PRACTICE EXERCISE*

Determine I_B , I_C , I_E , V_{CE} , and V_{CB} in Figure 3–7 for the following values: $R_B = 22 \text{ k}\Omega$, $R_C = 220 \Omega$, $V_{BB} = 6 \text{ V}$, $V_{CC} = 9 \text{ V}$, and $\beta_{DC} = 90$.

* Answers are at the end of the chapter.

MULTISIM

Open file F03-07 found on the companion website. This simulation demonstrates the relationship between the various currents in both *npn* and *pn*p BJTs.

Characteristic Curves for a BJT

BASE-EMITTER CHARACTERISTIC The characteristic IV curve for the base-emitter junction is shown in Figure 3–8. As you can see, it is identical to that of an ordinary diode. You can model the base-emitter junction with any of the three diode models presented in Chapter 2. For most work, the offset model is sufficiently accurate. This means, if you are troubleshooting a bipolar transistor circuit, you can look for 0.7 V across the base-emitter junction (as in a forward-biased diode) to determine if the transistor is conducting. If the voltage is zero, the transistor is not conducting; if it is much larger than 0.7 V, it is likely that the transistor has an open base-emitter junction.

 



FIGURE 3–8 Base-emitter characteristic.

COLLECTOR CHARACTERISTIC Recall that the collector current is proportional to the base current ($I_C = \beta_{DC} I_B$). If there is no base current, the collector current is zero. In order to plot the collector characteristic, a base current must be selected and held constant. A circuit such as that in Figure 3–9(a) can be used to generate a set of collector IV curves to show how I_C varies with V_{CE} for a given base current. These curves are called the **collector characteristic curves**.


Notice in the circuit diagram that both dc supply voltages, V_{BB} and V_{CC} , are adjustable. If V_{BB} is set to produce a specific value of I_B and V_{CC} is zero, then $I_C = 0$ and $V_{CE} = 0$. Now, as V_{CC} is gradually increased, V_{CE} will increase and so will I_C , as indicated on the color-shaded portion of the curve between points *A* and *B* in Figure 3–9(b).

When V_{CE} reaches $\approx 0.7 \text{ V}$, the base-collector junction becomes reverse-biased and I_C reaches its full value determined by the relationship $I_C = \beta_{DC} I_B$. Ideally, I_C levels off to an almost constant value as V_{CE} continues to increase. This action appears to the right of point *B* on the curve. In practice, I_C increases slightly as V_{CE} increases due to the widening of the base-collector depletion region, which results in fewer holes for recombination in the base region. The steepness of this rise is determined by a parameter called the *forward Early voltage*, named after J. M. Early.


By setting I_B to other constant values, you can produce additional I_C versus V_{CE} curves, as shown in Figure 3–9(c). These curves constitute a “family” of collector curves for a given transistor. A family of curves allows you to visualize the complex situation when three variables interact. By holding one of them (I_B) constant, you can see the relation between the other two (I_C versus V_{CE}).

 

(a) Circuit

 

 (b) I_C versus V_{CE} curve for one value of I_B



(c) Family of I_C versus V_{CE} curves for several values of I_B ($I_{B1} < I_{B2} < I_{B3}$, etc.)

FIGURE 3-9 Collector characteristic curves.

EXAMPLE 3-2

Sketch the family of collector curves for the circuit in Figure 3-10 for $I_B = 5 \mu A$ to $25 \mu A$ in $5 \mu A$ increments. Assume that $\beta_{DC} = 100$.

 


FIGURE 3-10

SOLUTION

Table 3-1 shows the calculations of I_C using the relationship $I_C = \beta_{DC} I_B$. The resulting curves are plotted in Figure 3-11. To account for the forward Early voltage, the resulting curves are shown with an arbitrary upward slope as previously discussed.

TABLE 3-1

I_B	I_C
$5 \mu\text{A}$	0.5 mA
$10 \mu\text{A}$	1.0 mA
$15 \mu\text{A}$	1.5 mA
$20 \mu\text{A}$	2.0 mA
$25 \mu\text{A}$	2.5 mA

 


FIGURE 3-11

PRACTICE EXERCISE

Ideally, where would the curve for $I_B = 0$ appear on the graph?

Cutoff and Saturation

When $I_B = 0$, the transistor is in **cutoff** and there is essentially no collector current except for a very tiny amount of collector leakage current, I_{CEO} , which can usually be neglected. In cutoff, both the base-emitter and the base-collector junctions are reverse-biased. When you are troubleshooting a transistor that is in cutoff, you can assume the collector current is zero; therefore, there is no voltage drop across the collector resistor. As a result, the collector-to-emitter voltage will be very nearly equal to the supply voltage.

Now let's consider the opposite situation. When the base-emitter junction in Figure 3-9 becomes forward-biased and the base current is increased, the collector current also increases and V_{CE} decreases as a result of more voltage drop across R_C . According to Kirchhoff's voltage law, if the voltage across R_C increases, the drop across the transistor must decrease. Ideally, when the base current is high enough, the entire V_{CC} is dropped across R_C with no voltage between the collector and emitter. This condition is known as **saturation**. Saturation occurs when the supply voltage, V_{CC} , is across the total resistance of the collector circuit, R_C . The saturation current for this particular configuration is given by Ohm's law.

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C}$$

Once the base current is high enough to produce saturation, further increases in base current have no effect on the collector current, and the relationship $I_C = \beta_{DC} I_B$ is no


longer valid. When V_{CE} reaches its saturation value, $V_{CE(sat)}$, which is ideally zero, the base-collector junction becomes forward-biased.

When you are troubleshooting transistor circuits, a quick check for cutoff or saturation provides useful information. Remember a transistor in cutoff has nearly the entire supply voltage between collector and emitter; a saturated transistor, in practice, has a very small voltage drop between collector and emitter (typically 0.1 V).

DC Load Line


Recall from Section 1-3 that a Thevenin circuit is drawn as a voltage source in series with a resistor. Consider the circuit in Figure 3-12(a). The collector voltage source, V_{CC} , and the collector resistor, R_C , form a Thevenin source; the transistor is the load. The minimum and maximum current that can be provided from this source are zero and V_{CC}/R_C . These are, of course, the cutoff and saturation values as previously defined. Note that the saturation and cutoff points depend only on the Thevenin circuit; the transistor does not affect these points. A straight line drawn between cutoff and saturation defines the dc load line for this circuit, as shown in Figure 3-12(b). This line represents all possible dc operating points for the circuit.

 The IV curve for any type of load can be added to the same plot as the dc load line to obtain a graphical picture of the circuit operation, as shown earlier in Section 1-3. Figure 3-12(c) shows a dc load line superimposed on a set of ideal collector characteristic curves.



(a) The collector circuit, shown in the blue box, is a Thevenin circuit. The transistor circuit, shown in the gray box, is the load.

 (b) DC load line for the Thevenin circuit in (a)



(c) Collector characteristic curves superimposed on the dc load line

FIGURE 3-12

Any value of I_C and the corresponding V_{CE} will fall on this line, as long as dc operation is maintained.

Now let's see how the dc load line and the characteristic curves for a transistor can be used to illustrate transistor operation. Assume you have a transistor with the characteristic curves shown in Figure 3–13(a) and you install it in the dc test circuit shown in Figure 3–13(b). A graphical solution can be used to find currents and voltages by drawing a dc load line. First, the cutoff point on the load line is determined. When the transistor is cut off, there is essentially no collector current. Thus, the collector-emitter voltage and current are

$$V_{CE(\text{cutoff})} = V_{CC} = 12 \text{ V}$$

and


$$I_{C(\text{cutoff})} = 0 \text{ mA}$$

Next, the saturation point on the load line is determined. When the transistor is saturated, V_{CE} is nearly zero. Therefore, V_{CC} is dropped across R_C . The saturation value of the collector current, $I_{C(\text{sat})}$, is found by applying Ohm's law to the collector resistor.


$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{12 \text{ V}}{2.0 \text{ k}\Omega} = 6.0 \text{ mA}$$

This value is the maximum value for I_C . It cannot possibly be increased without changing V_{CC} or R_C .

 
Next, the cutoff and saturation points are plotted on the same plot as the characteristic curves and a straight line, which is the load line, is drawn between them. This represents all possible operating points for the circuit. Figure 3–13(c) shows the load line and the characteristic curves for the transistor together on the same plot.




(a) Characteristic curves

 

(b) DC test circuit

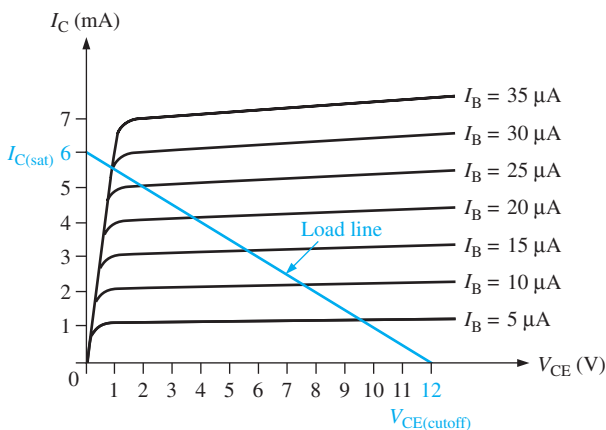

(c) Load line and characteristic curves

 

(d) Locating the Q-point

FIGURE 3–13

Q-Point

Before the actual collector current can be found, the value of the base current, I_B , needs to be established. Referring to the original circuit, it is apparent that the base power supply, V_{BB} , is across the series combination of the base resistor, R_B , and the forward-biased base-emitter junction. This means that the voltage across the base resistor is

$$V_{R_B} = V_{BB} - V_{BE} = 12 \text{ V} - 0.7 \text{ V} = 11.3 \text{ V}$$

By applying Ohm's law, you can find the base current.

$$I_B = \frac{V_{R_B}}{R_B} = \frac{11.3 \text{ V}}{1.0 \text{ M}\Omega} = 11.3 \mu\text{A}$$

The point at which the actual base current line intersects the load line is the quiescent or Q-point for the circuit. The Q-point is found on the graph by interpolating between the $10 \mu\text{A}$ and $15 \mu\text{A}$ base current lines. The coordinates of the Q-point are the values for I_C and V_{CE} at that point, as illustrated in Figure 3-13(d). Reading these values from the plot, you find the value of I_C to be approximately 2.6 mA and V_{CE} to be approximately 7.0 V.

The plot in Figure 3-13(d) completely describes the dc operating conditions for the amplifier circuit. When troubleshooting, you won't take the time to draw load lines; rather you will learn to apply the basic math for circuits to obtain an idea of what should be occurring with a given circuit. However, the load line provides a useful mental picture for describing the dc conditions for the transistor.

SECTION 3-1 CHECKUP*

1. What are the three BJT currents called?
2. Explain the difference between *saturation* and *cutoff*.
3. What is the definition of β_{DC} ?

* Answers are at the end of the chapter.

3-2 BJT BIAS CIRCUITS

In this section, methods for biasing a bipolar junction transistor are presented. Biasing is the application of the appropriate dc voltages to cause the transistor to operate properly. It can be accomplished with any of several basic circuits. The choice of biasing circuit depends largely on the application. You will learn about four biasing methods and see the advantages and disadvantages of each method.

After completing this section, you should be able to

- Explain the operation of the four basic BJT bias circuits
 - Describe a base bias circuit
 - Describe a collector-feedback bias circuit
 - Describe a voltage-divider bias circuit
 - Describe an emitter bias circuit

For linear amplifiers, the signal must swing in both the positive and negative directions. Transistors operate with current in one direction only. In order for a transistor to amplify an ac signal, the ac signal needs to be superimposed on a dc level that sets the operating

point. Bias circuits set the dc level at a point that allows the ac signal to vary in both the positive and negative directions without driving the transistor into saturation or cutoff.

Base Bias

The simplest biasing circuit is **base bias**. For the *npn* transistor, shown in Figure 3–14(a), a resistor (R_B) is connected between the base and supply voltage. Note that this is essentially the same circuit that was introduced in Figure 3–9(a) and used to plot the characteristic curve. The only difference is that the base and the collector power supplies have been combined into a single supply (referred to as V_{CC}). Although this bias method is simple, it is not a good choice for linear amplifiers for reasons that will be discussed.

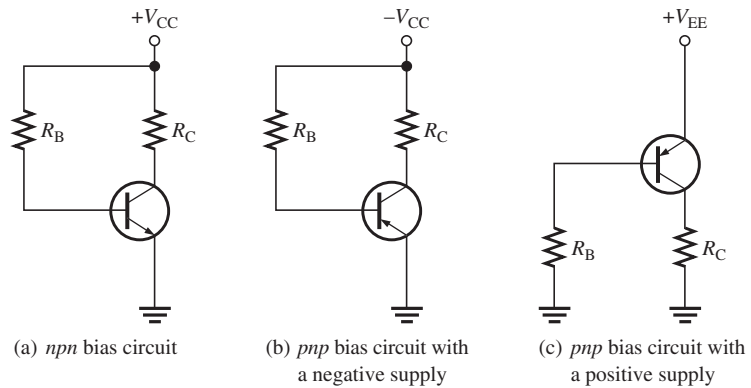


FIGURE 3–14 Base bias circuits.

The *npn* transistor can be set up using a negative supply as shown in Figure 3–14(b) or it can be run with a positive supply by applying the positive supply voltage to the emitter as shown in Figure 3–14(c). Either of these arrangements provide a path for base current through the base-emitter junction. In turn, this base current causes a collector current that is β_{DC} times larger than the base current (assuming linear operation). Thus, the collector current, for linear operation, is

$$I_C = \beta_{DC} I_B$$

The base resistor, R_B , has the base current, I_B , through it. From Ohm's law, you can substitute for I_B and obtain

$$I_C = \beta_{DC} \left(\frac{V_{R_B}}{R_B} \right)$$

$$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right) \quad (3-3)$$


This formula gives the collector current for base bias as long as the transistor is not in saturation. It is derived for the case with no emitter resistor, so this formula can only be applied to this configuration.

As mentioned previously, transistors can have very different current gains. Typical transistors of the same type can have β_{DC} values that vary by a factor of 3! In addition, current gain is a function of the temperature; as temperature increases, the base-emitter voltage decreases and β_{DC} increases. As a result, the collector current can vary widely between similar circuits with base bias. Circuits that depend on a particular β_{DC} cannot be expected to operate in a consistent manner. For this reason, base bias is rarely used for linear circuits.

Because it uses only a single resistor for bias, base bias is a good choice in switching applications, where the transistor is always operated in either saturation or cutoff. For switching amplifiers, Equation (3–3) does not apply.

 EXAMPLE 3-3

The manufacturer's specification for a 2N3904 transistor shows that β_{DC} has a range from 100 to 300 (given in Fig. 3-25). Assume a 2N3904 is used in the base-biased circuit shown in Figure 3-15. Compute the minimum and maximum collector current based on this specification. (Note that this is effectively the same circuit that was solved with load line analysis in Figure 3-13 except it now is shown with a single power supply.)



SOLUTION

The base-emitter junction is forward-biased, causing a 0.7 V drop. The voltage across R_B is

$$V_{R_B} = V_{CC} - V_{BE} = 12 \text{ V} - 0.7 \text{ V} = 11.3 \text{ V}$$

The base current can be found by applying Ohm's law to the base resistor.

$$I_B = \frac{V_{R_B}}{R_B} = \frac{11.3 \text{ V}}{1.0 \text{ M}\Omega} = 11.3 \mu\text{A}$$

With linear operation, the collector current is β_{DC} times larger than the base current. Therefore, the minimum collector current is

$$I_{C(\min)} = \beta_{DC} I_B = (100)(11.3 \mu\text{A}) = \mathbf{1.13 \text{ mA}}$$

The maximum collector current is

$$I_{C(\max)} = \beta_{DC} I_B = (300)(11.3 \mu\text{A}) = \mathbf{3.39 \text{ mA}}$$

Notice that a 300% change in β_{DC} caused a 300% change in collector current.

PRACTICE EXERCISE

If you measured 2.5 mA of collector current in the circuit of Figure 3-15, what is the β_{DC} for the transistor?

Collector-Feedback Bias

Another type of bias arrangement is the **collector-feedback bias** circuit shown in Figure 3-16 for an *nnp* transistor. (A *pnp* transistor can be operated identically except for a negative supply voltage.) The base resistor, R_B , is connected to the collector rather than to V_{CC} , as in the base bias arrangement discussed previously. The base resistor will be a smaller value than in base bias because the collector voltage is less than V_{CC} in normal operation.

Collector feedback uses an important idea in electronics called **negative feedback** to achieve stability. Negative feedback returns a portion of the output back to the input in a manner to cancel changes that may occur. The negative feedback connection provides a relatively stable Q-point as a result.

Let's see how it works. In Figure 3-16, the collector voltage provides the bias to the base-emitter junction. The negative feedback creates a compensating effect that tends to keep the Q-point stable. Assume the β_{DC} increases due to a temperature increase. This causes I_C to increase and, in turn, more voltage drops across R_C . With more voltage dropped across R_C , V_C will decrease which, in turn, means it will supply *less* bias current. Thus, the original increase in β_{DC} has been compensated for, in part, by a smaller bias current. This compensating action is what is meant by negative feedback. Other applications for negative feedback will be described later.

 


FIGURE 3-16 Collector-feedback bias.

The collector current for collector-feedback bias is derived from the application of Kirchhoff's voltage law (KVL). By writing a loop equation around the base circuit, the following equation for the collector current can be derived:

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}} \quad (3-4)$$

This equation is valid for either an *npn* or a *pnp* transistor (be careful of signs). Equation (3-4) is applied in the next example to show how the effect of a different β_{DC} is compensated for by feedback.

EXAMPLE 3-4

As you saw earlier, a 2N3904 transistor has a β_{DC} range from 100 to 300. Assume a 2N3904 is used in the collector-feedback biased circuit shown in Figure 3-17. Compute the minimum and maximum collector current based on this specification.

 


FIGURE 3-17

SOLUTION

Substitute the values given for $\beta_{DC} = 100$ into Equation (3-4).

$$I_{C(\min)} = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}} = \frac{12 \text{ V} - 0.7 \text{ V}}{2.0 \text{ k}\Omega + 150 \text{ k}\Omega/100} = 3.2 \text{ mA}$$

Repeat the calculation for $\beta_{DC} = 300$.

$$I_{C(\max)} = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}} = \frac{12 \text{ V} - 0.7 \text{ V}}{2.0 \text{ k}\Omega + 150 \text{ k}\Omega/300} = 4.5 \text{ mA}$$

Note that a 300% change in β_{DC} resulted in only a 40% change in collector current for this case, which is a considerable improvement over the base-bias case in Example 3-3.

PRACTICE EXERCISE

Compute the minimum and maximum value of V_{CE} for the range of β_{DC} given in the problem. Notice that $V_E = 0$; therefore, $V_{CE} = V_C$.

MULTISIM



Open file F03-17 found on the companion website. This simulation demonstrates how collector feedback limits the effects of a changing dc beta on collector current.

As illustrated by Example 3-4, collector-feedback bias offers greater stability than base bias with the same number of components. It still doesn't have the highest degree of stability required for many linear circuits. The highest stability for single supply operation is offered by voltage-divider bias.

Voltage-Divider Bias

As you have seen, the principal disadvantage to base bias is its dependency on β_{DC} . Collector-feedback bias offered greater stability than base bias, but an even higher degree of stability can be obtained with **voltage-divider bias**. Voltage-divider bias is the most widely used form of biasing because it uses only one supply voltage and produces bias that is essentially independent of β_{DC} . In fact, looking at the equations for voltage-divider bias reveals that neither β_{DC} nor any other transistor parameter is included. Essentially, good voltage-divider designs are independent of the transistor that is used.

The voltage-divider rule, one of the most useful rules from your basic dc/ac circuits course, allows you to compute the voltage across a series resistive branch in a circuit. Figure 3-18(a) illustrates a basic voltage divider. To find the output voltage, a ratio of the resistance to total resistance is set up and multiplied by the input voltage.

$$V_{\text{OUT}} = \left(\frac{R_2}{R_1 + R_2} \right) V_{\text{IN}}$$

When setting up the ratio for the voltage-divider rule, the resistor that the output is taken across (in this case, R_2) is the numerator and the sum of the resistances is the denominator.

When a load resistor is placed across the output of a voltage divider, as in Figure 3-18(b), the output voltage decreases because of the loading effect. *As long as the load resistor is large compared to the divider resistors, the loading effect is small and can be ignored.*

Voltage-divider bias is shown in Figure 3-19. In this configuration, two resistors, R_1 and R_2 , form a voltage divider that keeps the base voltage nearly the same for any load that requires a small current. This voltage forward-biases the base-emitter junction, resulting in a small base current. With voltage-divider bias, the transistor acts as a high resistance load on the divider. This will tend to make the base voltage slightly less than the unloaded value. In actual voltage-divider bias circuits, the effect is generally small, so the loading effects can be ignored. In any case, this loading effect can be minimized by the choice of R_1 and R_2 . As a rule of thumb, these resistors should have a current that is at least ten times larger than the base current to avoid variations in the base voltage when a transistor with a different β_{DC} is used. This is called *stiff bias* because the base voltage is relatively independent of the base current.

The steps in computing the parameters for a voltage-divider bias circuit are straightforward applications of the voltage-divider rule and Ohm's law. Based on the assumption of no significant loading effect, you can use the voltage-divider rule described earlier to compute the base voltage. The voltage-divider rule applied to Figure 3-19 is

$$V_{\text{B}} = \left(\frac{R_2}{R_1 + R_2} \right) V_{\text{CC}} \quad (3-5)$$

The emitter voltage is one diode drop less than the base voltage. (For *npn* transistors, it is one diode drop higher).

$$V_{\text{E}} = V_{\text{B}} - V_{\text{BE}}$$

$$V_{\text{E}} = V_{\text{B}} - 0.7 \text{ V} \quad (3-6)$$

With the emitter voltage known, the emitter current is found by Ohm's law.

$$I_{\text{E}} = \frac{V_{\text{E}}}{R_{\text{E}}}$$

The collector current is approximately the same as the emitter current.

$$I_{\text{C}} \cong I_{\text{E}}$$

The collector voltage can now be found. It is V_{CC} less the drop across the collector resistor, found by Ohm's law. Writing this as an equation,

$$V_{\text{C}} = V_{\text{CC}} - I_{\text{C}}R_{\text{C}} \quad (3-7)$$

To find the collector-emitter voltage, V_{CE} , subtract the emitter voltage, V_{E} , from the collector voltage, V_{C} .

$$V_{\text{CE}} = V_{\text{C}} - V_{\text{E}}$$

Example 3-5 illustrates this procedure for finding the dc parameters for a circuit.

 


FIGURE 3-18 Voltage dividers.

 
 


FIGURE 3-19 Voltage-divider bias.

EXAMPLE 3–5

Find V_B , V_E , I_E , I_C , and V_{CE} for the circuit in Figure 3–20.

FIGURE 3–20**SOLUTION**

Begin by finding the base voltage using the voltage-divider rule.

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{3.9 \text{ k}\Omega}{27 \text{ k}\Omega + 3.9 \text{ k}\Omega} \right) 18 \text{ V} = \mathbf{2.27 \text{ V}}$$

The emitter voltage is one diode drop less than the base voltage.

$$V_E = V_B - V_{BE} = 2.27 \text{ V} - 0.7 \text{ V} = \mathbf{1.57 \text{ V}}$$

Next, find the emitter current from Ohm's law.

$$I_E = \frac{V_E}{R_E} = \frac{1.57 \text{ V}}{470 \Omega} = \mathbf{3.34 \text{ mA}}$$

Using the approximation $I_C \cong I_E$,

$$I_C = \mathbf{3.34 \text{ mA}}$$

Now find the collector voltage.

$$V_C = V_{CC} - I_C R_C = 18 \text{ V} - (3.34 \text{ mA})(2.7 \text{ k}\Omega) = 8.98 \text{ V}$$

The collector-emitter voltage is

$$V_{CE} = V_C - V_E = 8.98 \text{ V} - 1.57 \text{ V} = \mathbf{7.41 \text{ V}}$$

PRACTICE EXERCISE

Find V_B , V_E , I_E , I_C , and V_{CE} for the circuit in Figure 3–20 if the power supply voltage was incorrectly set to +12 V.

Figure 3–21 shows two configurations for voltage-divider bias with a *pnp* transistor. As in the case of base bias, either negative or positive supply voltages can be used for bias. With a negative supply, shown in Figure 3–21(a), the voltage is applied to the collector. With a positive supply, shown in Figure 3–21(b), the voltage is applied to the emitter. The transistor is frequently drawn upside down to place the supply voltage on top; this means that the emitter resistor is also on top. The equations for *npn* transistors can be applied to *pnp* transistors, but you need to be careful of algebraic signs.

 


FIGURE 3-21 Voltage-divider bias for *pnp* transistors.

EXAMPLE 3-6

Find V_B , V_E , I_E , I_C , and V_{CE} for the *pnp* circuit in Figure 3-22.

 


FIGURE 3-22

SOLUTION

Begin by finding the base voltage using the voltage-divider rule.

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{4.7 \text{ k}\Omega}{27 \text{ k}\Omega + 4.7 \text{ k}\Omega} \right) (-12 \text{ V}) = -1.78 \text{ V}$$

The equation for V_E is the same one used for the *nnp* transistor but note the signs. The emitter voltage is one diode drop *greater* than the base voltage for a forward-biased *pnp* transistor.

$$V_E = V_B - V_{BE} = -1.78 - (-0.7 \text{ V}) = -1.08 \text{ V}$$

Now find the emitter current using Ohm's law.

$$I_E = \frac{V_E}{R_E} = \frac{-1.08 \text{ V}}{1.0 \text{ k}\Omega} = -1.08 \text{ mA}$$

Using the approximation $I_C \cong I_E$,

$$I_C = -1.08 \text{ mA}$$

Now find the collector voltage.

$$V_C = V_{CC} - I_C R_C = -12 \text{ V} - (-1.08 \text{ mA})(5.6 \text{ k}\Omega) = -5.96 \text{ V}$$

MULTISIM



Open file F03-22 found on the companion website. This simulation will be used to perform a dc analysis of a voltage-divider biased *pn*p circuit.

The collector-emitter voltage is

$$V_{CE} = V_C - V_E = -5.96 \text{ V} - (-1.08 \text{ V}) = -4.88 \text{ V}$$

Notice that V_{CE} is negative for a *pn*p circuit.

PRACTICE EXERCISE

Find V_B , V_E , I_E , I_C , and V_{CE} for the circuit in Figure 3–22 if R_E is changed to 1.2 k Ω .

Emitter Bias

Emitter bias is a very stable form of bias that uses both positive and negative power supplies and a single bias resistor that, in the usual configuration, puts the base voltage near ground potential. It is the type of bias used in most integrated circuit amplifiers.

Emitter bias circuits for *npn* and *pn*p configurations are shown in Figure 3–23. As in the other bias circuits, the key difference between the *npn* and *pn*p versions is that the polarity of the power supplies are opposite to each other.

For stable bias, the base resistor is selected to drop only a few tenths of a volt. For the *npn* case, the emitter voltage is approximately -1 V due to the small drop across R_B and the forward-bias drop of the base-emitter junction of 0.7 V . For the *pn*p version, the emitter voltage is approximately $+1 \text{ V}$. When troubleshooting, a quick check of the emitter voltage will reveal if the transistor is conducting and if the bias voltage is correct.

The emitter current is computed by applying Ohm's law to the emitter resistor. The approximation that $I_C \cong I_E$ is used to calculate the collector current and the collector voltage is again found by applying the following equation:

$$V_C = V_{CC} - I_C R_C$$


 


FIGURE 3–23 Emitter bias circuits.

EXAMPLE 3–7

Find V_E , I_E , I_C , and V_{CE} for the emitter bias circuit in Figure 3–24.

FIGURE 3–24

 

SOLUTION

Start with the approximation $V_E \cong -1 \text{ V}$. This implies the voltage across R_E is 11 V . Applying Ohm's law to the emitter resistor,

$$I_E = \frac{V_{R_E}}{R_E} = \frac{11 \text{ V}}{15 \text{ k}\Omega} = 0.73 \text{ mA}$$

The collector current is approximately equal to the emitter current.

$$I_C \cong 0.73 \text{ mA}$$

Now find the collector voltage.

$$V_C = V_{CC} - I_C R_C = 12 \text{ V} - (0.73 \text{ mA})(6.8 \text{ k}\Omega) = 7.0 \text{ V}$$

Find V_{CE} by subtracting V_E from V_C .

$$V_{CE} = V_C - V_E = 7.0 \text{ V} - (-1 \text{ V}) = 8.0 \text{ V}$$

PRACTICE EXERCISE

Find V_E if the base of the transistor in Figure 3-24 were shorted to ground.

SYSTEM EXAMPLE 3-1

TEMPERATURE CONTROL SYSTEM

The purpose of the temperature control system in Figure SE3-1 is to keep the temperature of the liquid in the tank at a specified value. The temperature in the tank is monitored by a thermistor sensor whose resistance changes with temperature. The resistance of the thermistor is ultimately converted to a voltage that is proportional to the resistance. This voltage is then applied to a valve interface circuit that adjusts the valve to control the fuel flow to the burner. If the tank temperature exceeds the specified value, the fuel to the burner is reduced, causing a decrease in the temperature. If the tank temperature drops below the specified value, the fuel to the burner is increased, causing an increase in the temperature.


 
 


FIGURE SE3-1 Temperature-control system.

 The voltage-divider biased amplifier, shown in Figure SE3-2(a), is used for the temperature-to-voltage conversion circuit. The thermistor is used as one of the resistors in the voltage-divider bias. The thermistor has a positive temperature coefficient so its resistance



(a) Circuit


TEMPERATURE, °C	THERMISTOR RESISTANCE, kΩ
60	1.256
65	1.481
70	1.753
75	2.084
80	2.490

(b) Temperature characteristic of the thermistor for the specified range


FIGURE SE3-2 Temperature-to-voltage conversion circuit.

is directly proportional to the temperature of the liquid in the tank. The transistor base voltage changes proportionally to the change in thermistor resistance. The transistor output voltage is inversely proportional to the base voltage, so as the temperature goes down, the output voltage increases and allows more fuel to the burner.

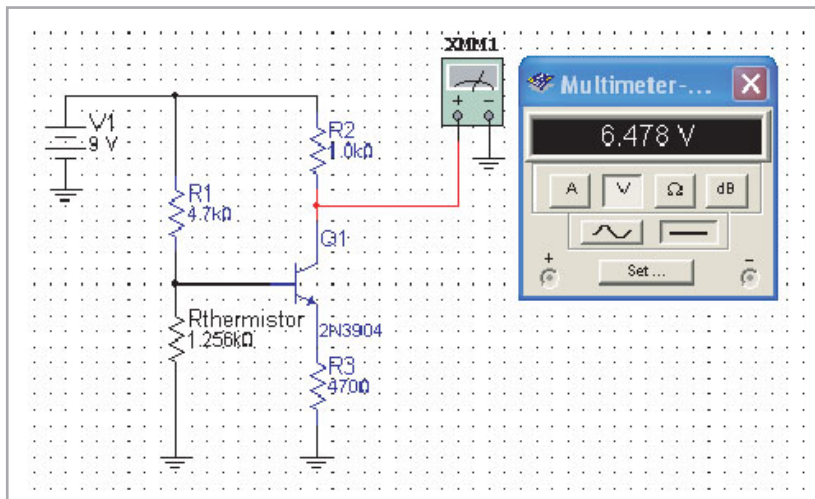For illustration, assume the temperature is to be maintained at $70^\circ \pm 5^\circ\text{C}$. The table in Figure SE3-2(b) shows the how the thermistor resistance changes for a given temperature range. A Multisim simulation in Figure SE3-3 shows the operation of the temperature-to-voltage conversion circuit.



(a) Circuit output voltage at 60°C

 

$R_{\text{therm}} = 1.481\text{ k}\Omega$

$R_{\text{therm}} = 1.753\text{ k}\Omega$

$R_{\text{therm}} = 2.084\text{ k}\Omega$

$R_{\text{therm}} = 2.490\text{ k}\Omega$

(b) Circuit output voltages at 65° , 70° , 75° , and 80°

FIGURE SE3-3 Operation of the temperature-to-voltage conversion circuit.

SECTION 3-2 CHECKUP

1. Name the four types of bias circuits for BJTs.
2. What are the steps for finding V_{CE} with stiff voltage-divider bias?
3. What dc emitter voltage do you expect to find with emitter bias on a *pnp* transistor?

3-3 DATA SHEET PARAMETERS AND AC CONSIDERATIONS

The backbone of analog electronics is the linear amplifier, a circuit that produces a larger signal that is a replica of a smaller one. In the last section, you saw how bias is used to provide the necessary dc conditions for the transistor to operate. In this section, we look at factors that affect the ac signal.

After completing this section, you should be able to

- Discuss transistor parameters and use them to analyze a transistor circuit
- Compare the notation used for dc and ac quantities
- Discuss principal characteristics given on manufacturer's data sheets for BJTs
- Explain the function of coupling and bypass capacitors
- Explain how an amplifier produces voltage gain

DC and AC Quantities

In the first part of this chapter, dc values were used to set up the operating conditions for transistors. These dc quantities of voltage and current used the standard italic capital letters with nonitalic capital-letter subscripts such as V_E , I_E , I_C , and V_{CE} . Lowercase italic subscripts are used to show ac quantities of rms, peak, and peak-to-peak voltages and currents such as V_e , I_e , I_c , and V_{ce} . Instantaneous quantities are indicated with both lowercase italic letters and subscripts such as v_e , i_e , i_c , and v_{ce} .

In addition to currents and voltages, resistances often have different values from an ac viewpoint compared to a dc viewpoint (see Section 1-1 for a review of dc versus ac resistance). Lowercase italic subscripts are used to identify ac resistance values. For example, R_C represents a dc collector resistance and R_c represents an ac collector resistance. You will see the need for this distinction as we discuss amplifiers. Internal resistances that are part of the transistor's equivalent circuit are written as lowercase italic letters (sometimes with a prime) and subscripts. For example, r'_e represents the internal ac emitter resistance and $R_{in(tot)}$ represents the total ac resistance that an amplifier presents to a signal source.

One parameter that is different for dc and ac circuits is β . The dc beta (β_{DC}) for a circuit was previously defined as the ratio of the collector current, I_C , to the base current, I_B . The **ac beta** (β_{ac}) is defined as a small *change* in collector current divided by a corresponding *change* in base current. A changing quantity is written using ac notation and is a ratio of the collector current, I_c , to the base current, I_b (note the lowercase italic subscripts). On manufacturer's data sheets, β_{ac} is usually shown as h_{fe} . In equation form,

$$\beta_{ac} = \frac{I_c}{I_b} \quad (3-8)$$

The difference between β_{ac} and β_{DC} for a given transistor is normally quite small and is due to small nonlinearities in the characteristic curves. For almost all designs, these differences are not important but should be understood when reading data sheets.

Manufacturer’s Data Sheet


Figure 3–25 shows a partial data sheet for the 2N3903 and 2N3904 *npn* transistors. Notice that the maximum collector-emitter voltage (V_{CEO}) is 40 V. The “O” in the subscript indicates that the voltage is measured from collector (C) to emitter (E) with the base open (O). In this textbook, we use $V_{CE(max)}$ for clarity. Also notice that the maximum collector current is 200 mA.

Maximum Ratings

Rating	Symbol	Value	Unit
Collector-Emitter voltage	V_{CEO}	40	V dc
Collector-Base voltage	V_{CBO}	60	V dc
Emitter-Base voltage	V_{EBO}	6.0	V dc
Collector current — continuous	I_C	200	mA dc
Total device dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Total device dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5 12	Watts mW/°C
Operating and storage junction Temperature range	T_J, T_{stg}	-55 to +150	°C

Thermal Characteristics

Characteristic	Symbol	Max	Unit
Thermal resistance, junction to case	$R_{\theta JC}$	83.3	°C/W
Thermal resistance, junction to ambient	$R_{\theta JA}$	200	°C/W

 

Electrical Characteristics ($T_A = 25^\circ\text{C}$ unless otherwise noted.)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

OFF Characteristics

Collector-Emitter breakdown voltage ($I_C = 1.0$ mA dc, $I_B = 0$)	$V_{(BR)CEO}$	40	—	V dc
Collector-Base breakdown voltage ($I_C = 10$ μA dc, $I_E = 0$)	$V_{(BR)CBO}$	60	—	V dc
Emitter-Base breakdown voltage ($I_E = 10$ μA dc, $I_C = 0$)	$V_{(BR)EBO}$	6.0	—	V dc
Base cutoff current ($V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	I_{BL}	—	50	nA dc
Collector cutoff current ($V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	I_{CEX}	—	50	nA dc

ON Characteristics

DC current gain ($I_C = 0.1$ mA dc, $V_{CE} = 1.0$ V dc)	h_{FE}	2N3903	20	—	—
		2N3904	40	—	
($I_C = 1.0$ mA dc, $V_{CE} = 1.0$ V dc)		2N3903	35	—	
		2N3904	70	—	
($I_C = 10$ mA dc, $V_{CE} = 1.0$ V dc)		2N3903	50	150	
		2N3904	100	300	
($I_C = 50$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903	30	—	—	
	2N3904	60	—		
($I_C = 100$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903	15	—	—	
	2N3904	30	—		
Collector-Emitter saturation voltage ($I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ($I_C = 50$ mA dc, $I_B = 5.0$ mA dc)	$V_{CE(sat)}$	—	0.2 0.3	V dc	
Base-Emitter saturation voltage ($I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ($I_C = 50$ mA dc, $I_B = 5.0$ mA dc)	$V_{BE(sat)}$	0.65	0.85 0.95	V dc	

FIGURE 3–25 Partial data sheet for 2N3903 and 2N3904 *npn* transistors.

On this data sheet, the dc current gain (β_{DC}) is given as h_{FE} . Minimum values of h_{FE} are listed on the data sheet under *ON Characteristics*. Note that the dc current gain is not really a constant but varies with the collector current. The current gain also changes with temperature as shown in Figure 3-26. The three variables, β_{DC} , I_C , and temperature, are plotted with a family of curves for a typical transistor. Keeping the junction temperature constant and increasing I_C causes β_{DC} to increase gradually to a maximum. A further increase in I_C beyond this maximum point causes β_{DC} to decrease. If I_C is held constant and the temperature is varied, β_{DC} changes directly with the temperature.

 


FIGURE 3-26 Variation of β_{DC} with I_C for several temperatures.

A transistor data sheet usually specifies β_{DC} at specific I_C values. Even at fixed values of I_C and temperature, β_{DC} varies from device to device for a given transistor. The β_{DC} specified at a certain value of I_C is usually the minimum value, $\beta_{DC(\min)}$, although the maximum and typical values are sometimes specified.


The dc power dissipated in any component is the product of the current and voltage. For a transistor, the product of V_{CE} and I_C gives the power dissipated by the transistor. Like any other electronic device, the transistor has limitations on its operation. These limitations are stated in the form of maximum ratings and are normally specified on the manufacturer's data sheet. Typically, maximum ratings are given for collector-to-emitter voltage (V_{CE}), collector-to-base voltage (V_{CB}), emitter-to-base voltage (V_{EB}), collector current (I_C), and power dissipation (P_D). The product of V_{CE} and I_C must not exceed the maximum power dissipation specification. Both V_{CE} and I_C cannot be at their individual maximum values at the same time. If V_{CE} is maximum, I_C can be calculated as

$$I_C = \frac{P_{D(\max)}}{V_{(CE)}}$$

If I_C is maximum, V_{CE} can be calculated as


$$V_{CE} = \frac{P_{D(\max)}}{I_C}$$

For a given transistor, a maximum power dissipation curve can be plotted on the collector characteristic curves, as shown in Figure 3-27(a). These values are tabulated in Figure 3-27(b). For this transistor, $P_{D(\max)}$ is 500 mW, $V_{CE(\max)}$ is 20 V, and $I_{C(\max)}$ is 50 mA. The curve shows that this particular transistor cannot be operated in the shaded portion of the graph. $I_{C(\max)}$ is the limiting rating between points A and B, $P_{D(\max)}$ is the limiting rating between points B and C, and $V_{CE(\max)}$ is the limiting rating between points C and D.

 
FIGURE 3-27 Maximum power dissipation curve.

EXAMPLE 3-8

The transistor in Figure 3-28 has the following maximum ratings: $P_{D(\max)} = 800$ mW, $V_{CE(\max)} = 15$ V, $I_{C(\max)} = 100$ mA, $V_{CB(\max)} = 20$ V, and $V_{EB(\max)} = 10$ V. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?

 
FIGURE 3-28

SOLUTION

First, find I_B so that you can determine I_C .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{22 \text{ k}\Omega} = 195 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (100)(195 \mu\text{A}) = 19.5 \text{ mA}$$

I_C is much less than $I_{C(\max)}$ and will not change with V_{CC} . It is determined only by I_B and β_{DC} .

The voltage drop across R_C is

$$V_{R_C} = I_C R_C = (19.5 \text{ mA})(1.0 \text{ k}\Omega) = 19.5 \text{ V}$$

Now you can determine the maximum value of V_{CC} when $V_{CE} = V_{CE(\max)} = 15$ V.

$$V_{R_C} = V_{CC} - V_{CE}$$

Thus,

$$V_{CC(\max)} = V_{CE(\max)} + V_{R_C} = 15 \text{ V} + 19.5 \text{ V} = \mathbf{34.5 \text{ V}}$$

V_{CC} can be increased to 34.5 V, under the existing conditions, before $V_{CE(max)}$ is exceeded. However, at this point it is not known whether or not $P_{D(max)}$ has been exceeded.

$$P_D = V_{CE(max)}I_C = (15\text{ V})(19.5\text{ mA}) = 293\text{ mW}$$

Since $P_{D(max)}$ is 800 mW, it is *not* exceeded when $V_{CC} = 34.5\text{ V}$. Thus, $V_{CE(max)} = 15\text{ V}$ is the limiting rating in this case. If the base current is removed causing the transistor to turn off, $V_{CE(max)}$ will be exceeded because the entire supply voltage, V_{CC} , will be dropped across the transistor.

PRACTICE EXERCISE

Assume the transistor in Figure 3-28 has the following maximum ratings: $P_{D(max)} = 500\text{ mW}$, $V_{CE(max)} = 25\text{ V}$, $I_{C(max)} = 200\text{ mA}$, $V_{CB(max)} = 30\text{ V}$, $V_{EB(max)} = 15\text{ V}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first?

AC and DC Equivalent Circuits

In Section 3-2, you solved the dc bias conditions necessary to set the operating conditions for the transistor. The first step in analyzing or troubleshooting any transistor amplifier is to find the dc conditions. After checking that the dc voltages are correct, the next step is to check ac signals. The equivalent ac circuit is quite different from the dc circuit. For example, a capacitor prevents dc from passing; thus, it appears as an open circuit to dc but looks like a short circuit to most ac signals. For this reason, you need to be able to look at the dc and ac equivalent circuits quite differently.

Recall from your dc/ac circuits course that the superposition principle allows you to find the voltage or current anywhere in a linear circuit due to a single voltage or current source acting alone. This is done by reducing all other sources to zero. To compute ac parameters, reduce the dc power supply to zero by mentally replacing it with a short and computing the ac parameters as if they were acting alone. Replacing the power supply with a short means that V_{CC} is actually at ground potential for the ac signal. This is called an *ac ground*. The concept of a ground point that is an ac signal ground but not a dc ground may be new to you. Just remember that an ac ground is a common reference point for the ac signal.

Coupling and Bypass Capacitors

A basic BJT amplifier is shown in Figure 3-29. The difference between this circuit and the one in Figure 3-19 is the addition of an ac signal source, three capacitors, and a load resistor. In addition, the emitter resistor is divided into two resistors.

The ac signal is brought into and out of the amplifier through series capacitors (C_1 and C_3) called **coupling capacitors**. As mentioned previously, a capacitor normally appears as a short to the ac signal and an open to dc. This means that coupling capacitors can pass the ac signal while simultaneously blocking the dc voltage. The input coupling capacitor, C_1 , passes the ac signal from the source to the base while isolating the source from the dc bias voltage. The output coupling capacitor, C_3 , passes the signal on to the load while isolating the load from the power supply voltage. Notice that the coupling capacitors are in series with the signal path.

Capacitor C_2 is different; it is connected in parallel with one of the emitter's resistors. This causes the ac signal to *bypass*

 


FIGURE 3-29 A basic transistor amplifier.

the emitter resistor; thus, it is called a **bypass capacitor**. The purpose of the bypass capacitor is to increase the gain of the amplifier for reasons you will learn later. Since the bypass capacitor is an ac short, *both* ends of the capacitor are at ac ground. Whenever one side of a capacitor is connected to ground, the other side is also a ground to the ac signal. Remember this if you are troubleshooting; you shouldn't find an ac signal on either side of a bypass capacitor. If you do, the capacitor may be open.

Amplification

The signal source, V_s , shown in Figure 3–29 causes variations in base current which, in turn, cause the much larger emitter and collector currents to vary about the Q-point in phase with the base current. However, when the collector current *increases*, the collector voltage *decreases* and viceversa. Thus, the sinusoidal collector-to-emitter voltage varies above and below its Q-point value 180° out of phase with the base voltage. A transistor always inverts the signal between the base and the collector. Amplification occurs because a small swing in base current produces a large variation in collector voltage.

SECTION 3–3 CHECKUP

1. Does the β_{DC} of a transistor increase or decrease with temperature?
2. Generally, what effect does an increase in I_C have on the β_{DC} ?
3. How can you find the dc power dissipated in a transistor?
4. What is the allowable collector current in a transistor with $P_{D(max)} = 320 \text{ mW}$ when $V_{CE} = 8 \text{ V}$?
5. Explain the difference between a coupling capacitor and a bypass capacitor.


3–4 COMMON-EMITTER AMPLIFIERS

The **common-emitter (CE)** is a type of BJT amplifier configuration in which the emitter is the reference for the input and output signals. In this section, a specific CE amplifier is introduced and used to illustrate certain ac parameters.


After completing this section, you should be able to

- Understand and analyze the operation of common-emitter amplifiers
- Draw the equivalent ac circuit for a CE amplifier
- Compute the voltage gain and the input and output resistances for a CE amplifier
- Discuss why the ac load line differs from the dc load line
- Draw the ac load line for a CE amplifier and find the Q-point

The **common-emitter (CE)** amplifier, the most widely used type of BJT amplifier, has the emitter as the reference terminal for the input and output signal. Figure 3–30(a) shows a CE amplifier that produces an amplified and inverted output signal at the load resistor. The input signal, V_{in} , is capacitively coupled to the base through C_1 , causing the base current to vary above and below its dc bias value. This variation in base current produces a corresponding variation in collector current. The variation in collector current is much larger than the variation in base current because of the current gain through the transistor. This produces a larger variation in the collector voltage which is out of phase with the base signal voltage. This variation in collector voltage is then capacitively coupled to the load and appears as the output voltage, V_{out} .

 

(a) Schematic

 

(b) DC load line

FIGURE 3-30 A basic common-emitter amplifier.

Now let's look closely at the amplifier in Figure 3-30(a) and examine its dc and ac parameters. The dc parameters were worked out in Example 3-5 (Figure 3-20) and the method is briefly reviewed here. Notice that the original 470 Ω emitter resistor is now composed of two series resistors, R_{E1} and R_{E2} , that add to the same 470 Ω . This has no effect on the dc currents or voltages, but because of the presence of the bypass capacitor, C_2 , the ac resistance of the emitter circuit is different.

There is voltage-divider bias, so first find the dc base voltage by applying the voltage-divider rule. The emitter voltage is 0.7 V less than the base voltage due to the base-emitter diode drop. Next, find the emitter current by applying Ohm's law to the emitter resistor. This calculates to 3.34 mA of emitter current, which is approximately the same as the collector current; therefore, the voltage drop across R_C can also be found by Ohm's law. The results from Example 3-5 showed that V_C is 8.98 V and that V_{CE} is 7.41 V. Recall that I_C and V_{CE} define the Q-point for the circuit. Because these are the values of I_C and V_{CE} at the Q-point, they are given special labels: I_{CQ} and V_{CEQ} , respectively.


A graphical picture of the parameters just reviewed may help you visualize the dc parameters. You can determine the load line by finding the saturation current and the collector-emitter cutoff voltage for the circuit. Recall that the saturation current is the current when the collector-to-emitter voltage is approximately zero. Thus,

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C + R_{E1} + R_{E2}} = \frac{18 \text{ V}}{2.7 \text{ k}\Omega + 200 \Omega + 270 \Omega} = 5.68 \text{ mA}$$

At cutoff, there is no current, so the entire supply voltage, V_{CC} , is across the collector to emitter. These two points, saturation and cutoff, allow you to construct the dc load line, as shown in Figure 3-30(b). All possible operating points, with no ac signal, are shown. The Q-point is located on the load line using the earlier calculation.

The AC Equivalent Circuit

Recall that the ac signal "sees" a different circuit than does the dc source for several reasons. If you apply the superposition theorem to the circuit in Figure 3-30(a) and show the capacitors as shorts, you can redraw the CE amplifier from the perspective of the ac signal. This is shown in Figure 3-31. The power supply has been replaced with an ac ground, shown in color. The capacitors have been replaced with shorts, and R_{E2} is eliminated because it is bypassed with C_2 .

 
FIGURE 3-31 AC equivalent circuit for Figure 3-30(a).

The ac equivalent circuit also shows an internal resistance in the base-emitter diode (using the offset-resistance model described in Section 2–4). This internal resistance, called r'_e , plays a role in the gain and input impedance of the amplifier so is generally included in the ac equivalent circuit. Because it is an ac resistance, it is sometimes called the **dynamic emitter resistance**. The value of this ac resistance is related to the dc emitter current as follows:

$$r'_e = \frac{25 \text{ mV}}{I_E} \quad (3-9)$$

The derivation of this formula is in Appendix A.

EXAMPLE 3-9

Find the dynamic emitter resistance, r'_e , for the circuit in Figure 3–30(a).

SOLUTION

The emitter current was found to be 3.34 mA (see Example 3–5). Substituting into Equation (3–9),

$$r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{3.34 \text{ mA}} = 7.5 \Omega$$

PRACTICE EXERCISE

Compute r'_e for a transistor with an emitter current of 100 μA .

Voltage Gain

The voltage gain, A_v , of the CE amplifier is the ratio of the output signal voltage to the input signal voltage, V_{out}/V_{in} . The output voltage, V_{out} , is measured at the collector and the input voltage, V_{in} , is measured at the base. Because the base-emitter junction is forward-biased, the signal voltage at the emitter is approximately equal to the signal voltage at the base. Thus, since $V_b = V_e$, the voltage gain is

$$A_v = -\frac{V_c}{V_e} = -\frac{I_c R_c}{I_e R_e}$$

Since $I_c \cong I_e$, the voltage gain reduces to the ratio of ac collector resistance to ac emitter resistance.

$$A_v \cong -\frac{R_c}{R_e} \quad (3-10)$$

The negative sign in the gain formula is added to indicate inversion, meaning the output signal is out of phase with the input signal. Note that the gain is written as a ratio of two ac resistances; you will see this idea again with the other amplifier configurations.

The gain formula is a useful and simple way to quickly determine what the voltage gain of a CE amplifier should be. When you're troubleshooting, you need to know what signal to expect; remember that the collector and emitter resistances used in calculating gain are the *total ac* resistance. The following summarizes these ideas:

- **The emitter ac circuit** In the emitter circuit, you need to include the internal base-emitter diode resistance (r'_e) and the fixed resistor that is not bypassed with a capacitor. The internal r'_e appears to be in series with the unbypassed emitter resistance in the ac emitter circuit. Incidentally, this unbypassed resistor, shown as R_{E1} in Figure 3–30(a),

serves an important role in determining the gain and keeping the gain stable. It also increases the input resistance of the amplifier as you will see later. Sometimes it is called a *swamping resistor* because it tends to “swamp” out the uncertain value of r'_e .

- **The collector ac circuit** From the vantage point of the collector, the collector resistor and the load resistor appear to be in parallel. Thus the ac resistance, R_c , of the collector is simply $R_C \parallel R_L$. An example should clarify this.

EXAMPLE 3-10

Find A_v for the circuit in Figure 3-30(a).

SOLUTION

The ac resistance in the emitter circuit, R_e , is composed of r'_e in series with the unbypassed R_{E1} . From Example 3-9, $r'_e = 7.5 \Omega$. Therefore,

$$R_e = r'_e + R_{E1} = 7.5 \Omega + 200 \Omega = 207.5 \Omega$$

Next, find the ac resistance as viewed from the transistor's collector.

$$R_c = R_C \parallel R_L = 2.7 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega = 1.71 \text{ k}\Omega$$

Substituting into Equation (3-10),

$$A_v \cong -\frac{R_c}{R_e} = -\frac{1.71 \text{ k}\Omega}{207.5 \Omega} = -8.3$$

Again, the negative sign is used to show that the amplifier inverts the signal.

PRACTICE EXERCISE

Assume the bypass capacitor in Figure 3-30(a) were open. What effect would this have on the gain?

MULTISIM



Open file F03-30 found on the companion website. This simulation will be used to examine how changes in load resistance affect amplifier voltage gain.

Input Resistance

The input resistance for an amplifier, $R_{in(tot)}$, (called the input impedance when capacitive or inductive effects are included) was introduced in Section 1-4 and Figure 1-19. It is an ac parameter that acts like a load in series with the source resistance. As long as the input resistance is high compared to the source resistance, most of the voltage will appear at the input and the loading effect is small. If the input resistance is small compared to the source resistance, most of the source voltage will drop across its own series resistance, leaving little for the amplifier to amplify.

One of the problems with the CE amplifier is that the input resistance is dependent on β_{ac} . As you have seen, this parameter is highly variable, so you can't calculate input resistance *exactly* for a given amplifier without knowing the β_{ac} . Despite this, you can minimize the effect of β_{ac} and increase the total input resistance by adding a swamping resistor to the emitter circuit. You can then obtain a reasonable estimate of the input resistance, which for most purposes will enable you to determine if a given amplifier is appropriate for the job at hand.

The input circuit for the CE amplifier in Figure 3-30(a) has been redrawn in Figure 3-32 to eliminate the output circuit. R_C is not part of the input circuit because of the reverse-biased base-collector junction. For the input ac signal, there are three parallel paths to ground. Looking in from the source, the three paths consist of R_1 , R_2 , and a path through the transistor's base-emitter circuit. It is these three parallel paths that comprise the input resistance of the circuit. We define this resistance as $R_{in(tot)}$ because it represents the total input resistance including the bias resistors. The base-emitter path, however, has β_{ac} dependency because of the transistor's current gain. The equivalent

 


FIGURE 3-32 Equivalent ac input circuit for the CE amplifier in Figure 3-30(a).

resistances, R_{E1} and r'_e , appear to be larger in the base circuit than in the emitter circuit because of this current gain. The resistors in the emitter circuit must be multiplied by β_{ac} to obtain their equivalent resistance in the base circuit. Therefore, the formula for calculating total input resistance is

$$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_{E1})] \quad (3-11)$$

EXAMPLE 3-11

Find $R_{in(tot)}$ for the circuit in Figure 3-30(a). Assume the β_{ac} is 120.

SOLUTION

The internal ac emitter resistance, r'_e , was found to be 7.5Ω in Example 3-9. Substituting into Equation (3-11),

$$\begin{aligned} R_{in(tot)} &= R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_{E1})] \\ &= 27 \text{ k}\Omega \parallel 3.9 \text{ k}\Omega \parallel [120(7.5 \Omega + 200 \Omega)] = \mathbf{3.0 \text{ k}\Omega} \end{aligned}$$

PRACTICE EXERCISE

Compute $R_{in(tot)}$ for the circuit in Figure 3-30(a) if β_{ac} is 200.

 


FIGURE 3-33 Equivalent ac output circuit for the CE amplifier.

Output Resistance

Recall that the model for an amplifier (Section 1-4) includes a Thevenin voltage source driving a series resistance or a Norton current source driving a parallel resistance. In both of these models, the resistance is the same. It is the equivalent output resistance of the amplifier.

To find the output resistance of any CE amplifier, look back from the output coupling capacitor as illustrated in Figure 3-33. The transistor appears as a current source in parallel with the collector resistor. This is the same as the equivalent Norton circuit in Figures 1-11 and 1-19(b).

Recall that the internal resistance of an ideal current source is infinite. With this in mind, you can see that the output resistance for the CE amplifier is simply the collector resistance, R_C .

The AC Load Line

For most troubleshooting work, it is useful to be able to quickly estimate a circuit's voltage and current values. Although technicians seldom use them in their normal work, load lines are a useful tool for understanding a transistor's operation and may offer insight into a circuit's limitations, such as clipping levels.

As discussed in Section 3-1, a dc load line can be drawn for a basic transistor circuit that consists of a series collector resistor, R_C , and a voltage source, V_{CC} . As shown in Figure 3-12(a), this series combination formed a Thevenin circuit that was represented graphically by a dc load line that crossed the y-axis at saturation. Recall that the load line in Figure 3-12(b) was independent of the transistor, which served as the load.

For ac, the Thevenin resistance is more complicated because of the presence of capacitors and an internal emitter resistance, r'_e . In high-frequency circuits, inductors may also play a role. Even though r'_e is internal to the transistor, it is considered part of the Thevenin resistance. Capacitive coupling and bypass capacitors are also present in most practical ac circuits. Capacitors are normally treated as shorts for the ac signal, meaning that the ac resistance (R_{ac}) of the collector-emitter circuit is reduced. Example 3-12 will illustrate this concept.

A dc and an ac load line are shown together in Figure 3-34 for a capacitively coupled amplifier. The Q-point is the same for both load lines because when the ac signal is reduced to zero, operation must still occur at the Q-point. Notice that the ac saturation current is

greater than the dc saturation current (because the ac resistance is smaller). In addition, the ac collector-emitter cutoff voltage is less than the dc collector-emitter cutoff voltage. The ac load line locates all possible operation points (collector current versus collector-emitter voltage) for the ac signal.

 


FIGURE 3-34 The dc and ac load lines.

The ac saturation and ac cutoff points can be computed for the ac load line. The ac load line crosses the y axis at $I_{c(sat)}$. This point is found by starting at the dc Q-point (I_{CQ}) and adding a term that includes the ac resistance of the collector-emitter circuit, R_{ac} , as shown on Figure 3-34. The equation for ac saturation is

$$I_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

The ac load line touches the x axis at $V_{ce(cutoff)}$. This point is also found by starting at the dc Q-point (V_{CEQ}) and adding a term that includes the ac resistance, R_{ac} . The equation for ac cutoff is

$$V_{ce(cutoff)} = V_{CEQ} + I_{CQ}R_{ac}$$

EXAMPLE 3-12

Draw the ac load line for the circuit in Figure 3-30(a).

SOLUTION

The dc load line for this circuit was shown in Figure 3-30(b) and is shown in Figure 3-35 for reference. The Q-point coordinates are $V_{CEQ} = 7.41$ V and $I_{CQ} = 3.34$ mA.

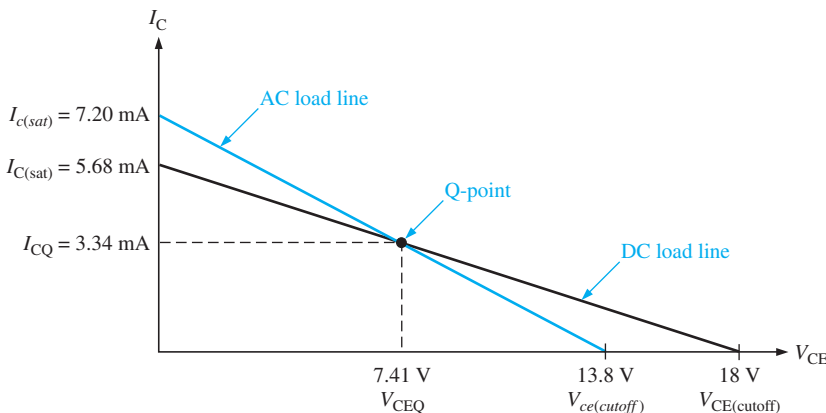


FIGURE 3-35 DC and ac load lines for the circuit in Figure 3-30(a).

Before locating the ac load line, it is necessary to find the ac resistance of the collector-emitter circuit. As you know, the emitter circuit has $r'_e + R_{E1}$ in series. The collector circuit has the parallel combination of $R_C \parallel R_L$. The total ac resistance of the collector-emitter circuit is

$$R_{ac} = r'_e + R_{E1} + (R_C \parallel R_L)$$

In Example 3–9, r'_e was found to be 7.5Ω . Substituting this value and the other fixed resistors into the previous equation results in

$$R_{ac} = 7.5 \Omega + 200 \Omega + (2.7 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega) = 1.92 \text{ k}\Omega$$

Now, find the ac collector saturation current.

$$I_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 3.34 \text{ mA} + \frac{7.41 \text{ V}}{1.92 \text{ k}\Omega} = 7.20 \text{ mA}$$

Next, find the ac collector-emitter cutoff voltage.

$$V_{ce(cutoff)} = V_{CEQ} + I_{CQ}R_{ac} = 7.41 \text{ V} + (3.34 \text{ mA})(1.92 \text{ k}\Omega) = 13.8 \text{ V}$$

Together, the ac collector saturation current, the Q-point, and the ac collector-emitter cutoff voltage establish a straight line. The ac load line can now be drawn and is shown in Figure 3–35.

PRACTICE EXERCISE

What happens to the Q-point and the ac load line if the load resistor is changed from $4.7 \text{ k}\Omega$ to $2.7 \text{ k}\Omega$?

 


FIGURE 3–36 AC load line superimposed on a typical transistor characteristic.

One interesting way of viewing the operation of an amplifier is to superimpose a set of characteristic curves for the transistor on the ac load line. This is shown in Figure 3–36 for a typical transistor that could be used with the CE amplifier from Figure 3–30(a). Lines projected from the peaks of the base current across to the I_C axis and lines from the ac load line down to the V_{CE} axis indicate the peak-to-peak variations of the collector current and collector-to-emitter voltage, as shown. For the transistor in this example, if an input signal causes the base current to vary from approximately $13 \mu\text{A}$ to $18 \mu\text{A}$, the output collector current will vary from approximately 2.9 mA to 3.9 mA . In addition, V_{CE} varies from approximately 6.3 V to 8.1 V for this same signal. The ac load line also gives a quick visual indication when the signal exceeds the linear range of the amplifier and shows the current and voltage range that a particular signal will encompass.

SECTION 3–4 CHECKUP

- Which terminal of a CE amplifier is the input terminal? Which is the output terminal?
- What is the advantage of a high input resistance in an amplifier?
- How is the gain determined in a CE amplifier?

3-5 COMMON-COLLECTOR AMPLIFIERS

The common-collector (CC) amplifier, commonly referred to as an emitter-follower, is the second of the three basic amplifier configurations. The input is applied to the base and the output is at the emitter. The CC amplifier provides current gain; the voltage gain is approximately 1. It is frequently used as a buffer or driver because of its high input resistance.

After completing this section, you should be able to

- Understand and analyze the operation of common-collector amplifiers
- Draw the equivalent ac circuit for a CC amplifier
- Explain why the voltage gain for a CC amplifier is approximately 1
- Compute the current gain and the input and output resistances for a CC amplifier
- Explain why a darlington pair has a very high β

Figure 3-37(a) shows a **common-collector (CC)** circuit with a voltage-divider bias. The collector is connected directly to the dc power supply, which is an ac ground. Notice that the input is applied to the base and the output is taken from the emitter. The output signal is in phase with the input signal. Looking from the input coupling capacitor to the base, the equivalent ac circuit has the bias resistors and the resistors in the emitter circuit as shown in Figure 3-37(b).

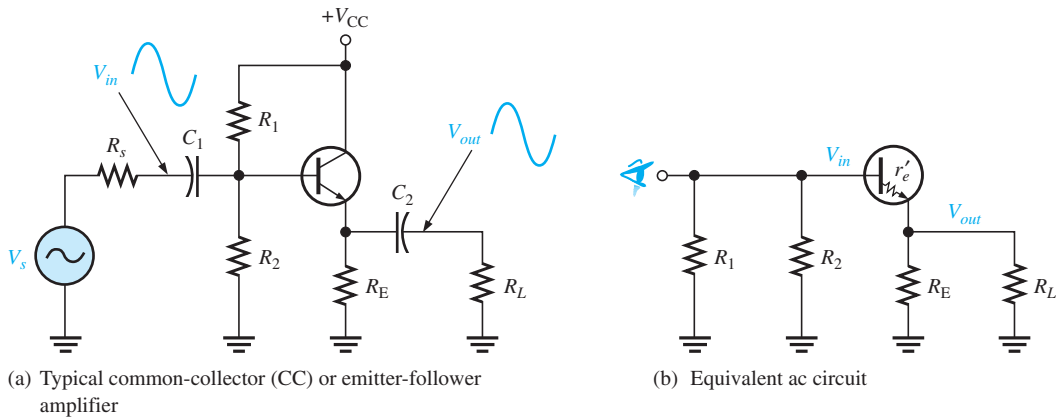


FIGURE 3-37

Voltage Gain

The ac circuit of Figure 3-37(b) can be simplified by combining the parallel emitter and load resistors into one equivalent resistor ($R_E \parallel R_L$), as shown in Figure 3-38. This circuit is used to analyze the voltage gain of the CC amplifier.

As in all linear amplifiers, the voltage gain in a CC amplifier is $A_v = V_{out}/V_{in}$. In the analysis of the gain, the bias resistors are not included because they do not directly affect the input signal (although they do cause a loading effect on the source). Notice in Figure 3-38 that the input voltage is across r'_e in series with $R_E \parallel R_L$. The output is across only $R_E \parallel R_L$. As long as r'_e is small compared to $R_E \parallel R_L$ (the usual case), you can ignore the small drop across r'_e . This means that the input and output voltages are nearly the same. Therefore,

$$A_v \cong 1$$

 


FIGURE 3-38 Equivalent ac input circuit for the CC amplifier.

$$(3-12)$$

Because of the small drop across r'_e , the actual gain is slightly less than 1. For practical circuits, this difference is not important. If you are checking the input and output of a

CC amplifier with an oscilloscope, expect to see nearly identical signals. Since the output voltage on the emitter follows the input voltage, the CC amplifier is often called an *emitter-follower*. There is no phase inversion in a CC amplifier.

You might wonder, if the CC amplifier has unity voltage gain, what is its value? The answer is that it has current gain. CC amplifiers are used when it is necessary to drive a low-impedance load, such as a speaker. In order to solve for current gain, you need to first analyze the input and output ac resistance.

Input Resistance

The emitter-follower is characterized by a high input resistance, which makes it a very useful circuit. Because of the high input resistance, the emitter-follower can be used as a buffer to minimize loading effects when one circuit is driving another. The derivation of the input resistance viewed from the base is similar to that for the CE amplifier. Looking in from the source, the CC amplifier has the same parallel paths as in the CE amplifier with voltage-divider bias, as shown in the equivalent circuit in Figure 3–38. In this case, however, there are no bypass capacitors in the emitter circuit. The total input resistance has a similar equation as in the CE case but with a different ac emitter resistance ($R_E \parallel R_L$).

$$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_E \parallel R_L)] \quad (3-13)$$

In most practical circuits, r'_e is much smaller than $R_E \parallel R_L$ and is ignored in the calculation. Further, the ac resistance of the transistor's emitter circuit is generally much larger than the paths through the bias resistors (because of β_{ac}). For a quick approximation of the total input resistance, you can just find the equivalent resistance of R_1 in parallel with R_2 .

 


FIGURE 3–39 Equivalent ac output circuit for the CC amplifier.

Output Resistance

The equivalent CC amplifier output circuit is shown in Figure 3–39 with the perspective of looking back from the output coupling capacitor. Resistor R_{base} represents the source and bias resistors in the base circuit. From the vantage point of the emitter circuit, these appear to be very small (their value is divided by β_{ac}). In practical circuits, they can be ignored; from the emitter's perspective, the base appears to be nearly at ac ground. This leaves only r'_e in parallel with R_E . Since R_E is much larger than r'_e , it also can be ignored.¹ For basic analysis purposes, the output resistance for the CC amplifier is quite simple—it's just r'_e !

Current Gain

The signal current gain for the emitter-follower is I_{load}/I_s where I_{load} is the ac current in the load resistor and I_s is the ac signal current from the source. The current I_s is calculated using Ohm's law as $V_{in}/R_{in(tot)}$. Since the voltage gain is approximately 1, the input voltage is also across the load. Thus, the load current is V_{in}/R_L . Taking the ratio of the currents results in the current gain.

$$A_i = \frac{I_{load}}{I_s} = \frac{V_{in}/R_L}{V_{in}/R_{in(tot)}}$$

$$A_i = \frac{R_{in(tot)}}{R_L} \quad (3-14)$$

This is a useful result and shows that the current gain, A_i , for the loaded CC amplifier is a ratio of the total input resistance to the load resistance. As noted with the earlier voltage gain equations, current gain can also be written as a ratio of resistances.

¹ Notice that the small equivalent series base resistor tends to be cancelled by the larger parallel emitter resistor, justifying the simplifying assumptions.

EXAMPLE 3-13

Determine the total input resistance, $R_{in(tot)}$, and the approximate voltage gain and current gain to the load of the emitter-follower in Figure 3-40. Assume the β_{ac} is 140.

 


FIGURE 3-40

SOLUTION

Although r'_e can be ignored for the calculation of the total input resistance, it is useful to review the method for finding r'_e . The value of r'_e is determined from I_E , so the first step is to find the dc conditions. The base voltage is found from the voltage-divider rule.

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{27 \text{ k}\Omega}{10 \text{ k}\Omega + 27 \text{ k}\Omega} \right) 12 \text{ V} = 8.76 \text{ V}$$

The emitter voltage is approximately $V_B - V_{BE} = 8.06 \text{ V}$. The emitter current is found from Ohm's law.

$$I_E = \frac{V_E}{R_E} = \frac{8.06 \text{ V}}{560 \Omega} = 14.4 \text{ mA}$$

The value of r'_e is

$$r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{14.4 \text{ mA}} = 1.7 \Omega$$

Since this value is small compared to the emitter and load resistors, it can be ignored.

The total input resistance is

$$\begin{aligned} R_{in(tot)} &= R_1 \parallel R_2 \parallel [\beta_{ac}(R_E \parallel R_L)] \\ &= 10 \text{ k}\Omega \parallel 27 \text{ k}\Omega \parallel [140(560 \Omega \parallel 560 \Omega)] = \mathbf{6.15 \text{ k}\Omega} \end{aligned}$$

Neglecting r'_e , the voltage gain is

$$A_v = \mathbf{1}$$

The current gain (to the load resistor) is

$$A_i = \frac{R_{in(tot)}}{R_L} = \frac{6.15 \text{ k}\Omega}{560 \Omega} = \mathbf{11}$$

PRACTICE EXERCISE

Assume R_1 and R_2 were both doubled in value. How would this change affect the voltage gain? How would the change affect the current gain?

MULTISIM

Open file F03-40 found on the companion website. This simulation will be used to examine how changes in load resistance affect CC amplifier current gain.

The Darlington Pair

 


FIGURE 3-41 Darlington pair.


One reason for using a CC amplifier is that it offers high input resistance. The input resistance of the CC amplifier is limited by the size of the bias resistors and the β_{ac} of the transistor. If β_{ac} could be made higher, larger-value bias resistors can still supply the necessary base current and the transistor's input resistance would look higher still.

One way to boost input resistance is to use a darlington pair, as shown in Figure 3-41. A darlington pair consists of two cascaded transistors with the collectors connected; the emitter of the first drives the base of the second. This configuration achieves β_{ac} multiplication. In effect, the darlington pair is a “super beta” transistor that looks like a single transistor with a beta equal to the product of the individual betas.

$$\beta_{ac} = \beta_{ac1}\beta_{ac2}$$

The main advantage of the darlington pair is that the circuit can achieve high input resistance and high current gain. Darlington pairs can be used in any circuit in which a very high β is desirable. Darlington transistors are available in a single package configuration that look like any other transistor. For example, the 2N6426 is a small-signal darlington transistor with a minimum β of 30,000.

SYSTEM EXAMPLE 3-2

 

A DARLINGTON FEEDBACK REGULATOR

Almost every type of electronic system requires one or more internal dc voltages in order to operate properly. The dc voltage should remain reasonably stable despite changes in input voltage (line regulation) and load demand (load regulation). In Chapter 2 you saw how a zener diode can be used as a crude voltage regulator. You were also introduced to the 78XX series IC voltage regulators, a much more sophisticated means of voltage regulation.

 


FIGURE SE3-4 A basic pass-transistor voltage regulator

A 78XX series regulator is a relatively complex circuit constructed on a single chip. It may contain over 20 BJTs (both NPN and PNP), two or more zener diodes, and a variety of resistors, capacitors, and conventional *pn*-junction diodes. Along with voltage regulation, the IC may also contain circuits for input over-voltage protection, thermal overload protection, and output short-circuit protection. However, at the heart of the IC voltage regulator is a relatively simple circuit built around a zener diode and one or more BJTs. This circuit is the pass-transistor regulator. The name comes from the fact that all load current must pass through the series transistor. The most basic form of a pass-transistor regulator is illustrated in Figure SE3-4.

The operation of this circuit is relatively simple. Resistor R_1 provides current limiting for the zener diode. The voltage at the base of Q_1 is held at a relatively fixed value by the zener. This means that the load voltage will equal the zener voltage less the Q_1 base-emitter voltage drop. By formula

$$V_L = V_Z - V_{BE}$$

If load voltage were to decrease, the value of V_{BE} increases, causing Q_1 conduction to increase. This increases load current, offsetting the decrease in load voltage. If load voltage increases, V_{BE} will decrease. Load current will decrease since transistor conduction decreases with a decrease in V_{BE} .

This basic circuit can be improved by using a Darlington pair in place of a single pass transistor, as illustrated in Figure SE3-5. The increased current gain of the Darlington pair means that zener current variations due to changes in load demand are reduced. This results in a more stable zener voltage and better voltage regulation. Load voltage is now found as $V_L = V_Z - 2V_{BE}$.

 


FIGURE SE3-5 A Darlington pass-transistor voltage regulator

 


FIGURE SE3-6 A Darlington feedback regulator

The Darlington pass-transistor regulator can be improved even more by adding a voltage divider on the output as an error detection circuit and another transistor, as shown in Figure SE3-6. If load voltage increases, so does the voltage at the base of Q_3 , causing it to conduct harder. As Q_3 conduction increases, V_{CE} for Q_3 decreases and the voltage at the base of Q_2 also decreases. This means that Q_1 passes less current to the load and load voltage decreases to compensate for the initial increase. The opposite occurs if load voltage tries to decrease. Voltage regulator circuits will be covered in more detail in Chapter 11.

SECTION 3-5 CHECKUP

1. What is another name for a common-collector amplifier?
2. What is the ideal maximum voltage gain of a CC amplifier?
3. What are the most important characteristics of the CC amplifier?
4. What advantage does a Darlington series pass transistor in a regulator have over a single pass transistor?

3-6 COMMON-BASE AMPLIFIERS

The third basic amplifier configuration is the common-base (CB). The CB amplifier provides high voltage gain but has low input resistance. For this reason, it is not as widely used as other types but is used in certain high-frequency applications and in a circuit called a differential amplifier that we will discuss in Chapter 6.

After completing this section, you should be able to

- Understand and analyze the operation of common-base amplifiers
- Draw the equivalent ac circuit for a CB amplifier
- Compute the voltage gain and the input and output resistances for a CB amplifier

A typical **common-base (CB)** amplifier using voltage-divider bias is shown in Figure 3–42(a). The base is at signal (ac) ground due to C_3 , and the input signal is applied to the emitter. The output is coupled through C_2 from the collector to the load resistor. Figure 3–42(b) shows the equivalent ac circuit. Capacitors and the dc source have been replaced with shorts. This causes the bias resistors to be shorted in the equivalent circuit. The basic difference between this circuit and the common-emitter circuit is how the signal is fed to the amplifier.

 


FIGURE 3–42

Voltage Gain

As in the CE and CC amplifiers, the voltage gain of the CB amplifier is the ratio of V_{out}/V_{in} . For the CB amplifier, V_{out} is the ac collector voltage, V_c , and V_{in} is the ac emitter voltage, V_e . With this in mind, the voltage gain formula is developed as follows:

$$A_v = \frac{V_c}{V_e} = \frac{I_c(R_C \parallel R_L)}{I_e(r'_e \parallel R_E)}$$

The ac collector and emitter currents are nearly the same, so they cancel. Since $R_E \gg r'_e$, you can approximate $r'_e \parallel R_E$ as just r'_e . Further, $R_C \parallel R_L$ represents the ac resistance of the collector, R_c . Thus, the voltage gain is again a ratio of resistances.

$$A_v = \frac{R_C \parallel R_L}{r'_e \parallel R_E}$$

or

$$A_v \cong \frac{R_c}{r'_e}$$

This equation says the voltage gain is approximately equal to the ratio of the ac collector resistance to the internal ac emitter resistance. In this case, the emitter resistance is composed only of r'_e . The more general case is when a swamping resistor is added in the emitter circuit, considered next.

VOLTAGE GAIN WITH A SWAMPING RESISTOR One problem with the basic CB amplifier in Figure 3–42 is that it tends to distort larger signals because the only resistance on the input side is r'_e , which depends, to some extent, on the signal amplitude. A large signal causes changes in r'_e and therefore the gain. Figure 3–43 shows a modification of the basic amplifier with typical values for a small-signal transistor shown. The modification is the addition of a small-value swamping resistor, R_{E1} , in series with r'_e . As in the case of a CE amplifier, this additional fixed resistor produces greater gain stability

 


FIGURE 3-43 CB amplifier with swamping resistor.

and increases the input resistance but at the price of reduced gain. For the CB amplifier, it can also significantly improve linearity because the swamping resistor is a fixed quantity, independent of the signal amplitude.

Since the swamping resistor is in series with r'_e , its value is added to r'_e to obtain the approximate ac emitter resistance (ignoring the much larger parallel R_{E2}). The voltage gain of the CB amplifier is still the ac collector resistance, R_C , divided by the ac emitter resistance, R_e , but now includes the swamping resistor.

$$A_v \cong \frac{R_C \parallel R_L}{r'_e + R_{E1}}$$

$$A_v \cong \frac{R_C}{R_e} \quad (3-15)$$

Note that this gain equation is the same as that for the CE amplifier except that the CB amplifier does not invert the signal so the sign of the gain is positive.

Input Resistance

For the basic amplifier without a swamping resistor (Figure 3-42), R_E appears in parallel with r'_e when viewed from the source. However, r'_e is normally small compared to R_E , so you can generally ignore R_E when finding the input resistance. Therefore, the total input resistance of a CB amplifier without a swamping resistor is approximately r'_e . This is the main disadvantage to the CB amplifier. Although the input resistance is small compared to the CE and CC amplifiers, in certain high-frequency applications, this can be an advantage.

As in the case of the CE amplifier, a swamping resistor increases the input resistance. With a swamping resistor, the input resistance is approximately $r'_e + R_{E1}$. This approximation again ignores the contribution of resistor R_{E2} , which appears to be a large parallel path for the input signal. Thus,

$$R_{in(tot)} \cong r'_e + R_{E1} \quad (3-16)$$

Output Resistance

The output circuit of the CB amplifier is identical to that of the CE amplifier; therefore, the output resistance is the same (see discussion in Section 3-4). When looking back from the output coupling capacitor, the output resistance for both the CB and CE amplifiers is simply the collector resistance, R_C .

$$R_{out} = R_C$$

EXAMPLE 3–14

Find the total input resistance and the voltage gain for the CB amplifier in Figure 3–43.

SOLUTION

In order to determine r'_e , it is first necessary to find I_E . Find the dc voltage on the base using the voltage-divider rule.

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{15 \text{ k}\Omega}{36 \text{ k}\Omega + 15 \text{ k}\Omega} \right) 15 \text{ V} = 4.41 \text{ V}$$

The emitter voltage is one diode drop less than the base.

$$V_E = V_B - V_{BE} = 4.41 \text{ V} - 0.7 \text{ V} = 3.71 \text{ V}$$

From Ohm's law, the emitter current is

$$I_E = \frac{V_E}{R_E} = \frac{3.71 \text{ V}}{1.53 \text{ k}\Omega} = 2.43 \text{ mA}$$

The value of r'_e can now be found.

$$r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{2.43 \text{ mA}} = 10.3 \Omega$$

Looking from the input coupling capacitor, the total input resistance is the sum of the swamping resistor and r'_e .

$$R_{in(tot)} = r'_e + R_{E1} = 10.3 \Omega + 27 \Omega = \mathbf{37.3 \Omega}$$

The signal voltage gain is the ratio of the collector ac resistance to the emitter ac resistance. The collector ac resistance, R_c , is equal to $R_C \parallel R_L$. The emitter ac resistance is equal to $r'_e + R_{E1}$. Therefore, the voltage gain is

$$A_v \cong \frac{R_c}{R_e} = \frac{R_C \parallel R_L}{r'_e + R_{E1}} = \frac{3.6 \text{ k}\Omega \parallel 3.6 \text{ k}\Omega}{10.3 \Omega + 27 \Omega} = \mathbf{48}$$

PRACTICE EXERCISE

What is the output voltage if the input voltage at the coupling capacitor is a 50 mV peak-to-peak sinusoidal wave?

The bias methods introduced in Section 3–2 can be applied to CB amplifiers. Emitter bias requires fewer components but requires dual power supplies. With emitter bias on a CB amplifier, the base can be connected directly to ground, rather than through a capacitor and there are no bias resistors. Example 3–15 illustrates emitter bias with a CB amplifier using a *pnp* transistor. Try estimating the dc parameters and the gain before you look at the solution.

EXAMPLE 3–15

Find the total input resistance and voltage gain for the CB amplifier in Figure 3–44.

SOLUTION

Since the base is grounded, the emitter voltage is 0.7 V above ground. It can be shown with an equation as

$$V_E = V_B - V_{BE} = 0 \text{ V} - (-0.7 \text{ V}) = +0.7 \text{ V}$$

Applying Ohm's law for the emitter current,

$$I_E = \frac{V_{R_E}}{R_E} = \frac{V_{EE} - V_E}{R_E} = \frac{15 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 1.43 \text{ mA}$$

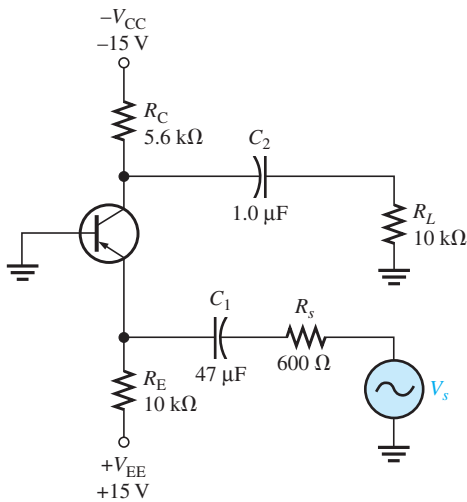


FIGURE 3-44

The value of r'_e is

$$r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.43 \text{ mA}} = 17.5 \Omega$$

Since there is no swamping resistor, the total input resistance (looking from the input coupling capacitor) is just r'_e . Therefore, the total input resistance is

$$R_{in(tot)} = r'_e = 17.5 \Omega$$

The signal voltage gain, measured from the input coupling capacitor to the load resistor, is

$$A_v \cong \frac{R_c}{R_e} \cong \frac{R_c \parallel R_L}{r'_e} = \frac{5.6 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{17.5 \Omega} = 205$$


PRACTICE EXERCISE

What dc collector voltage should be observed for the circuit in Figure 3-44?

The common-base amplifier has two primary systems applications. In some systems, one of the drawbacks of the CB amp can actually be an attribute. The low input resistance of the CB amplifier is a good impedance match for moving-coil microphones and is often found in microphone preamplifiers. Amplifiers with low input resistance tend to have better noise immunity than those with high input resistance. This is important in moving-coil microphones as they output a very low-level signal.

The most common application for CB amplifiers is in VHF and UHF systems. The grounded base helps isolate the emitter input from the collector output. This means there is very little feedback, which increases stability and helps reduce the chance of oscillation. CB amplifiers have a wider bandwidth than an equivalent CE amplifier. With the input at the emitter, this configuration is not as affected by internal transistor junction capacitances compared to the CE amplifier. These internal capacitances, between base-emitter and base-collector, limit amplifier high frequency response particularly in inverting amplifiers like the CE amplifier.

SYSTEM NOTE

 

Summary of AC Parameters for CE, CC, and CB Amplifiers

Table 3-2 summarizes the important ac characteristics of each of the three basic voltage amplifier configurations. Also, relative values are indicated for general comparison of the

amplifiers. The input resistance depends on the particular circuit, including the type of bias. Voltage-divider bias is assumed for all amplifiers with an unbypassed emitter resistor (R_{E1}) in the CE and CB configurations. These configurations are the same as have been discussed in the previous sections.

TABLE 3–2 • Comparison of amplifier ac parameters. Voltage-divider bias is assumed for all amplifiers with an unbypassed emitter resistor in the CE and CB configurations.

	CE	CC	CB
Voltage gain	$A_v \cong -\frac{R_c}{R_e}$ High	$A_v \cong 1$ Low	$A_v \cong \frac{R_c}{R_e}$ High
Input resistance	$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_{E1})]$ Low	$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_E \parallel R_L)]$ High	$R_{in(tot)} = r'_e + R_{E1}$ Very low
Output resistance	R_C High	$\cong r'_e$ Low	R_C High

SECTION 3–6 CHECKUP

1. Can the same voltage gain be achieved with a CB as with a CE amplifier?
2. Is the input resistance of a CB amplifier very low or very high?
3. What is the advantage of using a swamping resistor with a CB amplifier?
4. Why does the CB amplifier have a higher frequency response than an equivalent CE amplifier?

3–7 THE BIPOLAR TRANSISTOR AS A SWITCH

In the previous sections, we discussed the transistor as a linear amplifier. Another major application area is switching applications used in digital systems. The first large-scale use of digital circuits was in telephone systems. Today, computers form the most important application of switching circuits using integrated circuits (ICs). Discrete transistor switching circuits are used when it is necessary to supply higher currents or operate at a different voltage than can be obtained from ICs.

After completing this section, you should be able to

- Explain how a transistor can be used as a switch
- Compute the saturation current for a transistor switch
- Explain how a transistor switching circuit with hysteresis changes states

Figure 3–45 illustrates the basic operation of a transistor as a **switch**. A switch is a two-state device that is either open or closed. In part (a), the transistor is in cutoff because the base-emitter pn junction is not forward-biased. In this condition, there is, ideally, an open between collector and emitter, as indicated by the open switch equivalent. In part (b), the transistor is in saturation because the base-emitter pn junction is forward-biased and the base current is large enough to cause the collector current to reach its saturated value. In this condition, there is, ideally, a short between collector and emitter, as indicated by the

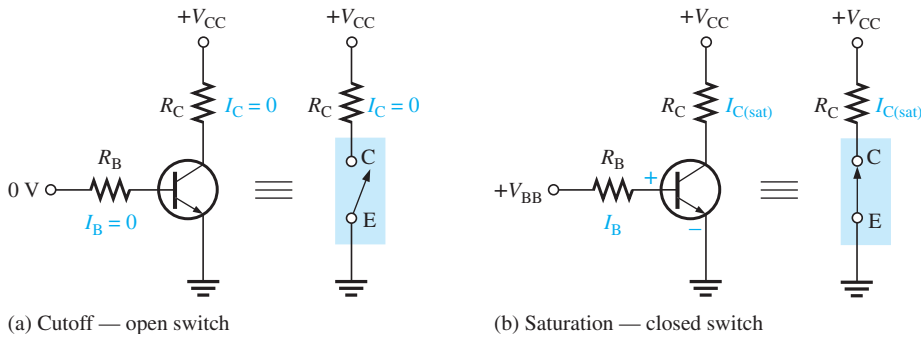


FIGURE 3-45 Ideal switching action of a transistor.

closed-switch equivalent. Actually, a voltage drop of a few tenths of a volt normally occurs across the transistor when it is saturated.

Conditions in Cutoff

As mentioned before, a transistor is in cutoff when the base-emitter pn junction is not forward-biased. Neglecting leakage current, all of the currents are zero, and V_{CE} is equal to V_{CC} .

$$V_{CE(\text{cutoff})} = V_{CC}$$

Conditions in Saturation

When the emitter junction is forward-biased and there is enough base current to produce a maximum collector current, the transistor is saturated. Since V_{CE} is very small at saturation, the entire power supply voltage drops across the collector resistor. An approximation for the collector current is

$$I_{C(\text{sat})} \cong \frac{V_{CC}}{R_C}$$

The minimum value of base current needed to produce saturation is

$$I_{B(\text{min})} \cong \frac{I_{C(\text{sat})}}{\beta_{DC}}$$

I_B should be significantly greater than $I_{B(\text{min})}$ to keep the transistor well into saturation and to account for beta variations in different transistors.

EXAMPLE 3-16

(a) For the transistor switching circuit in Figure 3-46, what is V_{CE} when $V_{IN} = 0$ V?

 


FIGURE 3-46

- (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Assume $V_{CE(sat)} = 0\text{ V}$.
- (c) Calculate the maximum value of R_B when $V_{IN} = 5\text{ V}$.

SOLUTION

- (a) When $V_{IN} = 0\text{ V}$, the transistor is in cutoff (acts like an open switch) and $V_{CE} = V_{CC} = 10\text{ V}$.
- (b) Since $V_{CE(sat)} = 0\text{ V}$,

$$I_{C(sat)} \cong \frac{V_{CC}}{R_C} = \frac{10\text{ V}}{1.0\text{ k}\Omega} = 10\text{ mA}$$

$$I_{B(\min)} = \frac{I_{C(sat)}}{\beta_{DC}} = \frac{10\text{ mA}}{200} = \mathbf{0.05\text{ mA}}$$

This is the value of I_B necessary to drive the transistor to the point of saturation. Any further increase in I_B will drive the transistor deeper into saturation but will not increase I_C .

- (c) When the transistor is saturated, $V_{BE} = 0.7\text{ V}$. The voltage across R_B is


$$V_{R_B} = V_{IN} - V_{BE} = 5\text{ V} - 0.7\text{ V} = 4.3\text{ V}$$

The maximum value of R_B needed to allow a minimum I_B of 0.05 mA is calculated by Ohm's law as follows:

$$R_B = \frac{V_{R_B}}{I_B} = \frac{4.3\text{ V}}{0.05\text{ mA}} = \mathbf{86\text{ k}\Omega}$$

PRACTICE EXERCISE

 Determine the minimum value of I_B required to saturate the transistor in Figure 3-46 if β_{DC} is 125 and $V_{CE(sat)}$ is 0.2 V.



One common application for BJT switching circuits is in digital systems. The two main types of BJT-based logic gates are transistor-transistor logic (TTL) and emitter-coupled logic (ECL). TTL is the more popular of the two. Although CMOS is now the most widely used digital circuit technology, TTL was the leading family in the small-scale and medium-scale integration categories up until about 1990. TTL does have one advantage over CMOS. TTL ICs are less susceptible to electrostatic discharge than CMOS chips, so they are more practical for laboratory work and prototyping.

SYSTEM NOTE

Improvements to the One-Transistor Switching Circuit

The basic switching circuit shown in Figure 3-45 has a threshold voltage at which it changes from *off to on* or *on to off*. Unfortunately, the threshold is not an absolute point because a transistor can operate between cutoff and saturation, a condition not desirable in a switching circuit. A second transistor can dramatically improve the switching action, providing a sharp threshold. The circuit is shown in Figure 3-47, designed with a light-emitting diode (LED) output so that you can construct it if you choose and observe the switching action. The circuit works as follows. When V_{IN} is very low, Q_1 is off since it

does not have sufficient base current. Q_2 will be in saturation because it can obtain ample base current through R_2 and the LED is on. As the base voltage for Q_1 is increased, Q_1 begins to conduct. As Q_1 approaches saturation, the base voltage of Q_2 suddenly drops, causing it to go from a saturated to cutoff condition rapidly. The output voltage of Q_2 drops and the LED goes out.

Another improvement for basic switching circuits is the addition of hysteresis. For switching circuits, **hysteresis** means that there are two threshold voltages depending on whether the output is already high or already low. Figure 3-48 illustrates the situation. When the input voltage rises, it must cross the upper threshold before switching takes place. It does not switch at A or B because the lower threshold is inactive. When the signal crosses the upper threshold at point C, the output switches, and immediately the threshold changes to a lower value. The output does not switch back at D but instead must cross the lower threshold at E before returning to the original state. Again, the threshold changes to the upper level, so switching does not take place at point F. The major advantage of hysteresis in a switching circuit is noise immunity. As you can see from this example, the output only changed twice despite a very noisy input.

 


FIGURE 3-47 A two-transistor switching circuit with a sharp threshold.

 


FIGURE 3-48 Hysteresis causes the circuit to switch at points C and E but not at the other points.

The schematic for a transistor circuit with hysteresis is shown in Figure 3-49. As the potentiometer is turned in one direction, the output will switch once, even if the potentiometer is “noisy.” When the output switches, the common-emitter resistor, R_E , causes the threshold voltage to change. This is caused by the different saturation currents for the two transistors; the threshold is different when the output is in cutoff than when the output is saturated.

 


FIGURE 3-49 A discrete transistor switching circuit with hysteresis.

SYSTEM EXAMPLE 3-3



SECURITY ALARM SYSTEM

A circuit using transistor switches will be developed for use in an alarm system for detecting forced entry into a building. In its simplest form, the alarm system will accommodate four zones with any number of openings. It can be expanded to cover additional zones. For the purposes of this system example, a zone is one room in a house or other building. The sensor used for each opening can be either a mechanical switch, a magnetically operated switch, or an optical sensor. Detection of an intrusion can be used to initiate an audible alarm signal and/or to initiate transmission of a signal over the phone line to a monitoring service.

Designing the Circuit

A basic block diagram of the system is shown in Figure SE3-7. The sensors for each zone are connected to the switching circuits, and the output of the switching circuit goes to an audible alarm circuit and/or to a telephone dialing circuit. The focus of this example is the transistor switching circuits.

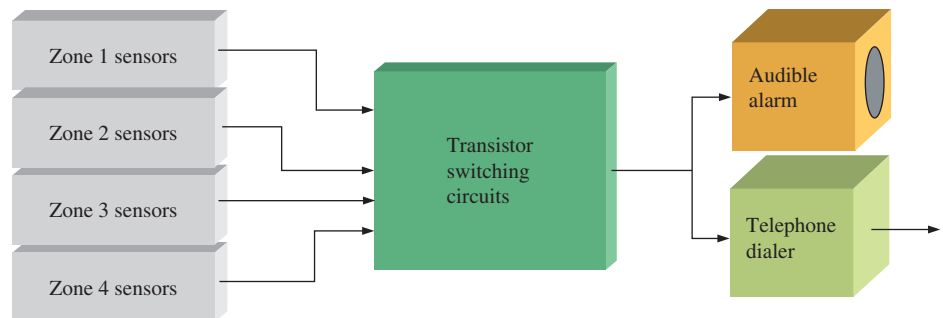


FIGURE SE3-7 Block diagram of security alarm system.

A zone sensor detects when a window or door is opened. They are normally in a closed position and are connected in series to a dc voltage source, as shown in Figure SE3-8(a). When a window or door is opened, the corresponding sensor creates an open circuit, as shown in part (b). The sensors are represented by switch symbols.

A circuit for one zone is shown in Figure SE3-9. It consists of two BJTs, Q_1 and Q_2 . As long as the zone sensors are closed, Q_2 is in the *on* state (saturated). The very low saturation voltage at the Q_1 collector keeps Q_2 *off*. Notice that the collector of Q_2 is left open with no load connected. This allows for all four of the zone circuit outputs to be tied together and a common load connected externally to drive the alarm and/or dialing circuits. If one of the zone sensors opens, indicating a break-in, Q_1 turns *off* and its collector voltage goes to V_{CC} . This turns on Q_2 , causing it to saturate. The *on* state of Q_2 will then activate the audible alarm and the telephone dialing sequence.

 
 


FIGURE SE3-8 Zone sensor configuration.

 


FIGURE SE3-9 One of the four identical transistor switching circuits.

SECTION 3-7 CHECKUP

1. When a transistor is used as a switching device, in what two states is it operated?
2. When does the collector current reach its maximum value?
3. When is the collector current approximately zero?
4. When is V_{CE} equal to V_{CC} ?
5. What is meant by hysteresis in a switching circuit?

3-8 TRANSISTOR PACKAGES AND TERMINAL IDENTIFICATION

Transistors are available in a wide range of package types for various applications. Those with mounting studs or heat sinks are usually power transistors. Low-power and medium-power transistors are usually found in smaller metal or plastic cases. Still another package classification is for high-frequency devices. You should be familiar with common transistor packages and be able to identify the emitter, base, and collector terminals. This section is about transistor packages and terminal identification.

After completing this section, you should be able to

- Identify various types of transistor package configurations
- List three broad categories of transistors
- Recognize various types of cases and identify the pin configurations

Transistor Categories

Manufacturers generally classify their bipolar junction transistors into three broad categories: general-purpose/small-signal devices, power devices, and RF (radio frequency/microwave) devices. Although each of these categories, to a large degree, has its own unique package

types, you will find certain types of packages used in more than one device category. While keeping in mind there is some overlap, we will look at transistor packages for each of the three categories so that you will be able to recognize a transistor when you see one on a circuit board and have a good idea of what general category it is in.

GENERAL-PURPOSE/SMALL-SIGNAL TRANSISTORS General-purpose/small-signal transistors are generally used for low- or medium-power amplifiers or switching circuits. The packages are either plastic or metal cases. Certain types of packages contain multiple transistors. Figure 3–50 illustrates common plastic cases, Figure 3–51 shows packages called *metal cans*, and Figure 3–52 shows multiple-transistor packages. Some of the multiple-transistor packages such as the dual-in-line (DIP) and the small-outline (SO) are the same as those used for many integrated circuits. Typical pin connections are shown so you can identify the emitter, base, and collector.

 


FIGURE 3–50 Plastic cases for general-purpose/small-signal transistors. Both old and new JEDEC TO numbers are given. Pin configurations may vary. Always check the data sheet.

 


FIGURE 3–51 Metal cans for general-purpose/small-signal transistors.

POWER TRANSISTORS Power transistors are used to handle large currents (typically more than 1 A) and/or large voltages. For example, the final audio stage in a stereo system uses a power transistor amplifier to drive the speakers. Figure 3–53 shows some common package configurations. In most applications, the metal tab or the metal case is common to the collector and is thermally connected to a heat sink for heat dissipation. Notice in part (g) how the small transistor chip is mounted inside the much larger package.

 


FIGURE 3-52 Typical multiple-transistor packages.

 


FIGURE 3-53 Typical power transistors.

RF TRANSISTORS RF transistors are designed to operate at extremely high frequencies and are commonly used for various purposes in communications systems and other high-frequency applications. Their unusual shapes and lead configurations are designed to optimize certain high-frequency parameters. Figure 3-54 shows some examples.

 


FIGURE 3-54 Examples of RF transistors.

SECTION 3-8 CHECKUP

- List the three broad categories of bipolar junction transistors.
- In a single-transistor metal case, how do you identify the leads?
- In power transistors, the metal mounting tab or case is connected to which transistor region?

3-9 TROUBLESHOOTING

As you already know, a critical skill in electronics is the ability to identify a circuit malfunction and to isolate the failure to a single component if possible. In this section, the basics of troubleshooting transistor bias circuits and testing individual transistors are covered.

After completing this section, you should be able to

- Troubleshoot various faults in transistor circuits
 - Define *floating point*
 - Use voltage measurements to identify a fault in a transistor circuit
 - Use a DMM to test a transistor
 - Explain how a transistor can be viewed in terms of a diode equivalent
 - Discuss in-circuit and out-of-circuit testing
 - Discuss point-of-measurement in troubleshooting
 - Discuss leakage and gain measurements

 


FIGURE 3-55 A basic transistor bias circuit.

Troubleshooting a Biased Transistor

Several faults can occur in a simple transistor bias circuit. Possible faults are open bias resistors, open or resistive connections, shorted connections, and opens or shorts internal to the transistor itself. Figure 3-55 is a basic transistor bias circuit with all voltages referenced to ground. The two bias voltages are $V_{BB} = 3\text{ V}$ and $V_{CC} = 9\text{ V}$. The correct voltages at the base and collector are shown. Analytically, these voltages are determined as follows. A $\beta_{DC} = 200$ is taken as midway between the minimum and maximum values of h_{FE} given on the data sheet for the 2N3904 in Figure 3-25. A different h_{FE} (β_{DC}), of course, will produce different results for the given circuit.

$$V_B = V_{BE} = 0.7\text{ V}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3\text{ V} - 0.7\text{ V}}{56\text{ k}\Omega} = \frac{2.3\text{ V}}{56\text{ k}\Omega} = 41.1\text{ }\mu\text{A}$$

$$I_C = \beta_{DC} I_B = 200(41.1\text{ }\mu\text{A}) = 8.2\text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 9\text{ V} - (8.2\text{ mA})(560\text{ }\Omega) = 4.4\text{ V}$$

Several faults that can occur in the circuit and the accompanying symptoms are illustrated in Figure 3-56. Symptoms are shown in terms of measured voltages that are incorrect. The term **floating point** refers to a point in the circuit that is not electrically connected to ground or a “solid” voltage. Normally, very small and sometimes fluctuating voltages in the μV to low mV range are generally observed at floating points. The faults in Figure 3-56 are typical but do not represent all possible faults that may occur.

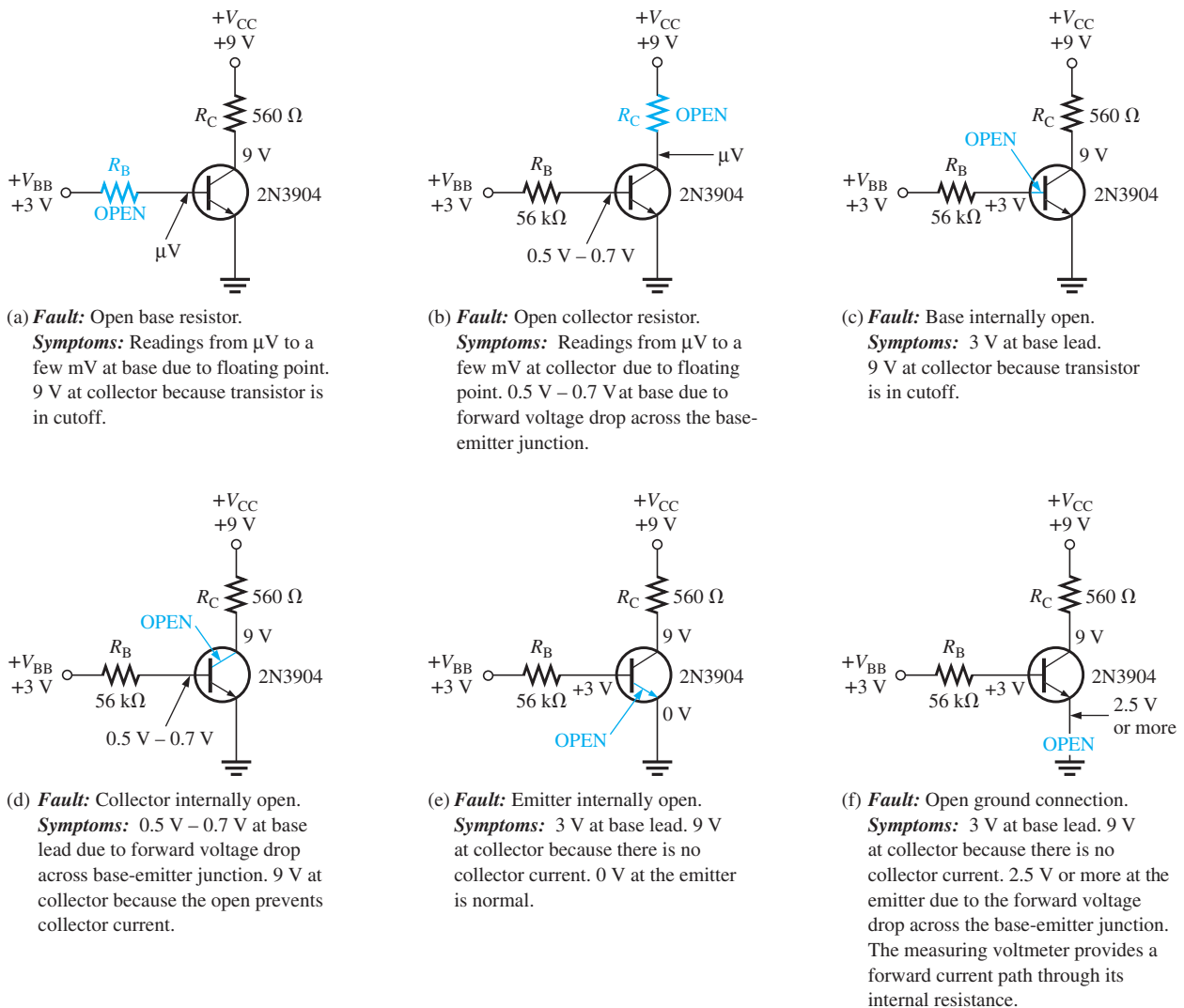


FIGURE 3-56 Typical faults and symptoms in the basic transistor bias circuit.

Testing a Transistor with a DMM

A digital multimeter can be used as a fast and simple way to check a transistor for open or shorted junctions. For this test, you can view the transistor as two diodes connected as shown in Figure 3-57 for both *nnp* and *pnp* transistors. The base-collector junction is one diode and the base-emitter junction is the other.

Recall that a good diode will show an extremely high resistance (or open) with reverse bias and a very low resistance with forward bias. A defective open diode will show an extremely high resistance (or open) for both forward and reverse bias. A defective shorted or resistive diode will show zero or a very low resistance for both forward and reverse bias. An open diode is the most common type of failure. Since the transistor *pn* junctions are, in effect diodes, the same basic characteristics apply.

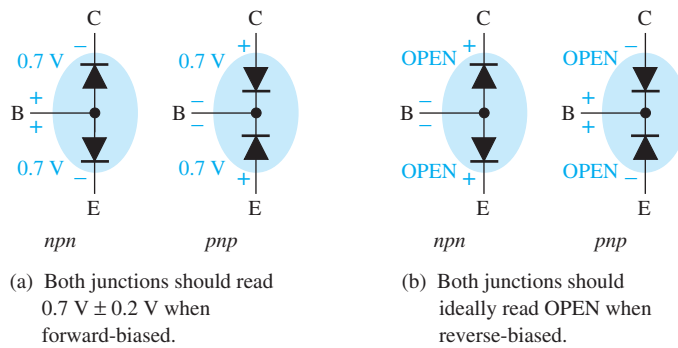
 


FIGURE 3-57 A transistor viewed as two diodes.

THE DMM DIODE TEST POSITION Many digital multimeters (DMMs) have a *diode test* position that provides a convenient way to test a transistor. A typical DMM, as shown in Figure 3-58, has a small diode symbol to mark the position of the function switch. When set to diode test, the meter provides an internal voltage sufficient to forward-bias and reverse-bias a transistor junction. This internal voltage may vary among different makes of DMM, but 2.5 V to 3.5 V is a typical range of values. The meter provides a voltage reading to indicate the condition of the transistor junction under test.


FIGURE 3-58 Typical DMM test of a properly functioning *nnp* transistor. Leads are reversed for a *pnp* test.

WHEN THE TRANSISTOR IS NOT DEFECTIVE In Figure 3-58(a), the V Ω (positive) lead of the meter is connected to the base of an *nnp* transistor and the COM (negative) lead is connected to the emitter to forward-bias the base-emitter junction. If the junction is good, you will get a reading of between 0.5 V and 0.9 V, with 0.7 V being typical for forward bias.

In Figure 3-58(b), the leads are switched to reverse-bias the base-emitter junction, as shown. If the transistor is working properly, you will get an open circuit (OL) indication. The OL reading indicates that the junction has an extremely high reverse resistance.

The process just described is repeated for the base-collector junction as shown in Figure 3-58(c) and (d). For a *pnp* transistor, the polarity of the meter leads are reversed for each test.

WHEN THE TRANSISTOR IS DEFECTIVE When a transistor has failed with an open junction or internal connection, you get an open circuit (OL) reading for both the forward-bias and the reverse-bias conditions for that junction, as illustrated in Figure 3-59(a). If a junction is shorted, the meter reads 0 V in both forward- and reverse-bias tests, as indicated in part (b). Sometimes, a failed junction may exhibit a small resistance for both bias

 

(a) Forward-bias test and reverse-bias test give the same reading (OL is typical) for an open BC junction.

(b) Forward- and reverse-bias tests for a shorted junction give the same 0 V reading.

FIGURE 3-59 Testing a defective *nnp* transistor. Leads are reversed for a *npn*.

conditions rather than a pure short. In this case, the meter will show a small voltage much less than the correct open voltage. For example, a resistive junction may result in a reading of 1.1 V in both directions rather than the correct readings of 0.7 V forward and OL reverse.

Some DMMs provide a test socket on their front panel for testing a transistor for the h_{FE} (β_{DC}) value. If the transistor is inserted improperly in the socket or if it is not functioning properly due to a faulty junction or internal connection, a typical meter will flash a 1 or display a 0. If a value of β_{DC} within the normal range for the specific transistor is displayed, the device is functioning properly. The normal range of β_{DC} can be determined from the data sheet.

CHECKING A TRANSISTOR WITH THE OHMS FUNCTION DMMs that do not have a diode test position or an h_{FE} socket can be used to test a transistor for open or shorted junctions by setting the function switch to an OHMs range. For the forward-bias check of a good transistor *pn* junction, you will get a resistance reading that can vary depending on the meter's internal battery. Many DMMs do not have sufficient voltage on the OHMs range to fully forward-bias a junction, and you may get a reading of from several hundred to several thousand ohms.

For the reverse-bias check of a good transistor, you will get an out-of-range indication on most DMMs because the reverse resistance is too high to measure.

Even though you may not get accurate forward and reverse resistance readings on a DMM, the relative readings are sufficient to indicate a properly functioning transistor *pn* junction. The out-of-range indication shows that the reverse resistance is very high, as you expect. The reading of a few hundred to a few thousand ohms for forward bias indicates that the forward resistance is small compared to the reverse resistance, as you expect.

Transistor Testers

A comprehensive test of a transistor can be performed with a transistor curve tracer, shown in Figure 3-60. The curve tracer can show the characteristic curve for all types of transistors, as well as other solid-state devices. It can measure most of the important parameters for these devices. Some advanced curve tracers can perform these measurements automatically and include automated setup and sequencing through a variety of measurements, data storage, and direct hard copy output of measurements for documentation.

There are various reasons for measuring the characteristics of a device. In engineering work, it is useful to know certain parameters to completely understand a circuit's



FIGURE 3-60 Transistor curve tracer. Copyright © Tektronix, Inc. Reprinted with permission.

performance. Component manufacturers measure characteristics in order to develop better products and to characterize production runs. Sometimes a curve tracer is used for incoming test, quality control, or sorting components. Finally, of course, there are educational reasons to study the parameters of various active devices.

Although a curve tracer is the ultimate transistor tester, it is better to test a transistor in the circuit, particularly if it is soldered in place. Good troubleshooting practice dictates that you do not unsolder a component unless you are reasonably sure it is bad or you simply cannot isolate the trouble any other way. A circuit that is not working may have a good transistor or a bad one as illustrated in the simplified circuit in the following two cases.

CASE 1 If the transistor tests defective, it should be carefully removed and replaced with a known good one. An out-of-circuit check of the replacement device is usually a good idea, just to make sure it is OK. The transistor is plugged into the socket on the transistor tester for out-of-circuit tests.

CASE 2 If the transistor tests good in-circuit but the circuit is not working properly, examine the circuit board for a poor connection at the collector pad or for a break in the connecting trace. A poor solder joint often results in an open or a highly resistive contact. A troubleshooter can isolate the problem with voltage measurements. The physical point at which you actually measure the voltage is very important in this case. For example, if you check the collector lead when there is an external open at the collector pad, you will get a floating point. If you measure on the connecting trace or on the R_C lead, you will read V_{CC} . This situation is illustrated in Figure 3-61.

 


FIGURE 3-61 The indication of an open, when it is in the external circuit, depends on where you measure.

IMPORTANCE OF POINT-OF-MEASUREMENT IN TROUBLESHOOTING

In case 2, if you had taken the initial measurement on the transistor lead itself and the open were *internal* to the transistor as shown in Figure 3-62, you would have measured V_{CC} . This would have indicated a defective transistor even before the tester was used. This simple concept emphasizes the importance of point-of-measurement in certain troubleshooting situations.

 


FIGURE 3-62 Illustration of an internal open. Compare with Figure 3-61.

EXAMPLE 3-17

What fault do the measurements in Figure 3-63 indicate? (The probe is shown in three different locations.)

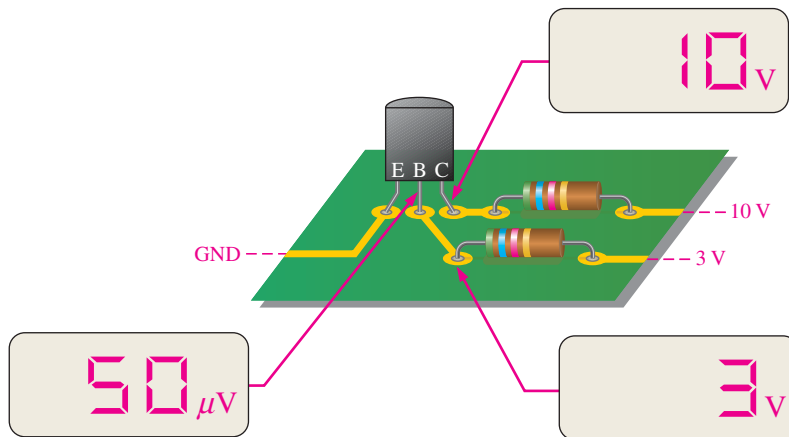


FIGURE 3-63

SOLUTION

The transistor is in cutoff, as indicated by the 10 V measurement on the collector lead. The base bias voltage of 3 V appears on the PC board contact but not on the transistor lead as indicated by the floating point measurement. This shows that there is an open external to the transistor between the two measured base points. Check the solder joint at the base contact on the PC board. If the open were internal, there would be 3 V on the base lead.

PRACTICE EXERCISE

If the meter in Figure 3-63 that now reads 3 V indicates a floating point when touching the circuit board pad, what is the most likely fault?

Leakage Measurement

Very small leakage currents exist in all transistors and, in most cases, are small enough to neglect (usually nA). When a transistor is connected as shown in Figure 3–64(a) with the base open ($I_B = 0$), it is in cutoff. Ideally $I_C = 0$, but actually there is a small current from collector to emitter, as mentioned earlier, called I_{CEO} (collector-to-emitter current with base open). This leakage current is usually in the nA range for silicon. A faulty transistor will often have excessive leakage current and can be checked in a transistor tester, which connects an ammeter as shown in part (a). Another leakage current in transistors is the reverse collector-to-base current, I_{CBO} . This is measured with the emitter open, as shown in Figure 3–64(b). If it is excessive, a shorted collector-base junction is likely.

 


FIGURE 3–64 Leakage current test circuits.

Gain Measurement

In addition to leakage tests, the typical transistor tester also checks the β_{DC} . A known value of I_B is applied and the resulting I_C is measured. The reading will indicate the value of the I_C/I_B ratio, although in some units only a relative indication is given. Most testers provide for an in-circuit β_{DC} check, so that a suspected device does not have to be removed from the circuit for testing.

SECTION 3–8 CHECKUP

1. If a transistor on a circuit board is suspected of being faulty, what should you do?
2. In a transistor bias circuit, such as the one in Figure 3–55, what happens if R_B opens?
3. In a circuit such as the one in Figure 3–55, what are the base and collector voltages if there is an external open between the emitter and ground?

SUMMARY

- A bipolar junction transistor (BJT) consists of three regions: emitter, base, and collector. The term *bipolar* refers to two types of current: electron current and hole current.
- The three regions of a BJT are separated by two *pn* junctions.
- The two types of bipolar transistor are the *npn* and the *pnp*.
- In normal operation, the base-emitter (BE) junction is forward-biased and the base-collector (BC) junction is reverse-biased.
- The three currents in a BJT are base current, emitter current, and collector current. They are related to each other by this formula: $I_E = I_C + I_B$.
- Characteristic collector curves for a BJT are a family of curves showing I_C versus V_{CE} for a given set of base currents.
- When a BJT is in cutoff, there is essentially no collector current except for a very tiny amount of collector leakage current, I_{CEO} . V_{CE} is a maximum.

- When a BJT is saturated, there is maximum collector current as determined by the external circuit.
- A load line represents all possible operating points for a circuit, including cutoff and saturation. The point at which the actual base current line intersects the load line is the quiescent or Q-point for the circuit.
- Base bias uses a single resistor between the power supply and the base terminal.
- Collector-feedback bias uses a single resistor between the collector and base terminals.
- Voltage-divider bias is a very stable form of bias that uses two resistors to form a voltage divider in the base circuit.
- Emitter bias is a very stable form of bias that uses both positive and negative power supplies and a single resistor between the base terminal and ground.
- DC values are identified with capital-letter nonitalic subscripts; ac values are identified with lowercase italic subscripts.
- Manufacturer's data sheets typically show maximum voltage, current, and power ratings for various parameters.
- Coupling capacitors are connected in series with the ac signal to bring it into and out of the amplifier.
- Bypass capacitors are connected in parallel with a resistor to provide an ac path around the resistor.
- Common-emitter (CE), common-collector (CC), and common-base (CB) designations refer to the common terminal for the ac signal.
- Voltage gain for CE, CC, and CB amplifiers can be found using a ratio of ac resistances.
- A darlington pair is a two-transistor configuration that is equivalent to a single very high-beta transistor.
- In switching circuits, transistors are designed to operate at either cutoff or saturation, the equivalent of an open or closed switch.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

ac beta (β_{ac}) The ratio of a change in collector current to a corresponding change in base current in a bipolar junction transistor.

Base One of the semiconductor regions in a BJT.

Bipolar junction transistor (BJT) A transistor constructed with three doped semiconductor regions separated by two *pn* junctions.

Collector One of the semiconductor regions in a BJT.

Common-base (CB) A BJT amplifier configuration in which the base is the common terminal to an ac signal or ground.

Common-collector (CC) A BJT amplifier configuration in which the collector is the common terminal to an ac signal or ground.

Common-emitter (CE) A BJT amplifier configuration in which the emitter is the common terminal to an ac signal or ground.

Cutoff The nonconducting state of a transistor.

dc beta (β_{DC}) The ratio of collector current to base current in a bipolar junction transistor.

Emitter One of the three semiconductor regions in a BJT.

Negative feedback The process of returning a portion of the output back to the input in a manner to cancel changes that may occur at the input.

Saturation The state of a BJT in which the collector current has reached a maximum and is independent of the base current.

KEY FORMULAS

(3-1) $I_E = I_C + I_B$ Relationship of key transistor currents

(3-2) $\beta_{DC} = \frac{I_C}{I_B}$ Definition of β_{DC}

(3-3)	$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$	Collector current for base bias
(3-4)	$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}}$	Collector current for collector-feedback bias
(3-5)	$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$	Base voltage for voltage-divider bias
(3-6)	$V_E = V_B - 0.7 \text{ V}$	Emitter voltage for voltage-divider bias
(3-7)	$V_C = V_{CC} - I_C R_C$	Collector voltage for CE and CB amplifiers
(3-8)	$\beta_{ac} = \frac{I_c}{I_b}$	Definition of β_{ac}
(3-9)	$r'_e = \frac{25 \text{ mV}}{I_E}$	AC emitter resistance
(3-10)	$A_v \cong -\frac{R_c}{R_e}$	Voltage gain for CE amplifier
(3-11)	$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_{E1})]$	Input resistance for CE amplifier with voltage-divider bias (R_{E1} is not bypassed)
(3-12)	$A_v \cong 1$	Voltage gain for CC amplifier
(3-13)	$R_{in(tot)} = R_1 \parallel R_2 \parallel [\beta_{ac}(r'_e + R_E \parallel R_L)]$	Input resistance for CC amplifier with voltage-divider bias and load resistor
(3-14)	$A_i = \frac{R_{in(tot)}}{R_L}$	Current gain for CC amplifier
(3-15)	$A_v \cong \frac{R_c}{R_e}$	Voltage gain for a CB amplifier
(3-16)	$R_{in(tot)} \cong r'_e + R_{E1}$	Input resistance for CB amplifier with swamping resistor

SELF-TEST

Answers are at the end of the chapter.

- The n -type regions in an npn bipolar junction transistor are
 - collector and base
 - collector and emitter
 - base and emitter
 - collector, base, and emitter
- The n -region in a pnp transistor is the
 - base
 - collector
 - emitter
 - case
- For normal operation of an npn transistor, the base must be
 - disconnected
 - negative with respect to the emitter
 - positive with respect to the emitter
 - positive with respect to the collector
- Beta (β) is the ratio of
 - collector current to emitter current
 - collector current to base current
 - emitter current to base current
 - output voltage to input voltage
- Two currents that are nearly the same in normal operation are
 - collector and base
 - collector and emitter
 - base and emitter
 - input and output
- If the base current for a transistor operating below saturation is increased, the collector current
 - increases and the emitter current decreases
 - decreases and the emitter current decreases
 - increases and the emitter current does not change
 - increases and the emitter current increases


7. A saturated bipolar transistor can be recognized by
- a very small voltage between the collector and emitter
 - V_{CC} between collector and emitter
 - a base emitter drop of 0.7 V
 - no base current
8. The voltage gain for a common-emitter (CE) amplifier can be expressed as a ratio of
- ac collector resistance to ac input resistance
 - ac emitter resistance to ac input resistance
 - dc collector resistance to dc emitter resistance
 - none of the above
9. The voltage gain for a common-collector (CC) amplifier
- depends on the input signal
 - depends on the transistor's β
 - is approximately 1
 - none of the above
10. In a CE amplifier, the capacitor from emitter to ground is called the
- coupling capacitor
 - decoupling capacitor
 - bypass capacitor
 - tuning capacitor
11. If the capacitor from emitter to ground in a CE amplifier is removed, the voltage gain
- increases
 - decreases
 - is not affected
 - becomes erratic
12. When the collector resistor in a CE amplifier is increased in value, the voltage gain
- increases
 - decreases
 - is not affected
 - becomes erratic
13. The input resistance of a CE amplifier is affected by
- the bias resistors
 - the collector resistor
 - answers (a) and (b)
 - neither (a) nor (b)
14. The output signal of a CB amplifier is always
- in phase with the input signal
 - out of phase with the input signal
 - larger than the input signal
 - equal to the amplitude of the input signal
15. The output signal of a CC amplifier is always
- in phase with the input signal
 - out of phase with the input signal
 - larger than the input signal
 - exactly equal to the input signal
16. A darlington pair is two transistors connected to give
- very high voltage gain
 - very high β
 - very low input resistance
 - very low output resistance
17. Compared to CE and CC amplifiers, the common-base (CB) amplifier has a
- lower input resistance
 - much larger voltage gain
 - larger current gain
 - higher input resistance
18. Compared to a normal transistor switch, a transistor switch with hysteresis has
- high input impedance
 - faster switching time
 - higher output current
 - two switching thresholds

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 3–71.

 - If R_2 is open,
 - V_B will
 - increase
 - decrease
 - not change
 - V_C will
 - increase
 - decrease
 - not change



- If R_C is open,
 3. V_B will
 - (a) increase (b) decrease (c) not change
 4. V_C will
 - (a) increase (b) decrease (c) not change

Refer to Figure 3–74.

- If R_E is $560\ \Omega$ instead of $390\ \Omega$,
 5. The dc collector voltage will
 - (a) increase (b) decrease (c) not change
 6. The voltage gain will
 - (a) increase (b) decrease (c) not change
- If C_2 is open,
 7. The dc emitter voltage will
 - (a) increase (b) decrease (c) not change
 8. The voltage gain will
 - (a) increase (b) decrease (c) not change
 9. The input impedance will
 - (a) increase (b) decrease (c) not change

Refer to Figure 3–76.

- If V_{CC} is $15\ \text{V}$,
 10. The voltage gain will
 - (a) increase (b) decrease (c) not change
 11. The input impedance will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 3–1 Structure of Bipolar Junction Transistors

1. What is the exact value of I_C for $I_E = 5.34\ \text{mA}$ and $I_B = 47.5\ \mu\text{A}$?
2. A certain transistor has an $I_C = 25\ \text{mA}$ and an $I_B = 200\ \mu\text{A}$. Determine the β_{DC} .
3. In a certain transistor circuit, the base current is 2% of the 30 mA emitter current. Determine the approximate collector current.
4. Find V_E and I_C in Figure 3–65.
5. Determine the I_B , I_C , and V_C for the transistor circuit in Figure 3–66. Assume $\beta_{DC} = 75$.
6. Draw the dc load line for the transistor circuit in Figure 3–67.
7. Determine I_B , I_C , and V_C in Figure 3–67.

 


FIGURE 3–65

 


FIGURE 3–66

 


FIGURE 3-67

SECTION 3-2 BJT Bias Circuits

8. For the base-biased *nnp* transistor in Figure 3-68, assume $\beta_{DC} = 100$. Find I_C and V_{CE} .
9. Repeat Problem 8 for $\beta_{DC} = 300$. (*Hint*: The transistor is now saturated!)
10. For the base-biased *pnnp* transistor in Figure 3-69, assume $\beta_{DC} = 200$. Find I_C and V_{CE} .
11. For each of the following conditions in the circuit of Figure 3-69, determine if the collector current will increase, decrease, or remain the same:
 - (a) the base is shorted to ground
 - (b) R_C is smaller
 - (c) the transistor has a higher β
 - (d) the temperature increases
 - (e) R_B is smaller
12. For the collector-feedback bias circuit in Figure 3-70, determine I_C and V_{CE} . Assume $\beta_{DC} = 100$.

 


FIGURE 3-68

 


FIGURE 3-69

 


FIGURE 3-70

13. For the voltage-divider biased circuit in Figure 3-71, determine I_C and V_{CE} .
14. For the voltage-divider biased (*pnnp*) circuit in Figure 3-72, determine I_C and V_{CE} .
15. Determine the end points for the dc load line, $I_{C(sat)}$ and $V_{CE(cutoff)}$ for Figure 3-72.
16. For the emitter-bias circuit in Figure 3-73, determine I_C and V_{CE} .

 


FIGURE 3-71

 


FIGURE 3-72

 


FIGURE 3-73

SECTION 3-3 Data Sheet Parameters and AC Considerations

17. For the circuit in Figure 3-73, determine dc power dissipated in the transistor.
18. Assume the transistor in Figure 3-73 is a 2N3904. Can the power supplies be increased to 24 V without exceeding $P_{D(\max)}$? (Data sheet is Figure 3-25.)
19. Assume that R_C in Figure 3-73 was replaced with a 330 Ω resistor.
 - (a) What is the new value of I_C and V_{CE} ?
 - (b) What is the power dissipated in R_C as a result of this change?
 - (c) What is the power dissipated in the transistor as a result of this change?
20. A certain transistor is to be operated at a collector current of 50 mA. How high can V_{CE} go without exceeding a $P_{D(\max)}$ of 1.2 W?

SECTION 3-4 Common-Emitter Amplifiers

21. Determine the dc voltages, V_B , V_E , and V_C , with respect to ground in Figure 3-74.
22. Determine the voltage gain for the CE amplifier in Figure 3-74.
23. The amplifier in Figure 3-75 has a variable gain control, using a 100 Ω potentiometer for R_E with the wiper ac grounded. As the potentiometer is adjusted, more or less of R_E is bypassed to ground, thus varying the gain. The total R_E remains constant to dc, keeping the bias fixed. Determine the maximum and minimum gains for this amplifier.
24. If a load resistance of 600 Ω is placed on the output of the amplifier in Figure 3-75, what is the maximum gain?

 


FIGURE 3-74


 


FIGURE 3-75

SECTION 3-5 Common-Collector Amplifiers

25. For the CC amplifier in Figure 3-76, compute the total ac input resistance and the current gain to the load. Assume $\beta_{ac} = 150$.
26. Draw the ac equivalent circuit for the CC amplifier in Figure 3-76.
27. Compute the ac saturation current ($I_{c(sat)}$) and ac cutoff voltage ($V_{ce(cutoff)}$) for the CC amplifier in Figure 3-76.
28. For the *npn* CC amplifier in Figure 3-72, show where the input and output signals should be connected.

FIGURE 3-76

 

SECTION 3-6 Common-Base Amplifiers

- 29. What is the main disadvantage of the CB amplifier compared to the CE and the emitter-follower?
- 30. For the CB amplifier in Figure 3-77, compute the following: V_B , V_E , V_C , V_{CE} , r'_e , A_v .
- 31. For the CB amplifier in Figure 3-77, compute the input resistance, $R_{in(tot)}$.
- 32. For the CB amplifier in Figure 3-77, what is the purpose of R_{E1} ?

SECTION 3-7 The Bipolar Transistor as a Switch

- 33. Determine $I_{C(sat)}$ for Q_1 and Q_2 in Figure 3-43.
- 34. The transistor in Figure 3-78 has $\beta_{DC} = 100$. Determine the maximum value of R_B that will ensure saturation when V_{IN} is 5 V.

 


FIGURE 3-77

 


FIGURE 3-78

SECTION 3-8 Transistor Packages and Terminal Identification

- 35. Identify the leads on the transistors in Figure 3-79. Bottom views are shown.
- 36. What is the most probable category of each transistor in Figure 3-80?

 


FIGURE 3-79

 


FIGURE 3-80

SECTION 3-9 Troubleshooting

- 37. In an out-of-circuit test of a good npn transistor, what should an analog ohmmeter indicate when its positive probe is touching the emitter and the negative probe is touching the base? When its positive probe is touching the base and the negative probe is touching the emitter?

38. What is the most likely problem, if any, in each circuit of Figure 3–81? Assume $\beta_{DC} = 75$.
 39. What is the value of the dc beta of each transistor in Figure 3–82?

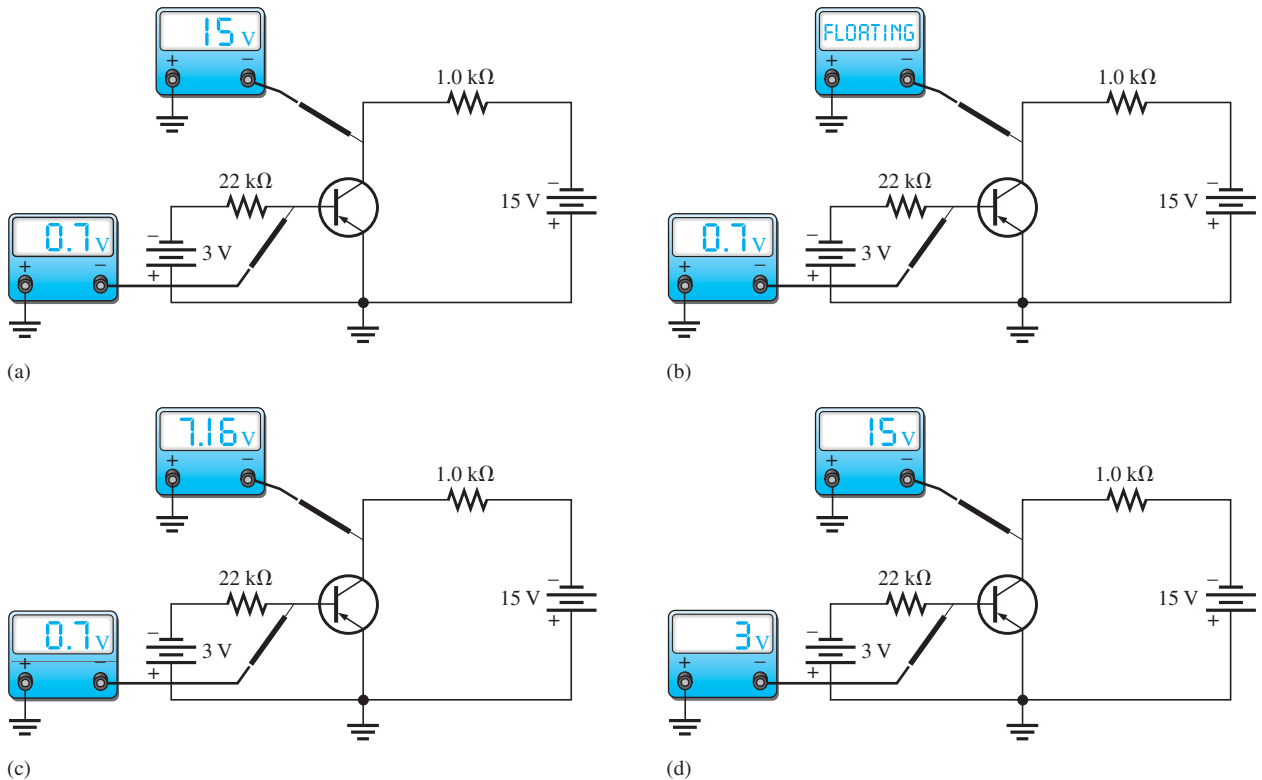


FIGURE 3–81

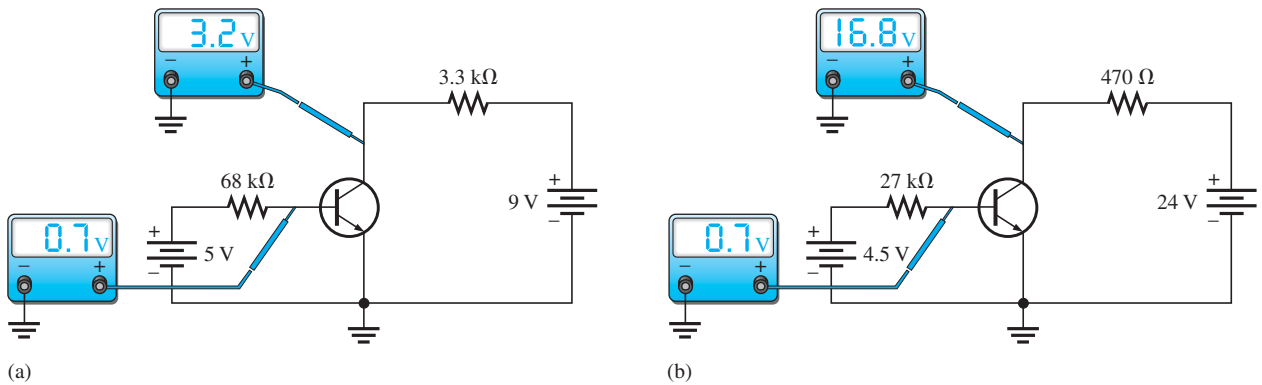


FIGURE 3–82

MULTISIM



MULTISIM TROUBLESHOOTING PROBLEMS

40. Open file P03-40 and determine the fault.
41. Open file P03-41 and determine the fault.
42. Open file P03-42 and determine the fault.
43. Open file P03-43 and determine the fault.
44. Open file P03-44 and determine the fault.
45. Open file P03-45 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 3-1

1. Emitter, base, collector
2. Saturation means there is maximum conduction and the voltage from collector to emitter is close to zero. Cutoff is essentially when there is no collector current and the power supply voltage appears between the collector and the emitter.
3. The ratio of collector current to base current in a bipolar junction transistor

SECTION 3-2

1. Base, collector-feedback, voltage-divider, and emitter
2. The following steps are for an *npn* transistor with a positive supply voltage:
 - (a) Compute the base voltage using the voltage-divider rule.
 - (b) Subtract 0.7 V to obtain the emitter voltage.
 - (c) Apply Ohm's law to the emitter resistor to obtain the approximate collector current.
 - (d) Using the collector current, find the voltage across the collector resistor by Ohm's law.
 - (e) Subtract the drop across the collector resistor from the power supply to obtain the collector voltage.
 - (f) Subtract the emitter voltage from the collector voltage to obtain V_{CE} .
3. Approximately +1 V. (This result assumes the base resistor is connected to ground and drops a few tenths of a volt.)

SECTION 3-3

1. Increases
2. β_{DC} increases with I_C to a certain value and then decreases.
3. Multiply I_C by V_{CE} .
4. 40 mA
5. A coupling capacitor is in series with the signal and passes it to or from a transistor. A bypass capacitor is in parallel with the signal and provides an ac path around a resistor.

SECTION 3-4

1. The input terminal is the base; the output terminal is the collector.
2. High input resistance reduces the loading effect on a source.
3. The ac collector resistance is divided by the ac emitter resistance.

SECTION 3-5

1. Emitter-follower
2. 1.0
3. Current gain, high input resistance, low output resistance
4. A Darlington series pass transistor has very high gain, which reduces the required bias current and produces a more stable zener reference voltage.

SECTION 3-6

1. Yes
2. Very low
3. Improved linearity, gain stability, increased input impedance
4. The CB amplifier is not affected by internal capacitances as much as the CE amplifier because the CB amplifier does not invert the signal and the CE amplifier does.

SECTION 3-7

1. Saturation (on) and cutoff (off)
2. At saturation
3. At cutoff
4. At cutoff
5. Two different switching thresholds

SECTION 3-8

1. Three categories of BJT are small signal/general purpose, power, and RF.
2. Going clockwise from tab: emitter, base, and collector (bottom view).
3. The metal mounting tab or case in power transistors is connected to the collector terminal.

SECTION 3-9

1. First, test it in-circuit.
2. If R_B opens, the transistor is in cutoff.
3. The base voltage is +3 V and the collector voltage is +9 V.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

3-1 $I_B = 0.241 \text{ mA}$, $I_C = 21.7 \text{ mA}$, $I_E = 21.9 \text{ mA}$, $V_{CE} = 4.23 \text{ V}$, $V_{CB} = 3.53 \text{ V}$

3-2 Along the x -axis

3-3 221

3-4 When β_{DC} is 100, V_{CE} is 5.6 V; when β_{DC} is 300, V_{CE} is 3.0 V.

3-5 $V_B = 1.51 \text{ V}$, $V_E = 0.81 \text{ V}$, $I_E = 1.73 \text{ mA}$, $I_C = 1.73 \text{ mA}$, $V_{CE} = 6.51 \text{ V}$

3-6 $V_B = -1.78 \text{ V}$, $V_E = -1.08 \text{ V}$, $I_E = 0.90 \text{ mA}$, $I_C = 0.90 \text{ mA}$, $V_{CE} = -5.88 \text{ V}$

3-7 $V_E = -0.7 \text{ V}$

3-8 $V_{CC(\max)} = 44.5 \text{ V}$; $V_{CE(\max)}$ is exceeded first.

3-9 250Ω

3-10 Gain is reduced to -3.65 .

3-11 $3.15 \text{ k}\Omega$

3-12 No effect on Q-point but the ac load line is steeper; $I_{c(\text{sat})} = 8.1 \text{ mA}$ and $V_{ce(\text{cutoff})} = 12.6 \text{ V}$.

3-13 The voltage gain is still 1.0. The current gain rises to 19.

3-14 2.4 V pp

3-15 -6.99 V

3-16 $78.4 \mu\text{A}$

3-17 R_B is open (this can be due to a broken trace or pad at the contact).

ANSWERS TO SELF-TEST

- | | | | | | | |
|---------|---------|---------|---------|---------|---------|---------|
| 1. (b) | 2. (a) | 3. (c) | 4. (b) | 5. (b) | 6. (d) | 7. (a) |
| 8. (d) | 9. (c) | 10. (c) | 11. (b) | 12. (a) | 13. (a) | 14. (a) |
| 15. (a) | 16. (b) | 17. (a) | 18. (d) | | | |

ANSWERS TO TROUBLESHOOTER'S QUIZ

- | | | | |
|-------------|----------------|----------------|-------------|
| 1. increase | 2. decrease | 3. decrease | 4. decrease |
| 5. increase | 6. decrease | 7. not change | 8. decrease |
| 9. increase | 10. not change | 11. not change | |

CHAPTER 4

FIELD-EFFECT TRANSISTORS (FETs)

OUTLINE

- 4-1 Structure of Field-Effect Transistors
- 4-2 JFET Characteristics
- 4-3 JFET Biasing
- 4-4 MOSFET Characteristics
- 4-5 MOSFET Biasing
- 4-6 FET Linear Amplifiers
- 4-7 MOSFET Switching Circuits
- 4-8 A System

OBJECTIVES

- Describe the basic classifications for field-effect transistors (FETs)
- Describe the construction and operation of junction field-effect transistors (JFETs)
- Describe three bias methods for JFETs and explain how each method works
- Explain the operation of metal-oxide semiconductor field-effect transistors (MOSFETs)
- Discuss and analyze MOSFET bias circuits
- Describe the operation of FET linear amplifiers
- Discuss MOSFET analog and digital switching circuits

KEY TERMS

Field-effect transistor (FET)	Drain
Source	Gate
	Junction field-effect

transistor (JFET)	Depletion mode
Ohmic region	Enhancement mode
Constant-current region	Common-source (CS)
Pinch-off voltage	Common-drain (CD)
Transconductance	Common-gate (CG)
MOSFET	

INTRODUCTION

This chapter introduces the field-effect transistor (FET), a transistor that works on an entirely different principle than the bipolar junction transistor (BJT). Although the idea for the FET precedes the invention of the BJT by decades, it wasn't until the 1960s that commercial production of FETs was possible. For certain applications, the FET is superior to the BJT. In other applications, a mix of the two types produces a circuit with optimum characteristics. There are two basic types of FETs: the junction field-effect transistor (JFET) and the metal-oxide semiconductor FET (MOSFET). Even though the MOSFET is the more common device, we will begin our discussion with JFETs as their construction is simpler and they share many of the same basic characteristics as MOSFETs.

In this chapter, JFETs and MOSFETs are shown in different small systems. Each illustrates an application that takes advantage of the unique characteristics of

VISIT THE WEBSITE

Study aids for this chapter are available at <http://pearsonhighered.com/floyd>

these transistors. In addition, each of the system examples illustrates a different application of field-effect transistors, including both linear and switching circuit applications.

The chapter ends with a section covering a solar tracking system using MOSFET switching transistors.

4–1 STRUCTURE OF FIELD-EFFECT TRANSISTORS (FETs)

Recall that the bipolar junction transistor (BJT) is a current-controlled device; that is, the base current controls the amount of collector current. The field-effect transistor (FET) is a voltage-controlled device in which the voltage at the gate terminal controls the amount of current through the device. Both the BJT and the FET can be used as an amplifier and in switching applications.

After completing this section, you should be able to

- Describe the basic classifications for field-effect transistors (FETs)
- Discuss principal differences between FETs and BJTs

The FET Family

Field-effect transistors (FETs) are a class of semiconductors that operate on an entirely different principle than bipolar transistors. In a FET, a narrow conducting channel is connected to two leads called the **source** and the **drain**. This channel is made from either an *n*-type or *p*-type material. As the name *field-effect* implies, conduction in the channel is controlled by an electric field, established by a voltage applied to a third lead called the **gate**. In a *junction* FET (or JFET), the gate forms a *pn* junction with the channel. The other type of FET, called the *MOSFET* (for *Metal Oxide Semiconductor FET*), uses an insulated gate to control conduction in the channel. (The terms *insulated gate* and *MOSFET* refer to the same type of device.) The insulation is an extremely thin layer ($<1\ \mu\text{m}$) of glass (typically SiO_2). Figure 4–1 is an overview of the FET family, showing the various types available. All of these types are discussed in this chapter.

FETs were actually thought of long before bipolar junction transistors (BJTs). J. E. Lilienfeld applied for a patent for a FET in 1925 (granted in 1930), but it wasn't until the 1960s that FETs became commercially available. Today, MOSFETs are used in most digital integrated circuits (ICs) because of several important advantages they have over BJTs, particularly with respect to manufacturing of large-scale ICs. MOSFETs have become the dominant type of transistor for digital circuits for several reasons. They can be fabricated in much smaller areas than BJTs, they are relatively easy to manufacture on ICs, and they produce simpler circuits with no resistors or diodes. All microprocessors and computer memories use FET technology. A brief look at how FETs are used in certain ICs is included in Section 4–7.

Compared to the BJT, the FET family is more diverse. A characteristic that differs between various types of FETs is their dc behavior. For example, JFETs are biased differently than E-MOSFETs. For this reason, the dc bias characteristics for each type are discussed in this chapter separately. Fortunately, bias circuits are fairly easy to understand. Before proceeding to bias circuits, the characteristics of the transistors that make up the FET family will be discussed.

Common to all FETs is very high input resistance and low electrical noise. In addition, both JFETs and MOSFETs respond the same way to ac signals and have similar ac equivalent circuits. JFETs achieve their high input resistance because the input *pn* junction is always operated with reverse bias; MOSFETs achieve their high input resistance because

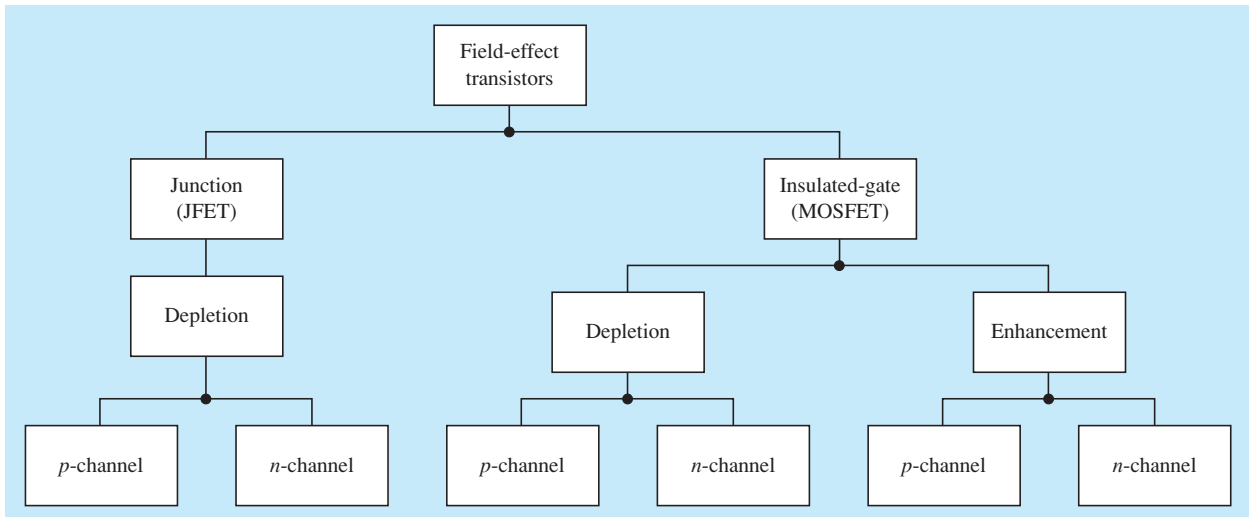


FIGURE 4-1 Classification of field-effect transistors.

of the insulated gate. Although all FETs have high input resistance, they do not have the high gain of bipolar junction transistors. BJTs are also inherently more linear than FETs. For certain applications, FETs are superior; for other applications, BJTs are superior. Many designs take advantage of both types and include a mix of FETs and BJTs. You need to understand both types of transistors.

SECTION 4-1 CHECKUP*

1. What are the three terminals of a FET called?
2. What is another name for an insulated-gate FET?
3. Why are MOSFETs the dominant type of transistor used in ICs?
4. What are some important differences between BJTs and FETs?

*Answers are at the end of the chapter.

4-2 JFET CHARACTERISTICS

In this section, you will see how the JFET operates as a voltage-controlled, constant-current device and study the drain characteristic curve and the transconductance curve. You will also learn about cutoff and pinch-off as well as JFET input resistance and capacitance.

After completing this section, you should be able to

- Describe the construction and operation of junction field-effect transistors (JFETs)
- Draw the symbol for an n -channel or a p -channel JFET
- Interpret the drain characteristic curve for a JFET including the ohmic and constant-current regions
- Explain the parameters g_m , I_{DSS} , I_{GSS} , C_{iss} , $V_{GS(off)}$, and V_P
- Describe the transconductance curve for a JFET and explain how it relates to the drain characteristic curve

 


FIGURE 4-2 Basic structure of the two types of JFET.

JFET Operation

Figure 4-2(a) shows the basic structure of an *n*-channel **junction field-effect transistor (JFET)**. Wire leads are connected to each end of the *n* channel; the drain is shown at the upper end, and the source is at the lower end. This channel is a conductor: for an *n*-channel JFET, electrons are the carrier; for a *p*-channel JFET, holes are the carrier. With no external voltages, the channel can conduct current in either direction.

In an *n*-channel device, a *p* material is diffused into the *n*-channel to form a *pn* junction and is connected to the gate lead. The diagram in Figure 4-2(a) shows *p*-material diffused into two regions that are normally connected internally by the manufacturer to form a single gate. (A special-purpose JFET, called a dual-gate JFET, has a separate lead to each of these regions.) In the structure diagrams, the interconnection of both *p* regions is omitted for simplicity, with a connection to only one shown. A *p*-channel JFET is shown in Figure 4-2(b).

As previously stated, the channel in a JFET is a narrow conduction path between the gate and the source. The width of the channel, and therefore its ability to conduct current, is controlled by the gate voltage. With no gate voltage, the channel conducts the maximum current. When reverse bias is applied to the gate, the channel width narrows, and the conductivity drops.

To illustrate this operation, Figure 4-3(a) shows normal operating voltages applied to an *n*-channel device. V_{DD} provides a positive drain-to-source voltage, causing electrons to flow from the source to the drain. For an *n*-channel JFET, reverse-biasing of the gate-source junction is done with a negative gate voltage. V_{GG} sets the reverse-biased voltage between the gate and the source, as shown. Notice that there should *never* be any forward-biased junctions in a FET; this is one of the principal differences between FETs and BJTs.

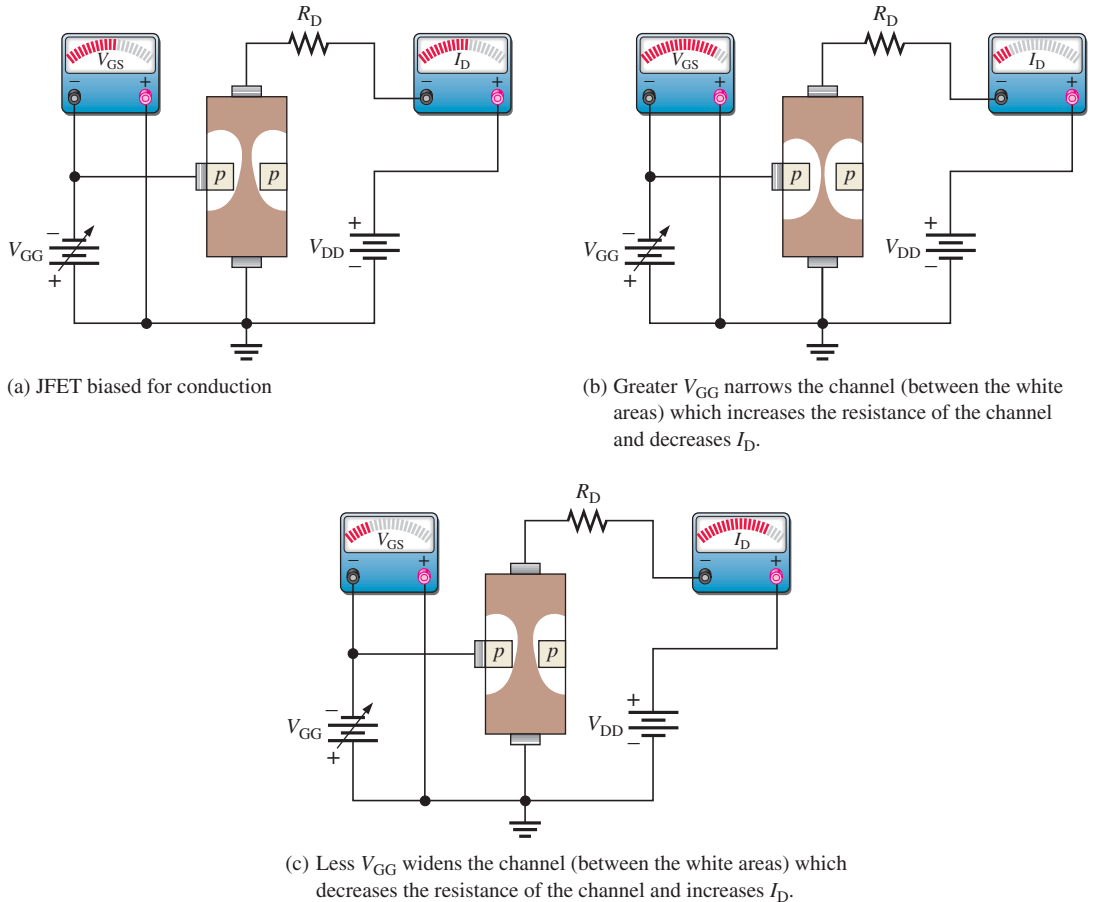


FIGURE 4-3 Effects of V_{GG} on channel width, resistance, and drain current ($V_{GG} = V_{GS}$).

The channel width, and thus the channel resistance, is controlled by varying the gate voltage, thereby controlling the amount of drain current, I_D . This concept is illustrated in Figure 4-3(b) and (c). The white areas represent the depletion region created by the reverse bias. It is wider toward the drain end of the channel because the reverse-biased voltage between the gate and the drain is greater than that between the gate and the source.

JFET Symbols

The schematic symbols for both n -channel and p -channel JFETs are shown in Figure 4-4. Notice that the arrow on the gate points “in” for n -channel and “out” for p -channel.

 


FIGURE 4-4 JFET schematic symbols.

Drain Characteristic Curve

The drain characteristic curve is a plot of the drain current, I_D , versus the drain-to-source voltage, V_{DS} , which corresponds to a BJT’s collector current, I_C , versus collector-to-emitter voltage, V_{CE} . There are, however, some significant differences between BJT characteristics and FET characteristics. Since the FET is a voltage-controlled device, the third variable on the FET characteristic (V_{GS}) has units of voltage instead of current (I_B) in the case of the BJT. The characteristics for n -channel devices are introduced in this section. P -channel devices operate in the same way but with opposite polarities. Generally, n -channel JFETs have better specifications than their p -channel counterparts, so they are more popular.

Consider an n -channel JFET where the gate-to-source voltage is zero ($V_{GS} = 0$ V). This zero voltage is produced by shorting the gate to the source, as in Figure 4-5(a) where both are grounded. As V_{DD} (and thus V_{DS}) is increased from 0 V, I_D will increase proportionally, as shown in the graph of Figure 4-5(b) between points A and B . In this region, the channel resistance is essentially constant because the depletion region is not large enough to have a significant effect. This region is called the **ohmic region** because V_{DS} and I_D are related by Ohm’s law. The value of the resistance can be changed by the gate voltage; thus, it is possible to use a JFET as a voltage-controlled resistor. An application will be shown later in Figure 10-11 (Wien bridge). Further applications are found in Experiments 14, 15, and 27 in the accompanying Laboratory Exercises Manual.

At point B in Figure 4-5(b), the curve levels off and I_D becomes essentially constant. As V_{DS} increases from point B to point C , the reverse-bias voltage from gate to drain (V_{GD}) produces a depletion region large enough to offset the increase in V_{DS} , thus keeping I_D relatively constant. This region is called the **constant-current region**.

 


FIGURE 4-5 The drain characteristic curve of a JFET for $V_{GS} = 0$ V showing pinch-off.

Pinch-Off Voltage

For $V_{GS} = 0$ V, the value of V_{DS} at which I_D becomes essentially constant (point *B* on the curve in Figure 4–5 (b)) is the **pinch-off voltage**, V_P . Notice that the pinch-off voltage is a positive value for an *n*-channel JFET. For a given JFET, V_P has a fixed value. As you can see, a continued increase in V_{DS} above the pinch-off voltage produces an almost constant drain current. This value of drain current is I_{DSS} (Drain to Source current with gate Shorted) and is always specified on JFET data sheets. I_{DSS} is the maximum drain current that a specific JFET can produce regardless of the external circuit, and it is always specified for the condition, $V_{GS} = 0$ V.

Continuing along the graph in Figure 4–5(b), breakdown occurs at point *C* when I_D begins to increase very rapidly with any further increase in V_{DS} . Breakdown can result in irreversible damage to the device, so JFETs are always operated below breakdown and usually within the constant-current region (between points *B* and *C* on the graph). For this reason the constant-current region is also known as the active region.

V_{GS} Controls I_D

Let's connect a bias voltage, V_{GG} , from gate to source as shown in Figure 4–6(a). As V_{GS} is set to increasingly more negative values by adjusting V_{GG} , a family of drain characteristic curves is produced as shown in Figure 4–6(b). Notice that I_D decreases as the magnitude of V_{GS} is increased to larger negative values because of the narrowing of the channel. Also notice that, for each increase in V_{GS} , the JFET reaches pinch-off (where constant current begins) at values of V_{DS} less than V_P . So the amount of drain current is controlled by V_{GS} .

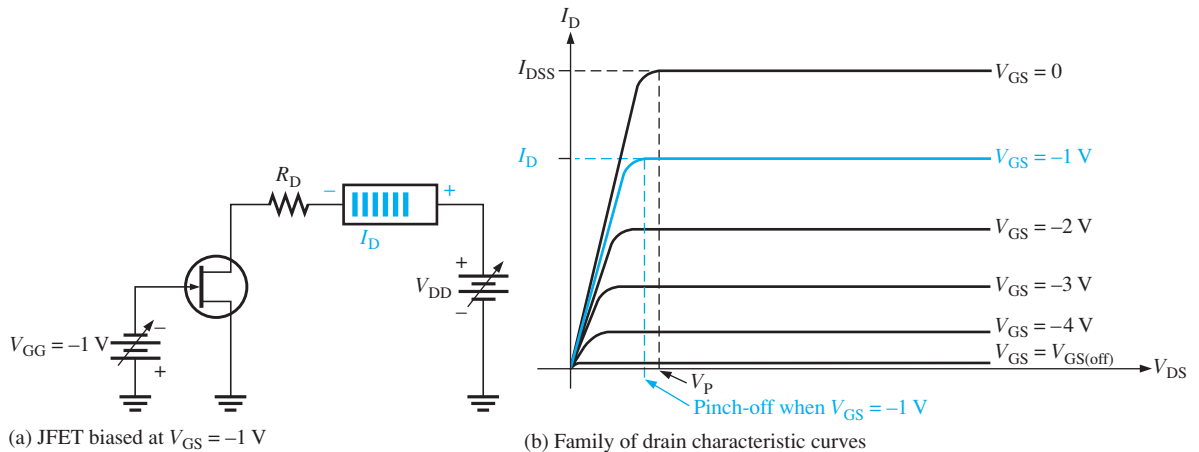


FIGURE 4–6 Pinch-off occurs at a lower V_{DS} as V_{GS} is increased to more negative values.

Cutoff Voltage

The value of V_{GS} that makes I_D approximately zero is the cutoff voltage, $V_{GS(off)}$. The JFET must be operated between $V_{GS} = 0$ V and $V_{GS(off)}$. For this range of gate-to-source voltages, I_D will vary from a maximum of I_{DSS} to a minimum of almost zero.

As you have seen, for an *n*-channel JFET, the more negative V_{GS} is, the smaller I_D becomes in the constant-current region. When V_{GS} has a sufficiently large negative value, I_D is reduced to zero. This cutoff effect is caused by the widening of the depletion region to a point where it completely closes the channel as shown in Figure 4–7.

Comparison of Pinch-Off and Cutoff

The pinch-off voltage is measured on the drain characteristic. For an *n*-channel device, it is the positive voltage at which the drain current becomes constant when $V_{GS} = 0$ V. Cutoff

 


FIGURE 4-7 JFET at cutoff.

can also be measured on the drain characteristic and represents the negative gate-to-source voltage that reduces the drain current to zero.

$V_{GS(off)}$ and V_P are always equal in magnitude but opposite in sign. A data sheet usually will give either $V_{GS(off)}$ or V_P , but not both. However, when you know one, you have the other. For example, if $V_{GS(off)} = -5\text{ V}$, then $V_P = +5\text{ V}$.

EXAMPLE 4-1

For the n -channel JFET in Figure 4-8, $V_{GS(off)} = -4\text{ V}$ and $I_{DSS} = 12\text{ mA}$. Determine the *minimum* value of V_{DD} required to put the device in the constant-current region of operation.

 


FIGURE 4-8

SOLUTION

Since $V_{GS(off)} = -4\text{ V}$, $V_P = 4\text{ V}$. The minimum value of V_{DS} for the JFET to be in its constant-current region is

$$V_{DS} = V_P = 4\text{ V}$$

In the constant-current region with $V_{GS} = 0\text{ V}$,

$$I_D = I_{DSS} = 12\text{ mA}$$

The drop across the drain resistor is

$$V_{R_D} = (12\text{ mA})(560\ \Omega) = 6.7\text{ V}$$

Applying Kirchhoff's law around the drain circuit gives

$$V_{DD} = V_{DS} + V_{R_D} = 4\text{ V} + 6.7\text{ V} = \mathbf{10.7\text{ V}}$$

This is the minimum value of V_{DD} to make $V_{DS} = V_P$ and to put the device in the constant-current region.

PRACTICE EXERCISE*

If V_{DD} is increased to 15 V, what is the drain current?

*Answers are at the end of the chapter.

JFET Transconductance Curves

A useful way of looking at any circuit is to show the output for a given input, as done earlier in Section 1–4 for an amplifier. This characteristic is called a *transfer curve*.

Since the JFET is controlled by a negative voltage on the input (gate) and the output is drain current, the transfer curve is a plot of I_D , plotted on the y -axis, as a function of V_{GS} , plotted on the x -axis. When the output unit (mA) is divided by the input unit (V), the result is the unit of conductance (mS). You can think of a voltage at the input being transferred to the output as a current; thus, the prefix “trans” is added to the word *conductance* to form the word **transconductance**. The transconductance curve is a plot of the transfer characteristic (I_D versus V_{GS}) of a FET. Transconductance is listed in data sheets as g_m or y_{fs} .

A representative curve for an n -channel JFET is shown in Figure 4–9(a). Generally, all types of FETs have a transconductance curve with this same basic shape. The curves shown are typical for the MPF102¹, a general-purpose n -channel JFET.

 


FIGURE 4–9 Representative characteristic curves for an MPF102 n -channel JFET.

The transconductance characteristic is directly related to the drain characteristic as shown in Figure 4–9(b). Notice that both plots have the same vertical axis, representing I_D . Transconductance is an ac parameter so its value is found at any point on the curve by dividing a small change in drain current by a small change in gate-to-source voltage.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

This equation can be written with ac notation as simply

$$g_m = \frac{I_d}{V_{gs}} \quad (4-1)$$

The transconductance curve is not a straight line, implying that the relation between the output current and the input voltage is nonlinear. This is an important point: FETs have a nonlinear transconductance curve. This means that they tend to add distortion to an input signal. Distortion is not always a bad thing; for example, in radio frequency mixers, JFETs have an advantage over BJTs because of this characteristic. However, some JFETs (such as the 2N4339) are designed with physical geometries that minimize distortion for audio applications. In addition, the designer can minimize distortion by keeping the signal level low (below about 100 mV). Other design techniques (such as the biasing method used in System Example 4–2) have been used to minimize distortion.

¹Data sheet for MPF102 available at www.onsemi.com

EXAMPLE 4-2

For the curve in Figure 4-10, determine the transconductance at $I_D = 1.0$ mA.

 


FIGURE 4-10

SOLUTION

Select a small change in I_D and divide it by the corresponding change in V_{GS} at 1.0 mA. The graphical method is shown in Figure 4-10. From the graph, the transconductance is

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{1.25 \text{ mA} - 0.75 \text{ mA}}{-1.1 \text{ V} - (-1.8 \text{ V})} = \mathbf{0.714 \text{ mS}}$$

PRACTICE EXERCISE

Find the transconductance at $I_D = 1.5$ mA.

JFET Input Resistance and Capacitance

As you know, a *pn* junction has a very high resistance when it is reverse-biased. A JFET operates with its gate-source junction reverse-biased; therefore, the input resistance at the gate is very high. This very high input resistance is a major advantage of the JFET over the bipolar junction transistor with its forward-biased base-emitter junction.

JFET data sheets often specify the input resistance by giving a value for the gate reverse current, I_{GSS} , at a certain gate-to-source voltage. The input resistance can then be determined using the following equation. The vertical lines indicate an absolute value (an unsigned value).

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| \quad (4-2)$$

For example, the 2N5457² data sheet lists a maximum I_{GSS} of -1 nA for $V_{GS} = -15$ V at 25°C. Using these values, you find that the input resistance is

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \frac{15 \text{ V}}{1 \text{ nA}} = 15 \text{ G}\Omega$$

As you can see from this result, the input resistance of this JFET is incredibly high. However, R_{IN} drops considerably as temperature increases (as shown in Example 4-3).

²Data sheet for 2N5457 available at www.onsemi.com

The reverse-biased pn junction at the input provides the high input resistance associated with a reverse-biased diode, but it also means that a JFET will generally have higher input capacitance than a bipolar junction transistor. Recall that a reverse-biased pn junction acts as a capacitor whose capacitance depends on the amount of reverse voltage (see Section 2–8). The input capacitance, C_{iss} , of a JFET is greater than that of a BJT because of this reverse-biased pn junction. For example, the 2N5457 has a maximum C_{iss} of 7 pF for $V_{GS} = 0$ V.

EXAMPLE 4–3

The data sheet for an n -channel JFET shows a maximum I_{GSS} of -0.1 nA at 25°C for $V_{GS} = -30$ V and a maximum I_{GSS} of -100 nA at 150°C for $V_{GS} = -30$ V. Determine the minimum input resistance at 25°C .

SOLUTION

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \frac{30 \text{ V}}{0.1 \text{ nA}} = 300 \text{ G}\Omega$$

PRACTICE EXERCISE

Determine the minimum input resistance for this JFET at a temperature of 150°C .

SECTION 4–2 CHECKUP

1. What is another name for the transfer curve for a JFET?
2. Does a p -channel JFET require a positive or a negative voltage for V_{GS} ?
3. How is the drain current controlled in a JFET?
4. The drain-to-source voltage at the pinch-off point of a particular JFET is 7 V. If the gate-to-source voltage is zero, what is V_P ?
5. The V_{GS} of a certain n -channel JFET is increased negatively. Does the drain current increase or decrease?
6. What value must V_{GS} have to produce cutoff in a p -channel JFET with a $V_P = -3$ V?

4–3 JFET BIASING

Using some of the JFET characteristics discussed in the previous section, we will now see how to dc bias JFETs. The purpose of biasing is to select a proper dc gate-to-source voltage to establish a desired value of drain current. Because the gate is reverse-biased, the methods for applying bias with a bipolar junction transistor do not work for JFETs.

After completing this section, you should be able to

- Describe three bias methods for JFETs and explain how each method works
- Use a transconductance curve to choose a reasonable value for a self-bias resistor
- Explain how voltage-divider bias or current-source bias produces a more stable Q-point than self-bias

Self-Biasing a JFET

Biasing a FET is relatively easy. An n -channel JFET is shown for the following examples. Keep in mind that a p -channel JFET just reverses the polarities. To set up reverse bias

requires a negative V_{GS} for an n -channel JFET. This can be achieved using the self-bias arrangement shown in Figure 4-11. Notice that the gate is biased at 0 V by resistor R_G connected to ground. Although reverse leakage current, I_{GSS} , does produce a very tiny voltage across R_G , it is neglected in most cases; it can be assumed that R_G has no current and no voltage drop across it. The purpose of R_G is to tie the gate to a solid 0 V without affecting any ac signal that will be added later. Since the gate current is negligible, R_G can be large (typically 1.0 M Ω or more), resulting in very high input resistance to low frequency ac signals.³

If the gate is at zero volts, how do you obtain the required negative bias on the gate-source junction? The answer is that you make the source *positive* with respect to the gate, producing the required reverse bias. For the n -channel JFET in Figure 4-11, I_D produces a voltage drop across R_S with the polarity shown, making the source terminal positive with respect to ground. Since $V_G = 0$ V, and $V_S = I_D R_S$, the gate-to-source voltage is

$$V_{GS} = V_G - V_S = 0 - I_D R_S$$

Thus,

$$V_{GS} = -I_D R_S$$

This result shows that the gate-to-source voltage is negative, producing the required reverse bias. In this analysis, an n -channel JFET was used for illustration. Again, the p -channel JFET also requires reverse bias, but the polarity of all voltages is opposite those of the n -channel JFET.

The drain voltage with respect to ground is determined as follows:

$$V_D = V_{DD} - I_D R_D \quad (4-3)$$

Since $V_S = I_D R_S$, the drain-to-source voltage is

$$V_{DS} = V_D - V_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \quad (4-4)$$

 


FIGURE 4-11 Self-biased n -channel JFET.

EXAMPLE 4-4

Find V_{DS} and V_{GS} in Figure 4-12. For the particular JFET in this circuit, the internal parameter values such as g_m , $V_{GS(off)}$, and I_{DSS} are such that a drain current (I_D) of approximately 5.0 mA is produced. Another JFET, even of the same type, may not produce the same results when connected in this circuit due to variations in parameter values.

 


FIGURE 4-12

³The capacitance effect at high frequencies can significantly reduce the effective input impedance.

MULTISIM



Open file F04-12 found on the companion website. This simulation demonstrates the variations in circuit values that occur when one device is substituted for another in a self-bias circuit.

SOLUTION

$$V_S = I_D R_S = (5.0 \text{ mA})(220 \Omega) = 1.10 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 10 \text{ V} - (5.0 \text{ mA})(1.0 \text{ k}\Omega) = 5.00 \text{ V}$$

Therefore,

$$V_{DS} = V_D - V_S = 5.00 \text{ V} - 1.10 \text{ V} = \mathbf{3.90 \text{ V}}$$

and

$$V_{GS} = V_G - V_S = 0 \text{ V} - 1.10 \text{ V} = \mathbf{-1.10 \text{ V}}$$

PRACTICE EXERCISE

Determine V_{DS} and V_{GS} in Figure 4–12 when $I_D = 3.0 \text{ mA}$.

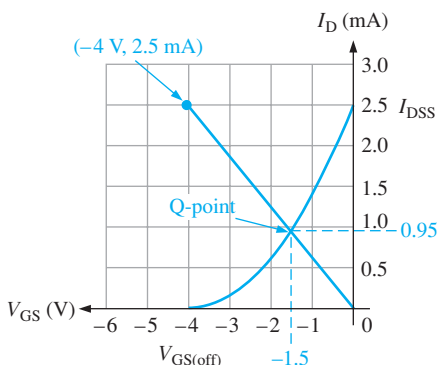


FIGURE 4-13 Graphical analysis of self-bias.

Graphical Methods

Recall that the IV curve for a resistor, R , is a straight line with a slope of $1/R$. To compare the plot of the self-bias resistor with the transconductance curve, both lines are plotted in the second quadrant; the resistance is plotted with a slope of $-1/R$.

The transconductance curve for the MPF3821 can be used to illustrate how a reasonable value of a self-bias resistor (R_S) is selected. Assume you have an MPF3821 with the transconductance curve shown in Figure 4–13. Draw a straight line from the origin to the point where $V_{GS(\text{off})}$ (-4 V) intersects I_{DSS} (2.5 mA). The reciprocal of the slope of this line represents a reasonable choice for R_S .

$$R_S = \frac{|V_{GS(\text{off})}|}{I_{DSS}} = \frac{4 \text{ V}}{2.5 \text{ mA}} = 1.6 \text{ k}\Omega$$

The absolute (unsigned) value of $V_{GS(\text{off})}$ is used. The resulting $1.6 \text{ k}\Omega$ resistor is available as a standard 5% value. The point where the two lines cross represents the Q-point.⁴ This Q-point represents V_{GS} and I_D for this particular case; it shows that $V_{GS} = -1.5 \text{ V}$ at $I_D = 0.95 \text{ mA}$.

Self-bias produces a form of negative feedback to help compensate for different device characteristics between various JFETs. For instance, assume the transistor is replaced with one with a lower transconductance. As a result, the new drain current will be less, causing a smaller voltage drop across R_S . This reduced voltage tends to turn the JFET on more, compensating for the lower transconductance of the new transistor. The effect of a range of transconductance curves is best illustrated by two examples.

EXAMPLE 4-5

A 2N5457 general-purpose JFET has the following specifications: $I_{DSS(\text{min})} = 1 \text{ mA}$, $I_{DSS(\text{max})} = 5 \text{ mA}$, $V_{GS(\text{off})(\text{min})} = -0.5 \text{ V}$, $V_{GS(\text{off})(\text{max})} = -6 \text{ V}$. Select a self-bias resistor for this JFET.

SOLUTION

Typical of small-signal JFETs, the range of I_{DSS} and $V_{GS(\text{off})}$ is very large. To select the best resistor, check the extremes of the specified values $V_{GS(\text{off})}$ and I_{DSS} .

⁴This is a form of load line analysis. This type of load line is called the *bias load line*.

$$R_S = \frac{|V_{GS(off)(min)}|}{I_{DSS(min)}} = \frac{0.5 \text{ V}}{1.0 \text{ mA}} = 500 \Omega$$

$$R_S = \frac{|V_{GS(off)(max)}|}{I_{DSS(max)}} = \frac{6 \text{ V}}{5.0 \text{ mA}} = 1.2 \text{ k}\Omega$$

A good choice is **820 Ω**, a standard value between these extremes. To see what this looks like on the transconductance curve, sketch the curves with this resistor and plot the maximum and minimum Q-points. This is done in Figure 4-14. Despite the extreme variation between the minimum and maximum specification, the 820 Ω resistor represents a good choice for either.

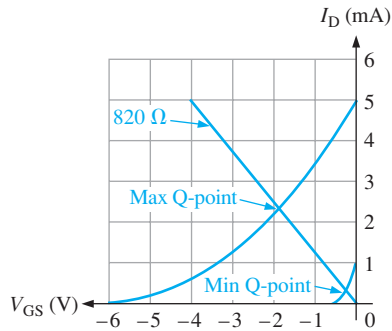



FIGURE 4-14 Effect of a wide range of transconductance curves on the Q-point.

PRACTICE EXERCISE


Estimate the largest and smallest I_D expected for a 2N5457 that is self-biased with an 820 Ω resistor.

 EXAMPLE 4-6


The JFET shown in the circuit of Figure 4-15(a) has the transconductance curve shown in Figure 4-15(b). From the transconductance curve, determine V_S and I_D . Using this result, determine the value of V_{DS} .



(a) Circuit

 

(b) Transconductance curve

 

(c) Transconductance curve with self-bias resistor plotted

FIGURE 4-15

SOLUTION

Plot the line representing a $2.0\text{ k}\Omega$ resistor by selecting the origin and any point on the resistor's line. A convenient point is $V_{GS} = -4\text{ V}$, $I_D = 2\text{ mA}$. The line between the origin and this point represents a $2.0\text{ k}\Omega$ self-bias resistor as shown in Figure 4-15(c).

The intersection of the $2.0\text{ k}\Omega$ resistor and the transconductance curve represents V_{GS} and I_D for this case. Reading the plot, you can see that $V_{GS} = -1.75\text{ V}$ and I_D is **0.85 mA** . Since $V_G = 0\text{ V}$, $V_S = +1.75\text{ V}$.

The voltage across the drain resistor is found by Ohm's law.

$$V_{R_D} = I_D R_D = (0.85\text{ mA})(2.7\text{ k}\Omega) = 2.3\text{ V}$$

To obtain the drain voltage, subtract the previous result from V_{DD} .

$$V_D = V_{DD} - V_{R_D} = 9.0\text{ V} - 2.3\text{ V} = 6.7\text{ V}$$

$$V_{DS} = V_D - V_S = 6.7\text{ V} - 1.75\text{ V} = \mathbf{4.95\text{ V}}$$

Interestingly, this result can be obtained graphically by load line analysis. The load line for the circuit is superimposed on the drain curves (from Figure 4-9(b)) as shown in Figure 4-16.

 


FIGURE 4-16

PRACTICE EXERCISE

Confirm that the load line, drawn in Figure 4-16 represents the circuit in Figure 4-15(a).

 


FIGURE 4-17
Voltage-divider bias

Voltage-Divider Bias

Although self-bias is satisfactory for many applications, the operating point is dependent on the transconductance curve as you have seen. The bias can be made more stable with the addition of a voltage divider on the gate circuit, forcing the gate to a positive voltage. Since the JFET must still operate with a negative gate-source bias, a larger source resistor is used than in normal self-bias. The circuit is shown in Figure 4-17.

The gate voltage is found by applying the voltage-divider rule to R_1 and R_2 .


$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} \quad (4-5)$$

Remember, if you are troubleshooting any JFET circuit, the source voltage has to be equal or larger than the gate voltage. The drain current is in both R_D and R_S . Since I_D is dependent on the transconductance of the JFET, the precise value of V_D and V_S cannot be determined from the circuit values alone because of the manufacturing spread of JFETs. In general, a JFET linear amplifier should be designed such that V_{DS} is in the range from about 25% to 50% of V_{DD} . Even without knowing the parameters for the transistor, you can verify that the bias is set up correctly by checking V_{DS} .

EXAMPLE 4-7

Assume you are troubleshooting the JFET shown in Figure 4-18. You do not know the transconductance of the transistor, but you need to find out if the circuit is working properly.

- Estimate the expected V_G and V_S .
- Assume you measured the source voltage and found it was +5.4 V. Is the circuit functioning as expected? Based on this measurement, what is the drain voltage?
- Assume you replace the transistor. The measured source voltage for the new transistor is +4.0 V. From this measurement, what is the expected drain voltage?

 **FIGURE 4-18****SOLUTION**

- Start with V_G because this value can be computed accurately and quickly with the voltage-divider rule. The gate voltage is about one-fourth of V_{DD} as shown in the following equation:

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{330 \text{ k}\Omega}{1.0 \text{ M}\Omega + 330 \text{ k}\Omega} \right) 12 \text{ V} = \mathbf{2.98 \text{ V}}$$

You know immediately that if the circuit is operating properly, the source voltage must be more positive than this value. Your estimate of the source voltage should be about **+4 V**.

- The measured value of +5.4 V may indicate a problem. This is larger than the expected 4 V and is nearly half of V_{DD} . Since R_D is even larger than R_S , it should drop even more of the total voltage. A quick check of V_{DS} shows that it is 0 V! This confirms a problem with the circuit; there is probably a drain-to-source short in the transistor, causing V_D to also be **5.4 V**.
- The drain current for the new transistor can be found by applying Ohm's law to the source resistor.

$$I_D = \frac{4.0 \text{ V}}{1.8 \text{ k}\Omega} = 2.2 \text{ mA}$$

Subtracting V_{RD} from V_{DD} gives V_D .

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - (2.2 \text{ mA})(2.2 \text{ k}\Omega) = \mathbf{7.16 \text{ V}}$$

PRACTICE EXERCISE

Assume the drain resistor were open in the circuit of Figure 4-18. What voltage do you expect in this case for V_G , V_S , and V_D ?

MULTISIM

Open file F04-18 found on the companion website. This simulation demonstrates the increased stability of voltage-divider bias.

Current Sources

Before discussing current-source biasing, let's review current sources. An ideal current source is a device that provides a fixed current that is independent of any load connected to it. The IV curve for an ideal current source is shown with a horizontal line in Figure 4–19(a). Recall that the slope of an IV curve is inversely proportional to resistance. A horizontal line implies that the internal resistance of the ideal source is infinite. A circuit model of an ideal current source is shown in Figure 4–19(b).

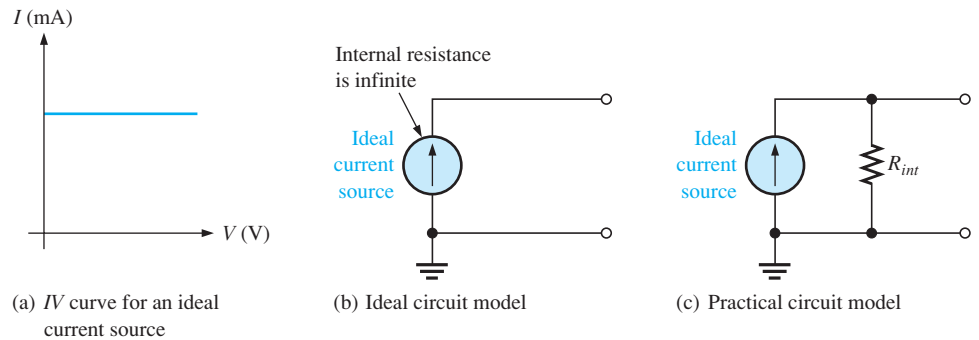


FIGURE 4–19 Current sources. The arrow in the current source symbol always points to the positive side of the source.

As you have seen, both FETs and BJTs have a region called the constant-current region on their characteristic curves. This region is depicted with a nearly horizontal line, representing the internal resistance of the source, which is very high, indeed. For most applications, a FET or a BJT can be assumed to be an ideal current source. In those cases where the internal resistance is taken into account, the Norton model, discussed in Section 1–3, is used. The Norton model for a practical current source is shown in Figure 4–19(c) with the Norton resistance representing the internal resistance of the current source.

Current-Source Biasing

This form of bias is widely used in ICs but requires an extra transistor. One transistor acts as a current source to force I_D to stay constant, creating a very stable form of bias. Current-source biasing also can improve the gain, as you will see later.

Two examples of current-source biasing are shown in Figure 4–20. In Figure 4–20(a), Q_2 is a JFET constant-current source that provides a current to Q_1 . The amount of current is

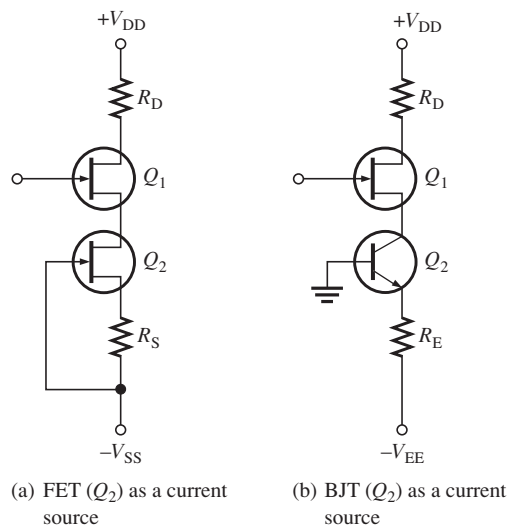


FIGURE 4–20 Current-source biasing.

determined by the I_{DSS} of Q_2 and the value of R_S . Since I_{DSS} varies between transistors, the amount of current depends on the particular transistor that is selected. The current source must *not* provide more current than the I_{DSS} of Q_1 to ensure that the V_{GS} of Q_1 is negative.

For consistency between transistors, the arrangement in Figure 4-20(b) is better. Here the current is provided by a BJT. Since the base is grounded, the emitter voltage will be -0.7 V due to the forward-biased base-emitter junction. This means there is a constant voltage across R_E , thus, a constant current in the JFET. Again, it is important that this current is less than the I_{DSS} of Q_1 .

EXAMPLE 4-8

Figure 4-21 shows a current-source biasing circuit. What is I_D ?

 


FIGURE 4-21

SOLUTION

You should recognize emitter bias for the bipolar junction transistor but with no base resistor. Since the base is connected directly to ground, the emitter voltage is -0.7 V due to the forward-biased base-emitter pn junction. This means that the voltage across R_E is 14.3 V and the current in R_E is constant. From Ohm's law, find the emitter current as

$$I_E = \frac{V_{R_E}}{R_E} = \frac{14.3 \text{ V}}{15 \text{ k}\Omega} = 0.95 \text{ mA}$$

This current is provided to the JFET. Therefore, $I_D = 0.95 \text{ mA}$.

PRACTICE EXERCISE

What is the minimum I_{DSS} for the JFET (for proper operation) in Figure 4-21?

MULTISIM



Open file F04-21 found on the companion website. This simulation demonstrates current source bias.

SECTION 4-3 CHECKUP

1. What two parameters for a JFET could you use to choose a reasonable value of self-bias resistor?
2. Why can't the bias circuits for BJTs be used for JFETs?
3. In a certain self-biased n -channel JFET circuit, $I_D = 8 \text{ mA}$ and $R_S = 1.0 \text{ k}\Omega$. What is V_{GS} ?
4. For a JFET with current-source biasing, what parameter must not be exceeded by the current source?

4-4 MOSFET CHARACTERISTICS

The metal-oxide semiconductor field-effect transistor (MOSFET) is the other major category of field-effect transistors. The MOSFET differs from the JFET in that it has no pn junction structure; instead, the gate of the MOSFET is insulated from the channel by a very thin silicon dioxide (SiO_2) layer. The two basic types of MOSFETs are depletion (D) and enhancement (E). Of the two types of MOSFETs, the E-MOSFET is more widely used. Because polycrystalline silicon is now used for the gate material instead of metal, MOSFETs are sometimes called IGFETs (insulated-gate FETs).

After completing this section, you should be able to

- Explain the operation of metal-oxide semiconductor field-effect transistors (MOSFETs)
- Describe the differences in the construction of MOSFETs
- Draw the symbol for an n -channel or a p -channel D-MOSFET or E-MOSFET
- Explain how a MOSFET functions in the depletion and the enhancement modes
- Interpret the drain characteristic curve for a MOSFET
- Describe the transconductance curve for a MOSFET and explain how it relates to the drain characteristic curve
- Discuss specific handling precautions for MOSFET devices

Depletion MOSFET (D-MOSFET)

One type of **MOSFET** is the depletion MOSFET (D-MOSFET) and Figure 4-22 illustrates its basic structure. The drain and source are diffused into the substrate material and then connected by a narrow channel adjacent to the insulated gate. Both n -channel and p -channel devices are shown in the figure; however, p -channel D-MOSFETs are not widely used. The basic operation is the same for both types, except the voltage polarities for the p -channel device are opposite those of the n -channel. For simplicity, n -channel devices are described in this section.

 


FIGURE 4-22 Basic structure of D-MOSFETs.

The D-MOSFET can be operated in either of two modes—the depletion mode or the enhancement mode—and is sometimes called a *depletion-enhancement MOSFET*. Since the gate is insulated from the channel, either a positive or a negative gate voltage can be applied. The n -channel D-MOSFET operates in the **depletion mode** when a negative gate-to-source voltage is applied and in the **enhancement mode** when a positive gate-to-source voltage is applied. These devices are generally operated in the depletion mode.

DEPLETION MODE Visualize the gate as one plate of a parallel-plate capacitor and the channel as the other plate. The silicon dioxide insulating layer is the dielectric. With a negative gate voltage, the negative charges on the gate repel conduction electrons from the

channel, leaving positive ions in their place. Thereby, the n -channel is depleted of some of its electrons, thus decreasing the channel conductivity. The greater the negative voltage on the gate, the greater the depletion of n -channel electrons. At a sufficiently negative gate-to-source voltage, $V_{GS(off)}$, the channel is totally depleted and the drain current is zero. This depletion mode is illustrated in Figure 4-23(a). Like the n -channel JFET, the n -channel D-MOSFET conducts drain current for gate-to-source voltages between $V_{GS(off)}$ and 0 V. In addition, the D-MOSFET conducts for values of V_{GS} above 0 V.

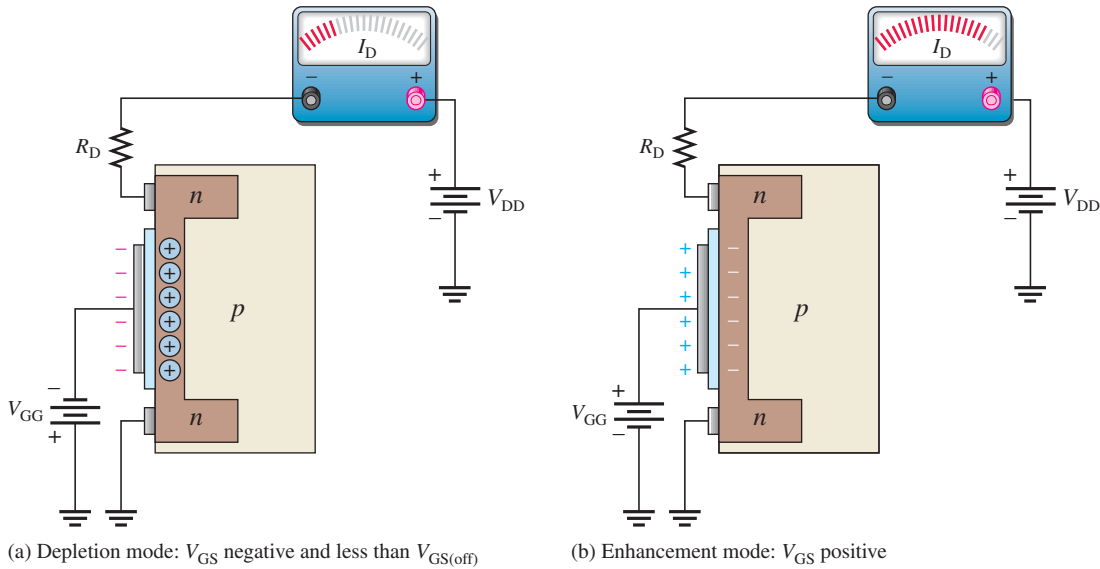


FIGURE 4-23 Operation of n -channel D-MOSFETs.

ENHANCEMENT MODE With an n -channel device and with a positive gate voltage, more conduction electrons are attracted into the channel, thus increasing (enhancing) the channel conductivity, as illustrated in Figure 4-23(b).

D-MOSFET SYMBOLS Figure 4-24 shows the schematic symbols for both the n -channel and the p -channel D-MOSFETs. The substrate, indicated by the arrow, is normally (but not always) connected internally to the source. Sometimes the substrate is brought out as another lead. An inward substrate arrow is for n -channel, and an outward arrow is for p -channel.

 


FIGURE 4-24 D-MOSFET schematic symbols.

Because the MOSFET is a field-effect device like the JFET, you might expect it to have similar characteristics as the JFET. This is indeed the case. The transfer characteristic (I_D versus V_{GS}) for an n -channel D-MOSFET, is shown in Figure 4-25. It has the same shape as the one given earlier for the n -channel JFET (Figure 4-9(a)), but note that both negative and positive values of V_{GS} are shown on the transfer characteristic representing

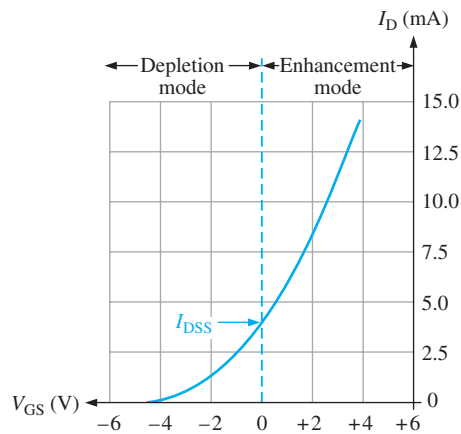


FIGURE 4-25 Transfer characteristic for a D-MOSFET.

operation in the depletion region and the enhancement region, respectively. This particular curve indicates that I_D is approximately 4.0 mA when V_{GS} is 0 V. Since V_{GS} is 0 V, the point is I_{DSS} . Notice that operation with currents higher than I_{DSS} is permissible with a D-MOSFET but not with a JFET.

Enhancement MOSFET (E-MOSFET)

This type of MOSFET operates only in the enhancement mode and has no depletion mode. It differs in construction from the D-MOSFET in that it has no physical channel. Notice in Figure 4-26(a) that the substrate extends completely to the SiO_2 layer.

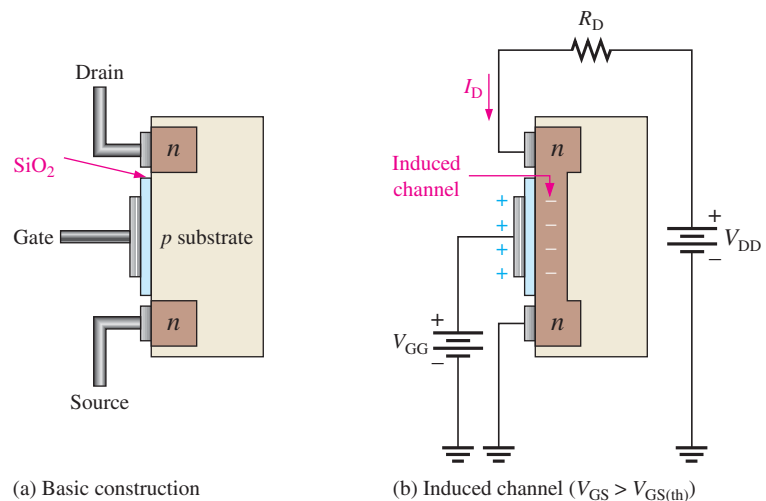


FIGURE 4-26 E-MOSFET construction and operation (n -channel).

For an n -channel device, a positive gate voltage above a threshold value, $V_{GS(th)}$, induces a channel by creating a thin layer of negative charges in the substrate region adjacent to the SiO_2 layer, as shown in Figure 4-26(b). The conductivity of the channel is enhanced by increasing the gate-to-source voltage, thus pulling more electrons into the channel. For any gate voltage below the threshold value, there is no channel.

The schematic symbols for the n -channel and p -channel E-MOSFETs are shown in Figure 4-27. The broken lines symbolize the absence of a physical channel.

Because the channel is closed unless a voltage is applied to the gate, an E-MOSFET can be thought of as a normally-off device. Again the transfer characteristic has the same shape as the JFET and D-MOSFET, but now the gate of an n -channel device must be made positive in order to cause conduction. This means that the $V_{GS(off)}$ specification will be a positive voltage for an n -channel E-MOSFET. A typical characteristic is shown in Figure 4-28. Compare it to the D-MOSFET characteristic in Figure 4-25.

 


FIGURE 4-27 E-MOSFET schematic symbols.

 


FIGURE 4-28 Transfer characteristic for a typical E-MOSFET.

Dual-Gate MOSFETs

The dual-gate MOSFET can be either a depletion or an enhancement type. The only difference is that it has two gates, as shown in Figure 4-29. One drawback of a FET is its high input capacitance, which restricts its use at higher frequencies. By using a dual-gate device, the input capacitance is reduced, thus making the device more useful in high-frequency RF amplifier applications. Another advantage of the dual-gate arrangement is that it allows for an automatic gain control (AGC) input in RF amplifiers. Another application is demonstrated in System Example 4-1 where the bias on the second gate is used to adjust the transconductance curve.

 


FIGURE 4-29 Dual-gate n -channel MOSFET symbols.

A Data Sheet

The partial datasheet for the BF998 D-MOSFET is shown in Figure 4-30. In this application, the MOSFET is used as a dc amplifier. Recall that a D-MOSFET can operate with both positive and negative gate voltages, making it ideal for this particular application where the input voltage can have either polarity. The graph in Figure 4-30 shows that the transconductance curve depends on the value of the voltage on the second gate which, in this particular design, is set at 6 V by the R_1 - R_2 voltage divider. The input from the sensor is applied to the first gate.

Absolute Maximum Ratings

$T_{amb} = 25^{\circ}\text{C}$, unless otherwise specified

Parameter	Test Conditions	Symbol	Value	Unit
Drain - source voltage		V_{DS}	12	V
Drain current		I_D	30	mA
Gate 1/Gate 2 - source peak current		$\pm I_{G1/G2SM}$	10	mA
Gate 1/Gate 2 - source voltage		$\pm V_{G1S/G2S}$	7	V
Total power dissipation	$T_{amb} \leq 60^{\circ}\text{C}$	P_{tot}	200	mW
Channel temperature		T_{Ch}	150	$^{\circ}\text{C}$
Storage temperature range		T_{stg}	-65 to +150	$^{\circ}\text{C}$

Electrical DC Characteristics


$T_{amb} = 25^{\circ}\text{C}$, unless otherwise specified

Parameter	Test Conditions	Type	Symbol	Min	Typ	Max	Unit
Drain - source breakdown voltage	$I_D = 10 \mu\text{A}$, $-V_{G1S} = -V_{G2S} = 4 \text{ V}$		$V_{(BR)DS}$	12			V
Gate 1 - source breakdown voltage	$\pm I_{G1S} = 10 \text{ mA}$, $V_{G2S} = V_{DS} = 0$		$\pm V_{(BR)G1SS}$	7		14	V
Gate 2 - source breakdown voltage	$\pm I_{G2S} = 10 \text{ mA}$, $V_{G1S} = V_{DS} = 0$		$\pm V_{(BR)G2SS}$	7		14	V
Gate 1 - source leakage current	$\pm V_{G1S} = 5 \text{ V}$, $V_{G2S} = V_{DS} = 0$		$\pm I_{G1SS}$			50	nA
Gate 2 - source leakage current	$\pm V_{G2S} = 5 \text{ V}$, $V_{G1S} = V_{DS} = 0$		$\pm I_{G2SS}$			50	nA
Drain current	$V_{DS} = 8 \text{ V}$, $V_{G1S} = 0$, $V_{G2S} = 4 \text{ V}$	BF998/BF998R/ BF998RW	I_{DSS}	4		18	mA
		BF998A/BF998RA/ BF998RAW	I_{DSS}	4		10.5	mA
		BF998B/BF998RB/ BF998RBW	I_{DSS}	9.5		18	mA
Gate 1 - source cut-off voltage	$V_{DS} = 8 \text{ V}$, $V_{G2S} = 4 \text{ V}$, $I_D = 20 \mu\text{A}$		$-V_{G1S(OFF)}$		1.0	2.0	V
Gate 2 - source cut-off voltage	$V_{DS} = 8 \text{ V}$, $V_{G1S} = 0$, $I_D = 20 \mu\text{A}$		$-V_{G2S(OFF)}$		0.6	1.0	V

Electrical AC Characteristics

$V_{DS} = 8 \text{ V}$, $I_D = 10 \text{ mA}$, $V_{G2S} = 4 \text{ V}$, $f = 1 \text{ MHz}$, $T_{amb} = 25^{\circ}\text{C}$, unless otherwise specified

Parameter	Test Conditions	Symbol	Min	Typ	Max	Unit
Forward transadmittance		$ y_{21s} $	21	24		mS
Gate 1 input capacitance		C_{issg1}		2.1	2.5	pF
Gate 2 input capacitance	$V_{G1S} = 0$, $V_{G2S} = 4 \text{ V}$	C_{issg2}		1.1		pF
Feedback capacitance		C_{rss}		25		fF
Output capacitance		C_{oss}		1.05		pF
Power gain	$G_S = 2 \text{ mS}$, $G_L = 0.5 \text{ mS}$, $f = 200 \text{ MHz}$	G_{ps}		28		dB
	$G_S = 3.3 \text{ mS}$, $G_L = 1 \text{ mS}$, $f = 800 \text{ MHz}$	G_{ps}	16.5	20		dB
AGC range	$V_{G2S} = 4 \text{ to } -2 \text{ V}$, $f = 800 \text{ MHz}$	ΔG_{ps}	40			dB
Noise figure	$G_S = 2 \text{ mS}$, $G_L = 0.5 \text{ mS}$, $f = 200 \text{ MHz}$	F		1.0		dB
	$G_S = 3.3 \text{ mS}$, $G_L = 1 \text{ mS}$, $f = 800 \text{ MHz}$	F		1.5		dB

 

12816

FIGURE 4-30 Partial data sheet for a BF998 MOSFET. Data sheet courtesy of Vishay Intertechnology, Inc.

SYSTEM EXAMPLE 4-1

WASTEWATER NEUTRALIZATION SYSTEM

This system example involves electronic instrumentation in a waste water treatment facility. The BF998 dual-gate D-MOSFET will be used as a dc voltage amplifier in the pH sensor circuit. The system controls the amount of acid and base reagent added to waste water in order to neutralize it. The diagram of the waste water neutralization pH system is shown in Figure SE4-1. Our focus is on the pH sensor circuits. The system measures and controls the pH of the water, which is a measure of the degree of acidity or alkalinity. The pH scale ranges from 0 for the strongest acids through 7 for neutral solutions and up to 14 for the strongest bases (caustics). Typically, the pH for waste water ranges from greater than 2 and less than 11. The pH of the water is measured by sensor probes at the inlets and outlets of the tanks. The processor and controller unit uses the inputs from the pH sensor circuits to adjust the amount of acid or base introduced into the neutralization tank. The pH should be 7 at the outlet of the smoothing tank.

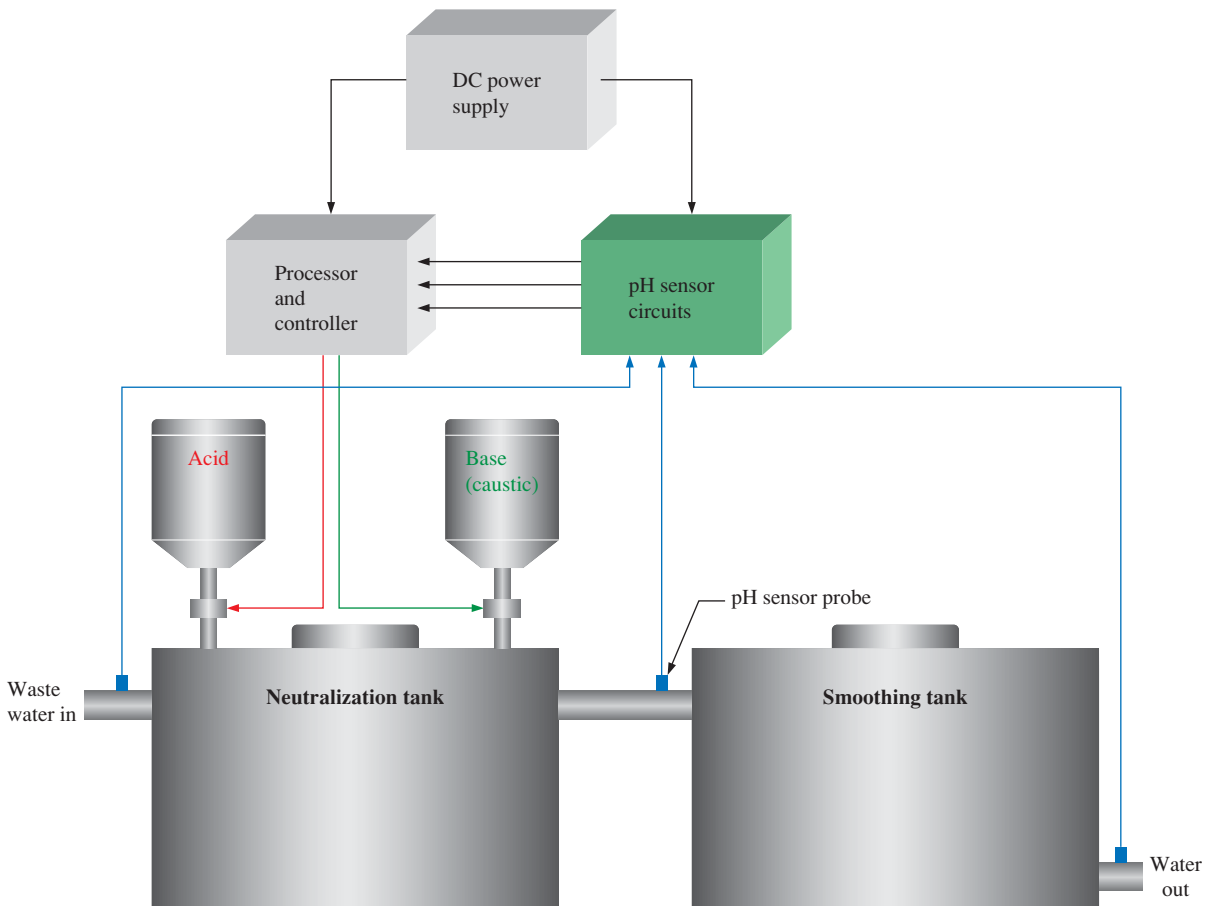
 


FIGURE SE4-1 Simplified waste water pH neutralization system.

Generally, waste water treatment is done in three steps as follows:

- **Primary treatment** Collecting, screening, and initial storage
- **Secondary treatment** Removal of solids and the majority of contaminants using filters, coagulation, flocculation, and membranes
- **Tertiary treatment** Polishing, pH adjustment, carbon treatment to remove taste and smells, disinfection, and temporary storage to allow the disinfecting agent to work

In this example, we are focusing on the process of pH adjustment in the tertiary stage of treatment.

The Sensor Circuit

There are three identical pH sensor circuits, one for each of the inlet/outlets indicated in Figure SE4-1. The pH sensor produces a small voltage (mV) proportional to the pH of the water in which it is immersed. The pH sensor produces a negative voltage if the water is acidic, no voltage if it is neutral, and a positive voltage if it is basic. The sensor output goes to the gate of a MOSFET circuit, which amplifies the sensor voltage for processing by the digital controller.

Figure SE4-2 shows the pH sensor probe and a graph of output voltage versus pH. Figure SE4-3 is the sensor circuit using a BF998 dual-gate *n*-channel MOSFET. A rheostat in the drain of the MOSFET is used to calibrate the circuit so that each of the three sensor circuits produce the same output voltage for a given value of pH. Notice that the voltage on G_2 , which controls the transconductance is set by the voltage divider consisting of R_1 and R_2 .

 


FIGURE SE4-2 pH sensor and graph of pH vs. output voltage.

 


FIGURE SE4-3 pH sensor circuit.

Simulation

The PH sensor circuit is simulated in Multisim and the results for a series of sensor input voltage are shown in Figure SE4-4. The sensor is modeled as a dc source in series with an internal resistance. The output of the circuit increase as the sensor input decreases. Rheostat R_3 is used to calibrate each of the three sensor circuit so that they have an identical output voltage for a given sensor input voltage.

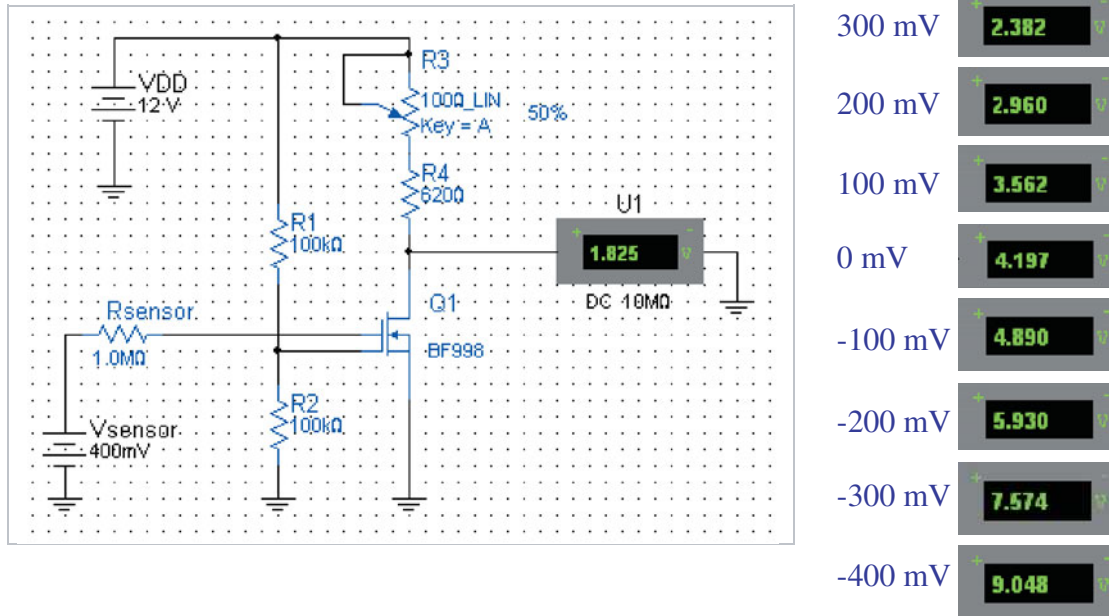


FIGURE SE4-4

Handling Precautions

Because the gate of a MOSFET is insulated from the channel, the input resistance is extremely high (ideally infinite). The gate leakage current, I_{GSS} , for a typical MOSFET is in the pA range, whereas the gate reverse current for a typical JFET is in the nA range. The input capacitance, of course, results from the insulated gate structure. Excess static charge can accumulate because the input capacitance combines with the very high input resistance and can result in damage to the device as a result of electrostatic discharge (ESD). In fact, ESD is the single largest cause of failure with MOSFET devices. To avoid ESD and possible damage, the following precautions should be taken:

1. Metal-oxide semiconductor (MOS) devices should be shipped and stored in conductive foam.
2. All instruments and metal benches used in assembly or testing should be connected to earth ground (round prong of wall outlets).
3. The assembler's or handler's wrist should be connected to earth ground with a length of wire and a high-value series resistor.
4. Never remove a MOS device (or any other device, for that matter) from the circuit while the power is on.
5. Do not apply signals to a MOS device while the dc power supply is off.

SECTION 4-4 CHECKUP

1. Name two types of MOSFETs, and describe the major difference in construction.
2. If the gate-to-source voltage in a D-MOSFET is zero, is there current from drain to source?
3. If the gate-to-source voltage in an E-MOSFET is zero, is there current from drain to source?
4. Can a D-MOSFET have a higher current than I_{DSS} and remain within the specified drain current?

4-5 MOSFET BIASING

As with BJTs and JFETs, bias establishes the appropriate dc operating conditions that provide a stable operating point for centering the ac signal. MOSFET biasing circuits are similar to those you have already seen for BJTs and JFETs. The particular bias circuit depends on whether one or two supplies are used and the type of MOSFET (depletion or enhancement).

After completing this section, you should be able to

- Discuss and analyze MOSFET bias circuits
 - Explain why a D-MOSFET has more bias options than any other type of transistor
 - Explain zero bias
 - Discuss three methods for biasing an E-MOSFET

 


FIGURE 4-31 A zero-biased D-MOSFET.

D-MOSFET Bias

As you know, D-MOSFETs can be operated with either positive or negative values of V_{GS} . When V_{GS} is negative, operation is in the depletion mode; when it is positive, operation is in the enhancement mode. A D-MOSFET has the advantage of being able to operate in both modes; it is the only type of transistor that can do this.


ZERO BIAS The most basic bias method is to set $V_{GS} = 0$ V so that an ac signal at the gate varies the gate-to-source voltage above and below this bias point. Figure 4-31 shows the circuit. Because it is effective and simple, it is the preferred method for biasing a D-MOSFET. The operating point is set between depletion and enhancement operation. Since $V_{GS} = 0$ V, $I_D = I_{DSS}$, as indicated. The drain-to-source voltage is expressed as follows:

$$V_{DS} = V_{DD} - I_{DSS}R_D$$

EXAMPLE 4-9

Determine the drain-to-source voltage in the circuit of Figure 4-32. The MOSFET data sheet gives $I_{DSS} = 12$ mA.

FIGURE 4-32

 

SOLUTION

Since $I_D = I_{DSS} = 12$ mA, the drain-to-source voltage is

$$V_{DS} = V_{DD} - I_{DSS}R_D = 18 \text{ V} - (12 \text{ mA})(560 \Omega) = \mathbf{11.28 \text{ V}}$$

PRACTICE EXERCISE

Find V_{DS} in Figure 4-32 when $I_{DSS} = 20$ mA.

OTHER BIAS ARRANGEMENTS As you know, the D-MOSFET can operate in the depletion or enhancement mode. Because of this versatility, any of the bias circuits you have studied for the BJT and the JFET can also be applied to D-MOSFETs. Figure 4-33 illustrates three popular methods for biasing, but you may see other methods in practice.

The bias circuit in Figure 4-33(a) uses a combination of voltage divider and self-bias as seen earlier with JFETs. The voltage at the gate is computed by the voltage-divider formula, which is quite accurate for any FET device because of the negligible loading effect. The gate voltage is the same as given for JFETs (see Equation (4-5)):

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$$

The resistors that form the voltage divider are usually quite large (in the megohm range) because of the high input resistance of the gate terminal. The voltages at the other terminals depend on specific device parameters.

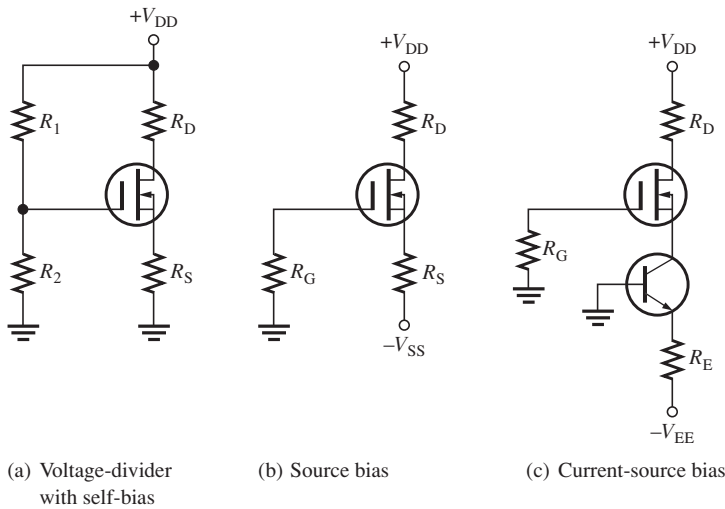


FIGURE 4-33 Other D-MOSFET bias circuits.

When positive and negative supplies are used, the source-bias arrangement in Figure 4-33(b) is frequently used. This is similar to emitter bias seen with BJTs. Ideally, the gate circuit looks like an open circuit, so you would expect the gate voltage to be at ground potential.

Current-source biasing is a form of bias that is common in operational amplifiers and is shown with a BJT current source in Figure 4-33(c). Other current sources, including FETs can be used. The current source sets the value of the source and drain current. By analyzing the current source (as in Example 4-8), the expected drop across the drain resistor can be computed from Ohm's law.

E-MOSFET Bias

E-MOSFETs must have a V_{GS} greater than the threshold value, $V_{GS(th)}$. Any of the bias circuits developed for BJTs (except base bias) could be used with appropriate values for E-MOSFETs. Figure 4-34 shows two common ways to bias an n -channel E-MOSFET. (D-MOSFETs can also be biased using these methods.) In either the drain-feedback or the voltage-divider bias arrangement, the purpose is to make the gate voltage more positive than the source by an amount exceeding $V_{GS(th)}$.

In the drain-feedback bias circuit in Figure 4-34(a), there is negligible gate current and, therefore, no voltage drop across R_G . As a result, $V_{GS} = V_{DS}$.

The voltage-divider bias is a straight forward application of the voltage-divider rule you have already seen. Again, the voltage divider

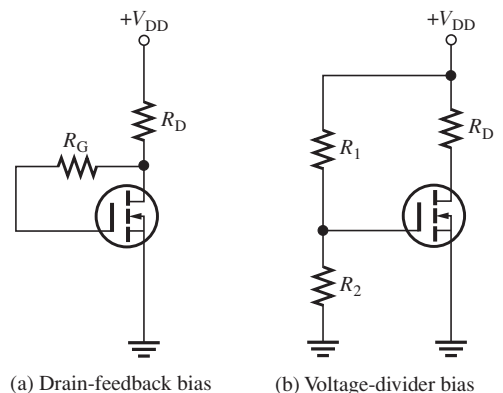



FIGURE 4-34 E-MOSFET biasing arrangements.

appears to be unloaded because of the high input resistance, so you can compute the gate voltage accurately using Equation (4-5).

EXAMPLE 4-10

Determine the amount of drain current in Figure 4-35. The E-MOSFET has a $V_{GS(th)}$ of 3 V.

FIGURE 4-35

 

SOLUTION

The meter indicates that $V_{GS} = 8.5$ V. Since this is a drain-feedback configuration, $V_{DS} = V_{GS} = 8.5$ V.

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{15 \text{ V} - 8.5 \text{ V}}{4.7 \text{ k}\Omega} = 1.38 \text{ mA}$$

PRACTICE EXERCISE

Determine I_D if the meter in Figure 4-35 reads 5 V.

MULTISIM



Open file F04-35 found on the companion website. This simulation demonstrates drain-feedback bias.

 


FIGURE 4-36 IGBT schematic symbol.


The IGBT

The IGBT (insulated gate bipolar transistor) is a device that has the input characteristics of a MOSFET and the output characteristics of a BJT. Its schematic symbol is shown in Figure 4-36. Essentially, the IGBT can be viewed as a voltage-controlled BJT. Because it has an insulated gate instead of a base, there is no input current and it will not load down a driving circuit. IGBTs are superior to MOSFETs in some ways and superior to BJTs in others. They are used primarily in high-voltage high-current switching applications.

It is not an easy task to determine when a given system should use IGBTs or MOSFETs. The applications overlap in a variety of areas. Here are some general guidelines.

For voltages below 200 V, systems usually employ MOSFETs—above 1000 V expect IGBTs. For voltages between 200 V and 1000 V and frequencies below 20 kHz, IGBTs will be used more often. For voltages between 200 V and 1000 V, and frequencies from 20 kHz to 200 kHz, either device may be used. For frequencies above 200 kHz and voltages below 1000 V, expect to find MOSFETs used in the system.

SYSTEM NOTE

 

SECTION 4-5 CHECKUP

- For a D-MOSFET biased at $V_{GS} = 0$ V, is the drain current equal to 0, I_{GSS} , or I_{DSS} ?
- Why can't an E-MOSFET use zero bias?
- For an n -channel E-MOSFET with $V_{GS(th)} = 2$ V, V_{GS} must be in excess of what value in order to conduct?
- What is a common application for IGBTs?

4-6 FET LINEAR AMPLIFIERS

Although MOSFETs are primarily used in switching applications, both JFETs and MOSFETs can be used as linear amplifiers in any of three circuit configurations similar to the bipolar junction transistor's CE, CC, and CB amplifiers you studied earlier. The FET configurations are common-source (CS), common-drain (CD), and common-gate (CG). The CS and CD amplifiers are characterized by high input impedance and low noise, making them excellent choices as the first stage of an amplifier. The common-gate amplifier has few applications, so it is discussed only briefly here.

After completing this section, you should be able to

- Describe the operation of FET linear amplifiers
- Describe the three FET configurations for linear amplifiers: common-source (CS), common-drain (CD), and common-gate (CG)
- Given the transconductance, compute the gain for any FET amplifier
- Explain why a CD amplifier with current-source biasing is significantly better than a single-stage CD amplifier

Transconductance of FETs

The transfer characteristic for a FET is the transconductance curve as was shown in Figure 4-9(a). FETs are fundamentally different than BJTs because they are voltage-controlled devices. The output drain *current* is controlled by the input gate *voltage*. As an ac parameter, transconductance was earlier defined as

$$g_m = \frac{I_d}{V_{gs}}$$

Considered in terms of output current (I_d) divided by input voltage (V_{gs}), transconductance is essentially the gain of the FET by itself. Unlike β_{ac} , a pure number, transconductance (g_m) has units of the siemen (the reciprocal of resistance). Many data sheets continue to use the older unit, the mho (ohm spelled backwards). The transconductance of a particular FET can be measured directly as shown in Figure 4-37(a). Notice that the transconductance is the slope of the transfer curve and it is *not* a constant, but depends on the drain current.

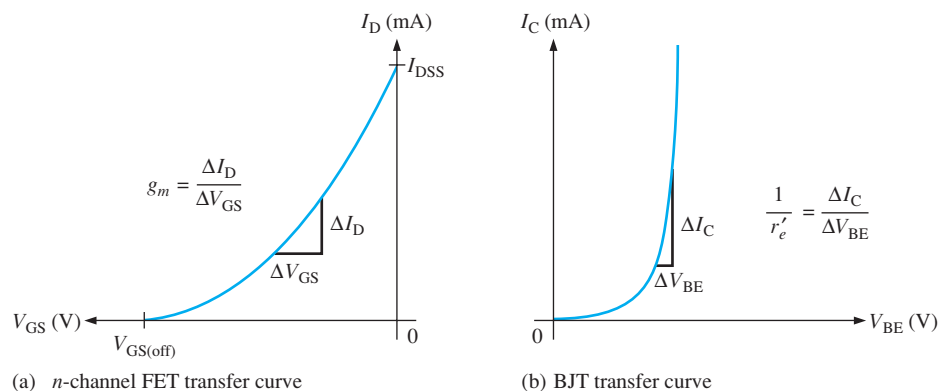


FIGURE 4-37 Comparison of the transfer curve for an *n*-channel FET with a BJT.

Figure 4-37(b) shows an analogous situation for the input to a BJT. The base voltage, applied across the base-emitter *pn* junction, “sees” an ac resistance that depends on the dc emitter current. This small ac resistance plays an important role in determining the gain of a BJT amplifier as you saw in Section 3-4.

The reciprocal of g_m is analogous to r_e' for BJTs. Most ac models for a FET use g_m as one of the key parameters; however, to make the transition from BJT amplifiers to FET amplifiers, it is useful to define a parameter representing the ac source resistance of the FET.

$$r_s' = \frac{1}{g_m} \quad (4-6)$$

 


FIGURE 4-38 The internal source resistance r_s' is analogous to r_e' for a BJT. The dotted line is a reminder that gate current is negligible because of extremely high input resistance.

The concept of r_s' leads to voltage gain equations that are analogous to those developed in Chapter 3 for BJTs. A mental picture of r_s' for a JFET is shown in Figure 4-38. The gate is shown with a dotted line to remind you that, from the gate's perspective, the input resistance is nearly infinite (because of the input's reverse-biased diode). Although the gate voltage controls the drain current, it does it with negligible current. Unfortunately, r_s' for a FET is not as predictable as r_e' is for a BJT and it is generally larger than r_e' . Data sheets don't show this parameter, but they do show a range of values for g_m (also shown as y_{fs}), so you can obtain an approximate value of r_s' by taking the reciprocal of the typical value of g_m . For example, if y_{fs} is shown as $2000 \mu\text{S}$ on a data sheet, $r_s' = 500 \Omega$.

Common-Source Amplifiers

JFET Figure 4-39 shows a **common-source (CS)** amplifier with a self-biased n -channel JFET. An ac source is capacitively coupled to the gate. The resistor, R_G , serves two purposes: (a) It keeps the gate at approximately 0 V dc (because I_{GSS} is extremely small), and (b) its large value (usually several megohms) prevents loading of the ac signal source. The bias voltage is created by the drop across R_S . The bypass capacitor, C_2 , keeps the source of the FET effectively at ac ground.

 


FIGURE 4-39 JFET common-source amplifier.

 


FIGURE 4-40 Zero-biased D-MOSFET common-source amplifier.

The signal voltage causes the gate-to-source voltage to swing above and below its Q-point value, causing a swing in drain current. As the drain current increases, the voltage drop across R_D also increases, causing the drain voltage (with respect to ground) to decrease.

The drain current swings above and below its Q-point value in phase with the gate-to-source voltage. The drain-to-source voltage swings above and below its Q-point value 180° out of phase with the gate-to-source voltage, as illustrated in Figure 4-39.

D-MOSFET Figure 4-40 shows a zero-biased n -channel D-MOSFET with an ac source capacitively coupled to the gate. The gate is at approximately 0 V dc and the source terminal is at ground, thus making $V_{GS} = 0 \text{ V}$.

The signal voltage causes V_{gs} to swing above and below its 0 value, producing a swing in I_d . The negative swing in V_{gs} produces the depletion mode, and I_d decreases. The positive swing in V_{gs} produces the enhancement mode, and I_d increases.

E-MOSFET Figure 4-41 shows a voltage-divider biased, n -channel E-MOSFET with an ac signal source capacitively coupled to the gate. The gate is biased with a positive voltage such that $V_{GS} > V_{GS(th)}$. As with the JFET and D-MOSFET, the signal voltage produces a swing in V_{gs} above and below its Q-point value. This swing, in turn, causes a swing in I_d . Operation is entirely in the enhancement mode.

 


FIGURE 4-41 Common-source E-MOSFET amplifier with voltage-divider bias.

VOLTAGE GAIN Voltage gain, A_v , of an amplifier always equals V_{out}/V_{in} . In the case of the CS amplifier, V_{in} is equal to V_{gs} (due to the bypass capacitor) and V_{out} is equal to the signal voltage developed across R_d , the ac drain resistance. In a CS amplifier with no load, the ac and dc drain resistances are equal: $R_d = R_D$. Thus, $V_{out} = I_d R_d$.

$$A_v = \frac{V_{out}}{V_{in}} = \frac{I_d R_d}{V_{gs}}$$

Since $g_m = I_d/V_{gs}$, the common-source voltage gain is

$$A_v = -g_m R_d \tag{4-7}$$

This is the traditional voltage gain equation for the CS amplifier. The negative sign is added to Equation (4-7) to indicate that it is an inverting amplifier. The gain for the CS amplifier can be expressed in a similar form to the common-emitter (CE) amplifier as a ratio of ac resistances. By substituting $1/r'_s$ for g_m , the voltage gain can be written as

$$A_v = -\frac{R_d}{r'_s} \tag{4-8}$$

Compare this result with Equation (3-10) that gives the voltage gain for a CE amplifier: $A_v = -R_c/R_e$. Both equations show voltage gain as a ratio of ac resistances.

INPUT RESISTANCE Because the input to a CS amplifier is at the gate, the input resistance to the transistor is extremely high. As you know, this extremely high resistance is produced by the reverse-biased pn junction in a JFET and by the insulated gate structure in a MOSFET. For practical work, the transistor's input circuit looks open.

When the transistor's internal resistance is ignored, the input resistance seen by the signal source is determined only by the bias resistor (or resistors). With self-bias, it is simply the gate resistor, R_G , as shown in the equivalent ac circuit looking into the gate in Figure 4-42.

 


FIGURE 4-42 Input resistance is determined by the bias resistors.

With voltage-divider bias, the power supply is at ac ground and the gate again appears as an open. The two voltage-divider resistors are seen by the ac source in parallel. The input resistance is the parallel combination of R_1 and R_2 .

$$R_{in} \cong R_1 \parallel R_2$$

EXAMPLE 4-11

- (a) What is the dc drain voltage and the ac output voltage of the amplifier in Figure 4-43? The g_m is $1500 \mu\text{S}$, I_D is 2.0 mA , and $V_{GS(\text{off})}$ is 3 V .
 (b) What is the input resistance seen by the signal source?

 


FIGURE 4-43

SOLUTION

- (a) First, find the dc drain voltage.

$$V_D = V_{DD} - I_D R_D = 15 \text{ V} - (2 \text{ mA})(3.3 \text{ k}\Omega) = \mathbf{8.4 \text{ V}}$$

Next, find the voltage gain.

$$A_v = -g_m R_d = -(1500 \mu\text{S})(3.3 \text{ k}\Omega) = -5.0$$

Alternatively, the voltage gain could be found by computing r'_s and using the ratio of ac drain resistance to ac source resistance.

$$r'_s = \frac{1}{g_m} = \frac{1}{1500 \mu\text{S}} = 667 \Omega$$

$$A_v = -\frac{R_d}{r'_s} = -\frac{3.3 \text{ k}\Omega}{667 \Omega} = -5.0$$

The ac output voltage is the gain times the input voltage.

$$V_{out} = A_v V_{in} = (-5.0)(100 \text{ mV}) = \mathbf{-0.5 \text{ V rms}}$$

The negative sign indicates the output waveform is inverted.

- (b) The input resistance is

$$R_{in} \cong R_G = \mathbf{10 \text{ M}\Omega}$$

PRACTICE EXERCISE

What happens to the g_m if the source resistor is made larger? Does this affect the gain?

Common-Drain (CD) Amplifier

A **common-drain (CD)** JFET amplifier is shown in Figure 4-44 with voltages indicated. Self-biasing is used in this circuit. The input signal is applied to the gate through a coupling capacitor, and the output is at the source terminal. There is no drain resistor. This circuit, of course, is analogous to the BJT emitter-follower and is sometimes called a *source-follower*. It is a widely used FET circuit because of its very high input impedance.

 


FIGURE 4-44 JFET common-drain amplifier (source-follower).

VOLTAGE GAIN As in all amplifiers, the voltage gain is $A_v = V_{out}/V_{in}$. Like the emitter-follower, the source-follower has an ideal voltage gain of 1, but in practice it is less (typically between 0.5 and 1.0). To compute the voltage gain, the voltage-divider rule can be applied to the circuit shown in Figure 4-45(a). First, the circuit is simplified to the ac equivalent shown in Figure 4-45(b). The gate resistor does not affect the ac, so it is not shown. The load and source resistors are in parallel and can be combined to form an equivalent ac source resistance, R_s , that is in series with the internal resistance r'_s (or $1/g_m$). The input is across both R_s and r'_s , but the output is taken across R_s only. Therefore, the output voltage is

$$V_{out} = V_{in} \left(\frac{R_s}{r'_s + R_s} \right)$$

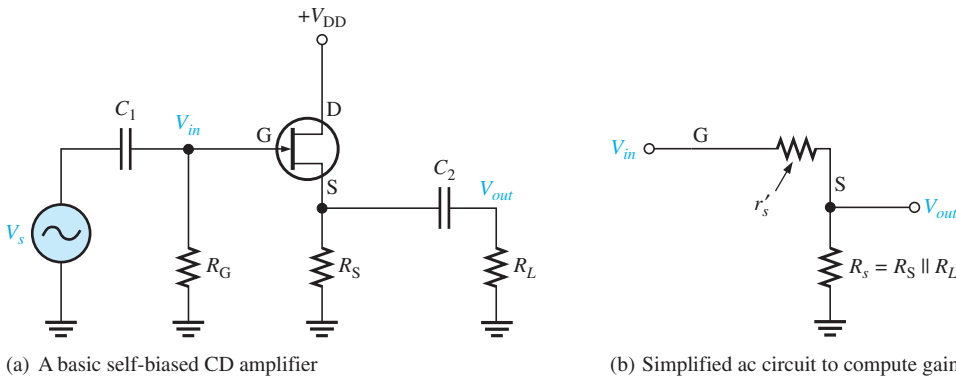


FIGURE 4-45

Dividing by V_{in} results in the equation for voltage gain.

$$A_v = \frac{R_s}{r'_s + R_s} \tag{4-9}$$

Again, note that gain can be written as a ratio of ac resistances. This equation is easy to recall if you keep in mind that it is based on the voltage-divider rule.

An alternate voltage-gain equation, derived in Appendix A, is as follows:

$$A_v = \frac{g_m R_s}{1 + g_m R_s} \tag{4-10}$$

This formula yields the same result as Equation (4-9).

INPUT RESISTANCE Because the input signal is applied to the gate, the input resistance seen by the input signal source is the same as the CS-amplifier configuration

discussed previously. For practical work, you can ignore the very high resistance of the transistor's input. The input resistance is determined by the bias resistor or resistors as done with the CS amplifier. For self-bias, the input resistance is equal to the gate resistor R_G .


$$R_{in} \cong R_G$$

With voltage-divider bias, the voltage-divider resistors are seen by the source as a parallel path to ground. Thus for voltage-divider bias, the input resistance is

$$R_{in} \cong R_1 \parallel R_2$$

 EXAMPLE 4-12

Determine the minimum and maximum voltage gain of the amplifier in Figure 4-46(a) based on the data sheet information in Figure 4-46(b).



(a)

Electrical Characteristics ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF Characteristics				
Gate-Source breakdown voltage ($I_G = 10 \mu\text{A}$ dc, $V_{DS} = 0$)	$V_{(BR)GSS}$	20	–	V dc
Gate-Source cutoff voltage ($V_{DS} = -10$ V dc, $I_D = 1.0 \mu\text{A}$ dc)	$V_{GS(off)}$	0.7	10	V dc
Gate-reverse current ($V_{GS} = 15$ V dc, $V_{DS} = 0$) ($V_{GS} = 15$ V dc, $V_{DS} = 0$, $T_A = 65^\circ\text{C}$)	I_{GSS}	–	10	nA dc
		–	0.5	μA dc
ON Characteristics				
Zero-Gate voltage drain current* ($V_{DS} = -10$ V dc, $V_{GS} = 0$)	I_{DSS}	3.0	30	mA dc
Gate-source voltage ($V_{DS} = -10$ V dc, $I_D = 0.3$ mA dc)	V_{GS}	0.4	9.0	V dc
Small-Signal Characteristics				
Drain-Source "ON" resistance ($V_{GS} = 0$, $I_D = 0$, $f = 1.0$ kHz)	$r_{ds(on)}$	–	700	Ohms
Forward-transadmittance* ($V_{DS} = -10$ V dc, $V_{GS} = 0$, $f = 1.0$ kHz)	$ y_{fs} $	2000	8000	μmhos
Forward-transconductance ($V_{DS} = -10$ V dc, $V_{GS} = 0$, $f = 1.0$ MHz)	$\text{Re}(y_{fs})$	1500	–	μmhos
Output admittance ($V_{DS} = -10$ V dc, $V_{GS} = 0$, $f = 1.0$ kHz)	$ y_{os} $	–	100	μmhos
Input capacitance ($V_{DS} = -10$ V dc, $V_{GS} = 0$, $f = 1.0$ MHz)	C_{iss}	–	20	pF
Reverse transfer capacitance ($V_{DS} = -10$ V dc, $V_{GS} = 0$, $f = 1.0$ MHz)	C_{rss}	–	5.0	pF
Common-Source noise figure ($V_{DS} = -10$ V dc, $I_D = 1.0$ mA dc, $R_G = 1.0$ Megohm, $f = 100$ Hz)	NF	–	5.0	dB
Equivalent short-circuit input noise voltage ($V_{DS} = -10$ V dc, $I_D = 1.0$ mA dc, $f = 100$ Hz, BW = 15 Hz)	E_n	–	0.19	$\mu\text{V}/\sqrt{\text{Hz}}$

*Pulse test: Pulse width ≤ 630 ms, Duty cycle $\leq 10\%$

(b)

FIGURE 4-46

SOLUTION

On the data sheet, g_m is shown as y_{fs} . The range is $2000 \mu\text{S}$ to $8000 \mu\text{S}$ (shown as $2000 \mu\text{mhos}$ on the data sheet). The maximum value of r'_s is

$$r'_s = \frac{1}{g_m} = \frac{1}{2000 \mu\text{S}} = 500 \Omega$$

The ac source resistance, R_s , is simply the load resistor, R_L , which is R_S . Substituting into Equation (4-9), the minimum voltage gain is

$$A_{v(\min)} = \frac{R_s}{r'_s + R_s} = \frac{10 \text{ k}\Omega}{500 \Omega + 10 \text{ k}\Omega} = \mathbf{0.95}$$

The minimum value of r'_s is

$$r'_s = \frac{1}{g_m} = \frac{1}{8000 \mu\text{S}} = 125 \Omega$$

The maximum voltage gain is then

$$A_{v(\max)} = \frac{R_s}{r'_s + R_s} = \frac{10 \text{ k}\Omega}{125 \Omega + 10 \text{ k}\Omega} = \mathbf{0.99}$$

Notice that the gain is slightly less than 1. When r'_s is small compared to the ac source resistance, then a good approximation is $A_v = 1$. Since the output voltage is at the source, it is in phase with the gate (input) voltage.

PRACTICE EXERCISE

Determine the approximate input resistance seen by the source for the amplifier in Figure 4-46(a).

CD AMPLIFIER WITH CURRENT-SOURCE BIASING The CD amplifier can be improved significantly by the addition of a current source as shown in Figure 4-47. The current source not only provides bias (as described in Section 4-3) but also acts as the load for the CD amplifier. As you know, a current source looks like a very high resistance to the ac signal, so the voltage gain is very close to the ideal value of 1.0.

The current source load offers other significant advantages including higher input resistance, lower distortion, and the ability to dc couple the signal at both the input and output (no coupling capacitors). The output voltage from a regular source-follower (such as given in the previous example) is riding on a dc level that is equal to the magnitude of V_{GS} (since the gate is at 0 V). For a p -channel device, the dc offset is negative; for an n -channel device, it is positive. Ideally, current-source biasing does not add *any* dc offset to the output. This is particularly useful in applications such as the preamp to an oscilloscope that must pass any dc component of the signal to the rest of the vertical amplifier.

For optimum results, the two FETs and two resistors in Figure 4-47 should match. This means that both transistors will have identical transfer and output characteristics. Both transistors will have the same V_{GS} (since they have the same drain current). This drain current drops the same voltage (V_{GS} again) across both resistors, compensating for the bias. This ensures that the output will be close to 0 V when the input is 0 V. One way to ensure matching transistors is to use a dual device (two matching transistors in one package).

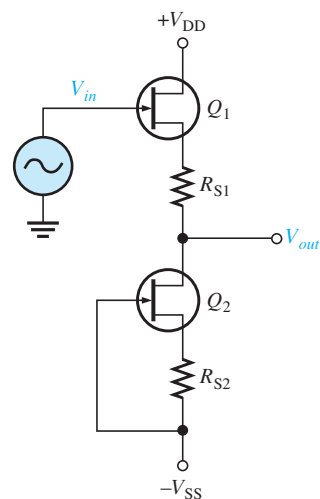


FIGURE 4-47 CD amplifier with current-source bias.

EXAMPLE 4-13

Determine the drain current, I_D , and the source voltage, V_S , of Q_1 for the CD amplifier with current-source bias shown in Figure 4-48(a). Assume the FETs are matched and each has a transconductance curve as shown in Figure 4-48(b).


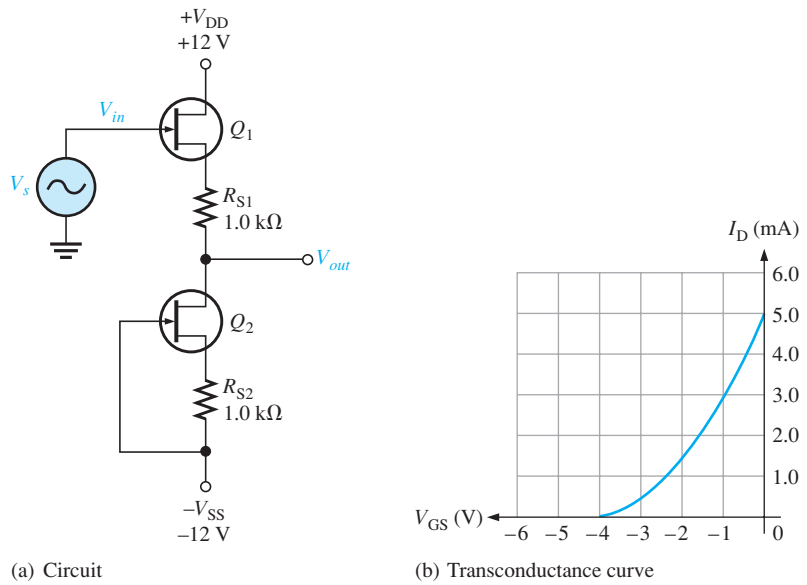


FIGURE 4-48

SOLUTION

On the transconductance curve draw a line representing the 1.0 kΩ bias resistor for the current source (Q_2). This is shown in Figure 4-49. The crossing point indicates that I_D is approximately **1.8 mA** at V_{GS} of **-1.8 V**. This current in R_{S1} causes the source of Q_1 to be at **+1.8 V**.

FIGURE 4-49

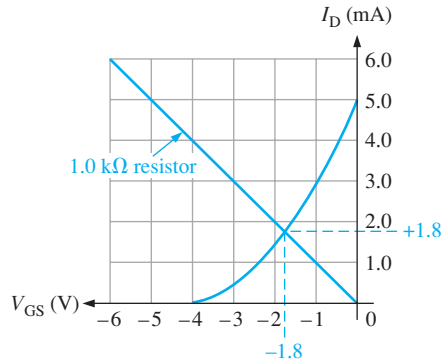

PRACTICE EXERCISE

Determine I_D and $V_{S(Q1)}$ if both resistors are changed to 2.0 kΩ.

Common-Gate Amplifier

As mentioned in the section introduction, the **common-gate (CG)** amplifier has limited use by itself, but it is used in the second stage of a FET differential amplifier (discussed in Chapter 6). It also has application at high frequencies. Although it has a voltage gain comparable to the CD amplifier, the input resistance is low, cancelling one of the major advantages of FETs. A basic CG amplifier is shown in Figure 4-50. The input signal is applied to the source terminal through C_1 and taken from the drain terminal through C_2 . The voltage gain is the same as that of a CS amplifier but with no phase inversion.

$$A_v = \frac{R_d}{r'_s}$$

 


FIGURE 4-50 JFET common-gate amplifier.

An alternate gain formula is

$$A_v = g_m R_d$$

The principal advantage of FETs for linear applications is their high input resistance. Looking into the CG amplifier, you see the source resistor in parallel with r'_s . Usually the source resistor is large enough to ignore; therefore, the input resistance is approximately

$$R_{in} \cong r'_s$$

Alternatively, the input resistance is approximately

$$R_{in} \cong \frac{1}{g_m}$$

This result shows why the CG amplifier has low input resistance.

One application for the common-gate configuration is the cascode amplifier. A cascode amplifier is one in which a common-source and a common-gate amplifier are connected in series. A JFET cascode amplifier is shown in Figure 4-51(a). A low-voltage cascode amplifier using two matched D-MOSFETs is shown in Figure 4-51(b). Cascode amplifiers are used primarily in RF (radio frequency) applications.

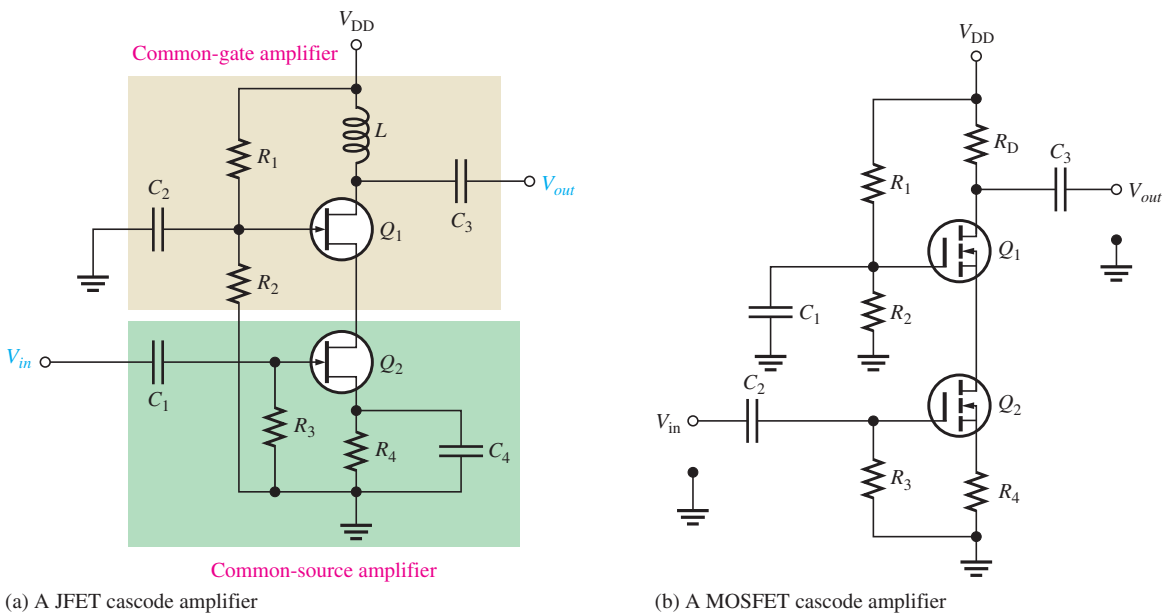


FIGURE 4-51

SYSTEM EXAMPLE 4-2



A TEMPERATURE MEASURING SYSTEM

The block diagram for a typical RTD instrumentation system is shown in Figure SE4-5. The input is from the RTD and is a very small voltage; the output of the system is a current representing the temperature. The preamplifier (in yellow) is our focus. The functions of other blocks will be covered in later chapters. A preamp is an electronic amplifier designed to amplify a small signal before the main part of a system. Preamps are used in many different types of systems and are normally positioned as closely as possible to the signal source to increase the signal before it is contaminated by any noise. Although it is common to think of a preamp as a part of a higher end stereo system, they are also used in instrumentation systems for amplifying the output from a sensitive device like a thermocouple or resistance temperature detector (RTD).


 


FIGURE SE4-5 A temperature measuring system

JFET Preamp

The circuit shown in Figure SE4-6 is a high-input resistance, low-noise dc coupled preamplifier that is used in the system. It uses both FETs and BJTs to take advantage of the best characteristics of both. It is designed to boost input signals of 1 mV or lower from a low level source such as an RTD that requires a dc output. The input signal is applied to a common-source JFET amplifier with current-source biasing as described in Section 4-6. These two transistors should be matched so that the dc voltage at the base of Q_3 is 0 V. This

FIGURE SE4-6 Low-noise preamplifier.

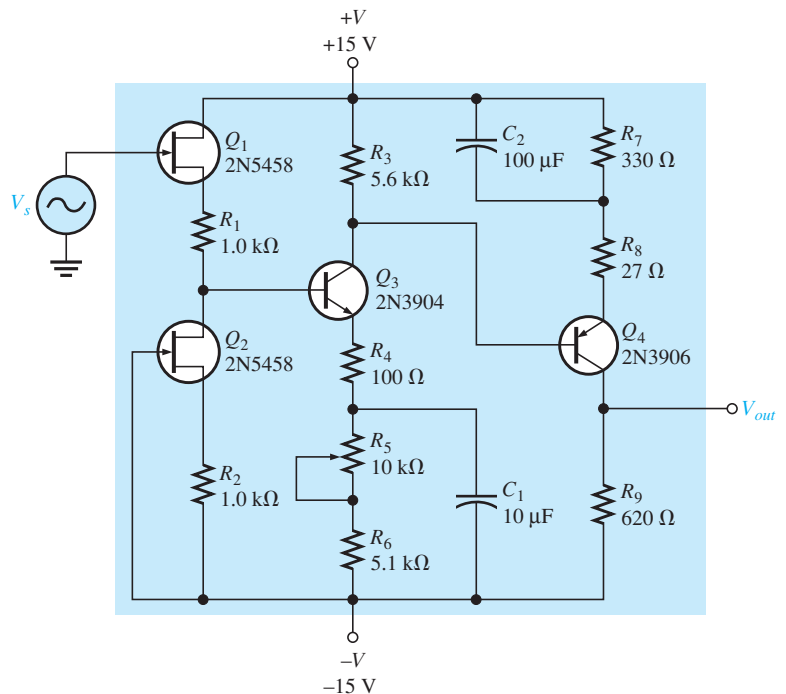

means that no coupling capacitor is required. There are also no bias resistors or coupling capacitor between the collector of Q_3 and the base of Q_4 . The entire circuit is direct coupled. The dc voltage at the base of Q_4 is set by the emitter current of Q_3 and can be adjusted using R_5 . The purpose of the Q_3 common-emitter stage is to provide additional gain and to move the output dc level back to 0 V.

MOSFET Preamp

Figure SN4-1 shows a single channel MOSFET preamp for a higher level signal input such as from a tuner, CD, or DVD player. It is ac coupled so is not a good choice for a dc source such as a temperature transducer. Figure SE4-6 is one channel of a high-voltage high-biased stereo audio preamp. It is a very simple design, with only one E-MOSFET stage. Although designed primarily for switching applications, the IRF510 works quite well as a linear amplifier. R_1 , R_2 , and R_3 set the gate voltage to about 8 V. V_{GS} is close to 4 V and I_D is just over 40 mA. The gate input resistor R_4 is included to suppress oscillations. The zener diode D_1 prevents the gate-to-source rating of the MOSFET from being exceeded.


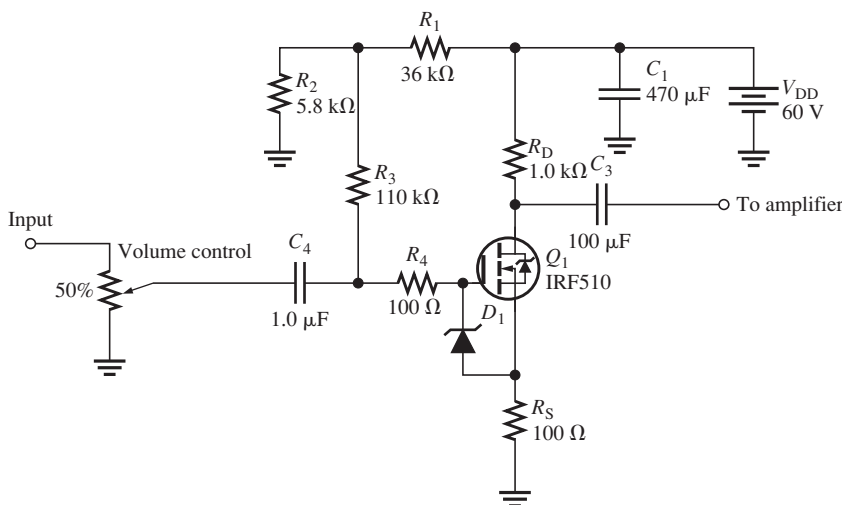


FIGURE SN4-1 A simple one-channel MOSFET preamplifier.

SYSTEM NOTE

 

SECTION 4-6 CHECKUP

1. How is the gain computed for a CS amplifier?
2. What are the principal advantages of a CD amplifier with current-source biasing over a single-stage CD amplifier?
3. Which of the three configurations (CS, CD, or CG) do not invert the input signal?
4. What is the principal disadvantage of a CG amplifier?
5. Which characteristics of FETs make them excellent choices for the first stage of an amplifier?

4-7 MOSFET SWITCHING CIRCUITS

Although both BJTs and JFETs can be used in switching circuits, the MOSFET is now the device of choice for most switching applications. MOSFETs make excellent switching devices because they have very low on-resistance, very high off-resistance, and fast switching times. There are two basic types of MOSFET switching circuits: analog and digital. In this section we will examine both analog and digital MOSFET switching circuits.

After completing this section, you should be able to

- Describe how MOSFETs are used in both analog and digital switching applications
 - Explain how a MOSFET acts like a switch
 - Describe a MOSFET analog switch
 - Discuss analog switch applications
 - Describe a switched capacitor circuit
 - Describe how MOSFETs are used in digital switching applications
 - Discuss complementary MOS (CMOS) logic
 - Explain the operation of several CMOS digital gates
 - Discuss several power MOSFET structures

MOSFET Switching Operation

E-MOSFETs are generally used for switching applications because of their threshold characteristic, $V_{GS(th)}$. When the gate-to-source voltage is less than the threshold value, the MOSFET is *off*. When the gate-to-source voltage is greater than the threshold value, the MOSFET is *on*. When V_{GS} is varied between $V_{GS(th)}$ and $V_{GS(on)}$, the MOSFET is being operated as a switch, as illustrated in Figure 4-52. In the *off* state, when $V_{GS} < V_{GS(th)}$, the device is operating at the lower end of the load line and acts like an open switch (very high R_{DS}). When V_{GS} is sufficiently greater than $V_{GS(th)}$, the device is operating at the upper end of the load line in the ohmic region and acts like a closed switch (very low R_{DS}).

 


FIGURE 4-52 Switching operation on the load line.

THE IDEAL SWITCH Refer to Figure 4-53(a). When the gate voltage of the *n*-channel MOSFET is $+V$, the gate is more positive than the source by an amount exceeding $V_{GS(th)}$. The MOSFET is *on* and appears as a closed switch between the drain and

source. When the gate voltage is zero, the gate-to-source voltage is 0 V. The MOSFET is *off* and appears as an open switch between the drain and source.

Refer to Figure 4-53(b). When the gate voltage of the *p*-channel MOSFET is 0 V, the gate is less positive than the source by an amount exceeding $V_{GS(th)}$. The MOSFET is *on* and appears as a closed switch between the drain and source. When the gate voltage is +V, the gate-to-source voltage is 0 V. The MOSFET is *off* and appears as an open switch between the drain and source.

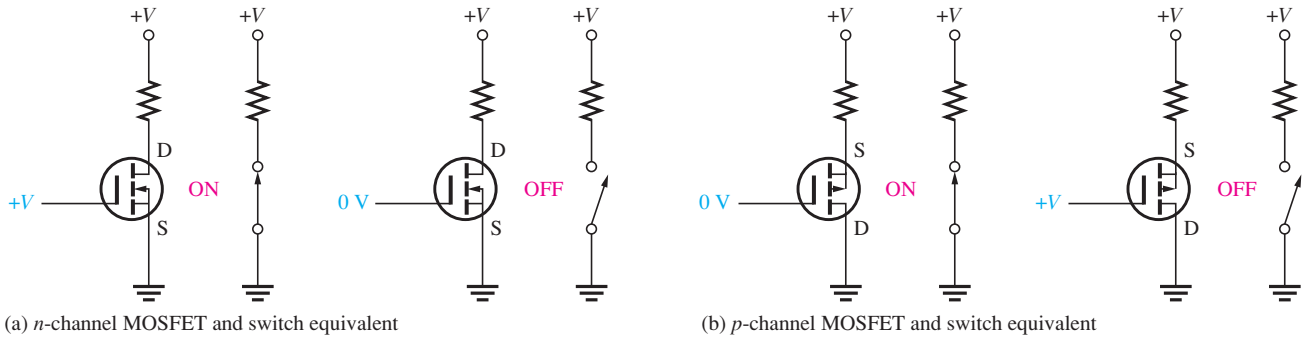


FIGURE 4-53 The MOSFET as a switch.

The Analog Switch

MOSFETs are commonly used for switching analog signals. Basically, a signal applied to the drain can be switched through to the source by a voltage on the gate. A major restriction is that the signal level at the source must not cause the gate-to-source voltage to drop below $V_{GS(th)}$.

A basic *n*-channel MOSFET analog switch is shown in Figure 4-54. The signal at the drain is connected to the source when the MOSFET is turned on by a positive V_{GS} and is disconnected when V_{GS} is 0, as indicated.

 


FIGURE 4-54 Operation of an *n*-channel MOSFET analog switch.

When the analog switch is *on*, as illustrated in Figure 4-55, the minimum gate-to-source voltage occurs at the negative peak of the signal. The difference in V_G and $-V_{p(out)}$ is the gate-to-source voltage at the instant of the negative peak and must be equal to or greater than $V_{GS(th)}$ to keep the MOSFET in conduction.

$$V_{GS} = V_G - V_{p(out)} \geq V_{GS(th)}$$

 


FIGURE 4-55 Signal amplitude is limited by $V_{GS(th)}$.

EXAMPLE 4-14

A certain analog switch similar to the one shown in Figure 4-55 uses an n -channel MOSFET with $V_{GS(th)} = 2\text{ V}$. A voltage of $+5\text{ V}$ is applied at the gate to turn the switch *on*. Determine the maximum peak-to-peak input signal that can be applied, assuming no voltage drop across the switch.

SOLUTION

The difference between the gate voltage and the negative peak of the signal voltage must equal or exceed the threshold voltage. For maximum $V_{p(out)}$,

$$\begin{aligned} V_G - V_{p(out)} &= V_{GS(th)} \\ V_{p(out)} &= V_G - V_{GS(th)} = 5\text{ V} - 2\text{ V} = 3\text{ V} \\ V_{pp(in)} &= 2V_{p(out)} = 2(3\text{ V}) = \mathbf{6\text{ V}} \end{aligned}$$

PRACTICE EXERCISE

What would happen if $V_{p(in)}$ exceeded the maximum value?

Analog Switch Applications

SAMPLING CIRCUIT One application of analog switches is in analog-to-digital conversion. The analog switch is used in a *sample-and-hold* circuit to sample the input signal at a certain rate. Each sampled signal value is then temporarily stored on a capacitor until it can be converted to a digital code by an analog-to-digital converter (ADC). To accomplish this, the MOSFET is turned *on* for short intervals during one cycle of the input signal by pulses applied to the gate. The basic operation, showing only a few samples for clarity, is illustrated in Figure 4-56.

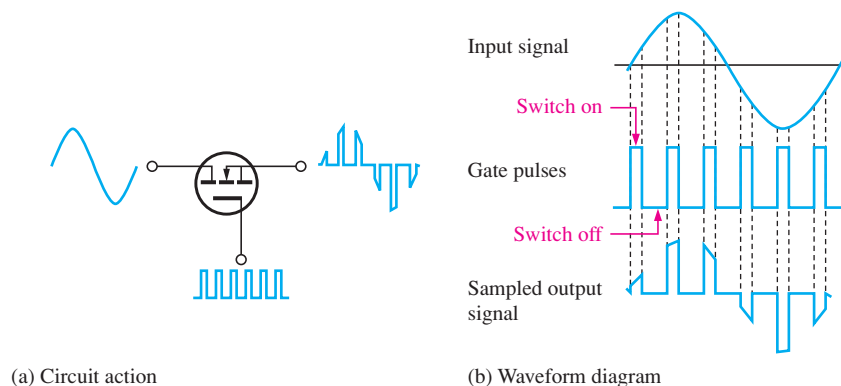


FIGURE 4-56 The analog switch operating as a sampling circuit.

The minimum rate at which a signal can be sampled and reconstructed from the samples must be more than twice the maximum frequency contained in the signal. The minimum sampling frequency is called the *Nyquist frequency*.

$$f_{\text{sample (min)}} > 2f_{\text{signal (max)}}$$

When a gate pulse is at its high level, the switch is turned *on* and the small portion of the input waveform occurring during that pulse appears on the output. When the pulse waveform is at its 0 V level, the switch is turned *off* and the output is also at 0 V .

ANALOG MULTIPLEXER Analog multiplexers are used where two or more signals are to be routed to the same destination. For example, a two-channel analog sampling multiplexer is shown in Figure 4-57. The MOSFETs are alternately turned *on* and *off* so that first one signal sample is connected to the output and then the other. The pulses are applied to the gate of switch A, and the inverted pulses are applied to the gate of switch B. A digital circuit known as an *inverter* is used for this. When the pulses are high, switch A is *on* and switch B is *off*. When the pulses are low, switch B is *on* and switch A is *off*. This is called *time-division multiplexing* because signal A appears on the output during time intervals when the pulse is high and signal B appears during the time intervals when the pulse is low. That is, they are interleaved on a time basis for transmission on a single line.

 


FIGURE 4-57 The analog multiplexer is alternately sampling two signals and interleaving them on a single output line.

SWITCHED-CAPACITOR CIRCUIT Another application of MOSFETs is in **switched-capacitor circuits** commonly used in integrated circuit programmable analog devices known as *analog signal processors*. Because capacitors can be implemented in ICs more easily than a resistor, they are used to emulate resistors. Capacitors also take up less space on a chip than an IC resistor and dissipate no power. Many types of analog circuits use resistors to determine voltage gain and other characteristics and by using switched capacitors to emulate resistors, dynamic programming of analog circuits can be achieved.

For example, in a certain type of IC amplifier circuit that you will study later, two external resistors are required as shown in Figure 4-58. The values of these resistors establish the voltage gain of the amplifier as $A_v = R_2/R_1$.

 


FIGURE 4-58 A type of IC amplifier.

A switched-capacitor can be used to emulate a resistor as shown in Figure 4-59 using a mechanical switch analogy (MOSFETs are actually used as the switches). Switch 1 and switch 2 are alternately turned *on* and *off* at a certain frequency to charge or discharge C , depending on the values of the voltage sources. In the case of R_1 in Figure 4-58, V_{in} and V_1

 


FIGURE 4-59 A switched capacitor emulates a resistance.

are represented by V_A and V_B , respectively. For R_2 , V_1 and V_{out} are represented by V_A and V_B , respectively.

It can be shown that the capacitor emulates a resistance with a value that depends on the frequency at which the switches are turned *on* and *off* and the capacitance value.

$$R = \frac{1}{fC}$$

By changing the frequency, the effective resistance value can be altered.

Complementary E-MOSFETs and capacitors can be used to replace the resistors in the amplifier, as shown in Figure 4-60. When Q_1 is *on*, Q_2 is *off*, and vice versa. The frequency f_1 and C_1 are selected to provide the required value of R_1 . Likewise, f_2 and C_2 provide the required value of R_2 . To reprogram the amplifier for a different gain, the frequencies are changed.

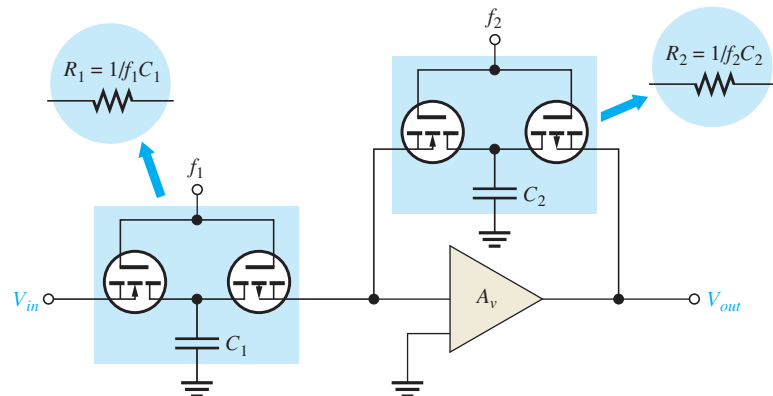


FIGURE 4-60 The IC amplifier in Figure 4-57 with switched-capacitor circuits replacing the resistors.

CMOS: A Digital Switching Application

CMOS combines n -channel and p -channel E-MOSFETs in a series arrangement as shown in Figure 4-61(a). The input voltage at the gates is either 0 V or V_{DD} . Notice that V_{DD} and ground are both connected to the source terminals of the transistors. To avoid confusion, the term V_{DD} is used for the positive voltage, which is on the p -channel device's source terminal. When $V_{in} = 0$ V, Q_1 is *on* and Q_2 is *off*, as shown in part (b). Because Q_1 is acting as a closed switch, the output is approximately V_{DD} . When $V_{in} = V_{DD}$, Q_2 is *on* and Q_1 is *off*, as shown in part (c). Because Q_2 is acting as a closed switch, the output is essentially connected to ground (0 V).

A major advantage of CMOS is that it consumes very little dc power. Because the MOSFETs are in series and one of them is always *off*, there is essentially no current from the dc supply in the quiescent state. When the MOSFETs are switching, there is current for a very short time because both transistors are *on* during this very short transition from one state to the other.


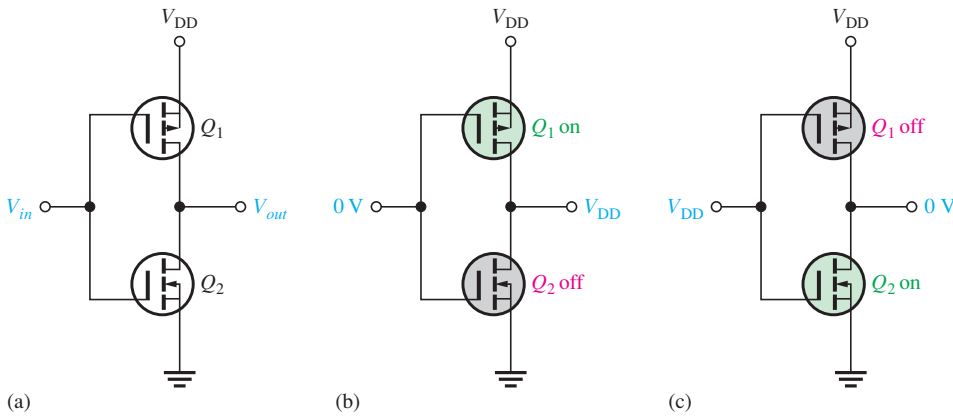


FIGURE 4-61 CMOS inverter operation.

INVERTER Notice that the circuit in Figure 4-61 actually inverts the input because when the input is 0 V or low, the output is V_{DD} or high. When the input is V_{DD} or high, the output is 0 V or low. For this reason, this circuit is called an *inverter* in digital electronics.

NAND GATE In Figure 4-62(a), two additional MOSFETs and a second input are added to the CMOS pair to create a digital circuit known as a NAND gate. Q_4 is connected in parallel with Q_1 and Q_3 is connected in series with Q_2 . When both inputs, V_A and V_B , are 0, Q_1 and Q_4 are *on* while Q_2 and Q_3 are *off*, making $V_{out} = V_{DD}$. When both inputs are equal to V_{DD} , Q_1 and Q_4 are *off* while Q_2 and Q_3 are *on*, making $V_{out} = 0$. You can verify that when the inputs are different, one at V_{DD} and the other at 0, the output is equal to V_{DD} . The operation is summarized in the table of Figure 4-62(b) and can be stated:

 When V_A AND V_B are high, the output is low; otherwise, the output is high.




V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0	on	off	off	on	V_{DD}
0	V_{DD}	off	off	off	on	V_{DD}
V_{DD}	0	on	off	off	off	V_{DD}
V_{DD}	V_{DD}	off	on	on	off	0

FIGURE 4-62 CMOS NAND gate operation.

NOR GATE In Figure 4-63(a), two additional MOSFETs and a second input are added to the CMOS pair to create a digital circuit known as a NOR gate. Q_4 is connected in parallel with Q_2 , and Q_3 is connected in series with Q_1 . When both inputs, V_A and V_B , are 0, Q_1 and Q_3 are *on* while Q_2 and Q_4 are *off*, making $V_{out} = V_{DD}$. When

both inputs are equal to V_{DD} , Q_1 and Q_3 are *off* while Q_2 and Q_4 are *on*, making $V_{out} = 0$. You can verify that when the inputs are different, one at V_{DD} and the other at 0, the output is equal to 0. The operation is summarized in the table of Figure 4–63(b) and can be stated:

 When V_A OR V_B OR both are high, the output is low; otherwise, the output is high.



V_A	V_B	Q_1	Q_2	Q_3	Q_4	V_{out}
0	0	on	off	on	off	V_{DD}
0	V_{DD}	off	on	on	off	0
V_{DD}	0	on	off	on	off	0
V_{DD}	V_{DD}	off	on	off	on	0

(a)

(b)

FIGURE 4–63 CMOS NOR gate operation.

MULTISIM



Open file F04-63 found on the companion website. This simulation demonstrates the operation of a CMOS NOR gate.


MOSFETs in Power Switching Applications

The power MOSFET has largely replaced the BJT in most high-power switching applications for a variety of reasons. MOSFETs turn off faster, require no drive current, have lower on-resistance (dissipate less power), and have a positive temperature coefficient—as they get hotter their resistance increases. This means they are less subject to thermal runaway compared to BJTs, which have a negative temperature coefficient. Power MOSFETs are used in motor control, dc-to-ac and dc-to-dc conversion, load switching, or any application that requires high power and precise digital control. For example, the 2SK4124 has a drain-to-source voltage (V_{DSS}) rating of 500 V, a drain current rating of 20 A continuous and 60 A pulsed. It can dissipate up to 170 W if properly installed on a heat sink.

Power MOSFET Structures

The conventional enhancement MOSFETs have a long thin lateral channel as shown in the structural view in Figure 4–64. The red arrow in the figure shows the movement of majority carriers from source to drain. This results in a relatively high drain-to-source resistance and limits the E-MOSFET to low power applications. When the gate is positive, the channel is formed close to the gate between the source and the drain, as shown.

FIGURE 4–64 Cross section of conventional E-MOSFET structure. Channel is shown as white area.

 

LATERALLY DIFFUSED MOSFET (LDMOSFET) The LDMOSFET has a lateral channel structure and is a type of enhancement MOSFET designed for power applications. This device has a shorter channel between drain and source than the conventional E-MOSFET. The shorter channel results in lower resistance, which allows higher current and voltage.

Figure 4-65 shows the basic structure of an LDMOSFET. When the gate is positive, a very short n channel is induced in the p layer between the lightly doped source and the n^- region. Majority carriers travel from source to drain through the n regions and the induced channel as indicated.

 


FIGURE 4-65 Cross section of LDMOSFET lateral channel structure.

There is a constant push to make transistors smaller, to reduce the physical size of systems. The FinFET is a three-dimensional transistor that moves the conducting channel into a 3-D ridge (or fin) and drapes the gate over it. A simplified illustration of FinFet construction is shown in Figure SN4-2. This reduces the size of the transistor to 22 nm. There is one other very important advantage aside from denser integration. As 2-D transistors got smaller they ran into a voltage limit of 0.9 V in order to turn the transistor off. The FinFET promises to operate at lower voltages with less leakage current. This translates into higher efficiency.


 


FIGURE SN4-2 FinFET construction.

But now there is another player on the field. The ultra-thin body silicon-on-insulator, or UTB SOI, may be a competitor to the FinFET. The channel of a UTB is very thin (5 nm, or only 15 silicon atoms) and flat. UTB devices need less development work, but they do not have the current capacity of FinFETs. Both devices are currently in development.

SYSTEM NOTE

 

VMOSFET The V-groove MOSFET is another example of an E-MOSFET designed to achieve higher power capability by creating a shorter and wider channel with less resistance between the drain and source using a vertical channel structure. The shorter, wider channels allow for higher currents and, thus, greater power dissipation. Frequency response is also improved.

The VMOSFET has two source connections, a gate connection on top, and a drain connection on the bottom, as shown in Figure 4-66. The channel is induced vertically along both sides of the V-shaped groove between the drain (n^+ substrate where n^+ means a higher doping level than n^-) and the source connections. The channel length is set by the thickness of the layers, which is controlled by doping densities and diffusion time.

TMOSFET The vertical channel structure of the TMOSFET is illustrated in Figure 4-67. The gate structure is embedded in a silicon dioxide layer, and the source contact is continuous over the entire surface area. The drain is on the bottom. TMOSFET achieves greater packing density than VMOSFET, while retaining the short vertical channel advantage.

 


FIGURE 4-66 Cross section of VMOSFET vertical channel structure.

 


FIGURE 4-67 Cross section of TMOSFET vertical channel structure.

SECTION 4-7 CHECKUP

1. What is the difference between an analog and a digital switch?
2. What are the attributes of an ideal analog switch?
3. What advantage do MOSFETs have for digital switches?
4. How does a CMOS inverter work?
5. Name several types of high-power MOSFETs.

4-8 A SYSTEM

MOSFETs are often used in stand-alone control systems. Motor control circuits are an important control circuit for many systems. In this application, the tracking circuit for a solar panel is the focus, but keep in mind that the idea can be applied to other similar systems.

After completing this section, you should be able to

- Show how MOSFET transistors are used in a small system
- Describe the operation of an H-bridge for motor control
- Explain the purpose of each block in a solar tracking system

In this example we will examine a solar tracking system that includes photodiode sensors and a MOSFET-based motor controller. We will begin with a discussion of solar tracking.

Solar tracking is the process of moving the solar panel to track the daily movement of the sun and the seasonal changes in elevation of the sun in the southern sky. The purpose of a solar tracker is to increase the amount of solar energy that can be collected by the system. For flat-panel collectors, an increase of 30% to 50% in collected energy can be realized with sun tracking compared to fixed solar panels.

Before looking at methods for tracking, let's review how the sun moves across the sky. The daily motion of the sun follows the arc of a circle from east to west that has its axis pointed north near the location of the North Star. As the seasons change from the winter solstice to the summer solstice, the sun rises a little further to the north each day. Between the summer solstice and the winter solstice, the sun moves further south each day. The amount of the north-south motion depends on your distance from the equator.

Single-Axis Solar Tracking

For flat-panel solar collectors, the most economical and generally most practical solution to tracking is to follow the daily east-west motion, and not the annual north-south motion. The daily east-to-west motion can be followed with a single-axis tracking system. There are two basic single-axis systems: polar and azimuth. In a polar system, the main axis is pointed to the polar north (North Star), as shown in Figure 4-68(a). (In telescope terminology, this is called an equatorial mounting.) The advantage is that the solar panel is kept at an angle facing the sun at all times because it tracks the sun from east to west and is angled toward the southern sky. In an azimuth tracking system, the motor drives the solar panel and frequently multiple panels. The panels can be oriented horizontally but still track the east-to-west motion of the sun. Although this does not intercept as much of the sunlight during the seasons, it has less wind loading and is more feasible for long rows of solar panels. Figure 4-68(b) shows a solar array that is oriented horizontally with the axis pointing to true north and uses azimuth tracking (east to west). As you can see, sunlight will strike the polar-aligned panel more directly during the seasonal movement of the sun than it will with the horizontal orientation of the azimuth tracker.

 


FIGURE 4-68 Types of single-axis solar tracking.

Some solar tracking systems combine both the azimuth and the elevation tracking, which is known as dual-axis tracking. Ideally, the solar panel should always face directly toward the sun so that the sun light rays are perpendicular to the panel. With dual-axis tracking, the annual north-south motion of the sun can be followed in addition to the daily east-to-west movement. This is particularly important with concentrating collectors that need to be oriented correctly to focus the sun on the active region.

Figure 4-69 is an example showing the improvement in energy collection of a typical tracking panel versus a nontracking panel for a flat solar collector. As you can see, tracking extends the time that a given output can be maintained.

 


FIGURE 4-69 Graphs of voltages in tracking and nontracking (fixed) solar panels.

Sensor-Controlled Solar Tracking

This type of tracking control uses photosensitive devices such as photodiodes. Typically, there are two light sensors for the azimuth control and two for the elevation control. Each pair senses the direction of light from the sun and activates the motor control to move the solar panel to align perpendicular to the sun's rays.

Figure 4–70 shows the basic idea of a sensor-controlled tracker. Two photodiodes with a light-blocking partition between them are mounted on the same plane as the solar panel.

 


FIGURE 4-70 Simplified illustration of a light-sensing control for a solar-tracking system. Relative sizes are exaggerated to demonstrate the concept.

If the solar panel is not facing directly toward the sun, the light strikes the panel and the photodiode assembly at an angle so that one of the diodes is shaded or partially shaded by the partition and receives less light than the other, as illustrated in Figure 4–70(a). As a result, the photodiode with the most light produces a higher current than the partially-shaded device. The difference in currents from the two diodes is processed by the position-control circuit, which sends control signals to the motor control. The motor rotates the solar panel until both photodiodes produce the same current and then is stopped by the control circuit, as illustrated in Figure 4–70(b). The light-blocking partition between the diodes is oriented vertically for azimuth tracking and horizontally for elevation tracking. The photodiode assemblies must face in the same direction as the solar panel, so they are mounted on the solar panel frame.

DUAL-AXIS SOLAR TRACKING As mentioned, a dual-axis system tracks the sun in both azimuth and elevation. It requires two photo-sensing elements and two motors, as shown in Figure 4–71. The outputs from the two pairs of sensors go to the position-control circuits. A circuit detects the differential between the two azimuth sensor outputs and, if the differential is sufficient, the azimuth motor is advanced westward until a balance occurs between the two sensors. Similarly, another circuit detects the differential between the two elevation sensor outputs and, correspondingly, advances the elevation motor to rotate the solar panel either up or down until a balance occurs between the two sensors. When night falls and the solar panel is at its western most position, the position-control circuits detect no output from the azimuth sensors and send a reset command to the azimuth motor to

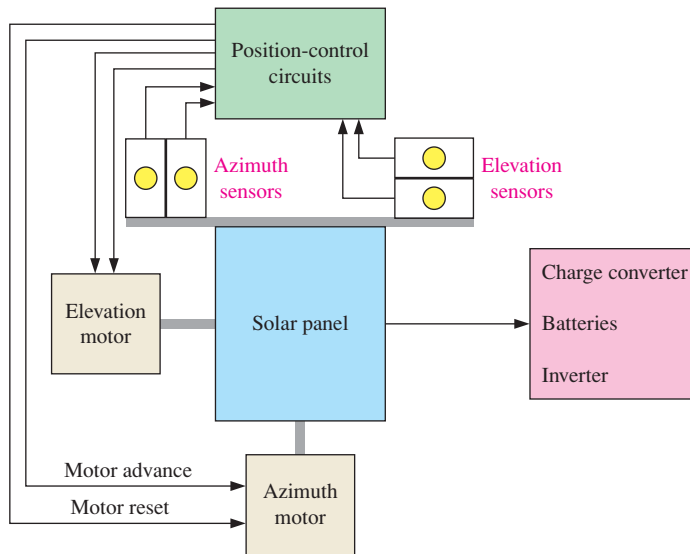


FIGURE 4-71 Block diagram of a dual-axis sensor-controlled tracking solar power system.

cause it to turn the solar panel back to its eastmost position to await sunrise the next day. The system must be sensitive enough to detect very small differences in photodiode output because the more closely the sun is tracked, the better the energy collection efficiency.

H-bridge Motor Control Circuit

One possible circuit for controlling an axis tracking motor is the MOSFET-based H-bridge circuit shown in Figure 4-72. The motor is controlled by two pairs of *n*- and *p*-channel MOSFETs, one pair on either side of the bridge. The bridge is connected to either the

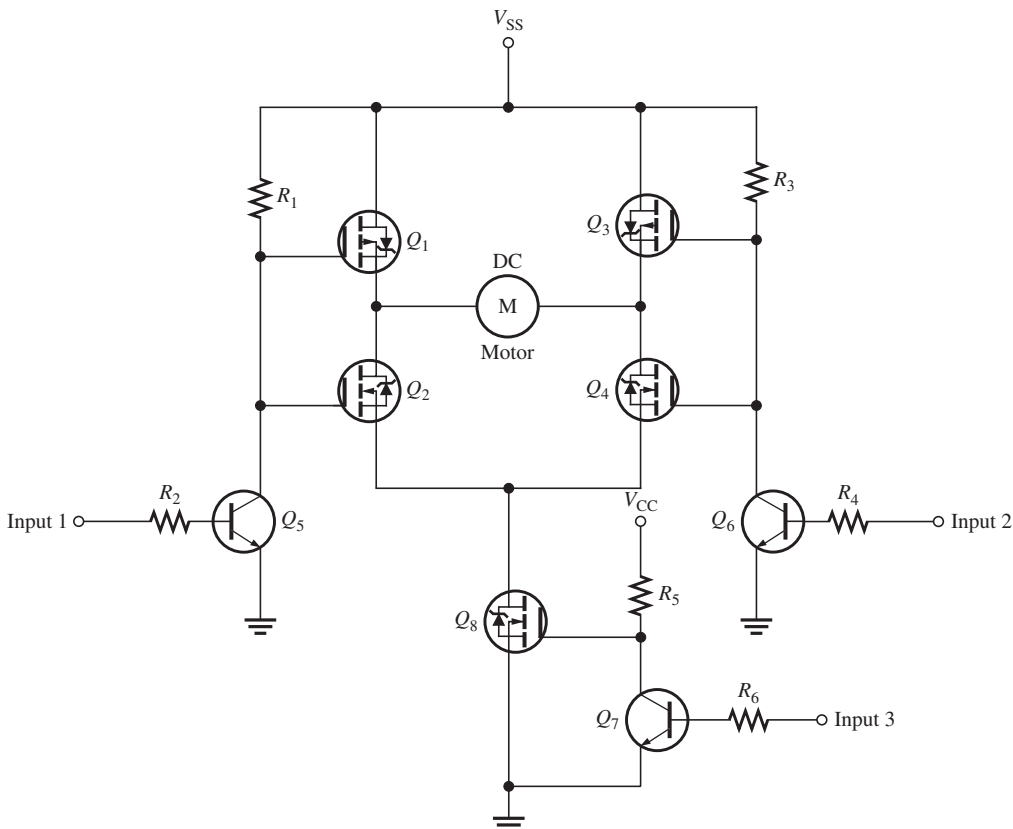


FIGURE 4-72 H-bridge motor control circuit. The motor connection shown is to the armature or field but not both.

armature or the field coil, but not both. Reversing the polarity of the applied voltage to both would not result in a change of direction. Control inputs to the bridge are supplied by the position control circuit, which processes the data from the photodiodes.

If Input 1 is high and Input 2 is low, then Q_1 and Q_4 are biased ON and Q_2 and Q_3 are biased OFF. Current passes through the motor causing it to turn in one direction. If Input 1 is low and Input 2 is high, then Q_1 and Q_4 are biased OFF and Q_2 and Q_3 are biased ON. Current passes through and it turns in the opposite direction. If both Inputs 1 and 2 are either high or low, the motor brake is set and it is held in position. A high signal on Input 3 turns off Q_8 , disables the bridge, and the motor is off. These relationships are summarized in the Table 4–1.

To ensure precise motor control resolution, transistor characteristics should be matched as closely as possible. One method is to use a MOSFET transistor array IC rather than discrete components. The layout of a four-device array IC is shown in Figure 4–73. This is referred to as a full-bridge configuration. You can also get half-bridge configuration arrays that contain one pair of MOSFETs. Array devices have much closer device-to-device consistency than discrete transistors.

INPUT 1	INPUT 2	INPUT 3	RESULT
0	0	0	N Channel Brake
1	1	0	P Channel Brake
1	0	0	Forward
0	1	0	Reverse
X	X	1	Motor Off

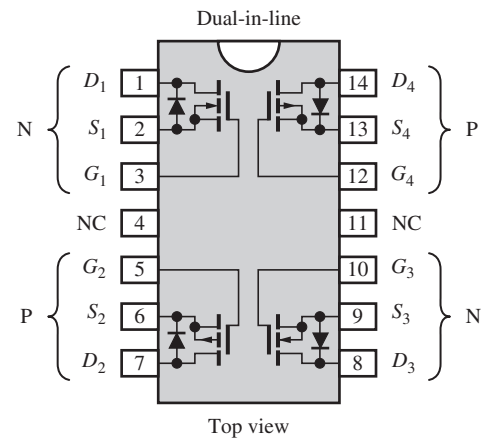


FIGURE 4–73 Enhancement-mode MOSFET transistor array.

SECTION 4–8 CHECKUP

1. What is the difference between an equatorial tracker and an altitude-azimuth tracker?
2. What is the advantage of an H bridge for motor tracking?
3. What is the advantage of using MOSFET transistors for the H bridge?

SUMMARY

- FETs can be broadly classified into JFETs and MOSFETs. JFETs have a reverse-biased gate-source pn junction at the input; MOSFETs have an insulated-gate input.
- MOSFETs are classified as either depletion mode or enhancement mode. The D-MOSFET has a physical channel between the drain and the source; the E-MOSFET does not.
- All FETs are either n -channel or p -channel.
- The three terminals on a FET are the source, drain, and gate that correspond to the emitter, collector, and base of a BJT.
- JFETs have very high input resistance due to the reverse-biased gate-source pn junction. MOSFETs have a very high input resistance due to the insulated gate input.
- JFETs are normally on devices. Drain current is controlled by the amount of reverse bias on the gate-source pn junction.

- D-MOSFETs are normally on devices. Drain current is controlled by the amount of bias on the gate-source pn junction. A D-MOSFET can have either forward bias or reverse bias on the gate-source pn junction.
- E-MOSFETs are normally off devices. Drain current is controlled by the amount of forward bias on the gate-source pn junction.
- The drain characteristic curve for FETs is divided between an ohmic region and a constant-current region.
- The transconductance curve is a plot of drain current versus gate-source voltage.
- MOSFET devices need special handling procedures to avoid destructive static electricity.
- JFETs can be biased by self-bias, a combination of self-bias and voltage-divider bias, or current-source bias.
- A D-MOSFET can operate with a positive, negative, or zero gate-to-source voltage so it can be biased by several different methods.
- An E-MOSFET can be biased by the same methods as a BJT (except base bias).
- A common-source (CS) amplifier has high voltage gain and high input resistance.
- A common-drain (CD) amplifier has unity (or less) voltage gain and high input resistance.
- A CD amplifier can be improved significantly with current-source biasing.
- A common-gate (CG) amplifier has high voltage gain but low input resistance.
- The voltage gain of various amplifiers can be computed by a ratio of resistances (including internal resistance).
- Analog switches pass or block a signal.
- Digital switches turn on or off a device.
- Digital switches are designed to operate in either saturation or cutoff.
- MOSFETs have important advantages as digital switches, particularly for high-current applications.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Common-drain (CD) A FET amplifier configuration in which the drain is the grounded terminal.

Common-gate (CG) A FET amplifier configuration in which the gate is the grounded terminal.

Common-source (CS) A FET amplifier configuration in which the source is the grounded terminal.

Constant-current region The region on the drain characteristic of a FET in which the drain current is independent of the drain-to-source voltage.

Depletion mode A class of FETs that is on with zero-gate voltage and is turned off by gate voltage. All JFETs and some MOSFETs are depletion-mode devices.

Drain One of the three terminals of a field-effect transistor; it is one end of the channel.

Enhancement mode A MOSFET in which the channel is formed (or enhanced) by the application of a gate voltage.

Field-effect transistor (FET) A voltage-controlled device in which the voltage at the gate terminal controls the amount of current through the device.

Gate One of the three terminals of a field-effect transistor. A voltage applied to the gate controls drain current.

Junction field-effect transistor (JFET) A type of FET that operates with a reverse-biased pn junction to control current in a channel. It is a depletion-mode device.

MOSFET Metal-oxide semiconductor field-effect transistor; one of two major types of FET. It uses a SiO_2 layer to insulate the gate lead from the channel. MOSFETs can be either depletion mode or enhancement mode.

Ohmic region The region on the drain characteristic of a FET with low values of V_{DS} in which the channel resistance can be changed by the gate voltage; in this region the FET can be operated as a voltage-controlled resistor.

Pinch-off voltage The value of the drain-to-source voltage of a FET at which the drain current becomes constant when the gate-to-source voltage is zero.

Source One of the three terminals of a field-effect transistor; it is one end of the channel.

Transconductance The gain of a FET; it is determined by a small change in drain current divided by a corresponding change in gate-to-source voltage. It is measured in siemens or mhos.

KEY FORMULAS

(4-1)	$g_m = \frac{I_d}{V_{gs}}$	Transconductance of a FET
(4-2)	$R_{IN} = \left \frac{V_{GS}}{I_{GSS}} \right $	Input resistance. It is the gate-source voltage divided by the gate-reverse current.
(4-3)	$V_D = V_{DD} - I_D R_D$	DC drain voltage for a FET
(4-4)	$V_{DS} = V_{DD} - I_D(R_D + R_S)$	DC drain-to-source voltage for a FET
(4-5)	$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD}$	Gate voltage with voltage-divider bias
(4-6)	$r'_s = \frac{1}{g_m}$	Equivalent internal ac source resistance for computing voltage gain
(4-7)	$A_v = -g_m R_d$	Voltage gain for a CS amplifier
(4-8)	$A_v = -\frac{R_d}{r'_s}$	Alternate voltage gain for a CS amplifier
(4-9)	$A_v = \frac{R_s}{r'_s + R_s}$	Voltage gain for a CD amplifier
(4-10)	$A_v = \frac{g_m R_s}{1 + g_m R_s}$	Alternate voltage gain for a CD amplifier
(4-11)	$r_{DS(on)} = -\frac{V_{GS(off)}}{2I_{DSS}}$	Channel resistance

SELF-TEST

Answers are at the end of the chapter.

- A type of transistor that is normally on when the gate-to-source voltage is zero is
 - JFET
 - D-MOSFET
 - E-MOSFET
 - answers (a) and (b)
 - answers (a) and (c)
- A bias method that can be used for D-MOSFETs is
 - voltage divider
 - drain feedback
 - current source
 - self
 - either (a), (b), (c), or (d)
- In normal operation, the gate-source *pn* junction for a JFET is
 - reverse-biased
 - forward-biased
 - either (a) or (b)
 - neither (a) nor (b)
- When the voltage between the gate and source of a JFET is zero, the drain current will be
 - zero
 - I_{DSS}
 - I_{GSS}
 - none of these answers
- One reason an *n*-channel D-MOSFET can have zero bias is it
 - can operate in either depletion mode or enhancement mode
 - does not have an insulated gate
 - does not have a channel
 - will not have drain current when operated with zero bias
- A feature of FETs that is superior to BJTs is their
 - high gain
 - low distortion
 - high input resistance
 - all of these answers
- An amplifier with high voltage gain and high input resistance is a common-
 - gate
 - source
 - drain
 - answers (a), (b), and (c)
 - neither (a), (b), nor (c)

8. An amplifier that inverts the signal between input and output is a common-
 (a) gate (b) source (c) drain
 (d) answers (a), (b), and (c) (e) neither (a), (b), nor (c)
9. A transistor that has a closed channel unless a voltage is applied to the gate is
 (a) a JFET (b) a D-MOSFET (c) an E-MOSFET
 (d) all of these answers (e) none of these answers
10. The value of the drain-to-source voltage of a FET at which the drain current becomes constant when the gate-to-source voltage is zero is called the
 (a) bias voltage (b) pinch-off voltage (c) saturation voltage (d) cutoff voltage
11. The voltage gain of a common-drain amplifier cannot exceed
 (a) 1.0 (b) 2.0 (c) 10 (d) 100
12. A type of electronic switching circuit which can be used to connect a given signal to the input of an analog-to-digital converter (ADC) is a(n)
 (a) analog switch (b) digital switch
 (c) logic switch (d) bipolar switch
13. Refer to Figure 4–74. The schematic symbol for a *p*-channel E-MOSFET is
 (a) a (b) b (c) c (d) d (e) e (f) f

 


FIGURE 4-74

14. Refer to Figure 4–74. The schematic symbol for an *n*-channel D-MOSFET is
 (a) a (b) b (c) c (d) d (e) e (f) f
15. The type of device used in a CMOS switching circuit is
 (a) *n*-channel D-MOSFET (b) *p*-channel D-MOSFET
 (c) both (a) and (b) (d) neither (a) nor (b)

TROUBLESHOOTER'S QUIZ


Answers are at the end of the chapter.

Refer to Figure 4–78(a).

- If R_G is $1.0\text{ M}\Omega$ instead of $10\text{ M}\Omega$,
 1. The gate voltage will
 (a) increase (b) decrease (c) not change
 2. The drain current will
 (a) increase (b) decrease (c) not change
 3. The input resistance will
 (a) increase (b) decrease (c) not change

Refer to Figure 4–79.

 - If the positive power supply falls to $+9.0\text{ V}$, but the negative supply voltage is unchanged,
 4. The drain current will
 (a) increase (b) decrease (c) not change
 5. The voltage across R_D will
 (a) increase (b) decrease (c) not change



Refer to Figure 4–86.

- If capacitor C_2 is open,
 6. The dc voltage at the source terminal of the MOSFET will
 - (a) increase (b) decrease (c) not change
 7. The ac voltage at the source terminal of the MOSFET will
 - (a) increase (b) decrease (c) not change
 8. The gain will
 - (a) increase (b) decrease (c) not change
- If resistor R_2 is open,
 9. The dc gate voltage will
 - (a) increase (b) decrease (c) not change
 10. The drain current will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 4–1 Structure of Field-Effect Transistors

1. What type of transistor conducts with a reverse-biased pn junction at the input?
2. What type of transistor has an insulated gate?

SECTION 4–2 JFET Characteristics

3. The V_{GS} of a p -channel JFET is increased from +1 V to +3 V.
 - (a) Does the depletion region narrow or widen?
 - (b) Does the resistance of the channel increase or decrease?
 - (c) Does the transistor conduct more current or less?
4. Why must the gate-to-source voltage of an n -channel JFET always be either zero or negative?
5. A JFET has a specified pinch-off voltage of -5 V. When $V_{GS} = 0$, what is V_{DS} at the point where I_D becomes constant?
6. An n -channel JFET is biased such that $V_{GS} = -2$ V using self-bias. The gate resistor is connected to ground.
 - (a) What is V_S ?
 - (b) What is the value of $V_{GS(off)}$ if V_P is specified to be 6 V?
7. A certain JFET data sheet gives $V_{GS(off)} = -8$ V, $I_{DSS} = 10$ mA, and $I_{GSS} = 1.0$ nA at 25°C .
 - (a) When $V_{GS} = 0$, what is I_D for values of V_{DS} above pinch-off?
 - (b) When $V_{GS} = -4$ V, what is R_{IN} at 25°C ?
 - (c) What happens to R_{IN} if the temperature increases?
8. A certain p -channel JFET has a $V_{GS(off)} = +6$ V. What is I_D when $V_{GS} = +8$ V?
9. The JFET in Figure 4–75 has a $V_{GS(off)} = -4$ V and an $I_{DSS} = 2.5$ mA. Assume that you increase the supply voltage, V_{DD} , beginning at 0 until the ammeter reaches a steady value. At this point,
 - (a) What does the voltmeter read?
 - (b) What does the ammeter read?
 - (c) What is V_{DD} ?
10. Assume a JFET has the transconductance curve shown in Figure 4–76.
 - (a) What is I_{DSS} ?
 - (b) What is $V_{GS(off)}$?
 - (c) What is the transconductance at a drain current of 2.0 mA?

 


FIGURE 4-75

 


FIGURE 4-76

SECTION 4-3 JFET Biasing

11. Assume the JFET with the transconductance curve shown in Figure 4-76 is connected in the circuit shown in Figure 4-77.
- (a) What is V_S ?
 - (b) What is I_D ?
 - (c) What is V_{DS} ?

 


FIGURE 4-77

12. Assume the JFET in Figure 4-77 is replaced with one with a lower transconductance.
- (a) What will happen to V_{GS} ?
 - (b) What will happen to V_{DS} ?
13. For each circuit in Figure 4-78, determine V_{DS} and V_{GS} .

 


FIGURE 4-78

 


FIGURE 4-79

14. Assume the circuit shown in Example 4-6 has $R_S = 1.0 \text{ k}\Omega$ and $R_D = 3.7 \text{ k}\Omega$. (The load line does not change as a result of these changes, but the Q-point moves). Find the new I_D and V_{GS} .
15. Find I_D and V_D for the current-source biased JFET in Figure 4-79.

SECTION 4-4 MOSFET Characteristics

16. Sketch the schematic symbols for *n*-channel and *p*-channel D-MOSFETs and E-MOSFETs. Label the terminals.
17. Explain why MOSFETs have an extremely high input resistance at the gate.
18. An *n*-channel D-MOSFET with a positive V_{GS} is operating in what mode?
19. A certain E-MOSFET has a $V_{GS(th)} = 3 \text{ V}$. What is the minimum V_{GS} for the device to turn on?

SECTION 4-5 MOSFET Biasing

20. Determine in which mode (depletion or enhancement) each D-MOSFET in Figure 4-80 is biased.

 


FIGURE 4-80

21. Each E-MOSFET in Figure 4-81 has a $V_{GS(th)}$ of +5 V or -5 V, depending on whether it is an *n*-channel or a *p*-channel device. Determine whether each MOSFET is on or off.
22. The drain current for the E-MOSFET shown in Figure 4-82 is 3.0 mA.
 - (a) What type of bias is this?
 - (b) Can a JFET use this type of bias?
 - (c) Compute the value of V_D .
 - (d) Compute the value of V_G .
23. Sketch the load line for the circuit of Figure 4-82 and indicate the Q-point ($I_D = 3.0 \text{ mA}$).

 


FIGURE 4-81

 
 


FIGURE 4-82

SECTION 4-6 FET Linear Amplifiers

24. (a) Assume $V_{GS} = -2.0$ V for the circuit in Figure 4-83. Determine V_G , V_S , and V_D .
 (b) If $g_m = 3000$ μ mho, what is the voltage gain?
 (c) What is V_{out} ?

 


FIGURE 4-83

25. Determine the gain of the amplifier in Figure 4-83 when a 27 kΩ load is connected from the output to ground ($g_m = 3000$ μ mhos).
 26. For the circuit in Figure 4-83, what effect would an open R_1 have on
 (a) V_G (b) A_v (c) I_D
 27. The minimum specified value of g_m for a 2N5457 is 1000 μ mhos and the maximum specified value is 5000 μ mhos. From these values, find the minimum and maximum gain for the CD amplifier in Figure 4-84.
 28. Assume the g_m of Q_1 is 1500 μ mhos for the amplifier in Figure 4-85.
 (a) Compute I_D .
 (b) If $g_m = 1500$ μ mho, what is the voltage gain?
 (c) What is V_{out} ?
 (d) What is the purpose of C_2 ? What happens if it is open?

 


FIGURE 4-84

 


FIGURE 4-85

29. Assume the amplifier in Figure 4–85 has no output voltage. A check of the dc conditions reveals that the drain voltage is 15 V. Name at least three failures that can account for this.
30. Refer to Figure 4–85. Assume the dc voltages and the ac input voltage are correct, but V_{out} is very small. What failure can account for this?
31. Refer to Figure 4–85. What is the minimum value of I_{DSS} that Q_1 can have before the gate-source pn junction is forward-biased?
32. Assume the source voltage for the D-MOSFET in Figure 4–86 is measured and found to be 1.6 V.
 - (a) Compute I_D and V_{DS} .
 - (b) If $g_m = 2000 \mu\text{mho}$, what is the voltage gain?
 - (c) Compute the input resistance of the amplifier.
 - (d) Is the D-MOSFET operating in the depletion or the enhancement mode?
33. Repeat Problem 32(a) and (b) if a 5.1 k Ω load is connected between V_{out} and ground.
34. Assume Q_1 and Q_2 in Figure 4–87 have matching characteristics and I_{DSS} is 1.5 mA.
 - (a) What is I_D ?
 - (b) What is the approximate gain?
 - (c) If Q_2 is replaced with a transistor with an I_{DSS} of 1.0 mA, what problem will occur?

 


FIGURE 4–86

 


FIGURE 4–87

SECTION 4–7 MOSFET Switching Circuits

35. Explain why $r_{DS(on)}$ is one of the most important specifications for an analog switch.
36. The MOSFET used in an analog switch has a $V_{GS(th)}$ rating of 1.3 V; 3.8 V is applied to the gate to turn the switch on. What is the maximum peak-to-peak input signal that can be applied to the source of the switch?
37. Explain why a CMOS digital switch dissipates very little power.
38. Explain why a MOSFET power switch is less susceptible to thermal runaway than a BJT power switch.

MULTISIM



MULTISIM TROUBLESHOOTING PROBLEMS

39. Open file P04-39 and determine the fault.
40. Open file P04-40 and determine the fault.
41. Open file P04-41 and determine the fault.
42. Open file P04-42 and determine the fault.
43. Open file P04-43 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 4-1

1. Drain, source, and gate
2. MOSFET
3. They require smaller areas than BJTs, are easy to manufacture in ICs, and produce simpler circuits.
4. BJTs are controlled by a current, FETs are controlled by a voltage. BJT circuits have higher gain but lower input resistance.

SECTION 4-2

1. Transconductance curve
2. Positive
3. By the gate-to-source voltage
4. 7 V
5. Decrease
6. +3 V

SECTION 4-3

1. $V_{GS(off)}$ and I_{DSS} .
2. The base-emitter pn junction in a BJT is forward biased; the gate-source pn junction in a JFET is reverse biased.
3. -8 V
4. I_{DSS}

SECTION 4-4

1. Depletion MOSFET and enhancement-only MOSFET. The D-MOSFET has a physical channel; the E-MOSFET does not.
2. Yes; the current is I_{DSS} .
3. No
4. Yes

SECTION 4-5

1. I_{DSS}
2. It is a normally off device. It must have forward bias to turn it on.
3. +2 V
4. High-voltage high-current switching circuits.

SECTION 4-6

1. It is the transconductance (g_m) times the ac drain resistance (R_d) or the ratio of the ac drain resistance (R_d) to the internal ac source resistance (r'_s).
2. A CD amplifier with current-source biasing has higher input resistance, no bias resistors, and can be dc coupled with 0 V dc output.
3. CD and CG
4. Low input resistance
5. High input resistance and low noise

SECTION 4-7

1. An analog switch passes or blocks an ac signal; a digital switch turns on or off a device.
2. When closed, it has no resistance to the signal; when open, it is an infinite resistance.
3. They are voltage controlled and draw no drive current. They can control a large current to a device and they are immune to thermal runaway.
4. N -channel and p -channel E-MOSFETs are connected with common gates and drains, and the output is connected to the drains. The n -channel source is connected to ground and the

p -channel source is connected to a positive supply voltage. When the input is greater than one-half the power supply voltage, the n -channel device is on, causing the output to be near ground; when the input is less than one-half the power supply voltage, the p -channel MOSFET is on causing the output to be near the power supply voltage.

5. The LDMOSFET, the VMOSFET, and the TMOSFET.

SECTION 4-8

1. An equatorial tracker is aligned to the north-south axis of the earth and for solar tracking requires only one axis to follow the sun's daily east-west motion. (Seasonal variations require a north-south adjustment). An altitude-azimuth is aligned to the earth's surface and requires dual tracking motors to follow the sun's daily and seasonal motions.
2. The H bridge configuration enables reversing or stopping the motor with simple control signals.
3. MOSFETS have low on-resistance and are simple to control with no drive current. They are available for high power switching.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 4-1 I_D remains at approximately 12 mA.
 4-2 ≈ 1.0 mS
 4-3 300 M Ω
 4-4 $V_{DS} = 6.34$ V, $V_{GS} = -0.66$ V
 4-5 $I_{D(\min)} \cong 0.3$ mA; $I_{D(\max)} \cong 2.3$ mA
 4-6 The dc cutoff is +9 V; the dc saturation current is 1.91 mA. These represent the end points on the x -axis and the y -axis for the load line.
 4-7 The open on the drain leaves the gate forward-biased through the voltage divider on the base. About 11 μ A is in the path that includes the source resistor and the 1.0 M Ω bias resistor. The source voltage is therefore approximately 20 mV; the drain voltage is the same as the source voltage because of the common channel, and the gate voltage is about 500 mV since the gate source pn junction has only a very small forward current.
 4-8 I_{DSS} cannot be less than 0.95 mA.
 4-9 6.8 V
 4-10 2.13 mA
 4-11 A larger source resistor reduces (slightly) the transconductance. As a result, the gain will be reduced.
 4-12 10 M Ω
 4-13 I_D is approximately 1.1 mA; $V_{S(Q1)}$ is approximately 2.2 V.
 4-14 The transistor will turn off, clipping the bottom of the output waveform.

ANSWERS TO SELF-TEST

1. (a) 2. (e) 3. (a) 4. (b) 5. (a) 6. (c) 7. (b) 8. (b)
 9. (c) 10. (b) 11. (a) 12. (a) 13. (d) 14. (a) 15. (d)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. not change 2. not change 3. decrease 4. not change
 5. decrease 6. not change 7. increase 8. decrease
 9. increase 10. increase

CHAPTER 5

MULTISTAGE, RF, AND POWER AMPLIFIERS

OUTLINE

- 5-1 Capacitively Coupled Amplifiers
- 5-2 RF Amplifiers
- 5-3 Transformer-Coupled Amplifiers
- 5-4 Direct-Coupled Amplifiers
- 5-5 Class A Power Amplifiers
- 5-6 Class B Power Amplifiers
- 5-7 Class C and Class D Power Amplifiers
- 5-8 IC Power Amplifiers

OBJECTIVES

- Determine the ac parameters for a capacitively coupled multistage amplifier
- Describe the characteristics of high-frequency amplifiers and give practical considerations for implementing high-frequency circuits
- Describe the characteristics of transformer-coupled amplifiers, tuned amplifiers, and mixers
- Determine basic dc and ac parameters for direct-coupled amplifiers and describe how negative feedback can stabilize the gain of an amplifier
- Compute key ac and dc parameters for class A power amplifiers and discuss operation along the ac load line
- Compute key ac and dc parameters for class B power amplifiers including bipolar and FET types
- Describe the characteristics of class C and class D power amplifiers

- Give principal features and describe applications for IC power amplifiers
- Show systems using components and circuits discussed in this chapter

KEY TERMS

Quality factor (Q)	Class B
Intermediate frequency	Push-pull
Mixer	Class AB
Open-loop voltage gain	Current mirror
Closed-loop voltage gain	Class C
Class A	Class D
Power gain	Pulse-width modulation
Efficiency	(PWM)

INTRODUCTION

The previous two chapters have introduced single-stage amplifiers whose primary function was to increase the voltage of a signal. You should be familiar with the biasing and ac parameters for both BJTs and FETs.

When very small signals must be amplified, such as from an antenna, variations about the Q-point are relatively small. Amplifiers designed to amplify these signals are called small-signal amplifiers. They may also be designed specifically for high frequencies. Frequently, it is useful to have additional stages of gain; this is particularly true in

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

high-frequency communication systems, where the frequencies of interest are restricted to a certain bandwidth.

In this chapter, you will study various types of multistage amplifiers, with particular emphasis on high-frequency considerations including noise, cabling, and

eliminating unwanted oscillations. Then, the emphasis shifts to the important requirement of delivering power to a load. For these applications, power amplifiers are needed. The chapter ends with an introduction to integrated circuit (IC) power amplifiers.

5-1 CAPACITIVELY COUPLED AMPLIFIERS

Two or more transistors can be connected together to form an amplifier called a multistage amplifier. In Section 1-4, a simplified amplifier model was introduced. You are now ready to apply this simplified model to actual amplifier circuits to determine their overall performance. In this section, you will learn about capacitively coupled amplifiers, also called *RC* coupled amplifiers. Capacitive coupling is the most widely used method for passing the ac signal to the next stage.

After completing this section, you should be able to

- Determine the ac parameters for a capacitively coupled multistage amplifier
- Compute the overall gain, the input resistance, and the output resistance of a two-stage capacitively coupled amplifier
- Discuss how oscillation and noise problems can be alleviated in multistage amplifiers

Two or more transistors can be connected together to enhance the performance of an amplifier. Each transistor that amplifies the signal is considered a **stage**. Frequently, the first stage of an amplifier must have very high input resistance to avoid loading the source. In addition, the first stage needs to be designed for low noise operation because the very small signal voltage can easily be obscured by noise. Succeeding stages are designed to increase the amplitude of the signal without adding distortion.

Probably the simplest way to add gain to an amplifier is to capacitively couple two stages together as shown in Figure 5-1. In this case, both stages are identical CE amplifiers with the output of the first connected to the input of the second stage. Capacitive

 


FIGURE 5-1 A two-stage CE amplifier.

coupling prevents the dc bias of one stage from affecting the dc bias of another stage because capacitors block dc. Although the dc path is open, the coupling capacitor provides almost no opposition to the ac signal and the signal passes to the next stage.

The analysis of the circuit starts with the dc conditions, as explained in Section 3-2. To compute the base voltage of either stage, use the voltage-divider rule.

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{10 \text{ k}\Omega}{47 \text{ k}\Omega + 10 \text{ k}\Omega} \right) 10 \text{ V} = 1.7 \text{ V}$$

This estimate is slightly high because it is made for an unloaded voltage divider. After subtracting 0.7 V for the base-emitter diode, the emitter voltage is 1.0 V, which results in an emitter current of

$$I_E = \frac{V_E}{R_E} = \frac{1.0 \text{ V}}{1.0 \text{ k}\Omega} = 1.0 \text{ mA}$$

The emitter current is also approximately equal to the collector current.

Loading Effects

Recall from Section 1-4 that amplifiers were shown as a block diagram with essential parameters only. The ac model is simply a dependent voltage source with a series resistance (a Thevenin circuit). To compute the overall gain of the amplifier, each transistor stage in Figure 5-2 can be modeled in a similar manner. Only three parameters need to be known: the unloaded (No-Load) voltage gain ($A_{v(NL)}$), the total input resistance ($R_{in(tot)}$), and the output resistance (R_{out}). Notice that the unloaded output voltage is the input voltage times the unloaded gain.

 


FIGURE 5-2

Start by finding the unloaded gain of one stage. Because the two stages are identical, the unloaded gain is the same for both. The input resistance of the second stage acts as a load on the first stage. Thus, the loaded gain of the first stage can be found by assuming it has a load resistor equal to $R_{in(tot)}$ of stage 2. This lowers the gain of the first stage but can be considered separately from the unloaded gain calculation. An illustration of this idea should clarify how the basic amplifier model can simplify determining the overall gain.

As you know, the unloaded gain of a CE amplifier is the ratio of the ac collector resistance to the ac emitter resistance. This unloaded gain is dependent on r'_e , which in turn depends on I_E , so the calculation should be considered approximate.

Since the unloaded gain is being computed, the ac collector resistance, R_c , is the same as the actual collector resistor, R_C , which is 4.7 k Ω . The ac emitter resistance is approximately

$$r'_e \cong \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.0 \text{ mA}} = 25 \Omega$$

The unloaded gain, $A_{v(NL)}$, is approximately

$$A_{v(NL)} = -\frac{R_c}{R_e} = -\frac{R_C}{r'_e} = -\frac{4.7 \text{ k}\Omega}{25 \Omega} = -188$$

The input resistance of the CE amplifier was discussed in Section 3–4. The equation for input resistance with voltage-divider bias and no swamping resistor is

$$R_{in(tot)} = R_1 \parallel R_2 \parallel (\beta_{ac} r'_e)$$

By substitution, the input resistance of the amplifier, assuming a β_{ac} of 150, in Figure 5–1 is

$$R_{in(tot)} \cong 47 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel [150(25 \Omega)] \cong 2.58 \text{ k}\Omega$$

The output resistance is the resistance looking back to the collector circuit and is simply the collector resistor.

$$R_{out} = R_C = 4.7 \text{ k}\Omega$$

These values can be entered onto the model as shown in Figure 5–2(b).

The two stages that comprise the amplifier are now connected in Figure 5–3. In this drawing, the unloaded gain for each stage is shown below the Thevenin source, and the model is used to find the overall gain. The overall gain is the product of three terms:

1. The unloaded voltage gain of the first stage
2. The gain of the voltage divider consisting of the input resistance of the second stage with the output resistance of the first stage
3. The unloaded gain of the second stage

If a load resistor is added to the output, it can be included as another voltage-divider term. (This will be shown in Example 5–1.)

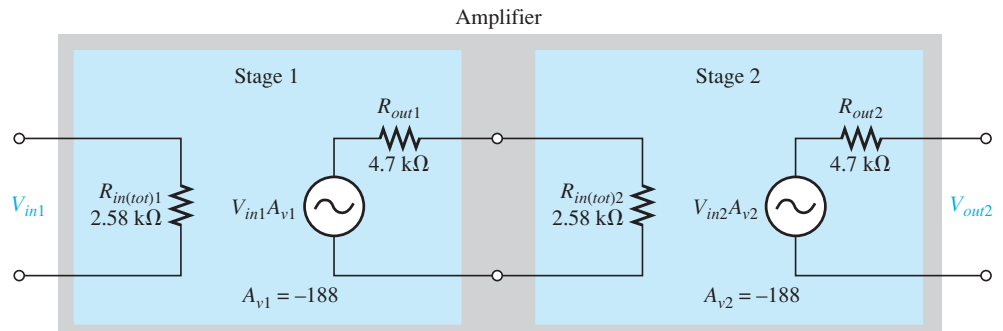


FIGURE 5–3 AC model of the complete two-stage amplifier.

The unloaded gain of each stage is -188 , as previously calculated. The voltage divider between the stages accounts for loading effects. It consists of $R_{in(tot)2}$ for stage 2 and R_{out1} for stage 1. The gain (attenuation) of this voltage divider is

$$A_{v(divider)} = \frac{R_{in(tot)2}}{R_{out1} + R_{in(tot)2}} = \frac{2.58 \text{ k}\Omega}{4.7 \text{ k}\Omega + 2.58 \text{ k}\Omega} = 0.35$$

The overall voltage gain is the product of the three gains.

$$A_{v(tot)} = A_{v1} A_{v(divider)} A_{v2} = (-188)(0.35)(-188) \cong 12,400$$

This product indicates the voltage gain is fairly large. If an input signal of $100 \mu\text{V}$, for example, is applied to the first stage and the attenuation of the input base circuit is neglected, an output from the second stage of $(100 \mu\text{V})(12,400) = 1.24 \text{ V}$ will result. Again, a factor that must be kept in mind is that this answer is approximate because the gain is very dependent on the value of r'_e and the specific transistors used. At the price of reduced gain, greater stability can be achieved by adding a swamping resistor in the emitter circuit. This will tend to make the circuit produce consistent gain that is independent of the specific transistor.

The gain for amplifiers is frequently expressed as a decibel voltage gain. For the amplifier just considered, the unloaded decibel voltage gain of each stage is

$$A'_v = 20 \log A_{v,h} = 20 \log(188) = 45.5 \text{ dB}$$

The gain (attenuation) of the voltage divider between the stages is

$$A'_{v(\text{divider})} = 20 \log(0.35) = -9.1 \text{ dB}$$

The overall decibel voltage gain is the sum of the individual decibel voltage gains.

$$A'_{v(\text{tot})} = A'_{v1} + A'_{v(\text{divider})} + A'_{v2} = 45.5 \text{ dB} - 9.1 \text{ dB} + 45.5 \text{ dB} = 81.9 \text{ dB}$$

MULTISIM




Open file F05-04 found on the companion website. This simulation will be used to determine if the dc and ac calculations in Example 5-1 are accurate.

EXAMPLE 5-1

Draw the simplified ac model and compute the overall gain for the two-stage preamplifier in Figure 5-4. Assume the g_m of Q_1 is $1500 \mu\text{mhos}$ (typical for a 2N5458) and the β_{ac} is 150 (typical of the 2N3904). The first stage provides a very high input resistance circuit with low noise. The second stage provides voltage gain.

FIGURE 5-4

 

SOLUTION

Start with the dc parameters. The input stage shown in Figure 5-4 is composed of a FET (Q_1) that uses current-source biasing from Q_2 . The drain of Q_2 should be approximately 0 V. The second stage is composed of the BJT, Q_3 , with emitter biasing. Because of emitter biasing, the emitter voltage will be close to -1 V. Applying Ohm's law, the emitter current is approximately

$$I_E = \frac{V_E - (-V_{EE})}{R_{E1} + R_{E2}} = \frac{-1 \text{ V} - (-15 \text{ V})}{100 \Omega + 22 \text{ k}\Omega} = 0.63 \text{ mA}$$

The collector dc voltage is

$$V_C = V_{CC} - I_E R_C = 15 \text{ V} - (0.63 \text{ mA})(15 \text{ k}\Omega) = 5.6 \text{ V}$$

Now determine the ac parameters. The input resistance of the first stage, $R_{in(\text{tot})1}$, is that of a reverse-biased pn junction. It is very high; a precise value depends on I_{GSS} . It is sufficient to estimate it as $>1 \text{ M}\Omega$. The output resistance of the first stage is the 560Ω source resistor in series with r'_s . Therefore,

$$R_{out1} = R_1 + r'_s = 560 \Omega + \frac{1}{g_m} = 560 \Omega + \frac{1}{1500 \mu\text{mhos}} = 1.23 \text{ k}\Omega$$

The value of r'_e is

$$r'_e = \frac{25 \text{ mV}}{I_E} \cong \frac{25 \text{ mV}}{0.63 \text{ mA}} \cong 40 \Omega$$

The unloaded voltage gain of the first stage is 1.0 (because of the current-source biasing). The unloaded voltage gain of the second stage is

$$A_{v2} = -\frac{R_C}{R_e} = -\frac{R_C}{r'_e + R_{E1}} \cong -\frac{15 \text{ k}\Omega}{40 \text{ }\Omega + 100 \text{ }\Omega} \cong -107$$

The input resistance of the second stage acts as a load on the first stage. To find the input resistance, note that the emitter-bias resistor and the ac resistance of the base form a parallel combination given by

$$R_{in(tot)2} = R_3 \parallel [\beta_{ac}(r'_e + R_{E1})]$$

Assuming a β_{ac} of 150,

$$R_{in(tot)2} \cong 100 \text{ k}\Omega \parallel [150(40 \text{ }\Omega + 100 \text{ }\Omega)] \cong 17.3 \text{ k}\Omega$$

The output resistance is just the collector resistor, R_C .

$$R_{out2} = R_C = 15 \text{ k}\Omega$$

These values are shown on the simplified circuit in Figure 5-5; the unloaded gain values are also shown. The output resistance and the load resistor form a voltage divider that reduces the gain of the last stage. Thus, the overall voltage gain is

$$\begin{aligned} A_{v(tot)} &= (A_{v1}) \left(\frac{R_{in(tot)2}}{R_{out1} + R_{in(tot)2}} \right) (A_{v2}) \left(\frac{R_L}{R_{out2} + R_L} \right) \\ &= (1) \left(\frac{17.3 \text{ k}\Omega}{1.23 \text{ k}\Omega + 17.3 \text{ k}\Omega} \right) (-107) \left(\frac{10 \text{ k}\Omega}{15 \text{ k}\Omega + 10 \text{ k}\Omega} \right) = -40 \end{aligned}$$

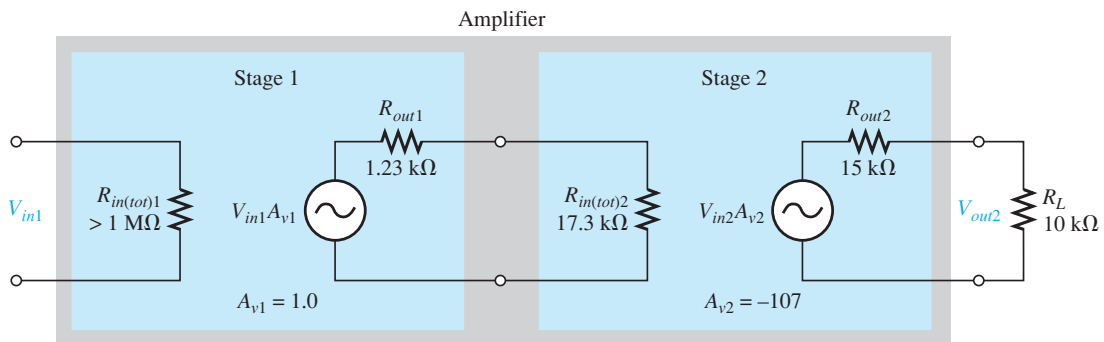



FIGURE 5-5

PRACTICE EXERCISE*

- If the input voltage in Figure 5-4 is 10 mV, what is the output voltage?
- What is the voltage gain of the amplifier in Figure 5-4 if the load resistor is removed?

*Answers are at the end of the chapter.

SYSTEM EXAMPLE 5-1

 

An Active FM Antenna

High-frequency communication systems are often characterized by very small signals that are in the presence of noise. When these signals are transmitted on a coax or other type of transmission line some distance to the main receiver, they tend to be attenuated (reduced in amplitude) and are subject to interference, further degrading the signal. This is a case where the addition of an active antenna is useful. Typically the active antenna is located close to the antenna and it may be followed by a low-output impedance buffer amplifier as

shown in the block diagram in Figure SE5-1. This arrangement allows it to amplify a weak signal before it is further degraded by the receiver.

 


FIGURE SE5-1 An active antenna driving a receiver or buffer amplifier.

An active antenna is designed to be a low noise preamp; that is, it amplifies the high-frequency signal and introduces only a minimal amount of noise. JFETs are suited to this application because they have low-noise and high input impedance. They can run on very low power, so it is supplied by a battery, which has the advantage of isolating the sensitive circuits from noise conducted in the power supply lines. It also enables the amplifier to be placed physically close to the antenna itself to provide gain before the transmission line (usually coax). The added signal strength at the output is sufficient to enable the rest of the receiver system process the signal for the final application.

Figure SE5-2 shows the basic active antenna circuit. It uses two low-noise, high-frequency JFETs in a cascode arrangement. L_1 serves as a peaking coil that will optimize the frequency response curve for the desired band. The gain of this circuit is about 25 from 88 MHz to 108 MHz with a slightly higher peak at the center of the band, which makes it suitable for an FM radio active antenna.

 


FIGURE SE5-2 An active antenna.

MULTISIM



Open file SE05-02 found on the companion website. You can view the frequency response with the Bode plotter.

Unwanted Oscillation and Noise


Multistage amplifiers require careful design to avoid unwanted oscillations. When large signals are present in the same circuit as small signals, the large signal can have an adverse effect on the small signal due to unwanted feedback paths. This problem is compounded in high-frequency amplifiers because feedback paths tend to have lower reactance, causing more unwanted feedback. For example, protoboards have stray capacitances between rows that can lead to feedback and noise problems when constructing multistage amplifiers on them. It is usually helpful to isolate the various stages by connecting a capacitor between

V_{CC} and ground at each stage; this technique is seen frequently in commercial printed circuit (PC) boards. Capacitors should be connected very close to the point that V_{CC} is applied to a stage and should have short lead lengths.

In addition to unwanted oscillations, noise voltages (unwanted electrical disturbances) can be a problem for multistage amplifiers. The ratio of signal to noise determines if the noise is sufficient to disrupt the signal. When the signal is small, a little noise voltage has a greater effect than when the signal is large. This means the first stage of an amplifier is the most important stage because of the very small signal level. FETs have the advantage for high-impedance sources; but when the source impedance is lower ($<1\text{ M}\Omega$), bipolar transistors can provide excellent low-noise performance.

Much has been written on the subject of noise in circuits. The “cure” for noise problems depends on the source of the noise, the path into the circuit, the type of noise, and other details. Many times, there is no *one* solution to a noise problem. Noise can enter a circuit from sources external to the circuit (such as fluorescent lighting) by capacitive or inductive coupling, through the power supply, or from within the circuit (thermal noise). The following are suggestions for avoiding noise problems:

 1. Keep wiring short to avoid “antennas” in circuits (particularly low-level input lines) and make signal return loops as small as possible.
2. Use capacitors between power supply and ground at each stage and make sure the power supply is properly filtered.
3. Reduce noise sources, if possible, and separate or shield the noise source and the circuit. Use shielded wiring, twisted pair, or shielded twisted pair wiring for low-level signals.
4. Ground circuits at a single point, and isolate grounds that have high currents from those with low currents by running separate ground lines back to the single point. Ground current from a high current ground can generate noise in another part of a circuit because of IR drops in the conductive paths.
5. Keep the bandwidth of amplifiers no larger than necessary to amplify only the desired signal, not extra noise.




An ECG Sensor and Preamp

Electrocardiography (ECG) is a diagnostic method to monitor proper heart function. An ECG system is discussed in Section 12-1; in this system note our focus is the electrode connections to the body that pick up the signal for the rest of the system.

Traditionally, conductive electrodes have been directly attached to the skin using contact gel to provide a resistive connection. Unfortunately, this type of electrode has certain disadvantages due to direct body contact, such as degradation of the sensor surface due to drying of the gel over long-term use. Also, metal allergies can cause skin irritations, especially in infants.

An alternative method of picking up the signal is with dry non-contact electrodes that are capacitively coupled to a preamp that can amplify the ECG signal even through clothing without making a conductive contact to the body. Figure SN5-1 shows one channel of the input portion of a capacitively-coupled ECG system. Notice that the body serves as the source of the heart signal and one plate of the capacitor and a conductive electrode forms the second plate. The patient’s clothing can form the insulating dielectric; in the case illustrated, it is the shirt. The ECG signal is connected to a small preamplifier to amplify the signal before it is contaminated by noise. A JFET is ideally suited as a first stage to the preamp, because it has very high input resistance and very low noise.

FIGURE SN5-1 A capacitively coupled signal from an ECG sensor.

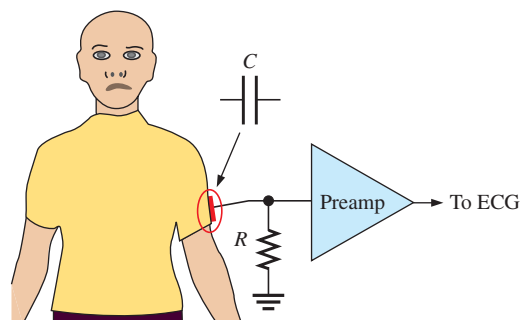

SECTION 5-1 CHECKUP*

1. What three parameters are needed for each stage of a multi-stage amplifier to determine the gain?
2. What is the decibel gain of the amplifier in Example 5-1?
3. What advantages do FETs have as the input stage to a multi-stage amplifier?
4. Why is the first stage of a multistage amplifier the most important for reducing noise?

* Answers are at the end of the chapter.

5-2 RF AMPLIFIERS

In general, radio frequencies (RF) are those frequencies that are useful for radio transmission—from a practical low frequency of about 10 kHz to above 300 GHz. Above approximately 100 kHz, amplifiers often use tuned resonant circuits at the input, output, or load, so many people prefer to consider amplifiers that use frequencies above 100 kHz as RF amplifiers. At these higher frequencies, amplifiers are designed to provide gain only for those frequencies within a certain band. In this section, practical considerations for high-frequency amplifiers are given. In the next section, you will see how high-frequency signals can be coupled with transformers from one stage to another.

After completing this section, you should be able to

- Describe the characteristics of high-frequency amplifiers and give practical considerations for implementing high-frequency circuits
- Explain the need for transmission lines when working with high frequencies
- Find the characteristic impedance of a cable, given the inductance and capacitance per unit length
- Explain the proper way to terminate a cable to avoid reflections
- Describe important ac considerations for RF amplifiers
- Explain what is meant by neutralization
- Explain how AGC works

Transmission Lines

When high-frequency signals or fast-rising digital signals are transferred from one point to another, the wiring can have adverse effects such as attenuation of the signal, a decrease in high-frequency response, and noise pickup. These effects are important for signal path lengths of a few inches when the frequency is above approximately 100 MHz or the rise time of a digital signal is less than approximately 4 ns.

Consider two wires that form a transmission line to send a high-frequency signal from one point to another. The wires have an inductance, L , that appears to be in series along the wires and a capacitance, C , that appears to be in parallel between the conductors. (Two conductors separated by an insulator form a capacitor.) At high frequencies, the reactance of the series inductance increases and the reactance of the parallel capacitance decreases. The L and C of the wiring is not “lumped” in one place but is distributed over the entire length of the line.

Figure 5-6(a) illustrates an equivalent circuit for a very short section of transmission line in which the inductance and capacitance are drawn as discrete components, but keep in mind they are distributed evenly throughout the wire. The inductance is shown as four inductors, each with an inductance of $L/4$. The capacitance of the short section is shown as

 


FIGURE 5-6 Equivalent circuit for a transmission line at high frequencies.

C . Resistance is also present but forms a minor part of the impedance at high frequencies, so it can be ignored.

To help you understand a transmission line, the equivalent circuit for a very short section is extended into a series of short sections of discrete inductors and capacitors connected together as shown in Figure 5-6(b). If additional sections are added to the equivalent circuit, you would observe an interesting effect; after about ten sections, the impedance of the line hardly changes as more and more sections are added. *The impedance does not depend on the length of the line!* The constant value of impedance is known as the *characteristic impedance* of the line. At high frequencies, the value of the characteristic impedance of a line is given by the following equation:

$$Z_0 = \sqrt{\frac{L}{C}} \quad (5-1)$$

where Z_0 = characteristic impedance of the line, in ohms (Ω)

L = inductance per unit length of line, in henries (H)

C = capacitance per unit length of line, in farads (F)

Note that L and C have to be measured for the same length of line. Since the equation uses a ratio, the length used does not matter, only that the lengths used are the same. The impedance of a cable is a function of its geometry and the type of dielectric that is used to construct the cable. There are various types of cables for high-frequency applications. They should all have a relatively high bandwidth and have a constant impedance independent of the length.

One common type of high-frequency transmission line is called **coax**. With coax, a center conductor is surrounded by a tubular conducting shield. At high frequencies, this outer conductor acts as a shield and helps avoid radiating signals from the cable or adding unwanted external interference noise to the signal. Various types of coax are available with a range of characteristics, including power handling, high-frequency characteristics, and the characteristic impedance.

It is important to install the type of cable that was designed for use in a given system. For example, video systems are standardized on 75 Ω coaxial cable. Depending on the type of line, transmission lines have characteristic impedances that are typically between 50 Ω and 100 Ω for coax cable and up to several hundred ohms for parallel conductors.

Because of its high bandwidth, coax is applied to some communication systems where many different voice channels can be put on the same cable. Frequency separation filters allow transmission in both directions at the same time.

EXAMPLE 5-2

Determine the characteristic impedance of RG58C coaxial cable, which has a capacitance of 28.5 pF per foot and an inductance of 7.12 μH per 100 feet. (RG means Radio Grade.)

SOLUTION

To determine the characteristic impedance, the capacitance and inductance must be specified for the same length of cable. To convert the capacitance to pF per

100 feet, multiply the capacitance per foot by 100. Therefore, C is 2850 pF per 100 feet. Substituting into Equation (5-1),

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{7.12 \mu\text{H}}{2850 \text{ pF}}} = 50 \Omega$$

PRACTICE EXERCISE

Compute the characteristic impedance of RG59B coaxial cable, which has a capacitance of 21.0 pF per foot and an inductance of 11.8 μH per 100 feet.

Terminating Transmission Lines


At high frequencies, even a short transmission line may be long compared to the wavelength of the signal. When the signal from the source (the incident wave) reaches the end of the line, it can be reflected back toward the source (the reflected wave). The incident and reflected waves interact along the length of the line, creating a **standing wave** on the line. A standing wave is a stationary wave formed by the interaction of an incident and reflected wave.

Standing waves create undesired effects such as “ghosts” in a television signal and increased noise. To prevent standing waves, transmission lines are terminated with a resistive load equal to the characteristic impedance of the line. The entire transmission line looks resistive to the source when it is terminated in this manner. When properly terminated, all of the signal power is dissipated in the terminating resistor. Improper termination can result in reflections and the wrong signal level.

If a transmission line is damaged or broken, the change in characteristic impedance results in signal reflections. A piece of test equipment called a time-domain reflectometer (TDR) can be used to find the location where the cable is damaged. The TDR applies a voltage pulse to the cable and times the arrival of any reflected signal. If the cable is undamaged and properly terminated, there should be little if any reflected signal measured. If the cable is damaged or broken, then there will be a reflection of the applied pulse from the point at which the cable is damaged. Since the propagation speed of a given cable is a constant, by measuring the time it takes for the signal to reflect back to the source, the location of the damage can be determined.

TDR is used in a wide variety of applications such as long coaxial cable runs and fiber optic systems (optical TDR). It can also be used in surveillance security to find wire taps. The tap causes a slight change in cable impedance that a sensitive TDR system can detect. TDR can even be used to find faults in high-frequency circuit boards where the traces are designed to act like transmission lines.

SYSTEM NOTE

 

High-Frequency Considerations

INDUCTIVE EFFECTS At high frequencies (above approximately 10 MHz), wire is no longer a simple conductive path but becomes an effective inductor. This happens because of an effect known as **skin effect**, which causes current to move to the outside surface of conductors. The addition of inductance in a signal path is generally undesirable because it increases the reactance in the signal line and can increase noise in the circuit. To avoid adverse inductive effects, wiring in high-frequency circuits should be kept as short as possible.

CAPACITANCE EFFECTS At high frequencies, transistor amplifiers are less effective because of the increased effect of capacitance. All active devices have internal capacitances between their terminals. These internal capacitances appear as a low-impedance path for high-frequency analog signals, reducing the effectiveness of the device. In digital

circuits, internal capacitances limit the speed at which a pulse can change from one level to another. Transistors for high frequencies are specially designed to minimize the internal capacitances.

The adverse effects of capacitance are magnified by inverting amplifiers (such as a common-source or common-emitter amplifier) due to a form of positive feedback called the *Miller effect*. As a rule, it is best to try to minimize capacitance in high-frequency circuits by keeping wiring as short as possible and by avoiding high-gain inverting type amplifiers.

Another effect of capacitance is that undesired oscillations can be produced in high-frequency amplifiers. Oscillations are eliminated by a technique called *neutralization*, discussed later in this section.

Tuned Amplifiers

Amplifiers with resonant circuits are common in communication applications because communication systems use high frequencies. Frequencies greater than 100 kHz are commonly referred to as RF for *Radio Frequency*. Amplifiers that are designed for these high frequencies are called RF amplifiers. The techniques you learned for finding dc bias conditions with low-frequency amplifiers are the same for RF amplifiers but need to be modified for ac considerations. Low-frequency amplifiers are untuned; they are designed to amplify a wide band of frequencies.

Tuned amplifiers are different; they are designed to amplify a specific band of frequencies while eliminating any signals outside the band. They use a parallel *LC* resonant circuit for a load to provide a high impedance to the ac signal and thus produce a high gain at the resonant frequency. The center frequency (assuming *Q* is large) of the tuned circuit can be computed from the basic resonant frequency equation:

$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad (5-2)$$

The bandwidth of a tuned amplifier is determined by the *Q* (quality factor) of the resonant circuit. The **quality factor (*Q*)** is a dimensionless number that is the ratio of the maximum energy stored in a cycle to the energy lost in a cycle. From a practical view, the inductor almost always determines the *Q*; consequently *Q* is often expressed as the ratio of the inductive reactance, X_L , to the resistance, *R*. It is also the ratio of the center (resonant) frequency, f_r , to the bandwidth, *BW*.

$$Q = \frac{X_L}{R} = \frac{f_r}{BW} \quad (5-3)$$

The response of a parallel resonant circuit depends on the *Q* of the circuit, as illustrated in Figure 5-7. The *Q* for an RF circuit depends on the type of inductor; it can range from 50 to 250 for ferrite-core inductors and even higher for air-core inductors.

A basic tuned RF amplifier, using a JFET, is shown in Figure 5-8. The gate and drain circuits each have a parallel resonant circuit using a transformer coil and a capacitor to form the resonant circuit. (Transformer coupling is discussed in Section 5-3.) The dashed-line capacitor between the drain and gate represents an internal capacitance of the transistor, a capacitance of only a few pF. The drain circuit presents a high impedance to the ac signal but easily passes the dc quiescent current through the transformer's primary coil, which looks like a small resistance to dc.

Despite the fact that the internal capacitance between the drain and gate is very small, at high frequencies it may produce sufficient positive feedback (in phase) from the output back to the input to cause the amplifier to break into undesired oscillation. To prevent this, a neutralization circuit is sometimes necessary, particularly for high-impedance circuits.

Neutralization is the process of adding the same amount of negative feedback (out of phase) to just cancel the positive (in phase) feedback due to the internal capacitances of an amplifier. Figure 5-9 shows a popular neutralization circuit called

 


FIGURE 5-7 Impedance of a parallel resonant circuit as a function of frequency.

 


FIGURE 5-8 A tuned RF amplifier.

Hazeltine neutralization. The neutralization is accomplished by sending a negative feedback signal from the output back to the input through a small neutralization capacitor, C_n , which is adjusted to just cancel the undesired positive-feedback signal. Notice that the drain power supply is now connected through a center-tapped transformer.

Figure 5-10 shows another popular circuit for an RF amplifier that uses a dual-gate D-MOSFET to amplify antenna signals. The dual-gate configuration simplifies adding **automatic gain control (AGC)** to the circuit because the signals are combined within the MOSFET. The AGC reduces the gain when a larger signal is received and increases the gain for smaller signals. The RF signal is connected to the lower gate while the upper gate is used to control the gain. The AGC signal is a negative dc voltage (for an n -channel device) that is developed from a later stage in the amplifier. The AGC voltage is proportional to the input signal strength. A large input signal produces a larger AGC voltage, tending to pinch off the channel and thus reducing the gain.

 


FIGURE 5-9 Hazeltine neutralization. C_n cancels the internal capacitance.

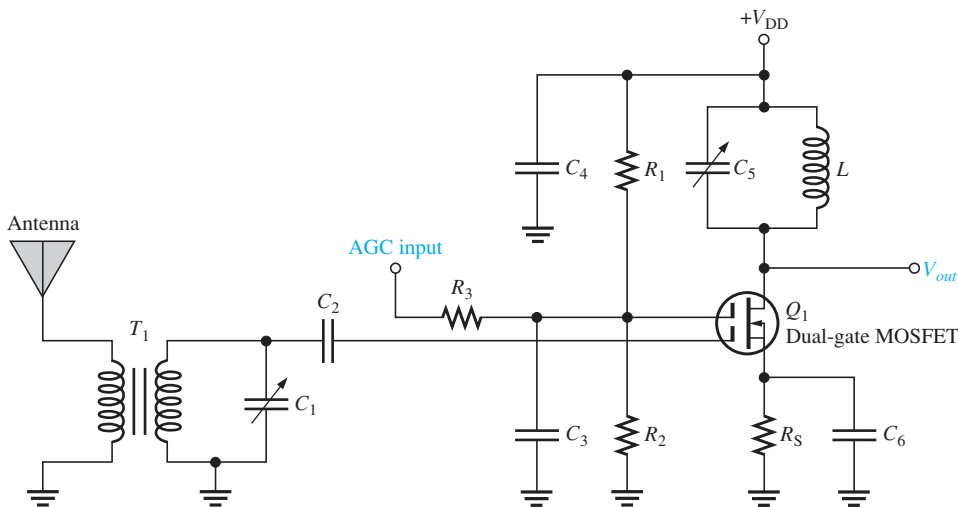


FIGURE 5-10 RF amplifier using a dual-gate depletion-mode MOSFET.

SECTION 5-2 CHECKUP

1. What are the advantages of coax cable for passing an RF signal?
2. What is meant by neutralization?
3. What is AGC?
4. What is the definition of Q ?

5-3 TRANSFORMER-COUPLED AMPLIFIERS

Transformers can be used to couple a signal from one stage to another. Although principally used in high-frequency designs, they are also found in low-frequency power amplifiers. When the signal frequency is in the RF range (> 100 kHz), stages within an amplifier are frequently coupled with tuned transformers, which form a resonant circuit. In this section, you will see examples of transformer-coupled amplifiers—both low-frequency and high-frequency tuned amplifiers.

After completing this section, you should be able to

- Describe the characteristics of transformer-coupled amplifiers, tuned amplifiers, and mixers
- Describe in general how a transformer-coupled amplifier operates
- Determine the ac and dc load line for a transformer-coupled amplifier
- Explain how a high frequency is converted to a lower frequency with a mixer
- Give advantages for using an IF amplifier in a high-frequency application

Low-Frequency Applications

Most amplifiers require that the dc signal be isolated from the ac signal. In Section 5-1, you learned how a capacitor could be used to pass the ac signal while blocking the dc signal. Transformers also block dc (because they provide no direct path) and pass ac.

In addition, transformers provide a useful means of matching the impedance of one part of a circuit to another. From basic dc/ac circuits courses, recall that a load on the secondary side of a transformer is changed by the transformer when looking from the primary side. A step-down transformer causes the load to look larger on the primary side as expressed by

$$R'_L = \left(\frac{N_{pri}}{N_{sec}} \right)^2 R_L \quad (5-4)$$

where R'_L = reflected resistance on the primary side
 N_{pri}/N_{sec} = ratio of primary turns to secondary turns
 R_L = load resistance on the secondary side

Transformers can be used at the input, the output, or between stages to couple the ac signal from one part of a circuit to another. By matching impedances in a power transformer, maximum power can be transferred (discussed in Section 5-4). Transformers can also be used for matching the impedance of a source to a line. Line-matching transformers are used primarily for low-impedance circuits ($< 200 \Omega$). For voltage amplifiers, a transformer can also step up the voltage to the next stage (but never the power).

Figure 5-11 shows examples of transformer coupling in a two-stage amplifier. Small low-frequency transformers are occasionally used in certain microphones or other transducers to couple a signal to an amplifier.

 


FIGURE 5-11 A basic transformer-coupled amplifier showing input, coupling, and output transformers.

Although transformer coupling can give higher efficiency than RC coupling, transformer coupling is not widely applied to low-frequency designs because of two major drawbacks. First, transformers are more expensive and are much bulkier than capacitors. Second, they tend to have poorer response at high frequencies due to the reactance of the coils. For these reasons, low-frequency transformer coupling is not commonly used except in certain class A power amplifiers.

EXAMPLE 5-3

Assume the component values for the second stage of Figure 5-11 are as follows: $R_4 = 5.1 \text{ k}\Omega$, $R_5 = 2.7 \text{ k}\Omega$, $R_6 = R_E = 680 \text{ }\Omega$, and $R_L = 50 \text{ }\Omega$; transformer T_3 is a 5:1 step-down transformer and $V_{CC} = 12 \text{ V}$. Draw the dc and ac load lines for the stage.

SOLUTION

Start with the dc conditions. Find the base voltage by applying the voltage-divider rule to the bias resistors.

$$V_B = \left(\frac{R_5}{R_4 + R_5} \right) V_{CC} = \left(\frac{2.7 \text{ k}\Omega}{5.1 \text{ k}\Omega + 2.7 \text{ k}\Omega} \right) 12 \text{ V} = 4.2 \text{ V}$$

Next, calculate the emitter voltage and current.

$$V_E = V_B - V_{BE} = 4.2 \text{ V} - 0.7 \text{ V} = 3.5 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{3.5 \text{ V}}{680 \text{ }\Omega} = 5.15 \text{ mA}$$

The emitter current is approximately equal to the collector current and represents the current at the Q-point, I_{CQ} . The dc resistance of the transformer primary is small and can be ignored. With this assumption, the transformer has no effect on the dc load line. V_{CE} is the difference between V_{CC} and the drop across the emitter resistor.

$$V_{CEQ} \cong V_{CC} - V_E = 12 \text{ V} - 3.5 \text{ V} = 8.5 \text{ V}$$

You can now draw the dc load line because you know two of the points on the line (the Q-point and $V_{CE(\text{cutoff})}$). As confirmation, determine the dc saturation current by finding the current if the transistor's collector is shorted to the emitter.

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_E} = \frac{12 \text{ V}}{680 \text{ }\Omega} = 17.6 \text{ mA}$$

Now proceed to find the ac load line by starting with the ac resistance in the collector circuit. To find the equivalent reflected resistance of the load resistor on the primary side, apply equation (5-4).

$$R'_L = \left(\frac{N_{pri}}{N_{sec}} \right)^2 R_L = \left(\frac{5}{1} \right)^2 50 \Omega = 1.25 \text{ k}\Omega$$

This represents the entire ac resistance (ignoring r'_e) for the collector-emitter circuit as the emitter resistor is bypassed by C_4 . Recall from Section 3-4 that the ac saturation current is found from

$$I_{c(sat)} = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

Substituting the values of I_E and R'_L for I_{CQ} and R_{ac} , the ac saturation current is

$$I_{c(sat)} = 5.15 \text{ mA} + \frac{8.5 \text{ V}}{1.25 \text{ k}\Omega} = 11.95 \text{ mA}$$

From the two points found (the Q-point and $I_{c(sat)}$), you can construct the ac load line. As confirmation, determine the ac cutoff voltage, $V_{ce(cutoff)}$.

$$V_{ce(cutoff)} = V_{CEQ} + I_{CQ}R_{ac} = 8.5 \text{ V} + (5.15 \text{ mA})(1.25 \text{ k}\Omega) = 14.9 \text{ V}$$

The result is shown in Figure 5-12.

 


FIGURE 5-12

PRACTICE EXERCISE

If you replaced the transformer in this example with one with a turns ratio of 6:1, what, if anything, happens to the Q-point? What happens to the ac load line?

Example 5-3 illustrates an important point about transformer-coupled amplifiers. Unlike previous examples that showed capacitively coupled amplifiers, the ac load line is not as steep as the dc load line. The ac saturation current is *lower* than the dc saturation current and the ac cutoff voltage is *larger* than the dc cutoff voltage (V_{CC}).

High-Frequency Applications

At higher frequencies, transformers are much smaller, are less expensive, and offer important advantages for coupling signals over a limited bandwidth. As you saw in the last section, at high frequencies a transformer primary can be connected with a parallel capacitor

to form a high- Q resonant circuit. Frequently, the secondary winding, with an appropriate capacitor across it, is also connected as a resonant circuit.

From basic dc/ac courses, you learned that a parallel resonant circuit is an LC combination that has an impedance maximum at the resonant frequency. This high impedance at the resonant frequency means that the gain of the amplifier can be very high at frequencies near the resonant frequency while offering little opposition to dc. This forms a very efficient narrow bandwidth amplifier (typically 10 kHz) with gains as high as 1000 or so. Furthermore, the amplifier is tailored to amplify a very narrow band of frequencies containing the signal of interest and not amplify other frequencies.

During signal processing, a radio frequency is usually converted to a lower frequency by mixing the RF with an oscillator. The new lower frequency that is produced is called an **Intermediate Frequency** or IF. Tuned transformer coupling is important in both RF and IF amplifiers.

The principal advantage to using IF is that it is a fixed frequency and requires no changes in the tuned circuit for any given RF signal (within design limits). This is accomplished by causing the oscillator to “track” the RF. Since the IF is fixed, it is easy to amplify with a fixed-resonant circuit, without need for the user to adjust any controls. This idea, first developed by Major Edwin Armstrong during World War I, is found in most communication equipment and is also used in the spectrum analyzer, an important piece of high-frequency test equipment.

Figure 5-13 shows an example of a two-stage tuned amplifier that uses resonant circuits at both the input to the first stage and the output from the second stage. Transformer coupling is used between the stages. A circuit similar to this is part of most communication equipment and consists of an RF amplifier and a mixer. The RF amplifier tunes and amplifies the high-frequency signal from a station. The **mixer** is a nonlinear circuit that combines this signal with a sine wave generated from an oscillator.

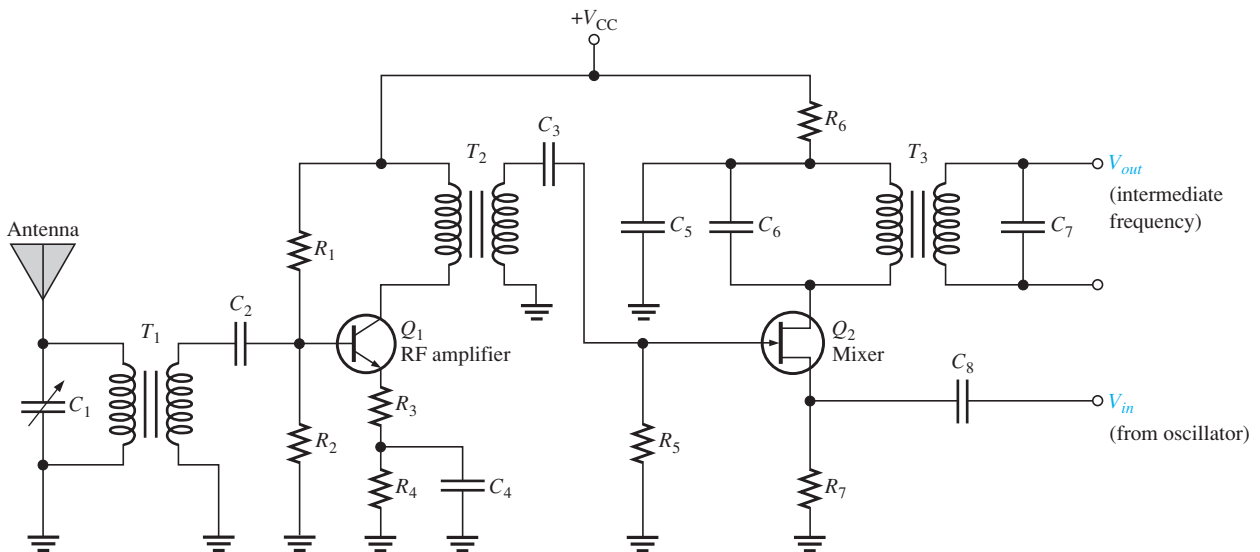


FIGURE 5-13 A tuned amplifier consisting of an RF stage and a mixer.

The oscillator’s frequency is set to a fixed difference from the RF. When the RF and oscillator signals are mixed in a nonlinear circuit, they produce two new frequencies: the sum of the input signals and the difference of the input signals. The second resonant circuit is tuned to the difference frequency, while rejecting all other frequencies. This difference frequency is the IF signal that is amplified further by the IF amplifier section. The advantage of an IF section is that it is specifically designed to process a single frequency.

Let’s examine the circuit in Figure 5-13(a) further. The first tuned circuit consists of the primary of T_1 , which resonates with C_1 to tune a station. Stations not at the resonant

frequency are rejected by the resonant circuit. Notice that Q_1 is biased with stable voltage-divider bias. There is no collector resistor, but instead, the ac signal “sees” the primary of transformer T_2 as a load. The gain for this stage is determined by the reactance in the collector circuit divided by the ac emitter resistance consisting of R_3 and r'_e .

The RF signal is passed to the gate of Q_2 by transformer T_2 where it is combined with the signal from the oscillator (not shown). Note that Q_2 is a CS amplifier for the RF signal, but a CG amplifier for the oscillator signal. The resonant circuit in the output of Q_2 is tuned to the desired difference frequency. Thus, the output of Q_2 is the intermediate frequency (IF), which is sent to the next stage for further amplification. In order to generate the intermediate frequency, Q_2 must operate as a nonlinear amplifier. FETs fulfill this role nicely. Often, the mixer is combined with the RF amplifier using a two-gate MOSFET such as introduced earlier.

Notice in Figure 5–13(a) that a resistor, R_6 , is in series with the voltage from the power supply. This resistor and C_5 form a low-pass filter called a **decoupling network** that helps isolate the circuit from other amplifiers and helps prevent unwanted oscillations. The resistor is a small value (typically 100 Ω) and the capacitor is selected to have a reactance that is $<10\%$ of this value at the operating frequency. (For example, a 100 Ω resistor can be bypassed with a capacitor that has a reactance of approximately 10 Ω .)

Figure 5–14 illustrates a MOSFET alternative to the JFET mixer circuit in Figure 5–13. This mixer is built around a dual-gate MOSFET as discussed in Section 4–5. The output from the RF amplifier is applied to one gate, and the signal from the oscillator is applied to the other gate. Like the JFET, the MOSFET functions as a nonlinear device producing the intermediate frequency.

 


FIGURE 5–14 A dual-gate MOSFET mixer.

An IF amplifier is shown in Figure 5–15. The IF transformer is designed for the specific intermediate frequency selected. The IF amplifier is in all respects an RF amplifier; the only difference between an IF and an RF amplifier is the function it serves in a given circuit. An IF amplifier uses a tuned input circuit and tuned output circuit to selectively amplify the intermediate frequency. The capacitor that forms the primary resonant circuit and the transformer are inside a metal enclosure that provides shielding. The exact intermediate frequency is adjusted with a tuning slug that is moved in and out of the core. Again, a decoupling network is included (R_3 and C_3). When tuning the IF circuit, it is important to use a high-impedance, low-capacitance test instrument to avoid changing the circuit response due to instrument loading.


 


FIGURE 5-15 An IF amplifier.

If you are using an oscilloscope to tune an RF amplifier in a system, you should use an active scope probe. An active probe has a specially designed IC amplifier in the probe tip. Active probes have very high input resistance, but more important, they have very low input capacitance. Modern active probes can have C_{in} values of less than 0.8 pF. The higher the signal frequency that you are trying to measure, the more effect that probe capacitance has (X_C decreases as f increases). Active probes are more expensive than passive probes, but they decrease instrument loading dramatically. Probe capacitance will change the resonant frequency of the tank circuit. This means that the resonant frequency of the circuit you have just tuned will change as soon as you remove your probe. The lower the probe capacitance, the less effect it will have on the circuit.

SYSTEM NOTE

 

The dc parameters for the circuit in Figure 5-14 are found the same way as in any CE amplifier. However, the tuned circuit affects the ac parameters differently than a circuit with just a collector resistor. With the parallel resonant circuit in the collector, the voltage gain of the amplifier is the ratio of the impedance of the resonant circuit to the ac resistance of the emitter circuit.

$$A_v = \frac{Z_c}{R_e}$$

where Z_c = impedance of the collector circuit

R_e = ac resistance of the emitter circuit

The impedance of the resonant circuit depends on the frequency and the Q of the resonant circuit. You can find the impedance, Z_c , at the resonance if you know X_L and Q .

$$Z_c = QX_L$$

Because of transformer action, the load resistor is part of the equivalent primary circuit and affects the frequency response of the tuned circuit; a smaller load resistor produces a lower Q and a broader response. Example 5-4 illustrates these ideas.

EXAMPLE 5-4

Assume the IF amplifier in Figure 5-16 has an IF transformer tuned to 455 kHz (a standard intermediate frequency). The primary has an inductance of 99.5 μH

and a resistance of 5.6Ω . Internally, there is a 1250 pF capacitor connected in parallel with the primary.

- Find the Q of the resonant circuit, the unloaded voltage gain, $A_{v(\text{NL})}$, and the bandwidth, BW .
- Find the voltage gain and new bandwidth if a $1.0 \text{ k}\Omega$ load resistor is connected across the secondary, causing the Q of the resonant circuit to be reduced to 20.

 


FIGURE 5-16

SOLUTION

- Compute the dc parameters first. The dc drop across R_3 is very small and can be ignored.

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC} = \left(\frac{4.7 \text{ k}\Omega}{15 \text{ k}\Omega + 4.7 \text{ k}\Omega} \right) 9 \text{ V} = 2.15 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.15 \text{ V} - 0.7 \text{ V} = 1.45 \text{ V}$$

$$I_E = \frac{V_E}{R_{E1} + R_{E2}} = \frac{1.45 \text{ V}}{100 \Omega + 510 \Omega} = 2.38 \text{ mA}$$

The ac parameters are

$$r'_e \cong \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{2.38 \text{ mA}} = 10.5 \Omega$$

$$X_L = 2\pi fL = 2\pi(455 \text{ kHz})(99.5 \mu\text{H}) = 284 \Omega$$

$$Q = \frac{X_L}{R} = \frac{284 \Omega}{5.6 \Omega} = 50.7$$

$$Z_c \cong QX_L = (50.7)(284 \Omega) = 14.4 \text{ k}\Omega$$

$$A_{v(\text{NL})} = \frac{Z_c}{R_e} = \frac{Z_c}{r'_e + R_{E1}} = \frac{14.4 \text{ k}\Omega}{10.5 \Omega + 100 \Omega} = 130$$

$$BW = \frac{f_r}{Q} = \frac{455 \text{ kHz}}{50.7} = 9.0 \text{ kHz}$$

- The addition of a load has no effect on the dc parameters, r'_e , or X_L . The reflected resistance of the secondary reduces the Q and therefore the impedance of the resonant circuit. The new impedance of the resonant circuit is

$$Z_c = QX_L = (20)(284 \Omega) = 5.68 \text{ k}\Omega$$

The voltage gain and bandwidth are

$$A_v = \frac{Z_c}{R_e} = \frac{Z_c}{r'_e + R_{E1}} = \frac{5.68 \text{ k}\Omega}{10.5 \Omega + 100 \Omega} = 51$$

$$BW = \frac{f_r}{Q} = \frac{455 \text{ kHz}}{20} = 23 \text{ kHz}$$


PRACTICE EXERCISE

What effect, if any, would an open C_2 have on the voltage gain? On the bandwidth?

Cable TV Systems

The concept of frequency shifting that was the key idea for the original superheterodyne radio is applied to many types of systems today, including satellite and microwave systems. One common application of frequency shifting is in cable TV transmission, in which a signal is up-converted to a new higher frequency. A single coaxial cable channel may carry hundreds of television channels, each with its own frequency. The cable provider converts each channel to a unique higher frequency using the principle of heterodyning, where the television signal frequency is *added* to a local oscillator frequency, creating the new sum frequency. At the receiver, the cable box converts a selected high frequency signal back to the original (or *base-band*) frequency by combining the incoming signal with the same local oscillator frequency. The restored signal is sent on to the television receiver.

SYSTEM NOTE

 

SECTION 5-3 CHECKUP

1. What is the difference between an RF and an IF signal?
2. What is the function of a mixer?
3. What are the two signals mixed in a mixer?
4. What effect does a load resistor on the secondary of a tuned transformer have on the Q of the tuned circuit?
5. Why should a high-impedance, low-capacitance instrument be used to test an IF stage?

5-4 DIRECT-COUPLED AMPLIFIERS

Another important method for coupling signals is called **direct coupling**. With direct coupling, there are no coupling capacitors or transformers between stages. Depending on how the input and output signals are coupled, some amplifiers can operate with frequencies all the way down to dc. In this section, a direct-coupled amplifier is introduced, then negative feedback is added to stabilize the bias and the gain. Direct coupling will be applied again in Section 5-5 to power amplifiers.

After completing this section, you should be able to

- Determine basic dc and ac parameters for direct-coupled amplifiers and describe how negative feedback can stabilize the gain of an amplifier
- Describe how direct-coupled stages obtain bias
- Compute dc and ac parameters for a direct-coupled amplifier
- Explain how negative feedback can stabilize bias and gain

Figure 5–17 shows a direct-coupled amplifier. Direct coupling is from the collector of Q_1 to the base of Q_2 . Since the stages are direct coupled, bias current for Q_2 is supplied by Q_1 , eliminating the need for any bias resistors for Q_2 and eliminating a coupling capacitor between the stages. Although the stages are direct coupled, it is necessary in this particular amplifier to ac couple the input and output signals (through capacitors) to prevent the external signal source and the load from disturbing the dc voltages.

 


FIGURE 5–17 A direct-coupled amplifier without feedback.

Bias for Q_2 is supplied through R_{C1} , the collector resistor for Q_1 . Transistor Q_1 is relatively independent of β because it has voltage-divider bias, but Q_2 uses base bias, a method not desired in linear amplifiers because of the variation in β . In addition, thermal changes will cause the circuit to drift. Although this particular amplifier has fewer components than comparable capacitively coupled amplifiers, the drawbacks mentioned may outweigh the advantages. A relatively simple change—the addition of negative feedback—can cure the problem of β dependency and drift.

Negative Feedback for Bias Stability

The circuit in Figure 5–18 is a modification that greatly improves the bias stability of the amplifier in Figure 5–17 with an added bonus of reducing the parts count. Again, the input and output signals are capacitively coupled to avoid disturbing the bias voltages. Because there are two transistors, the feedback network, shown in red, takes advantage of the extra

 


FIGURE 5–18 A direct-coupled amplifier with negative feedback that produces bias stability.

gain over a single transistor and produces excellent stability for variations in β and for variations in temperature. This is similar to the negative feedback introduced in Section 3-2 for collector-feedback bias.

Let's look at how the feedback works in Figure 5-17. Start with Q_2 and note that its base is forward-biased by R_{C1} , causing a collector current in Q_2 or $I_{C(Q2)}$. This current causes the emitter voltage of Q_2 to rise, turning on Q_1 . As Q_1 conducts more, its collector voltage drops, reducing the bias on Q_2 . This action reduces the bias on Q_2 to a stable point determined by the particular design values.

The collector current for Q_1 can be computed by writing Kirchhoff's voltage law (KVL) around the path that includes V_{CC} , R_{C1} , $V_{BE(Q2)}$, R_F , $V_{BE(Q1)}$, and R_{E1} . From this, the collector current in Q_1 is approximately

$$I_{C(Q1)} = \frac{V_{CC} - 2V_{BE}}{R_{C1} + \frac{R_F}{\beta} + R_{E1}}$$

The circuit is designed such that R_{C1} is much larger than R_F/β or R_{E1} . Thus, $I_{C(Q1)}$ is almost completely independent of the value of β , producing a stable value of collector voltage in Q_1 and a stable base voltage in Q_2 . Thus, the β dependency problem associated with base bias is no longer a factor.

The collector current in Q_1 causes the collector voltage of Q_1 to be

$$V_{C(Q1)} = V_{CC} - I_{C(Q1)}R_{C1}$$

which is also the base voltage of Q_2 . The emitter voltage of Q_2 is $V_{C(Q1)} - 0.7$ V and the emitter current is found from Ohm's law.

$$I_{E(Q2)} = \frac{V_{C(Q1)} - 0.7 \text{ V}}{R_{E2}}$$

The feedback resistor, R_F , is not included in the calculation of $I_{E(Q2)}$ because it is much larger than R_{E2} . The approximation that $I_C \cong I_E$ enables you to find the collector current in Q_2 . Subtracting the voltage drop across R_{C2} from V_{CC} allows you to find $V_{C(Q2)}$. The following example illustrates a typical set of parameters for this circuit.

MULTISIM



Open file F05-18 found on the companion website. This simulation demonstrates the use of negative feedback for bias stability.

EXAMPLE 5-5

- For the circuit in Figure 5-19(a), find the dc parameters, $I_{C(Q1)}$, $V_{C(Q1)}$, $I_{E(Q2)}$, and $V_{C(Q2)}$ if the β of each transistor is 200.
- Compute the voltage gain and the output voltage if a 5 mV input signal is applied to the amplifier.

 


FIGURE 5-19(a)

SOLUTION

(a) Begin with the dc parameters. The collector current in Q_1 is approximately

$$I_{C(Q1)} = \frac{V_{CC} - 2V_{BE}}{R_{C1} + \frac{R_F}{\beta} + R_{E1}} = \frac{12 \text{ V} - 2(0.7 \text{ V})}{47 \text{ k}\Omega + \frac{100 \text{ k}\Omega}{200} + 100 \Omega} = \mathbf{0.223 \text{ mA}}$$

This current is in R_{C1} (plus the small base current of Q_2 that is not included). Find $V_{C(Q1)}$ as follows:

$$V_{C(Q1)} = V_{CC} - I_{C(Q1)}R_{C1} = 12 \text{ V} - (0.223 \text{ mA})(47 \text{ k}\Omega) = \mathbf{1.52 \text{ V}}$$

The emitter current in Q_2 is

$$I_{E(Q2)} = \frac{V_{C(Q1)} - 0.7 \text{ V}}{R_{E2}} = \frac{1.52 \text{ V} - 0.7 \text{ V}}{270 \Omega} = \mathbf{3.03 \text{ mA}}$$

Since $I_{C(Q2)} \cong I_{E(Q2)}$, this implies that the collector voltage of Q_2 is

$$V_{C(Q2)} = V_{CC} - I_{C(Q2)}R_{C2} = 12 \text{ V} - (3.03 \text{ mA})(2.0 \text{ k}\Omega) = \mathbf{5.94 \text{ V}}$$

Although this is a very stable arrangement, the calculation is sensitive to the exact collector current in Q_1 and the V_{BE} drop across Q_2 . Measured dc parameters will vary somewhat from the computed values depending on the particular transistors used.

(b) To compute the voltage gain, it is first necessary to find r'_e for each transistor. Assume $I_E = I_C$.

$$r'_{e(Q1)} = \frac{25 \text{ mV}}{I_{E(Q1)}} = \frac{25 \text{ mV}}{0.223 \text{ mA}} = 112 \Omega$$

$$r'_{e(Q2)} = \frac{25 \text{ mV}}{I_{E(Q2)}} = \frac{25 \text{ mV}}{3.03 \text{ mA}} = 9 \Omega$$

Then the unloaded voltage gain for each amplifier can be computed.

$$A_{v1(NL)} = -\frac{R_c}{R_e} = -\frac{R_{C1}}{R_{E1} + r'_{e(Q1)}} = -\frac{47 \text{ k}\Omega}{100 \Omega + 112 \Omega} = -222$$

$$A_{v2(NL)} = -\frac{R_c}{R_e} = -\frac{R_{C2}}{R_{E2} + r'_{e(Q2)}} = -\frac{2.0 \text{ k}\Omega}{270 \Omega + 9 \Omega} = -7.2$$

Next, compute the input and output resistance for each amplifier stage. Notice that the input resistance shows β dependency.

$$R_{in(tot)1} = [\beta_{ac}(R_{E1} + r'_{e(Q1)})] \parallel R_F = [200(100 \Omega + 112 \Omega)] \parallel 100 \text{ k}\Omega = 29.8 \text{ k}\Omega$$

$$R_{out1} = R_{C1} = 47 \text{ k}\Omega$$

$$R_{in(tot)2} = \beta_{ac}(R_{E2} + r'_{e(Q2)}) = 200(270 \Omega + 9 \Omega) = 55.8 \text{ k}\Omega$$

$$R_{out2} = R_{C2} = 2.0 \text{ k}\Omega$$

You can now compute the overall gain. Use the model of a multistage amplifier, introduced in Chapter 1 and shown in Figure 5–19(b). The overall voltage gain is

$$A_{v(overall)} = (A_{v1(NL)}) \left(\frac{R_{in(tot)2}}{R_{out1} + R_{in(tot)2}} \right) (A_{v2(NL)})$$

$$= (-222) \left(\frac{55.8 \text{ k}\Omega}{47 \text{ k}\Omega + 55.8 \text{ k}\Omega} \right) (-7.2) = \mathbf{867}$$

Although this is a relatively high gain, measured values are likely to vary somewhat due to simplifying assumptions and β dependency. The variation is mainly due to the second term, which is dependent on β .

With the gain calculation completed, the output voltage can be found.

$$V_{out} = A_{v(overall)}V_{in} = (867)(5 \text{ mV}) = \mathbf{4.34 \text{ V}}$$

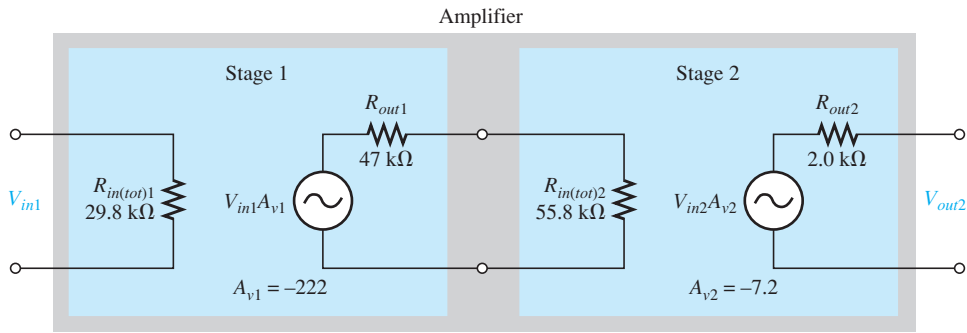


FIGURE 5-19(b)

PRACTICE EXERCISE

Determine the overall voltage gain of the amplifier if the β is 100 for each transistor.

Negative Feedback for Gain Stability

The amplifier illustrated in Example 5-5 has high gain but the gain is somewhat dependent on the β . Negative feedback provided excellent bias stability that was not dependent on a particular β . It's also possible to provide excellent gain stability that is independent of β by using negative feedback with the ac signal. As you will see, negative feedback produces a self-correcting action that stabilizes the voltage gain. The modification in Figure 5-20 shows how this is achieved.

 


FIGURE 5-20 Modification of the circuit in Example 5-5 to improve gain stability.

MULTISIM

Open file F05-20 found on the companion website. This simulation demonstrates the use of negative feedback for gain stability.

First, a bypass capacitor, C_2 , is connected in parallel with R_{E2} in order to boost the voltage gain even higher; this will produce greater gain stability when feedback is added. The gain without feedback is called **open-loop voltage gain**, which will be described further when you study operational amplifiers in Chapter 6. For the amplifier in Figure 5-20, the addition of the emitter capacitor boosts the open-loop voltage gain by a factor of approximately two.¹ Then a new path is added, consisting of C_3 and R_{F2} , to return a fraction of the output ac signal back to Q_1 . The fraction that is returned is determined by the

¹The gain would be even higher except for the adverse loading effect on Q_1 due to lower input resistance of Q_2 .

voltage divider consisting of R_{F2} and R_{E1} . For the amplifier in Figure 5–20, the feedback voltage, V_f , is equal to the output voltage multiplied by the feedback fraction.

$$V_f = \left(\frac{R_{E1}}{R_{E1} + R_{F2}} \right) V_{out}$$

This feedback voltage tends to cancel the original input signal. The signal that is amplified by the open-loop voltage gain is the small *difference* in the input and negative feedback signals. As a result, the net voltage gain of the amplifier is controlled by the amount of feedback. This net gain with feedback is called the **closed-loop voltage gain**. As mentioned, the closed-loop voltage gain is determined by the amount of output signal that is returned.

An implication of a very large open-loop voltage gain is that the difference between the feedback and input signals is very small at the input to Q_1 . For the amplifier in Figure 5–20, the ac signal on the base and emitter of Q_1 will have nearly the same amplitude.

Here’s how the negative feedback works to achieve gain stability. Suppose the voltage gain increases due to heating (causing r'_e to be smaller). The increased open-loop gain causes the output voltage to increase and, in turn, increases the negative feedback voltage. This reduces the difference voltage at Q_1 . Thus, the original change in gain is almost completely canceled by the self-correcting action of negative feedback.

Now assume a technician replaces one of the transistors with one with a lower β than in the original circuit. This causes a decrease in the open-loop gain of the amplifier. Now there will be a smaller feedback voltage that causes the difference voltage to be larger. Since there is a larger difference voltage, the original effect of a lower β has little net effect on the output voltage and, again, gain stability is achieved.

The net voltage gain of the amplifier is approximately equal to the reciprocal of the feedback fraction. For the amplifier in Figure 5–20, the net gain is

$$A_v = \left(\frac{R_{E1} + R_{F2}}{R_{E1}} \right) = \left(\frac{100 \Omega + 4.7 \text{ k}\Omega}{100 \Omega} \right) = 48$$

As you can see, it is easy to change the gain by simply changing the value of R_{F2} . In fact, a gain control can be easily added by using a variable resistor in place of R_{F2} .

Another dc coupled amplifier is the circuit introduced in Chapter 4 as System Example 4-2. It is shown again in Figure 5–21 for reference. An important advantage of this circuit is the ability to amplify low frequencies all the way down to dc. The potentiometer

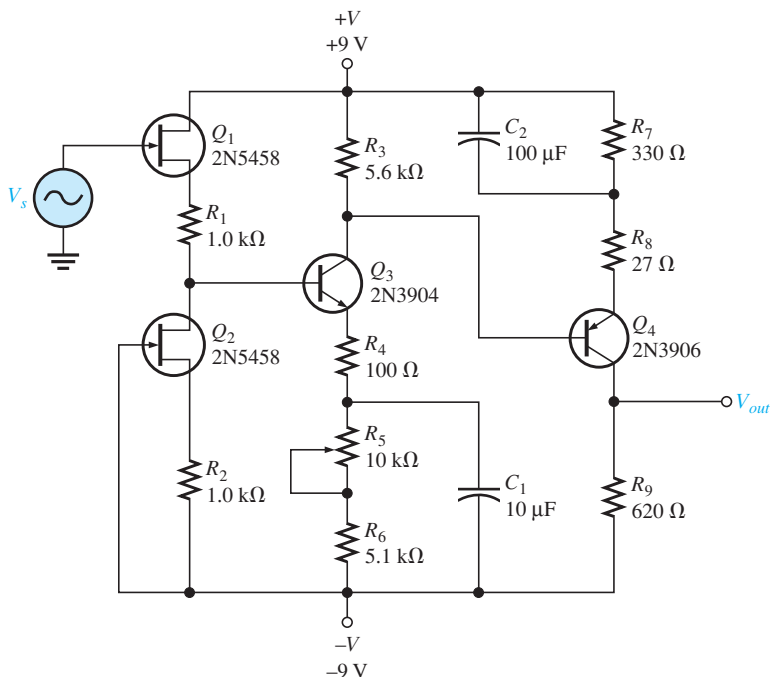


FIGURE 5–21 The direct-coupled preamp from System Example 4-2.

(R_5) is adjusted so that the output voltage is zero when the input voltage is zero. For this particular design, zero output is obtained by using a *pnp* transistor for the last stage.

The amplifier in Figure 5-21 uses unbypassed emitter resistors (R_4 and R_8) to achieve gain stability. This is a form of negative feedback that produces gain stability (at the price of reduced gain) that you saw earlier in Chapters 3 and 4. The FET input stage gave the added advantage of extremely high input resistance.

SECTION 5-4 CHECKUP

1. What are the main advantages of a direct-coupled amplifier?
2. How does negative feedback produce bias or gain stability?
3. Why does the addition of a bypass capacitor in the emitter circuit of a CE amplifier improve the gain stability but not the bias stability?
4. How is gain determined for the circuit in Figure 5-20?

5-5 CLASS A POWER AMPLIFIERS

When an amplifier is biased such that it always operates in the linear region where the output signal is an amplified replica of the input signal, it is a class A amplifier. The discussion and formulas in the previous sections apply to class A operation. Power amplifiers are those amplifiers that have the objective of delivering power to a load. This means that components must be considered in terms of their ability to dissipate heat.


After completing this section, you should be able to

- Compute key ac and dc parameters for class A power amplifiers and discuss operation along the ac load line
- Explain why a centered Q-point is important for a class A power amplifier
- Determine the voltage gain and power gain for a multistage amplifier
- Determine the efficiency of a class A power amplifier

In a small-signal amplifier, the ac signal moves over a small percentage of the total ac load line. When the output signal is larger and approaches the limits of the ac load line, the amplifier is a **large-signal** type. Both large-signal and small-signal amplifiers are considered to be **class A** if they operate in the active region at all times. Class A power amplifiers are large-signal amplifiers with the objective of providing power (rather than voltage) to a load. As a rule of thumb, an amplifier may be considered to be a power amplifier if it is necessary to consider the problem of heat dissipation in components ($>1/4$ W).

Heat Dissipation

Power transistors (and other power devices) must dissipate excessive internally generated heat. For bipolar power transistors, the collector terminal is the critical junction; for this reason, the transistor's case is always connected to the collector terminal. The case of all power transistors is designed to provide a large contact area between it and an external heat sink. Heat from the transistor flows through the case to the heat sink and then dissipates in the surrounding air. Heat sinks vary in size, number of fins, and type of material. Their size depends on the heat dissipation requirement and the maximum ambient temperature in which the transistor is to operate. In high-power applications (a few hundred watts), a cooling fan may be necessary.

 

Many systems require that power amplifiers or other circuits that add unwanted heat as a by-product. This is especially true of inefficient Class-A amplifier systems, which limits their usefulness to low-power applications.

The power handling ability of a device is determined by a number of factors. One important factor is the ambient temperature in which the device will be used. Most spec sheets specify an ambient temperature above which a device must be derated. *Derating* is usually specified in milliwatts per degree C ($\text{mW}/^\circ\text{C}$). For example, assume a given power transistor is rated at 15 W when the ambient temperature is 25°C . The spec sheet states that for every degree above that temperature the device must be derated 120 $\text{mW}/^\circ\text{C}$. This means that if the ambient temperature is 80°C , then the device can only dissipate $15\text{ W} - (120\text{ mW} \times 55^\circ\text{C}) = 8.4\text{ W}$.

SYSTEM NOTE

Centered Q-Point

Recall (from Section 3–4) that the dc and ac load lines cross at the Q-point. When the Q-point is at the center of the ac load line, a maximum class A signal can be obtained. You can see this concept by examining the graph of the load line for a given amplifier in Figure 5–22(a). This graph shows the ac load line with the Q-point at its center. The collector current can vary from its Q-point value, I_{CQ} , up to its saturation value, $I_{c(sat)}$, and down to its cutoff value of zero. Likewise, the collector-to-emitter voltage can swing from its Q-point value, V_{CEQ} , up to its cutoff value, $V_{ce(cutoff)}$, and down to its saturation value of near zero. This operation is indicated in Figure 5–22(b). The peak value of the collector current equals I_{CQ} , and the peak value of the collector-to-emitter voltage equals V_{CEQ} in this case. This signal is the maximum that can be obtained from the class A amplifier. Actually, the output cannot quite reach saturation or cutoff, so the practical maximum is slightly less.

 


FIGURE 5–22 Maximum class A output occurs when the Q-point is centered on the ac load line.

If the Q-point is not centered on the ac load line, the output signal is limited. Figure 5–23 shows a load line with the Q-point moved away from center toward cutoff. The output variation is limited by cutoff in this case. The collector current can only swing down to near zero and an equal amount above I_{CQ} . The collector-to-emitter voltage can only swing up to its cutoff value and an equal amount below V_{CEQ} . This situation is illustrated in Figure 5–23(a). If the amplifier is driven any further than this, it will “clip” at cutoff, as shown in Figure 5–23(b).

Figure 5–24 shows a load line with the Q-point moved away from center toward saturation. In this case, the output variation is limited by saturation. The collector current can only swing up to near saturation and an equal amount below I_{CQ} . The collector-to-emitter voltage can only swing down to its saturation value and an equal amount above V_{CEQ} . This situation is illustrated in Figure 5–24(a). If the amplifier is driven any further, it will “clip” at saturation, as shown in Figure 5–24(b).

 


FIGURE 5-23 Q-point closer to cutoff.

 


FIGURE 5-24 Q-point closer to saturation.

MULTISIM



Open file F05-24 found on the companion website. This simulation demonstrates both saturation and cutoff clipping due to changes in the Q-point.

Power Gain

A power amplifier delivers power to a load. The **power gain** of an amplifier is the ratio of the power delivered to the load to the input power. In general, power gain is

$$A_p = \frac{P_L}{P_{in}} \tag{5-5}$$

where A_p = power gain

P_L = signal power delivered to the load

P_{in} = signal power delivered to the amplifier

The power gain can be computed by any of several formulas, depending on what is known. Frequently, the easiest way to obtain power gain is from input resistance, load resistance, and voltage gain. To see how this is done, recall that power can be expressed in terms of voltage and resistance as

$$P = \frac{V^2}{R}$$

For ac power, the voltage is expressed as rms. The output power delivered to the load is

$$P_L = \frac{V_L^2}{R_L}$$

The input power delivered to the amplifier is

$$P_{in} = \frac{V_{in}^2}{R_{in}}$$

By substituting into Equation (5-5), the following useful relationship can be found:

$$A_p = \frac{V_L^2}{V_{in}^2} \left(\frac{R_{in}}{R_L} \right)$$

$$A_p = A_v^2 \left(\frac{R_{in}}{R_L} \right) \quad (5-6)$$

Equation (5-6) says that the power gain to an amplifier is the voltage gain squared times the ratio of the input resistance to the output load resistance. It can be applied to any amplifier. For example, assume a common-collector (CC) amplifier has an input resistance of 10 k Ω and a load resistance of 100 Ω . Since a CC amplifier has a voltage gain of approximately 1, the power gain is

$$A_p = A_v^2 \left(\frac{R_{in}}{R_L} \right) = 1^2 \left(\frac{10 \text{ k}\Omega}{100 \Omega} \right) = 100$$

For a CC amplifier, A_p is approximately equal to the ratio of the input resistance to the output load resistance.

DC Quiescent Power

The power dissipation of a transistor with no signal input is the product of its Q-point current and voltage.

$$P_{DQ} = I_{CQ} V_{CEQ} \quad (5-7)$$

The only way a class A power amplifier can supply power to a load is to maintain a quiescent current that is at least as large as the peak current requirement for the load current. A signal will not increase the power dissipated by the transistor but actually causes less total power to be dissipated. The quiescent power, given in Equation (5-3), is the maximum power that a class A amplifier must handle. The transistor's power rating will normally exceed this value.

Output Power

In general, the output signal power is the product of the rms load current and the rms load voltage. The maximum unclipped ac signal occurs when the Q-point is centered on the ac load line. For a CE amplifier with a centered Q-point, the maximum peak voltage swing is

$$V_{c(max)} = I_{CQ} R_c$$

The rms value is $0.707V_{c(max)}$.

The maximum peak current swing is

$$I_{c(max)} = \frac{V_{CEQ}}{R_c}$$

The rms value is $0.707I_{c(max)}$.

To find the maximum power output of the signal, you use the rms values of maximum current and voltage. The maximum power out from a class A amplifier is

$$P_{out(max)} = (0.707I_c)(0.707V_c)$$

$$P_{out(max)} = 0.5I_{CQ}V_{CEQ} \quad (5-8)$$

EXAMPLE 5-6

Determine the ac model for the class A power amplifier in Figure 5-25. Use the ac model of a two-stage amplifier to compute the voltage gain and power gain.

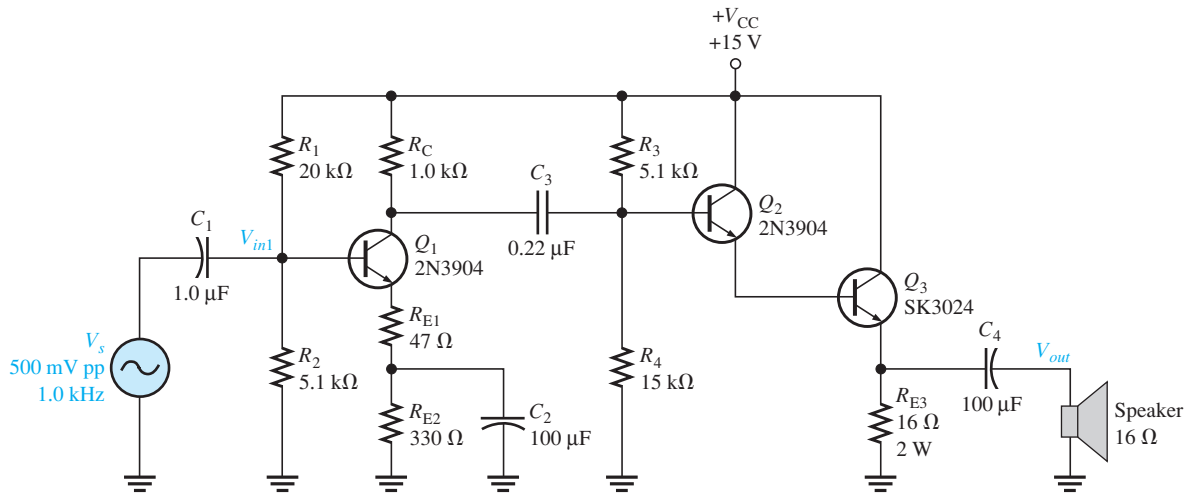


FIGURE 5-25

SOLUTION

Begin by finding the basic parameters for each amplifier stage: $A_{v(NL)}$, R_{in} , and R_{out} . (Q_2 and Q_3 will be treated as a single transistor, named $Q_{2,3}$, in the second stage.)

Stage 1 parameters (Q_1):

The unloaded voltage gain of the first stage is the collector resistance, R_C , divided by the ac emitter resistance, which is the sum of R_{E1} and $r'_e(Q_1)$. To estimate $r'_e(Q_1)$, you first need to find I_E . The base voltage is approximately 2.7 V due to the loading effects on the input voltage divider. The emitter voltage is approximately one diode drop less, or 2.0 V. By Ohm's law, the emitter current is

$$I_{E(Q1)} = \frac{V_{E(Q1)}}{R_{E1} + R_{E2}} = \frac{2.0 \text{ V}}{47 \Omega + 330 \Omega} = 5.3 \text{ mA}$$

and $r'_e(Q_1)$ is approximately $25 \text{ mV}/5.3 \text{ mA} = 5 \Omega$. The unloaded voltage gain is

$$A_{v1(NL)} = \frac{R_C}{R_e} = \frac{R_C}{R_{E1} + r'_e(Q_1)} = \frac{1000 \Omega}{47 \Omega + 5 \Omega} = -19.2$$

The input resistance of the first stage is composed of three parallel paths (as discussed in Section 3-4). These include the two bias resistors and the ac resistance of the emitter circuit multiplied by β_{ac} of Q_1 . The path through Q_1 has a small effect on R_{in} and is also dependent on β_{ac} . A reasonable estimate is to assume a β_{ac} for Q_1 of 200.

$$\begin{aligned} R_{in(tot)1} &= [(R_{E1} + r'_e(Q_1))\beta_{ac(Q1)}] \parallel R_1 \parallel R_2 \\ &= [(47 \Omega + 5 \Omega)200] \parallel 20 \text{ k}\Omega \parallel 5.1 \text{ k}\Omega = 2.9 \text{ k}\Omega \end{aligned}$$

The output resistance of the first stage is just the collector resistor, R_C , which is 1.0 k Ω .

Stage 2 parameters ($Q_{2,3}$):

$Q_{2,3}$ is a darlington pair that is configured as a CC amplifier. The voltage gain of the second stage is approximately 1 for a CC amplifier. Therefore,

$$A_{v2} = 1.0$$

Find the input resistance of the second stage by the same method as that used for the first stage. There are three parallel paths to ac ground. Looking into the base of Q_2 from the coupling capacitor (C_3), the three paths are one path through R_3 , a separate path through R_4 , and a path through $Q_{2,3}$.

Only the bias resistors are important in this calculation because the path through the darlington transistors has a much higher resistance. You can obtain a reasonable estimate of the input resistance of the second stage by ignoring the path through the transistors and computing only the parallel combination of R_3 and R_4 .

$$R_{in(tot)2} \cong R_4 \parallel R_3 = 15 \text{ k}\Omega \parallel 5.1 \text{ k}\Omega = 3.8 \text{ k}\Omega$$

A more precise calculation includes the path through $Q_{2,3}$.

$$R_{in(tot)2} \cong [(R_L \parallel R_{E3})\beta_{ac(Q3)}\beta_{ac(Q2)}] \parallel R_4 \parallel R_3$$

Generally, the β_{ac} of a power transistor is smaller than for signal transistors. A nominal value of 50 for the power transistor (Q_3) and 200 for the signal transistor (Q_2) is reasonable. Therefore, substituting values, the input resistance of the second stage is

$$R_{in(tot)2} = [(16 \Omega \parallel 16 \Omega)50 \times 200] \parallel 15 \text{ k}\Omega \parallel 5.1 \text{ k}\Omega = 3.6 \text{ k}\Omega$$

Notice that the more precise calculation changes the answer by only 6%.

The output resistance of the second stage is very small (less than 1Ω) and can be ignored.

$$R_{out2} \cong 0 \Omega$$

Overall result:

Using the computed parameters, the ac model of the amplifier is shown in Figure 5–26.

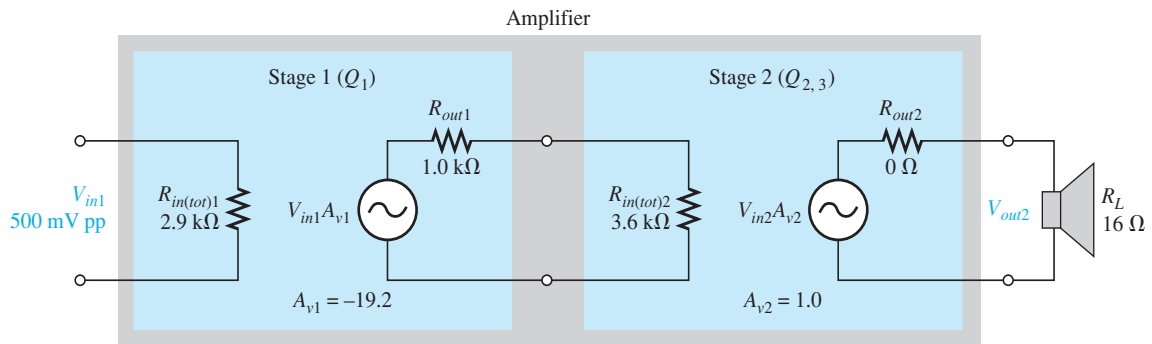


FIGURE 5–26 Amplifier model. (V_{in} is shown as V_{in1} for the first stage).

The overall voltage gain is computed by the method introduced in Section 1–4. The last voltage divider consisting of the speaker and output resistance is not included in the calculation because the output resistance is negligible.

$$A_{v(tot)} = A_{v1} \left(\frac{R_{in(tot)2}}{R_{out1} + R_{in(tot)2}} \right) A_{v2} = -19.2 \left(\frac{3.6 \text{ k}\Omega}{1.0 \text{ k}\Omega + 3.6 \text{ k}\Omega} \right) 1.0 = -15$$

The power gain can be computed using Equation (5–6).

$$A_p = A_{v(tot)}^2 \left(\frac{R_{in(tot)1}}{R_L} \right) = (-15)^2 \left(\frac{2.9 \text{ k}\Omega}{16 \Omega} \right) = 41,000$$

PRACTICE EXERCISE

Express the power gain as a decibel power gain. (Review Section 1–4 if necessary.)

Efficiency

The **efficiency** of any amplifier is the ratio of the signal power supplied to the load to the power from the dc supply. The maximum signal power that can be obtained is given by Equation (5–8). The average power supply current, I_{CC} , is equal to I_{CQ} and the supply voltage is at least $2V_{CEQ}$. Therefore, the dc power is

$$P_{DC} = I_{CC}V_{CC} = 2I_{CQ}V_{CEQ}$$

The maximum efficiency of a capacitively coupled load is

$$eff_{max} = \frac{P_{out}}{P_{DC}} = \frac{0.5I_{CQ}V_{CEQ}}{2I_{CQ}V_{CEQ}} = 0.25$$

The maximum efficiency of a capacitively coupled class A amplifier cannot be higher than 0.25, or 25%, and, in practice, is usually considerably less (about 10%). Although the efficiency can be made higher by transformer coupling the signal to the load, there are drawbacks to transformer coupling. These drawbacks include the size and cost of transformers as well as potential distortion problems when the transformer core begins to saturate. In general, the low efficiency of class A power amplifiers limits their usefulness to small power applications that require only a few watts of load power.

EXAMPLE 5-7

Determine the efficiency of the power amplifier in Figure 5-25.

SOLUTION

The efficiency is the ratio of the signal power in the load to the power supplied by the dc source. The input voltage is 500 mV peak-to-peak, which is 176 mV rms. The input power is, therefore,

$$P_{in} = \frac{V_{in}^2}{R_{in}} = \frac{(176 \text{ mV})^2}{2.9 \text{ k}\Omega} = 10.7 \mu\text{W}$$

The output power is

$$P_{out} = P_{in}A_p = (10.7 \mu\text{W})(41,000) = 0.44 \text{ W}$$

Most of the power from the dc source is supplied to the output stage. The current in the output stage can be computed from the emitter voltage of Q_3 , which is approximately 9.5 V, producing a current of 0.60 A. Neglecting the other transistors and bias circuits, the total dc supply current is about 0.6 A. The power from the dc source is

$$P_{DC} = I_{CC}V_{CC} = (0.6 \text{ A})(15 \text{ V}) = 9 \text{ W}$$

Therefore, the efficiency of the amplifier for this input is

$$eff = \frac{P_{out}}{P_{DC}} = \frac{0.44 \text{ W}}{9 \text{ W}} \cong 0.05$$

This represents an efficiency of 5%.

PRACTICE EXERCISE

Explain what happens to the efficiency if R_{E3} were replaced with the speaker. What disadvantage does this have?

SECTION 5-5 CHECKUP

1. What is the purpose of a heat sink?
2. Which lead of a bipolar transistor is connected to the case?
3. What are the two types of clipping with a class A amplifier?
4. What is the maximum theoretical efficiency for a class A amplifier?
5. How can the power gain of a CC amplifier be expressed in terms of a ratio of resistances?

5–6 CLASS B POWER AMPLIFIERS

When an amplifier is biased such that it operates in the linear region for 180° of the input cycle and is in cutoff for 180° , it is a class B amplifier. The primary advantage of a class B amplifier over a class A amplifier is that the class B is much more efficient; you can get more output power for a given amount of input power. Class B amplifiers are generally configured with at least two active devices that alternately amplify the positive and negative part of the input waveform. This arrangement is called push-pull.

After completing this section, you should be able to

- Compute key ac and dc parameters for class B power amplifiers including bipolar and FET types
- Describe two configurations for push-pull amplifiers
- Describe crossover distortion and how to overcome it
- Explain how class AB operation differs from class B operation
- Describe how to avoid thermal problems with bipolar class AB amplifiers
- Discuss characteristics of MOSFET class B amplifiers

Class B operation refers to operation when the Q-point is located at cutoff, causing the output current to vary only during one-half of the input cycle. In a linear amplifier, two devices are required for a complete cycle; one amplifies the positive cycle and the other amplifies the negative cycle. As you will see, this arrangement has a great advantage for power amplifiers as it greatly increases the efficiency. For this reason, they are widely used as power amplifiers.

The Q-point Is at Cutoff

The class B amplifier is biased at cutoff so that $I_{CQ} = 0$ and $V_{CEQ} = V_{CE(\text{cutoff})}$. Thus, there is *no dc current or power dissipated* when there is no signal as in the case of the class A amplifier. When a signal drives a class B amplifier into conduction, it then operates in its linear region. This is illustrated in Figure 5–27 with an emitter-follower circuit.

 


FIGURE 5–27 Common-collector class B amplifier.

Push-Pull Operation

As you can see, the circuit in Figure 5–27 only conducts for the positive half of the cycle. To amplify the entire cycle, it is necessary to add a second class B amplifier that operates on the negative half. The combination of two class B amplifiers working together is called **push-pull** operation.

There are two common approaches for using push-pull amplifiers to reproduce the entire waveform. The first approach uses transformer coupling. The second uses two **complementary symmetry transistors**; these are a matching pair of *npn/pnp* BJTs or a matching pair of *n-channel/p-channel* FETs.

TRANSFORMER COUPLING Transformer coupling is illustrated in Figure 5-28. The input transformer has a center-tapped secondary that is connected to ground, producing phase inversion of one side with respect to the other. The input transformer thus converts the input signal to two out-of-phase signals for the transistors. Notice that both transistors are *npn* types. Because of the signal inversion, Q_1 will conduct on the positive part of the cycle and Q_2 will conduct on the negative part. The output transformer combines the signals by permitting current in both directions, even though one transistor is always cut off. The positive power supply signal is connected to the center tap of the output transformer.

 


FIGURE 5-28 Transformer coupled push-pull amplifiers. Q_1 conducts during the positive half-cycle; Q_2 conducts during the negative half-cycle. The two halves are combined by the output transformer.

COMPLEMENTARY SYMMETRY TRANSISTORS Figure 5-29 shows one of the most popular types of push-pull class B amplifiers using two emitter-followers and both positive and negative power supplies. This is a complementary amplifier because one emitter-follower uses an *npn* transistor and the other a *pnp*, which conduct on opposite alternations of the input cycle. Notice that there is no dc base bias voltage ($V_B = 0$). Thus, only the signal voltage drives the transistors into conduction. Transistor Q_1 conducts during the positive half of the input cycle, and Q_2 conducts during the negative half.

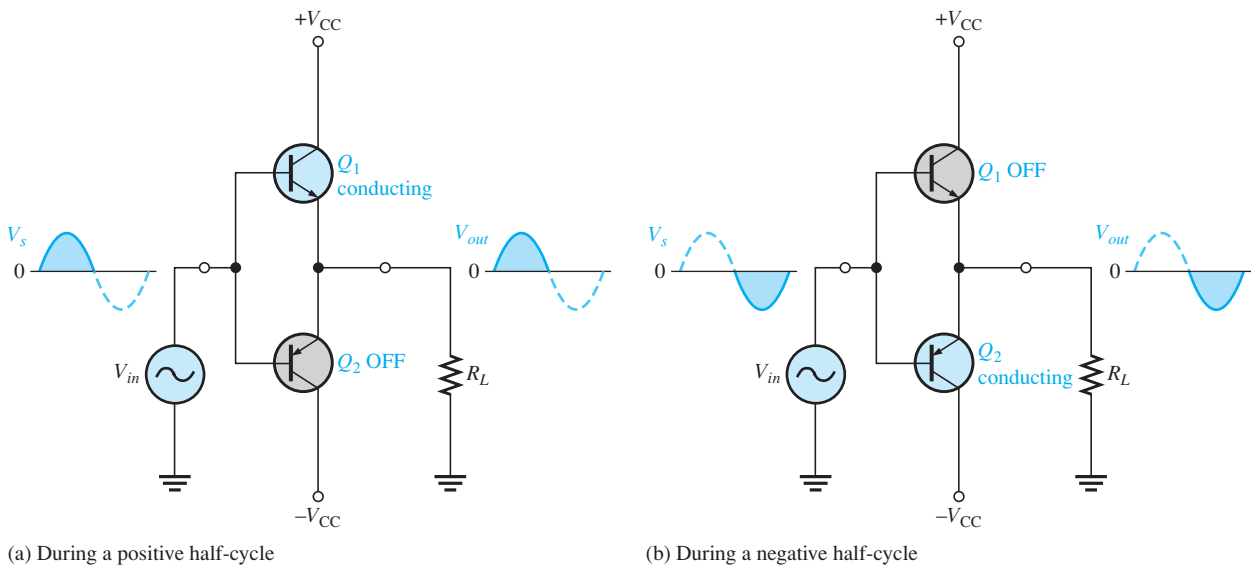


FIGURE 5-29 Class B push-pull operation.

Crossover Distortion

When the dc base voltage is zero, the input signal voltage must exceed V_{BE} before a transistor conducts. As a result, there is a time interval between the positive and negative alternations of the input when neither transistor is conducting, as shown in Figure 5-30. The resulting distortion in the output waveform is called **crossover distortion**.

 


FIGURE 5-30 Crossover distortion in a class B amplifier.

 




FIGURE 5-31 Biasing the push-pull amplifier to eliminate crossover distortion.

Biasing the Push-Pull Amplifier

To overcome crossover distortion, the biasing is adjusted to just overcome the V_{BE} of the transistors; this results in a modified form of operation called **class AB**. In class AB operation, the push-pull stages are biased into slight conduction, even when no input signal is present. This can be done with a voltage divider and diode arrangement, as shown in Figure 5-31. When the diode characteristics of D_1 and D_2 are closely matched to the characteristics of the transistor base-emitter junctions, the current in the diodes and the current in the transistors is the same; this is called a **current mirror**. This current mirror produces the desired class AB operation and eliminates crossover distortion.

In systems such as audio systems where low distortion is necessary, class AB power amplifiers are used. Frequently, an integrated circuit is present with multiple transistors that can be used for the current mirror. For it to function properly the transistors should have characteristics that are as closely matched as possible. Transistor array ICs are available from a number of manufacturers that offer matched pairs of *nnp* and *pnp* transistors. The arrays may have one, two, or four matched pairs in the array. As noted earlier, the transistors in an array are more closely matched than discrete devices. A two pair array is shown in Figure SN5-1.

FIGURE SN5-2 A two pair transistor array.

  

SYSTEM NOTE

In the bias path, R_1 and R_2 are of equal value, as are the positive and negative supply voltages. This forces the voltage at point A to equal 0 V and eliminates the need for an

input coupling capacitor. The dc voltage on the output is also 0 V. Assuming that both diodes and both transistors are identical, the drop across D_1 equals the V_{BE} of Q_1 , and the drop across D_2 equals the V_{BE} of Q_2 . Since they are matched, the diode current will be the same as I_{CQ} . The diode current and I_{CQ} can be found by applying Ohm's law to either R_1 or R_2 as follows:

$$I_{CQ} = \frac{V_{CC} - 0.7 \text{ V}}{R_1}$$

This small current required of class AB operation eliminates the crossover distortion but has the potential for thermal instability if the transistor's V_{BE} drops are not matched to the diode drops or if the diodes are not in thermal equilibrium with the transistors. Heat in the power transistors decreases the base-emitter voltage and tends to increase current. If the diodes are warmed the same amount, the current is stabilized; but if the diodes are in a cooler environment, they cause I_{CQ} to increase even more. More heat is produced in an unrestrained cycle known as *thermal runaway*.² To keep this from happening, the diodes should have the same thermal environment as the transistors. In stringent cases, a small resistor in the emitter of each transistor can alleviate thermal runaway.

Crossover distortion also occurs in transformer-coupled amplifiers such as that shown in Figure 5-28. To eliminate it in this case, a 0.7 V is applied to the input transformer's secondary that just biases both transistors into conduction. The bias voltage to produce this drop can be derived from the power supply using a single diode as shown in Figure 5-32.

 


FIGURE 5-32 Eliminating crossover distortion in a transformer-coupled push-pull amplifier. The diode compensates for the base-emitter drop of the transistors and produces class AB operation.

AC Operation

Consider the ac load line for Q_1 of the class AB amplifier in Figure 5-31. The Q-point is slightly above cutoff. (In a true class B amplifier, the Q-point is at cutoff.) The ac cutoff voltage for a two-supply operation is at V_{CC} with an I_{CQ} as given earlier. The ac saturation current for a two-supply operation with a push-pull amplifier is

$$I_{c(sat)} = \frac{V_{CC}}{R_L} \quad (5-9)$$

The ac load line for the *npn* transistor is as shown in Figure 5-33. The dc load line can be found by drawing a line that passes through V_{CEQ} and the dc saturation current, $I_{C(sat)}$. The the saturation current for dc is the current if the collector to emitter is shorted on both transistors! This assumed short across the power supplies obviously would cause maximum current from the supplies and implies the dc load line passes almost vertically through the cutoff as shown. Operation along the dc load line, such as caused by thermal runaway, could produce such a high current that the transistors are destroyed.

²The base-emitter voltage in a BJT drops about 2 mV/°C.

FIGURE 5–33 Load lines for a complementary symmetry push-pull amplifier. Only the load lines for the *n*pn transistor are shown.

 


Figure 5–34(a) illustrates the ac load line for Q_1 of the class B amplifier in Figure 5–34(b). In the case illustrated, a signal is applied that swings over the region of the ac load line shown in bold. At the upper end of the ac load line, the voltage across the transistor (V_{ce}) is a minimum, and the output voltage is maximum.

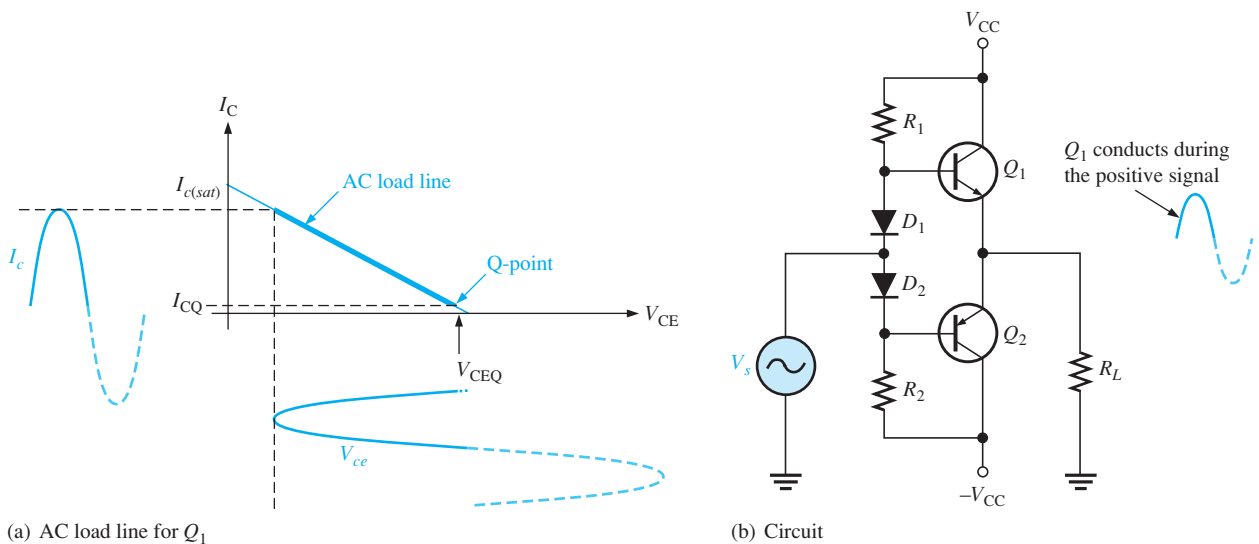


FIGURE 5–34

Under maximum conditions, transistors Q_1 and Q_2 are alternately driven from near cutoff to near saturation. During the positive alternation of the input signal, the Q_1 emitter is driven from its Q-point value of 0 to nearly V_{CC} , producing a positive peak voltage a little less than V_{CC} . Likewise, during the negative alternation of the input signal, the Q_2 emitter is driven from its Q-point value of 0 V, to near $-V_{CC}$, producing a negative peak voltage almost equal to $-V_{CC}$. Although it is possible to operate close to the saturation current, this type of operation results in increased distortion of the signal.

The ac saturation current given in Equation (5–9) is also the peak output current. Each transistor can essentially operate over its entire load line. Recall that in class A operation, the transistor can also operate over the entire load line but with a significant difference. In class A operation, the Q-point is near the middle and there is significant current in the transistors even with no signal. In class B operation, when there is no signal, the transistors have only a very small current and therefore dissipate very little power. Thus, the efficiency of a class B amplifier can be much higher than a class A amplifier. It can be shown that the maximum theoretical efficiency of a class B amplifier is 79%.

Single-Supply Operation

Push-pull amplifiers using complementary symmetry transistors can be operated from a single voltage source as shown in Figure 5–35. The circuit operation is the same as that described previously, except the bias is set to force the output emitter voltage to be $V_{CC}/2$ instead of zero volts used with two supplies. Because the output is not biased at zero volts,

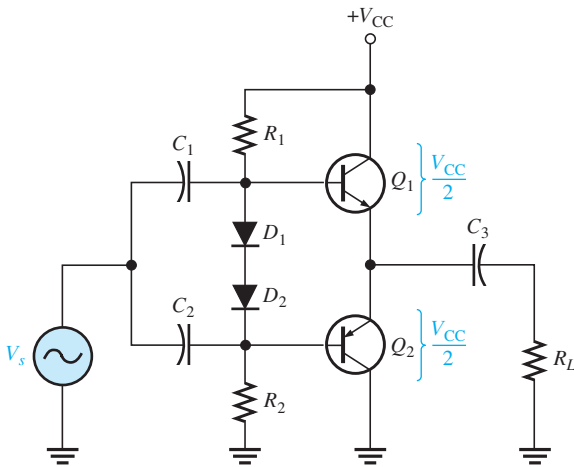


FIGURE 5-35 Single-ended push-pull amplifier.

capacitive coupling for the input and output is necessary to block the bias voltage from the source and the load resistor. Ideally, the output voltage can swing from zero to V_{CC} , but in practice it does not quite reach these ideal values.

EXAMPLE 5-8

Determine the ideal maximum peak output voltage and current for the circuit shown in Figure 5-36.

 


FIGURE 5-36

SOLUTION

The ideal maximum peak output voltage is

$$V_{p(out)} \cong V_{CEQ} \cong \frac{V_{CC}}{2} = \frac{20 \text{ V}}{2} = 10 \text{ V}$$

The ideal maximum peak current is

$$I_{p(out)} \cong I_{c(sat)} \cong \frac{V_{CEQ}}{R_L} = \frac{10 \text{ V}}{16 \Omega} = 0.63 \text{ A}$$

The actual maximum values of voltage and current are slightly smaller.

PRACTICE EXERCISE

Compute the maximum peak output voltage and current if the supply voltage is raised to +30 V.

MULTISIM



Open file F05-36 found on the companion website. This simulation compares class B and AB amplifiers.

MOSFET Push-Pull Amplifiers

When MOSFETs were first introduced to the commercial market, they were unable to handle the large currents required of power devices. In recent years, the advances in MOSFET technology have made high-power MOSFETs available and offer some important advantages in the design of power amplifiers for both digital and analog circuits. MOSFETs are very reliable, providing their specified voltage, current, and temperature ratings are not exceeded.

Comparing MOSFETs to BJTs, there are several important advantages but also some disadvantages to MOSFETs. The principal advantages of MOSFETs over BJTs is that their biasing networks are simpler, their drive requirements are simpler, and they can be connected in parallel for added drive capability. In addition, MOSFETs are not generally prone to thermal instability; as they get hotter, they tend to have less current (just the opposite of bipolar transistors).³ In switching applications (discussed in Section 4–7), they can switch faster than BJTs. MOSFET switches are widely used in both digital logic and in high-power switching circuits.

The BJT has the edge when the voltage drop across the transistor is important and, as a result, may be more efficient than a MOSFET in certain cases. In addition, bipolar transistors are not as prone to **electrostatic discharge (ESD)** that can kill a MOSFET. Most MOSFETs are shipped with the pins shorted together with a ring; they should be soldered into a circuit before the shorting ring is removed.

A simplified class B amplifier using complementary symmetry E-MOSFETs and two-supply operation is shown in Figure 5–37(a). Recall that an E-MOSFET is normally off but can be turned on when the input exceeds the threshold voltage. For logic devices, the on voltage is typically between 1 V and 2 V; for standard devices the threshold is higher. When the signal exceeds the positive threshold voltage of Q_1 , it conducts; likewise, when the signal is below the negative threshold voltage of Q_2 , it conducts. Thus, the n -channel device conducts on the positive cycle; the p -channel device conducts on the negative cycle.

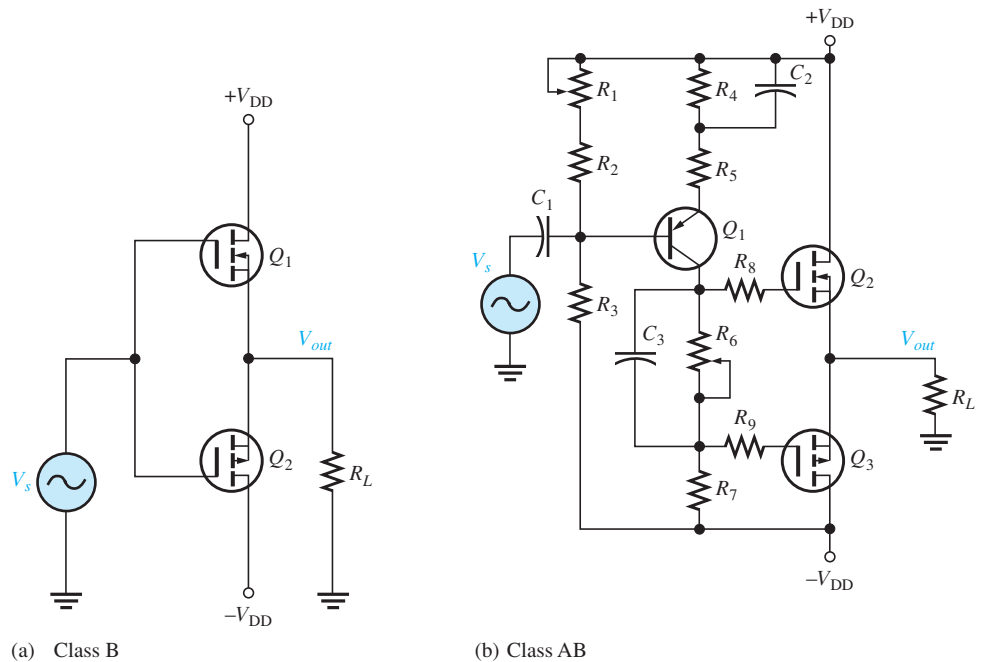


FIGURE 5–37 MOSFET push-pull amplifiers.

³An exception to this rule is with high voltages and low currents; the temperature characteristics are reversed, and MOSFETs *can* experience thermal runaway problems.

As in the case of the BJT push-pull amplifier, the transistor does not conduct just above zero signal voltage, which causes crossover distortion. If each transistor is biased just at the threshold voltage, the MOSFETs will operate in class AB, as shown in the circuit in Figure 5-37(b). This amplifier includes a bipolar transistor amplifier as a driver and other components to assure a reasonably linear output from an E-MOSFET push-pull stage. Of course, there are other features to this basic design in commercial amplifiers.

The basic class AB push-pull amplifier shown in Figure 5-37(b) includes a common-emitter stage that amplifies the input signal and couples the signal to the gates of the push-pull stage, consisting of Q_2 and Q_3 . Notice that R_6 is bypassed with capacitor C_3 to allow identical ac signals to be applied to the push-pull stage. Potentiometer R_6 is used to develop the proper dc voltage to set the bias to the threshold voltages of Q_2 and Q_3 . It is adjusted to minimize cross over distortion. Potentiometer R_1 is adjusted to zero the output dc output voltage with no input signal.

This type of amplifier can give increased power out by simply adding another pair of MOSFETs in parallel; however, this can sometimes cause unwanted oscillations. To prevent this, gate resistors can be used to isolate the MOSFETs from each other. Although not strictly required in this simplified amplifier, they are shown as R_8 and R_9 . Power amplifiers with parallel E-MOSFET transistors can deliver over 100 W of power.

EXAMPLE 5-9

The n -channel E-MOSFET shown in Figure 5-38 has a threshold voltage of $+2.0$ V and the p -channel E-MOSFET has a threshold voltage of -2.0 V. What resistance setting for R_6 will bias the transistors to class AB operation? At this setting, what power is delivered to the load if the input signal is 100 mV? Assume that potentiometer R_1 is set to 440 Ω .

 


FIGURE 5-38

SOLUTION

Start by computing the dc parameter for the CE amplifier. The base voltage is determined by the voltage divider composed of R_1 , R_2 , and R_3 . The standard

voltage-divider equation is modified to account for the fact that the divider is not referenced to ground.

$$\begin{aligned} V_B &= V_{R3} - V_{DD} = \left(V_{DD} - (-V_{DD}) \right) \left(\frac{R_3}{R_1 + R_2 + R_3} \right) - V_{DD} \\ &= \left(24 \text{ V} - (-24 \text{ V}) \right) \left(\frac{100 \text{ k}\Omega}{440 \Omega + 5.1 \text{ k}\Omega + 100 \text{ k}\Omega} \right) - 24 \text{ V} = 21.5 \text{ V} \end{aligned}$$

The emitter voltage is one diode drop higher than the base voltage (because the transistor is a *pn*p type).

$$V_E = V_B + 0.7 \text{ V} = 21.5 \text{ V} + 0.7 \text{ V} = 22.2 \text{ V}$$

Calculate the emitter current from Ohm's law.

$$I_E = \frac{V_{DD} - V_E}{R_4 + R_5} = \frac{24 \text{ V} - 22.2 \text{ V}}{1.1 \text{ k}\Omega} = 1.64 \text{ mA}$$

The required drop across R_6 is the difference in the threshold voltages.

$$V_{R6} = V_{TH(Q1)} - V_{TH(Q2)} = 2.0 \text{ V} - (-2.0 \text{ V}) = 4.0 \text{ V}$$

Use Ohm's law to determine the required setting for R_6 .

$$R_6 = \frac{V_{R6}}{I_{R6}} = \frac{4.0 \text{ V}}{1.64 \text{ mA}} = \mathbf{2.4 \text{ k}\Omega}$$

This setting produces class AB operation, so the output voltage replicates the input of the MOSFET (less a small drop across the internal MOSFET resistance). Determine the gain of the CE amplifier using the ratio of unbypassed collector resistance (R_7) to the unbypassed emitter resistance (R_5) and r'_e .

$$r'_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.64 \text{ mA}} = 15.2 \Omega$$

and

$$A_v = \frac{R_7}{R_5 + r'_e} = \frac{15 \text{ k}\Omega}{100 \Omega + 15.2 \Omega} = 130$$

Assuming no internal drop in the MOSFETs, the output voltage is

$$V_{out} = A_v V_{in} = (130)(100 \text{ mV}) = 13 \text{ V}$$

The power out is

$$P_L = \frac{V_{out}^2}{R_L} = \frac{13 \text{ V}^2}{33 \Omega} = \mathbf{5.1 \text{ W}}$$

PRACTICE EXERCISE


Compute the setting of R_6 if the threshold voltages for the MOSFETs are +1.5 V and -1.5 V.



BD135/137/139

Medium Power Linear and Switching Applications

 - Complement to BD136, BD138 and BD140 respectively



NPN Epitaxial Silicon Transistor

Absolute Maximum Ratings $T_C = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CBO}	Collector-Base Voltage : BD135	45	V
	: BD137	60	V
	: BD139	80	V
V_{CEO}	Collector-Emitter Voltage : BD135	45	V
	: BD137	60	V
	: BD139	80	V
V_{EBO}	Emitter-Base Voltage	5	V
I_C	Collector Current (DC)	1.5	A
I_{CP}	Collector Current (Pulse)	3.0	A
I_B	Base Current	0.5	A
P_C	Collector Dissipation ($T_C = 25^\circ\text{C}$)	12.5	W
P_C	Collector Dissipation ($T_a = 25^\circ\text{C}$)	1.25	W
T_J	Junction Temperature	150	$^\circ\text{C}$
T_{STG}	Storage Temperature	-55 ~ 150	$^\circ\text{C}$

Electrical Characteristics $T_C = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Typ.	Max.	Units	
$V_{CEO(sus)}$	Collector-Emitter Sustaining Voltage : BD135	$I_C = 30\text{mA}, I_B = 0$	45			V	
	: BD137		60			V	
	: BD139		80			V	
I_{CBO}	Collector Cut-off Current	$V_{CB} = 30\text{V}, I_E = 0$			0.1	μA	
I_{EBO}	Emitter Cut-off Current	$V_{EB} = 5\text{V}, I_C = 0$			10	μA	
h_{FE1}	DC Current Gain : ALL DEVICE	$V_{CE} = 2\text{V}, I_C = 5\text{mA}$	25				
h_{FE2}		$V_{CE} = 2\text{V}, I_C = 0.5\text{A}$	25				
h_{FE3}		: BD135	$V_{CE} = 2\text{V}, I_C = 150\text{mA}$	40		250	
		: BD137, BD139		40		160	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 500\text{mA}, I_B = 50\text{mA}$			0.5	V	
$V_{BE(on)}$	Base-Emitter ON Voltage	$V_{CE} = 2\text{V}, I_C = 0.5\text{A}$			1	V	

h_{FE} Classification


Classification	6	10	16
h_{FE3}	40 ~ 100	63 ~ 160	100 ~ 250

FIGURE 5-39 Partial data sheet for the BD135 power transistors. Copyright Fairchild Semiconductor Corporation. Used by permission.

SYSTEM EXAMPLE 5-2

A PA SYSTEM POWER AMPLIFIER

In this system example we will look at a power amplifier that can be used in a public address (PA) system in conjunction with the low-noise JFET preamp from System Example 4-2. A block diagram of the PA system is shown in Figure SE5-3. The power amplifier will deliver up to 6 W to an 8 Ω speaker and have a frequency bandwidth of 70 Hz to 5 kHz.

 

 


FIGURE SE5-3

MULTISIM



Open file SE05-03 found on the companion website. This simulation connects the JFET preamp from System Example 4-2 to the power amplifier in this example.

The Power Amplifier Circuit

The schematic of the power amplifier is shown in Figure SE5-4. The output stage is a darlington class AB amplifier with diode current-mirror bias. There are two darlington configurations used, a traditional darlington pair (Q_1 and Q_2) and a complementary darlington pair (Q_3 and Q_4). This complementary configuration is also known as a *Sziklai pair*. A standard push-pull amplifier uses one *npn* and one *pnp* transistor. By making one of the Darlington's a Sziklai pair, both output transistors are *npns*. This makes for better thermal matching and improved sound quality. Also note that only one diode is used to bias the Sziklai pair. This is because there is only one barrier potential (Q_4) to overcome.

 


FIGURE SE5-4 Class AB push-pull power amplifier schematic.

The input from the preamp is coupled to the driver stage, Q_5 . This stage provides additional gain and also prevents excessive loading on the preamp. The resistor R_1 serves two functions. It provides biasing for Q_5 from the dc output voltage (0 V). It also provides negative feedback for gain stability as discussed in Section 5-4. Since the output from Q_5 is inverted and the darlington output stage is non-inverting, this means that the output signal will be 180° out of phase with the input from the preamp at the base of Q_5 . This provides the negative feedback.

SECTION 5-6 CHECKUP

1. What is the advantage to two-supply operation with a class B complementary symmetry amplifier?
2. What is crossover distortion and how is it avoided?
3. What is the maximum theoretical efficiency for a class B amplifier?
4. Where should an E-MOSFET, operating as a class AB amplifier, be biased?
5. Explain why there are only three diodes in the circuit in Figure SE5-2.

5-7 CLASS C AND CLASS D POWER AMPLIFIERS

The last two amplifier classes that we will discuss in this chapter are very different in many ways, but they are both highly efficient amplifier designs. Class C amplifiers are used primarily in RF circuits such as FM transmitters. They are normally built around BJTs or JFETs. Class D amplifiers are non linear switching amplifiers that are built around MOSFETs. At one time class D amplifiers were used primarily for switching applications like motor control, but there are now several high-quality class D audio amplifiers on the market. We will begin with the class C amplifier.

After completing this section, you should be able to

- Explain the operation of class C and class D amplifiers
 - Explain basic class C operation
 - Describe class C biasing
 - Explain tuned operation of a class C amplifier
 - Determine maximum power output for a class C amplifier
 - Discuss the operation of a class D amplifier
 - Explain pulse-width modulation (PWM)
 - Discuss harmonics and frequency spectra in class D amplifiers
 - Explain the purpose of the low-pass filter in a class D amplifier

Basic Class C Operation

The basic concept of class C operation is illustrated in Figure 5-40. A common-emitter class C amplifier with a resistive load is shown in Figure 5-41(a). A **Class C amplifier** is normally operated with a resonant circuit load, so the resistive load is used only for the purpose of illustrating the concept. It is biased below cutoff with the negative V_{BB} supply. The ac source voltage has a peak value that is slightly greater than $|V_{BB}| + V_{BE}$ so that the base voltage exceeds the barrier potential of the base-emitter junction for a short time near the positive peak of each cycle, as illustrated in Figure 5-41(b). During this short interval, the transistor is turned on. When the entire ac load line is used, as shown in Figure 5-41(c), the ideal maximum collector current is $I_{c(sat)}$ and the ideal minimum collector voltage is $V_{ce(sat)}$.

 


FIGURE 5-40 Basic class C amplifier operation (noninverting).

 


FIGURE 5-41 Basic class C operation.

Power Dissipation

The power dissipation of the transistor in a class C amplifier is low because it is on for only a small percentage of the input cycle. Figure 5-42(a) shows the collector current pulses. The time between the pulses is the period (T) of the ac input voltage. The collector current

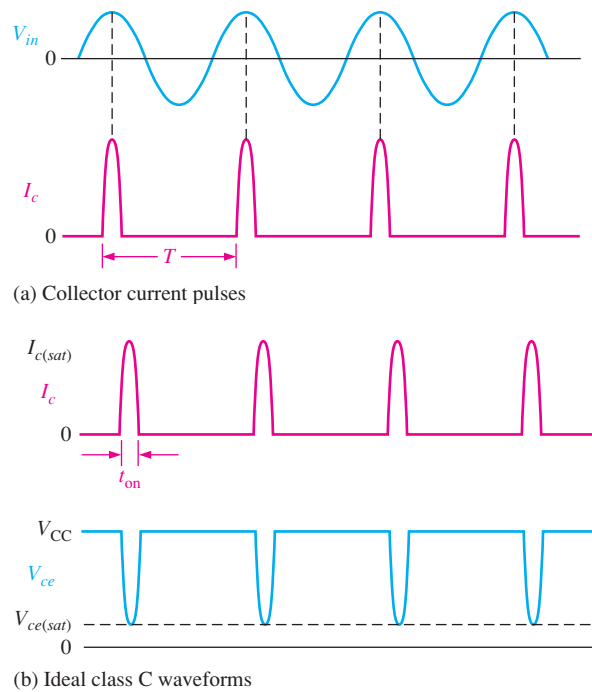


FIGURE 5-42 Class C waveforms.

and the collector voltage during the *on* time of the transistor are shown in Figure 5-42(b). To avoid complex mathematics, we will assume ideal pulse approximations. Using this simplification, if the output swings over the entire load, the maximum current amplitude is $I_{c(sat)}$ and the minimum voltage amplitude is $V_{ce(sat)}$ during the time the transistor is on. The power dissipation during the *on* time is, therefore,

$$P_{D(on)} = I_{c(sat)}V_{ce(sat)}$$

The transistor is on for a short time, t_{on} , and off for the rest of the input cycle. Therefore, assuming the entire load line is used, the power dissipation averaged over the entire cycle is

$$P_{D(avg)} = \left(\frac{t_{on}}{T}\right)P_{D(on)} = \left(\frac{t_{on}}{T}\right)I_{c(sat)}V_{ce(sat)}$$

Tuned Operation

Because the collector voltage (output) is not a replica of the input, the resistively loaded class C amplifier alone is of no value in linear applications. It is therefore necessary to use a class C amplifier with a parallel resonant circuit (tank), as shown in Figure 5-43(a). The resonant frequency of the tank circuit is determined by the formula $f_r = 1/(2\pi r\sqrt{LC})$. The short pulse of collector current on each cycle of the input initiates and sustains the oscillation of the tank circuit so that an output sinusoidal voltage is produced, as illustrated in Figure 5-43(b). The tank circuit has high impedance only near the resonant frequency, so the gain is large only at this frequency.

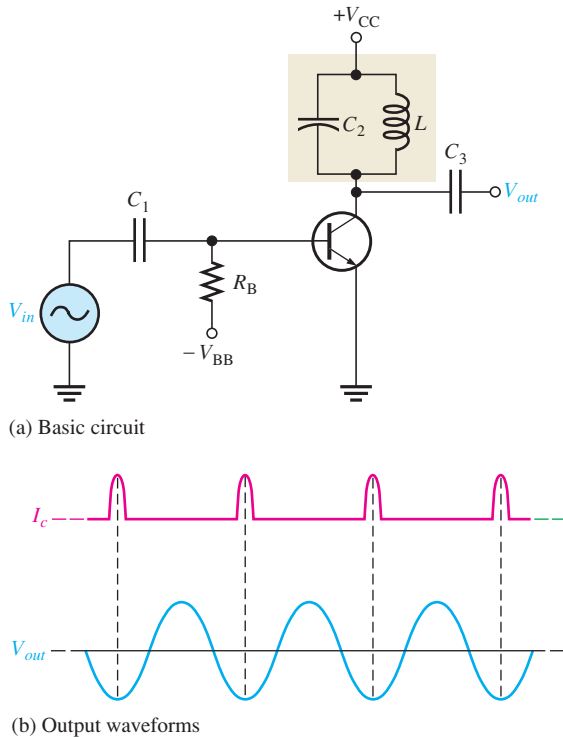


FIGURE 5-43 Tuned class C amplifier.

Initially the capacitor charges to approximately $+V_{CC}$, as shown in Figure 5-44(a). The red arrow shows the flow of charge. After the pulse, the capacitor quickly discharges, thus charging the inductor. Then, after the capacitor completely discharges, the inductor's magnetic field collapses and then quickly recharges C to near V_{CC} but with a polarity opposite to the previous charge. This completes one half-cycle of the oscillation, as shown in parts (b) and (c) of Figure 5-44. Next, the capacitor discharges again, increasing the

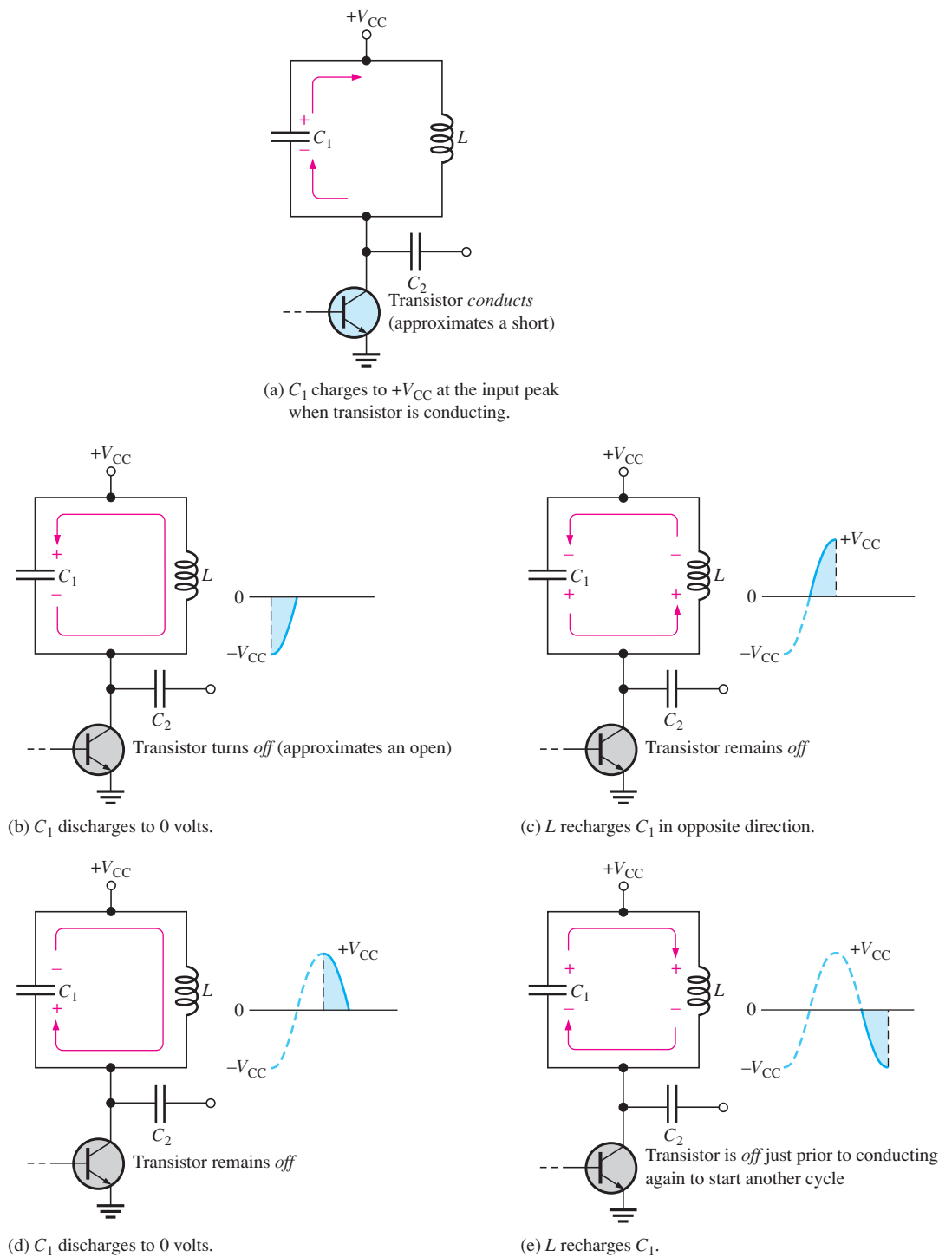


FIGURE 5-44 Resonant circuit action.

inductor's magnetic field. The inductor then quickly recharges the capacitor back to a positive peak slightly less than the previous one, due to energy loss in the winding resistance. This completes one full cycle, as shown in parts (d) and (e) of Figure 5-44. The peak-to-peak output voltage is therefore approximately equal to $2V_{CC}$.

The amplitude of each successive cycle of the oscillation will be less than that of the previous cycle because of energy loss in the resistance of the tank circuit, as shown in Figure 5-45(a), and the oscillation will eventually die out. However, the regular recurrences of the collector current pulse reenergizes the resonant circuit and sustains the oscillations at a constant amplitude.

When the tank circuit is tuned to the frequency of the input signal (fundamental), reenergizing occurs on each cycle of the tank voltage, V_r , as shown in Figure 5-45(b). When the tank circuit is tuned to the second harmonic of the input signal, reenergizing occurs on alternate cycles as shown in Figure 5-45(c). In this case, a class C amplifier operates as a frequency multiplier ($\times 2$). By tuning the resonant tank circuit to higher harmonics, further frequency multiplication factors are achieved.

Maximum Output Power

Since the voltage developed across the tank circuit has a peak-to-peak value of approximately, $2V_{CC}$, the maximum output power can be expressed as

$$P_{out} = \frac{V_{rms}^2}{R_c} = \frac{(0.707V_{CC})^2}{R_c}$$

$$P_{out} = \frac{0.5 V_{CC}^2}{R_c}$$

R_c is the equivalent parallel resistance of the collector tank circuit at resonance and represents the parallel combination of the coil resistance and the load resistance. It usually has a low value. Since the transistor is only on for a small portion of the input cycle, and since there is no bias current, class C amplifiers are very efficient. Practical class C amplifiers can achieve efficiencies of greater than 90%.

Clamper Bias for a Class C Amplifier

Figure 5-46 shows a class C amplifier with a base bias clamping circuit. The base-emitter junction functions as a diode.

When the input signal goes positive, capacitor C_1 is charged to the peak value with the polarity shown in Figure 5-47(a). This action produces an average voltage at the base of approximately $-V_p$. This places the transistor in cutoff except at the positive peaks, when the transistor conducts for a short interval. For good clamping action, the R_1C_1 time constant of the clamping circuit must be much greater than the period of the input signal. Parts (b) through (f) of Figure 5-47 illustrate the bias clamping action in more detail. During the time up to the positive peak of the input (t_0 to t_1), the capacitor charges to $V_p - 0.7$ V through the base-emitter diode, as shown in part (b). During the time from t_1 to t_2 , as shown

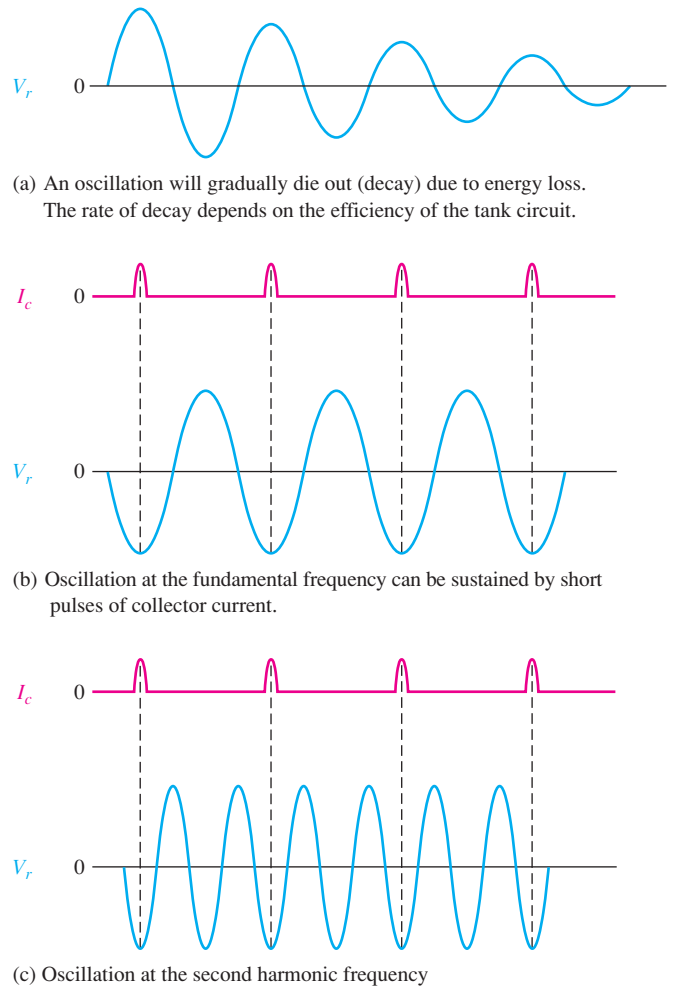


FIGURE 5-45 Tank circuit oscillations. V_r is the voltage across the tank circuit.

 
 


FIGURE 5-46 Tuned class C amplifier with clamper bias.


FIGURE 5-47 Clamper bias action.

in part (c), the capacitor discharges very little because of the large RC time constant. The capacitor, therefore, maintains an average charge slightly less than $V_p - 0.7\text{ V}$.

Since the dc value of the input signal is zero (positive side of C_1), the dc voltage at the base (negative side of C_1) is slightly more positive than $-(V_p - 0.7\text{ V})$, as indicated in Figure 5-47(d). As shown in Figure 5-47(e), the capacitor couples the ac input signal through to the base so that the voltage at the transistor's base is the ac signal riding on a dc level slightly more positive than $-(V_p - 0.7\text{ V})$. Near the positive peaks of the input voltage, the base voltage goes slightly above 0.7 V and causes the transistor to conduct for a short time, as shown in Figure 5-47(f).

EXAMPLE 5-10

Determine the voltage at the base of the transistor, the resonant frequency, and the peak-to-peak value of the output signal voltage for the class C amplifier in Figure 5-48.

 


FIGURE 5-48

SOLUTION

$$V_{s(p)} = (1.414)(1 \text{ V}) \cong 1.4 \text{ V}$$

The base is clamped at

$$-(V_{s(p)} - 0.7) = -0.7 \text{ V dc}$$

The signal at the base has a positive peak of +0.7 V and a negative peak of

$$-V_{s(p)} + (-0.7 \text{ V}) = -1.4 \text{ V} - 0.7 \text{ V} = -2.1 \text{ V}$$

The resonant frequency is

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1 \text{ s}}{2\pi\sqrt{(220 \mu\text{H})(680 \text{ pF})}} = 411 \text{ kHz}$$

The output signal has a peak-to-peak value of

$$V_{pp} = 2V_{CC} = 2(15 \text{ V}) = 30 \text{ V}$$

PRACTICE EXERCISE

How could you make the circuit in Figure 5-48 a frequency double?

Basic Class D Operation

In a **class D amplifier**, the output transistors are operated as switches instead of operating linearly as in the classes A, B, and AB. An advantage in audio applications is that a class D amplifier can operate at a maximum theoretical efficiency of 100% compared to class A at 25% and class B/AB at 79%. In practice, efficiencies over 90% can be achieved with class D.

A basic block diagram of a class D amplifier driving a speaker is shown in Figure 5-49. It consists of a pulse-width modulator driving complementary MOSFET output transistors operating as switches and followed by a low-pass filter. Most class D amplifiers operate on dual-polarity power supplies. The MOSFETs are basically push-pull amplifiers that are operated as switching devices, rather than linear devices as in the case of class B amplifiers.

 


FIGURE 5-49 Basic class D audio amplifier.

Pulse-Width Modulation (PWM)

Pulse-width modulation is a process in which an input signal is converted to a series of pulses with widths that vary proportionally to the amplitude of the input signal. This is illustrated in Figure 5–50 for one cycle of a sinusoidal signal. Notice that the pulse width is wider when the amplitude is positive and narrower when the amplitude is negative. The output will be a square wave if the input is zero.

 


FIGURE 5–50 Pulse-width modulated sine wave.

The PWM signal is typically produced using a comparator circuit. Comparators are discussed in more detail in Chapter 8 but here is a basic explanation of how they work. A comparator has two inputs and one output, as shown by the symbol in Figure 5–51. The input labeled $+$ is called the noninverting input, and the input labeled $-$ is the inverting input. When the voltage on the inverting input exceeds the voltage on the noninverting input, the comparator switches to its *negative* saturated output state. When the voltage on the noninverting input exceeds the voltage on the inverting input, the comparator switches to its *positive* saturated output state. This is illustrated in Figure 5–51 for one cycle of a sine wave voltage on the noninverting input and a higher frequency triangular wave voltage on the inverting input.

 


FIGURE 5–51 A basic pulse-width modulator.

The comparator inputs are typically very small voltages (mV range); the comparator output is “rail-to-rail,” which means that the positive maximum is near the positive dc supply voltage and the negative maximum is near the negative dc supply voltage. An output of ± 12 V or 24 V peak-to-peak is not unusual. From this, you can see that the gain can be

quite high. For example, if the input signal is 10 mV_{pp}, the voltage gain is $24 \text{ V}_{pp} / 10 \text{ mV}_{pp} = 2400$. Since the comparator output amplitude is constant for a specified range of input voltages, the gain is dependent on the input signal voltage. If the input signal is 100 mV_{pp}, the output is still 24 V_{pp}, and the gain is 240 instead of 2400.

FREQUENCY SPECTRA All nonsinusoidal waveforms are made up of harmonic frequencies. The frequency content of a particular waveform is called its *spectrum*. When the triangular waveform modulates the input sine wave, the resulting spectrum contains the sine wave frequency, f_{input} , plus the fundamental frequency of the triangular modulating signal, f_m , and harmonic frequencies above and below the fundamental frequency. These harmonic frequencies are due to the fast rise and fall times of the PWM signal and the flat areas between the pulses. A simplified frequency spectrum of a PWM signal is shown in Figure 5-52. The frequency of the triangular waveform must be significantly higher than the highest input signal frequency so that the lowest frequency harmonic is well above the range of input signal frequencies.

 


FIGURE 5-52 Frequency spectrum of a PWM signal.

The Complementary MOSFET Stage

The MOSFETs are arranged in a common-source complementary configuration to provide power gain. Each transistor switches between the *on* state and the *off* state and when one transistor is *on*, the other one is *off*, as shown in Figure 5-53. When a transistor is *on*, there is very little voltage across it and, therefore, there is very little power dissipated even though it may have a high current through it. Remember, the on-resistance of a MOSFET is very low. When a transistor is *off*, there is no current through it and, therefore, there is no power dissipated. The only time power is dissipated in the transistors is during the short switching time. Power delivered to a load can be very high because a load will have a voltage across it nearly equal to the supply voltages and a high current through it.

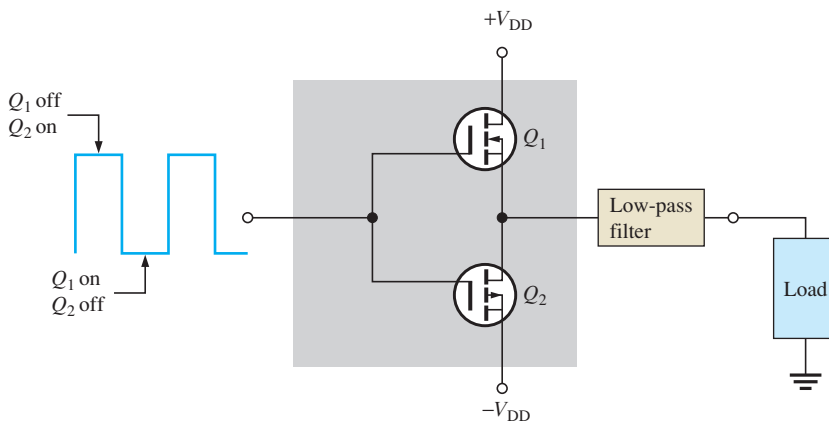


FIGURE 5-53 Complementary MOSFETs operating as switches to amplify power.

EFFICIENCY When Q_1 is *on*, it is providing current to the load. However, ideally the voltage across it is zero so the internal power dissipated by Q_1 is

$$P_{DQ} = V_{Q1}I_L = (0 \text{ V})I_L = 0 \text{ W}$$

At the same time, Q_2 is *off* and the current through it is zero, so the internal power is

$$P_{DQ} = V_{Q2}I_L = V_{Q2}(0 \text{ A}) = 0 \text{ W}$$

Ideally, the output power to the load is $2V_Q I_L$. The maximum ideal efficiency is, therefore,

$$eff_{max} = \frac{P_{out}}{P_{tot}} = \frac{P_{out}}{P_{out} + P_{DQ}} = \frac{2V_Q I_L}{2V_Q I_L + 0 \text{ W}} = 1$$

As a percentage, $eff_{max} = 100\%$.

In a practical case, each MOSFET would have a few tenths of a volt across it in the *on* state. There is also a small internal power dissipation in the comparator and triangular wave generator. Also, power is dissipated during the finite switching time, so the ideal efficiency of 100% can never be reached in practice.

Low-Pass Filter

The low-pass filter removes the modulating frequency and harmonics and passes only the original signal to the output. The filter has a bandwidth that passes only the input signal frequencies, as illustrated in Figure 5–54.

 


FIGURE 5–54 The low-pass filter removes all but the input signal frequency from the PWM signal.

Signal Flow

Figure 5–55 shows the signals at each point in a class D amplifier. A small audio signal is applied and pulse-width modulated to produce a PWM signal at the output of the modulator where voltage gain is achieved. The PWM drives the complementary MOSFET stage to achieve power amplification. The PWM signal is filtered and the amplified audio signal appears on the output with sufficient power to drive a speaker.

 


FIGURE 5–55 Signal flow in a class D amplifier.

SECTION 5-7 CHECKUP

1. How is a class C amplifier normally biased?
2. What is the purpose of the tuned circuit in a class C amplifier?
3. Name the three stages of a class D amplifier.
4. What is the pulse width proportional to in pulse-width modulation?
5. What is the function of the low-pass filter in a class D amplifier?

5-8 IC POWER AMPLIFIERS

An integrated circuit (IC) is a network of interconnected circuit elements (transistors, diodes, resistors) in a single piece of silicon that forms a functioning circuit. For analog electronics, the operational amplifier, introduced in Chapter 6, is the most common type of IC. In this section, you will learn about IC circuits specifically designed to provide power to a load. Two specific IC audio amplifiers, the National Semiconductor LM384 and the Freescale Semiconductor MC34119, are introduced.

After completing this section, you should be able to

- Give principal features and describe applications for IC power amplifiers
- Describe principal specifications of an integrated circuit power amplifier
- Show how to configure an LM384 audio power amplifier as a basic amplifier
- Explain how an LM384 can be used as the amplifier for an intercom system

Originally, small integrated circuit (IC) power amplifiers were designed for audio applications; they were designed to directly connect a speaker to the output. As applications were expanded, so was the proliferation of device types. Today, there are many IC amplifiers specifically designed as power amplifiers. Their principal advantages over small discrete power amplifiers are high reliability and low cost.

IC power amplifiers are used in applications ranging from small consumer appliances to power supplies, industrial motor controllers, and regulator designs. Most contain a class A or AB power amplifier stage along with associated driver stages and frequently include voltage gain.

The typical output power from a power IC is a few watts although some ICs can provide 100 W or more to a load with external power transistors. The maximum output power from any power amplifier is very dependent on proper heat sinking. Manufacturers' data sheets provide information on heat sinks required for IC power amplifiers.

The National Semiconductor LM384

An example of a typical small-power audio amplifier is the LM384.⁴ It is available in a standard 14-pin dual-in-line package that contains a metal heat sink tab as shown in Figure 5-56. A copper frame is connected to the center three pins on either side (pins 3, 4, 5, and 10, 11, 12) to form a heat sink that is connected to ground.

The LM384 has an internally fixed gain of 50 and operates on a single supply voltage in the range from 9 V to 24 V. The output voltage is centered at one-half the supply voltage. Choice

 


FIGURE 5-56 LM384 dual-in-line packages.

⁴Data sheet for LM384 available at www.national.com

of supply voltage depends on the required power out and the load. In addition, like many IC power amplifiers, it features short-circuit protection and thermal shutdown circuitry. It can provide up to 5 W of power to a load with appropriate heat sinking. Without an external heat sink, the maximum power output is reduced to 1.5 W.

Internally, the circuit has an emitter-follower and a differential voltage amplifier (discussed in Chapter 6). This is followed by a CE driver stage and a single-ended push-pull output stage. All stages are dc coupled. The LM384 has two inputs, one is an inverting input (labeled -), and the other is a noninverting input (labeled +).

Operation of the LM384 as a basic power amplifier requires only the addition of a few external components, as shown in Figure 5-57. In this illustration, the load consists of a small speaker, capacitively coupled through C_3 to the output. The inverting input of the LM384 is connected to the variable leg of R_1 , a potentiometer that serves as a volume control. The noninverting input is shown connected to ground. Depending on the application, either input can be used by itself or the signal can be connected between the inputs. The RC network, composed of R_2 and C_2 , suppresses by low-pass filtering action the very high-frequency oscillation that can interfere with any nearby sensitive RF circuits.


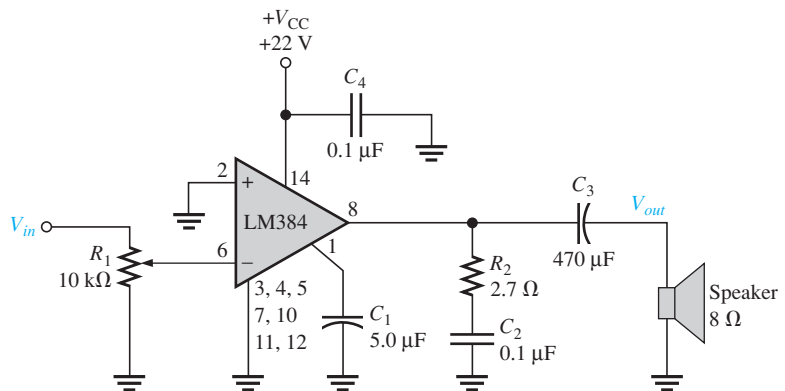



FIGURE 5-57 A basic amplifier using the LM384 audio power amplifier.

POWER OUTPUT The data sheet for the LM384 gives a curve of the output power to a load as a function of device dissipation, as shown in Figure 5-58. The curves are different for various load resistors; an 8 Ω load resistor is shown. The power supply voltage can be selected based on the required output power and minimum distortion required. The heat sink must be capable of dissipating the device power. For example, if the heat sink can handle 3 W of power from the device, a 22 V power supply can be used to deliver nearly 5 W to the load at 3% total harmonic distortion (THD).

FIGURE 5-58 LM384 power dissipation as a function of output power in an 8 Ω load.

 

SYSTEM EXAMPLE 5-3

 

With a few modifications, the basic amplifier can become the heart of a small system, such as the intercom system shown in Figure SE5-5. In this system, a small step-up transformer of 1:25 multiplies the basic gain of 50 to 1250. One speaker acts as a microphone while the second serves the traditional role of speaker. The DPDT switch controls which speaker is the talker and which is the listener. In the talk position, speaker 1 is the microphone while speaker 2 is the speaker; in the listen position, the roles are reversed.

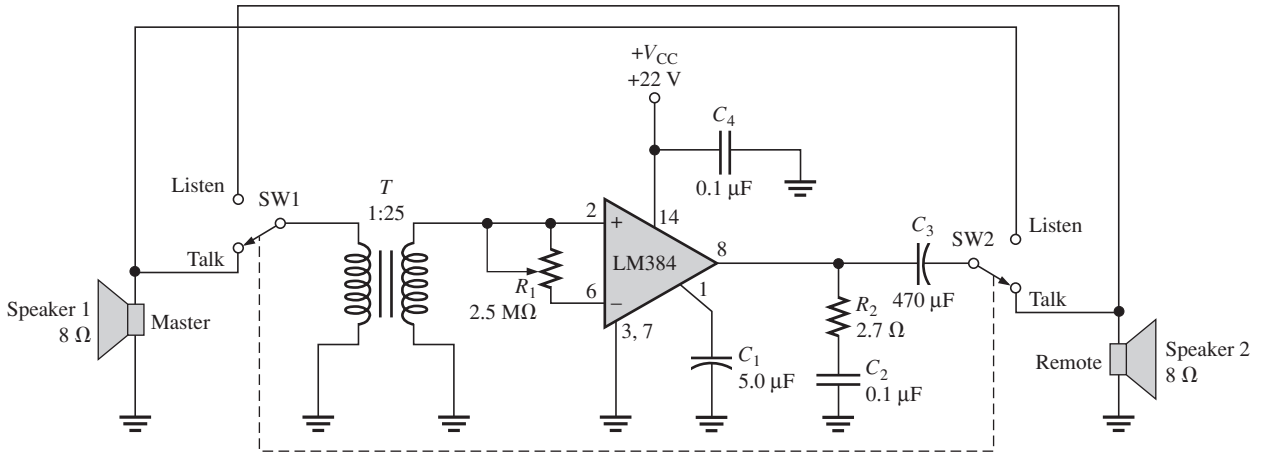


FIGURE SE5-5 A basic intercom using an LM384 as the amplifier.

The Freescale Semiconductor MC34119 Low-Power Audio Amplifier

The Freescale Semiconductor MC34119 is a low-power IC audio amplifier that is designed to run on battery power for telephone applications such as telephone speaker phones. It is contained in an 8-pin DIP package (and is available in a surface-mount package). It can drive a small load (8 Ω to 100 Ω) with more than 250 mW for a 6 V supply voltage and can deliver more power using higher supply voltages. A chip-disable input allows for powering down or muting the input and reduces the current drain from the battery to 65 μA (typical).

Figure 5-59 illustrates a basic amplifier with the MC34119. The voltage gain can be controlled by two external resistors, (R_f and R_i) that can set the gain from less than 1 to 200

 


FIGURE 5-59 A small IC amplifier designed to operate from a battery.

and is equal to the ratio of R_f to R_i . (Gain control is discussed in Chapter 6.) For the circuit shown, the voltage gain is 5.0. The output is coupled directly to the load (in this case, a speaker) with no coupling capacitor.

SECTION 5–8 CHECKUP

1. What are some applications for IC power amplifiers?
2. What advantage do IC power amplifiers have over discrete designs?
3. What is the voltage gain of an LM384?
4. What are the two inputs to an LM384 called?

SUMMARY

- Three ways to couple amplifier stages together are capacitive coupling, transformer coupling, and direct coupling.
- Capacitive coupling and transformer coupling provide a low-impedance ac path while blocking dc. Direct coupling requires that the dc conditions from one stage are compatible with the requirements of the next stage.
- General points to alleviate noise problems in amplifiers are
 1. Keep wiring short and make signal return loops as small as possible.
 2. Use bypass capacitors between power supply and ground.
 3. Reduce noise sources and separate or shield the noise source and the circuit.
 4. Ground circuits at a single point, and isolate grounds that have high currents from those with low currents.
 5. Keep the bandwidth of amplifiers no larger than necessary.
- One common type of high-frequency cable is coax, a form of shielded wiring. Coax typically has a characteristic impedance between 50 Ω and 100 Ω . It should be terminated in its characteristic impedance to prevent reflections.
- Tuned amplifiers use one or more resonant circuits to select a band of frequencies.
- A mixer combines a radio frequency (RF) signal with a sine wave generated from a local oscillator to produce an intermediate frequency (IF) that is amplified by an amplifier tuned to the IF.
- Negative feedback produces a self-correcting action that can produce excellent bias stability and gain stability in amplifiers.
- The voltage gain of an amplifier without feedback is called open-loop voltage gain. The voltage gain of an amplifier with feedback is called closed-loop voltage gain.
- A class A amplifier operates entirely in the linear region of the transistor's characteristic curves. The transistor conducts during the full 360° of the input cycle.
- The Q-point must be centered on the ac load line for maximum class A output signal swing.
- The maximum efficiency of a class A amplifier is 25%.
- A class B amplifier operates in the linear region for half of the input cycle (180°), and it is in cutoff for the other half.
- The Q-point is at cutoff for class B operation.
- Class B amplifiers are normally operated in a push-pull configuration in order to produce an output that is a replica of the input.
- The maximum efficiency of a class B amplifier is 79%.
- A class AB amplifier is biased slightly above cutoff and operates in the linear region for slightly more than 180° of the input cycle.
- Class AB eliminates the crossover distortion found in pure class B.
- Class C amplifiers are biased below cutoff and usually have a tuned circuit load.
- Class D amplifiers are nonlinear switching amplifiers. They employ pulse-width modulation in conjunction with a MOSFET push-pull switching amplifier and a low-pass filter.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Class A An amplifier that operates in the active region at all times.

Class AB An amplifier that is biased into slight conduction; the Q-point is slightly above cutoff.

Class B An amplifier that has the Q-point located at cutoff, causing the output current to vary only during one-half of the input cycle.

Class C An amplifier that is biased below cutoff and has a tuned circuit load.

Class D A nonlinear switching amplifier that uses pulse-width modulation, a push-pull switching amplifier, and a low-pass filter.

Closed-loop voltage gain The net voltage gain of an amplifier when negative feedback is included.

Current mirror A circuit that uses matching diode junctions to form a current source. The current in a diode is reflected as a matching current in the other junction (which is typically the base-emitter junction of a transistor). Current mirrors are commonly used to bias a push-pull amplifier.

Efficiency (power) The ratio of the signal power supplied to the load to the power from the dc supply.

Intermediate frequency A fixed frequency that is lower than the RF, produced by beating an RF signal with an oscillator frequency.

Mixer A nonlinear circuit that combines two signals and produces the sum and difference frequencies.

Open-loop voltage gain The voltage gain of an amplifier without external feedback.

Power gain The ratio of the power delivered to the load to the input power of an amplifier.

Pulse-width modulation A process in which the input signal is converted to a series of pulses whose width is proportional to the signal amplitude.

Push-pull A type of class B amplifier with two transistors in which one transistor conducts for one half-cycle and the other conducts for the other half-cycle.

Quality factor (Q) A dimensionless number that is the ratio of the maximum energy stored in a cycle to the energy lost in a cycle.

KEY FORMULAS

- (5-1) $Z_0 = \sqrt{\frac{L}{C}}$ Characteristic impedance of a transmission line
- (5-2) $f_r = \frac{1}{2\pi\sqrt{LC}}$ Resonant frequency (high Q resonant circuit)
- (5-3) $Q = \frac{X_L}{R} = \frac{f_r}{BW}$ Quality factor of a resonant circuit
- (5-4) $R'_L = \left(\frac{N_{pri}}{N_{sec}}\right)^2 R_L$ Reflected resistance of a load resistor by a transformer
- (5-5) $A_p = \frac{P_L}{P_{in}}$ Amplifier power gain
- (5-6) $A_p = A_v^2 \left(\frac{R_{in}}{R_L}\right)$ Alternate amplifier power gain
- (5-7) $P_{DQ} = I_{CQ}V_{CEQ}$ Power dissipation of a transistor
- (5-8) $P_{out(max)} = 0.5I_{CQ}V_{CEQ}$ Maximum power from a class A amplifier
- (5-9) $I_{c(sat)} = \frac{V_{CC}}{R_L}$ AC saturation current for a two-supply operation with a push-pull amplifier

SELF-TEST


Answers are at the end of the chapter.

- If an amplifier has a decibel voltage gain of 60 dB, the actual gain is
 (a) 60 (b) 1000 (c) 1200 (d) 1,000,000

2. If two identical stages with a gain of 25 dB each are connected together and the equivalent voltage divider has an attenuation of 5 dB, the overall gain of the amplifier is
 (a) 20 dB (b) 45 dB (c) 55 dB (d) 70 dB
3. Noise can enter a circuit
 (a) by capacitive or inductive coupling (b) through the power supply
 (c) from within the circuit (d) all of these answers
4. The impedance of coax cable is typically
 (a) less than 10 Ω (b) 50 Ω to 100 Ω
 (c) 200 Ω to 500 Ω (d) answer depends on the length of the line
5. Neutralization is a technique used with high-frequency amplifiers to eliminate
 (a) oscillations (b) noise
 (c) distortion (d) all of these answers
6. The quality factor, Q , is a pure number that is the ratio of
 (a) X_L to X_C (b) X_L to R
 (c) X_C to R (d) none of these answers
7. In a tuned circuit, if the Q is high, the
 (a) resistance is high (b) bandwidth is small
 (c) frequency is low (d) power is high
8. Negative feedback can provide excellent
 (a) bias stability (b) gain stability
 (c) both (a) and (b) (d) neither (a) nor (b)
9. The peak current a class A amplifier can deliver to a load depends on the
 (a) maximum rating of the power supply (b) quiescent current
 (c) current in the bias resistors (d) size of the heat sink
10. An amplifier that operates in the linear region at all times is
 (a) Class A (b) Class AB
 (c) Class B (d) all of these answers
11. The efficiency of a power amplifier is the ratio of the power delivered to the load to the
 (a) input signal power (b) power dissipated in the last stage
 (c) power from the power supply (d) none of these answers
12. Crossover distortion is a problem for
 (a) Class A amplifiers (b) Class AB amplifiers
 (c) Class B amplifiers (d) all of these answers
13. A current mirror in a push-pull amplifier should give an I_{CQ} that is
 (a) equal to the current in the bias resistors and diodes
 (b) twice the current in the bias resistors and diodes
 (c) half the current in the bias resistors and diodes
 (d) zero
14. To avoid crossover distortion with an E-MOSFET push-pull amplifier, you should bias the MOSFETs with
 (a) a current mirror (b) self-bias
 (c) a voltage divider (d) a separate power supply
15. The transistor in a class C amplifier conducts for
 (a) 360° (b) 180°
 (c) slightly less than 180° (d) much less than 180°
16. The final stage of a class D amplifier is the
 (a) switching amplifier (b) low-pass filter
 (c) comparator (d) PWM
17. Typically, an IC power amplifier
 (a) does not need a heat sink (b) costs more than a discrete circuit
 (c) has high reliability (d) all of these answers

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

 

Refer to Figure 5–60.

- If C_3 is open,
 1. The dc drain voltage of Q_1 will
(a) increase (b) decrease (c) not change
 2. The ac drain voltage of Q_1 will
(a) increase (b) decrease (c) not change
- If R_{E1} is $0\ \Omega$ because of a direct short across it,
 3. The dc emitter current will
(a) increase (b) decrease (c) not change
 4. The overall voltage gain of the amplifier will
(a) increase (b) decrease (c) not change
 5. The input resistance of Q_2 will
(a) increase (b) decrease (c) not change

Refer to Figure 5–67.

- If Q_2 has an open emitter,
 6. The positive side of the ac output voltage will
(a) increase (b) decrease (c) not change
 7. The negative side of the ac output voltage will
(a) increase (b) decrease (c) not change
- If D_1 is shorted,
 8. The bias current in R_1 will
(a) increase (b) decrease (c) not change
 9. The ac output voltage will
(a) increase (b) decrease (c) not change

Refer to Figure 5–69.

- If C_2 is open,
 10. The gain will
(a) increase (b) decrease (c) not change
- If C_3 is open,
 11. The distortion will
(a) increase (b) decrease (c) not change
- If R_8 is shorted,
 12. The gain will
(a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 5-1 Capacitively Coupled Amplifiers

1. For the two-stage capacitively coupled amplifier shown in Figure 5–60, compute the overall voltage gain, the input resistance, and the output resistance. Assume the g_m of the JFET is $2700\ \mu\text{S}$ and β_{ac} of the BJT is 150.

 


FIGURE 5-60

- Using the results of Problem 1, draw the ac amplifier model for the two-stage amplifier in Figure 5-60. (See Figure 5-5 for an example.)
- For the two-stage amplifier modeled in Figure 5-61, determine the ordinary gain and the decibel voltage gain.
- Assume a $1.0\text{ k}\Omega$ load is connected to the amplifier modeled in Figure 5-61. What is the new gain?

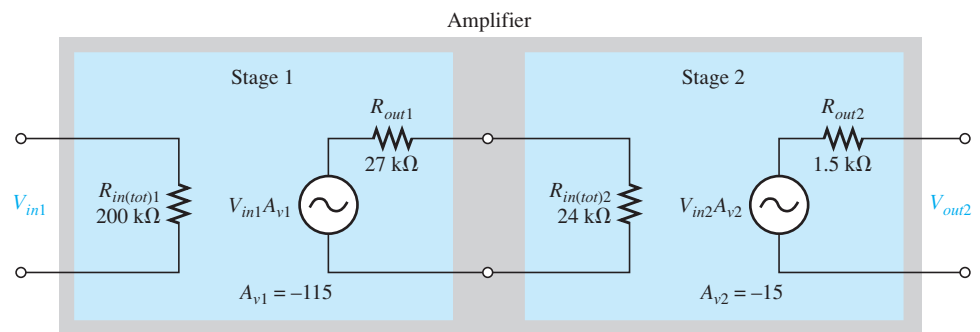


FIGURE 5-61

- Assume a two-stage amplifier is constructed from two identical amplifiers with the following specifications: $R_{in} = 30\text{ k}\Omega$, $R_{out} = 2\text{ k}\Omega$, $A_{v(NL)} = 80$.
 - Draw the ac model of the amplifier.
 - What is the overall gain when the two stages are connected together?
 - If a $3\text{ k}\Omega$ load resistor is connected to the amplifier, what is the overall gain?
- Determine the decibel gain for the amplifier in Problem 5(b).
- Assume Q_3 in Figure 5-4 is replaced with a darlington transistor with a β_{ac} of 10,000. What effect will this have on the amplifier's gain?


SECTION 5-2 RF Amplifiers

- RG180B/U is a coaxial cable with a nominal impedance of $95\ \Omega$ and a capacitance per foot of 15.5 pF/foot . Determine the inductance per foot for this cable.
- Why is it important to terminate a high-frequency cable in its characteristic impedance?
- For the circuit in Figure 5-9, assume the capacitor in the drain circuit is 68 pF and the coil has an inductance of $300\ \mu\text{H}$ with a resistance of $15.2\ \Omega$. What is the center frequency for the amplifier?
- For the circuit in Figure 5-9, what happens to the gain if the input signal is larger? Explain your answer.
- Assume a parallel resonant circuit is constructed from a $200\ \mu\text{H}$ inductor with $9.5\ \Omega$ of resistance and a 1000 pF capacitor.
 - What is the resonant frequency?
 - What is the Q ?
 - What is the bandwidth?

SECTION 5-3 Transformer-Coupled Amplifiers

13. Assume a 10:1 step-down transformer has a load of 100 Ω connected across the secondary. What is the reflected resistance in the primary circuit?
14. The audio frequency power amplifier shown in Figure 5-62 has a 3:1 step-down transformer in the collector circuit with a 16 Ω load resistor connected to the secondary. Determine the gain of the circuit. (Since r'_e is small compared to R_{E1} , it can be ignored.)

FIGURE 5-62

 

15. Draw the dc and ac load lines for the circuit in Figure 5-62. (Assume the dc resistance of the transformer is very small and can be ignored.)
16. The amplifier in Figure 5-63 is a low-power audio amplifier with collector-feedback bias. The transformer is a step-down impedance-matching transformer designed to give a reflected resistance in the primary of 1000 Ω when the load is 8 Ω (such as the speaker). The dc resistance of the primary winding is 66 Ω.
 - (a) Compute V_{CE} and the I_E for the transistor assuming $\beta_{ac} = \beta_{DC} = 150$.
 - (b) Compute A_v , A_p , and power delivered to the load when the input is 500 mV pp.

 


FIGURE 5-63

17. Assume the IF amplifier in Figure 5-64 has an IF transformer with a primary inductance of 180 μH and a resistance of 6.5 Ω. Internally, there is a 680 pF capacitor connected in parallel with the primary. Find the Q of the resonant circuit, the unloaded voltage gain, $A_{v(NL)}$, and the bandwidth, BW .
18. What is the purpose of R_3 and C_3 in the circuit of Figure 5-64?

 



FIGURE 5-64

SECTION 5-4 Direct-Coupled Amplifiers

19. Figure 5-65 shows two dc coupled CC amplifiers (Q_2 and Q_3) with no coupling capacitors required at the input or output. Q_1 is a current source for Q_2 and produces very high input resistance for the amplifier.

- (a) Assuming the base of Q_2 is at zero volts, determine the following dc parameters: $I_{C(Q2)}$, $V_{B(Q3)}$, $I_{C(Q3)}$, $V_{E(Q3)}$.
- (b) Assuming a 5 V rms input signal, what power is delivered to the load resistor?

FIGURE 5-65

 

- 20. What are advantages of a dc coupled CC amplifier such as shown in Figure 5-65?
- 21. Draw the dc load line for Q_3 in Figure 5-65.
- 22. Assume the emitter resistor for Q_3 is open. Will the base-emitter junction of Q_3 still be forward-biased? What happens to the collector current in Q_3 ?
- 23. For the circuit in Figure 5-20, assume a 10 k ohm resistor is substituted for R_{F2} . What effect, if any, does this change have on
 - (a) the dc emitter voltage of Q_1 ?
 - (b) the voltage gain?
 - (c) the input resistance of the amplifier?
- 24. Each of three cascaded amplifiers has a decibel voltage gain of 15. What is the overall decibel voltage gain? What is the overall linear voltage gain?

SECTION 5-5 Class A Power Amplifiers

25. Figure 5-66 shows a CE power amplifier in which the collector resistor serves also as the load resistor. Assume $\beta_{DC} = \beta_{ac} = 100$.
- Determine the dc Q-point (I_{CQ} and V_{CEQ}).
 - Determine the voltage gain and the power gain.

 


FIGURE 5-66

- For the circuit in Figure 5-66, determine the following:
 - the power dissipated in the transistor with no load.
 - the total power from the power supply with no load.
 - the signal power in the load with a 500 mV input.
- Refer to the circuit in Figure 5-66. What changes would be necessary to convert the circuit to a *pn*p transistor with a positive supply? What advantage would this have?
- Assume a CC amplifier has an input resistance of 2.2 kΩ and drives an output load of 50 Ω. What is the power gain?

SECTION 5-6 Class B Power Amplifiers

- Refer to the Class AB amplifier in Figure 5-67.
 - Determine the dc parameters $V_{B(Q1)}$, $V_{B(Q2)}$, V_E , I_{CQ} , $V_{CEQ(Q1)}$, $V_{CEQ(Q2)}$.
 - For the 5 V rms input, determine the power delivered to the load resistor.
- Draw the load line for the *npn* transistor in Figure 5-67. Label the saturation current, $I_{C(sat)}$, and show the Q-point.

 


FIGURE 5-67

31. Refer to the Class AB amplifier in Figure 5–68 operating with a single power supply.
 - (a) Determine the dc parameters $V_{B(Q1)}$, $V_{B(Q2)}$, V_E , I_{CQ} , $V_{CEQ(Q1)}$, $V_{CEQ(Q2)}$.
 - (b) Assuming the input voltage is 10 V pp, determine the power delivered to the load resistor.
32. Refer to the Class AB amplifier in Figure 5–68.
 - (a) What is the maximum power that could be delivered to the load resistor?
 - (b) Assume the power supply voltage is raised to 24 V. What is the new maximum power that could be delivered to the load resistor?
33. Refer to the Class AB amplifier in Figure 5–68. What fault or faults could account for each of the following troubles?
 - (a) a positive half-wave output signal
 - (b) zero volts on both bases and the emitters
 - (c) no output; emitter voltage = +15 V
 - (d) crossover distortion observed on the output waveform
34. Assume the n -channel E-MOSFET shown in Figure 5–69 has a threshold voltage of 2.75 V and the p -channel E-MOSFET has a threshold voltage of -2.75 V.
 - (a) What resistance setting for R_5 will bias the output transistors to class AB operation?
 - (b) Assuming the input voltage is 150 mV rms, what is the rms voltage delivered to the load?
 - (c) What is the power delivered to the load with this setting?

 


FIGURE 5–68

 


FIGURE 5–69

SECTION 5-7 Class C and Class D Power Amplifiers

35. A class C amplifier has a tuned circuit in the collector containing a 330 μ H coil and a 470 pF capacitor. Assume that you want this amplifier to pass a 455 kHz IF signal. How much capacitance must you add, and would you add it in parallel or series with the 470 pF capacitor?
36. The sine wave input signal to a pulse-width modulator is crossing the zero axis going positive. What is happening to the output of the PWM?

SECTION 5-8 IC Power Amplifiers

37. Refer to Figure 5–58. Assume you are operating an LM384 from a +18 V power supply and are dissipating 3 W in the load. How much power must the LM384 and its heat sink dissipate?
38. Assume you want to increase the voltage gain of the MC34119 in Figure 5–59 by changing R_f . What value should you specify if the gain required is 15?

MULTISIM TROUBLESHOOTING PROBLEMS

MULTISIM



39. Open file P05-39 and determine the fault.
40. Open file P05-40 and determine the fault.
41. Open file P05-41 and determine the fault.
42. Open file P05-42 and determine the fault.
43. Open file P05-43 and determine the fault.
44. Open file P05-44 and determine the fault.
45. Open file P05-45 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 5-1

1. R_{in} , R_{out} , and $A_{v(NL)}$
2. 32 dB
3. Low noise and high input resistance
4. The signal levels are small and can easily be obscured by noise.

SECTION 5-2

1. Coax is a high-frequency cable with constant impedance independent of length. The outer conductor helps shield the signal and prevent interference.
2. Neutralization is a method of preventing unwanted oscillations by adding *negative* feedback to just cancel the *positive* feedback caused by internal capacitances of an amplifier.
3. Automatic Gain Control
4. Q is a dimensionless number that is the ratio of the maximum energy stored in a cycle to the energy lost in a cycle. It can be expressed as $Q = X_L/R = f_r/BW$.

SECTION 5-3

1. RF indicates *Radio Frequency* and is any frequency useful for radio transmission. IF means *Intermediate Frequency*; it represents a frequency that has been shifted for processing.
2. A mixer combines two signals in a nonlinear circuit, producing the sum and difference frequencies as a result. The difference frequency becomes the IF.
3. The RF signal and a signal from the local oscillator
4. A load resistor affects the Q by reflecting a resistance into the primary side. Since Q is the ratio of X_L to R , the increase in R decreases Q .
5. Any instrument connected to the circuit can change the Q of the circuit because of resistance loading and can change the frequency because of capacitance loading.

SECTION 5-4

1. Direct coupling reduces the parts count and allows for frequencies down to dc.
2. Negative feedback returns a portion of the output in a way that tends to cancel changes in the bias circuit or the gain.
3. The capacitor has no effect on the dc circuit, but it increases the open-loop gain. A higher open-loop gain means a small change in a circuit parameter will have less effect.
4. The gain is determined by the reciprocal of the feedback fraction.

SECTION 5-5

1. To dissipate excessive heat
2. The collector
3. Cutoff and saturation clipping
4. 25%
5. It is the ratio of the input resistance to the output resistance.

SECTION 5-6

1. The signal can be direct coupled at the input and output; parts count can be reduced.
2. Crossover distortion occurs when the input signal is less than the base-emitter drop of the push-pull amplifier. It can be avoided by biasing the class B amplifier on slightly, producing class AB operation.
3. 79%
4. At the threshold voltage
5. The diodes compensate for the effects of the three base-emitter junctions.

SECTION 5-7

1. It is biased below cutoff.
2. The tuned circuit provides high gain for only a small bandwidth of frequencies near its resonant frequency.
3. The three stages are the pulse-width modulator, the switching amplifier, and the low-pass filter.
4. It is proportional to the amplitude of the input signal.
5. The low-pass filter removes the modulating frequency and its harmonics and passes only the input signal.

SECTION 5-8

1. Small amplifiers for consumer products (TVs, radios, telephone speaker phones), alarms, intercoms, small motor controls, and the like
2. Simplified application, reliability, and cost
3. 50
4. Inverting and noninverting

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 5-1 (a) 400 mV (b) 99.9
- 5-2 75 Ω
- 5-3 The Q-point is unchanged; the ac load line is flatter due to increased resistance.
- 5-4 An open C_2 reduces the gain. The BW is not affected.
- 5-5 The β affects the input resistance of both stages. The gain is affected only by the input resistance of Q_2 and reduces the gain to 595.
- 5-6 46 dB
- 5-7 The efficiency goes up because no power is wasted in R_{E3} . The disadvantage is that the speaker has a dc current (the emitter current) in the coil.
- 5-8 15 V, 0.94 A
- 5-9 1.83 k Ω
- 5-10 Change L to 55 μ H or change C to 17 nF.

ANSWERS TO SELF-TEST

1. (b) 2. (b) 3. (d) 4. (b) 5. (a) 6. (b) 7. (b)
8. (c) 9. (b) 10. (a) 11. (c) 12. (c) 13. (a) 14. (c)
15. (d) 16. (b) 17. (c)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. not change 2. increase 3. increase 4. increase
5. decrease 6. not change 7. decrease 8. increase
9. decrease 10. decrease 11. increase 12. not change

CHAPTER 6

OPERATIONAL AMPLIFIERS

OUTLINE

- 6-1 Introduction to Operational Amplifiers
- 6-2 The Differential Amplifier
- 6-3 Op-Amp Data Sheet Parameters
- 6-4 Negative Feedback
- 6-5 Op-Amp Configurations with Negative Feedback
- 6-6 Op-Amp Impedances and Noise
- 6-7 Troubleshooting

OBJECTIVES

- Describe the basic op-amp and its characteristics
- Discuss the differential amplifier and its operation
- Discuss several op-amp parameters
- Explain negative feedback in op-amp circuits
- Analyze three op-amp configurations
- Describe impedances of the three op-amp configurations
- Troubleshoot op-amp circuits

KEY TERMS

Operational amplifier **Single-ended mode**
Differential amplifier **Differential-mode**

Common-mode **Negative feedback**
Common-mode rejection ratio (CMRR) **Closed-loop voltage gain**
Open-loop voltage gain **Noninverting amplifier**
Slew rate **Voltage-follower**
 Inverting amplifier

INTRODUCTION

So far, you have studied a number of important electronic devices. These devices, such as the diode and the transistor, are separate devices that are individually packaged and interconnected in a circuit with other devices to form a complete, functional unit. Such devices are referred to as *discrete components*.

Now you will learn more about analog (linear) integrated circuits where many transistors, diodes, resistors, and capacitors are fabricated on a single tiny chip of semiconductive material and packaged in a single case to form a functional circuit. You were introduced to a specific integrated circuit (IC) in Chapter 5 that was designed for the specific purpose of audio amplification.

In this chapter, you are introduced to a general-purpose IC, the operational amplifier (op-amp), which is the most versatile and widely used of all linear integrated circuits. Although the op-amp is made up of many resistors, diodes, and transistors, it is treated as a single device. This means that you will be concerned with what the circuit does more from an external viewpoint than from an internal, component-level viewpoint.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

6-1 INTRODUCTION TO OPERATIONAL AMPLIFIERS

Early operational amplifiers (op-amps) were used primarily to perform mathematical operations such as addition, subtraction, integration, and differentiation, thus the term *operational*. These early devices were constructed with vacuum tubes and worked with high voltages. Today, op-amps are linear integrated circuits that use relatively low supply voltages and are reliable and inexpensive.

After completing this section, you should be able to

- Describe the basic op-amp and its characteristics
- Recognize the op-amp symbol
- Identify the terminals on op-amp packages
- Describe the ideal op-amp
- Describe the practical op-amp

Symbol and Terminals

The standard **operational amplifier** (op-amp) symbol is shown in Figure 6-1(a). It has two input terminals, the inverting (−) input and the noninverting (+) input, and one output terminal. The typical op-amp operates with two dc supply voltages, one positive and the other negative, as shown in Figure 6-1(b). Usually these dc voltage terminals are left off the schematic symbol for simplicity but are always understood to be there. Some typical op-amp IC packages are shown in Figure 6-1(c).

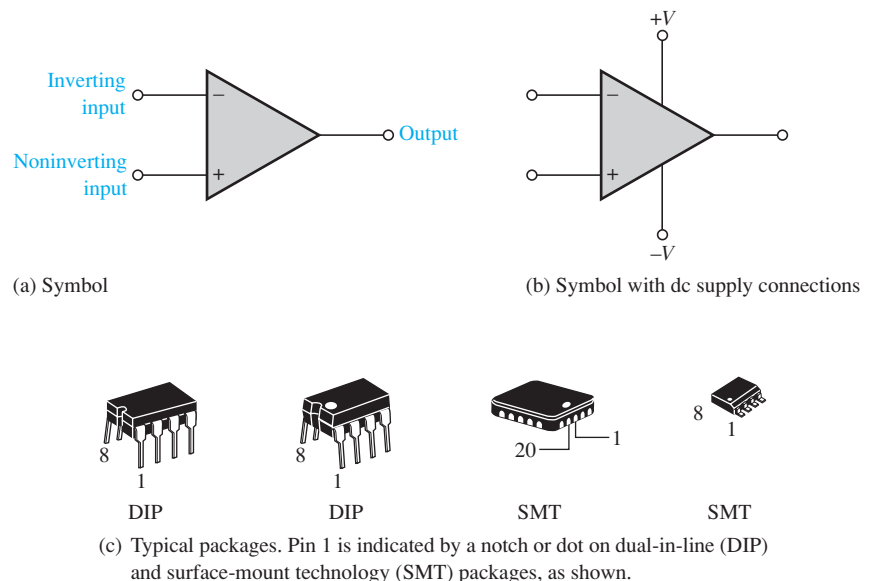


FIGURE 6-1 Op-amp symbols and packages.

The Ideal Op-Amp

To illustrate what an op-amp is, let's consider its *ideal* characteristics. A practical op-amp, of course, falls short of these ideal standards, but it is much easier to understand and analyze the device from an ideal point of view.

First, the ideal op-amp has *infinite voltage gain* and an *infinite input impedance* (open), so that it does not load the driving source. Finally, it has a *zero output impedance*. These characteristics are illustrated in Figure 6-2. The input voltage V_{in} appears between

the two input terminals, and the output voltage is $A_v V_{in}$, as indicated by the internal voltage source symbol. The concept of infinite input impedance is a particularly valuable analysis tool for the various op-amp configurations, which will be discussed in Section 6-5.

 


FIGURE 6-2 Ideal op-amp representation.

The Practical Op-Amp

Although modern integrated circuit (IC) op-amps approach parameter values that can be treated as ideal in many cases, no practical op-amp can be ideal. Any device has limitations, and the IC op-amp is no exception. Op-amps have both voltage and current limitations. Peak-to-peak output voltage, for example, is usually limited to slightly less than the difference between the two supply voltages. Output current is also limited by internal restrictions such as power dissipation and component ratings.

Characteristics of a practical op-amp are *high voltage gain*, *high input impedance*, *low output impedance*, and *wide bandwidth*. Some of these are illustrated in Figure 6-3.

 


FIGURE 6-3 Practical op-amp representation.

SECTION 6-1 CHECKUP*

1. What are the connections to a basic op-amp?
2. Describe some of the characteristics of a practical op-amp.

*Answers are at the end of the chapter.

6–2 THE DIFFERENTIAL AMPLIFIER

The op-amp typically consists of at least one differential amplifier stage. Because the differential amplifier (diff-amp) is the input stage of an op-amp, it is fundamental to the op-amp's internal operation. Therefore, it is useful to have a basic understanding of this type of circuit.

After completing this section, you should be able to

- Discuss the differential amplifier and its operation
- Explain single-ended input operation
- Explain differential-input operation
- Explain common-mode operation
- Define *common-mode rejection ratio*
- Discuss the use of differential amplifiers in op-amps

A basic **differential amplifier** (diff-amp) circuit and its symbol are shown in Figure 6–4. The diff-amp stage that makes up part of an op-amp provides high voltage gain and common-mode rejection (defined later in this section).

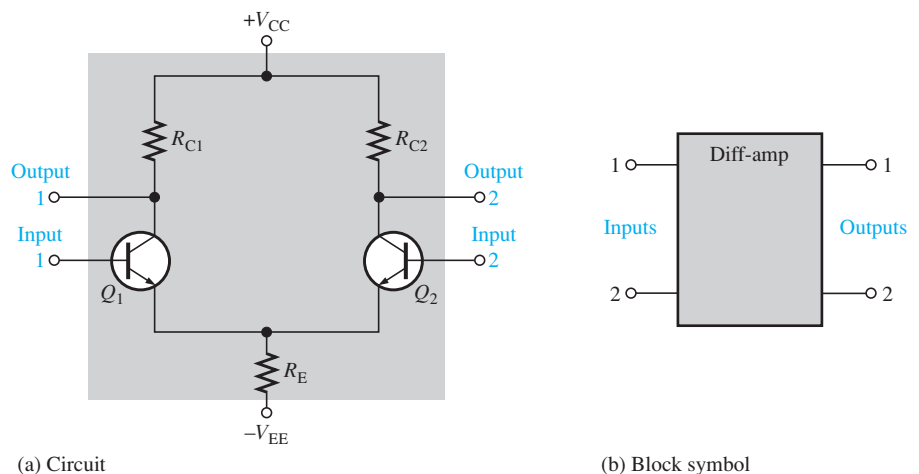


FIGURE 6–4 Basic differential amplifier.

Basic Operation

The following discussion is in relation to Figure 6–5 and consists of a basic dc analysis of the diff-amp's operation.

First, when both inputs are grounded (0 V), the emitters are at -0.7 V, as indicated in Figure 6–5(a). It is assumed that the transistors, Q_1 and Q_2 , are identically matched by careful process control during manufacturing so that their dc emitter currents are the same when there is no input signal. Thus,


$$I_{E1} = I_{E2}$$

Since both emitter currents combine through R_E ,

$$I_{E1} = I_{E2} = \frac{I_{R_E}}{2}$$


where

$$I_{R_E} = \frac{V_E - V_{EE}}{R_E}$$

 

(a) Both inputs grounded

 (b) Bias voltage on input 1 with input 2 grounded



(c) Bias voltage on input 2 with input 1 grounded

FIGURE 6-5 Basic operation of a differential amplifier (ground is zero volts) showing relative changes in currents and voltages.

Based on the approximation that $I_C \cong I_E$, it can be stated that

$$I_{C1} = I_{C2} \cong \frac{I_{R_E}}{2}$$

Since both collector currents and both collector resistors are equal (when the input voltage is zero),

$$V_{C1} = V_{C2} = V_{CC} - I_{C1}R_{C1}$$

This condition is illustrated in Figure 6-5(a).

Next, input 2 remains grounded, and a positive bias voltage is applied to input 1, as shown in Figure 6-5(b). The positive voltage on the base of Q_1 increases I_{C1} and raises the emitter voltage to

$$V_E = V_B - 0.7 \text{ V}$$

This action reduces the forward bias (V_{BE}) of Q_2 because its base is held at 0 V (ground), thus causing I_{C2} to decrease as indicated in part (b) of the diagram. The net result is that the

MULTISIM



Open file F06-05 found on the companion website. This simulation will be used to examine the dc operating characteristics of the differential amplifier.

increase in I_{C1} causes a decrease in V_{C1} , and the decrease in I_{C2} causes an increase in V_{C2} , as shown.

Finally, input 1 is grounded and a positive bias voltage is applied to input 2, as shown in Figure 6–5(c). The positive bias voltage causes Q_2 to conduct more, thus increasing I_{C2} . Also, the emitter voltage is raised. This reduces the forward bias of Q_1 , since its base is held at ground, and causes I_{C1} to decrease. The result is that the increase in I_{C2} produces a decrease in V_{C2} , and the decrease in I_{C1} causes V_{C1} to increase, as shown.

Modes of Signal Operation

SINGLE-ENDED INPUT In the **single-ended mode**, one input is grounded and the signal voltage is applied only to the other input, as shown in Figure 6–6. In the case where the signal voltage is applied to input 1 as in part (a), an inverted, amplified signal voltage appears at output 1 as shown. Also, a signal voltage appears in phase at the emitter of Q_1 . Since the emitters of Q_1 and Q_2 are common, the emitter signal becomes an input to Q_2 , which functions as a common-base amplifier. The signal is amplified by Q_2 and appears, noninverted, at output 2. This action is illustrated in part (a).

In the case where the signal is applied to input 2 with input 1 grounded, as in Figure 6–6(b), an inverted, amplified signal voltage appears at output 2. In this situation, Q_1 acts as a common-base amplifier, and a noninverted, amplified signal appears at output 1. This action is illustrated in part (b) of the figure.


 


FIGURE 6-6 Single-ended operation of a differential amplifier.

DIFFERENTIAL INPUT In the **differential mode**, two opposite-polarity (out-of-phase) signals are applied to the inputs, as shown in Figure 6–7(a). This type of operation is also referred to as *double-ended*. As you will see, each input affects the outputs.

Figure 6–7(b) shows the output signals due to the signal on input 1 acting alone as a single-ended input. Figure 6–7(c) shows the output signals due to the signal on input 2 acting

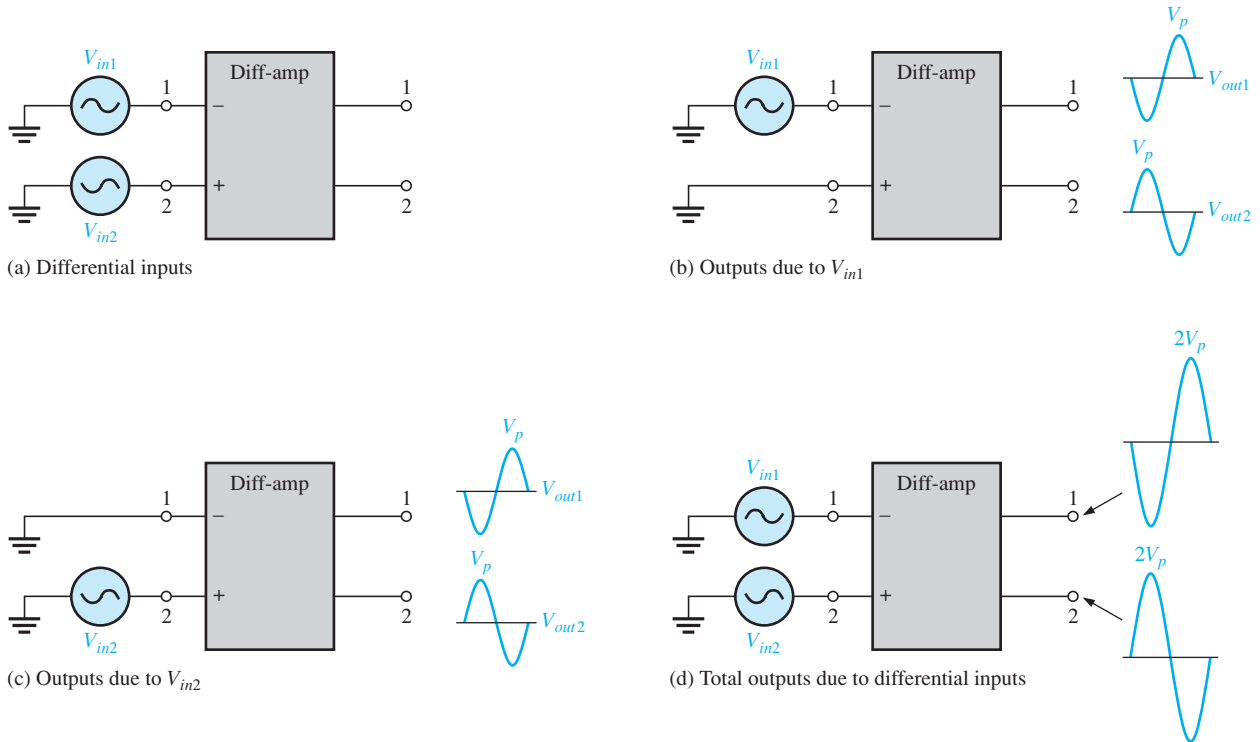alone as a single-ended input. Notice in parts (b) and (c) that the signals on output 1 are of the same polarity. The same is also true for output 2. By superimposing both output 1 signals and both output 2 signals, you get the total differential operation, as shown in Figure 6-7(d).



(a) Differential inputs

(b) Outputs due to V_{in1}

(c) Outputs due to V_{in2}

(d) Total outputs due to differential inputs


FIGURE 6-7 Differential operation of a differential amplifier.

MULTISIM



Open file F06-07 found on the companion website. This simulation demonstrates the differential operation of the differential amplifier.

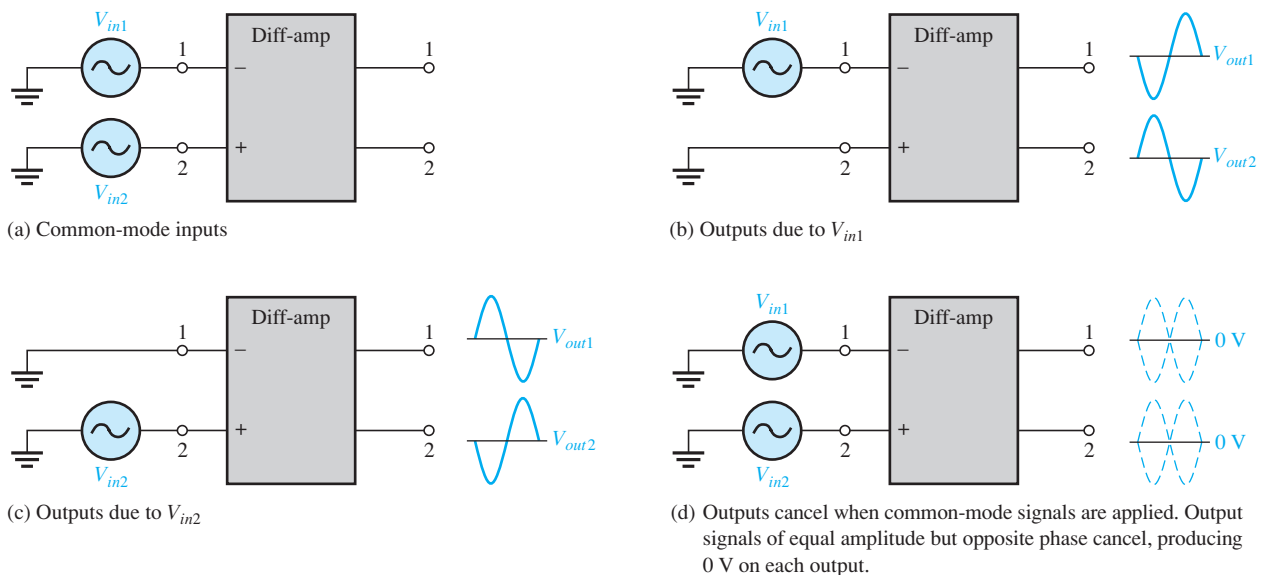COMMON-MODE INPUT One of the most important aspects of the operation of a differential amplifier can be seen by considering the **common-mode** condition where signal voltages of the same phase, frequency, and amplitude are applied to the two inputs, as shown in Figure 6-8(a). Again, by considering each input signal as acting alone, you can understand the basic operation.



(a) Common-mode inputs

(b) Outputs due to V_{in1}

(c) Outputs due to V_{in2}

(d) Outputs cancel when common-mode signals are applied. Output signals of equal amplitude but opposite phase cancel, producing 0 V on each output.

FIGURE 6-8 Common-mode operation of a differential amplifier.

MULTISIM



Open file F06-08 found on the companion website. This simulation demonstrates the common-mode operation of the differential amplifier.

Figure 6–8(b) shows the output signals due to the signal on only input 1, and Figure 6–8(c) shows the output signals due to the signal on only input 2. Notice that the corresponding signals on output 1 are of the opposite polarity, and so are the ones on output 2. When the input signals are applied to both inputs, the outputs are superimposed and they cancel, resulting in a zero output voltage, as shown in Figure 6–8(d).

This action is called *common-mode rejection*. Its importance lies in the situation where an unwanted signal appears commonly on both diff-amp inputs. Common-mode rejection means that this unwanted signal will not appear on the outputs to distort the desired signal. Common-mode signals (noise) generally are the result of the pick-up of radiated energy on the input lines, from adjacent lines, the 60 Hz power line, or other sources.

Common-Mode Rejection Ratio

Wanted signals appear on only one input or with opposite polarities on both input lines. These wanted signals are amplified and appear on the outputs as previously discussed. Unwanted signals (noise) appearing with the same polarity on both input lines are essentially cancelled by the diff-amp and do not appear on the outputs. The measure of an amplifier's ability to reject common-mode signals is a parameter called the **common-mode rejection ratio (CMRR)**.

Ideally, a differential amplifier provides a very high gain for desired signals (single-ended or differential) and zero gain for common-mode signals. Practical diff-amps, however, do exhibit a very small common-mode gain (usually much less than 1), while providing a high differential voltage gain (usually several thousand). The higher the differential gain with respect to the common-mode gain, the better the performance of the diff-amp in terms of rejection of common-mode signals. This suggests that a good measure of the diff-amp's performance in rejecting unwanted common-mode signals is the ratio of the differential gain $A_{v(d)}$ to the common-mode gain, A_{cm} . This ratio is the common-mode rejection ratio, CMRR.

$$\text{CMRR} = \frac{A_{v(d)}}{A_{cm}} \quad (6-1)$$

The higher the CMRR, the better. A very high value of CMRR means that the differential gain $A_{v(d)}$ is high and the common-mode gain A_{cm} is low.

The CMRR is often expressed in decibels (dB) as

$$\text{CMRR}' = 20 \log \left(\frac{A_{v(d)}}{A_{cm}} \right) \quad (6-2)$$

EXAMPLE 6-1

A certain diff-amp has a differential voltage gain of 2000 and a common-mode gain of 0.2. Determine the CMRR and express it in decibels.

SOLUTION

$A_{v(d)} = 2000$, and $A_{cm} = 0.2$. Therefore,

$$\text{CMRR} = \frac{A_{v(d)}}{A_{cm}} = \frac{2000}{0.2} = \mathbf{10,000}$$

Expressed in dB,

$$\text{CMRR}' = 20 \log(10,000) = \mathbf{80 \text{ dB}}$$

PRACTICE EXERCISE*

Determine the CMRR and express it in dB for an amplifier with a differential voltage gain of 8500 and a common-mode gain of 0.25.

*Answers are at the end of the chapter.

A CMRR of 10,000, for example, means that the desired input signal (differential) is amplified 10,000 times more than the unwanted noise (common-mode). So, as an example, if the amplitudes of the differential input signal and the common-mode noise are equal, the desired signal will appear on the output 10,000 times greater in amplitude than the noise. Thus, the noise or interference has been essentially eliminated.

Example 6-2 illustrates further the idea of common-mode rejection and the general signal operation of the differential amplifier.

EXAMPLE 6-2

The differential amplifier shown in Figure 6-9 has a differential voltage gain of 2500 and a CMRR of 30,000. In part (a), a single-ended input signal of $500\ \mu\text{V}$ rms is applied. At the same time, a 1 V, 60 Hz common-mode interference signal appears on both inputs as a result of radiated pick-up from the ac power system. In part (b), differential input signals of $500\ \mu\text{V}$ rms each are applied to the inputs. The common-mode interference is the same as in part (a).

- Determine the common-mode gain.
- Express the CMRR in dB.
- Determine the rms output signal for Figure 6-9(a) and (b).
- Determine the rms interference voltage on the output.

 


FIGURE 6-9

SOLUTION

- (a) $\text{CMRR} = \frac{A_{v(d)}}{A_{cm}}$. Therefore,

$$A_{cm} = \frac{A_{v(d)}}{\text{CMRR}} = \frac{2500}{30,000} = \mathbf{0.083}$$

- (b) $\text{CMRR}' = 20 \log(30,000) = \mathbf{89.5\ \text{dB}}$

- (c) In Figure 6-9(a), the differential input voltage is the difference between the voltage on input 1 and that on input 2. Since input 2 is grounded, its voltage is zero. Therefore,

$$V_{in(d)} = V_{in1} - V_{in2} = 500\ \mu\text{V} - 0\ \text{V} = 500\ \mu\text{V}$$

The output signal voltage in this case is taken at output 1.

$$V_{out1} = A_{v(d)}V_{in(d)} = (2500)(500\ \mu\text{V}) = \mathbf{1.25\ \text{V rms}}$$

In Figure 6-9(b), the differential input voltage is the difference between the two opposite-polarity, $500\ \mu\text{V}$ signals.

$$V_{in(d)} = V_{in1} - V_{in2} = 500\ \mu\text{V} - (-500\ \mu\text{V}) = 1000\ \mu\text{V} = 1\ \text{mV}$$

The output voltage signal is

$$V_{out1} = A_{v(d)}V_{in(d)} = (2500)(1\ \text{mV}) = \mathbf{2.5\ \text{V rms}}$$

This shows that a differential input (two opposite-polarity signals) results in a gain that is double that for a single-ended input.

- (d) The common-mode input is 1 V rms. The common-mode gain A_{cm} is 0.083. The interference (common-mode) voltage on the output is, therefore,

$$A_{cm} = \frac{V_{out(cm)}}{V_{in(cm)}}$$

$$V_{out(cm)} = A_{cm}V_{in(cm)} = (0.083)(1 \text{ V}) = \mathbf{0.083 \text{ V}}$$

PRACTICE EXERCISE

The amplifier in Figure 6–9 has a differential voltage gain of 4200 and a CMRR of 25,000. For the same single-ended and differential input signals as described in the example: (a) Find A_{cm} . (b) Express the CMRR in dB. (c) Determine the rms output signal for parts (a) and (b) of the figure. (d) Determine the rms interference (common-mode) voltage appearing on the output.

Internal Block Diagram of an Op-Amp

A typical op-amp is made up of three types of amplifier circuits: a *differential amplifier*, a *voltage amplifier*, and a *push-pull amplifier*, as shown in Figure 6–10.

 


FIGURE 6–10 Basic internal arrangement of an op-amp.

A differential amplifier is the input stage for the op-amp; it has two inputs and provides amplification of the difference voltage between the two inputs. The voltage amplifier is usually a class A amplifier that provides additional op-amp gain. Some op-amps may have more than one voltage amplifier stage. A push-pull class B amplifier is used for the output stage.

SECTION 6–2 CHECKUP

1. Distinguish between differential and single-ended inputs.
2. Define *common-mode rejection*.
3. For a given value of differential gain, does a higher CMRR result in a higher or lower common-mode gain?

6-3 OP-AMP DATA SHEET PARAMETERS

In this section, several important op-amp parameters are defined. (These are listed in the objectives that follow.) Also several IC op-amps are compared in terms of these parameters.

After completing this section, you should be able to

- Discuss several op-amp parameters
 - Define *input offset voltage*
 - Discuss *input offset voltage drift with temperature*
 - Define *input bias current*
 - Define *input impedance*
 - Define *input offset current*
 - Define *output impedance*
 - Discuss *common-mode input voltage range*
 - Discuss *open-loop voltage gain*
 - Define *common-mode rejection ratio*
 - Define *slew rate*
 - Discuss *frequency response*
 - Compare the parameters of several types of IC op-amps

Input Offset Voltage


The ideal op-amp produces zero volts out for zero volts in. In a practical op-amp, however, a small dc voltage, $V_{OUT(error)}$, appears at the output when no differential input voltage is applied. Its primary cause is a slight mismatch of the base-emitter voltages of the differential input stage of an op-amp, as illustrated in Figure 6-11(a).

The output voltage of the differential input stage is expressed as

$$V_{OUT(error)} = I_{C2}R_C - I_{C1}R_C$$

A small difference in the base-emitter voltages of Q_1 and Q_2 causes a small difference in the collector currents. This results in a nonzero value of V_{OUT} , which is the error voltage. (The collector resistors are equal.)

 As specified on an op-amp data sheet, the **input offset voltage** (V_{OS}) is the differential dc voltage required between the inputs to force the differential output to zero volts. V_{OS} is



(a) A V_{BE} mismatch (V_{BE1} different than V_{BE2}) causes a small output error voltage.

(b) The input offset voltage is the difference in the voltage between the inputs that is necessary to eliminate the output error voltage (makes $V_{OUT} = 0$).

FIGURE 6-11 Illustration of input offset voltage, V_{OS} .

demonstrated in Figure 6–11(b). Typical values of input offset voltage are in the range of 2 mV or less. In the ideal case, it is 0 V.

Input Offset Voltage Drift with Temperature

The **input offset voltage drift** is a parameter related to V_{OS} that specifies how much change occurs in the input offset voltage for each degree change in temperature. Typical values range anywhere from about $5\ \mu\text{V}$ per degree Celsius to about $50\ \mu\text{V}$ per degree Celsius. Usually, an op-amp with a higher nominal value of input offset voltage exhibits a higher drift.

Input Bias Current

You have seen that the input terminals of a bipolar differential amplifier are the transistor bases and, therefore, the input currents are the base currents.

The **input bias current** is the dc current required by the inputs of the amplifier to properly operate the first stage. By definition, the input bias current is the *average* of both input currents and is calculated as follows:

$$I_{\text{BIAS}} = \frac{I_1 + I_2}{2}$$

The concept of input bias current is illustrated in Figure 6–12.

 


FIGURE 6–12 Input bias current is the average of the two op-amp input currents.

Input Impedance

Two basic ways of specifying the input impedance of an op-amp are the differential and the common mode. The **differential input impedance** is the total resistance between the inverting and the noninverting inputs, as illustrated in Figure 6–13(a). Differential input impedance is measured by determining the change in bias current for a given change in differential input voltage. The **common-mode input impedance** is the resistance between each input and ground and is measured by determining the change in bias current for a given change in common-mode input voltage. It is depicted in Figure 6–13(b).

 


FIGURE 6–13 Op-amp input impedance.

Input Offset Current

Ideally, the two input bias currents are equal, and thus their difference is zero. In a practical op-amp, however, the bias currents are not exactly equal.

The **input offset current**, I_{OS} , is the difference of the input bias currents, expressed as an absolute value.

$$I_{OS} = |I_1 - I_2|$$

Actual magnitudes of offset current are usually at least an order of magnitude (ten times) less than the bias current. In many applications, the offset current can be neglected. However, high-gain, high-input impedance amplifiers should have as little I_{OS} as possible because the difference in currents through large input resistances develops a substantial offset voltage, as shown in Figure 6-14.

The offset voltage developed by the input offset current is

$$V_{OS} = |I_1 - I_2|R_{in} = I_{OS}R_{in}$$

 


FIGURE 6-14 Effect of input offset current.

The error created by I_{OS} is amplified by the gain A_v of the op-amp and appears in the output as

$$V_{OUT(error)} = A_v I_{OS} R_{in}$$

A change in offset current with temperature affects the error voltage. Values of temperature coefficient for the offset current in the range of 0.5 nA per degree Celsius are common.

Output Impedance

Output impedance is the resistance viewed from the output terminal of the op-amp, as indicated in Figure 6-15.

 


FIGURE 6-15 Op-amp output impedance.

Common-Mode Input Voltage Range

All op-amps have limitations on the range of voltages over which they will operate. The **common-mode input voltage range** is the range of input voltages which, when applied to both inputs, will not cause clipping or other output distortion. Many op-amps have common-mode ranges of no more than ± 10 V with dc supply voltages of ± 15 V, while in others the output can go as high as the supply voltages (this is called rail-to-rail).

Open-Loop Voltage Gain

The **open-loop voltage gain**, A_{ol} , of an op-amp is the internal voltage gain of the device and represents the ratio of output voltage to input voltage when there are no external components. The open-loop voltage gain is set entirely by the internal design. Open-loop voltage gain of over 200,000 are common but is *not a well-controlled parameter*. Data sheets often refer to the open-loop voltage gain as the *large-signal voltage gain*.

Common-Mode Rejection Ratio for an Op-Amp

The *common-mode rejection ratio* (CMRR) was discussed in conjunction with the diff-amp. Similarly, for an op-amp, CMRR is a measure of an op-amp's ability to reject common-mode signals. An infinite value of CMRR means that the output is zero when the same signal is applied to both inputs (common-mode).

An infinite CMRR is never achieved in practice, but a good op-amp does have a very high value of CMRR. As previously mentioned, common-mode signals are undesired interference voltages such as 60 Hz power-supply ripple and noise voltages due to pick-up of radiated energy. A high CMRR enables the op-amp to virtually eliminate these interference signals from the output.

The accepted definition of CMRR for an op-amp is the open-loop voltage gain (A_{ol}) divided by the common-mode gain.

$$\text{CMRR} = \frac{A_{ol}}{A_{cm}} \quad (6-3)$$

It is commonly expressed in decibels as follows:

$$\text{CMRR}' = 20 \log \left(\frac{A_{ol}}{A_{cm}} \right) \quad (6-4)$$

EXAMPLE 6-3

A certain op-amp has an open-loop voltage gain of 100,000 and a common-mode gain of 0.25. Determine the CMRR and express it in decibels.

SOLUTION

$$\begin{aligned} \text{CMRR} &= \frac{A_{ol}}{A_{cm}} = \frac{100,000}{0.25} = \mathbf{400,000} \\ \text{CMRR}' &= 20 \log(400,000) = \mathbf{112 \text{ dB}} \end{aligned}$$

PRACTICE EXERCISE

If a particular op-amp has a CMRR' of 90 dB and a common-mode gain of 0.4, what is the open-loop voltage gain?

Slew Rate

The maximum rate of change of the output voltage in response to a step input voltage is the **slew rate** of an op-amp. The slew rate is dependent upon the high-frequency response of the amplifier stages within the op-amp.

Slew rate is measured with an op-amp connected as shown in Figure 6-16(a). This particular op-amp connection is a unity-gain, noninverting configuration, which will be discussed later. It gives a worst-case (slowest) slew rate. Recall that the high-frequency components of a voltage step are contained in the rising edge and that the upper critical frequency of an amplifier limits its response to a step input. The lower the upper critical frequency is, the more gradual the slope on the output for a step input.

 


FIGURE 6-16 Slew rate measurement.

A pulse is applied to the input as shown in Figure 6-16(b), and the ideal output voltage is measured as indicated. The width of the input pulse must be sufficient to allow the output to “slew” from its lower limit to its upper limit, as shown. As you can see, a certain time interval, Δt , is required for the output voltage to go from its lower limit $-V_{max}$ to its upper limit $+V_{max}$ once the input step is applied. The slew rate is expressed as

$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t} \quad (6-5)$$

where $\Delta V_{out} = +V_{max} - (-V_{max})$. The unit of slew rate is volts per microsecond ($\text{V}/\mu\text{s}$).

EXAMPLE 6-4

The output voltage of a certain op-amp appears as shown in Figure 6-17 in response to a step input. Determine the slew rate.

 


FIGURE 6-17

SOLUTION

The output goes from the lower to the upper limit in $1 \mu\text{s}$. Since this response is not ideal, the limits are taken at the 90% points, as indicated. So the upper limit is $+9 \text{ V}$ and the lower limit is -9 V . The slew rate is

$$\text{Slew rate} = \frac{\Delta V}{\Delta t} = \frac{+9 \text{ V} - (-9 \text{ V})}{1 \mu\text{s}} = 18 \text{ V}/\mu\text{s}$$

PRACTICE EXERCISE

When a pulse is applied to an op-amp, the output voltage goes from -8 V to $+7 \text{ V}$ in $0.75 \mu\text{s}$. What is the slew rate?

Frequency Response

The internal amplifier stages that make up an op-amp have voltage gains limited by junction capacitances. Although the differential amplifiers used in op-amps are somewhat different from the basic amplifiers discussed, the same principles apply. An op-amp has no internal coupling capacitors, however; therefore, the low-frequency response extends down to dc (0 Hz). Frequency-related characteristics of op-amps will be discussed in the next chapter.

Comparison of Op-Amp Parameters

Table 6–1 provides a comparison of values of some of the parameters just described for several common IC op-amps. As you can see from the table, there is a wide difference in certain specifications. All system designs involve certain compromises, so in order for designers to optimize one parameter, they must often sacrifice another parameter. Choosing an op-amp for a particular application depends on which parameters are most important. For details on any of these parameters, refer to the data sheet for the device.

TABLE 6–1

OP-AMP	CMRR (dB) (TYP)	OPEN-LOOP GAIN (dB) (TYP)	GAIN-BANDWIDTH PRODUCT (MHz) (TYP)	INPUT OFFSET VOLTAGE (mV) (MAX)	INPUT BIAS CURRENT (nA) (MAX)	SLEW RATE (V/ μ s) (TYP)	COMMENT
AD8009	50	N/A	320 ¹	5	150	5500	Extremely fast, low distortion, uses current feedback
AD8055	82	71		5	1200	1400	Low noise; fast, wide bandwidth; gain flatness 0.1 dB; video driver
ADA4891	68	90 ²		2500	0.002	170	CMOS—extremely low bias current, very fast, useful as video amplifier
ADA4092	85	118	1.3	0.2	50	0.4	Single-supply (2.7 V to 36 V) or two-supply operation, low power
FAN4931	73	102	4	6	0.005	3	Low-cost CMOS, low power, output swings to within 10 mV of rail, extremely high input resistance
FHP3130	95	100	60	1	1800	110	High current output (to 100 mA)
FHP3350	90	55	190	1	50	800	High speed; useful as video amp
LM741C	70	106	1	6	500	0.5	General-purpose, overload protection, industry standard
LM7171	110	90	100	1.5	1000	3600	Very fast, high CMRR, useful as an instrumentation amplifier
LMH6629	87	79	800 ³	0.15	23000	530	Fast, ultra-low noise, low voltage
OP177	130	142		0.01	1.5	0.3	Ultra-precise, very high CMRR and stability
OPA369	114	134	0.012	0.25	0.010	0.005	Extremely low power, low voltage, rail-to-rail.
OPA378	100	110	0.9	0.02	0.15	0.4	Precision, very low drift, low noise
OPA847	110	98	3900	0.1	42,000	950	Ultra-low noise, wide bandwidth amplifier, voltage feedback

¹Depends on gain; gain = 10 is shown

²Depends on gain; gain = 2 is shown


³Small signal

Other Features

Most available op-amps have three important features: short-circuit protection, no latch-up, and input offset nulling. Short-circuit protection keeps the circuit from being damaged if the output becomes shorted, and the no latch-up feature prevents the op-amp from hanging up in one output state (high or low voltage level) under certain input conditions. Input offset nulling is achieved by an external potentiometer that sets the output voltage at precisely zero with zero input.

Switched capacitor circuits were discussed in Chapter 4. (Refer to Figure 4-60.) The switched capacitor acts like a resistor and when combined with an op-amp can operate at very low voltage. One interesting application for an op-amp switched-capacitor system is in pacemakers. A new design uses a CMOS switched-opamp switched-capacitor (SO-SC) preamplifier with a gain of 40 dB. The circuit includes an SO-SC filter. The key advantage combining an op-amp with switched capacitors for patients is that the circuit can use a very low supply voltage and will dissipate extremely low power. The entire system runs on a supply voltage of 0.8 V and consumes only 420 nW, an important advantage to patients using pacemakers.

SYSTEM NOTE

 

SECTION 6-3 CHECKUP

1. List ten or more op-amp parameters.
2. Which two parameters, not including frequency response, are frequency dependent?

6-4 NEGATIVE FEEDBACK

Negative feedback is one of the most useful concepts in electronics, particularly in op-amp applications. Negative feedback is the process whereby a portion of the output voltage of an amplifier is returned to the input with a phase angle that opposes (or subtracts from) the input signal.

After completing this section, you should be able to

- Explain negative feedback in op-amp circuits
- Describe the effects of negative feedback
- Discuss why negative feedback is used

Negative feedback is illustrated in Figure 6-18. The inverting ($-$) input effectively makes the feedback signal 180° out of phase with the input signal. The op-amp has extremely high gain and amplifies the *difference* in the signals applied to the inverting and noninverting inputs. A very tiny difference in these two signals is all the op-amp needs to produce the required output. *When negative feedback is present, the noninverting and inverting inputs are nearly identical.* This concept can help you figure out what signal to expect in many op-amp circuits.

Now let's review how negative feedback works and why the signals at the inverting and noninverting terminals are nearly identical when negative feedback is used. Assume a 1.0 V input signal is applied to the noninverting terminal and the open-loop gain of the op-amp is 100,000. The amplifier responds to the voltage at its noninverting input terminal and moves the output

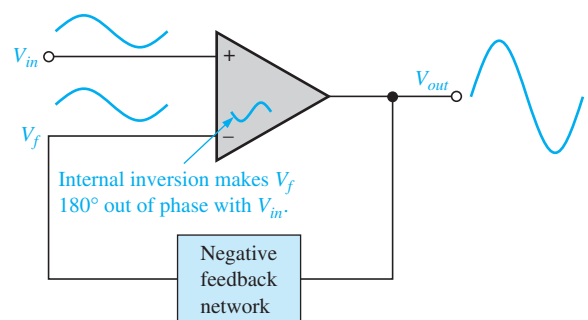


FIGURE 6-18 Illustration of negative feedback.

toward saturation. Immediately, a fraction of this output is returned to the inverting terminal through the feedback path. But if the feedback signal ever reaches 1.0 V, there is nothing left for the op-amp to amplify! Thus, the feedback signal tries (but never quite succeeds) in matching the input signal. The gain is controlled by the amount of feedback used. When you are troubleshooting an op-amp circuit with negative feedback present, remember that the two inputs will look identical on a scope but in fact are very slightly different.

Now suppose something happens that reduces the internal gain of the op-amp. This causes the output signal to drop a small amount, returning a smaller signal to the inverting input via the feedback path. This means the difference between the signals is larger than it was. The output increases, compensating for the original drop in gain. The net change in the output is so small, it can hardly be measured. The main point is that any variation in the amplifier is immediately compensated for by the negative feedback, resulting in a very stable, predictable output.

Why Use Negative Feedback?

As you have seen, the inherent open-loop gain of a typical op-amp is very high (usually greater than 100,000). Therefore, an extremely small difference in the two input voltages drives the op-amp into its saturated output states. In fact, even the input offset voltage of the op-amp can drive it into saturation. For example, assume $V_{in} = 1 \text{ mV}$ and $A_{ol} = 100,000$. Then,

$$V_{in}A_{ol} = (1 \text{ mV})(100,000) = 100 \text{ V}$$

Since the output level of an op-amp can never reach 100 V, it is driven into saturation and the output is limited to its maximum output levels, as illustrated in Figure 6–19 for both a positive and a negative input voltage of 1 mV.

 


FIGURE 6–19 Without negative feedback, an extremely small difference in the two input voltages drives the op-amp to its output limits and it becomes nonlinear.

The usefulness of an op-amp operated in this manner is severely restricted and is generally limited to comparator applications (to be studied in Chapter 8). With negative feedback, the overall closed-loop voltage gain (A_{cl}) can be reduced and controlled so that the op-amp can function as a linear amplifier. In addition to providing a controlled, stable voltage gain, negative feedback also provides for control of the input and output impedances and amplifier bandwidth. Table 6–2 summarizes the general effects of negative feedback on op-amp performance.


TABLE 6–2

	VOLTAGE GAIN	INPUT Z	OUTPUT Z	BANDWIDTH
Without negative feedback	A_{ol} is too high for linear amplifier applications	Relatively high (see Table 6–1)	Relatively low	Relatively narrow (because the gain is so high)
With negative feedback	A_{cl} is set to desired value by the feedback network	Can be increased or reduced to a desired value depending on type of circuit	Can be reduced to a desired value	Significantly wider

Op-amps can be used in some RF systems; of course, the op-amps must be very high-speed devices. There are several advantages, and one primary disadvantage to replacing traditional discrete components with op-amps in RF circuits. The major disadvantage is the cost. A transistor that costs a few pennies is being replaced with an IC that may cost several dollars. This may not be practical in mass produced products, but for high-performance RF equipment, op-amps make sense.

Designing with op-amps provides more flexibility than with discrete devices. When discrete transistors are used, the bias and operating point of the device can affect the gain and tuning of the amplifier stage. To bias an op-amp you simply connect the appropriate power supply voltages. The bias does not affect the gain or the tuning of the stage. Op-amps are also more thermally stable and reduce “drift” over the operating temperature range of the system.

SYSTEM NOTE

 

SECTION 6-4 CHECKUP

1. What are the benefits of negative feedback in an op-amp circuit?
2. Why is it necessary to reduce the gain of an op-amp from its open-loop value?
3. When troubleshooting an op-amp circuit in which negative feedback is present, what do you expect to observe on the input terminals?

6-5 OP-AMP CONFIGURATIONS WITH NEGATIVE FEEDBACK

In this section, we will discuss three basic ways in which an op-amp can be connected using negative feedback to stabilize the gain and increase frequency response. As mentioned, the extremely high open-loop gain of an op-amp creates an unstable situation because a small noise voltage on the input can be amplified to a point where the amplifier is driven out of its linear region. Also, unwanted oscillations can occur. In addition, the open-loop gain parameter of an op-amp can vary greatly from one device to the next. Negative feedback takes a portion of the output and applies it back out of phase with the input, creating an effective reduction in gain. This closed-loop gain is usually much less than the open-loop gain and independent of it.

After completing this section, you should be able to

- Analyze three op-amp configurations
 - Identify the noninverting amplifier configuration
 - Determine the voltage gain of a noninverting amplifier
 - Identify the voltage-follower configuration
 - Identify the inverting amplifier configuration
 - Determine the voltage gain of an inverting amplifier

Closed-Loop Voltage Gain, A_{cl}


The **closed-loop voltage gain** is the voltage gain of an op-amp with negative feedback. The amplifier configuration consists of the op-amp and an external feedback network that connects the output to the inverting input. The closed-loop voltage gain is then determined by the component values in the feedback network and can be precisely controlled by them.

Noninverting Amplifier

An op-amp connected in a closed-loop configuration as a **noninverting amplifier** is shown in Figure 6–20. The input signal is applied to the noninverting (+) input. A portion of the output is applied back to the inverting (–) input through the feedback network. This constitutes negative feedback. The feedback fraction, B , is the portion of the output returned to the inverting input and determines the gain of the amplifier as you will see. This smaller feedback voltage, V_f , can be written

$$V_f = BV_{out}$$

FIGURE 6–20 Noninverting amplifier.

 

The differential voltage, V_{diff} , between the op-amp's input terminals is illustrated in Figure 6–21 and can be expressed as

$$V_{diff} = V_{in} - V_f$$

This input differential voltage is forced to be very small as a result of the negative feedback and the high open-loop gain, A_{ol} . Therefore, a close approximation is

$$V_{in} \cong V_f$$

By substitution,

$$V_{in} \cong BV_{out}$$


Rearranging,

$$\frac{V_{out}}{V_{in}} \cong \frac{1}{B}$$

The ratio of the output voltage to the input voltage is the closed-loop gain. This result shows that the closed-loop gain for the noninverting amplifier, $A_{cl(NI)}$, is approximately

$$A_{cl(NI)} = \frac{V_{out}}{V_{in}} \cong \frac{1}{B}$$

FIGURE 6–21 Differential input, $V_{in} - V_f$.

 

The feedback fraction is determined by R_i and R_f , which form a voltage-divider network. The fraction of the output voltage, V_{out} , that is returned to the inverting input is found by applying the voltage-divider rule to the feedback network.

$$V_{in} \cong BV_{out} \cong \left(\frac{R_i}{R_i + R_f} \right) V_{out}$$

Rearranging,

$$\frac{V_{out}}{V_{in}} = \left(\frac{R_i + R_f}{R_i} \right)$$

which can be expressed as follows:

$$A_{cl(NI)} = \frac{R_f}{R_i} + 1 \quad (6-6)$$

Equation (6-6) shows that the closed-loop voltage gain, $A_{cl(NI)}$, of the noninverting (NI) amplifier is not dependent on the op-amp's open-loop gain but can be set by selecting values of R_i and R_f . This equation is based on the assumption that the open-loop gain is very high compared to the ratio of the feedback resistors, causing the input differential voltage, V_{diff} , to be very small. In nearly all practical circuits, this is an excellent assumption.

For those rare cases where a more exact equation is necessary, the output voltage can be expressed as

$$V_{out} = V_{in} \left(\frac{A_{ol}}{1 + A_{ol}B} \right)$$

The following formula gives the exact solution of the closed-loop gain:

$$A_{cl(NI)} = \frac{V_{out}}{V_{in}} = \left(\frac{A_{ol}}{1 + A_{ol}B} \right)$$

EXAMPLE 6-5

Determine the closed-loop voltage gain of the amplifier in Figure 6-22.

 


FIGURE 6-22

SOLUTION

This is a noninverting op-amp configuration. Therefore, the closed-loop voltage gain is

$$A_{cl(NI)} = \frac{R_f}{R_i} + 1 = \frac{100 \text{ k}\Omega}{4.7 \text{ k}\Omega} + 1 = 22.3$$

PRACTICE EXERCISE

If R_f in Figure 6-22 is increased to 150 kΩ, determine the closed-loop gain.

MULTISIM



Open file F06-22 found on the companion website. This simulation demonstrates the effect that load resistance has on the closed-loop voltage gain of the noninverting amplifier.

VOLTAGE-FOLLOWER The **voltage-follower** configuration is a special case of the noninverting amplifier where all of the output voltage is fed back to the inverting input by a straight connection, as shown in Figure 6-23. As you can see, the straight feedback connection has a voltage gain of approximately 1. The closed-loop voltage gain of a noninverting amplifier is $1/B$ as previously derived. Since $B = 1$, the closed-loop gain of the voltage-follower is

$$A_{cl(VF)} = 1 \quad (6-7)$$

The most important features of the voltage-follower configuration are its very high input impedance and its very low output impedance. These features make it a nearly ideal buffer amplifier for interfacing high-impedance sources and low-impedance loads. This is discussed further in Section 6–6.

 


FIGURE 6–23 Op-amp voltage-follower.

Inverting Amplifier

An op-amp connected as an **inverting amplifier** with a controlled amount of voltage gain is shown in Figure 6–24. The input signal is applied through a series input resistor (R_i) to the inverting input. Also, the output is fed back through R_f to the inverting input. The noninverting input is grounded.

 


FIGURE 6–24 Inverting amplifier.

At this point, the ideal op-amp parameters mentioned earlier are useful in simplifying the analysis of this circuit. In particular, the concept of infinite input impedance is of great value. An infinite input impedance implies that there is *no* current out of the inverting input. If there is no current through the input impedance, then there must be *no* voltage drop between the inverting and noninverting inputs. This means that the voltage at the inverting (–) input is zero because the noninverting (+) input is grounded. This zero voltage at the inverting input terminal is referred to as *virtual ground*. This condition is illustrated in Figure 6–25(a).

Since there is no current at the inverting input, the current through R_i and the current through R_f are equal, as shown in Figure 6–25(b).

$$I_{in} = I_f$$

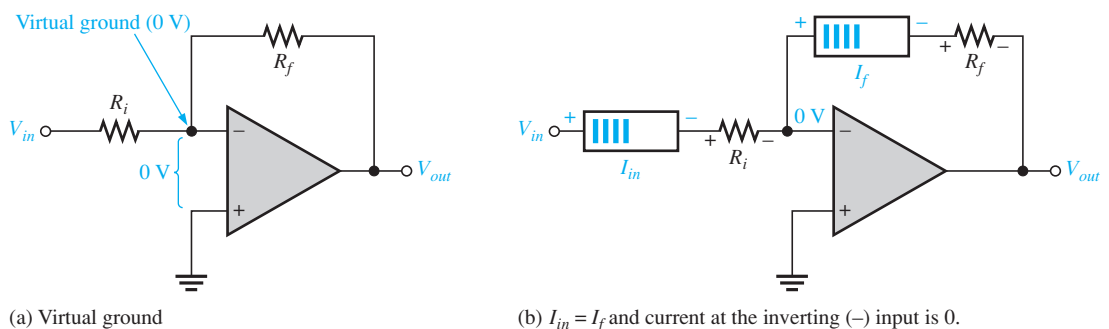


FIGURE 6–25 Virtual ground concept and closed-loop voltage gain development for the inverting amplifier.

The voltage across R_i equals V_{in} because of virtual ground on the other side of the resistor. Therefore,

$$I_{in} = \frac{V_{in}}{R_i}$$

Also, the voltage across R_f equals $-V_{out}$ because of virtual ground, and therefore

$$I_f = \frac{-V_{out}}{R_f}$$

Since $I_f = I_{in}$,

$$\frac{-V_{out}}{R_f} = \frac{V_{in}}{R_i}$$

Rearranging the terms,

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

Of course, V_{out}/V_{in} is the overall gain of the inverting amplifier.

$$A_{cl(I)} = -\frac{R_f}{R_i} \quad (6-8)$$

Equation (6-8) shows that the closed-loop voltage gain $A_{cl(I)}$ of the inverting amplifier is the ratio of the feedback resistance R_f to the input resistance R_i . *The closed-loop gain is independent of the op-amp's internal open-loop gain.* Thus, the negative feedback stabilizes the voltage gain. The negative sign indicates inversion.

EXAMPLE 6-6

Given the op-amp configuration in Figure 6-26, determine the value of R_f required to produce a closed-loop voltage gain of -100 .

 


FIGURE 6-26

SOLUTION

Knowing that $R_i = 2.2 \text{ k}\Omega$ and $A_{cl(I)} = -100$, calculate R_f as follows:

$$A_{cl(I)} = -\frac{R_f}{R_i}$$

$$R_f = -A_{cl(I)}R_i = -(-100)(2.2 \text{ k}\Omega) = \mathbf{220 \text{ k}\Omega}$$

PRACTICE EXERCISE


- If R_i is changed to $2.7 \text{ k}\Omega$ in Figure 6-26, what value of R_f is required to produce a closed-loop gain of -25 ?
- If R_f failed to open, what would you expect to see at the output?

MULTISIM



Open file F06-26 found on the companion website. This simulation demonstrates the effect of an open feedback resistor on the output of a noninverting amplifier.

SYSTEM EXAMPLE 6-1

 

A SPECTROPHOTOMETER SYSTEM

In medical laboratories, an instrument known as a spectrophotometer is used to analyze chemicals in solutions by determining how much absorption of light occurs over a range of wavelengths. An op-amp circuit is used to amplify the output of the photocell and send the signal to a processor and display instrument. Since every chemical and compound absorbs light in a different way, the output of the spectrophotometer can be used to accurately identify the contents of the solution. Spectrophotometry can also be used on transparent or opaque solids (such as glass) or on gases.

This type of system is common in medical laboratories as well as many other areas. It is an example of a mixed system in which electronic circuits interface with other types of systems, such as mechanical and optical, to accomplish a specific function. When you are a technician or technologist in industry, you will probably be working with different types of mixed systems from time to time.

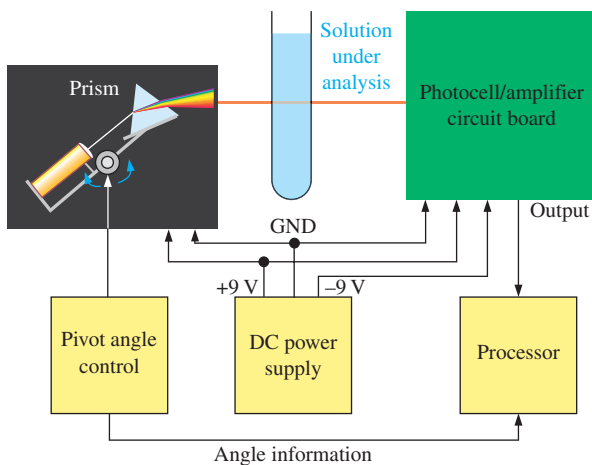


FIGURE SE6-1 A basic spectrophotometer system.

A Brief Description of the System

The light source shown in Figure SE6-1 produces a beam of visible light containing a wide spectrum of wavelengths. Each component wavelength in the beam of light is refracted at a different angle by the prism as indicated. Depending on the angle of the platform that is set by the pivot angle controller, a certain wavelength of light passes through a narrow slit and is projected through the solution under analysis. By precisely pivoting the light source and prism, a specific wavelength can be transmitted. Every chemical and compound absorbs different wavelengths of light in different ways, so the resulting light coming through the solution has a unique “signature” that can be used to define the chemicals in the solution.

The photocell produces a voltage that is proportional to the intensity of light and its wavelength. The op-amp circuit amplifies the photocell output and sends the resulting signal to the processing and display unit where the type of chemical(s)

in the solution is identified. The focus of this system example is the photocell/amplifier circuit board. The PCB layout for this circuit is shown in Figure SE6-2.

 


FIGURE SE6-2 Photocell/amplifier PCB layout.

The pin layout for the LM741 op-amp can be determined from the data sheet. If you carefully follow the PCB traces you will see that this is an inverting amplifier. This op-amp is housed in a surface-mount SO-8 package. Note that there are two interconnecting traces on the reverse side of the board indicated by the darker traces. A pad to which no component lead is connected represents a feed-through to the other side of the board. The potentiometer is used to calibrate the system using a reference solution.

The system light source produces wavelengths ranging from 400 nm to 700 nm, which is approximately the full range of visible light from violet to red. Refer to the photocell response characteristic curve in Figure SE6-3. The processing circuitry uses the amplified signal from the photocell, and information from the pivot-angle controller, to identify the type of solution under test.

 


FIGURE SE6-3 Photocell response curve.

SECTION 6-5 CHECKUP

1. What is the main purpose of negative feedback?
2. The closed-loop voltage gain of each of the op-amp configurations discussed is dependent on the internal open-loop voltage gain of the op-amp. (True or False)
3. The attenuation of the negative feedback network of a noninverting op-amp configuration is 0.02. What is the closed-loop gain of the amplifier?
4. Refer to the pc board in Figure SE6-2, If the 100 k Ω potentiometer is set to the middle, what is the gain?

6-6 OP-AMP IMPEDANCES AND NOISE

In this section, you will see how a negative feedback connection affects the input and output impedances of an op-amp. The effects on both inverting and noninverting amplifiers are examined.

After completing this section, you should be able to

- Describe impedances of the three op-amp configurations
- Determine input and output impedances of a noninverting amplifier
- Determine input and output impedances of a voltage-follower
- Determine input and output impedances of an inverting amplifier

Input Impedance of the Noninverting Amplifier

Recall that negative feedback causes the feedback voltage, V_f , to nearly equal the input voltage, V_{in} . The difference between the input and feedback voltage, V_{diff} , is approximately zero, and ideally, can be assumed to have this value. This assumption implies that the input signal current to the op-amp is also zero. Since the input impedance is the ratio of input voltage to input current, the input impedance of a noninverting amplifier is

$$Z_{in} = \frac{V_{in}}{I_{in}} \cong \frac{V_{in}}{0} = \text{infinity } (\infty)$$

For many practical circuits, this assumption is good for obtaining a basic idea of the operation. A more exact analysis takes into account the fact that the input signal current is not zero.

The exact input impedance of this op-amp configuration is developed with the aid of Figure 6–27. For this analysis, a small differential voltage, V_{diff} , is assumed to exist between the two inputs, as indicated. This means that you cannot assume the op-amp's input impedance to be infinite or the input current to be zero. The input voltage can be expressed as

 


FIGURE 6–27

Substituting BV_{out} for V_f ,

$$V_{in} = V_{diff} + BV_{out}$$

Since $V_{out} \cong A_{ol}V_{diff}$ (A_{ol} is the open-loop gain of the op-amp),

$$V_{in} = V_{diff} + A_{ol}BV_{diff} = (1 + A_{ol}B)V_{diff}$$

Because $V_{diff} = I_{in}Z_{in}$,

$$V_{in} = (1 + A_{ol}B)I_{in}Z_{in}$$

where Z_{in} is the open-loop input impedance of the op-amp (without feedback connections).

$$\frac{V_{in}}{I_{in}} = (1 + A_{ol}B)Z_{in}$$

V_{in}/I_{in} is the overall input impedance of the closed-loop noninverting configuration.

$$Z_{in(NI)} = (1 + A_{ol}B)Z_{in} \quad (6-9)$$

This equation shows that the input impedance of this amplifier configuration with negative feedback is much greater than the internal input impedance of the op-amp itself (without feedback).

Output Impedance of the Noninverting Amplifier

In addition to the input impedance, negative feedback also produces an advantage for the output impedance of an op-amp. The output impedance of an amplifier without feedback is relatively low. With feedback, the output impedance is even lower. For many applications,

the assumption that the output impedance with feedback is zero will produce sufficient accuracy. That is,

$$Z_{out(NI)} \cong 0$$

An exact analysis to find the output impedance with feedback is developed with the aid of Figure 6-28. By applying Kirchhoff's law to the output circuit,

$$V_{out} = A_{ol}V_{diff} - Z_{out}I_{out}$$

The differential input voltage is $V_{in} - V_f$; so, by assuming that $A_{ol}V_{diff} \gg Z_{out}I_{out}$, the output voltage can be expressed as

$$V_{out} \cong A_{ol}(V_{in} - V_f)$$

Substituting BV_{out} for V_f ,

$$V_{out} \cong A_{ol}(V_{in} - BV_{out})$$

Remember, B is the attenuation of the negative feedback network. Expanding, factoring, and rearranging terms,

$$A_{ol}V_{in} \cong V_{out} + A_{ol}BV_{out} = (1 + A_{ol}B)V_{out}$$

Since the output impedance of the noninverting configuration is $Z_{out(NI)} = V_{out}/I_{out}$, you can substitute $I_{out}Z_{out(NI)}$ for V_{out} ; therefore,

$$A_{ol}V_{in} = (1 + A_{ol}B)I_{out}Z_{out(NI)}$$

Dividing both sides of the above expression by I_{out} yields

$$\frac{A_{ol}V_{in}}{I_{out}} = (1 + A_{ol}B)Z_{out(NI)}$$

The term on the left is the internal output impedance of the op-amp (Z_{out}) because, without feedback, $A_{ol}V_{in} = V_{out}$. Therefore,

$$Z_{out} = (1 + A_{ol}B)Z_{out(NI)}$$

 


FIGURE 6-28

Thus,


$$Z_{out(NI)} = \frac{Z_{out}}{1 + A_{ol}B} \quad (6-10)$$

This equation shows that the output impedance of this amplifier configuration with negative feedback is much less than the internal output impedance of the op-amp itself (without feedback) because it is divided by the factor $1 + A_{ol}B$.

EXAMPLE 6-7

- Determine the input and output impedances of the amplifier in Figure 6-29. The op-amp data sheet gives $Z_{in} = 2 \text{ M}\Omega$, $Z_{out} = 75 \text{ }\Omega$, and $A_{ol} = 200,000$.
- Find the closed-loop voltage gain.

FIGURE 6–29

 **SOLUTION**

(a) The attenuation, B , of the feedback network is

$$B = \frac{R_i}{R_i + R_f} = \frac{10 \text{ k}\Omega}{230 \text{ k}\Omega} = 0.0435$$

$$\begin{aligned} Z_{in(\text{NI})} &= (1 + A_{ol}B)Z_{in} = [1 + (200,000)(0.0435)](2 \text{ M}\Omega) \\ &= (1 + 8700)(2 \text{ M}\Omega) = 17,402 \text{ M}\Omega = \mathbf{17.4 \text{ G}\Omega} \end{aligned}$$

$$Z_{out(\text{NI})} = \frac{Z_{out}}{1 + A_{ol}B} = \frac{75 \Omega}{1 + 8700} = 0.0086 \Omega = \mathbf{8.6 \text{ m}\Omega}$$

(b) $A_{cl(\text{NI})} = \frac{1}{B} = \frac{1}{0.0435} \cong \mathbf{23}$

PRACTICE EXERCISE

(a) Determine the input and output impedances in Figure 6–29 for op-amp data sheet values of $Z_{in} = 3.5 \text{ M}\Omega$, $Z_{out} = 82 \Omega$, and $A_{ol} = 135,000$.

(b) Find A_{cl} .

Voltage-Follower Impedances

Since the voltage-follower is a special case of the noninverting configuration, the same impedance formulas are used with $B = 1$.

$$Z_{in(\text{VF})} = (1 + A_{ol})Z_{in} \quad (6-11)$$

$$Z_{out(\text{VF})} = \frac{Z_{out}}{1 + A_{ol}} \quad (6-12)$$

As you can see, the voltage-follower input impedance is greater for a given A_{ol} and Z_{in} than for the noninverting configuration with the voltage-divider feedback network. Also, its output impedance is much smaller because B is normally much smaller than 1 for a noninverting configuration.

EXAMPLE 6–8

The same op-amp as in Example 6–7 is used in a voltage-follower configuration. Determine the input and output impedances.

SOLUTION

Since $B = 1$,

$$Z_{in(\text{VF})} = (1 + A_{ol})Z_{in} = (1 + 200,000)(2 \text{ M}\Omega) = \mathbf{400 \text{ G}\Omega}$$

$$Z_{out(\text{VF})} = \frac{Z_{out}}{1 + A_{ol}} = \frac{75 \Omega}{1 + 200,000} = \mathbf{375 \mu\Omega}$$

Notice that $Z_{in(VF)}$ is much greater than $Z_{in(NI)}$, and $Z_{out(VF)}$ is much less than $Z_{out(NI)}$ from Example 6-7.

PRACTICE EXERCISE

If the op-amp in this example is replaced with one having a higher open-loop gain, how are the input and output impedances affected?

Impedances of the Inverting Amplifier

The input and output impedances of the inverting amplifier are developed with the aid of Figure 6-30. Both the input signal and the negative feedback are applied, through resistors, to the inverting terminal as shown.

 


FIGURE 6-30 Inverting amplifier.

INPUT IMPEDANCE The input impedance for the inverting amplifier is

$$Z_{in(I)} \cong R_i \quad (6-13)$$

This is because the inverting input of the op-amp is at virtual ground (0 V) and the input source simply sees R_i to ground, as shown in Figure 6-31.

 


FIGURE 6-31

OUTPUT IMPEDANCE As with the noninverting amplifier, the output impedance of the inverting amplifier is decreased by the negative feedback. In fact, the expression is the same as for the noninverting case.

$$Z_{out(I)} \cong \frac{Z_{out}}{1 + A_{ol}B} \quad (6-14)$$

The output impedance of both the noninverting and the inverting configurations is very low; in fact, it is almost zero in practical cases. Because of this near zero output impedance, any load impedance connected to the op-amp output can vary greatly and not change the output voltage at all.

EXAMPLE 6-9

Find the values of the input and output impedances in Figure 6-32. Also, determine the closed-loop voltage gain. The op-amp has the following parameters: $A_{ol} = 50,000$; $Z_{in} = 4 \text{ M}\Omega$; and $Z_{out} = 50 \Omega$.

 


FIGURE 6-32

SOLUTION

$$Z_{in(l)} \cong R_i = 1.0 \text{ k}\Omega$$

The feedback attenuation, B , is

$$B = \frac{R_i}{R_i + R_f} = \frac{1.0 \text{ k}\Omega}{101 \text{ k}\Omega} = 0.0099$$


Then

$$Z_{out(l)} = \frac{Z_{out}}{1 + A_{ol}B} = \frac{50 \text{ }\Omega}{1 + (50,000)(0.0099)} = 101 \text{ m}\Omega \quad (\text{zero for all practical purposes})$$

$$A_{cl(l)} = -\frac{R_f}{R_i} = -\frac{100 \text{ k}\Omega}{1.0 \text{ k}\Omega} = -100$$

PRACTICE EXERCISE

Determine the input and output impedances and the closed-loop voltage gain in Figure 6-32. The op-amp parameters and circuit values are as follows: $A_{ol} = 100,000$; $Z_{in} = 5 \text{ M}\Omega$; $Z_{out} = 75 \text{ }\Omega$; $R_i = 560 \text{ }\Omega$; and $R_f = 82 \text{ k}\Omega$.

 SYSTEM EXAMPLE 6-2

Communication systems such as found in two-way radios generally operate at frequencies above 10 MHz, a frequency too high for most general purpose op-amps. Special high-frequency voltage feedback op-amps are available for RF and IF frequencies but will begin to be less effective above about 10 MHz. (Current feedback amplifiers, covered in Chapter 12, can reach higher frequencies.) In systems such as an FM receiver, the radio frequency is down-converted to a lower IF for processing. An FM broadcast receiver is designed for 88 MHz to 108 MHz and traditionally uses a first IF frequency of 10.7 MHz, which can be handled by a high-frequency op-amp. (A second lower IF frequency may also be used.) Most systems now use digital processing techniques, but even in these cases an IF frequency is produced and amplified by an analog amplifier. The front end of a traditional FM receiver is shown in the block diagram in Figure SE6-4. Our focus will be on the IF amplifier.

Figure SE6-5 shows a typical analog IF amplifier, using a high-frequency op-amp such as the THS4001. Looking into the amplifier and looking back from the load, the impedances must match the source; in this case 50 Ω . In high-frequency amplifiers, signals need to be terminated in the characteristic impedance throughout the system to prevent reflections, which can cancel the signal. To accomplish this, a traditional noninverting configuration can be used as shown but with the addition of input and output resistors (R_T

 


FIGURE SE6-4 Front end of an FM receiver.

 


FIGURE SE6-5 An IC IF amplifier.

and R_O) to set these impedances at $50\ \Omega$. (Recall that the op-amp itself with feedback has extremely high input impedance and near zero output impedance.) As in any noninverting amplifier, the gain is determined by R_f and R_i .

Special precautions must be taken by designers and technicians working with high-frequency circuits to prevent problems. One precaution with any high-frequency circuit is to keep component lead lengths and wiring as short as possible to minimize stray capacitance and inductive effects. Even pc board traces have inductance at high frequencies that can attenuate an RF signal. If you replace a part in a high-frequency circuit, use specified parts to avoid self-resonating effects. Frequently, capacitors are special ceramic chip capacitors that have no leads at all. RF circuits, including the power supply, are shielded in enclosures to prevent radiation or noise problems. Replace any covers or shields including all of the screws. Probing high-frequency circuits always needs to be done with awareness of loading effects, so probes should be low-capacitance types.

Noise


In electronics, noise is an unwanted random fluctuation in an electrical signal. We will look at op-amp noise specifications and how to solve for the signal-to-noise ratio of an op-amp. While interference from an external source qualifies as noise, only noise generated within the op-amp is considered in its noise specification. There are two basic forms of noise. At low frequencies, noise is inversely proportional to frequency; this is called $1/f$ noise or “pink noise.” Above a critical noise frequency (sometimes called the $1/f$ corner frequency), the noise level becomes flat across the frequency spectrum; this is called “white noise.” The critical noise frequency is a figure of merit for op-amp performance—the lower the better.

Noise in Operational Amplifiers

One of the ways that system designers are “going green” is to design circuits with lower system supply voltages and bias currents. As operating voltages are reduced, and accuracy requirements increase, system noise becomes a greater concern. Noise is defined as any unwanted signal that affects the quality of a desired signal. This relationship is usually expressed as a ratio. The *signal-to-noise ratio* is found as,

$$\frac{S_f}{N_f} = \frac{\text{rms signal}}{\text{rms noise}}$$

We can use a stereo system as a practical example of signal-to-noise. If you are playing your music very loud, chances are you will not be aware of the system noise since the signal (music) is swamping out the system noise; the signal-to-noise ratio is very high. Now if you stop the music and leave the amplifier turned up, you will be able to hear the system noise; the signal-to-noise ratio is now very low. Signal-to-noise is one of the reasons that CDs have largely replaced vinyl records and cassette tapes. Both of these mediums have much higher signal-to-noise ratios than CDs. In most cases the noise you hear in a modern stereo system is from the electronics, not from the medium.

 


SYSTEM NOTE

The power distribution of noise is measured in watts per hertz (W/Hz). Power is proportional to the square of the voltage, so noise voltage density is found by taking the square root of the noise power density, resulting in units of volts per square root hertz $\left(\frac{\text{V}}{\sqrt{\text{Hz}}}\right)$. For operational amplifiers the units are usually in $\frac{\text{nV}}{\sqrt{\text{Hz}}}$ at specific frequencies. However, even in very low-noise op-amps, below 10 Hz noise units of $\frac{\mu\text{V}}{\sqrt{\text{Hz}}}$ are possible due to the pink noise contribution. The white noise rating of different op-amps can vary from $\frac{1 \text{ nV}}{\sqrt{\text{Hz}}}$ to $\frac{20 \text{ nV}}{\sqrt{\text{Hz}}}$ or even higher. Bipolar op-amps tend to have lower voltage noise than JFET op-amps. It is possible to make a low-noise JFET op-amp, but input capacitance increases as a trade off which limits bandwidth.

A voltage noise level graph for a very low-noise op-amp is shown in Figure 6–33.

The input voltage noise density at 1 kHz for this op-amp is $\frac{1.1 \text{ nV}}{\sqrt{\text{Hz}}}$, a very low figure.

FIGURE 6–33 Voltage noise as a function of frequency.

 

At low frequencies, the noise density increases due to the $1/f$ noise contribution, as you can see from the graph.

Solving for the Signal-to-Noise Ratio

To simplify our calculations we will only solve for the noise contribution from the op-amp. Refer to the circuit in Figure 6-34. Assume that the op-amp will operate in the audio band from 20 Hz to 20 kHz and above its $1/f$ corner frequency. Assume that the white noise rating is $\frac{2.9 \text{ nV}}{\sqrt{\text{Hz}}}$, and the input signal is 12.5 mV.

 


FIGURE 6-34

The first step is to solve for the root Hz part as:

$$\sqrt{20,000 - 20} = 141.4$$

The noise input is found by multiplying this value by the noise specification of $\frac{2.9 \text{ nV}}{\sqrt{\text{Hz}}}$:

$$\frac{2.9 \text{ nV}}{\sqrt{\text{Hz}}} \times 141.4 \sqrt{\text{Hz}} = 410 \text{ nV}$$

The noise output is found by multiplying the noise input by the closed-loop voltage gain as

$$410 \text{ nV} \times (-200) = -82 \mu\text{V}$$

The output signal is found as $12.5 \text{ mV} \times (-200) = -2.5 \text{ V}$

Finally the signal-to-noise ratio (dB) is found as

$$20 \log (-2.5 \text{ V} \div (-82 \mu\text{V})) = 89.7 \text{ dB}$$

It is important to note that these calculations only take into account the op-amp itself. Noise from the circuit resistors will be added to the op-amp noise. The noise from resistors is called thermal or Johnson noise. Keeping the resistors at lower values will decrease the total noise, but increase circuit current and lower system efficiency—there are always trade-offs. Thermal noise is white noise and is proportional to resistance, temperature, and bandwidth. Thermal noise is found as

$$E_{\text{th}} = \sqrt{4kTRB}$$

where E_{th} = thermal noise in V_{rms}

k = a constant equal to 1.38×10^{-23}

T = the temperature in K

R = the resistance in Ω

B = the bandwidth in Hz

When there is more than one noise source contributor, the total noise (N_T) is the geometric sum of all noise sources, found as


$$N_T = \sqrt{N_1^2 + N_2^2 + \dots + N_n^2}$$

A full noise analysis of a practical op-amp circuit is complex and beyond the scope of this text.

SECTION 6–6 CHECKUP

- How does the input impedance of a noninverting amplifier configuration compare to the input impedance of the op-amp itself?
- When an op-amp is connected in a voltage-follower configuration, does the input impedance increase or decrease?
- Given that $R_f = 100\text{ k}\Omega$, $R_i = 2.0\text{ k}\Omega$, $A_{ol} = 120,000$, $Z_{in} = 2\text{ M}\Omega$, and $Z_{out} = 60\ \Omega$, what are $Z_{in(l)}$ and $Z_{out(l)}$ for an inverting amplifier configuration?
- What are the typical units for measuring noise in an operational amplifier?

6–7 TROUBLESHOOTING

 

As a technician, you will no doubt encounter situations in which an op-amp or its associated circuitry has malfunctioned. The op-amp is a complex integrated circuit with many types of internal failures possible. However, since you cannot troubleshoot the op-amp internally, you treat it as a single device with only a few connections to it. If it fails, you replace it just as you would a resistor, capacitor, or transistor.

After completing this section, you should be able to

- Troubleshoot op-amp circuits
 - Analyze faults in a noninverting amplifier
 - Analyze faults in a voltage-follower
 - Analyze faults in an inverting amplifier

In op-amp configurations, there are only a few components that can fail. Both inverting and noninverting amplifiers have a feedback resistor, R_f , and an input resistor, R_i . Depending on the circuit, a load resistor, bypass capacitors, or a voltage compensation resistor may also be present. Any of these components can appear to be open or appear to be shorted. An open is not always due to the component itself but may be due to a poor solder connection or a bent pin on the op-amp. Likewise, a short circuit may be due to a solder bridge. Of course, the op-amp itself can fail. Let's examine the basic configurations, considering only the feedback and input resistor failure modes and associated symptoms.

Faults in the Noninverting Amplifier

The first thing to do when you suspect a faulty circuit is to check for the proper power supply voltage. *The positive and negative supply voltages should be measured on the op-amp's pins* with respect to a nearby circuit ground. If either voltage is missing or incorrect, trace the power connections back toward the supply before making other checks. Check that the ground path is not open, giving a misleading power supply reading. If you have verified the supply voltages and ground path, possible faults with the basic amplifier are as follows.

OPEN FEEDBACK RESISTOR If the feedback resistor, R_f , in Figure 6–35 opens, the op-amp is operating with its very high open-loop gain, which causes the input signal to drive the device into nonlinear operation and results in a severely clipped output signal as shown in part (a).

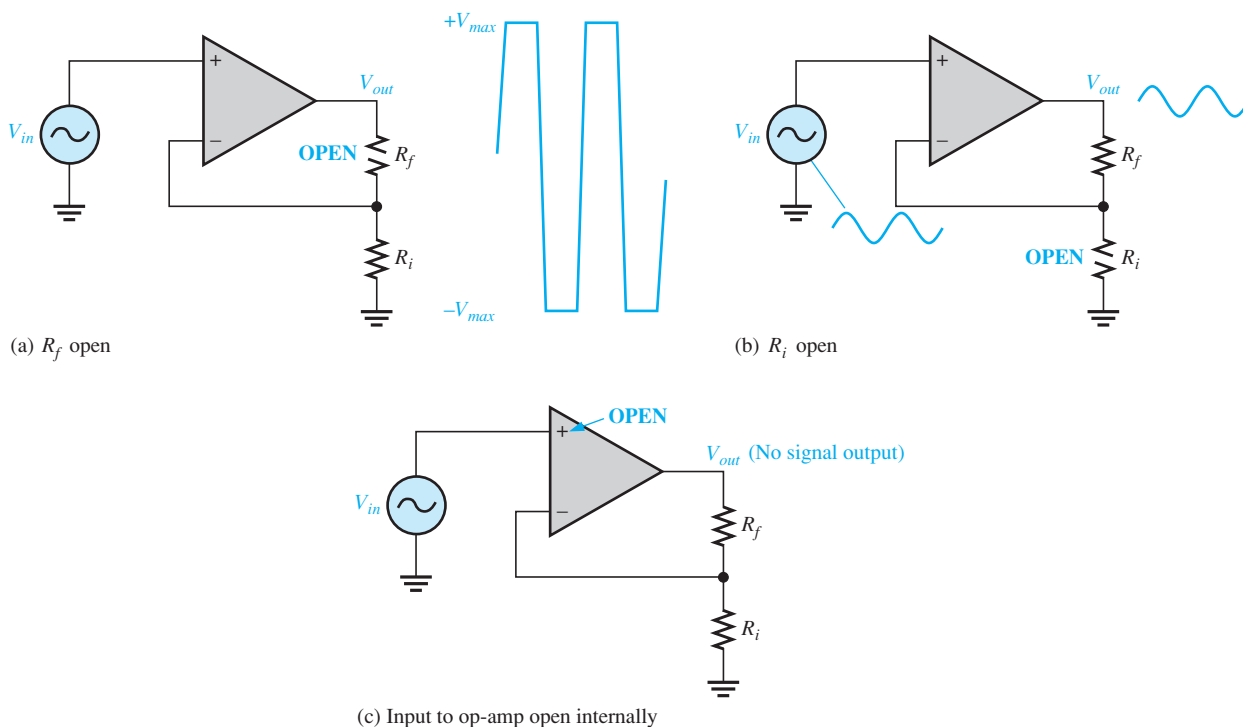


FIGURE 6-35 Faults in the noninverting amplifier.

OPEN INPUT RESISTOR In this case, you still have a closed-loop configuration. But, since R_i is open and effectively equal to infinity, ∞ , the closed-loop gain from Equation (6-6) is

$$A_{cl(NI)} = \frac{R_f}{R_i} + 1 = \frac{R_f}{\infty} + 1 = 0 + 1 = 1$$

This shows that the amplifier acts like a voltage-follower. You would observe an output signal that is the same as the input, as indicated in Figure 6-35(b).

INTERNALLY OPEN NONINVERTING OP-AMP INPUT In this situation, because the input voltage is not applied to the op-amp, the output is zero. This is indicated in Figure 6-35(c).

OTHER OP-AMP FAULTS In general, an internal failure will result in a loss or distortion of the output signal. The best approach is to first make sure that there are no external failures or faulty conditions. If everything else is good, then the op-amp must be bad.

Faults in the Voltage-Follower

The voltage-follower is a special case of the noninverting amplifier. Except for a bad power supply, a bad op-amp, or an open or short at a connection, about the only thing that can happen in a voltage-follower circuit is an open feedback loop. This would have the same effect as an open feedback resistor as previously discussed.

Faults in the Inverting Amplifier

POWER SUPPLY As in the case of the noninverting amplifier, the power supply voltages should be checked first. Power supply voltages should be checked on the op-amp's pins with respect to a nearby ground.

OPEN FEEDBACK RESISTOR If R_f opens as indicated in Figure 6–36(a), the input signal still feeds through the input resistor and is amplified by the high open-loop gain of the op-amp. This forces the device to be driven into nonlinear operation, and you will see an output something like that shown. This is the same result as in the noninverting configuration.

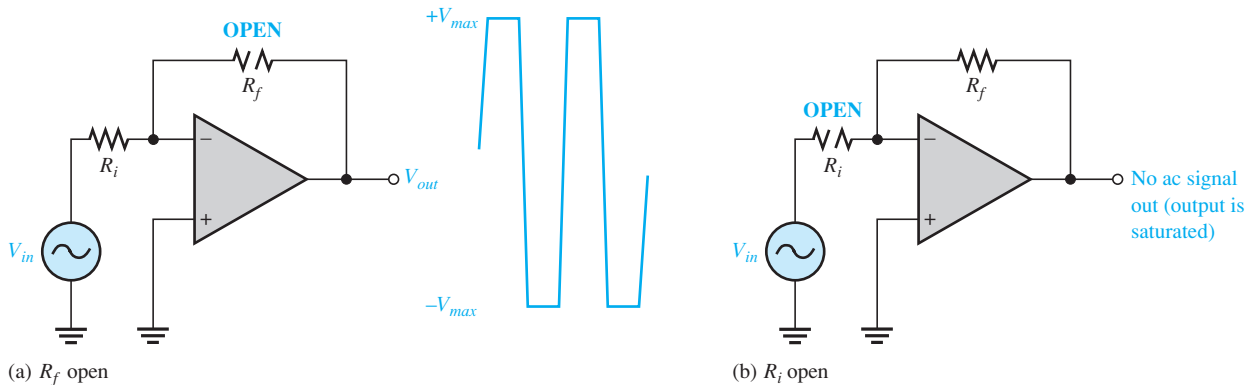


FIGURE 6–36 Faults in the inverting amplifier.

OPEN INPUT RESISTOR This prevents the input signal from getting to the op-amp input, so there will be no output signal, as indicated in Figure 6–36(b).

Failures in the op-amp itself have the same effects as previously discussed for the noninverting amplifier.

SECTION 6–7 CHECKUP

1. If you notice that the op-amp output is saturated, what should you check first?
2. If there is no op-amp output signal when there is a verified input signal, what should you check first?

SUMMARY

- The basic op-amp has three terminals not including power and ground: inverting (–) input, noninverting (+) input, and output.
- Most op-amps require both a positive and a negative dc supply voltage.
- The ideal (perfect) op-amp has infinite input impedance, zero output impedance, infinite open-loop voltage gain, infinite bandwidth, and infinite CMRR.
- A good practical op-amp has high input impedance, low output impedance, high open-loop voltage gain, and a wide bandwidth.
- A differential amplifier is normally used for the input stage of an op-amp.
- A differential input voltage appears between the inverting and noninverting inputs of a differential amplifier.
- A single-ended input voltage appears between one input and ground (with the other input grounded).
- A differential output voltage appears between two output terminals of a diff-amp.
- A single-ended output voltage appears between the output and ground of a diff-amp.
- Common mode occurs when equal in-phase voltages are applied to both input terminals.
- Input offset voltage produces an output error voltage (with no input voltage).

- Input bias current also produces an output error voltage (with no input voltage).
- Input offset current is the difference between the two bias currents.
- Open-loop voltage gain is the gain of an op-amp with no external feedback connections.
- Closed-loop voltage gain is the gain of an op-amp with external feedback.
- The common-mode rejection ratio (CMRR) is a measure of an op-amp's ability to reject common-mode inputs.
- Slew rate is the rate in volts per microsecond at which the output voltage of an op-amp can change in response to a step input.
- Figure 6–37 shows the op-amp symbol and the three basic op-amp configurations.

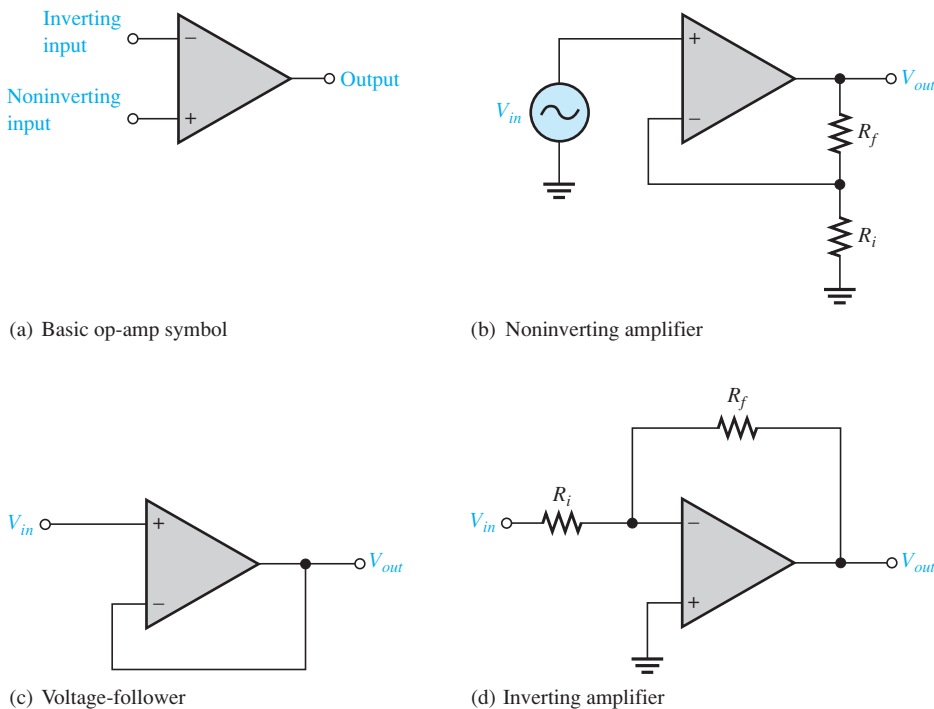


FIGURE 6–37

- All op-amp configurations listed use negative feedback. Negative feedback occurs when a portion of the output voltage is connected back to the inverting input such that it subtracts from the input voltage, thus reducing the voltage gain but increasing the stability and bandwidth.
- A noninverting amplifier configuration has a higher input impedance and a lower output impedance than the op-amp itself (without feedback).
- An inverting amplifier configuration has an input impedance approximately equal to the input resistor R_i and an output impedance that is lower than the output impedance of the op-amp itself (without feedback).
- The voltage-follower has the highest input impedance and the lowest output impedance of the three configurations.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Closed-loop voltage gain The net voltage gain of an amplifier when negative feedback is included.

Common mode A condition characterized by the presence of the same signal on both op-amp inputs.

Common-mode rejection ratio (CMRR) The ratio of open-loop gain to common-mode gain; a measure of an op-amp's ability to reject common-mode signals.

Differential amplifier (diff-amp) An amplifier that produces an output voltage proportional to the difference of the two input voltages.

Differential mode The input condition of an op-amp in which opposite polarity signals are applied to the two inputs.

Inverting amplifier An op-amp closed-loop configuration in which the input signal is applied to the inverting input.

Negative feedback The process of returning a portion of the output signal to the input of an amplifier such that it is out of phase with the input signal.

Noninverting amplifier An op-amp closed-loop configuration in which the input signal is applied to the noninverting input.

Open-loop voltage gain The internal gain of an op-amp without any external feedback.

Operational amplifier (op-amp) A type of amplifier that has very high voltage gain, very high input impedance, very low output impedance, and good rejection of common-mode signals.

Single-ended mode The input condition of an op-amp in which one input is grounded and the signal voltage is applied only to the other input.

Slew rate The rate of change of the output voltage of an op-amp in response to a step input.

Voltage-follower A closed-loop, noninverting op-amp with a voltage gain of 1.

KEY FORMULAS

DIFFERENTIAL AMPLIFIERS

$$(6-1) \quad \text{CMRR} = \frac{A_{v(d)}}{A_{cm}} \quad \text{Common-mode rejection ratio (diff-amp)}$$

$$(6-2) \quad \text{CMRR}' = 20 \log \left(\frac{A_{v(d)}}{A_{cm}} \right) \quad \text{Common-mode rejection ratio (dB) (diff-amp)}$$

OP-AMP PARAMETERS

$$(6-3) \quad \text{CMRR} = \frac{A_{ol}}{A_{cm}} \quad \text{Common-mode rejection ratio (op-amp)}$$

$$(6-4) \quad \text{CMRR}' = 20 \log \left(\frac{A_{ol}}{A_{cm}} \right) \quad \text{Common-mode rejection ratio (dB) (op-amp)}$$

$$(6-5) \quad \text{Slew rate} = \frac{\Delta V_{out}}{\Delta t} \quad \text{Slew rate}$$

OP-AMP CONFIGURATIONS

$$(6-6) \quad A_{cl(\text{NI})} = \frac{R_f}{R_i} + 1 \quad \text{Voltage gain (noninverting)}$$

$$(6-7) \quad A_{cl(\text{VF})} = 1 \quad \text{Voltage gain (voltage-follower)}$$

$$(6-8) \quad A_{cl(\text{I})} = -\frac{R_f}{R_i} \quad \text{Voltage gain (inverting)}$$

OP-AMP IMPEDANCES

$$(6-9) \quad Z_{in(\text{NI})} = (1 + A_{ol}B)Z_{in} \quad \text{Input impedance (noninverting)}$$

$$(6-10) \quad Z_{out(\text{NI})} = \frac{Z_{out}}{1 + A_{ol}B} \quad \text{Output impedance (noninverting)}$$

$$(6-11) \quad Z_{in(\text{VF})} = (1 + A_{ol})Z_{in} \quad \text{Input impedance (voltage-follower)}$$

$$(6-12) \quad Z_{out(\text{VF})} = \frac{Z_{out}}{1 + A_{ol}} \quad \text{Output impedance (voltage-follower)}$$

$$(6-13) \quad Z_{in(\text{I})} \cong R_i \quad \text{Input impedance (inverting)}$$


$$(6-14) \quad Z_{out(\text{I})} \cong \frac{Z_{out}}{1 + A_{ol}B} \quad \text{Output impedance (inverting)}$$

SELF-TEST

Answers are at the end of the chapter.

- An integrated circuit (IC) op-amp has
 - two inputs and two outputs
 - one input and one output
 - two inputs and one output
- Which of the following characteristics does not necessarily apply to an op-amp?
 - High gain
 - Low power
 - High input impedance
 - Low output impedance
- A differential amplifier
 - is part of an op-amp
 - has one input and one output
 - has two outputs
 - answers (a) and (c)
- When a differential amplifier is operated single-ended,
 - the output is grounded
 - one input is grounded and a signal is applied to the other
 - both inputs are connected together
 - the output is not inverted
- In the differential mode,
 - opposite polarity signals are applied to the inputs
 - the gain is 1
 - the outputs are different amplitudes
 - only one supply voltage is used
- In the common mode,
 - both inputs are grounded
 - the outputs are connected together
 - an identical signal appears on both inputs
 - the output signals are in phase
- Common-mode gain is
 - very high
 - very low
 - always unity
 - unpredictable
- Differential gain is
 - very high
 - very low
 - dependent on the input voltage
 - about 100
- If $A_{v(d)} = 3500$ and $A_{cm} = 0.35$, the CMRR is
 - 1225
 - 10,000
 - 80 dB
 - answers (b) and (c)
- With zero volts on both inputs, an op-amp ideally should have an output equal to
 - the positive supply voltage
 - the negative supply voltage
 - zero
 - the CMRR
- Of the values listed, the most realistic value for open-loop gain of an op-amp is
 - 1
 - 2000
 - 80 dB
 - 100,000
- A certain op-amp has bias currents of $50 \mu\text{A}$ and $49.3 \mu\text{A}$. The input offset current is
 - 700 nA
 - $99.3 \mu\text{A}$
 - $49.65 \mu\text{A}$
 - none of these
- The output of a particular op-amp increases 8 V in 12 μs . The slew rate is
 - $96 \text{ V}/\mu\text{s}$
 - $0.67 \text{ V}/\mu\text{s}$
 - $1.5 \text{ V}/\mu\text{s}$
 - none of these
- For an op-amp with negative feedback, the output is
 - equal to the input
 - increased
 - fed back to the inverting input
 - fed back to the noninverting input

 15. The use of negative feedback
- reduces the voltage gain of an op-amp
 - makes the op-amp oscillate
 - makes linear operation possible
 - answers (a) and (c)
16. Negative feedback
- increases the input and output impedances
 - increases the input impedance and the bandwidth
 - decreases the output impedance and the bandwidth
 - does not affect impedances or bandwidth
17. A certain noninverting amplifier has an R_i of 1.0 k Ω and an R_f of 100 k Ω . The closed-loop gain is
- 100,000
 - 1000
 - 101
 - 100
18. If the feedback resistor in Question 17 is open, the voltage gain
- increases
 - decreases
 - is not affected
 - depends on R_i
19. A certain inverting amplifier has a closed-loop gain of 25. The op-amp has an open-loop gain of 100,000. If another op-amp with an open-loop gain of 200,000 is substituted in the configuration, the closed-loop gain
- doubles
 - drops to 12.5
 - remains at 25
 - increases slightly
20. A voltage-follower
- has a gain of one
 - is noninverting
 - has no feedback resistor
 - answers (a), (b), and (c)



TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 6–42.

- If the collector of Q_1 opens,
 - The dc output voltage will
 - increase
 - decrease
 - not change
 - The current through R_3 will
 - increase
 - decrease
 - not change

Refer to Figure 6–46.

- If R_i is open,
 - The closed-loop gain will
 - increase
 - decrease
 - not change
 - For a given input signal, the output signal will
 - increase
 - decrease
 - not change
- If R_f is open,
 - The output voltage will
 - increase
 - decrease
 - not change
 - The open-loop gain will
 - increase
 - decrease
 - not change
 - The closed-loop gain will
 - increase
 - decrease
 - not change

Refer to Figure 6–50.

- If R_f is shorted,
 8. The closed-loop gain will
 - (a) increase (b) decrease (c) not change
 9. The input impedance will
 - (a) increase (b) decrease (c) not change
- If R_f is open,
 10. The open-loop gain will
 - (a) increase (b) decrease (c) not change
- If R_f is smaller than the specified value,
 11. The closed-loop gain will
 - (a) increase (b) decrease (c) not change
 12. The open-loop gain will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 6-1 Introduction to Operational Amplifiers

1. Compare a practical op-amp to the ideal.
2. Two IC op-amps are available to you. Their characteristics are listed below. Choose the one you think is more desirable.

Op-amp 1: $Z_{in} = 5 \text{ M}\Omega$, $Z_{out} = 100 \text{ }\Omega$, $A_{ol} = 50,000$

Op-amp 2: $Z_{in} = 10 \text{ M}\Omega$, $Z_{out} = 75 \text{ }\Omega$, $A_{ol} = 150,000$

SECTION 6-2 The Differential Amplifier

3. Identify the type of input and output configuration for each basic differential amplifier in Figure 6–38.

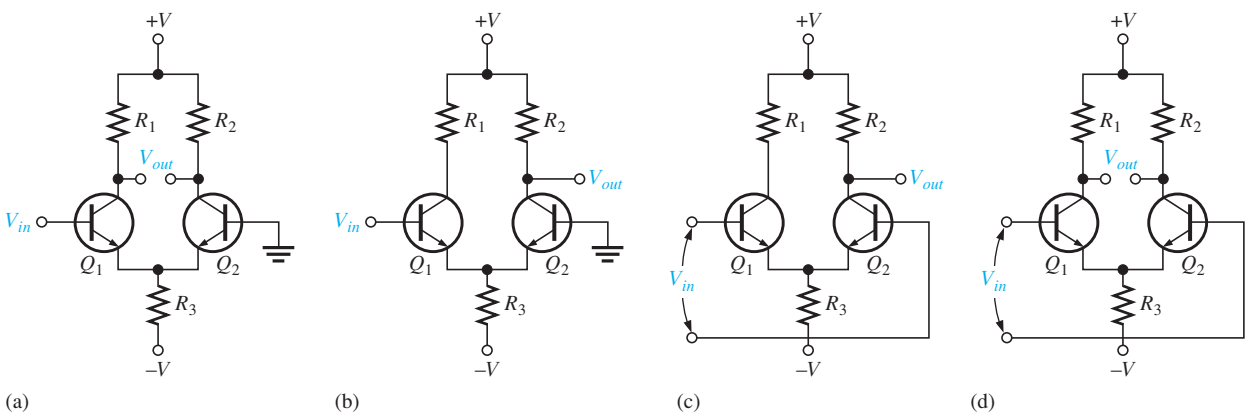


FIGURE 6-38

4. The dc base voltages in Figure 6–39 are zero. Using your knowledge of transistor analysis, determine the dc differential output voltage. Assume that for Q_1 , $I_C/I_E = 0.98$ and for Q_2 , $I_C/I_E = 0.975$.
5. Identify the quantity being measured by each meter in Figure 6–40.

 


FIGURE 6-39

 



FIGURE 6-40

6. A differential amplifier stage has collector resistors of 5.1 kΩ each. If $I_{C1} = 1.35 \text{ mA}$ and $I_{C2} = 1.29 \text{ mA}$, what is the differential output voltage?

SECTION 6-3 Op-Amp Data Sheet Parameters

7. Determine the bias current, I_{BIAS} , given that the input currents to an op-amp are $8.3 \mu\text{A}$ and $7.9 \mu\text{A}$.
8. Distinguish between input bias current and input offset current, and then calculate the input offset current in Problem 7.
9. A certain op-amp has a CMRR of 250,000. Convert this to dB.
10. The open-loop gain of a certain op-amp is 175,000. Its common-mode gain is 0.18. Determine the CMRR in dB.
11. An op-amp data sheet specifies a CMRR of 300,000 and an A_{ol} of 90,000. What is the common-mode gain?
12. Figure 6-41 shows the output voltage of an op-amp in response to a step input. What is the slew rate?
13. How long does it take the output voltage of an op-amp to go from -10 V to $+10 \text{ V}$, if the slew rate is $0.5 \text{ V}/\mu\text{s}$?

FIGURE 6-41

 

SECTION 6-5 Op-Amp Configurations with Negative Feedback

14. Identify each of the op-amp configurations in Figure 6-42.
15. A noninverting amplifier has an R_i of 1.0 kΩ and an R_f of 100 kΩ. Determine V_f and B if $V_{out} = 5 \text{ V}$.
16. For the amplifier in Figure 6-43, determine the following:
 - (a) $A_{cl(NI)}$
 - (b) V_{out}
 - (c) V_f
17. Determine the closed-loop gain of each amplifier in Figure 6-44.

 


FIGURE 6-42

 


FIGURE 6-43

 


FIGURE 6-44

18. Find the value of R_f that will produce the indicated closed-loop gain in each amplifier in Figure 6-45.

 


FIGURE 6-45

19. Find the gain of each amplifier in Figure 6–46.
 20. If a signal voltage of 10 mV rms is applied to each amplifier in Figure 6–46, what are the output voltages and what is their phase relationship with inputs?

 


FIGURE 6–46

21. Determine the approximate values for each of the following quantities in Figure 6–47.
 (a) I_{in} (b) I_f (c) V_{out} (d) Closed-loop gain

 


FIGURE 6–47

SECTION 6–6 Op-Amp Impedances

22. Determine the input and output impedances for each amplifier configuration in Figure 6–48.

 


FIGURE 6–48

23. Repeat Problem 22 for each circuit in Figure 6–49.
 24. Repeat Problem 22 for each circuit in Figure 6–50.

 


FIGURE 6-49

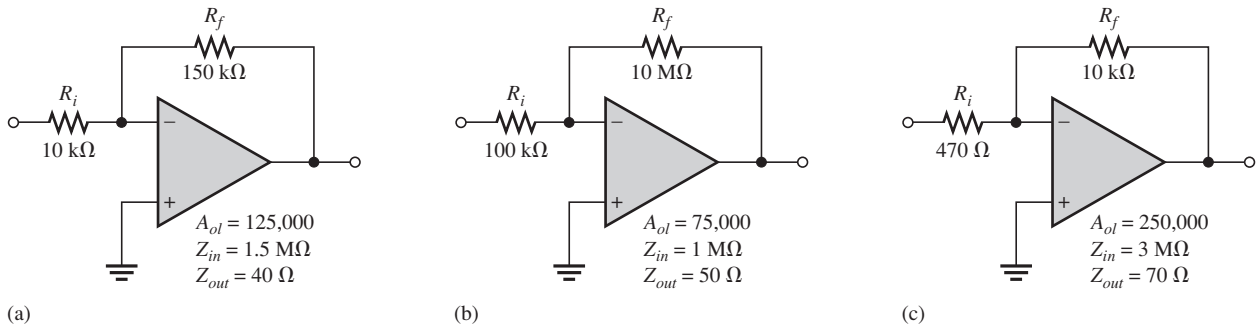


FIGURE 6-50

SECTION 6-7 Troubleshooting

25. Determine the most likely fault(s) for each of the following symptoms in Figure 6-51 with a 100 mV signal applied.
 - (a) No output signal.
 - (b) Output severely clipped on both positive and negative swings.
26. Determine the effect on the output if the circuit in Figure 6-51 has the following fault (one fault at a time).
 - (a) Output pin is shorted to the inverting input.
 - (b) R_3 is open.
 - (c) R_3 is 10 kΩ instead of 910 Ω.
 - (d) R_1 and R_2 are swapped.
27. On the circuit board in Figure 6-52, what happens if the middle lead (wiper) of the 100 kΩ potentiometer is broken?

 


FIGURE 6-51

 


FIGURE 6-52

MULTISIM



MULTISIM TROUBLESHOOTING PROBLEMS

28. Open file P06-28 and determine the fault.
29. Open file P06-29 and determine the fault.
30. Open file P06-30 and determine the fault.
31. Open file P06-31 and determine the fault.
32. Open file P06-32 and determine the fault.
33. Open file P06-33 and determine the fault.
34. Open file P06-34 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 6-1

1. Inverting input, noninverting input, output, positive and negative supply voltages
2. A practical op-amp has high input impedance, low output impedance, high voltage gain, and wide bandwidth.

SECTION 6-2

1. Differential input is between two input terminals. Single-ended input is from one input terminal to ground (with other input grounded).
2. Common-mode rejection is the ability of an op-amp to produce very little output when the same signal is applied to both inputs.
3. A higher CMRR results in a lower common-mode gain.

SECTION 6-3

1. Input bias current, input offset voltage, drift, input offset current, input impedance, output impedance, common-mode input voltage range, CMRR, open-loop voltage gain, slew rate, frequency response
2. Slew rate and voltage gain are both frequency dependent.

SECTION 6-4

1. Negative feedback provides a stable controlled voltage gain, control of input and output impedances, and wider bandwidth.
2. The open-loop gain is so high that a very small signal on the input will drive the op-amp into saturation.
3. Both inputs will be the same.

SECTION 6-5

1. The main purpose of negative feedback is to stabilize the gain.
2. False
3. $A_{cl} = 1/0.02 = 50$
4. $A_{CL} = 50$

SECTION 6-6

1. The noninverting configuration has a higher Z_{in} than the op-amp alone.
2. Z_{in} increases in a voltage-follower.
3. $Z_{in(I)} \cong R_i = 2.0 \text{ k}\Omega$, $Z_{out(I)} \cong Z_{out} = 26 \text{ m}\Omega$.
4. $\frac{\text{nV}}{\sqrt{\text{Hz}}}$

SECTION 6-7

1. Check power supply voltages with respect to ground. Verify ground connections. Check for an open feedback resistor.

2. Verify power supply voltages and ground leads. For inverting amplifiers, check for open R_f . For noninverting amplifiers, check that V_{in} is actually on (+) pin; if so, check (-) pin for identical signal.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

6-1 34,000; 90.6 dB

6-2 (a) 0.168 (b) 87.96 dB (c) 2.1 V rms, 4.2 V rms (d) 0.168 V

6-3 12,649

6-4 20 V/ μ s

6-5 32.9

6-6 (a) 67.5 k Ω (b) The amplifier would have an open-loop gain producing a square wave.

6-7 (a) 20.6 G Ω , 14 m Ω (b) 23

6-8 Input Z increases, output Z decreases.

6-9 $Z_{in(I)} = 560 \Omega$, $Z_{out(I)} = 110 \text{ m}\Omega$, $A_{cl} = -146$

ANSWERS TO SELF-TEST

1. (c) 2. (b) 3. (d) 4. (b) 5. (a) 6. (c) 7. (b)
 8. (a) 9. (d) 10. (c) 11. (d) 12. (a) 13. (b) 14. (c)
 15. (d) 16. (b) 17. (c) 18. (a) 19. (c) 20. (d)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. increase 2. not change 3. decrease 4. decrease
 5. increase 6. not change 7. increase 8. increase
 9. decrease 10. not change 11. decrease 12. not change

CHAPTER 7

OP-AMP RESPONSES

OUTLINE

- 7-1 Basic Concepts
- 7-2 Op-Amp Open-Loop Response
- 7-3 Op-Amp Closed-Loop Response
- 7-4 Positive Feedback and Stability
- 7-5 Op-Amp Compensation

OBJECTIVES

- Discuss the basic areas of op-amp responses
- Understand the open-loop response of an op-amp
- Understand the closed-loop response of an op-amp
- Discuss positive feedback and stability in op-amp circuits
- Explain op-amp phase compensation

KEY TERMS

Bandwidth	Loop gain
Phase shift	Phase margin
Positive feedback	Stability

INTRODUCTION

In this chapter, you will learn about frequency response, bandwidth, phase shift, and other frequency-related parameters in op-amps. The effects of negative feedback will be further examined, and you will learn about stability requirements and how to compensate op-amp circuits to ensure stable operation.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

7-1 BASIC CONCEPTS

In Chapter 6 you learned how closed-loop voltage gains of the basic op-amp configurations are determined, and the distinction between open-loop voltage gain and closed-loop voltage gain was established. Because of the importance of these two different types of voltage gain, the definitions are restated in this section.

After completing this section, you should be able to

- Discuss the basic areas of op-amp responses
- Explain open-loop gain
- Explain closed-loop gain
- Discuss the frequency dependency of gain
- Explain the open-loop bandwidth
- Explain the unity-gain bandwidth
- Determine phase shift

Open-Loop Gain

The *open-loop gain* (A_{ol}) of an op-amp is the internal voltage gain of the device and represents the ratio of output voltage to input voltage, as indicated in Figure 7-1(a). Notice that there are no external components, so the open-loop gain is set entirely by the internal design. Open-loop voltage gain varies widely for different op-amps. Table 6-1 listed the open-loop gain for some representative op-amps. Data sheets often refer to the open-loop gain as the *large-signal voltage gain*.

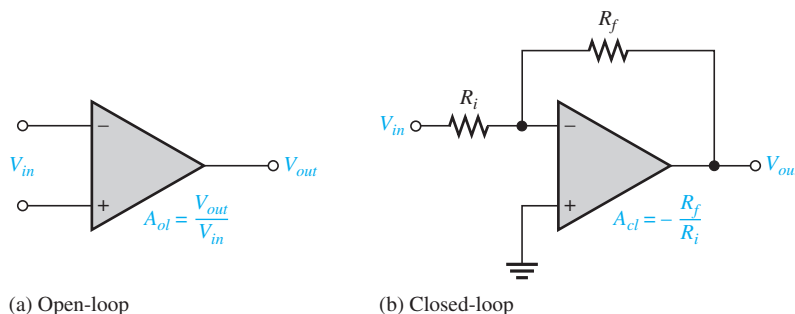


FIGURE 7-1 Open-loop and closed-loop op-amp configurations.

Closed-Loop Gain

The *closed-loop gain* (A_{cl}) is the voltage gain of an op-amp with external feedback. The amplifier configuration consists of the op-amp and an external negative feedback network that connects the output to the inverting ($-$) input. The closed-loop gain is determined by the external component values, as illustrated in Figure 7-1(b) for an inverting amplifier configuration. The closed-loop gain can be precisely controlled by external component values.

PROGRAMMABLE GAIN AMPLIFIERS A programmable gain amplifier (PGA) is a type of op-amp that has its gain selected by a digital input. They are popular in data acquisition systems where different inputs may have different signal levels. Typically a given channel is selected by a digital signal from a computer or controller and the PGA will have from two to ten or more inputs. Depending on the type of PGA and how it is configured, each channel can have its gain set to optimize its own sensor input or it can be digitally programmed to select a predetermined gain. For example, the PGA116 has 10 analog inputs, each of which can have any of 8 selected binary gains (from 1 to 128). The PGA116 and its cousin, the PGA117, has an internal multiplexer (channel selection circuit) as well as other features, including internal calibration capability.

SYSTEM EXAMPLE 7-1



INSTRUMENTATION SYSTEM FOR MULTIPLE TRANSDUCERS

In System Example 6-1 you saw a mixed system that combined mechanical and optical components with analog electronics. The system in this example is an industrial instrumentation system that combines both analog and digital circuitry in the same system.

Figure SE7-1 shows a simplified block diagram of the system. The manufacturer of airplane wings has a need to test wings in a wind tunnel. The wing is instrumented with a variety of sensors, including strain gauges to measure stress, flow rate sensors to check wind speed, and temperature sensors. The input signals from the sensors are different depending on the type of sensor and its sensitivity. For this reason, each channel needs a different gain. The output of the PGA is digitized by an analog-to-digital converter (which is described in SE8-2). The channels can be cycled rapidly by a controller and the data read to a computer for processing.


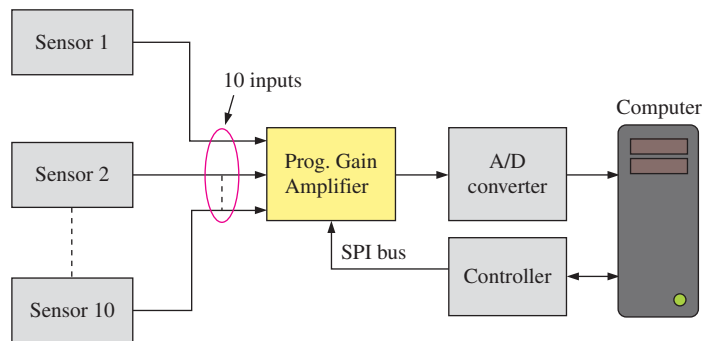


FIGURE SE7-1 Instrumentation system with programmable gain amplifier.

The focus in this example is the PGA. For this system, a PGA117 is selected because it has ten analog channels, each with a selectable range of gains that follow an oscilloscope 1-2-5 sequence (gains range from 1 to 200). The equivalent analog input circuit is shown in Figure SE7-2. The PGA117 has a three-wire serial peripheral interface (SPI) bus that allows the channel and gain to be selected from the controller. Channel select and gain data form the digital part of the circuit and are synchronized with a serial clock signal. When a channel is selected, the MUX switch closes and the value of R_f is programmed by the computer. The PGA analog supply (V_{DD}) can be run on +2.2 to +5.5 V. Despite the complexity of the overall IC, the basic op-amp operates like a standard single-ended, non-inverting amplifier with a closed-loop gain of $A_v = \frac{R_f}{R_i} + 1$.

amplifier with a closed-loop gain of $A_v = \frac{R_f}{R_i} + 1$.

FIGURE SE7-2 Equivalent input stage for the PGA116 and PGA117.

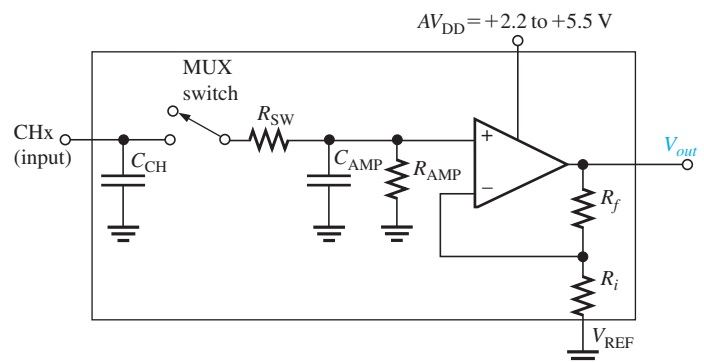

The Gain Is Frequency Dependent

In Chapter 6, all of the gain expressions applied to the midrange gain and were considered independent of the frequency. The midrange open-loop gain of an op-amp extends from zero frequency (dc) up to a critical frequency at which the gain is 3 dB less than the midrange value. The difference here is that op-amps are dc amplifiers (no capacitive coupling between stages), and therefore, there is no lower critical frequency. This means that the midrange gain extends down to zero frequency (dc), and dc voltages are amplified the same as midrange signal frequencies.

An open-loop response curve (Bode plot) for a certain op-amp is shown in Figure 7-2. Most op-amp data sheets show this type of curve or specify the midrange open-loop gain. Notice that the curve rolls off (decreases) at -20 dB per decade (-6 dB per octave). The midrange gain is 200,000, which is 106 dB, and the critical (cutoff) frequency is approximately 10 Hz.

 


FIGURE 7-2 Ideal plot of open-loop voltage gain versus frequency for a typical op-amp. The frequency scale is logarithmic.

3 dB Open-Loop Bandwidth

The **bandwidth** of an ac amplifier is the frequency range between the points where the gain is 3 dB less than the midrange gain. In general, the bandwidth equals the upper critical frequency (f_{cu}) minus the lower critical frequency (f_{cl}).

$$BW = f_{cu} - f_{cl}$$

Since f_{cl} for an op-amp is zero, the bandwidth is simply equal to the upper critical frequency.

$$BW = f_{cu} \quad (7-1)$$

From now on, we will refer to f_{cu} as simply f_c ; and we will use open-loop (*ol*) or closed-loop (*cl*) subscript designators. For example, $f_{c(ol)}$ is the open-loop upper critical frequency and $f_{c(cl)}$ is the closed-loop upper critical frequency.

Unity-Gain Bandwidth

Notice in Figure 7-2 that the gain steadily decreases to a point where it is equal to one (0 dB). The value of the frequency at which this unity gain occurs is the *unity-gain bandwidth*.

Gain-Versus-Frequency Analysis

The RC lag (low-pass) networks within an op-amp are responsible for the roll-off in gain as the frequency increases. From basic ac circuit theory, the attenuation of an RC lag network, such as in Figure 7-3, is expressed as

 


FIGURE 7-3 RC lag network.

$$\frac{V_{out}}{V_{in}} = \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

Dividing both the numerator and denominator to the right of the equal sign by X_C ,

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + R^2/X_C^2}}$$

The critical frequency of an RC network is

$$f_c = \frac{1}{2\pi RC}$$

Dividing both sides by f gives

$$\frac{f_c}{f} = \frac{1}{2\pi RCf} = \frac{1}{(2\pi fC)R}$$

Since $X_C = 1/(2\pi fC)$, the above expression can be written as

$$\frac{f_c}{f} = \frac{X_C}{R}$$

 


FIGURE 7-4 Op-amp represented by gain element and internal RC network.

Substituting this result into the second equation produces the following expression for the attenuation of an RC lag network:

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + f^2/f_c^2}}$$

If an op-amp is represented by a voltage gain element with a gain of $A_{ol(mid)}$ and a single RC lag network, as shown in Figure 7-4, then the total open-loop gain of the op-amp is the product of the midrange open-loop gain $A_{ol(mid)}$ and the attenuation of the RC network.

$$A_{ol} = \frac{A_{ol(mid)}}{\sqrt{1 + f^2/f_c^2}} \tag{7-2}$$

As you can see from Equation (7-2), the open-loop gain equals the midrange value when the signal frequency f is much less than the critical frequency f_c and drops off as the frequency increases. Since f_c is part of the open-loop response of an op-amp, we will refer to it as $f_{c(ol)}$.

The following example demonstrates how the open-loop gain decreases as the frequency increases above $f_{c(ol)}$.

EXAMPLE 7-1

Determine A_{ol} for the following values of f . Assume $f_{c(ol)} = 100$ Hz and $A_{ol(mid)} = 100,000$.

- (a) $f = 0$ Hz (b) $f = 10$ Hz (c) $f = 100$ Hz (d) $f = 1000$ Hz

SOLUTION

(a) $A_{ol} = \frac{A_{ol(mid)}}{\sqrt{1 + f^2/f_{c(ol)}^2}} = \frac{100,000}{\sqrt{1 + 0}} = 100,000$

(b) $A_{ol} = \frac{100,000}{\sqrt{1 + (0.1)^2}} = 99,500$

$$(c) A_{ol} = \frac{100,000}{\sqrt{1 + (1)^2}} = \frac{100,000}{\sqrt{2}} = 70,700$$

$$(d) A_{ol} = \frac{100,000}{\sqrt{1 + (10)^2}} = 9950$$

PRACTICE EXERCISE*

Find A_{ol} for the following frequencies. Assume $f_{c(ol)} = 200$ Hz and $A_{ol(mid)} = 80,000$.

(a) $f = 2$ Hz (b) $f = 10$ Hz (c) $f = 2500$ Hz

*Answers are at the end of the chapter.

Programmable Gain Amplifier Response

In a system that uses a Programmable Gain Amplifier, the bandwidth will be reduced when the gain is raised. To determine the bandwidth for a given gain setting, it is best to refer to the manufacturer's data sheet. The information may be given as a graph or in a table. For example, the PGA117 has a specified bandwidth of 10 MHz at a gain of 1 but it drops to 0.35 MHz at a gain of 128.

SYSTEM NOTE



Phase Shift

As you know, an RC network causes a propagation delay from input to output, thus creating a **phase shift** between the input signal and the output signal. An RC lag network such as found in an op-amp stage causes the output signal voltage to lag the input, as shown in Figure 7-5. From basic ac circuit theory, the phase shift, ϕ , is

$$\phi = -\tan^{-1}\left(\frac{R}{X_C}\right)$$

Since $R/X_C = f/f_c$,

$$\phi = -\tan^{-1}\left(\frac{f}{f_c}\right) \quad (7-3)$$

The negative sign indicates that the output lags the input. This equation shows that the phase shift increases with frequency and approaches -90° as f becomes much greater than f_c .

 


FIGURE 7-5 Output voltage lags input voltage.

EXAMPLE 7-2

Calculate the phase shift for an RC lag network for each of the following frequencies, and then plot the curve of phase shift versus frequency. Assume $f_c = 100$ Hz.

- (a) $f = 1$ Hz (b) $f = 10$ Hz (c) $f = 100$ Hz
 (d) $f = 1000$ Hz (e) $f = 10$ kHz

SOLUTION

$$(a) \phi = -\tan^{-1}\left(\frac{f}{f_c}\right) = -\tan^{-1}\left(\frac{1 \text{ Hz}}{100 \text{ Hz}}\right) = -0.6^\circ$$

$$(b) \phi = -\tan^{-1}\left(\frac{10 \text{ Hz}}{100 \text{ Hz}}\right) = -5.7^\circ$$

$$(c) \phi = -\tan^{-1}\left(\frac{100 \text{ Hz}}{100 \text{ Hz}}\right) = -45.0^\circ$$

$$(d) \phi = -\tan^{-1}\left(\frac{1000 \text{ Hz}}{100 \text{ Hz}}\right) = -84.3^\circ$$

$$(e) \phi = -\tan^{-1}\left(\frac{10 \text{ kHz}}{100 \text{ Hz}}\right) = -89.4^\circ$$

The phase shift versus frequency curve is plotted in Figure 7–6. Note that the frequency axis is logarithmic.

 


FIGURE 7-6

PRACTICE EXERCISE

At what frequency, in this example, is the phase shift -60° ?

MULTISIM

Open file F07-06 found on the companion website. This simulation will be used to confirm the RC lag network phase calculations in Example 7–2.

SECTION 7-1 CHECKUP*

- How do the open-loop gain and the closed-loop gain of an op-amp differ?
- The upper critical frequency of a particular op-amp is 100 Hz. What is its open-loop 3 dB bandwidth?
- Does the open-loop gain increase or decrease with frequency above the critical frequency?
- What is the purpose of the SPI bus in the PGA117?

*Answers are at the end of the chapter.

7-2 OP-AMP OPEN-LOOP RESPONSE

In this section, you will learn about the open-loop frequency response and the open-loop phase response of an op-amp. Open-loop responses relate to an op-amp with no external feedback. The frequency response indicates how the voltage gain changes with frequency, and the phase response indicates how the phase shift between the input and output signal changes with frequency. The open-loop gain, like the β of a transistor, varies greatly from one device to the next of the same type.

After completing this section, you should be able to


- Understand the open-loop response of an op-amp
 - Discuss how internal stages affect the overall response
 - Discuss critical frequencies and roll-off rates
 - Determine overall phase response

Frequency Response

In Section 7-1, an op-amp was assumed to have a constant roll-off of -20 dB/decade above its critical frequency. For a large number of op-amps, this is indeed the case. Op-amps that have a constant -20 dB/decade roll-off from f_c to unity gain are called *compensated op-amps*. A compensated op-amp has only one RC network that determines its frequency characteristic. Thus, the roll-off rate is the same as that of a basic RC network.

For some op-amp circuits, the situation is more complicated. The frequency response may be determined by several internal stages, where each stage has its own critical frequency. As a result, the overall response is affected by more than one cascaded stage and the overall response is a composite of the individual responses. An op-amp that has more than one critical frequency is called an **uncompensated op-amp**.

 Uncompensated op-amps require careful attention to the feedback network to avoid oscillation. As an example, a three-stage op-amp is represented in Figure 7-7(a), and the



(a) Representation of an op-amp with three internal stages

 
 


FIGURE 7-7 Op-amp open-loop frequency response.

frequency response of each stage is shown in Figure 7–7(b). As you have learned, dB gains are added so that the total op-amp frequency response is as shown in Figure 7–7(c). Since the roll-off rates are additive, the total roll-off rate increases by -20 dB/decade (-6 dB/octave) as each critical frequency is reached.

Phase Response

In a multistage amplifier, each stage contributes to the total phase lag. As you have seen, each RC lag network can produce up to a -90° phase shift. Since each stage in an op-amp includes an RC lag network, a three-stage op-amp, for example, can have a maximum phase lag of -270° . Also, the phase lag of each stage is less than -45° when the frequency is below the critical frequency, equal to -45° at the critical frequency, and greater than -45° when the frequency is above the critical frequency. The phase lags of the stages of an op-amp are added to produce a total phase lag, according to the following formula for three stages:

$$\phi_{tot} = -\tan^{-1}\left(\frac{f}{f_{c1}}\right) - \tan^{-1}\left(\frac{f}{f_{c2}}\right) - \tan^{-1}\left(\frac{f}{f_{c3}}\right)$$

EXAMPLE 7–3

A certain op-amp has three internal amplifier stages with the following gains and critical frequencies:

Stage 1: $A'_{v1} = 40$ dB, $f_{c1} = 2000$ Hz

Stage 2: $A'_{v2} = 32$ dB, $f_{c2} = 40$ kHz

Stage 3: $A'_{v3} = 20$ dB, $f_{c3} = 150$ kHz

Determine the open-loop midrange dB gain and the total phase lag when $f = f_{c1}$.

SOLUTION

$$A'_{ol(mid)} = A'_{v1} + A'_{v2} + A'_{v3} = 40 \text{ dB} + 32 \text{ dB} + 20 \text{ dB} = 92 \text{ dB}$$

$$\begin{aligned} \phi_{tot} &= -\tan^{-1}\left(\frac{f}{f_{c1}}\right) - \tan^{-1}\left(\frac{f}{f_{c2}}\right) - \tan^{-1}\left(\frac{f}{f_{c3}}\right) \\ &= -\tan^{-1}(1) - \tan^{-1}\left(\frac{2}{40}\right) - \tan^{-1}\left(\frac{2}{150}\right) \\ &= -45^\circ - 2.86^\circ - 0.76^\circ = -48.6^\circ \end{aligned}$$

PRACTICE EXERCISE

The internal stages of a two-stage amplifier have the following characteristics: $A'_{v1} = 50$ dB, $A'_{v2} = 25$ dB, $f_{c1} = 1500$ Hz, and $f_{c2} = 3000$ Hz. Determine the open-loop midrange gain in dB and the total phase lag when $f = f_{c1}$.

SECTION 7–2 CHECKUP

1. If the individual stage gains of an op-amp are 20 dB and 30 dB, what is the total gain in dB?
2. If the individual phase lags are -49° and -5.2° , what is the total phase lag?

7-3 OP-AMP CLOSED-LOOP RESPONSE

Op-amps are normally used in a closed-loop configuration with negative feedback in order to achieve precise control of the gain and bandwidth. In this section, you will see how feedback affects the gain and frequency response of an op-amp.

After completing this section, you should be able to

- Understand the closed-loop response of an op-amp
- Determine the closed-loop gain
- Explain the effect of negative feedback on bandwidth
- Explain gain-bandwidth product

Recall from Chapter 6 that midrange gain is reduced by negative feedback, as indicated by the following closed-loop gain expressions for the three configurations previously covered. For the noninverting amplifier,

$$A_{cl(NI)} = \frac{R_f}{R_i} + 1$$

For the voltage-follower,

$$A_{cl(VF)} \cong 1$$

For the inverting amplifier,

$$A_{cl(I)} \cong -\frac{R_f}{R_i}$$

Effect of Negative Feedback on Bandwidth

You have learned how negative feedback affects the gain; now you will learn how it affects the amplifier's bandwidth. The closed-loop critical frequency of an op-amp is

$$f_{c(cl)} = f_{c(ol)}(1 + BA_{ol(mid)}) \quad (7-4)$$

This expression shows that the closed-loop critical frequency, $f_{c(cl)}$, is higher than the open-loop critical frequency $f_{c(ol)}$ by the factor $1 + BA_{ol(mid)}$. Recall that B is the feedback attenuation, $R_i/(R_i + R_f)$. A derivation of Equation (7-4) can be found in Appendix A.

Since $f_{c(cl)}$ equals the bandwidth for the closed-loop amplifier, the bandwidth is also increased by the same factor.

$$BW_{cl} = BW_{ol}(1 + BA_{ol(mid)}) \quad (7-5)$$

EXAMPLE 7-4

A certain amplifier has an open-loop midrange gain of 150,000 and an open-loop 3 dB bandwidth of 200 Hz. The attenuation of the feedback loop is 0.002. What is the closed-loop bandwidth?

SOLUTION


$$BW_{cl} = BW_{ol}(1 + BA_{ol(mid)}) = 200 \text{ Hz}[1 + (0.002)(150,000)] = \mathbf{60.2 \text{ kHz}}$$

PRACTICE EXERCISE

If $A_{ol(mid)} = 200,000$ and $B = 0.05$, what is the closed loop bandwidth?

Figure 7–8 graphically illustrates the concept of closed-loop response for a compensated op-amp. When the open-loop gain of an op-amp is reduced by negative feedback, the bandwidth is increased. The closed-loop gain is independent of the open-loop gain up to the point of intersection of the two gain curves. This point of intersection is the critical frequency, $f_{c(cl)}$, for the closed-loop response. Notice that beyond the closed-loop critical frequency the closed-loop gain has the same roll-off rate as the open-loop gain.

FIGURE 7–8 Closed-loop gain compared to open-loop gain.

 

Gain-Bandwidth Product

An increase in closed-loop gain causes a decrease in the bandwidth, and vice versa, such that *the product of gain and bandwidth is a constant*. This is true as long as the roll-off rate is a fixed -20 dB/decade. If A_{cl} represents the gain of any of the closed-loop configurations and $f_{c(cl)}$ represents the closed-loop critical frequency (same as the bandwidth), then

$$A_{cl}f_{c(cl)} = A_{ol}f_{c(ol)}$$

The gain-bandwidth product is always equal to the frequency at which the op-amp's open-loop gain is unity (unity-gain bandwidth).¹

$$A_{cl}f_{c(cl)} = \text{unity-gain bandwidth} \quad (7-6)$$

EXAMPLE 7–5

Determine the bandwidth of each of the amplifiers in Figure 7–9. Both op-amps have an open-loop gain of 100 dB and a unity-gain bandwidth of 3 MHz.

SOLUTION

(a) For the noninverting amplifier in Figure 7–9(a), the closed-loop gain is

$$A_{cl(NI)} = \frac{R_f}{R_i} + 1 = \frac{220 \text{ k}\Omega}{3.3 \text{ k}\Omega} + 1 = 67.7$$

Use Equation (7–6) and solve for $f_{c(cl)}$ (where $f_{c(cl)} = BW_{cl}$).

$$f_{c(cl)} = BW_{cl} = \frac{\text{unity-gain BW}}{A_{cl}}$$

$$BW_{cl} = \frac{3 \text{ MHz}}{67.7} = \mathbf{44.3 \text{ kHz}}$$

¹Technically speaking, this equation is true only for noninverting configurations. Other cases are discussed in the lab manual.

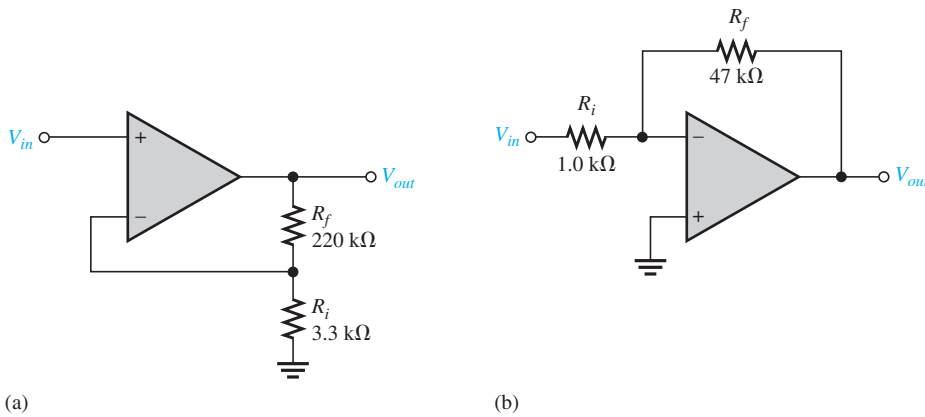


FIGURE 7-9

(b) For the inverting amplifier in Figure 7-9(b), the closed-loop gain is

$$A_{cl(i)} = -\frac{R_f}{R_i} = -\frac{47 \text{ k}\Omega}{1.0 \text{ k}\Omega} = -47$$

Using the absolute value of $A_{cl(i)}$, the closed-loop bandwidth is

$$BW_{cl} = \frac{3 \text{ MHz}}{47} = \mathbf{63.8 \text{ kHz}}$$

PRACTICE EXERCISE

Determine the bandwidth of each of the amplifiers in Figure 7-9. Both op-amps have an A'_{ol} of 90 dB and a unity-gain bandwidth of 2 MHz.

MULTISIM



Open file F07-09 found on the companion website. This simulation demonstrates the effect that closed-loop voltage gain has the bandwidth of operational amplifiers.

SECTION 7-3 CHECKUP

1. Is the closed-loop gain always less than the open-loop gain?
2. A certain op-amp is used in a feedback configuration having a gain of 30 and a bandwidth of 100 kHz. If the external resistor values are changed to increase the gain to 60, what is the new bandwidth?
3. What is the unity-gain bandwidth of the op-amp in Question 2?

7-4 POSITIVE FEEDBACK AND STABILITY

Stability is a consideration when using op-amps. Stable operation means that the op-amp does not oscillate under any condition. Instability produces oscillations, which are unwanted voltage swings on the output when there is no signal present on the input, or in response to noise or transient voltages on the input. This section may be treated as optional.

After completing this section, you should be able to

- Discuss positive feedback and stability in op-amp circuits
- Define *positive feedback*
- Define *loop gain*
- Define *phase margin* and discuss its importance
- Determine if an op-amp circuit is stable
- Summarize the criteria for stability

Positive Feedback

To understand stability, you must first examine instability and its causes. As you know, with negative feedback, the signal fed back to the input of an amplifier is out of phase with the input signal, thus subtracting from it and effectively reducing the voltage gain. As long as the feedback is negative, the amplifier is stable.

When the signal fed back from output to input is in phase with the input signal, a **positive feedback** condition exists and the amplifier can oscillate. That is, positive feedback occurs when the total phase shift through the op-amp and feedback network is 360° , which is equivalent to no phase shift (0°).

Loop Gain

For instability to occur, (a) there must be positive feedback, and (b) the loop gain of the closed-loop amplifier must be greater than 1. The **loop gain** of a closed-loop amplifier is defined to be the op-amp's open-loop gain times the attenuation of the feedback network.

$$\text{Loop gain} = A_{ol}B \quad (7-7)$$

Phase Margin

Notice that for each amplifier configuration in Figure 7-10, the feedback loop is connected to the inverting input. There is an inherent phase shift of 180° because of the *inversion* between

 


FIGURE 7-10 Feedback-loop phase shift.

input and output. Additional phase shift (ϕ_{tot}) is produced by the RC lag networks (not shown) within the amplifier. So the total phase shift around the loop is $180^\circ + \phi_{tot}$.

The **phase margin**, ϕ_{pm} , is the amount of additional phase shift required to make the total phase shift around the loop 360° (360° is equivalent to 0°).

$$180^\circ + \phi_{tot} + \phi_{pm} = 360^\circ$$

$$\phi_{pm} = 180^\circ - |\phi_{tot}| \quad (7-8)$$

If the phase margin is positive, the total phase shift is less than 360° and the amplifier is stable. If the phase margin is zero or negative, then the amplifier is potentially unstable because the signal fed back can be in phase with the input. As you can see from Equation (7-8), when the total lag network phase shift (ϕ_{tot}) equals or exceeds 180° , then the phase margin is 0° or negative and an unstable condition exists, which would cause the amplifier to oscillate.

Stability Analysis

Since most op-amp configurations use a loop gain greater than 1 ($A_{ol}B > 1$), the criteria for stability are based on the phase angle of the internal lag networks. As previously mentioned, operational amplifiers are composed of multiple stages, each of which has a critical frequency. For compensated op-amps, only one critical frequency is dominant, and stability due to the feedback is not a problem. Stability problems generally manifest themselves as unwanted oscillations. Feedback stability occurs near the unity-gain frequency for the op-amp.

To illustrate the concept of feedback **stability**, we will use an uncompensated three-stage op-amp with an open-loop response as shown in the Bode plot of Figure 7-11. For this case, there are three different critical frequencies, which indicate three internal RC lag networks. At the first critical frequency, f_{c1} , the gain begins rolling off at -20 dB/decade; when the second critical frequency, f_{c2} , is reached, the gain decreases at -40 dB/decade; and when the third critical frequency, f_{c3} , is reached, the gain drops at -60 dB/decade.

 


FIGURE 7-11 Bode plot of example of three-stage op-amp response.

To analyze an uncompensated closed-loop amplifier for stability, the phase margin must be determined. A positive phase margin will indicate that the amplifier is stable for a given value of closed-loop gain. Three example cases will be considered in order to demonstrate the conditions for instability.

CASE 1 The closed-loop gain intersects the open-loop response on the -20 dB/decade slope, as shown in Figure 7–12. The midrange closed-loop gain is 106 dB, and the closed-loop critical frequency is 5 kHz. If we assume that the amplifier is not operated out of its midrange, the maximum phase shift for the 106 dB amplifier occurs at the highest midrange frequency (in this case, 5 kHz). The total phase shift at this frequency due to the three lag networks is calculated as follows:

$$\phi_{tot} = -\tan^{-1}\left(\frac{f}{f_{c1}}\right) - \tan^{-1}\left(\frac{f}{f_{c2}}\right) - \tan^{-1}\left(\frac{f}{f_{c3}}\right)$$

where $f = 5$ kHz, $f_{c1} = 1$ kHz, $f_{c2} = 10$ kHz, and $f_{c3} = 100$ kHz. Therefore,

$$\begin{aligned}\phi_{tot} &= -\tan^{-1}\left(\frac{5 \text{ kHz}}{1 \text{ kHz}}\right) - \tan^{-1}\left(\frac{5 \text{ kHz}}{10 \text{ kHz}}\right) - \tan^{-1}\left(\frac{5 \text{ kHz}}{100 \text{ kHz}}\right) \\ &= -78.7^\circ - 26.6^\circ - 2.9^\circ = -108.1^\circ\end{aligned}$$

 


FIGURE 7–12 Case where closed-loop gain intersects open-loop gain on -20 dB/decade slope (stable operation).

The phase margin, ϕ_{pm} , is

$$\phi_{pm} = 180^\circ - |\phi_{tot}| = 180^\circ - 108.1^\circ = +71.9^\circ$$

The phase margin is positive, so the amplifier is stable for all frequencies in its midrange. In general, an amplifier is stable for all midrange frequencies if its closed-loop gain intersects the open-loop response curve on a -20 dB/decade slope.

CASE 2 The closed-loop gain is lowered to where it intersects the open-loop response on the -40 dB/decade slope, as shown in Figure 7–13. The midrange closed-loop gain in this case is 80 dB, and the closed-loop critical frequency is approximately 30 kHz. The total phase shift at $f = 30$ kHz due to the three lag networks is calculated as follows:

$$\begin{aligned}\phi_{tot} &= -\tan^{-1}\left(\frac{30 \text{ kHz}}{1 \text{ kHz}}\right) - \tan^{-1}\left(\frac{30 \text{ kHz}}{10 \text{ kHz}}\right) - \tan^{-1}\left(\frac{30 \text{ kHz}}{100 \text{ kHz}}\right) \\ &= -88.1^\circ - 71.6^\circ - 16.7^\circ = -176.4^\circ\end{aligned}$$

 


FIGURE 7-13 Case where closed-loop gain intersects open-loop gain on -40 dB/decade slope (marginally stable operation).

The phase margin is

$$\phi_{pm} = 180^\circ - 176.4^\circ = +3.6^\circ$$

The phase margin is positive, so the amplifier is still stable for frequencies in its midrange, but a very slight increase in frequency above f_c would cause it to oscillate. Therefore, it is marginally stable and may oscillate due to other paths. It is very close to instability because instability occurs where $\phi_{pm} = 0^\circ$. As a general rule, a minimum 45° phase margin is recommended to avoid marginal conditions.

CASE 3 The closed-loop gain is further decreased until it intersects the open-loop response on the -60 dB/decade slope, as shown in Figure 7-14. The midrange closed-loop

 


FIGURE 7-14 Case where closed-loop gain intersects open-loop gain on -60 dB/decade slope (unstable operation).

gain in this case is 18 dB, and the closed-loop critical frequency is 500 kHz. The total phase shift at $f = 500$ kHz due to the three lag networks is

$$\begin{aligned}\phi_{tot} &= -\tan^{-1}\left(\frac{500 \text{ kHz}}{1 \text{ kHz}}\right) - \tan^{-1}\left(\frac{500 \text{ kHz}}{10 \text{ kHz}}\right) - \tan^{-1}\left(\frac{500 \text{ kHz}}{100 \text{ kHz}}\right) \\ &= -89.9^\circ - 88.9^\circ - 78.7^\circ = -257.5^\circ\end{aligned}$$

The phase margin is

$$\phi_{pm} = 180^\circ - 257.5^\circ = -77.5^\circ$$

Here the phase margin is negative and the amplifier is unstable at the upper end of its midrange.

SUMMARY OF STABILITY CRITERIA The stability analysis of the three example cases has demonstrated that an amplifier's closed-loop gain must intersect the open-loop gain curve on a -20 dB/decade slope to ensure stability for all of its midrange frequencies. If the closed-loop gain is lowered to a value that intersects on a -40 dB/decade slope, then marginal stability or complete instability can occur. In the previous situations (Cases 1, 2, and 3), the closed-loop gain should be greater than 72 dB.

If the closed-loop gain intersects the open-loop response on a -60 dB/decade slope, instability will definitely occur at some frequency within the amplifier's midrange unless a specially designed feedback network is used. Therefore, to ensure stability for all of the midrange frequencies, an op-amp must be operated at a closed-loop gain such that the roll-off rate beginning at its dominant critical frequency does not exceed -20 dB/decade.

Troubleshooting Unwanted Oscillations

The stability problems mentioned in this section can be brought under control, even in the case of a negative phase margin (Case 3), by specially designed feedback networks. A lead network in the feedback path can be used to increase the phase margin and thus increase the stability. In some cases, a complicated feedback network with an amplifier or other active element is added to a design to increase stability.

Not all stability problems are due to the feedback network. If oscillations are not near the unity-gain frequency of the op-amp, the feedback loop is probably not the culprit. Causes of oscillations can include the presence of an external feedback path, a grounding problem, or an extraneous noise signal coupled into the power supply lines. When oscillations are a problem, a simple test is to increase the gain and see if they disappear. (This means the closed-loop gain will intersect the open-loop gain at a higher point.) If the oscillations persist, the problem may be something other than a negative phase margin.

To eliminate unwanted oscillations, check ground paths (try to use single-point grounding), add bypass capacitors to the supply voltages, and try to eliminate extraneous capacitive coupling paths to the input. A coupling path may not be obvious but can be due to a protoboard, especially if it has no ground plane, or may be caused by long leads in the circuit (remember that wires have capacitance). Power supply noise can produce feedback in the amplifier that can result in oscillations. At low frequencies, a simple bypass capacitor ($1 \mu\text{F}$ to $10 \mu\text{F}$ tantalum) may be all that is necessary to solve the problem. At high frequencies, a single bypass capacitor may have a self-resonance, requiring the addition of a secondary bypass capacitor.

Occasionally, oscillations are due to interference from nearby sources and may require shielding. It is also possible to induce oscillations when a low-level signal shares a common ground path with a high-level signal or because of long leads in the circuit layout. Try reconstructing the circuit with shorter leads, paying attention to ground paths and making sure a ground plane is present, if possible.

Noise in Systems

Many systems share power supplies between various assemblies. The longer runs of power supply cables are vulnerable to noise pickup and are conductive paths for noise. As mentioned in this section, power supply leads should have 0.1 to 1 μF tantalum capacitors installed at every circuit board and assembly at the entry point. On circuit boards, every 3 or 4 ICs should also have bypass capacitors on the supply lines. In some systems, the designer will install a separate regulator circuit in each board, to help isolate the main power supply. This is a simple modification but can cure conductive noise problems.

Systems such as radar systems have high power in the same system as sensitive receiver circuits. To avoid noise problems in these systems, it is important to isolate high power signals and utility cables from low level signal lines. Covers and shields should be checked and kept in place, both for safety and to avoid radiated noise. In many systems, electromagnetic shielding gaskets are used on doors and enclosures to block a path for electromagnetic interference (EMI). These shields are useless if a door or enclosure is left ajar, so it is important to maintain good housekeeping practices.



FIGURE SN7-1 Radio-frequency gasket material for EMI protection. (Courtesy of Leader Tech, Tampa, FL.)

SYSTEM NOTE**SECTION 7-4 CHECKUP**

- Under what feedback condition can an amplifier oscillate?
- How much can the phase shift of an amplifier's internal RC network be before instability occurs? What is the phase margin at the point where instability begins?
- What is the maximum roll-off rate of the open-loop gain of an op-amp for which the device will still be stable?

7-5 OP-AMP COMPENSATION

The last section demonstrated that instability can occur when an op-amp's response has roll-off rates exceeding -20 dB/decade and the op-amp is operated in a closed-loop configuration having a gain curve that intersects a higher roll-off rate portion of the open-loop response. In situations like those examined in the last section, the closed-loop voltage gain is restricted to very high values. In many applications, lower values of closed-loop gain are necessary or desirable. To allow op-amps to be operated at low closed-loop gain, phase lag compensation is required. This section may be treated as optional.


After completing this section, you should be able to

- Explain op-amp phase compensation
- Describe phase-lag compensation
- Explain a compensating circuit
- Apply single-capacitor compensation
- Apply feedforward compensation

Phase Lag Compensation

As you have seen, the cause of instability is excessive phase shift through an op-amp's internal lag networks. When these phase shifts equal or exceed 180° , the amplifier can oscillate. **Compensation** is used to either eliminate open-loop roll-off rates greater than -20 dB/decade or extend the -20 dB/decade rate to a lower gain. These concepts are illustrated in Figure 7-15.


FIGURE 7-15 Bode plot illustrating effect of phase compensation on open-loop gain of typical op-amp.

 

Compensating Network

There are two basic methods of compensation for integrated circuit op-amps: internal and external. In either case an RC network is added. The basic compensating action is as follows. Consider first the RC network shown in Figure 7-16(a). At low frequencies where the reactance of the compensating capacitor, X_{C_c} , is extremely large, the output voltage approximately equals the input voltage. When the frequency reaches its critical value, $f_c = 1/[2\pi(R_1 + R_2)C_c]$, the output voltage decreases at -20 dB/decade. This roll-off rate continues until $X_{C_c} \cong 0$, at which point the output voltage levels off to a value determined by R_1 and R_2 , as indicated in Figure 7-16(b). This is the principle used in the phase compensation of an op-amp.

FIGURE 7-16 Basic compensating network action.

 

To see how a compensating network changes the open-loop response of an op-amp, refer to Figure 7-17. This diagram represents a two-stage op-amp. The individual stages are within the color-shaded blocks along with the associated lag networks. A compensating network is shown connected at point A on the output of stage 1.

The critical frequency of the compensating network is set to a value less than the dominant (lowest) critical frequency of the internal lag networks. This causes the -20 dB/decade

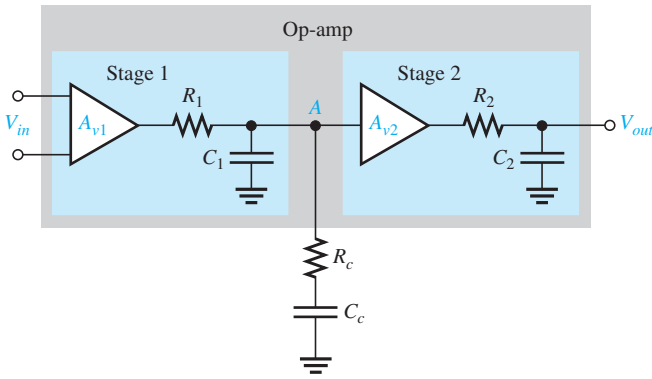


FIGURE 7-17 Representation of op-amp with compensation.

roll-off to begin at the compensating network’s critical frequency. The roll-off of the compensating network continues up to the critical frequency of the dominant lag network. At this point, the response of the compensating network levels off, and the -20 dB/decade roll-off of the dominant lag network takes over. The net result is a shift of the open-loop response to the left, thus reducing the bandwidth, as shown in Figure 7-18a. The response curve of the compensating network is shown in proper relation to the overall open-loop response in Figure 7-18(b).


 


FIGURE 7-18 Example of compensated op-amp frequency response.

 


EXAMPLE 7-6

A certain op-amp has the open-loop response in Figure 7-19. As you can see, the lowest closed-loop gain for which stability is assured is approximately 40 dB (where the closed-loop gain line still intersects the -20 dB/decade slope). In a particular application, a 20 dB closed-loop gain is required.

- (a) Determine the critical frequency for the compensating network.
- (b) Sketch the ideal response curve for the compensating network.
- (c) Sketch the total ideal compensated open-loop response.


FIGURE 7-19 Original open-loop response.

 


SOLUTION

- (a) The gain must be dropped so that the -20 dB/decade roll-off extends down to 20 dB rather than to 40 dB. To achieve this, the midrange open-loop gain must be made to roll off a decade sooner. Therefore, the critical frequency of the compensating network must be 10 Hz.
- (b) The roll-off of the compensating network must end at 100 Hz, as shown in Figure 7-20(a).
- (c) The total open-loop response resulting from compensation is shown in Figure 7-20(b).

FIGURE 7-20

 

(a) Compensating network response

 

(b) Compensated open-loop response

PRACTICE EXERCISE

In this example, what is the uncompensated bandwidth? What is the compensated bandwidth?

Extent of Compensation

A larger compensating capacitor will cause the open-loop roll-off to begin at a lower frequency and thus extend the -20 dB/decade roll-off to lower gain levels, as shown in Figure 7-21(a). With a sufficiently large compensating capacitor, an op-amp can be made unconditionally stable, as illustrated in Figure 7-21(b), where the -20 dB/decade slope is extended all the way down to unity gain. This is normally the case when internal compensation is provided by the manufacturer. An internally, fully compensated op-amp can be used for any value of closed-loop gain and remain stable. The 741 is an example of an internally fully compensated device.

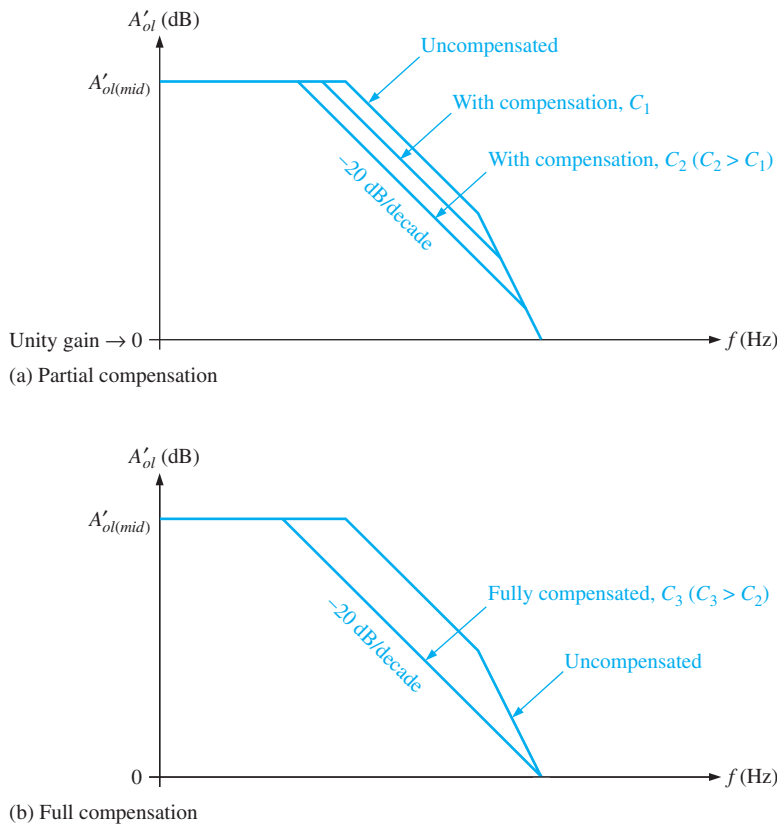


FIGURE 7-21 Extent of compensation.

A disadvantage of internally fully compensated op-amps is that bandwidth is sacrificed; thus the slew rate is decreased. Therefore, many IC op-amps have provisions for external compensation. Figure 7-22 shows typical package layouts of an LM101A op-amp with pins available for external compensation with a small capacitor. With provisions for external connections, just enough compensation can be used for a given application without sacrificing more performance than necessary.

Single-Capacitor Compensation

As an example of compensating an IC op-amp, a capacitor C_1 is connected to pins 1 and 8 of an LM101A in an inverting amplifier configuration, as shown in Figure 7-23(a). Part (b) of the figure shows the open-loop frequency response curves for two values of C_1 . The 3 pF compensating capacitor produces a unity-gain bandwidth approaching 10 MHz.

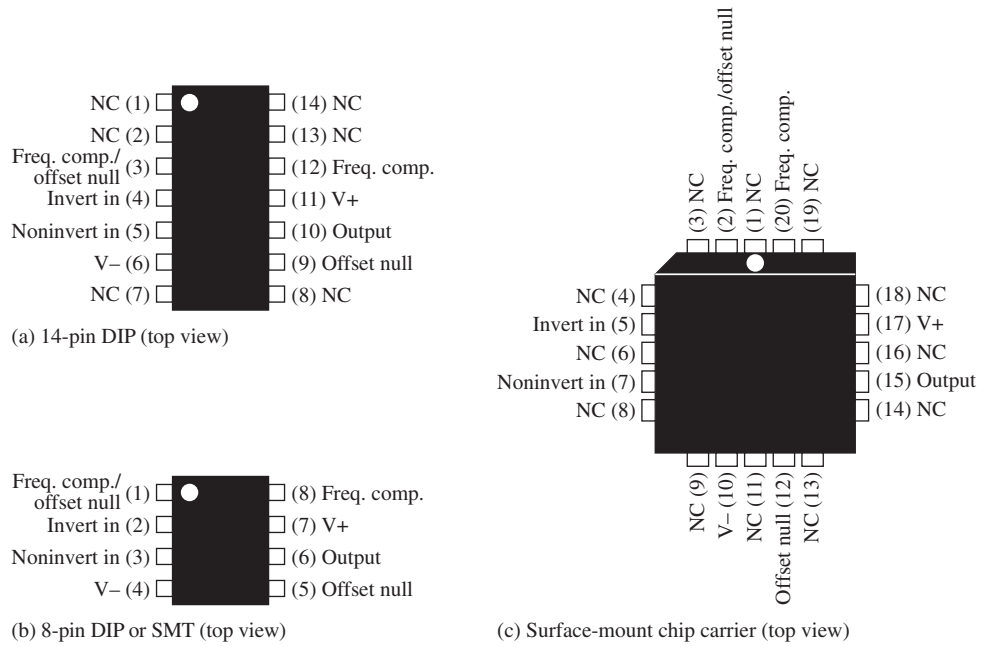


FIGURE 7-22 Typical op-amp packages.

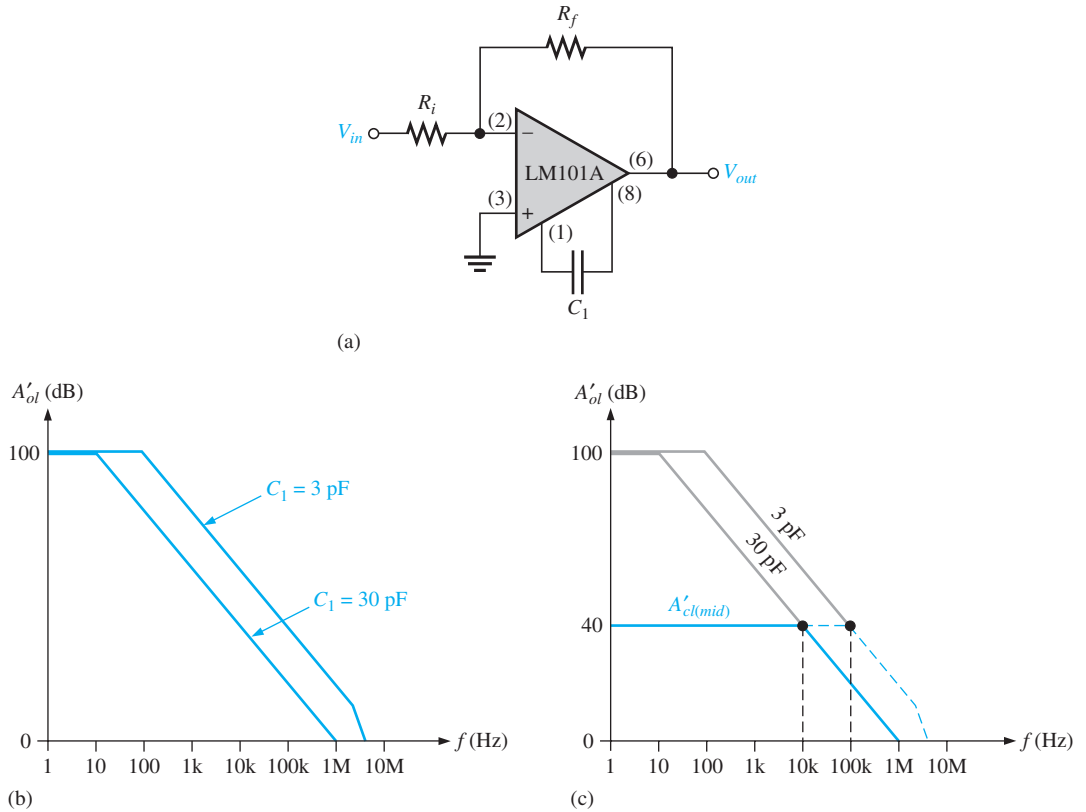


FIGURE 7-23 Example of single-capacitor compensation of an LM101A op-amp.

Notice that the -20 dB/decade slope extends to a very low gain value. When C_1 is increased ten times to 30 pF, the bandwidth is reduced by a factor of ten. Notice that the -20 dB/decade slope now extends through unity gain.


When the op-amp is used in a closed-loop configuration, as in Figure 7-23(c), the useful frequency range depends on the compensating capacitor. For example, with a

closed-loop gain of 40 dB as shown in part (c), the bandwidth is approximately 10 kHz for $C_1 = 30$ pF and increases to approximately 100 kHz when C_1 is decreased to 3 pF.


Feedforward Compensation

Another method of phase compensation is called **feedforward**. This type of compensation results in less bandwidth reduction than the method previously discussed. The basic concept is to bypass the internal input stage of the op-amp at high frequencies and drive the higher-frequency second stage, as shown in Figure 7–24.

Feedforward compensation of an LM101A is shown in Figure 7–25(a). The feedforward capacitor C_1 is connected from the inverting input to the compensating terminal. A small capacitor is needed across R_f to ensure stability. The Bode plot in Figure 7–25(b) shows the feedforward compensated response and the standard compensated response that was discussed previously. The use of feedforward compensation is restricted to the inverting amplifier configuration. Other compensation methods are also used. Often, recommendations are provided by the manufacturer on the data sheet.

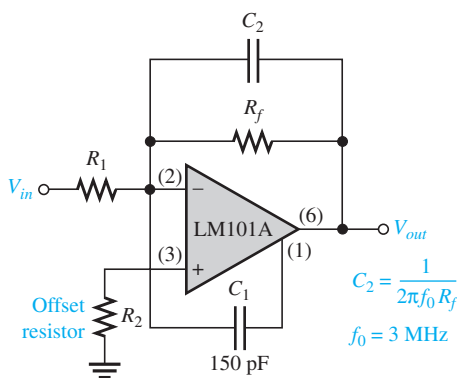

 (a) Manufacturers' recommended configuration



(b) Response

FIGURE 7–25 Feedforward compensation of an LM101A op-amp and the response curves.

 


FIGURE 7–24 Feedforward compensation showing high-frequency bypassing of first stage.

SECTION 7–5 CHECKUP

1. What is the purpose of phase compensation?
2. What is the main difference between internal and external compensation?
3. When you compensate an amplifier, does the bandwidth increase or decrease?

SUMMARY

- Open-loop gain is the voltage gain of an op-amp without feedback.
- Closed-loop gain is the voltage gain of an op-amp with negative feedback.
- The closed-loop gain is always less than the open-loop gain.
- The midrange gain of an op-amp extends down to dc.
- Above the critical frequency, the gain of an op-amp decreases.
- The internal RC lag networks that are inherently part of the amplifier stages cause the gain to roll off as frequency goes up.
- The internal RC lag networks also cause a phase shift between input and output signals.
- Negative feedback lowers the gain and increases the bandwidth.

- The product of gain and bandwidth is constant for a compensated op-amp.
- The gain-bandwidth product equals the frequency at which unity voltage gain occurs.
- Positive feedback occurs when the total phase shift through the op-amp (including 180° inversion) and feedback network is 0° (equivalent to 360°) or more.
- The phase margin is the amount of additional phase shift required to make the total phase shift around the loop 360°.
- When the closed-loop gain of an op-amp intersects the open-loop response curve on a –20 dB/decade (–6 dB/octave) slope, the amplifier is stable.
- When the closed-loop gain intersects the open-loop response curve on a slope greater than –20 dB/decade, the amplifier can be either marginally stable or unstable.
- A minimum phase margin of 45° is recommended to provide a sufficient safety factor for stable operation.
- A fully compensated op-amp has a –20 dB/decade roll-off all the way down to unity gain.
- Compensation reduces bandwidth and increases slew rate.
- Internally compensated op-amps such as the 741 are available. These are usually fully compensated with a large sacrifice in bandwidth.
- Externally compensated op-amps such as LM101A are available. External compensating networks can be connected to specified pins, and the compensation can be tailored to a specific application. In this way, bandwidth and slew rate are not degraded more than necessary.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Bandwidth The range of frequencies between the lower critical frequency and the upper critical frequency.

Loop gain An op-amp's open-loop voltage gain times the attenuation of the feedback network.

Phase shift The relative angular displacement of a time-varying function relative to a reference.

Phase margin The difference between the total phase shift through an amplifier and 180°; the additional amount of phase shift that can be allowed before instability occurs.

Positive feedback The return of a portion of the output signal to the input such that it reinforces the output. This output signal is in phase with the input signal.

Stability A condition in which an amplifier circuit does not oscillate.

KEY FORMULAS

$$(7-1) \quad BW = f_{cu} \quad \text{Op-amp bandwidth}$$

$$(7-2) \quad A_{ol} = \frac{A_{ol(mid)}}{\sqrt{1 + f^2/f_c^2}} \quad \text{Open-loop gain}$$

$$(7-3) \quad \phi = -\tan^{-1}\left(\frac{f}{f_c}\right) \quad \text{RC phase shift}$$

$$(7-4) \quad f_{c(cl)} = f_{c(ol)}(1 + BA_{ol(mid)}) \quad \text{Closed-loop critical frequency}$$

$$(7-5) \quad BW_{cl} = BW_{ol}(1 + BA_{ol(mid)}) \quad \text{Closed-loop bandwidth}$$

$$(7-6) \quad A_{cl}f_{c(cl)} = \text{unity-gain bandwidth}$$

$$(7-7) \quad \text{Loop gain} = A_{ol}B$$


$$(7-8) \quad \phi_{pm} = 180^\circ - |\phi_{tot}| \quad \text{Phase margin}$$

SELF-TEST

Answers are at the end of the chapter.

- The open-loop gain of an op-amp is always
 - less than the closed-loop gain
 - equal to the closed-loop gain
 - greater than the closed-loop gain
 - a very stable and constant quantity for a given type of op-amp
- The bandwidth of an ac amplifier having a lower critical frequency of 1 kHz and an upper critical frequency of 10 kHz is
 - 1 kHz
 - 9 kHz
 - 10 kHz
 - 11 kHz
- The bandwidth of a dc amplifier having an upper critical frequency of 100 kHz is
 - 100 kHz
 - unknown
 - infinity
 - 0 kHz
- The midrange open-loop gain of an op-amp
 - extends from the lower critical frequency to the upper critical frequency
 - extends from 0 Hz to the upper critical frequency
 - rolls off at -20 dB/decade beginning at 0 Hz
 - answers (b) and (c)
- The frequency at which the open-loop gain is equal to one is called
 - the upper critical frequency
 - the cutoff frequency
 - the notch frequency
 - the unity-gain frequency
- Phase shift through an op-amp is caused by
 - the internal RC networks
 - the external RC networks
 - the gain roll-off
 - negative feedback
- Each RC network in an op-amp
 - causes the gain to roll off at -6 dB/octave
 - causes the gain to roll off at -20 dB/decade
 - reduces the midrange gain by 3 dB
 - answers (a) and (b)
- When negative feedback is used, the gain-bandwidth product of an op-amp
 - increases
 - decreases
 - stays the same
 - fluctuates
- If a certain noninverting op-amp has a midrange open-loop gain of 200,000 and a unity-gain frequency of 5 MHz, the gain-bandwidth product is
 - 200,000 Hz
 - 5,000,000 Hz
 - 1×10^{12} Hz
 - not determinable from the information given
- If a certain noninverting op-amp has a closed-loop gain of 20 and an upper critical frequency of 10 MHz, the gain-bandwidth product is
 - 200 MHz
 - 10 MHz
 - the unity-gain frequency
 - answers (a) and (c)
- Positive feedback occurs when
 - the output signal is fed back to the input in-phase with the input signal
 - the output signal is fed back to the input out-of-phase with the input signal
 - the total phase shift through the op-amp and feedback network is 360°
 - answers (a) and (c)
- For a closed-loop op-amp circuit to be unstable,
 - there must be positive feedback
 - the loop gain must be greater than 1
 - the loop gain must be less than 1
 - answers (a) and (b)
- The amount of additional phase shift required to make the total phase shift around a closed loop equal to zero is called
 - the unity-gain phase shift
 - phase margin
 - phase lag
 - phase bandwidth

 14. For a given value of closed-loop gain, a positive phase margin indicates
- an unstable condition
 - too much phase shift
 - a stable condition
 - nothing
15. The purpose of phase-lag compensation is to
- make the op-amp stable at very high values of gain
 - make the op-amp stable at low values of gain
 - reduce the unity-gain frequency
 - increase the bandwidth



TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 7–29(a).

- If R_f is 100 k Ω instead of the specified 150 k Ω ,
 - For a low-frequency input signal, the gain will
 - increase
 - decrease
 - not change
 - The bandwidth will
 - increase
 - decrease
 - not change
 - The gain-bandwidth product will
 - increase
 - decrease
 - not change
- If the op-amp has an $f_{c(ol)}$ of 200 Hz instead of the specified 150 Hz,
 - The bandwidth will
 - increase
 - decrease
 - not change
 - For a low-frequency input signal, the gain will
 - increase
 - decrease
 - not change

Refer to Figure 7–25(a).

- Assume an input coupling capacitor for this circuit is specified to be 2.2 μF but instead a 0.22 μF capacitor is installed by mistake.
 - The lower cutoff frequency will
 - increase
 - decrease
 - not change
 - The upper cutoff frequency will
 - increase
 - decrease
 - not change
- If C_2 is open,
 - The stability will
 - increase
 - decrease
 - not change
- If R_f is larger than the specified value,
 - The bandwidth will
 - increase
 - decrease
 - not change
 - The gain-bandwidth product will
 - increase
 - decrease
 - not change
- If the compensating capacitor C_1 is open,
 - The bandwidth will
 - increase
 - decrease
 - not change
 - The stability will
 - increase
 - decrease
 - not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 7-1 Basic Concepts

- The midrange open-loop gain of a certain op-amp is 120 dB. Negative feedback reduces this gain by 50 dB. What is the closed-loop gain?
- The upper critical frequency of an op-amp's open-loop response is 200 Hz. If the midrange gain is 175,000, what is the ideal gain at 200 Hz? What is the actual gain? What is the op-amp's open-loop bandwidth?
- An RC lag network has a critical frequency of 5 kHz. If the resistance value is 1.0 kΩ, what is X_C when $f = 3$ kHz?
- Determine the attenuation of an RC lag network with $f_c = 12$ kHz for each of the following frequencies.
 (a) 1 kHz (b) 5 kHz (c) 12 kHz (d) 20 kHz (e) 100 kHz
- The midrange open-loop gain of a certain op-amp is 80,000. If the open-loop critical frequency is 1 kHz, what is the open-loop gain at each of the following frequencies?
 (a) 100 Hz (b) 1 kHz (c) 10 kHz (d) 1 MHz
- Determine the phase shift through each network in Figure 7-26 at a frequency of 2 kHz.

 


FIGURE 7-26

- An RC lag network has a critical frequency of 8.5 kHz. Determine the phase for each frequency and plot a graph of its phase angle versus frequency.
 (a) 100 Hz (b) 400 Hz (c) 850 Hz (d) 8.5 kHz (e) 25 kHz (f) 85 kHz

SECTION 7-2 Op-Amp Open-Loop Response

- A certain op-amp has three internal amplifier stages with midrange gains of 30 dB, 40 dB, and 20 dB. Each stage also has a critical frequency associated with it as follows: $f_{c1} = 600$ Hz, $f_{c2} = 50$ kHz, and $f_{c3} = 200$ kHz.
 (a) What is the midrange open-loop gain of the op-amp, expressed in dB?
 (b) What is the total phase shift through the amplifier, including inversion, when the signal frequency is 10 kHz?
- What is the gain roll-off rate in Problem 8 between the following frequencies?
 (a) 0 Hz and 600 Hz (b) 600 Hz and 50 kHz
 (c) 50 kHz and 200 kHz (d) 200 kHz and 1 MHz

SECTION 7-3 Op-Amp Closed-Loop Response

- A certain amplifier has an open-loop gain in midrange of 180,000 and an open-loop critical frequency of 1500 Hz. If the attenuation of the feedback path is 0.015, what is the closed-loop bandwidth?
- Determine the midrange gain in dB of each amplifier in Figure 7-27. Are these open-loop or closed-loop gains?
- Given that $f_{c(ol)} = 750$ Hz, $A'_{ol} = 89$ dB, and $f_{c(cl)} = 5.5$ kHz, determine the closed-loop gain in dB.
- What is the unity-gain bandwidth in Problem 12?
- For each amplifier in Figure 7-28, determine the closed-loop gain and bandwidth. The op-amps in each circuit exhibit an open-loop gain of 125 dB and a unity-gain bandwidth of 2.8 MHz.
- Which of the amplifiers in Figure 7-29 has the smaller bandwidth?

 


FIGURE 7-27

 


FIGURE 7-28

 


FIGURE 7-29

SECTION 7-4 Positive Feedback and Stability

- 16. It has been determined that the op-amp circuit in Figure 7-30 has three internal critical frequencies as follows: 1.2 kHz, 50 kHz, 250 kHz. If the midrange open-loop gain is 100 dB, is the amplifier configuration stable, marginally stable, or unstable?
- 17. Determine the phase margin for each value of phase lag.
 - (a) 30° (b) 60° (c) 120° (d) 180° (e) 210°
- 18. A certain op-amp has the following internal critical frequencies in its open-loop response: 125 Hz, 25 kHz, and 180 kHz. What is the total phase shift through the amplifier when the signal frequency is 50 kHz?
- 19. Each graph in Figure 7-31 shows both the open-loop and the closed-loop response of a particular op-amp configuration. Analyze each case for stability.

 


FIGURE 7-30

 


FIGURE 7-31

SECTION 7-5 Op-Amp Compensation

- 20. A certain operational amplifier has an open-loop response curve as shown in Figure 7-32. A particular application requires a 30 dB closed-loop midrange gain. In order to achieve a 30 dB gain, compensation must be added because the 30 dB line intersects the uncompensated open-loop gain on the -40 dB/decade slope and, therefore, stability is not assured.
 - (a) Find the critical frequency of the compensating network such that the -20 dB/decade slope is lowered to a point where it intersects the 30 dB gain line.
 - (b) Sketch the ideal response curve for the compensating network.
 - (c) Sketch the total ideal compensated open-loop response.

 


FIGURE 7-32

- 21. The open-loop gain of a certain op-amp rolls off at -20 dB/decade, beginning at $f = 250$ Hz. This roll-off rate extends down to a gain of 60 dB. If a 40 dB closed-loop gain is required, what is the critical frequency for the compensating network?
- 22. Repeat Problem 21 for a closed-loop gain of 20 dB.

ANSWERS TO SECTION CHECKUPS

SECTION 7-1

1. Open-loop gain is without feedback, and closed-loop gain is with negative feedback. Open-loop gain is larger.
2. $BW = 100 \text{ Hz}$
3. A_{ol} decreases.
4. The SPI bus carries digital information. For a PGA, it can select the channel and set the gain from a computer or controller command.

SECTION 7-2

1. $A'_{V(tot)} = 20 \text{ dB} + 30 \text{ dB} = 50 \text{ dB}$
2. $\phi_{tot} = -49^\circ + (-5.2^\circ) = -54.2^\circ$

SECTION 7-3

1. Yes, A_{cl} is always less than A_{ol} .
2. $BW = 3,000 \text{ kHz}/60 = 50 \text{ kHz}$
3. Unity-gain $BW = 3,000 \text{ kHz}/1 = 3 \text{ MHz}$

SECTION 7-4

1. Positive feedback
2. $180^\circ, 0^\circ$
3. -20 dB/decade (-6 dB/octave)

SECTION 7-5

1. Phase compensation increases the phase margin at a given frequency.
2. Internal compensation is full compensation; external compensation can be tailored to maximize bandwidth.
3. Bandwidth decreases.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

7-1 (a) 80,000 (b) 79,900 (c) 6400

7-2 173 Hz

7-3 75 dB; -71.6°

7-4 2.00 MHz

7-5 (a) 29.6 kHz (b) 42.6 kHz

7-6 100 Hz; 10 Hz

ANSWERS TO SELF-TEST

1. (c) 2. (b) 3. (a) 4. (b) 5. (d) 6. (a) 7. (d) 8. (c)
 9. (b) 10. (d) 11. (d) 12. (d) 13. (b) 14. (c) 15. (b)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. decrease 2. increase 3. not change 4. increase
 5. not change 6. increase 7. not change 8. decrease
 9. decrease 10. not change 11. increase 12. decrease

CHAPTER 8

BASIC OP-AMP CIRCUITS

OUTLINE

- 8-1 Comparators
- 8-2 Summing Amplifiers
- 8-3 Integrators and Differentiators
- 8-4 Converters and Other Op-Amp Circuits
- 8-5 Troubleshooting

OBJECTIVES

- Understand the operation of several basic comparator circuits
- Understand the operation of several types of summing amplifiers
- Understand the operation of integrators and differentiators
- Understand the operation of several special op-amp circuits
- Troubleshoot basic op-amp circuits

KEY TERMS

Comparator	Constant-current source
Hysteresis	Current-to-voltage converter
Schmitt trigger	Voltage-to-current converter
Bounding	Peak detector
Summing amplifier	
Integrator	
Differentiator	

INTRODUCTION

In the last two chapters, you learned about the principles, operation, and characteristics of the operational amplifier. Op-amps are used in such a wide variety of applications that it is impossible to cover all of them in one chapter, or even in one book. Therefore, in this chapter, we will examine some of the more fundamental applications to illustrate how versatile the op-amp is and to give you a foundation in basic op-amp circuits.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

8-1 COMPARATORS

Operational amplifiers are often used as nonlinear devices to compare the amplitude of one voltage with another. In this application, the op-amp is used in the open-loop con uration, with the input voltage on one input and a reference voltage on the other.

After completing this section, you should be able to

- Understand the operation of several basic comparator circuits
 - Describe the operation of a zero-level detector
 - Describe the operation of a nonzero-level detector
 - Discuss how input noise affects comparator operation
 - Define *hysteresis*
 - Explain how hysteresis reduces noise effects
 - Describe a Schmitt trigger circuit
 - Describe the operation of bounded comparators
 - Describe the operation of a window comparator
- Discuss applications for comparators in systems including analog-to-digital conversion

Zero-Level Detection

One application of an op-amp used as a **comparator** is to determine when an input voltage exceeds a certain level. Figure 8-1(a) shows a zero-level detector. Notice that the inverting (−) input is grounded to produce a zero level and that the input signal voltage is applied to the noninverting (+) input. Because of the high open-loop voltage gain, a very small difference voltage between the two inputs drives the amplifier into saturation, causing the output voltage to go to its limit.

MULTISIM



Open file F08-01 found on the companion website. This simulation demonstrates the operation of the zero-level detector.

 


FIGURE 8-1 The op-amp as a zero-level detector.

For example, consider an op-amp having $A_{ol} = 100,000$. A voltage difference of only 0.25 mV between the inputs could produce an output voltage of $(0.25 \text{ mV})(100,000) = 25 \text{ V}$ if the op-amp were capable. However, since most op-amps have output voltage limitations of $\pm 15 \text{ V}$ or less, the device would be driven into saturation. For many comparison applications, special op-amp comparators are selected. These ICs are generally uncompensated to maximize speed. In less stringent applications, a general-purpose op-amp works nicely as a comparator.



Figure 8-1(b) shows the result of a sinusoidal input voltage applied to the noninverting input of the zero-level detector. When the sine wave is negative, the output is at its maximum negative level. When the sine wave crosses 0, the amplifier is driven to its opposite state and the output goes to its maximum positive level, as shown. As you can see, the zero-level detector can be used as a squaring circuit to produce a square wave from a sine wave.

Nonzero-Level Detection

The zero-level detector in Figure 8-1 can be modified to detect positive and negative voltages by connecting a fixed reference voltage to the inverting (–) input, as shown in Figure 8-2(a). A more practical arrangement is shown in Figure 8-2(b) using a voltage divider to set the reference voltage as follows:

$$V_{\text{REF}} = \frac{R_2}{R_1 + R_2}(+V) \quad (8-1)$$

where $+V$ is the positive op-amp supply voltage. The circuit in Figure 8-2(c) uses a zener diode to set the reference voltage ($V_{\text{REF}} = V_Z$). As long as the input voltage V_{in} is less than V_{REF} , the output remains at the maximum negative level. When the input voltage exceeds the reference voltage, the output goes to its maximum positive state, as shown in Figure 8-2(d) with a sinusoidal input voltage.

 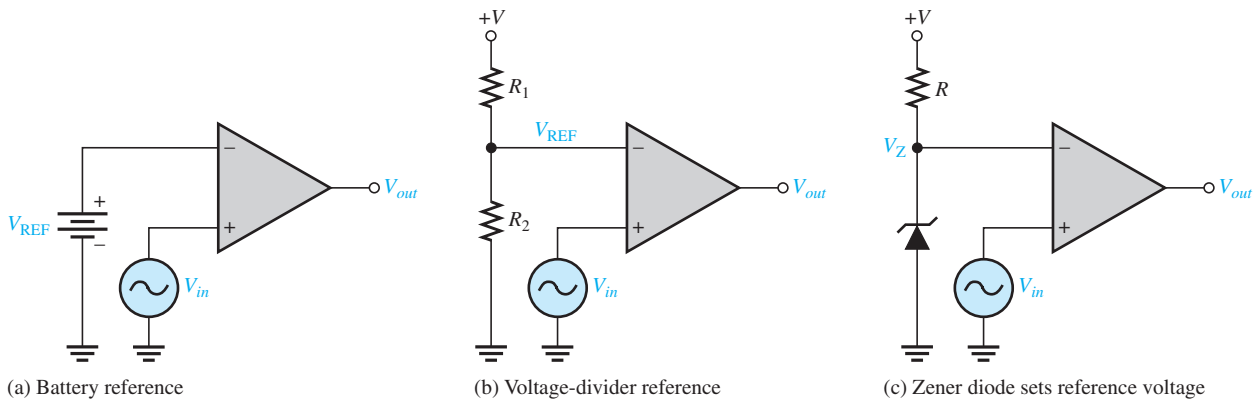

MULTISIM



Open file F08-02 found on the companion website. This simulation demonstrates how a potentiometer can be used to vary the reference voltage of a nonzero-level detector.

FIGURE 8-2 Nonzero-level detectors.

EXAMPLE 8-1

The input signal in Figure 8-3(a) is applied to the comparator circuit in Figure 8-3(b). Make a sketch of the output showing its proper relationship to the input signal. Assume the maximum output levels of the op-amp are ± 12 V.

 


FIGURE 8-3

SOLUTION

The reference voltage is set by R_1 and R_2 as follows:

$$V_{\text{REF}} = \frac{R_2}{R_1 + R_2}(+V) = \frac{1.0 \text{ k}\Omega}{8.2 \text{ k}\Omega + 1.0 \text{ k}\Omega}(+15 \text{ V}) = 1.63 \text{ V}$$

As shown in Figure 8-4, each time the input exceeds +1.63 V, the output voltage switches to its +12 V level, and each time the input goes below +1.63 V, the output switches back to its -12 V level.

 


FIGURE 8-4

PRACTICE EXERCISE*

Determine the reference voltage in Figure 8-3 if $R_1 = 22 \text{ k}\Omega$ and $R_2 = 3.3 \text{ k}\Omega$.

*Answers are at the end of the chapter.

Effects of Input Noise on Comparator Operation

In many practical situations, **noise** (unwanted voltage or current fluctuations) may appear on the input line. This noise voltage becomes superimposed on the input voltage, as shown in Figure 8-5, and can cause a comparator to erratically switch output states.

In order to understand the potential effects of noise voltage, consider a low-frequency sinusoidal voltage applied to the noninverting (+) input of an op-amp comparator used as a zero-level detector, as shown in Figure 8-6(a). Part (b) of the figure shows the input sine wave plus noise and the resulting output. As you can see, when the sine wave approaches 0, the fluctuations due to noise cause the total input to vary above and below 0 several times, thus producing an erratic output voltage.



 


FIGURE 8-5 Sine wave with superimposed noise.

 

(a)

 

(b)

FIGURE 8-6 Effects of noise on comparator circuit.

Reducing Noise Effects with Hysteresis

An erratic output voltage caused by noise on the input occurs because the op-amp comparator switches from its negative output state to its positive output state at the same input voltage level that causes it to switch in the opposite direction, from positive to negative. This unstable condition occurs when the input voltage hovers around the reference voltage, and any small noise fluctuations cause the comparator to switch first one way and then the other.

In order to make the comparator less sensitive to noise, a technique incorporating positive feedback, called **hysteresis**, can be used. Basically, hysteresis means that there is a higher reference level when the input voltage goes from a lower to higher value than when it goes from a higher to a lower value. A good example of hysteresis is a common household thermostat that turns the furnace on at one temperature and off at another.

The two reference levels are referred to as the upper trigger point (UTP) and the lower trigger point (LTP). This two-level hysteresis is established with a positive feedback arrangement, as shown in Figure 8-7. Notice that the noninverting (+) input is connected to a resistive voltage divider such that a portion of the output voltage is fed back to the input. The input signal is applied to the inverting (-) input in this case.

The basic operation of the comparator with hysteresis is as follows and is illustrated in Figure 8-8. Assume that the output voltage is at its positive maximum, $+V_{out(max)}$. The voltage fed back to the noninverting input is V_{UTP} and is expressed as

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)})$$

 


FIGURE 8-7 Comparator with positive feedback for hysteresis.

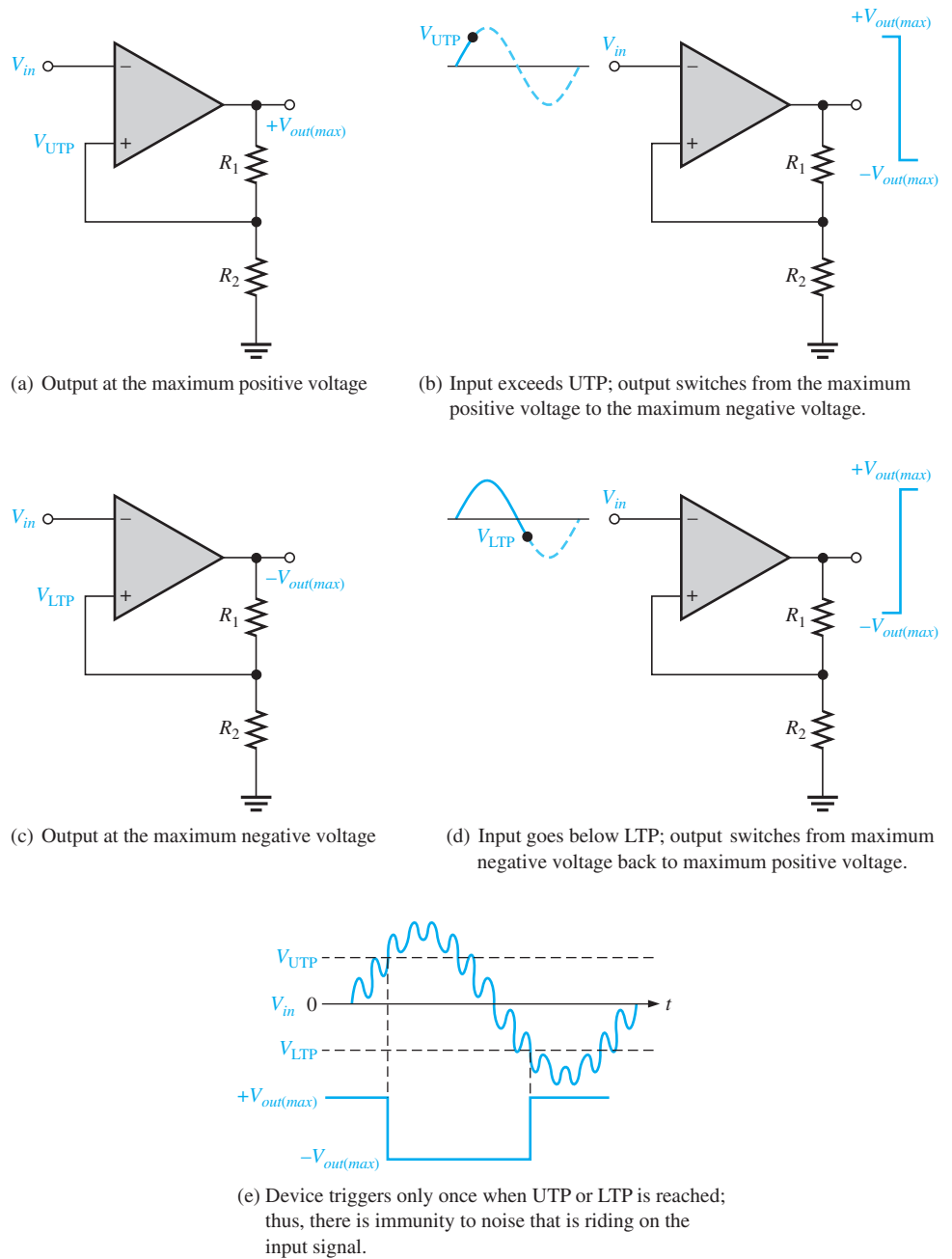


FIGURE 8-8 Operation of a comparator with hysteresis.

When the input voltage V_{in} exceeds V_{UTP} , the output voltage drops to its negative maximum, $-V_{out(max)}$. Now the voltage fed back to the noninverting input is V_{LTP} and is expressed as

$$V_{LTP} = \frac{R_2}{R_1 + R_2}(-V_{out(max)})$$

The input voltage must now fall below V_{LTP} before the device will switch back to its other voltage level. This means that a small amount of noise voltage has no effect on the output, as illustrated by Figure 8-8.

A comparator with hysteresis is sometimes known as a **Schmitt trigger**. The amount of hysteresis is defined by the difference of the two trigger levels.

$$V_{HYS} = V_{UTP} - V_{LTP} \tag{8-2}$$

EXAMPLE 8-2

Determine the upper and lower trigger points and the hysteresis for the comparator circuit in Figure 8-9. Assume that $+V_{out(max)} = +5\text{ V}$ and $-V_{out(max)} = -5\text{ V}$.

 


FIGURE 8-9

SOLUTION

$$V_{UTP} = \frac{R_2}{R_1 + R_2} (+V_{out(max)}) = 0.5(5\text{ V}) = +2.5\text{ V}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} (-V_{out(max)}) = 0.5(-5\text{ V}) = -2.5\text{ V}$$

$$V_{HYS} = V_{UTP} - V_{LTP} = 2.5\text{ V} - (-2.5\text{ V}) = 5\text{ V}$$

PRACTICE EXERCISE

Determine the upper and lower trigger points and the hysteresis in Figure 8-9 for $R_1 = 68\text{ k}\Omega$ and $R_2 = 82\text{ k}\Omega$. The maximum output voltage levels are $\pm 7\text{ V}$.

MULTISIM

Open file F08-09 found on the companion website. This simulation demonstrates the operation of a comparator with hysteresis.

Output Bounding

In some applications, it is necessary to limit the output voltage levels of a comparator to a value less than that provided by the saturated op-amp. A single zener diode can be used as shown in Figure 8-10 to limit the output voltage to the zener voltage in one direction and to the forward diode drop in the other. This process of limiting the output range is called **bounding**.



 


FIGURE 8-10 Comparator with output bounding.

The operation is as follows. Since the anode of the zener is connected to the inverting ($-$) input, it is at virtual ground ($\cong 0\text{ V}$) when it has a conducting path. Therefore, when the output voltage reaches a positive value equal to the zener voltage, it limits at that value, as illustrated in Figure 8-11. When the output switches negative, the zener acts as a regular diode and becomes forward-biased at 0.7 V , limiting the negative output voltage to this value, as shown. Turning the zener around limits the output voltage in the opposite direction.

 

(a) Bounded at a positive value

 

(b) Bounded at a negative value

FIGURE 8–11 Operation of a bounded comparator.

Two zener diodes arranged as in Figure 8–12 limit the output voltage to the zener voltage plus the forward voltage drop (0.7 V) of the forward-biased zener, both positively and negatively, as shown in Figure 8–12.

 


FIGURE 8–12 Double-bounded comparator.

EXAMPLE 8–3

Determine the output voltage waveform for Figure 8–13.

 


FIGURE 8–13

SOLUTION

This comparator has both hysteresis and zener bounding.

The voltage across D_1 and D_2 in either direction is $4.7\text{ V} + 0.7\text{ V} = 5.4\text{ V}$. This is because one zener is always forward-biased with a drop of 0.7 V when the other one is in breakdown.

The voltage at the inverting (–) op-amp input is $V_{out} \pm 5.4$ V. Since the differential voltage is negligible, the voltage at the noninverting (+) op-amp input is also approximately $V_{out} \pm 5.4$ V. Thus,

$$V_{R1} = V_{out} - (V_{out} \pm 5.4 \text{ V}) = \pm 5.4 \text{ V}$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{\pm 5.4 \text{ V}}{100 \text{ k}\Omega} = \pm 54 \mu\text{A}$$

Since the current at the noninverting input is negligible,

$$I_{R2} = I_{R1} = \pm 54 \mu\text{A}$$

$$V_{R2} = R_2 I_{R2} = (47 \text{ k}\Omega)(\pm 54 \mu\text{A}) = \pm 2.54 \text{ V}$$

$$V_{out} = V_{R1} + V_{R2} = \pm 5.4 \text{ V} \pm 2.54 \text{ V} = \pm 7.94 \text{ V}$$

The upper trigger point (UTP) and the lower trigger point (LTP) are as follows:

$$V_{\text{UTP}} = \left(\frac{R_2}{R_1 + R_2} \right) (+V_{out}) = \left(\frac{47 \text{ k}\Omega}{147 \text{ k}\Omega} \right) (+7.94 \text{ V}) = +2.54 \text{ V}$$

$$V_{\text{LTP}} = \left(\frac{R_2}{R_1 + R_2} \right) (-V_{out}) = \left(\frac{47 \text{ k}\Omega}{147 \text{ k}\Omega} \right) (-7.94 \text{ V}) = -2.54 \text{ V}$$

The output waveform for the given input voltage is shown in Figure 8–14.

 


FIGURE 8-14

PRACTICE EXERCISE

Determine the upper and lower trigger points for Figure 8–13 if $R_1 = 150 \text{ k}\Omega$, $R_2 = 68 \text{ k}\Omega$, and the zener diodes are 3.3 V devices.

MULTISIM



Open file F08-13 found on the companion website. This simulation demonstrates the operation of a double-bounded comparator.

Window Comparator

Two individual op-amp comparators arranged as in Figure 8–15 form what is known as a *window comparator*. This circuit detects when an input voltage is between two limits, an upper and a lower, called the “window.”

The upper and lower limits are set by reference voltages designated V_U and V_L . These voltages can be established with voltage dividers, zener diodes, or any type of voltage source. As long as V_{in} is within the window (less than V_U and greater than V_L), the output of each comparator is at its low saturated level. Under this condition, both diodes are reverse-biased and V_{out} is held at zero by the resistor to ground. When V_{in} goes above V_U or below V_L , the output of the associated comparator goes to its high saturated level. This action forward-biases the diode and produces a high-level V_{out} . This is illustrated in Figure 8–16 with V_{in} varying arbitrarily.


 
 


FIGURE 8-15 A basic window comparator.


FIGURE 8-16 Example of window comparator operation.

SYSTEM EXAMPLE 8-1

 

A COMPARATOR APPLICATION: OVER-TEMPERATURE SENSING CIRCUIT

In many types of industrial systems, such as food processing, the temperature of a particular solution must be kept under a certain limit. In this example, we will look at the circuit used to monitor for an over-temperature condition. Figure SE8-1 shows a comparator used in a precision over-temperature sensing circuit to determine when the temperature reaches a certain critical value. The circuit consists of a Wheatstone bridge with the comparator used to detect when the bridge is balanced. One leg of the bridge contains a thermistor (R_1), which is a temperature-sensing resistor with a negative temperature coefficient (its resistance decreases as temperature increases, and vice versa). The potentiometer (R_2) is set at a value equal to the resistance of the thermistor at the critical temperature. At normal temperatures (below critical), R_1 is greater than R_2 , thus creating an unbalanced condition that drives the comparator to its low saturated output level and keeps transistor Q_1 off.

 FIGURE SE8-1

As the temperature increases, the resistance of the thermistor decreases. When the temperature reaches the critical value, R_1 becomes equal to R_2 , and the bridge becomes balanced (since $R_3 = R_4$). At this point the comparator switches to its high saturated output level, turning Q_1 on. This energizes the relay, which can be used to activate an alarm or initiate an appropriate response to the over-temperature condition.

SYSTEM EXAMPLE 8-2

A COMPARATOR APPLICATION: ANALOG-TO-DIGITAL (A/D) CONVERSION

A/D conversion is a common interfacing process often used when a linear *analog* system must provide inputs to a *digital* system. The system described in System Example 7-2 is such a system, which is shown again in Figure SE8-2 with the emphasis on the A/D converter. The data is originally in analog form from a transducer and initially amplified by the PGA, but needs to be processed by a computer. Before sending the data to the computer, it is converted to digital form by the A/D converter. Many methods for A/D conversion are available and some of these will be covered thoroughly in Chapter 14. However, in this discussion, only one type is used to demonstrate the concept used by this system.

The *simultaneous*, or *flash*, method of A/D conversion uses parallel comparators to compare the linear input signal with various reference voltages developed by a voltage divider. When the input voltage exceeds the reference voltage for a given comparator, a high level is produced on that comparator's output. Figure SE8-3 shows an analog-to-digital converter (ADC) that produces three-digit binary numbers on its output, which represent

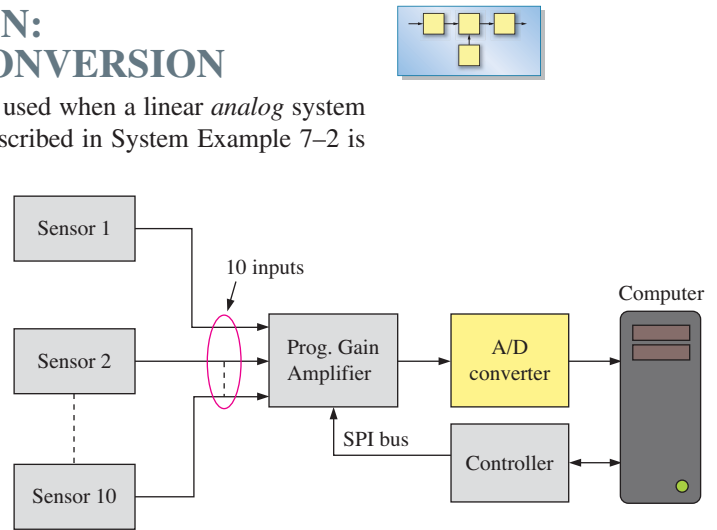


FIGURE SE8-2

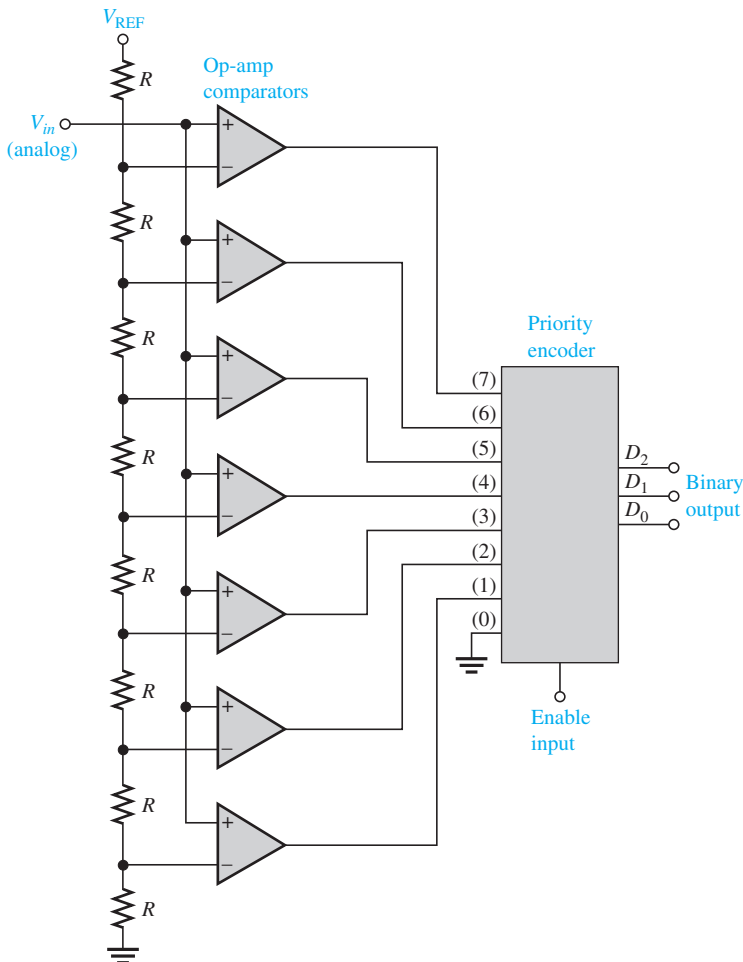


FIGURE SE8-3

the values of the analog input voltage as it changes. This converter requires seven comparators. In general, $2^n - 1$ comparators are required for conversion to an n -digit binary number. The large number of comparators necessary for a reasonably sized binary number is one of the drawbacks of this type of ADC. Its chief advantage is that it provides a fast conversion time, which is useful when many channels of data need to be converted.


The reference voltage for each comparator is set by the resistive voltage-divider network and V_{REF} . The output of each comparator is connected to an input of the priority encoder. The *priority encoder* is a digital device that produces a binary number on its outputs representing the highest-value input.

The encoder *samples* its input when a pulse occurs on the enable line (sampling pulse), and a three-digit binary number proportional to the value of the analog input signal appears on the encoder's outputs. The sampling rate determines the accuracy with which the sequence of binary numbers represents the changing input signal. The more samples taken in a given unit of time, the more accurately the analog signal is represented in digital form.

SECTION 8-1 CHECKUP*

1. What is the reference voltage for each comparator in Figure 8-17?
2. What is the purpose of hysteresis in a comparator?
3. Define the term *bounding* in relation to a comparator's output.
4. What is the purpose of the resistor divider-string in a simultaneous (flash) A/D converter?

FIGURE 8-17

 

*Answers are at the end of the chapter.

8-2 SUMMING AMPLIFIERS

The summing amplifier is a variation of the inverting op-amp configuration covered in Chapter 6. The summing amplifier has two or more inputs, and its output voltage is proportional to the negative of the algebraic sum of its input voltages. In this section, you will see how a summing amplifier works, and you will learn about the averaging amplifier and the scaling amplifier, which are variations of the basic summing amplifier.

After completing this section, you should be able to

- Understand the operation of several types of summing amplifiers
 - Describe the operation of a unity-gain summing amplifier
 - Discuss how to achieve any specified gain greater than unity
 - Describe the operation of an averaging amplifier
 - Describe the operation of a scaling adder
- Discuss a scaling adder used as a digital-to-analog converter
- Discuss analog systems in which summing amplifiers play a key role

Summing Amplifier with Unity Gain

A two-input **summing amplifier** is shown in Figure 8-18, but any number of inputs can be used.

The operation of the circuit and derivation of the output expression are as follows. Two voltages, V_{IN1} and V_{IN2} , are applied to the inputs and produce currents I_1 and I_2 , as shown. From the concepts of infinite input impedance and virtual ground, the voltage at the inverting ($-$) input of the op-amp is approximately 0 V, and therefore there is no current at the input. This means that both input currents I_1 and I_2 combine at this summing point and form the total current, which is through R_f as indicated ($I_T = I_1 + I_2$). Since $V_{OUT} = -I_T R_f$ the following steps apply.

$$V_{OUT} = -(I_1 + I_2)R_f = -\left(\frac{V_{IN1}}{R_1} + \frac{V_{IN2}}{R_2}\right)R_f$$

If all three of the resistors are equal in value ($R_1 = R_2 = R_f = R$), then

$$V_{OUT} = -\left(\frac{V_{IN1}}{R} + \frac{V_{IN2}}{R}\right)R = -(V_{IN1} + V_{IN2})$$

The previous equation shows that the output voltage has the same magnitude as the sum of the two input voltages but with a negative sign. A general expression is given in Equation (8-3) for a summing amplifier with n inputs, as shown in Figure 8-19 where all resistors are equal in value.

$$V_{OUT} = -(V_{IN1} + V_{IN2} + \cdots + V_{INn}) \quad (8-3)$$

 


FIGURE 8-18 Two-input inverting summing amplifier.

 


FIGURE 8-19 Summing amplifier with n inputs.

EXAMPLE 8-4

Determine the output voltage in Figure 8-20.

 


FIGURE 8-20

SOLUTION

$$V_{\text{OUT}} = -(V_{\text{IN1}} + V_{\text{IN2}} + V_{\text{IN3}}) = -(3 \text{ V} + 1 \text{ V} + 8 \text{ V}) = -12 \text{ V}$$

PRACTICE EXERCISE

If a fourth input of +0.5 V is added to Figure 8–20 with a 10 k Ω resistor, what is the output voltage?

Summing Amplifier with Gain Greater Than Unity

When R_f is larger than the input resistors, the amplifier has a gain of $-R_f/R$, where R is the value of each input resistor. The general expression for the output is

$$V_{\text{OUT}} = -\frac{R_f}{R}(V_{\text{IN1}} + V_{\text{IN2}} + \cdots + V_{\text{IN}n}) \quad (8-4)$$

As you can see, the output has the same magnitude as the sum of all the input voltages multiplied by a constant determined by the ratio $-R_f/R$.

EXAMPLE 8–5

Determine the output voltage for the summing amplifier in Figure 8–21.

 


FIGURE 8–21

SOLUTION

$R_f = 10 \text{ k}\Omega$ and $R = R_1 = R_2 = 1.0 \text{ k}\Omega$. Therefore,

$$V_{\text{OUT}} = -\frac{R_f}{R}(V_{\text{IN1}} + V_{\text{IN2}}) = -\frac{10 \text{ k}\Omega}{1.0 \text{ k}\Omega}(0.2 \text{ V} + 0.5 \text{ V}) = -10(0.7 \text{ V}) = -7 \text{ V}$$

PRACTICE EXERCISE

Determine the output voltage in Figure 8–21 if the two input resistors are 2.2 k Ω and the feedback resistor is 18 k Ω .

Averaging Amplifier

A summing amplifier can be made to produce the mathematical average of the input voltages. This is done by setting the ratio R_f/R equal to the reciprocal of the number of inputs (n); that is, $R_f/R = 1/n$.

You obtain the average of several numbers by first adding the numbers and then dividing by the quantity of numbers you have. Examination of Equation (8-4) and a little thought will convince you that a summing amplifier will do this. The next example illustrates this idea.

EXAMPLE 8-6

Show that the amplifier in Figure 8-22 produces an output whose magnitude is the mathematical average of the input voltages.

 


FIGURE 8-22

SOLUTION

Since the input resistors are equal, $R = 100 \text{ k}\Omega$. The output voltage is

$$\begin{aligned} V_{\text{OUT}} &= -\frac{R_f}{R}(V_{\text{IN1}} + V_{\text{IN2}} + V_{\text{IN3}} + V_{\text{IN4}}) \\ &= -\frac{25 \text{ k}\Omega}{100 \text{ k}\Omega}(1 \text{ V} + 2 \text{ V} + 3 \text{ V} + 4 \text{ V}) = -\frac{1}{4}(10 \text{ V}) = -2.5 \text{ V} \end{aligned}$$

A simple calculation shows that the average of the input values is the same magnitude as V_{OUT} but of opposite sign.

$$V_{\text{IN(avg)}} = \frac{1 \text{ V} + 2 \text{ V} + 3 \text{ V} + 4 \text{ V}}{4} = \frac{10 \text{ V}}{4} = 2.5 \text{ V}$$

PRACTICE EXERCISE

Specify the changes required in the averaging amplifier in Figure 8-22 in order to handle five inputs.

MULTISIM



Open file F08-22 found on the companion website. This simulation demonstrates the operation of a summing amplifier with both positive and negative dc inputs.

Scaling Adder


A different weight can be assigned to each input of a summing amplifier by simply adjusting the values of the input resistors. As you have seen, the output voltage can be expressed as

$$V_{\text{OUT}} = -\left(\frac{R_f}{R_1}V_{\text{IN1}} + \frac{R_f}{R_2}V_{\text{IN2}} + \cdots + \frac{R_f}{R_n}V_{\text{INn}}\right) \quad (8-5)$$

The weight of a particular input is set by the ratio of R_f to the resistance for that input. For example, if an input voltage is to have a weight of 1, then $R = R_f$. Or if a weight of 0.5 is required, $R = 2R_f$. The smaller the value of R , the greater the weight, and vice versa.

EXAMPLE 8–7

Determine the weight of each input voltage for the scaling adder in Figure 8–23 and find the output voltage.

 FIGURE 8–23**SOLUTION**

$$\text{Weight of input 1: } \frac{R_f}{R_1} = \frac{10 \text{ k}\Omega}{50 \text{ k}\Omega} = \mathbf{0.2}$$

$$\text{Weight of input 2: } \frac{R_f}{R_2} = \frac{10 \text{ k}\Omega}{100 \text{ k}\Omega} = \mathbf{0.1}$$


$$\text{Weight of input 3: } \frac{R_f}{R_3} = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega} = \mathbf{1}$$

The output voltage is

$$\begin{aligned} V_{\text{OUT}} &= -\left(\frac{R_f}{R_1}V_{\text{IN1}} + \frac{R_f}{R_2}V_{\text{IN2}} + \frac{R_f}{R_3}V_{\text{IN3}}\right) \\ &= -[0.2(3 \text{ V}) + 0.1(2 \text{ V}) + 1(8 \text{ V})] = -(0.6 \text{ V} + 0.2 \text{ V} + 8 \text{ V}) \\ &= \mathbf{-8.8 \text{ V}} \end{aligned}$$

PRACTICE EXERCISE

Determine the weight of each input voltage in Figure 8–23 if $R_1 = 22 \text{ k}\Omega$, $R_2 = 82 \text{ k}\Omega$, $R_3 = 56 \text{ k}\Omega$, and $R_f = 10 \text{ k}\Omega$. Also find V_{OUT} .

 SYSTEM EXAMPLE 8–3**DIGITAL-TO-ANALOG (D/A) CONVERSION**

D/A conversion is an important interface process for converting digital signals to analog (linear) signals in many types audio systems. An example is a voice signal that is digitized for storage, processing, or transmission and must be changed back into an approximation of the original audio signal in order to drive a speaker. In this example, we will look at a system that stores the voice signal as digital data, then later reads it back and converts it to sound. The system is diagramed in Figure SE-8–4. The emphasis in this system is the D/A conversion process. Digital-to-analog converters will be covered thoroughly in Chapter 14.

The method of D/A conversion used in this system uses a scaling adder with input resistor values that represent the binary weights of the digital input code. For simplicity, we will show a four-bit converter, although most actual converters use 10 or more bits. Figure SE8–5 shows a four-bit digital-to-analog converter (DAC) of this type (called a *binary-weighted resistor DAC*). The switch symbols represent transistor switches for applying each of the four binary digits to the inputs.

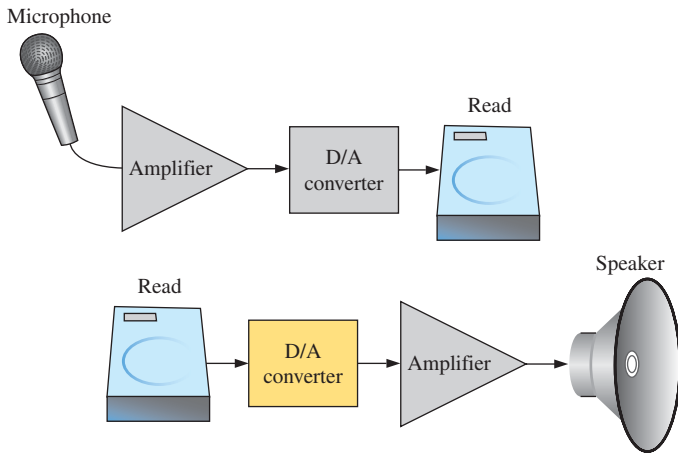


FIGURE SE8-4

 


FIGURE SE8-5 A scaling adder as a four-bit digital-to-analog converter (DAC).

The inverting ($-$) input is at virtual ground, so that the output voltage is proportional to the current through the feedback resistor R_f (sum of input currents). The lowest-value resistor R corresponds to the highest weighted binary input (2^3). All of the other resistors are multiples of R and correspond to the binary weights 2^2 , 2^1 , and 2^0 .

SYSTEM EXAMPLE 8-4

A 25 WATT FOUR-CHANNEL MIXER/AMPLIFIER

Almost every sound reinforcement system employs a device called a mixer. A mixer takes signals from different sources, such as instruments and/or vocalists, and combines them. Since the level of each input may vary significantly, each input must have its own volume control, independent of the rest of the system. This allows the sound technician to balance the sound so that each instrument or vocalist can be heard clearly. At the same time, a master volume control is required to raise or lower the overall sound level. The front panel controls of a basic four-channel mixer are shown in Figure SE8-6.

Note that the inputs are female XLR connectors. XLR connectors are commonly used in professional audio, and are sometimes used in lighting control and other applications as well. XLR connectors were invented by James Cannon and are sometimes called cannon connectors. The three-pin connectors shown are the most common type but XLR connectors can have up to seven pins, depending on the application. The center pin is the ground pin and is slightly longer than the other pins so that it makes contact before the other pins.

Refer to the circuit schematic shown in Figure SE8-7. In this circuit an op-amp is being used as both a summing amplifier and a preamp. First note the potentiometers and fixed resistors on each input. The potentiometers control the gain of the input signal from each microphone. As the resistance of the potentiometer decreases, the gain of that input signal increases. The fixed-value resistors are required because, if the potentiometer is lowered to $0\ \Omega$, the op-amp will immediately saturate, regardless of the setting of the master volume control.

The feedback potentiometer acts as the master volume control; as its value increases the gain of the summed inputs increases. No fixed-value feedback resistor is required. When the feedback resistance reaches $0\ \Omega$ the gain of the circuit is 0 and no sound is produced. Note that the LM4562 op-amp has been chosen for this mixer. This series of

 
 


FIGURE SE8-6 Mixer front panel controls.

 


FIGURE SE8-7 Schematic for a 25 W four-channel mixer/amplifier.

MULTISIM



Open file SE-8-7 found on the companion website. This simulation demonstrates the operation of this four-channel mixer/amplifier.

op-amps from National Semiconductor are ultra-low distortion amplifiers that have been optimized for high fidelity applications. The spec sheet for the LM4562 can be found at www.national.com.

Many mixers also include a power amplifier. This circuit uses a variation of the power amp that was introduced in System Example 5-1 with a few changes. The supply rails for the power amp have been increased to ± 45 V in order to allow for a higher output. It is quite common to have more than one supply rail voltage in a given system. This change required that the 2N3904 and the 2N3906 be changed for a higher voltage rated transistor; the 2N3904 and 2N3906 are rated for a maximum of 40 V from collector to emitter. The buffer stage was replaced with a class A amplification stage. This was because the op-amp could not produce a high enough output voltage swing. No buffer is required as the LM4562, with its low output impedance, could easily drive the class A amplifier. As designed, this mixer/amplifier can deliver 25 W continuous into an 8-ohm speaker before clipping. If higher power is required, one or more output stages can be added in parallel.

SECTION 8-2 CHECKUP

1. Define *summing point*.
2. What is the value of R_f/R for a five-input averaging amplifier?
3. A certain scaling adder has two inputs, one having twice the weight of the other. If the resistor value for the lower weighted input is 10 k Ω , what is the value of the other input resistor?
4. Refer to Figure SE8-7. What is the purpose of the fixed resistors in each channel of the mixer?

8-3 INTEGRATORS AND DIFFERENTIATORS

An op-amp integrator simulates mathematical integration, which is basically a summing process that determines the total area under the curve of a function. An op-amp differentiator simulates mathematical differentiation, which is a process of determining the instantaneous rate of change of a function. The integrators and differentiators shown in this section are idealized to show basic principles. Practical integrators often have an additional resistor or other circuitry in parallel with the feedback capacitor to prevent saturation. Practical differentiators may include a series resistor to reduce high frequency noise.

After completing this section, you should be able to

- Understand the operation of integrators and differentiators
 - Identify an integrator
 - Discuss how a capacitor charges
 - Determine the rate of change of an integrator's output
- Identify a differentiator
- Determine the output voltage of a differentiator

The Op-Amp Integrator

An ideal **integrator** is shown in Figure 8-24. Notice that the feedback element is a capacitor that forms an RC circuit with the input resistor.

 


FIGURE 8-24 An ideal op-amp integrator.

HOW A CAPACITOR CHARGES To understand how the integrator works, it is important to review how a capacitor charges. Recall that the charge Q on a capacitor is proportional to the charging current (I_C) and the time (t).

$$Q = I_C t$$

Also, in terms of the voltage, the charge on a capacitor is

$$Q = C V_C$$

From these two relationships, the capacitor voltage can be expressed as

$$V_C = \left(\frac{I_C}{C} \right) t$$

This expression is an equation for a straight line that begins at zero with a constant slope of I_C/C . (Remember from algebra that the general formula for a straight line is $y = mx + b$. In this case, $y = V_C$, $m = I_C/C$, $x = t$, and $b = 0$.)

Recall that the capacitor voltage in a simple RC network is not linear but is exponential. This is because the charging current continuously decreases as the capacitor charges and causes the rate of change of the voltage to continuously decrease. The key thing about using an op-amp with an RC network to form an integrator is that the capacitor's charging current is made constant, thus producing a straight-line (linear) voltage rather than an exponential voltage. Now let's see why this is true.

In Figure 8–25, the inverting input of the op-amp is at virtual ground (0 V), so the voltage across R_i equals V_{in} . Therefore, the input current is

$$I_{in} = \frac{V_{in}}{R_i}$$

If V_{in} is a constant voltage, then I_{in} is also a constant because the inverting input always remains at 0 V, keeping a constant voltage across R_i . Because of the very high input impedance of the op-amp, there is negligible current at the inverting input. This makes all of the input current charge the capacitor, so

$$I_C = I_{in}$$

 


FIGURE 8–25 Currents in an integrator.

THE CAPACITOR VOLTAGE Since I_{in} is constant, so is I_C . The constant I_C charges the capacitor linearly and produces a linear voltage across C . The positive side of the capacitor is held at 0 V by the virtual ground of the op-amp. The voltage on the negative side of the capacitor decreases linearly from zero as the capacitor charges, as shown in Figure 8–26. This voltage is called a *negative ramp* and is the consequence of a constant positive input.

 


FIGURE 8–26 A linear ramp voltage is produced across C by the constant charging current.

THE OUTPUT VOLTAGE V_{out} is the same as the voltage on the negative side of the capacitor. When a constant positive input voltage in the form of a step or pulse (a pulse has a constant amplitude when high) is applied, the output ramp decreases negatively until the op-amp saturates at its maximum negative level. This is indicated in Figure 8–27.

 


FIGURE 8–27 A constant input voltage produces a ramp on the output of the integrator.

RATE OF CHANGE OF THE OUTPUT The rate at which the capacitor charges, and therefore the slope of the output ramp, is set by the ratio I_C/C , as you have seen. Since $I_C = V_{in}/R_i$, the rate of change or slope of the integrator's output voltage is

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{R_i C} \quad (8-6)$$

Integrators are especially useful in triangular-wave generators as you will see in Chapter 10.

The ideal integrator shown in Figure 8-24 works fine in theory, but will not work in practice. If there is even the slightest dc offset at the input to the op-amp, it will eventually cause the output to be driven to saturation. The reason is that the capacitor acts like an almost infinite resistance to the dc voltage, and the dc voltage gain will be extremely high. Even if there is no dc component to the input signal, the input offset current of the op-amp itself can result in an output offset voltage.

The solution to this problem is to add a high-value resistor in parallel with the capacitor, as shown in Figure SN8-1. This circuit is known as a running-average, or *Miller integrator*. At high frequencies the resistor has little or no effect. At lower frequencies it allows a path for the capacitor to discharge and lowers the dc gain of the integrator.

 



FIGURE SN8-1 A Miller integrator.

SYSTEM NOTE




 EXAMPLE 8-8

- Determine the rate of change of the output voltage in response to the first input pulse in a pulse waveform, as shown for the ideal integrator in Figure 8-28(a). The output voltage is initially zero.
- Describe the output after the first pulse. Draw the output waveform.



(a)

 

(b)

FIGURE 8-28

SOLUTION

- (a) The rate of change of the output voltage during the time that the input pulse is high is

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{R_f C} = -\frac{5 \text{ V}}{(10 \text{ k}\Omega)(0.01 \text{ }\mu\text{F})} = -50 \text{ kV/s} = -50 \text{ mV}/\mu\text{s}$$

- (b) The rate of change was found to be $-50 \text{ mV}/\mu\text{s}$ in part (a). When the input is at $+5 \text{ V}$, the output is a negative-going ramp. When the input is at 0 V , the output is a constant level. In $100 \text{ }\mu\text{s}$, the voltage decreases.

$$\Delta V_{out} = (-50 \text{ mV}/\mu\text{s})(100 \text{ }\mu\text{s}) = -5 \text{ V}$$

Therefore, the negative-going ramp reaches -5 V at the end of the pulse. The output voltage then remains constant at -5 V for the time that the input is zero. On the next pulse, the output again is a negative-going ramp that reaches -10 V . Since this is the maximum limit, the output remains at -10 V as long as pulses are applied. The waveforms are shown in Figure 8–28(b).

PRACTICE EXERCISE

Modify the integrator in Figure 8–28 to make the output change from 0 to -5 V in $50 \text{ }\mu\text{s}$ with the same input.

MULTISIM



Open file F08-28 found on the companion website. This simulation demonstrates the effect that changing the input resistance and the feedback capacitance has on the output of an integrator circuit.

 


FIGURE 8–29 An ideal op-amp differentiator.

The Op-Amp Differentiator

An ideal **differentiator** is shown in Figure 8–29. Notice how the placement of the capacitor and resistor differ from that in the integrator. The capacitor is now the input element. A differentiator produces an output that is proportional to the rate of change of the input voltage. Although a small-value resistor is normally used in series with the capacitor to limit the gain, it does not affect the basic operation and is not shown for purposes of this analysis.

To see how the differentiator works, let's apply a positive-going ramp voltage to the input as indicated in Figure 8–30. In this case, $I_C = I_{in}$ and the voltage across the capacitor is equal to V_{in} at all times ($V_C = V_{in}$) because of virtual ground on the inverting input.

 


FIGURE 8–30 A differentiator with a ramp input.

From the basic formula, which is $V_C = (I_C/C)t$,

$$I_C = \left(\frac{V_C}{t}\right)C$$

Since the current at the inverting input is negligible, $I_R = I_C$. Both currents are constant because the slope of the capacitor voltage (V_C/t) is constant. The output voltage is also constant and equal to the voltage across R_f because one side of the feedback resistor is always 0 V (virtual ground).

$$V_{out} = I_R R_f = I_C R_f$$

$$V_{out} = -\left(\frac{V_C}{t}\right)R_f C \quad (8-7)$$

The output is negative when the input is a positive-going ramp and positive when the input is a negative-going ramp, as illustrated in Figure 8-31. During the positive slope of the input, the capacitor is charging from the input source with constant current through the feedback resistor. During the negative slope of the input, the constant current is in the opposite direction because the capacitor is discharging.

 



FIGURE 8-31 Output of a differentiator with a series of positive and negative ramps (triangle wave) on the input.

Notice in Equation (8-7) that the term V_C/t is the slope of the input. If the slope increases, V_{out} becomes more negative. If the slope decreases, V_{out} becomes more positive. So the output voltage is proportional to the negative slope (rate of change) of the input. The constant of proportionality is the time constant, $R_f C$.

The output of a differentiator is a function of the rate of change of the input signal. One common application for this circuit is in process instrumentation. Suppose an industrial furnace is being brought up to full operating temperature. If only the furnace temperature is monitored, no alarm would sound until it actually overheated. A safer control system would monitor the *rate* at which the furnace was heating up. If the furnace was heating too quickly, this would be an indication of a possible malfunction and corrective action could be taken *before* the furnace actually overheated.

If the input to an integrator was tied to a sensor that produced a dc voltage proportional to temperature, the differentiator would produce an output that was proportional to the rate at which the temperature increased. The output of the differentiator would then drive a comparator. If the rate of change of temperature exceeded a predetermined value, calibrated by the reference voltage of the comparator, the comparator output would trigger an alarm and the heating process would be aborted.

SYSTEM NOTE

 

EXAMPLE 8-9

Determine the output voltage of the ideal op-amp differentiator in Figure 8-32 for the triangular-wave input shown.

 


FIGURE 8-32

MULTISIM



Open file F08-32 found on the companion website. This simulation demonstrates the operation of the op-amp differentiator.

SOLUTION

Starting at $t = 0$, the input voltage is a positive-going ramp ranging from -5 V to $+5$ V (a $+10$ V change) in $5 \mu\text{s}$. Then it changes to a negative-going ramp ranging from $+5$ V to -5 V (a -10 V change) in $5 \mu\text{s}$.

Substituting into Equation (8-7), the output voltage for the positive-going ramp is

$$V_{out} = -\left(\frac{V_C}{t}\right)R_f C = -\left(\frac{10 \text{ V}}{5 \mu\text{s}}\right)(2.2 \text{ k}\Omega)(0.001 \mu\text{F}) = 24.4 \text{ V}$$

The output voltage for the negative-going ramp is calculated the same way.

$$V_{out} = -\left(\frac{V_C}{t}\right)R_f C = -\left(\frac{-10 \text{ V}}{5 \mu\text{s}}\right)(2.2 \text{ k}\Omega)(0.001 \mu\text{F}) = +4.4 \text{ V}$$

Finally, the output voltage waveform is graphed relative to the input as shown in Figure 8-33.

 


FIGURE 8-33

As mentioned previously, if this were a practical differentiator, there would be a small value resistor in series with the capacitor. The analysis is essentially the same.

PRACTICE EXERCISE

What would the output voltage be if the feedback resistor in Figure 8-32 is changed to $3.3 \text{ k}\Omega$?

SECTION 8-3 CHECKUP

1. What is the feedback element in an op-amp integrator?
2. For a constant input voltage to an integrator, why is the voltage across the capacitor linear?
3. What is the feedback element in an op-amp differentiator?
4. How is the output of a differentiator related to the input?

8-4 CONVERTERS AND OTHER OP-AMP CIRCUITS

This section introduces a few more op-amp circuits that represent basic applications of the op-amp. You will learn about the constant-current source, the current-to-voltage converter, the voltage-to-current converter, and the peak detector. This is, of course, not a comprehensive coverage of all possible op-amp circuits but is intended only to introduce you to some common and basic uses.

After completing this section, you should be able to

- Understand the operation of several special op-amp circuits
 - Identify and explain the operation of an op-amp constant-current source
 - Identify and explain the operation of an op-amp current-to-voltage converter
 - Identify and explain the operation of an op-amp voltage-to-current converter
 - Explain how an op-amp can be used as a peak detector

Constant-Current Source

A **constant-current source** delivers a load current that remains constant when the load resistance changes. Figure 8-34 shows a basic circuit in which a stable voltage source (V_{in}) provides a constant current (I_i) through the input resistor (R_i). Since the inverting input of the op-amp is at virtual ground (0 V), the value of I_i is determined by V_{IN} and R_i as

$$I_i = \frac{V_{IN}}{R_i}$$

 


FIGURE 8-34 A basic constant-current source.

Now, since the internal input impedance of the op-amp is extremely high (ideally infinite), practically all of I_i is through R_L , which is connected in the feedback path. Since $I_i = I_L$,

$$I_L = \frac{V_{IN}}{R_i} \quad (8-8)$$

If R_L changes, I_L remains constant as long as V_{IN} and R_i are held constant.

Current-to-Voltage Converter

A **current-to-voltage converter** converts a variable input current to a proportional output voltage. A basic circuit that accomplishes this is shown in Figure 8-35(a). Since practically all of I_i is through the feedback path, the voltage dropped across R_f is $I_i R_f$. Because the left side of R_f is at virtual ground (0 V), the output voltage equals the voltage across R_f , which is proportional to I_i .

$$V_{OUT} = I_i R_f \quad (8-9)$$

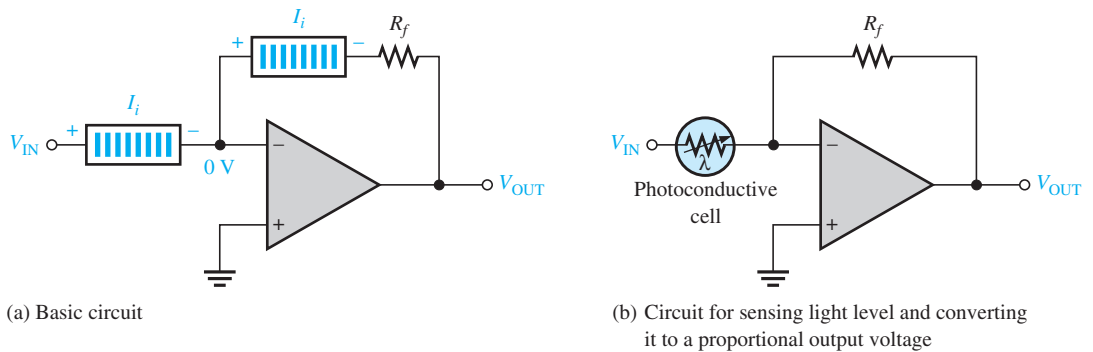


FIGURE 8-35 Current-to-voltage converter.

A specific application of this circuit is illustrated in Figure 8-35(b), where a photoconductive cell is used to sense changes in light level. As the amount of light changes, the current through the photoconductive cell varies because of the cell's change in resistance. This change in resistance produces a proportional change in the output voltage ($\Delta V_{OUT} = \Delta I_i R_f$).

 


FIGURE 8-36 Voltage-to-current converter.

Voltage-to-Current Converter

A basic **voltage-to-current converter** is shown in Figure 8-36. This circuit is used in applications where it is necessary to have an output (load) current that is controlled by an input voltage.

Neglecting the input offset voltage, both inverting and noninverting input terminals of the op-amp are at the same voltage, V_{IN} . Therefore, the voltage across R_1 equals V_{IN} . Since there is negligible current for the inverting input, the current through R_1 is the same as the current through R_L ; thus,

$$I_L = \frac{V_{IN}}{R_1} \tag{8-10}$$

In instrumentation systems, most physical measurements (such as temperature, weight, pressure, etc.) are represented by sensors as analog dc voltage signals. However, dc current signals are preferred over dc voltage signals since the dc current in a series circuit (sensor to measuring/recording device) will always be the same at any point in the signal path. DC voltage signals, even in a parallel arrangement, can still vary from one point in the circuit to another due to wiring losses. Also, current-sensing instruments have better noise immunity than voltage-sensing instruments due to their lower impedance.

The op-amp voltage-to-current converter is an ideal device for this application. It will produce a precise current for a given sensor input voltage even when the resistance of the path to the measuring device is not known.

SYSTEM NOTE

 
 


FIGURE 8-37 A basic peak detector.

Peak Detector

An interesting application of the op-amp is in a **peak detector** circuit such as the one shown in Figure 8-37. In this case the op-amp is used as a comparator. The purpose of this circuit is to detect the peak of the input voltage and store that peak voltage on a capacitor. For example, this circuit can be used to detect and store the maximum value of a voltage surge; this value can then be measured at the output with a voltmeter or recording device. The basic operation is as follows. When a positive voltage is applied to the noninverting input of the op-amp through R_i , the high-level output voltage of the op-amp


forward-biases the diode and charges the capacitor. The capacitor continues to charge until its voltage reaches a value equal to the input voltage and thus both op-amp inputs are at the same voltage. At this point, the op-amp comparator switches, and its output goes to the low level. The diode is now reverse-biased, and the capacitor stops charging. It has reached a voltage equal to the peak of V_{in} and will hold this voltage until the charge eventually leaks off. If a greater input peak occurs, the capacitor charges to the new peak.

SECTION 8-4 CHECKUP

1. For the constant-current source in Figure 8-34, the input reference voltage is 6.8 V and R_i is 10 k Ω . What value of constant current does the circuit supply to a 1 k Ω load? To a 5 k Ω load?
2. What element determines the constant of proportionality that relates input current to output voltage in the current-to-voltage converter?

 8-5 TROUBLESHOOTING

Although integrated circuit op-amps are extremely reliable and trouble-free, failures do occur from time to time. One type of internal failure mode is a condition where the op-amp output is “stuck” in a saturated state resulting in a constant high or constant low level, regardless of the input. Also, external component failures will produce various types of failure modes in op-amp circuits. Some examples are presented in this section.



After completing this section, you should be able to

- Troubleshoot basic op-amp circuits
 - Identify failures in comparator circuits
 - Identify failures in summing amplifiers

Figure 8-38 illustrates an internal failure of a comparator circuit that results in a “stuck” output.

 



FIGURE 8-38 Internal comparator failures typically result in the output being “stuck” in the HIGH or LOW state.

Symptoms of External Component Failures in Comparator Circuits

A comparator with zener-bounding is shown in Figure 8-39. In addition to a failure of the op-amp itself, a zener diode or the resistor could be faulty. For example, suppose one of the zener diodes opens. This effectively eliminates both zeners, and the circuit operates as an unbounded comparator, as indicated in Figure 8-40(a). With a shorted diode, the output is


limited to the zener voltage (bounded) only in one direction depending on which diode remains operational, as illustrated in Figure 8-40(b). In the other direction, the output is held at the forward diode voltage.

FIGURE 8-39 A bounded comparator.

 


Recall that R_1 and R_2 set the UTP and LTP for the hysteresis comparator shown in Figure 8-40, parts (c) and (d). Now, suppose that R_2 opens. Essentially all of the output voltage is fed back to the noninverting input, and, since the input voltage will never exceed the output, the device will remain in one of its saturated states. This symptom can also indicate a faulty op-amp, as mentioned before. Now, assume that R_1 opens. This leaves the noninverting input near ground potential and causes the circuit to operate as a zero-level detector.


FIGURE 8-40 Examples of comparator circuit failures and their effects.

 


(a) The effect of an open zener

 

(b) The effect of a shorted zener

 

 (c) Open R_2 causes output to “stick” in one state (either high or low)



(d) Open R_1 forces the circuit to operate as a zero-level detector

EXAMPLE 8-10

One channel of a dual-trace oscilloscope is connected to the comparator output and the other channel to the input signal, as shown in Figure 8-41. From the observed waveforms, determine if the circuit is operating properly, and if not, what the most likely failure is.

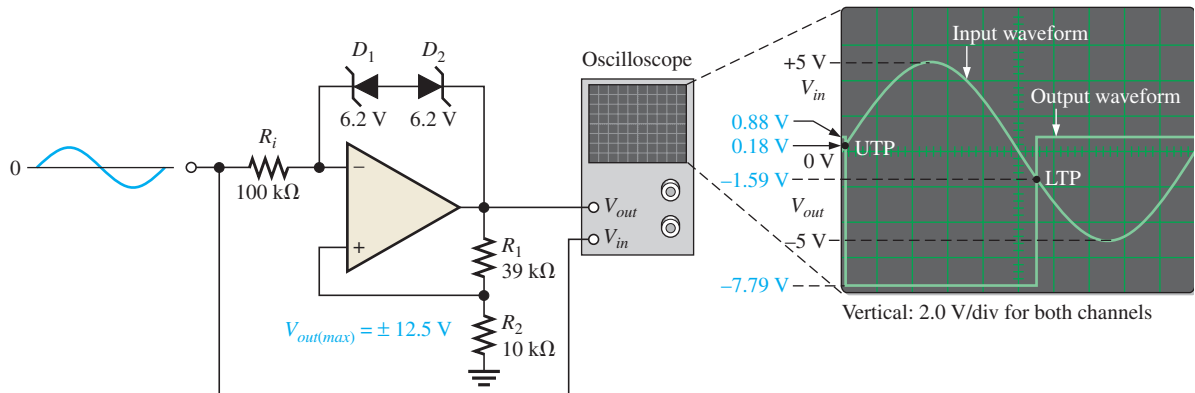


FIGURE 8-41

SOLUTION

The output should be limited to ± 8.67 V. However, the positive maximum is $+0.88$ V and the negative maximum is -7.79 V. This indicates that D_2 is shorted. Refer to Example 8-3 for analysis of the bounded comparator.

PRACTICE EXERCISE

What would the output voltage look like if D_1 shorted rather than D_2 ?

Symptoms of Component Failures in Summing Amplifiers

If one of the input resistors in a unity-gain summing amplifier opens, the output will be less than the normal value by the amount of the voltage applied to the open input. Stated another way, the output will be the sum of the remaining input voltages.

If the summing amplifier has a nonunity gain, an open input resistor causes the output to be less than normal by an amount equal to the gain times the voltage at the open input.

EXAMPLE 8-11

- What is the normal output voltage in Figure 8-42?
- What is the output voltage if R_2 opens?
- What happens if R_5 opens?

 


FIGURE 8-42

SOLUTION

- (a) $V_{OUT} = -(V_{IN1} + V_{IN2} + \cdots + V_{INn})$
 $= -(1\text{ V} + 0.5\text{ V} + 0.2\text{ V} + 0.1\text{ V}) = -1.8\text{ V}$
- (b) $V_{OUT} = -(1\text{ V} + 0.2\text{ V} + 0.1\text{ V}) = -1.3\text{ V}$
- (c) If R_5 opens, the circuit becomes a comparator and the output goes to $-V_{max}$.

PRACTICE EXERCISE

In Figure 8–42, assume $R_5 = 47\text{ k}\Omega$. What is the output voltage if R_1 opens?

As another example, let's look at an averaging amplifier. An open input resistor will result in an output voltage that is the average of all the inputs with the open input averaged in as a zero.

EXAMPLE 8–12

- (a) What is the normal output voltage for the averaging amplifier in Figure 8–43?
- (b) If R_4 opens, what is the output voltage? What does the output voltage represent?

 


FIGURE 8–43

SOLUTION

Since the input resistors are equal, $R = 100\text{ k}\Omega$, $R_f = R_6$.

- (a) $V_{OUT} = -\frac{R_f}{R}(V_{IN1} + V_{IN2} + \cdots + V_{INn})$
 $= -\frac{20\text{ k}\Omega}{100\text{ k}\Omega}(1\text{ V} + 1.5\text{ V} + 0.5\text{ V} + 2\text{ V} + 3\text{ V}) = -0.2(8\text{ V})$
 $= -1.6\text{ V}$
- (b) $V_{OUT} = -\frac{20\text{ k}\Omega}{100\text{ k}\Omega}(1\text{ V} + 1.5\text{ V} + 0.5\text{ V} + 3\text{ V}) = -0.2(6\text{ V}) = -1.2\text{ V}$

The 1.2 V result is the average of five voltages with the 2 V input replaced by 0 V. Notice that the output is not the average of the four remaining input voltages.

PRACTICE EXERCISE

If R_4 is open, as was the case in this example, what would you have to do to make the output equal to the average of the remaining four input voltages?

SECTION 8–5 CHECKUP

1. Describe one type of internal op-amp failure.
2. If a certain malfunction is attributable to more than one possible component failure, what would you do to isolate the problem?

SUMMARY

- In an op-amp comparator, when the input voltage exceeds a specified reference voltage, the output changes state.
- Hysteresis gives an op-amp noise immunity.
- A comparator switches to one state when the input reaches the upper trigger point (UTP) and back to the other state when the input drops below the lower trigger point (LTP).
- The difference between the UTP and the LTP is the hysteresis voltage.
- Bounding limits the output amplitude of a comparator.
- The output voltage of a summing amplifier is proportional to the sum of the input voltages.
- An averaging amplifier is a summing amplifier with a closed-loop gain equal to the reciprocal of the number of inputs.
- In a scaling adder, a different weight can be assigned to each input, thus making the input contribute more or contribute less to the output.
- Integration is a mathematical process for determining the area under a curve.
- Integration of a step produces a ramp with a slope proportional to the amplitude.
- Differentiation is a mathematical process for determining the rate of change of a function.
- Differentiation of a ramp produces a step with an amplitude proportional to the slope.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Bounding The process of limiting the output range of an amplifier or other circuit.

Comparator A circuit that compares two input voltages and produces an output in either of two states indicating the greater than or less than relationship of the inputs.

Constant-current source A circuit that delivers a load current that remains constant when the load resistance changes.

Current-to-voltage converter A circuit that converts a variable input current to a proportional output voltage.

Differentiator A circuit that produces an inverted output that approximates the rate of change of the input function.

Hysteresis The property that permits a circuit to switch from one state to the other at one voltage level and switch back to the original state at another lower voltage level.

Integrator A circuit that produces an inverted output that approximates the area under the curve of the input function.

Peak detector A circuit used to detect the peak of the input voltage and store that peak value on a capacitor.

Schmitt trigger A comparator with hysteresis.

Summing amplifier A variation of a basic comparator circuit that is characterized by two or more inputs and an output voltage that is proportional to the magnitude of the algebraic sum of the input voltages.

Voltage-to-current converter A circuit that converts a variable input voltage to a proportional output current.

KEY FORMULAS

COMPARATORS

$$(8-1) \quad V_{\text{REF}} = \frac{R_2}{R_1 + R_2} (+V) \quad \text{Comparator reference}$$

$$(8-2) \quad V_{\text{HYS}} = V_{\text{UTP}} - V_{\text{LTP}} \quad \text{Hysteresis voltage}$$

SUMMING AMPLIFIER

$$(8-3) \quad V_{\text{OUT}} = -(V_{\text{IN1}} + V_{\text{IN2}} + \cdots + V_{\text{INn}}) \quad n\text{-input adder}$$

$$(8-4) \quad V_{\text{OUT}} = -\frac{R_f}{R}(V_{\text{IN1}} + V_{\text{IN2}} + \cdots + V_{\text{INn}}) \quad \text{Scaling adder with gain}$$

$$(8-5) \quad V_{\text{OUT}} = -\left(\frac{R_f}{R_1}V_{\text{IN1}} + \frac{R_f}{R_2}V_{\text{IN2}} + \cdots + \frac{R_f}{R_n}V_{\text{INn}}\right) \quad \text{Scaling adder}$$

INTEGRATOR AND DIFFERENTIATOR

$$(8-6) \quad \frac{\Delta V_{\text{out}}}{\Delta t} = -\frac{V_{\text{in}}}{R_f C} \quad \text{Integrator output rate of change}$$

$$(8-7) \quad V_{\text{out}} = -\left(\frac{V_C}{t}\right)R_f C \quad \text{Differentiator output voltage with ramp input}$$

MISCELLANEOUS

$$(8-8) \quad I_L = \frac{V_{\text{IN}}}{R_i} \quad \text{Constant-current source}$$

$$(8-9) \quad V_{\text{OUT}} = I_i R_f \quad \text{Current-to-voltage converter}$$

$$(8-10) \quad I_L = \frac{V_{\text{IN}}}{R_1} \quad \text{Voltage-to-current converter}$$

SELF-TEST

Answers are at the end of the chapter.

- In a zero-level detector, the output changes state when the input
 - is positive
 - is negative
 - crosses zero
 - has a zero rate of change
- The zero-level detector is one application of a
 - comparator
 - differentiator
 - summing amplifier
 - diode
- Noise on the input of a comparator can cause the output to
 - hang up in one state
 - go to zero
 - change back and forth erratically between two states
 - produce the amplified noise signal
- The effects of noise can be reduced by
 - lowering the supply voltage
 - using positive feedback
 - using negative feedback
 - using hysteresis
 - answers (b) and (d)
- A comparator with hysteresis
 - has one trigger point
 - has two trigger points
 - has a variable trigger point
 - is like a magnetic circuit
- In a comparator with hysteresis,
 - a bias voltage is applied between the two inputs
 - only one supply voltage is used
 - a portion of the output is fed back to the inverting input
 - a portion of the output is fed back to the noninverting input


7. Using output bounding in a comparator
 (a) makes it faster (b) keeps the output positive
 (c) limits the output levels (d) stabilizes the output
8. A window comparator detects when the
 (a) input is between two specified limits
 (b) input is not changing
 (c) input is changing too fast
 (d) amount of light exceeds a certain value
9. A summing amplifier can have
 (a) only one input (b) only two inputs (c) any number of inputs
10. If the voltage gain for each input of a summing amplifier with a 4.7 k Ω feedback resistor is unity, the input resistors must have a value of
 (a) 4.7 k Ω
 (b) 4.7 k Ω divided by the number of inputs
 (c) 4.7 k Ω times the number of inputs
11. An averaging amplifier has five inputs. The ratio R_f/R_{in} must be
 (a) 5 (b) 0.2 (c) 1
12. In a scaling adder, the input resistors are
 (a) all the same value (b) all of different values
 (c) each proportional to the weight of its inputs (d) related by a factor of two
13. In an integrator, the feedback element is a
 (a) resistor (b) capacitor (c) zener diode (d) voltage divider
14. For a step input, the output of an integrator is a
 (a) pulse (b) triangular waveform (c) spike (d) ramp
15. The rate of change of an integrator's output voltage in response to a step input is set by
 (a) the RC time constant (b) the amplitude of the step input
 (c) the current through the capacitor (d) all of these
16. In a differentiator, the feedback element is a
 (a) resistor (b) capacitor
 (c) zener diode (d) voltage divider
17. The output of a differentiator is proportional to
 (a) the RC time constant
 (b) the rate at which the input is changing
 (c) the amplitude of the input
 (d) answers (a) and (b)
18. When you apply a triangular waveform to the input of a differentiator, the output is
 (a) a dc level
 (b) an inverted triangular waveform
 (c) a square waveform
 (d) the first harmonic of the triangular waveform

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 8-45.

 - If the value of R_1 is larger than specified,
 1. The hysteresis voltage will
 (a) increase (b) decrease (c) not change
 2. The sensitivity to noise voltage on the input will
 (a) increase (b) decrease (c) not change



Refer to Figure 8–48.

- If D_2 is open,
 3. The output voltage will
(a) increase (b) decrease (c) not change
 4. The upper trigger point voltage will
(a) increase (b) decrease (c) not change
 5. The hysteresis voltage will
(a) increase (b) decrease (c) not change

Refer to Figure 8–50.

- If the value of R_1 is less than specified,
 6. The output voltage will
(a) increase (b) decrease (c) not change
 7. The voltage at the inverting input will
(a) increase (b) decrease (c) not change

Refer to Figure 8–52.

- If C is open,
 8. The rate of change of the output voltage in response to the step input will
(a) increase (b) decrease (c) not change
 9. The maximum voltage at the output will
(a) increase (b) decrease (c) not change

Refer to Figure 8–53.

- If C is open,
 10. The output signal voltage in response to a periodic triangular input waveform will
(a) increase (b) decrease (c) not change
- If the value of R is larger than specified,
 11. The output voltage in response to the periodic triangular input waveform will
(a) increase (b) decrease (c) not change
 12. The period of the output will
(a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 8–1 Comparators

1. A certain op-amp has an open-loop gain of 80,000. The maximum saturated output levels of this particular device are ± 12 V when the dc supply voltages are ± 15 V. If a differential voltage of 0.15 mV rms is applied between the inputs, what is the peak-to-peak value of the output?
2. Determine the output level (maximum positive or maximum negative) for each comparator in Figure 8–44.

 


FIGURE 8–44

3. Calculate the V_{UTP} and V_{LTP} in Figure 8–45. $V_{out(max)} = -10\text{ V}$.
4. What is the hysteresis voltage in Figure 8–45?
5. Sketch the output voltage waveform for each circuit in Figure 8–46 with respect to the input. Show voltage levels.

 


FIGURE 8–45



 



FIGURE 8–46

 

 6. Determine the hysteresis voltage for each comparator in Figure 8–47. The maximum output levels are $\pm 11\text{ V}$.



(a)

 

(b)

FIGURE 8–47

7. A 6.2 V zener diode is connected from the output to the inverting input in Figure 8–45 with the cathode at the output. What are the positive and negative output levels?
8. Determine the output voltage waveform in Figure 8–48.

 


FIGURE 8–48

SECTION 8-2 Summing Amplifiers

9. Determine the output voltage for each circuit in Figure 8-49.

 


FIGURE 8-49

10. Refer to Figure 8-50. Determine the following:

- (a) V_{R1} and V_{R2}
- (b) Current through R_f
- (c) V_{OUT}

11. Find the value of R_f necessary to produce an output that is five times the sum of the inputs in Figure 8-50.

12. Design a summing amplifier that will average eight input voltages. Use input resistances of 10 kΩ each.

13. Find the output voltage when the input voltages shown in Figure 8-51 are applied to the scaling adder. What is the current through R_f ?

 


FIGURE 8-50

 



FIGURE 8-51

14. Determine the values of the input resistors required in a six-input scaling adder so that the lowest weighted input is 1 and each successive input has a weight twice the previous one. Use $R_f = 100 \text{ k}\Omega$.

SECTION 8-3 Integrators and Differentiators

15. Determine the rate of change of the output voltage in response to the step input to the integrator in Figure 8-52.

FIGURE 8-52

 

16. A triangular waveform is applied to the input of the circuit in Figure 8–53 as shown. Determine what the output should be and sketch its waveform in relation to the input.



 


FIGURE 8–53

 17. What is the magnitude of the capacitor current in Problem 16?
18. A triangular waveform with a peak-to-peak voltage of 2 V and a period of 1 ms is applied to the differentiator in Figure 8–54(a). What is the output voltage?
19. Beginning in position 1 in Figure 8–54(b), the switch is thrown into position 2 and held there for 10 ms, then back to position 1 for 10 ms, and so forth. Sketch the resulting output waveform. The saturated output levels of the op-amp are ± 12 V.



(a)

 


(b)


FIGURE 8–54

SECTION 8–4 Converters and Other Op-Amp Circuits

 20. Determine the load current in each circuit of Figure 8–55. (Hint: Thevenize the circuit to the left of R_L .)



(a)

 

(b)

FIGURE 8–55

21. Devise a circuit for remotely sensing temperature and producing a proportional voltage that can then be converted to digital form for display. A thermistor can be used as the temperature-sensing element.

SECTION 8–5 Troubleshooting

22. The waveforms given in Figure 8–56(a) are observed at the indicated points in Figure 8–56(b). Is the circuit operating properly? If not, what is a likely fault?

 


FIGURE 8-56

23. The waveforms shown for the window comparator in Figure 8-57 are measured. Determine if the output waveform is correct and, if not, specify the possible fault(s).

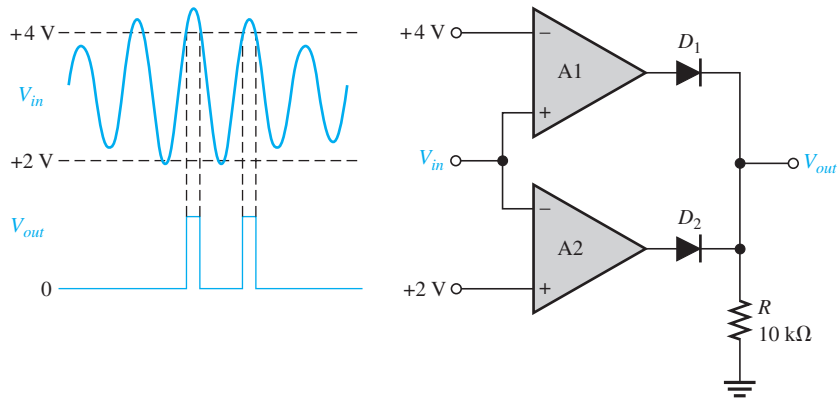


FIGURE 8-57

24. The sequences of voltage levels shown in Figure 8-58 are applied to the summing amplifier and the indicated output is observed. First, determine if this output is correct. If it is not correct, determine the fault.

 


FIGURE 8-58

25. The given ramp voltages are applied to the op-amp circuit in Figure 8–59. Is the given output correct? If it isn't, what is the problem?

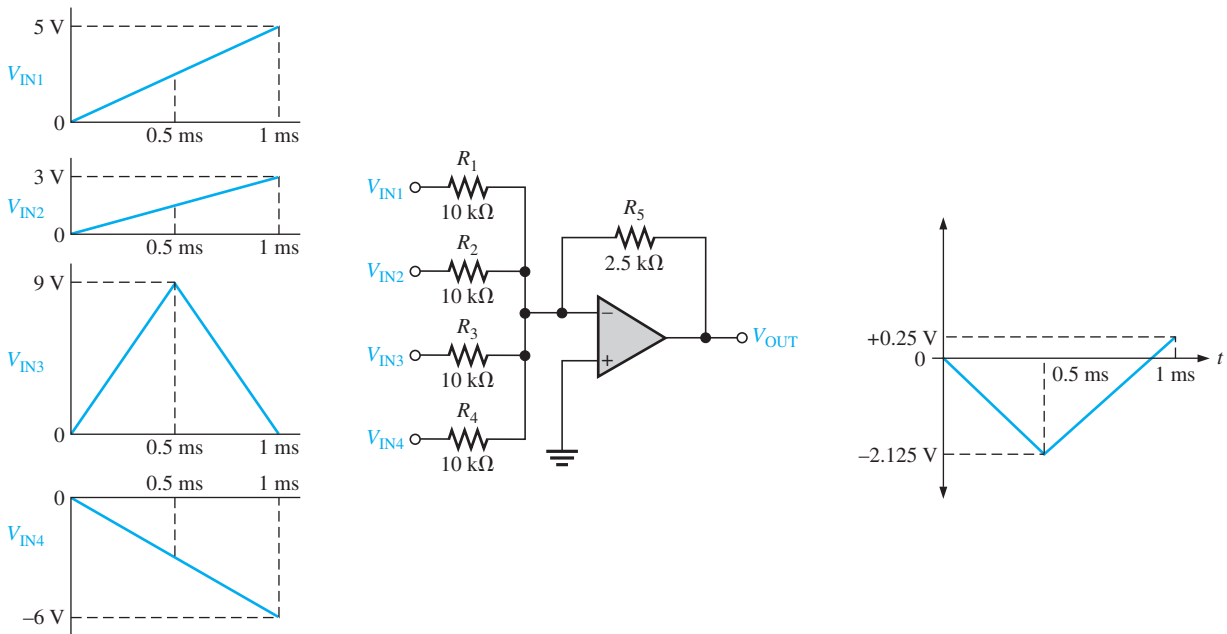


FIGURE 8–59

26. The ADC board from System Example 8–2 has just come off the assembly line and a pass/fail test indicates that it doesn't work. The board now comes to you for troubleshooting. What is the very first thing you should do? Can you isolate the problem(s) by this first step in this case?

MULTISIM TROUBLESHOOTING PROBLEMS

MULTISIM



27. Open file P08-27 and determine the fault.
28. Open file P08-28 and determine the fault.
29. Open file P08-29 and determine the fault.
30. Open file P08-30 and determine the fault.
31. Open file P08-31 and determine the fault.
32. Open file P08-32 and determine the fault.
33. Open file P08-33 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 8-1

1. (a) $V = (10\text{ k}\Omega/110\text{ k}\Omega)15\text{ V} = 1.36\text{ V}$
 (b) $V = (22\text{ k}\Omega/69\text{ k}\Omega)(-12\text{ V}) = -3.83\text{ V}$
2. Hysteresis makes the comparator noise-free.
3. Bounding limits the output amplitude to a specified level.
4. The divider string sets up a separate threshold voltage for each comparator.

SECTION 8-2

1. The summing point is the point where the input resistors are commonly connected.
2. $R_f/R = 1/5 = 0.2$
3. $5\text{ k}\Omega$
4. The fixed resistors set the maximum gain for the channel.

SECTION 8-3

1. The feedback element in an integrator is a capacitor.
2. The capacitor voltage is linear because the capacitor current is constant.
3. The feedback element in a differentiator is a resistor.
4. The output of a differentiator is proportional to the rate of change of the input.

SECTION 8-4

1. $I_L = 6.8 \text{ V}/10 \text{ k}\Omega = 0.68 \text{ mA}$; same value to $5 \text{ k}\Omega$ load.
2. The feedback resistor is the constant of proportionality.

SECTION 8-5

1. An op-amp can fail with a shorted output.
2. Replace suspected components one by one.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 8-1 1.96 V
 8-2 +3.83 V, -3.83 V, $V_{\text{HYS}} = 7.65 \text{ V}$
 8-3 +1.81 V, -1.81 V
 8-4 -12.5 V
 8-5 -5.73 V
 8-6 Changes require an additional 100 k Ω input resistor and a change of R_f to 20 k Ω .
 8-7 0.45, 0.12, 0.18; $V_{\text{OUT}} = -3.03 \text{ V}$
 8-8 Change C to 5000 pF or change R to 5.0 k Ω .
 8-9 Same waveform with an amplitude of 6.6 V
 8-10 A pulse from -0.88 V to +7.79 V
 8-11 -3.76 V
 8-12 Change R_6 to 25 k Ω .

ANSWERS TO SELF-TEST

1. (c) 2. (a) 3. (c) 4. (e) 5. (b) 6. (d) 7. (c)
 8. (a) 9. (c) 10. (a) 11. (b) 12. (c) 13. (b) 14. (d)
 15. (d) 16. (a) 17. (d) 18. (c)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. decrease 2. increase 3. increase 4. increase
 5. increase 6. increase 7. not change 8. increase
 9. not change 10. decrease 11. increase 12. not change

CHAPTER 9

ACTIVE FILTERS

OUTLINE

- 9-1 Basic Filter Responses
- 9-2 Filter Response Characteristics
- 9-3 Active Low-Pass Filters
- 9-4 Active High-Pass Filters
- 9-5 Active Band-Pass Filters
- 9-6 Active Band-Stop Filters
- 9-7 Filter Response Measurements

OBJECTIVES

- Describe the gain-versus-frequency responses of the basic filters
- Describe the three basic filter response characteristics and other filter parameters
- Understand active low-pass filters
- Understand active high-pass filters
- Understand active band-pass filters
- Understand active band-stop filters
- Discuss two methods for measuring frequency response

KEY TERMS

Filter	High-pass filter
Critical frequency	Band-pass filter
Low-pass filter	Band-stop filter
Pole	Damping factor
Roll-off	Order

INTRODUCTION

Power supply filters were introduced in Chapter 2. In this chapter, active filters used for signal processing are introduced. Filters are circuits that are capable of passing input signals with certain selected frequencies through to the output while rejecting signals with other frequencies. This property is called *selectivity*.

Active filters use devices such as transistors or op-amps combined with passive RC , RL , or RLC networks. The active devices provide voltage gain and the passive networks provide frequency selectivity. In terms of general response, there are four basic categories of active filters: low-pass, high-pass, band-pass, and band-stop. In this chapter, you will study active filters using op-amps and RC networks.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

9–1 BASIC FILTER RESPONSES

Filters are usually categorized by the manner in which the output voltage varies with the frequency of the input voltage. The categories of active filters are low-pass, high-pass, band-pass, and band-stop. We will examine each of these general responses in this section.

After completing this section, you should be able to

- Describe the gain-versus-frequency responses of the basic filters
 - Explain the low-pass response
 - Determine the critical frequency and bandwidth of a low-pass filter
 - Explain the high-pass response
 - Determine the critical frequency of a high-pass filter
 - Explain the band-pass response
 - Explain the significance of the quality factor
 - Determine the critical frequency, bandwidth, quality factor, and damping factor of a band-pass filter
 - Explain the band-stop response

Low-Pass Filter Response

A **filter** is a circuit that passes certain frequencies and attenuates or rejects all other frequencies. The **passband** of a filter is the region of frequencies that are allowed to pass through the filter with minimum attenuation (usually defined as less than -3 dB). The **critical frequency**, f_c (also called the *cutoff frequency*), defines the end of the passband and is normally specified at the point where the response drops -3 dB (70.7%) from the passband response. Following the passband is a region called *the transition region* that leads into a region called the *stopband*. There is no precise point between the transition region and the stopband.

A **low-pass filter** is one that passes frequencies from dc to f_c and significantly attenuates all other frequencies. The passband of the ideal low-pass filter is shown in the blue shaded area of Figure 9–1(a); the response drops to zero at frequencies beyond the passband. This ideal response is sometimes referred to as a “brick wall” because nothing gets through beyond the wall. The bandwidth of an ideal low-pass filter is equal to f_c .

$$BW = f_c \quad (9-1)$$


The ideal response shown in Figure 9–1(a) is not attainable by any practical filter. Actual filter responses depend on the number of **poles**, a term used with filters to describe the number of bypass circuits contained in the filter.¹ The most basic low-pass filter is a simple RC network consisting of just one resistor and one capacitor; the output is taken across the capacitor as shown in Figure 9–1(b). This basic RC filter has a single pole and it rolls off at -20 dB/decade beyond the critical frequency. The actual response is indicated by the colored line in Figure 9–1(a). The response is plotted on a standard log plot that is used for filters to show details of the curve as the gain drops. Notice that the gain is almost constant until the frequency is at the critical frequency; after this, the gain drops rapidly at a fixed **roll-off** rate.

The -20 dB/decade roll-off rate for the gain of a basic RC filter means that at a frequency of $10f_c$, the output will be -20 dB (10%) of the input. This rather gentle roll-off is not a particularly good filter characteristic because too much of the unwanted frequencies (beyond the passband) are allowed through the filter.


The critical frequency of the simple low-pass RC filter occurs when $X_C = R$, where

$$f_c = \frac{1}{2\pi RC}$$

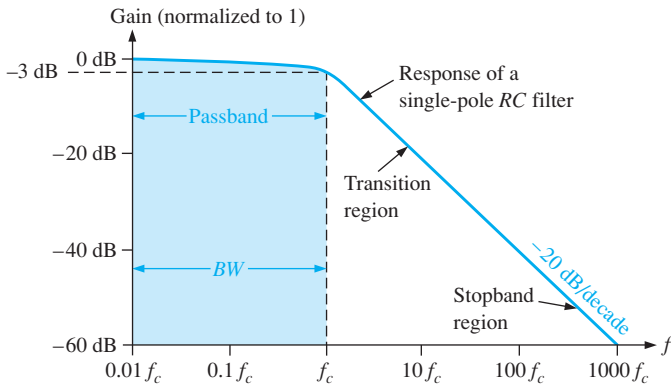
¹A pole is also used to describe certain complex mathematical characteristics of the transfer function for the filter.



 (a) Comparison of an ideal low-pass filter response with actual response



(b) Basic low-pass circuit

 

(c) Idealized low-pass filter responses

FIGURE 9-1 Low-pass filter responses.


Recall from your basic dc/ac course that the output at the critical frequency is 70.7% of the input. This response is equivalent to an attenuation of -3 dB.

Figure 9-1(c) illustrates several idealized low-pass response curves, including the basic one pole response (-20 dB/decade). The approximations show a *flat* response to the cutoff frequency and a roll-off at a constant rate after the cutoff frequency. Actual filters do not have a perfectly flat response to the cutoff frequency but have dropped to -3 dB at this point as described previously.


In order to produce a filter that has a steeper transition region (and hence form a more effective filter), it is necessary to add additional circuitry to the basic filter. Responses that are steeper than -20 dB/decade in the transition region cannot be obtained by simply cascading identical *RC* stages (due to loading effects). However, by combining an op-amp with frequency-selective feedback networks, filters can be designed with roll-off rates of -40 , -60 , or more dB/decade. Filters that include one or more op-amps in the design are called **active filters**. These filters can optimize the roll-off rate or other attribute (such as phase response) with a particular filter design. In general, the more poles the filter uses, the steeper its transition region will be. The exact response depends on the type of filter and the number of poles.

High-Pass Filter Response


A **high-pass filter** is one that significantly attenuates or rejects all frequencies below f_c and passes all frequencies above f_c . The critical frequency is, again, the frequency at which the output is 70.7% of the passband (or -3 dB) as shown in Figure 9-2(a). The ideal response, indicated by the color-shaded area, has an instantaneous drop at f_c , which, of course, is not achievable. Ideally, the passband of a high-pass filter is all frequencies above the critical frequency. The high-frequency response of practical circuits is limited by the op-amp or other components that make up the filter.

 

 (a) Comparison of an ideal high-pass filter response with actual response



(b) Basic high-pass circuit

 

(c) Idealized high-pass filter responses

FIGURE 9-2 High-pass filter responses.

A simple *RC* network consisting of a single resistor and capacitor can be configured as a high-pass filter by taking the output across the resistor as shown in Figure 9-2(b). As in the case of the low-pass filter, the basic *RC* network has a roll-off rate of -20 dB/decade as indicated by the colored line in Figure 9-2(a). Also, the critical frequency for the basic high-pass filter occurs when $X_C = R$, where

$$f_c = \frac{1}{2\pi RC}$$

Figure 9-2(c) illustrates several idealized high-pass response curves including the basic one pole response (-20 dB/decade) for a basic *RC* network. As in the case of the low-pass filter, the approximations show a *flat* response to the cutoff frequency and a roll-off at a constant rate after the cutoff frequency. Actual high-pass filters do not have the perfectly flat response indicated or the precise roll-off rate shown. Responses that are steeper than -20 dB/decade in the transition region are also possible with active high-pass filters; the particular response depends on the type of filter and the number of poles.

Band-Pass Filter Response

A **band-pass filter** passes all signals lying within a band between a lower-frequency limit and an upper-frequency limit and essentially rejects all other frequencies that are outside this specific band. The high-frequency tuned amplifiers introduced in Section 5-2 used tuned circuits as band-pass filters. A generalized band-pass response curve is shown in Figure 9-3. The *bandwidth (BW)* is defined as the difference between the upper critical frequency (f_{c2}) and the lower critical frequency (f_{c1}).

$$BW = f_{c2} - f_{c1} \tag{9-2}$$

 


FIGURE 9-3 General band-pass response curve.

The critical frequencies are the points at which the response curve is 70.7% of its maximum. These critical frequencies are also called *3 dB frequencies*. The frequency about which the passband is centered is called the *center frequency*, f_0 , defined as the geometric mean of the critical frequencies.

$$f_0 = \sqrt{f_{c1}f_{c2}} \quad (9-3)$$

QUALITY FACTOR Recall from Section 5-2 that the quality factor (Q) of a band-pass filter was defined as the ratio of the center frequency to the bandwidth.

$$Q = \frac{f_0}{BW} \quad (9-4)$$

The value of Q is an indication of the selectivity of a band-pass filter. The higher the value of Q , the narrower the bandwidth and the better the selectivity for a given value of f_0 . Band-pass filters are sometimes classified as narrow-band ($Q > 10$) or wide-band ($Q < 10$). The Q can also be expressed in terms of the damping factor (DF) of the filter as

$$Q = \frac{1}{DF}$$

You will study the damping factor in Section 9-2.

EXAMPLE 9-1

A certain band-pass filter has a center frequency of 15 kHz and a bandwidth of 1 kHz. Determine the Q and classify the filter as narrow-band or wide-band.

SOLUTION

$$Q = \frac{f_0}{BW} = \frac{15 \text{ kHz}}{1 \text{ kHz}} = 15$$

Because $Q > 10$, this is a **narrow-band** filter.

PRACTICE EXERCISE*

If the Q of the filter is doubled, what will the bandwidth be?


* Answers are at the end of the chapter.

Band-Stop Filter Response

Another category of active filter is the **band-stop filter**, also known as the *notch*, *band-reject*, or *band-elimination filter*. A general response curve for a band-stop filter is shown

in Figure 9–4. Notice that the bandwidth is the band of frequencies between the 3 dB points, just as in the case of the band-pass filter response. You can think of the operation as opposite to that of the band-pass filter because frequencies within a certain bandwidth are rejected, and frequencies outside the bandwidth are passed.

FIGURE 9–4 General band-stop filter response.

 

There is a less known category of active filter referred to as an *all-pass filter*. A basic schematic of a second-order all-pass filter is shown in Figure SN9–1. As the name implies, an all-pass filter has constant gain across its entire frequency range. Instead of attenuating some range of frequencies, the all-pass filter introduces a phase shift that is linear with frequency. Phase shift is 0° at the low end of its frequency range and -180° at the high end (or -180° to -360°). All-pass filters are usually described by the frequency at which the phase shift between input and output signals equals -90° , or one-quarter wavelength. Like other types of filters, all-pass filters can be cascaded to produce higher-order filters.


 


FIGURE SN9–1 A second-order all-pass filter schematic

One common system application for all-pass filters is in active audio used in stereo systems. An active crossover uses low-pass and high-pass active filters to separate the signals to the high-frequency amplifier that drives the tweeters and the low-frequency amplifier that drives the woofers. These filters introduce phase shift, and properly designed all-pass filters can be used to realign the phase of the low-and high-frequency signals. All-pass filters are also used extensively in digital audio signal processing and in high-frequency communication systems such as single-sideband suppressed carrier (SSB-SC) systems, which are used by the military and radio amateurs..

 

SECTION 9-1 CHECKUP*

1. What determines the bandwidth of a low-pass filter?
2. What limits the bandwidth of an active high-pass filter?
3. How are the Q and the bandwidth of a band-pass filter related? Explain how the selectivity is affected by the Q of a filter.
4. What is an all-pass filter and what characteristic is used to specify it?

* Answers are at the end of the chapter.

9-2 FILTER RESPONSE CHARACTERISTICS

Each type of filter (low-pass, high-pass, band-pass, or band-stop) can be tailored by circuit component values to have either a Butterworth, Chebyshev, or Bessel characteristic. Each of these characteristics is identified by the shape of the response curve, and each has an advantage in certain applications.

After completing this section, you should be able to

- Describe the three basic filter response characteristics and other filter parameters
 - Describe the Butterworth characteristic
 - Describe the Chebyshev characteristic
 - Describe the Bessel characteristic
- Define *damping factor* and discuss its significance
- Calculate the damping factor of a filter
- Discuss the order of a filter and its effect on the roll-off rate

Butterworth, Chebyshev, or Bessel response characteristics can be realized with most active filter circuit configurations by proper selection of certain component values. A general comparison of the three response characteristics for a low-pass filter response curve is shown in Figure 9-5. High-pass, band-pass, and band-stop filters can also be designed to have any one of the characteristics.

THE BUTTERWORTH CHARACTERISTIC The **Butterworth** characteristic provides a very flat amplitude response in the passband and a roll-off rate of -20 dB/decade/pole. The phase response is not linear, however, and the phase shift (thus, time delay) of signals passing through the filter varies nonlinearly with frequency. Therefore, a pulse applied to a filter with a Butterworth response will cause overshoots on the output because each frequency component of the pulse's rising and falling edges experiences a different time delay. Filters with the Butterworth response are normally used when all frequencies in the passband must have the same gain. The Butterworth response is often referred to as a *maximally flat response*.

THE CHEBYSHEV CHARACTERISTIC Filters with the **Chebyshev** response characteristic are useful when a rapid roll-off is required because it provides a roll-off rate greater than -20 dB/decade/pole. This is a greater rate than that of the Butterworth, so filters can be implemented with the Chebyshev response with fewer poles and less complex circuitry for a given roll-off rate. This type of filter response is characterized by overshoot or ripples in the passband (depending on the number of poles) and an even less linear phase response than the Butterworth.

 


FIGURE 9-5 Comparative plots of three types of filter response characteristics.

THE BESSEL CHARACTERISTIC The **Bessel** response exhibits a linear phase characteristic, meaning that the phase shift increases linearly with frequency. The result is almost no overshoot on the output with a pulse input. For this reason, filters with the Bessel response are used for filtering pulse waveforms without distorting the shape of the waveform.

The Damping Factor

As mentioned, an active filter can be designed to have either a Butterworth, Chebyshev, or Bessel response characteristic regardless of whether it is a low-pass, high-pass, band-pass, or band-stop type. The **damping factor (DF)** of an active filter circuit determines which response characteristic the filter exhibits. To explain the basic concept, a generalized active filter is shown in Figure 9–6. It includes an amplifier, a negative feedback network, and a filter section. The amplifier and feedback network are connected in a noninverting configuration. The damping factor is determined by the negative feedback network and is defined by the following equation:

$$DF = 2 - \frac{R_1}{R_2} \quad (9-5)$$

Basically, the damping factor affects the filter response by negative feedback action. Any attempted increase or decrease in the output voltage is offset by the opposing effect of the negative feedback. This tends to make the response curve flat in the passband of the filter if the value for the damping factor is precisely set. By advanced mathematics, which we will not cover, values for the damping factor have been derived for various orders of filters to achieve the maximally flat response of the Butterworth characteristic.

The value of the damping factor required to produce a desired response characteristic depends on the **order** (number of poles) of the filter. Recall that the more poles a filter has, the faster its roll-off rate is. To achieve a second-order Butterworth response, for example, the damping factor must be 1.414. To implement this damping factor, the feedback resistor ratio must be

$$\frac{R_1}{R_2} = 2 - DF = 2 - 1.414 = 0.586$$

This ratio gives the closed-loop gain of the noninverting filter amplifier, $A_{cl(NI)}$, a value of 1.586, derived as follows:

$$A_{cl(NI)} = \frac{1}{B} = \frac{1}{R_2/(R_1 + R_2)} = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + 1 = 0.586 + 1 = 1.586$$

EXAMPLE 9–2

If resistor R_2 in the feedback network of an active two-pole filter of the type in Figure 9–6 is 10 k Ω , what value must R_1 be to obtain a maximally flat Butterworth response?

SOLUTION

$$\frac{R_1}{R_2} = 0.586$$

$$R_1 = 0.586 R_2 = 0.586(10 \text{ k}\Omega) = \mathbf{5.86 \text{ k}\Omega}$$

Using the nearest standard 5 percent value of 5600 Ω will get very close to the ideal Butterworth response.

PRACTICE EXERCISE

What is the damping factor for $R_2 = 10 \text{ k}\Omega$ and $R_1 = 5.6 \text{ k}\Omega$?

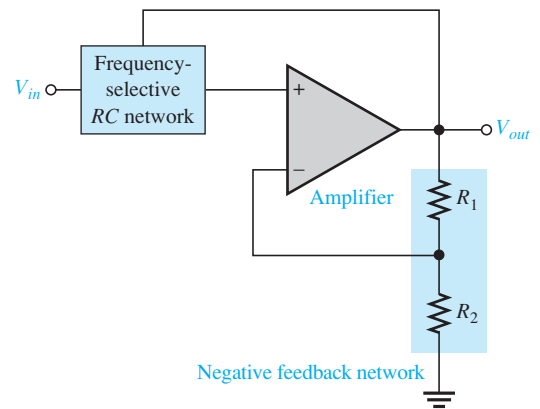


FIGURE 9–6 General diagram of an active filter. Note that R_1 corresponds to R_f and R_2 corresponds to R_i as defined in Chapter 6.

Critical Frequency and Roll-Off Rate

The critical frequency is determined by the values of the resistor and capacitors in the RC network, as shown in Figure 9-6. For a single-pole (first-order) filter, as shown in Figure 9-7, the critical frequency is

$$f_c = \frac{1}{2\pi RC}$$

Although we show a low-pass configuration, the same formula is used for the f_c of a single-pole high-pass filter. The number of poles determines the roll-off rate of the filter. A Butterworth response produces -20 dB/decade/pole. So a first-order (one-pole) filter has a roll-off of -20 dB/decade; a second-order (two-pole) filter has a roll-off rate of -40 dB/decade; a third-order (three-pole) filter has a roll-off rate of -60 dB/decade; and so on.

Generally, to obtain a filter with three poles or more, one-pole or two-pole filters are cascaded, as shown in Figure 9-8. To obtain a third-order filter, for example, cascade a second-order and a first-order filter; to obtain a fourth-order filter, cascade two second-order filters; and so on. Each filter in a cascaded arrangement is called a *stage* or *section*.

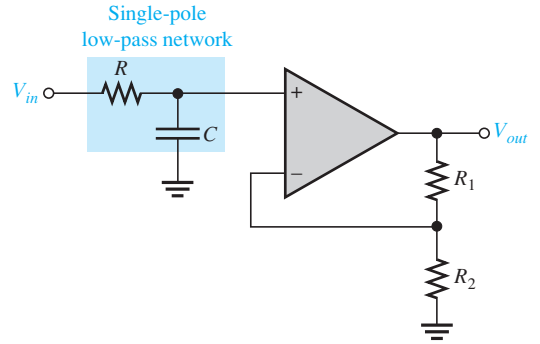


FIGURE 9-7 First-order (one-pole) low-pass filter.

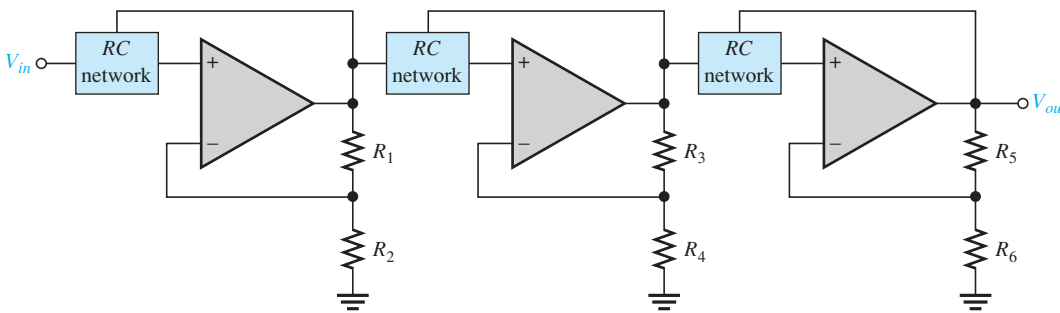


FIGURE 9-8 The number of filter poles can be increased by cascading.

Because of its maximally flat response, the Butterworth characteristic is the most widely used. Therefore, we will limit our coverage to the Butterworth response to illustrate basic filter concepts. Table 9-1 lists the roll-off rates, damping factors, and feedback resistor ratios for up to sixth-order Butterworth filters.

TABLE 9-1 • Values for the Butterworth response.										
ORDER	ROLL-OFF DB/DECADE	1ST STAGE			2ND STAGE			3RD STAGE		
		POLES	DF	R_1/R_2	POLES	DF	R_3/R_4	POLES	DF	R_5/R_6
1	-20	1	Optional							
2	-40	2	1.414	0.586						
3	-60	2	1.00	1	1	1.00	1			
4	-80	2	1.848	0.152	2	0.765	1.235			
5	-100	2	1.00	1	2	1.618	0.382	1	0.618	1.382
6	-120	2	1.932	0.068	2	1.414	0.586	2	0.518	1.482

SECTION 9-2 CHECKUP

1. Explain how Butterworth, Chebyshev, and Bessel responses differ.
2. What determines the response characteristic of a filter?
3. Name the basic parts of an active filter.

9-3 ACTIVE LOW-PASS FILTERS

Filters that use op-amps as the active element provide several advantages over passive filters (R , L , and C elements only). The op-amp provides gain so that the signal is not attenuated as it passes through the filter. The high input impedance of the op-amp prevents excessive loading of the driving source, and the low output impedance of the op-amp prevents the filter from being affected by the load that it is driving. Active filters are also easy to adjust over a wide frequency range without altering the desired response.

After completing this section, you should be able to

- Understand active low-pass filters
 - Identify a single-pole filter and determine its gain and critical frequency
 - Identify a two-pole Sallen-Key filter and determine its gain and critical frequency
 - Explain how a higher roll-off rate is achieved by cascading low-pass filters

MULTISIM



Open file F09-09 found on the companion website. This simulation demonstrates the operation of a single-pole low-pass active filter using a Bode plotter to measure frequency and phase response.

A Single-Pole Filter

Figure 9-9(a) shows an active filter with a single low-pass RC network that provides a roll-off of -20 dB/decade above the critical frequency, as indicated by the response curve in Figure 9-9(b). The critical frequency of the single-pole filter is $f_c = 1/2\pi RC$. The op-amp in this filter is connected as a noninverting amplifier with the closed-loop voltage gain in the passband set by the values of R_1 and R_2 .

$$A_{cl(NI)} = \frac{R_1}{R_2} + 1$$

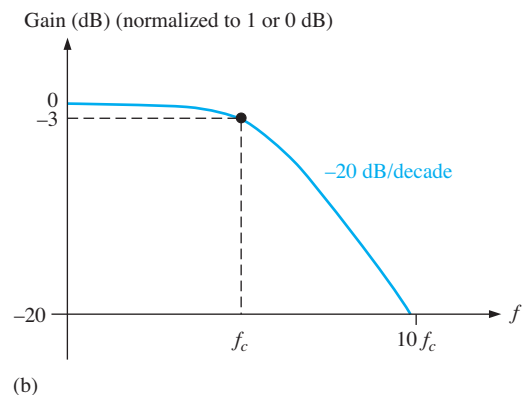
 


FIGURE 9-9 Single-pole active low-pass filter and response curve.


The Sallen-Key Low-Pass Filter

The Sallen-Key is one of the most common configurations for a second-order (two-pole) filter. It is also known as a VCVS (voltage-controlled voltage source) filter. A low-pass version of the Sallen-Key filter is shown in Figure 9-10. Notice that there are two low-pass RC networks that provide a roll-off of -40 dB/decade above the critical frequency (assuming a Butterworth characteristic). One RC network consists of R_A and C_A , and the second network consists of R_B and C_B . A unique feature is the capacitor C_A that provides feedback for shaping the response near the edge of the passband. The critical frequency for the second-order Sallen-Key filter is

$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}} \quad (9-6)$$

For simplicity, the component values can be made equal so that $R_A = R_B = R$ and $C_A = C_B = C$. In this case, the expression for the critical frequency simplifies to $f_c = 1/2\pi RC$.

FIGURE 9-10 Basic Sallen-Key second-order low-pass filter.

 

As in the single-pole filter, the op-amp in the second-order Sallen-Key filter acts as a noninverting amplifier with the negative feedback provided by the R_1/R_2 network. As you have learned, the damping factor is set by the values of R_1 and R_2 , thus making the filter response either Butterworth, Chebyshev, or Bessel. For example, from Table 9-1, the R_1/R_2 ratio must be 0.586 to produce the damping factor of 1.414 required for a second-order Butterworth response.

EXAMPLE 9-3

Determine the critical frequency of the low-pass filter in Figure 9-11, and set the value of R_1 for an approximate Butterworth response.

 


FIGURE 9-11

SOLUTION

Since $R_A = R_B = 1.0 \text{ k}\Omega$ and $C_A = C_B = 0.02 \text{ }\mu\text{F}$,

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.0 \text{ k}\Omega)(0.02 \text{ }\mu\text{F})} = 7.96 \text{ kHz}$$

For a Butterworth response, $R_1/R_2 = 0.586$.

$$R_1 = 0.586R_2 = 0.586(1.0 \text{ k}\Omega) = 586 \text{ }\Omega$$

Select a standard value as near as possible to this calculated value.

PRACTICE EXERCISE


Determine f_c for Figure 9–11 if $R_A = R_B = R_2 = 2.2 \text{ k}\Omega$ and $C_A = C_B = 0.01 \text{ }\mu\text{F}$. Also determine the value of R_1 for a Butterworth response.

MULTISIM


Open file F09-11 found on the companion website. This simulation demonstrates the operation of a Sallen-Key low-pass filter.

Cascaded Low-Pass Filters Achieve a Higher Roll-Off Rate

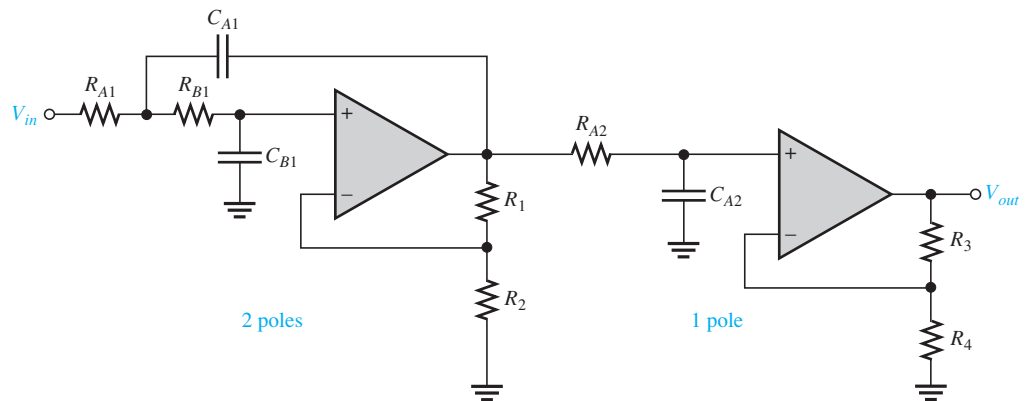A three-pole filter is required to get a third-order low-pass response (-60 dB/decade). This is done by cascading a two-pole low-pass filter and a single-pole low-pass filter, as shown in Figure 9–12(a). Figure 9–12(b) shows a four-pole configuration obtained by cascading two two-pole filters.



(a) Third-order configuration

 

(b) Fourth-order configuration

FIGURE 9–12 Cascaded low-pass filters.

EXAMPLE 9-4

For the four-pole filter in Figure 9-12(b), determine the capacitance values required to produce a critical frequency of 2680 Hz if all the resistors in the RC low-pass networks are 1.8 k Ω . Also select values for the feedback resistors to get a Butterworth response.

SOLUTION

Both stages must have the same f_c . Assuming equal-value capacitors,

$$f_c = \frac{1}{2\pi RC}$$

$$C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi(1.8 \text{ k}\Omega)(2680 \text{ Hz})} = 0.033 \mu\text{F}$$

$$C_{A1} = C_{B1} = C_{A2} = C_{B2} = \mathbf{0.033 \mu\text{F}}$$

Also select $R_2 = R_4 = 1.8 \text{ k}\Omega$ for simplicity. Refer to Table 9-1. For a Butterworth response in the first stage, $DF = 1.848$ and $R_1/R_2 = 0.152$. Therefore,

$$R_1 = 0.152R_2 = 0.152(1800 \Omega) = \mathbf{274 \Omega}$$

Choose $R_1 = 270 \Omega$.

In the second stage, $DF = 0.765$ and $R_3/R_4 = 1.235$. Therefore,

$$R_3 = 1.235R_4 = 1.235(1800 \Omega) = \mathbf{2.22 \text{ k}\Omega}$$

Choose $R_3 = 2.2 \text{ k}\Omega$.

PRACTICE EXERCISE

For the filter in Figure 9-12(b), determine the capacitance values for $f_c = 1 \text{ kHz}$ if all the filter resistors are 680 Ω . Also specify the values for the feedback resistors to produce a Butterworth response.

SYSTEM EXAMPLE 9-1**AN RFID SYSTEM**

The system in this example uses both analog and digital signals together. The system is for radio-frequency identification (RFID), which is widely used for tracking objects.

RFID systems are used in a number of applications including:

- Metering applications such as electronic toll collection
- Inventory control and tracking such as merchandise control
- Asset tracking and recovery
- Tracking parts moving through a manufacturing process
- Tracking goods in a supply chain

Typically, an RFID system contains an *RFID* tag that consists of an IC chip attached to the object being tracked, an *RFID* reader that receives transmitted data from the tag, and a *data-processing system* that processes and stores the data passed to it by the reader. A basic block diagram is shown in Figure SE9-1.

Data is stored on the RFID tag in digital form. When interrogated, the tag transmits the data to the reader via a radio signal. The system described here uses amplitude shift keying (ASK), in which a carrier signal is varied (modulated) by the digital data, in “bursts” that represent a stream of 1s and 0s. The digital waveform in Figure SE9-2(a) is

 


FIGURE SE9-1 Basic block diagram of an RFID system.



the signal of interest but the carrier enables it to be transmitted to the receiver. The modulated signal shown in (b) and is the signal received by the receiver.

 


FIGURE SE9-2 Example of ASK modulation transmitted by an RFID tag.

The block diagram of the receiver is shown in Figure SE9-3. The band-pass filter allows the 123 kHz signal to pass and reduces high-frequency noise and other signal sources. The amplifier increases the very small signal from the tag; the rectifier eliminates the negative portions of the modulated signal; the low-pass filter eliminates the 123 kHz carrier frequency but passes the digital modulating signal; and the comparator restores the digital signal to a usable stream of digital data. Our focus here is the low-pass filter in the system.

 


FIGURE SE9-3 Block diagram of RFID reader.

MULTISIM




Open file SE09-03 found on the companion website. This file has the entire schematic for the RFID reader, which allows you to view the signal at the output of each stage.

The schematic for the low-pass filter is shown in Figure SE9-4. Component numbering for this schematic is taken from the overall receiver circuit, which is on the companion website as a Multisim file. Because $R_9 = R_{10}$ and $C_3 = C_4$, the cutoff frequency can be found from

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.1 \text{ kHz})(10 \text{ nF})} = 14.5 \text{ kHz}$$

FIGURE SE9-4 Low-pass filter for RFID reader

 

The 14.5 kHz cutoff will pass the basic shape of the digital signal, but with poor rise and fall times because the rise and fall times have the highest frequency components associated with them. The last step before processing is to send the signal to a comparator, where it is converted to a usable digital signal. The processor can then process the information to identify the object.

SECTION 9-3 CHECKUP

1. How many poles does a second-order low-pass filter have? How many resistors and how many capacitors are used in the frequency-selective network?
2. Why is the damping factor of a filter important?
3. What is the primary purpose of cascading low-pass filters?

9-4 ACTIVE HIGH-PASS FILTERS

In high-pass filters, the roles of the capacitor and resistor are reversed in the RC networks. Otherwise, the basic parameters are the same as for the low-pass filters.

After completing this section, you should be able to

- Understand active high-pass filters
 - Identify a single-pole filter and determine its gain and critical frequency
 - Identify a two-pole Sallen-Key filter and determine its gain and critical frequency
 - Explain how a higher roll-off rate is achieved by cascading high-pass filters

A Single-Pole Filter

A high-pass active filter with a -20 dB/decade roll-off is shown in Figure 9-13(a). Notice that the input circuit is a single high-pass RC network. The negative feedback network is the same as for the low-pass filters previously discussed. The high-pass response curve is shown in Figure 9-13(b).



 


FIGURE 9-13 Single-pole active high-pass filter and response curve.

Ideally, a high-pass filter passes all frequencies above f_c without limit, as indicated in Figure 9–14(a), although in practice, this is not the case. As you have learned, all op-amps inherently have internal RC networks that limit the amplifier's response at high frequencies. Therefore, there is an upper-frequency limit on the high-pass filter's response which, in effect, makes it a band-pass filter with a very wide bandwidth. In the majority of applications, the internal high-frequency limitation is so much greater than that of the filter's f_c that the limitation can be neglected. In some applications, special current-feedback op-amps or discrete transistors are used for the gain element to increase the high-frequency limitation beyond that realizable with standard op-amps.

 

(a) Ideal

 


(b) Nonideal

FIGURE 9–14 High-pass filter response.

The Sallen-Key High-Pass Filter

A high-pass second-order Sallen-Key configuration is shown in Figure 9–15. The components R_A , C_A , R_B , and C_B form the two-pole frequency-selective network. Notice that the positions of the resistors and capacitors in the frequency-selective network are opposite to those in the low-pass configuration. As with the other filters, the response characteristic can be optimized by proper selection of the feedback resistors, R_1 and R_2 .

 **FIGURE 9–15** Basic Sallen-Key second-order high-pass filter.

EXAMPLE 9-5

Choose values for the Sallen-Key high-pass filter in Figure 9-15 to implement an equal-value second-order Butterworth response with a critical frequency of approximately 10 kHz.

SOLUTION

Start by selecting a value for R_A and R_B (R_1 or R_2 can also be the same value as R_A and R_B for simplicity).

$$R = R_A = R_B = R_2 = 3.3 \text{ k}\Omega \quad (\text{an arbitrary selection})$$

Next, calculate the capacitance value from $f_c = 1/2\pi RC$.

$$C = C_A = C_B = \frac{1}{2\pi R f_c} = \frac{1}{2\pi(3.3 \text{ k}\Omega)(10 \text{ kHz})} = 0.0048 \text{ }\mu\text{F}$$

For a Butterworth response, the damping factor must be 1.414 and $R_1/R_2 = 0.586$.

$$R_1 = 0.586R_2 = 0.586(3.3 \text{ k}\Omega) = 1.93 \text{ k}\Omega$$

If you had chosen $R_1 = 3.3 \text{ k}\Omega$, then

$$R_2 = \frac{R_1}{0.586} = \frac{3.3 \text{ k}\Omega}{0.586} = 5.63 \text{ k}\Omega$$

Either way, an approximate Butterworth response is realized by choosing the nearest standard values.

PRACTICE EXERCISE

Select values for all the components in the high-pass filter of Figure 9-15 to obtain an $f_c = 300 \text{ Hz}$. Use equal-value components and optimize for a Butterworth response.

Cascading High-Pass Filters

As with the low-pass configuration, first- and second-order high-pass filters can be cascaded to provide three or more poles and thereby create faster roll-off rates. Figure 9-16 shows a six-pole high-pass filter consisting of three two-pole stages. With this configuration optimized for a Butterworth response, a roll-off of -120 dB/decade is achieved.

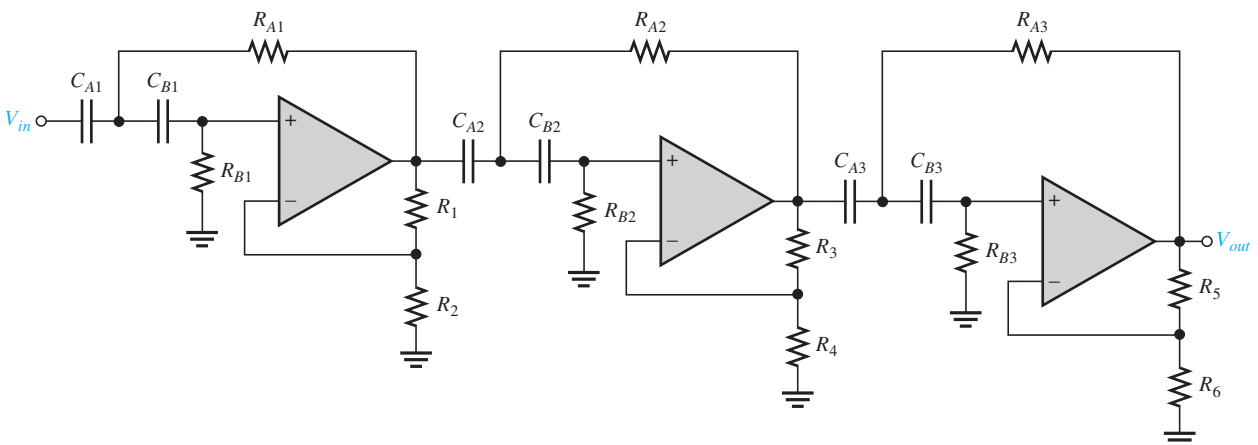


FIGURE 9-16 Sixth-order high-pass filter.

SECTION 9–4 CHECKUP

1. How does a high-pass Sallen-Key filter differ from the low-pass configuration?
2. To increase the critical frequency of a high-pass filter, would you increase or decrease the resistor values?
3. If three two-pole high-pass filters and one single-pole high-pass filter are cascaded, what is the resulting roll-off?

9–5 ACTIVE BAND-PASS FILTERS

As mentioned, band-pass filters pass all frequencies bounded by a lower-frequency limit and an upper-frequency limit and reject all others lying outside this specified band. A band-pass response can be thought of as the overlapping of a low-frequency response curve and a high-frequency response curve.

After completing this section, you should be able to

- Understand active band-pass filters
 - Describe a band-pass filter composed of a low-pass and a high-pass filter
 - Determine the critical frequencies and center frequency of a cascaded band-pass filter
 - Determine center frequency, bandwidth, and gain of multiple-feedback band-pass filters
 - Explain the operation of a state-variable band-pass filter

Cascaded Low-Pass and High-Pass Filters Achieve a Band-Pass Response

One way to implement a band-pass filter is a cascaded arrangement of a high-pass filter and a low-pass filter, as shown in Figure 9–17(a), as long as the critical frequencies are sufficiently separated. Each of the filters shown is a two-pole Sallen-Key Butterworth configuration so that the roll-off rates are -40 dB/decade, indicated in the composite response curve of Figure 9–17(b). The critical frequency of each filter is chosen so that the response curves overlap sufficiently, as indicated. The critical frequency of the high-pass filter must be sufficiently lower than that of the low-pass stage.


The lower frequency, f_{c1} , of the passband is the critical frequency of the high-pass filter. The upper frequency, f_{c2} , is the critical frequency of the low-pass filter. Ideally, as discussed earlier, the center frequency, f_0 , of the passband is the geometric mean of f_{c1} and f_{c2} . The following formulas express the three frequencies of the band-pass filter in Figure 9–17.

$$f_{c1} = \frac{1}{2\pi\sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$


$$f_{c2} = \frac{1}{2\pi\sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

 Of course, if equal-value components are used in implementing each filter, the critical frequency equations simplify to the form $f_c = 1/2\pi RC$.



(a)

 

(b)

FIGURE 9-17 Band-pass filter formed by cascading a two-pole high-pass and a two-pole low-pass filter (it does not matter in which order the filters are cascaded).

MULTISIM



Open file F09-17 found on the companion website. This simulation demonstrates the operation of a two-stage band-pass filter.

Multiple-Feedback Band-Pass Filter

Another type of filter configuration, shown in Figure 9-18, is a multiple-feedback band-pass filter. The two feedback paths are through R_2 and C_1 . Components R_1 and C_1 provide the low-pass response, and R_2 and C_2 provide the high-pass response. The maximum gain, A_0 , occurs at the center frequency. Q values of less than 10 are typical in this type of filter. An expression for the center frequency follows, recognizing that R_1 and R_3 appear in parallel as viewed from the C_1 feedback path (with the V_{in} source replaced by a short).

$$f_0 = \frac{1}{2\pi\sqrt{(R_1 \parallel R_3)R_2C_1C_2}}$$

Making $C_1 = C_2 = C$ gives the following formula (derived in Appendix A):

$$f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1R_2R_3}} \tag{9-7}$$

A convenient value for the capacitors is chosen; then the three resistor values are calculated based on the desired values for f_0 , BW , and A_0 . As you know, the Q can be determined from the relation $Q = f_0/BW$, and the resistors are found using the following formulas (stated without derivation).

 


FIGURE 9-18 Multiple-feedback band-pass filter.

$$R_1 = \frac{Q}{2\pi f_0 C A_0}$$

$$R_2 = \frac{Q}{\pi f_0 C}$$

$$R_3 = \frac{Q}{2\pi f_0 C (2Q^2 - A_0)}$$

To develop a gain expression, we solve for Q in the first two equations above.

$$Q = 2\pi f_0 A_0 C R_1$$

$$Q = \pi f_0 C R_2$$

Then,

$$2\pi f_0 A_0 C R_1 = \pi f_0 C R_2$$

An expression for the maximum gain at the center frequency is


$$A_0 = \frac{R_2}{2R_1} \quad (9-8)$$

In order for the denominator of the equation $R_3 = Q/[2\pi f_0 C (2Q^2 - A_0)]$ to be positive, $A_0 < 2Q^2$, which imposes a limitation on the gain.

EXAMPLE 9-6

Determine the center frequency, maximum gain, and bandwidth for the filter in Figure 9-19.

FIGURE 9-19

 

SOLUTION

$$f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} = \frac{1}{2\pi(0.01 \mu\text{F})} \sqrt{\frac{68 \text{ k}\Omega + 2.7 \text{ k}\Omega}{(68 \text{ k}\Omega)(180 \text{ k}\Omega)(2.7 \text{ k}\Omega)}} = 736 \text{ Hz}$$

$$A_0 = \frac{R_2}{2R_1} = \frac{180 \text{ k}\Omega}{2(68 \text{ k}\Omega)} = 1.32$$

$$Q = \pi f_0 C R_2 = \pi(736 \text{ Hz})(0.01 \mu\text{F})(180 \text{ k}\Omega) = 4.16$$

$$BW = \frac{f_0}{Q} = \frac{736 \text{ Hz}}{4.16} = 177 \text{ Hz}$$

PRACTICE EXERCISE

If R_2 in Figure 9-19 is increased to 330 kΩ, how does this affect the gain, center frequency, and bandwidth of the filter?

MULTISIM



Open file F09-19 found on the companion website. This simulation demonstrates the operation of a multiple-feedback band-pass filter.

SYSTEM EXAMPLE 9-2

System Example 9-1 introduced a radio-frequency identification system (RFID). The block diagram for the receiver is shown again here as Figure SE9-5, but this time the emphasis is on the input block, which is a multiple feedback band-pass filter. The center frequency is set to 123 kHz to allow the high-frequency signal to pass and the bandwidth is set fairly wide.

 
 


FIGURE SE9-5 Basic block diagram of the RFID reader.

Recall that the band-pass filter passes the 123 kHz signal and therefore reduces signals and noise that are outside this band. Our focus in this example is the band-pass filter in the first block of the system. The schematic for the band-pass filter is shown in Figure SE9-6. Component numbering for this schematic is taken from the overall receiver circuit, which is on the companion website as a Multisim file. The center frequency is

$$f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}} = \frac{1}{2\pi(910 \text{ pF})} \sqrt{\frac{1.3 \text{ k}\Omega + 1.0 \text{ k}\Omega}{(1.3 \text{ k}\Omega)(3.6 \text{ k}\Omega)(1.0 \text{ k}\Omega)}} = 123 \text{ kHz}$$

The Q is

$$Q = \pi f_0 C R_2 = \pi(123 \text{ kHz})(910 \text{ pF})(3.6 \text{ k}\Omega) = 1.26$$

The BW is

$$BW = \frac{f_0}{Q} = \frac{123 \text{ kHz}}{1.26} = 97.2 \text{ kHz}$$

 


FIGURE SE9-6 Band-pass filter for RFID reader

The low- Q is reasonable to pass harmonic content of the overall signal. You can test the actual circuit and view the frequency response using the Bode plotter in Multisim.

State-Variable Band-Pass Filter

The state-variable or universal active filter is widely used for band-pass applications. As shown in Figure 9-20, it consists of a summing amplifier and two op-amp integrators (which act as single-pole low-pass filters) that are combined in a cascaded arrangement to form a second-order filter. Although used primarily as a band-pass (BP) filter, the state-variable configuration also provides low-pass (LP) and high-pass (HP) outputs. The center frequency is set by the RC networks in both integrators. When used as a band-pass filter, the critical frequencies of the integrators are usually made equal, thus setting the center frequency of the passband.

 


FIGURE 9-20 State-variable band-pass filter.

BASIC OPERATION At input frequencies below f_c , the input signal passes through the summing amplifier and integrators and is fed back 180° out-of-phase. Thus, the feedback signal and input signal cancel for all frequencies below approximately f_c . As the low-pass response of the integrators rolls off, the feedback signal diminishes, thus allowing the input to pass through to the band-pass output. Above f_c , the low-pass response disappears, thus preventing the input signal from passing through the integrators. As a result, the band-pass output peaks sharply at f_c , as indicated in Figure 9-21. Stable Q s up to 100 can be obtained with this type of filter. The Q is set by the feedback resistors R_5 and R_6 according to the following equation.

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right)$$

The state-variable filter cannot be optimized for low-pass, high-pass, and band-pass performance simultaneously for this reason: To optimize for a low-pass or a high-pass Butterworth response, DF must equal 1.414. Since $Q = 1/DF$, a Q of 0.707 will result. Such a low Q provides a very poor band-pass response (large BW and poor selectivity). For optimization as a band-pass filter, the Q must be set high.

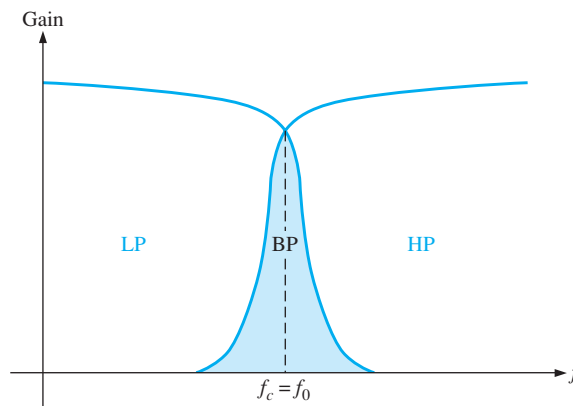


FIGURE 9-21 General state-variable response curves.

EXAMPLE 9-7

Determine the center frequency, Q , and BW for the band-pass output of the state-variable filter in Figure 9-22.

 


FIGURE 9-22

SOLUTION

For each integrator,

$$f_c = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2} = \frac{1}{2\pi(1.0 \text{ k}\Omega)(0.022 \text{ }\mu\text{F})} = 7.23 \text{ kHz}$$

The center frequency is approximately equal to the critical frequencies of the integrators.

$$f_0 = f_c = 7.23 \text{ kHz}$$

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right) = \frac{1}{3} \left(\frac{100 \text{ k}\Omega}{1.0 \text{ k}\Omega} + 1 \right) = 33.7$$

$$BW = \frac{f_0}{Q} = \frac{7.23 \text{ kHz}}{33.7} = 215 \text{ Hz}$$

PRACTICE EXERCISE


Determine f_0 , Q , and BW for the filter in Figure 9-22 if $R_4 = R_6 = R_7 = 330 \text{ }\Omega$ with all other component values the same as shown on the schematic.

MULTISIM

Open file F09-22 found on the companion website. This simulation demonstrates the operation of the state-variable filter as a band-pass filter.

One system application for band-pass filters is found in microwave repeaters. A repeater can be thought of as a rebroadcast station. Microwave systems use *line-of-sight* transmission, so if there is an obstruction between the transmitter and receiver the signal will not be received. A terrestrial repeater is usually mounted in a high-elevation location such as on a tall building, tower, or mountain top. Microwave repeaters can also be space-based on a satellite. To increase the reliability of a repeater, a technique called *frequency diversity* can be used. Two different RF carriers are modulated by the same IF intelligence. Temporary atmospheric conditions that can degrade an RF signal can be very frequency specific, so using more than one carrier frequency increases reliability. Here is how the system works.

At the transmitter the IF frequency is split in half; one half modulates carrier frequency A and the other modulates carrier frequency B. The output from each modulator is then sent through a band-pass filter tuned to that specific carrier frequency. The outputs of both filters are then combined by a channel-combining network and fed to the transmit antenna. At the receive end a channel separator splits the two carriers and each is passed through another band-pass filter. The output from each BPF is down-converted to IF and fed to a quality detector circuit that determines which signal is strongest. The strongest IF signal is then fed to the rest of the system for further demodulation, amplification, and/or signal processing.

 SYSTEM NOTE

SECTION 9-5 CHECKUP

1. What determines selectivity in a band-pass filter?
2. One filter has a $Q = 5$ and another has a $Q = 25$. Which has the narrower bandwidth?
3. List the elements that make up a state-variable filter.
4. What is the gain of the BP filter in Figure SE9-6?

9-6 ACTIVE BAND-STOP FILTERS

Band-stop filters reject a specified band of frequencies and pass all others. The response is opposite to that of a band-pass filter.


After completing this section, you should be able to

- Understand active band-stop filters
- Identify a multiple-feedback band-stop filter
- Explain the operation of a state-variable band-stop filter

Multiple-Feedback Band-Stop Filter

Figure 9-23 shows a multiple-feedback band-stop filter. Notice that this configuration is similar to the band-pass version except that R_3 has been moved and R_4 has been added.


FIGURE 9-23 Multiple-feedback band-stop filter.

 

State-Variable Band-Stop Filter

Summing the low-pass and the high-pass responses of the state-variable filter covered in Section 9-5 creates a band-stop response as shown in Figure 9-24.

FIGURE 9-24 State-variable band-stop filter.

 

EXAMPLE 9-8

Verify that the band-stop filter in Figure 9-25 has a center frequency of 60 Hz, and optimize the filter for a Q of 10.

 


FIGURE 9-25

SOLUTION

f_0 equals the f_c of the integrator stages.

$$f_0 = \frac{1}{2\pi R_4 C_1} = \frac{1}{2\pi R_7 C_2} = \frac{1}{2\pi(12 \text{ k}\Omega)(0.22 \text{ }\mu\text{F})} = 60.3 \text{ Hz}$$

You can obtain a $Q = 10$ by choosing R_6 and then calculating R_5 .

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right) \quad R_5 = (3Q - 1)R_6$$

Choose $R_6 = 3.3 \text{ k}\Omega$. Then

$$R_5 = [3(10) - 1]3.3 \text{ k}\Omega = 95.7 \text{ k}\Omega$$

Choose 100 kΩ as the nearest standard value.

PRACTICE EXERCISE

How would you change the center frequency to 120 Hz in Figure 9-25?

In Section 4-7 you were introduced to switched-capacitor circuits. Switched-capacitor technology is also used in active filters. There are many advantages to using monolithic switched-capacitor ICs over discrete op-amps. Switched-capacitor filters do not require external precision capacitors, their cutoff frequency accuracy is extremely high, and they are less sensitive to temperature variations. A number of parameters such as Q or gain can be controlled with a few external resistors. Another major advantage of switched-capacitor filters is that their cutoff frequency can be varied over a wide range simply by changing the frequency of the external clock, and thus changing the value of the switched-capacitor resistance values.


One example of a switched-capacitor filter IC is the LMF100. This device contains two switched-capacitor filter blocks configured in a manner similar to state-variable filters. Each filter block has three outputs, one for all-pass, high-pass, or band-stop functions. The other two perform band-pass and low-pass functions. With the use of two to four external resistors and an external clock, each block can produce first or second-order filters. By cascading the blocks a single LMF100 can produce a fourth-order filter, and higher-order filters can be realized by cascading ICs. A clock frequency of 3.5 MHz produces the maximum cutoff frequency of 100 kHz with an accuracy of $\pm 0.2\%$. It has an $f_0 \times Q$ range of up to 1.8 MHz, which means that even at 100 kHz the filter Q will be a minimum of 18. All basic filters such as Butterworth, Bessel, and Chebyshev can be produced using the LMF100. The data sheet for the LMF100 can be found at www.national.com.

SYSTEM NOTE

MULTISIM



Open file F09-25 found on the companion website. This simulation demonstrates the operation of the state-variable filter as a band-stop filter.

 

SECTION 9–6 CHECKUP

1. How does a band-stop response differ from a band-pass response?
2. How is a state-variable band-pass filter converted to a band-stop filter?
3. How can you change the frequency response of a switched capacitor filter?

9–7 FILTER RESPONSE MEASUREMENTS

In this section, we discuss two methods of determining a filter's response by measurement—discrete point measurement and swept frequency measurement.

After completing this section, you should be able to

- Discuss two methods for measuring frequency response
- Explain the discrete point measurement method
- Explain the swept frequency measurement method

Discrete Point Measurement

Figure 9–26 shows an arrangement for taking filter output voltage measurements at discrete values of input frequency using common laboratory instruments. The general procedure is as follows:

 


FIGURE 9–26 Test setup for discrete point measurement of the filter response. (Readings are arbitrary and for display only.)


1. Set the amplitude of the sine wave generator to a desired voltage level.
2. Set the frequency of the sine wave generator to a value well below the expected critical frequency of the filter under test. For a low-pass filter, set the frequency as near as possible to 0 Hz. For a band-pass filter, set the frequency well below the expected lower critical frequency.
3. Increase the frequency in predetermined steps sufficient to allow enough data points for an accurate response curve.
4. Maintain a constant input voltage amplitude while varying the frequency.
5. Record the output voltage at each value of frequency.
6. After recording a sufficient number of points, plot a graph of output voltage versus frequency.

If the frequencies to be measured exceed the response of the DMM, an oscilloscope may have to be used instead.


Swept Frequency Measurement

The swept frequency method requires more elaborate test equipment than does the discrete point method, but it is much more efficient and can result in a more accurate response curve. A general test setup is shown in Figure 9–27(a) using a swept frequency generator and a spectrum analyzer. Figure 9–27(b) shows how the test can be made with an oscilloscope instead of a spectrum analyzer.

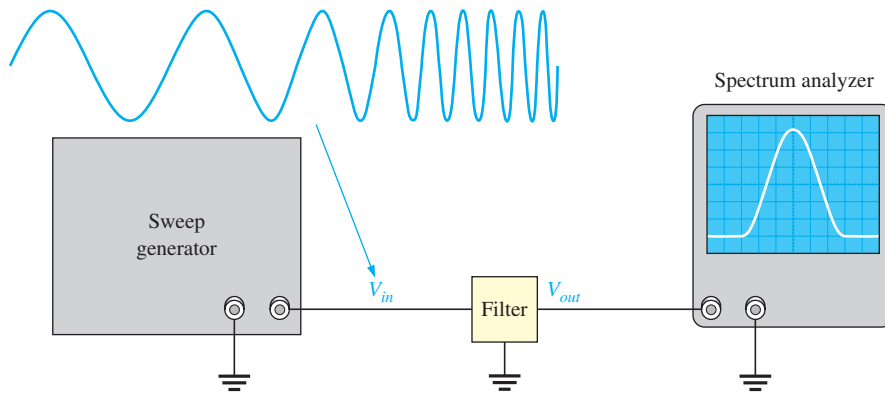The swept frequency generator produces a constant amplitude output signal whose frequency increases linearly between two preset limits, as indicated in Figure 9–27. In part (a),



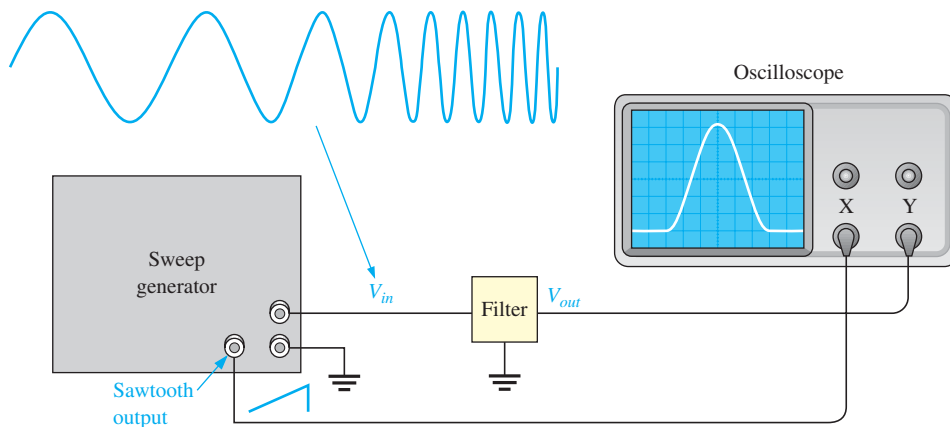(a) Test setup for a filter response using a spectrum analyzer



(b) Test setup for a filter response using an oscilloscope. The scope is put in X-Y mode. The sawtooth waveform from the sweep generator drives the X-channel of the oscilloscope.

FIGURE 9-27 Test setup for swept frequency measurement of the filter response.


the spectrum analyzer is an instrument that can be calibrated for a desired *frequency span/division* rather than for the usual *time/division* setting. Therefore, as the input frequency to the filter sweeps through a preselected range, the response curve is traced out on the screen of the spectrum analyzer. The test setup for using an oscilloscope to display the response curve is shown in part (b).

SYSTEM EXAMPLE 9-3

FILTER BOARD FOR AN FM STEREO RECEIVER

The radio signal that an FM stereo receiver must process is called a multiplex signal. In this example the emphasis is the filter board, which is part of the channel separation circuit of an FM stereo receiver.

It was in the late 1950s that stereo FM broadcasting was first introduced. At that time there were still many monaural receivers in use, so the stereo broadcast had to be compatible with mono receivers. For this reason the left and right channels of the stereo FM signal are encoded as sum ($L + R$) and difference ($L - R$) signals. The mono receivers would simply use the $L + R$ signal to hear both channels through a single speaker. A stereo receiver must do a little more work to recover the original two channels. The left channel is recovered by

 

adding the sum signal to the difference signal ($2L$), and the right channel is recovered by subtracting the difference signal from the sum signal ($2R$). A full description of how a multiplex signal is produced and demodulated is quite complex.

A Brief Description of the System

Stereo FM (frequency modulation) signals are transmitted on carrier frequencies of 88 MHz to 108 MHz. The standard transmitted stereo signal consists of three modulating signals. These are the sum of the left and right channel audio ($L + R$), the difference of the left and right channel audio ($L - R$), and a 19 kHz pilot subcarrier. The $L + R$ audio extends from 30 Hz to 15 kHz and the $L - R$ signal is contained in two sidebands centered on 38 kHz extending from 23 kHz to 53 kHz as indicated in Figure SE9-5. These frequencies come from the FM detector and are processed by the filter circuits where they are separated.

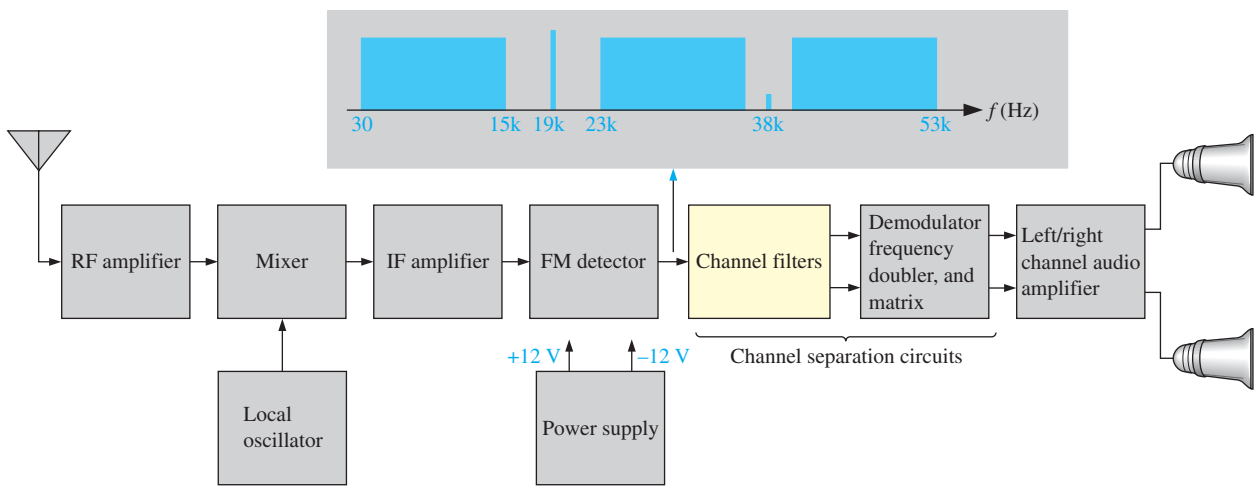


FIGURE SE9-7 FM stereo receiver block diagram.

The demodulator uses the frequency-doubled 19 kHz subcarrier to extract the audio signal from the 23 kHz to 53 kHz sidebands, after which the 30 Hz to 15 kHz $L - R$ baseband signal is passed through a filter. The $L + R$ and $L - R$ audio signals are then sent to the matrix where they are applied to the summing circuits to produce the left and right channel audio ($-2L$ and $-2R$). As stated earlier, our focus in this system example is on the filters.

Refer to the schematic of the left and right channel separation circuit shown in Figure SE9-6. There are four filter circuits in this schematic, two low-pass filters and two band-pass filters. IC1 is a low-pass filter that removes everything but the $L + R$ signal from 30 Hz to 15 kHz. This signal is sent to the two inverting summing amplifiers IC6 and IC8. The IC6 summing amplifier adds the $L + R$ signal to the $L - R$ signal and the output is equal to $-2L$.

The band-pass filter comprised of IC2 and IC4 (cascaded two-pole low-pass and high-pass filters, respectively) reject everything but the $L - R$ signal sidebands. The multiple feedback band-pass filter (IC3) passes only the 19 kHz pilot subcarrier, which is doubled in frequency and used by the demodulator to extract the $L - R$ baseband signal from the two sidebands. The low-pass filter (IC5) removes any harmonics from the $L - R$ baseband signal and its output is sent to the sum and difference amplifiers. The inverting amplifier IC7 converts the summing amplifier IC8 into a difference amplifier or subtractor. IC7 inverts the $L - R$ signal so the output from the inverting summing amplifier IC8 is equal to $-2R$. These three circuits (IC6, IC7, and IC8) comprise the matrix.

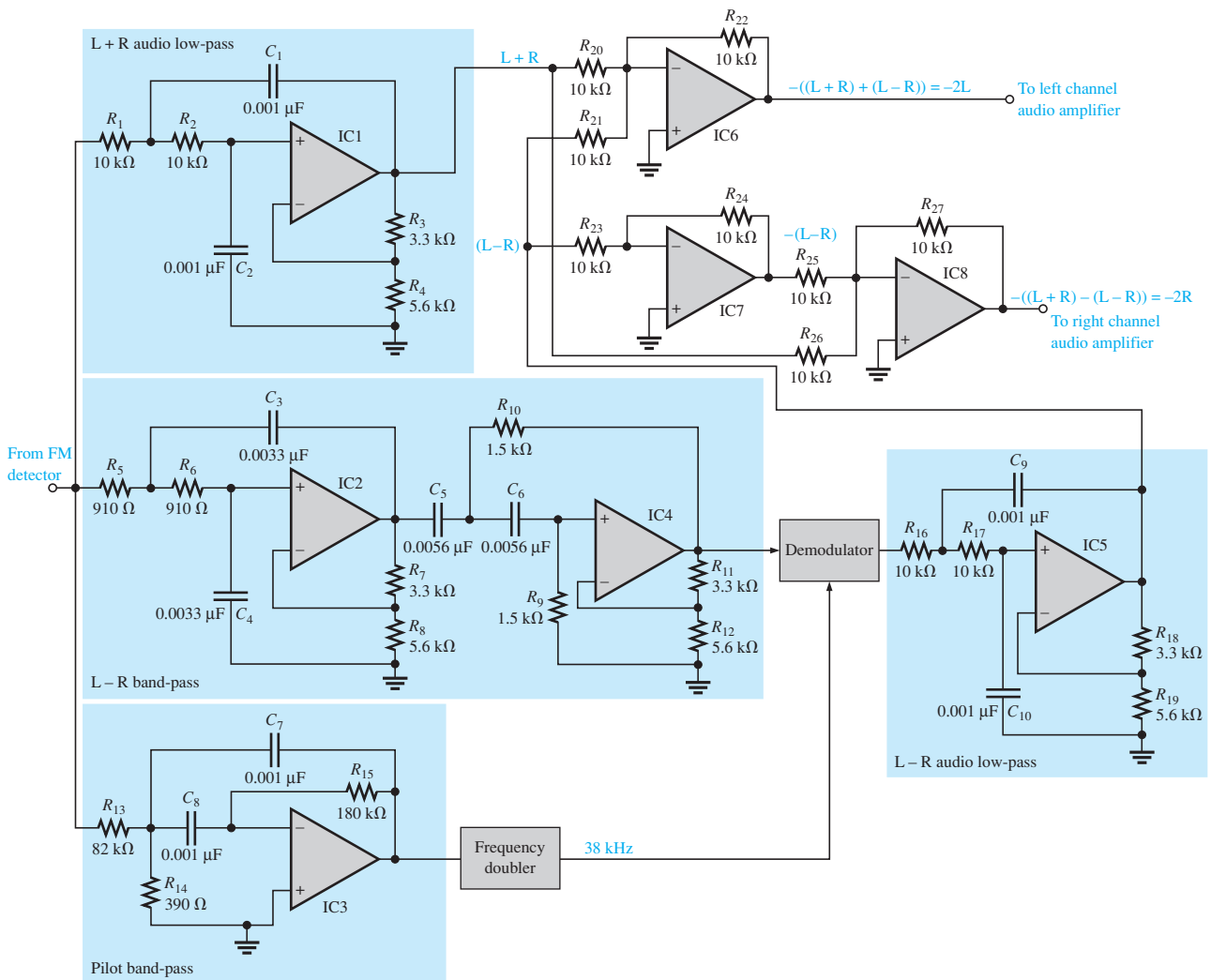


FIGURE SE9-8 Left and right channel separation circuits.

SECTION 9-7 CHECKUP

1. What is the purpose of the two tests discussed in this section?
2. Name one disadvantage and one advantage of each test method.

SUMMARY

- The bandwidth in a low-pass filter equals the critical frequency because the response extends to 0 Hz.
- The bandwidth in a high-pass filter extends above the critical frequency and is limited only by the inherent frequency limitation of the active circuit.
- A band-pass filter passes all frequencies within a band between a lower and an upper critical frequency and rejects all others outside this band.
- The bandwidth of a band-pass filter is the difference between the upper critical frequency and the lower critical frequency.
- A band-stop filter rejects all frequencies within a specified band and passes all those outside this band.

- Filters with the Butterworth response characteristic have a very flat response in the passband, exhibit a roll-off of -20 dB/decade/pole, and are used when all the frequencies in the passband must have the same gain.
- Filters with the Chebyshev characteristic have ripples or overshoot in the passband and exhibit a faster roll-off per pole than filters with the Butterworth characteristic.
- Filters with the Bessel characteristic are used for filtering pulse waveforms. Their linear phase characteristic results in minimal waveshape distortion. The roll-off rate per pole is slower than for the Butterworth.
- In filter terminology, a single RC network is called a *pole*.
- Each pole in a Butterworth filter causes the output to roll off at a rate of -20 dB/decade.
- The quality factor Q of a band-pass filter determines the filter's selectivity. The higher the Q , the narrower the bandwidth and the better the selectivity.
- The damping factor determines the filter response characteristic (Butterworth, Chebyshev, or Bessel).

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Band-pass filter A type of filter that passes a range of frequencies lying between a certain lower frequency and a certain higher frequency.

Band-stop filter A type of filter that blocks or rejects a range of frequencies lying between a certain lower frequency and a certain higher frequency.

Critical frequency (f_c) The frequency that defines the end of the passband of a filter; also called *cutoff frequency*.

Damping factor (DF) A filter characteristic that determines the type of response.

Filter A circuit that passes certain frequencies and attenuates or rejects all other frequencies.

High-pass filter A type of filter that passes frequencies above a certain frequency while rejecting lower frequencies.

Low-pass filter A type of filter that passes frequencies below a certain frequency while rejecting higher frequencies.

Order The number of poles in a filter.

Pole A network containing one resistor and one capacitor that contributes -20 dB/decade to a filter's roll-off rate.

Roll-off The rate of decrease in gain below or above the critical frequencies of a filter.


KEY FORMULAS

- | | | |
|-------|---|---|
| (9-1) | $BW = f_c$ | Low-pass bandwidth |
| (9-2) | $BW = f_{c2} - f_{c1}$ | Filter bandwidth of a band-pass filter |
| (9-3) | $f_0 = \sqrt{f_{c1}f_{c2}}$ | Center frequency of a band-pass filter |
| (9-4) | $Q = \frac{f_0}{BW}$ | Quality factor of a band-pass filter |
| (9-5) | $DF = 2 - \frac{R_1}{R_2}$ | Damping factor |
| (9-6) | $f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$ | Critical frequency for a second-order Sallen-Key filter |
| (9-7) | $f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3}}$ | Center frequency of a multiple-feedback filter |
| (9-8) | $A_0 = \frac{R_2}{2R_1}$ | Gain of a multiple-feedback filter |

SELF-TEST

Answers are at the end of the chapter.

 1. The term *pole* in filter terminology refers to
 - (a) a high-gain op-amp
 - (b) one complete active filter
 - (c) a single *RC* network
 - (d) the feedback circuit
2. A single resistor and a single capacitor can be connected to form a filter with a roll-off rate of
 - (a) -20 dB/decade
 - (b) -40 dB/decade
 - (c) -6 dB/octave
 - (d) answers (a) and (c)
3. A band-pass response has
 - (a) two critical frequencies
 - (b) one critical frequency
 - (c) a flat curve in the passband
 - (d) a wide bandwidth
4. The lowest frequency passed by a low-pass filter is
 - (a) 1 Hz
 - (b) 0 Hz
 - (c) 10 Hz
 - (d) dependent on the critical frequency
5. The *Q* of a band-pass filter depends on
 - (a) the critical frequencies
 - (b) only the bandwidth
 - (c) the center frequency and the bandwidth
 - (d) only the center frequency
6. The damping factor of an active filter determines the
 - (a) voltage gain
 - (b) critical frequency
 - (c) response characteristic
 - (d) roll-off rate
7. A maximally flat frequency response is known as
 - (a) Chebyshev
 - (b) Butterworth
 - (c) Bessel
 - (d) Colpitts
8. The damping factor of a filter is set by the
 - (a) negative feedback circuit
 - (b) positive feedback circuit
 - (c) frequency-selective circuit
 - (d) gain of the op-amp
9. The number of poles in a filter affect the
 - (a) voltage gain
 - (b) bandwidth
 - (c) center frequency
 - (d) roll-off rate
10. Sallen-Key filters are
 - (a) single-pole filters
 - (b) second-order filters
 - (c) Butterworth filters
 - (d) band-pass filters
11. When filters are cascaded, the roll-off rate
 - (a) increases
 - (b) decreases
 - (c) does not change
12. When a low-pass and a high-pass filter are cascaded to get a band-pass filter, the critical frequency of the low-pass filter must be
 - (a) equal to the critical frequency of the high-pass filter
 - (b) less than the critical frequency of the high-pass filter
 - (c) greater than the critical frequency of the high-pass filter
13. A state-variable filter consists of
 - (a) one op-amp with multiple-feedback paths
 - (b) a summing amplifier and two integrators
 - (c) a summing amplifier and two differentiators
 - (d) three Butterworth stages
14. When the gain of a filter is minimum at its center frequency, it is
 - (a) a band-pass filter
 - (b) a band-stop filter
 - (c) a notch filter
 - (d) answers (b) and (c)



TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 9–29(a).

- If C_1 is mistakenly replaced with a $0.15\ \mu\text{F}$ capacitor instead of $0.015\ \mu\text{F}$,
 1. The bandwidth will
 - (a) increase (b) decrease (c) not change
 2. The number of poles will
 - (a) increase (b) decrease (c) not change
 3. The roll-off rate will
 - (a) increase (b) decrease (c) not change

Refer to Figure 9–29(b).

- If C_2 is open,
 4. The ac output for a given ac input will
 - (a) increase (b) decrease (c) not change
- If R_4 is $10\ \text{k}\Omega$ instead of $1.0\ \text{k}\Omega$,
 5. The damping factor will
 - (a) increase (b) decrease (c) not change
 6. The critical frequency will
 - (a) increase (b) decrease (c) not change

Refer to Figure 9–29(c).

- If C_3 is open,
 7. The number of poles will
 - (a) increase (b) decrease (c) not change

Refer to Figure 9–33(b).

- If R_3 has an incorrect value of $1.0\ \text{k}\Omega$,
 8. The passband gain will
 - (a) increase (b) decrease (c) not change
- If R_2 is less than the specified value of $150\ \text{k}\Omega$,
 9. The center frequency will
 - (a) increase (b) decrease (c) not change
 10. The passband gain will
 - (a) increase (b) decrease (c) not change
 11. The bandwidth will
 - (a) increase (b) decrease (c) not change

Refer to Figure 9–33(c).

- If R_5 is larger than the specified value of $560\ \text{k}\Omega$,
 12. The bandwidth will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 9–1 Basic Filter Responses

1. Identify each type of filter response (low-pass, high-pass, band-pass, or band-stop) in Figure 9–28.
2. A certain low-pass filter has a critical frequency of $800\ \text{Hz}$. What is its bandwidth?

 


FIGURE 9-28

 


FIGURE 9-29

3. A single-pole high-pass filter has a frequency-selective network with $R = 2.2 \text{ k}\Omega$ and $C = 0.0015 \text{ }\mu\text{F}$. What is the critical frequency? Can you determine the bandwidth from the available information?
4. What is the roll-off rate of the filter described in Problem 3?
5. What is the bandwidth of a band-pass filter whose critical frequencies are 3.2 kHz and 3.9 kHz? What is the Q of this filter?
6. What is the center frequency of a filter with a Q of 15 and a bandwidth of 1.0 kHz?

SECTION 9-2 Filter Response Characteristics

7. What is the damping factor in each active filter shown in Figure 9-29? Which filters are approximately optimized for a Butterworth response characteristic?
8. For the filters in Figure 9-29 that do not have a Butterworth response, specify the changes necessary to convert them to Butterworth responses. (Use nearest standard values.)
9. Response curves for second-order filters are shown in Figure 9-30. Identify each as Butterworth, Chebyshev, or Bessel.

 


FIGURE 9-30

SECTION 9-3 Active Low-Pass Filters

10. Is the four-pole filter in Figure 9-31 approximately optimized for a Butterworth response? What is the roll-off rate?
11. Determine the critical frequency in Figure 9-31.
12. Without changing the response curve, adjust the component values in the filter of Figure 9-31 to make it an equal-value filter.
13. Modify the filter in Figure 9-31 to increase the roll-off rate to -120 dB/decade while maintaining an approximate Butterworth response.
14. Using a block diagram format, show how to implement the following roll-off rates using single-pole and two-pole low-pass filters with Butterworth responses.
 - (a) -40 dB/decade
 - (b) -20 dB/decade
 - (c) -60 dB/decade
 - (d) -100 dB/decade
 - (e) -120 dB/decade

 


FIGURE 9-31

SECTION 9-4 Active High-Pass Filters

- 15. Convert the equal-value filter from Problem 12 to a high-pass with the same critical frequency and response characteristic.
- 16. Make the necessary circuit modification to reduce by half the critical frequency in Problem 15.
- 17. For the filter in Figure 9-32,
 - (a) How would you increase the critical frequency?
 - (b) How would you increase the gain?

 


FIGURE 9-32

SECTION 9-5 Active Band-Pass Filters

- 18. Identify each band-pass filter configuration in Figure 9-33.
- 19. Determine the center frequency and bandwidth for each filter in Figure 9-33.
- 20. Optimize the state-variable filter in Figure 9-34 for $Q = 50$. What bandwidth is achieved?

 


FIGURE 9-33

SECTION 9-6 Active Band-Stop Filters

21. Show how to make a notch (band-stop) filter using the basic circuit in Figure 9-34.
22. Modify the band-stop filter in Problem 21 for a center frequency of 120 Hz.

 


FIGURE 9-34

MULTISIM

**MULTISIM TROUBLESHOOTING PROBLEMS**

23. Open file P09-23 and determine the fault.
24. Open file P09-24 and determine the fault.
25. Open file P09-25 and determine the fault.
26. Open file P09-26 and determine the fault.
27. Open file P09-27 and determine the fault.
28. Open file P09-28 and determine the fault.
29. Open file P09-29 and determine the fault.
30. Open file P09-30 and determine the fault.

ANSWERS TO SECTION CHECKUPS**SECTION 9-1**

1. The critical frequency determines the bandwidth.
2. The inherent frequency limitation of the op-amp limits the bandwidth.
3. Q and BW are inversely related. The higher the Q , the better the selectivity, and vice versa.
4. An all-pass filter passes all frequencies but has a phase shift associated with certain frequencies.

SECTION 9-2

1. Butterworth is very flat in the passband and has a -20 dB/decade/pole roll-off. Chebyshev has ripples in the passband and has greater than -20 dB/decade/pole roll-off. Bessel has a linear phase characteristic and less than -20 dB/decade/pole roll-off.
2. The damping factor determines the response characteristic.
3. Frequency-selection network, gain element, and negative feedback network are the parts of an active filter.

SECTION 9-3

1. A second-order filter has two poles. Two resistors and two capacitors make up the frequency-selective network.
2. The damping factor sets the response characteristic.
3. Cascading increases the roll-off rate.

SECTION 9-4

1. The positions of the R s and C s in the frequency-selection network are opposite for low-pass and high-pass configurations.
2. Decrease the R values to increase f_c .
3. -140 dB/decade

SECTION 9-5

1. Q determines selectivity.
2. $Q = 25$. Higher Q gives narrower BW .
3. A summing amplifier and two integrators make up a state-variable filter.
4. 1.38

SECTION 9-6

1. A band-stop rejects frequencies within the stopband. A band-pass passes frequencies within the passband.
2. The low-pass and high-pass outputs are summed.

SECTION 9-7

1. To check the frequency response of a filter
2. Discrete point measurement—tedious and less complete; simpler equipment.
Swept frequency measurement—uses more expensive equipment; more efficient; can be more accurate and complete.
3. Change the clock frequency.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

9-1 500 Hz

9-2 1.44

9-3 7.23 kHz, 1.29 k Ω 9-4 $C_{A1} = C_{A2} = C_{B1} = C_{B2} = 0.234 \mu\text{F}$; $R_2 = R_4 = 680 \Omega$, $R_1 = 103 \Omega$, $R_3 = 840 \Omega$ 9-5 $R_A = R_B = R_2 = 10 \text{ k}\Omega$, $C_A = C_B = 0.053 \mu\text{F}$, $R_1 = 5.86 \text{ k}\Omega$

9-6 Gain increases to 2.43, frequency decreases to 544 Hz, and bandwidth decreases to 96.5 Hz.

9-7 $f_0 = 21.9 \text{ kHz}$, $Q = 101$, $BW = 217 \text{ Hz}$

9-8 Decrease the input resistors or the feedback capacitors of the two integrator stages by half.

ANSWERS TO SELF-TEST

1. (c)
2. (d)
3. (a)
4. (b)
5. (c)
6. (c)
7. (b)
8. (a)
9. (d)
10. (b)
11. (a)
12. (c)
13. (b)
14. (d)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. decrease
2. not change
3. not change
4. decrease
5. increase
6. not change
7. decrease
8. not change
9. increase
10. decrease
11. increase
12. decrease

CHAPTER 10

OSCILLATORS AND TIMERS

OUTLINE

- 10-1 The Oscillator
- 10-2 Feedback Oscillator Principles
- 10-3 Sinusoidal Oscillators with *RC* Feedback Circuits
- 10-4 Oscillators with *LC* Feedback Circuits
- 10-5 Relaxation Oscillator Principles
- 10-6 The 555 Timer as an Oscillator
- 10-7 The 555 Timer as a One-Shot

OBJECTIVES

- Describe the basic operating principles for all oscillators
- Explain the operation of feedback oscillators
- Describe and analyze the operation of basic *RC* sinusoidal feedback oscillators
- Describe and analyze the operation of *LC* sinusoidal feedback oscillators.
- Describe and analyze the operation of basic relaxation oscillators
- Use a 555 timer in an oscillation application
- Use a 555 timer as a one-shot device

KEY TERMS

Feedback oscillator	Colpitts oscillator
Relaxation oscillator	Clapp oscillator
Positive feedback	Hartley oscillator
Wien-bridge oscillator	Armstrong oscillator
Phase-shift oscillator	Piezoelectric effect

Voltage-controlled oscillator (VCO)

Astable multivibrator One-shot

INTRODUCTION

Oscillators are circuits that generate a periodic waveform to perform timing, control, or communication functions. They are found in nearly all electronic systems, including analog and digital systems, and in most test instruments such as oscilloscopes and function generators.

Oscillators require a form of positive feedback, where a portion of the output signal is fed back to the input in a way that causes it to reinforce itself and thus sustain a continuous output signal. Although an external input is not strictly necessary, many oscillators use an external signal to control the frequency or to synchronize it with another source. Oscillators are designed to produce a controlled oscillation with one of two basic methods: the unity-gain method used with feedback oscillators and the timing method used with relaxation oscillators. Both will be discussed in this chapter.

Different types of oscillators produce various types of outputs including sine waves, square waves, triangular waves, and sawtooth waves. In this chapter, several types of basic oscillator circuits using both op-amps and discrete transistors as the gain element are introduced. Also, a very popular integrated circuit, called the 555 timer, is discussed.

VISIT THE WEBSITE

Study aids for this chapter are available at <http://pearsonhighered.com/floyd>

10-1 THE OSCILLATOR

An oscillator is a circuit that produces a periodic waveform on its output with only the dc supply voltage as a required input. A repetitive input signal is not required but is sometimes used to synchronize oscillations. The output voltage can be either sinusoidal or nonsinusoidal, depending on the type of oscillator. Two major classifications for oscillators are feedback oscillators and relaxation oscillators.

After completing this section, you should be able to

- Describe the basic operating principles for all oscillators
- Explain the purpose of an oscillator
- Discuss two important classifications for oscillators
- List the basic elements of a feedback oscillator

Types of Oscillators

Essentially, all **oscillators** convert electrical energy from the dc power supply to periodic waveforms that can be used for various timing, control, or signal-generating applications. A basic oscillator is illustrated in Figure 10-1. Oscillators are classified according to the technique for generating a signal.

 


FIGURE 10-1 The basic oscillator concept showing three common types of output waveforms.

FEEDBACK OSCILLATORS One type of oscillator is the **feedback oscillator** which returns a fraction of the output signal to the input with no net phase shift, resulting in a reinforcement of the output signal. After oscillations are started, the loop gain is maintained at 1.0 to maintain oscillations. A feedback oscillator consists of an amplifier for gain (either a discrete transistor or an op-amp) and a positive feedback network that produces phase shift and provides attenuation, as shown in Figure 10-2.

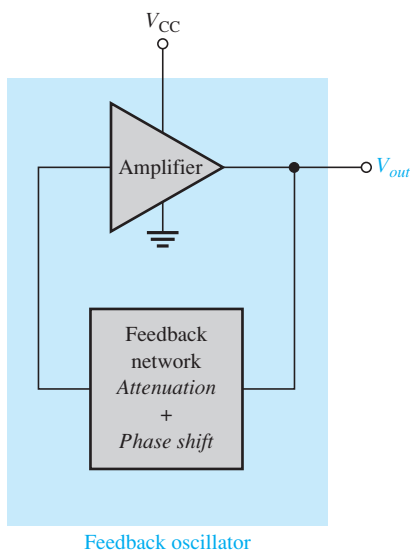


FIGURE 10-2 Basic elements of a feedback oscillator.

RELAXATION OSCILLATORS A second type of oscillator is the **relaxation oscillator**. A relaxation oscillator uses an RC timing circuit to generate a waveform that is generally a square wave or other nonsinusoidal waveform. Typically, a relaxation oscillator uses a Schmitt trigger or other device that changes states to alternately charge and discharge a capacitor through a resistor. Relaxation oscillators are discussed in Section 10–5.

SECTION 10–1 CHECKUP*

1. What is an oscillator?
2. What type of feedback does a feedback oscillator require?
3. What is the purpose of the feedback network?

*Answers are at the end of the chapter.

10–2 FEEDBACK OSCILLATOR PRINCIPLES

Feedback oscillator operation is based on the principle of positive feedback. In this section, we will examine this concept and look at the general conditions required for oscillation to occur. Feedback oscillators are widely used to generate sinusoidal waveforms.

After completing this section, you should be able to

- Explain the operation of feedback oscillators
- Explain positive feedback
- Describe the conditions for oscillation
- Discuss the start-up conditions

Positive Feedback

Positive feedback is characterized by the condition where an in-phase portion of the output voltage of an amplifier is fed back to the input. This basic idea is illustrated with the sinusoidal oscillator shown in Figure 10–3. As you can see, the in-phase feedback voltage is amplified to produce the output voltage, which in turn produces the feedback voltage. That is, a loop is created in which the signal sustains itself and a continuous sinusoidal output is produced. This phenomenon is called *oscillation*.

 


FIGURE 10–3 Positive feedback produces oscillation.

Conditions for Oscillation

Two conditions, illustrated in Figure 10-4, are required to sustain oscillations:

1. The phase shift around the feedback loop must be effectively 0° .
2. The voltage gain, A_{cl} , around the closed feedback loop (loop gain) must equal 1 (unity).

 


FIGURE 10-4 Conditions for oscillation.

The voltage gain around the closed feedback loop, A_{cl} , is the product of the amplifier gain, A_v , and the attenuation, B , of the feedback circuit.

$$A_{cl} = A_v B$$

If a sinusoidal wave is the desired output, a loop gain greater than 1 will rapidly cause the output to saturate at both peaks of the waveform, producing unacceptable distortion. To avoid this, some form of gain control must be used to keep the loop gain at exactly 1, once oscillations have started. For example, if the attenuation of the feedback network is 0.01, the amplifier must have a gain of exactly 100 to overcome this attenuation and not create unacceptable distortion ($0.01 \times 100 = 1.0$). An amplifier gain of greater than 100 will cause the oscillator to limit both peaks of the waveform.

Start-Up Conditions

So far, you have seen what it takes for an oscillator to produce a continuous sinusoidal output. Now let's examine the requirements for the oscillation to start when the dc supply voltage is turned on. As you know, the unity-gain condition must be met for oscillation to be sustained. For oscillation to *begin*, the voltage gain around the positive feedback loop must be greater than 1 so that the amplitude of the output can build up to a desired level. The gain must then decrease to 1 so that the output stays at the desired level and oscillation is sustained. (Several ways to achieve this reduction in gain after start-up are discussed in the next section.) The voltage-gain conditions for both starting and sustaining oscillation are illustrated in Figure 10-5.

A question that normally arises is this: If the oscillator is initially off and there is no output voltage, how does a feedback signal originate to start the positive feedback build-up process? Initially, a small positive feedback voltage develops from thermally produced broad-band noise in the resistors or other components or from power supply turn-on transients. The feedback circuit permits only a voltage with a frequency equal to the selected oscillation frequency to appear in phase on the amplifier's input. This initial feedback voltage is amplified and continually reinforced, resulting in a buildup of the output voltage as previously discussed.

 


FIGURE 10-5 When oscillation starts at t_0 , the condition $A_{cl} > 1$ causes the sinusoidal output voltage amplitude to build up to a desired level. Then A_{cl} decreases to 1 and maintains the desired amplitude.

SECTION 10-2 CHECKUP

1. What are the conditions required for a circuit to oscillate?
2. Define positive feedback.
3. What is the voltage gain condition for oscillator start-up?

10-3 SINUSOIDAL OSCILLATORS WITH RC FEEDBACK CIRCUITS

In this section, you will learn about three types of feedback oscillators that use *RC* circuits to produce sinusoidal outputs: the Wien-bridge oscillator, the phase-shift oscillator, and the twin-T oscillator. Generally, *RC* feedback oscillators are used for frequencies up to about 1 MHz. The Wien-bridge is by far the most widely used type of *RC* oscillator for this range of frequencies.

After completing this section, you should be able to

- Describe and analyze the operation of basic *RC* sinusoidal feedback oscillators
 - Identify a Wien-bridge oscillator
 - Determine the resonant frequency of a Wien-bridge oscillator
 - Analyze oscillator feedback conditions
 - Analyze oscillator start-up conditions
 - Describe a self-starting Wien-bridge oscillator
 - Identify a phase-shift oscillator
 - Calculate the resonant frequency and analyze the feedback conditions for a phase-shift oscillator
 - Identify a twin-T oscillator and describe its operation

The Wien-Bridge Oscillator

One type of sinusoidal *RC* feedback oscillator is the **Wien-bridge oscillator**. A fundamental part of the Wien-bridge oscillator is a lead-lag network like that shown in Figure 10-6(a). R_1 and C_1 together form the lag portion of the network; R_2 and C_2 form the lead portion. The

 


FIGURE 10-6 A lead-lag network and its response curve.

operation of this lead-lag network is as follows. At lower frequencies, the lead network dominates due to the high reactance of C_2 . As the frequency increases, X_{C2} decreases, thus allowing the output voltage to increase. At some specified frequency, the response of the lag network takes over, and the decreasing value of X_{C1} causes the output voltage to decrease.

The response curve for the lead-lag network shown in Figure 10-6(b) indicates that the output voltage peaks at a frequency called the resonant frequency, f_r . At this point, the attenuation (V_{out}/V_{in}) of the network is $1/3$ if $R_1 = R_2$ and $X_{C1} = X_{C2}$ as stated by the following equation, which is derived in Appendix A:

$$\frac{V_{out}}{V_{in}} = \frac{1}{3} \tag{10-1}$$

The formula for the resonant frequency is also derived in Appendix A and is

$$f_r = \frac{1}{2\pi RC} \tag{10-2}$$

To summarize, the lead-lag network in the Wien-bridge oscillator has a resonant frequency, f_r , at which the phase shift through the network is 0° and the attenuation is $1/3$. Below f_r , the lead network dominates and the output leads the input. Above f_r , the lag network dominates and the output lags the input.

THE BASIC CIRCUIT The lead-lag network is used in the positive feedback loop of an op-amp, as shown in Figure 10-7(a). A voltage divider is used in the negative feedback loop. The Wien-bridge oscillator circuit can be viewed as a noninverting amplifier

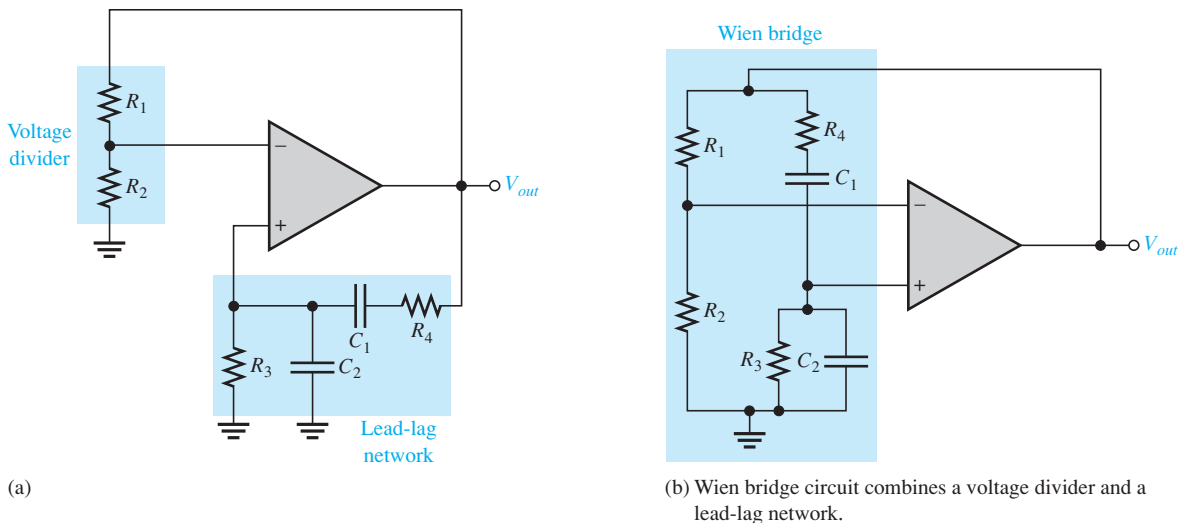


FIGURE 10-7 Two ways to draw the schematic of a Wien-bridge oscillator.

configuration with the input signal fed back from the output through the lead-lag network. Recall that the closed-loop gain of the amplifier is determined by the voltage divider.

$$A_{cl} = \frac{1}{B} = \frac{1}{R_2/(R_1 + R_2)} = \frac{R_1 + R_2}{R_2}$$

The circuit is redrawn in Figure 10–7(b) to show that the op-amp is connected across the bridge circuit. One leg of the bridge is the lead-lag network, and the other is the voltage divider.

POSITIVE FEEDBACK CONDITIONS FOR OSCILLATION As you know, for the circuit to produce a sustained sinusoidal output (oscillate), the phase shift around the positive feedback loop must be 0° and the gain around the loop must equal unity (1). The 0° phase-shift condition is met when the frequency is f_r because the phase shift through the lead-lag network is 0° and there is no inversion from the noninverting (+) input of the op-amp to the output. This is shown in Figure 10–8(a).

 


FIGURE 10–8 Conditions for oscillation.

The unity-gain condition in the feedback loop is met when

$$A_{cl} = 3$$

This offsets the $\frac{1}{3}$ attenuation of the lead-lag network, thus making the total gain around the positive feedback loop equal to 1, as depicted in Figure 10–8(b). To achieve a closed-loop gain of 3,


$$R_1 = 2R_2$$

Then


$$A_{cl} = \frac{R_1 + R_2}{R_2} = \frac{2R_2 + R_2}{R_2} = \frac{3R_2}{R_2} = 3$$

START-UP CONDITIONS Initially, the closed-loop gain of the amplifier itself must be more than 3 ($A_{cl} > 3$) until the output signal builds up to a desired level. Ideally, the gain of the amplifier must then decrease to 3 so that the total gain around the loop is 1 and the output signal stays at the desired level, thus sustaining oscillation. This is illustrated in Figure 10–9.

 
The circuit in Figure 10–10 illustrates a method for achieving sustained oscillations. Notice that the voltage-divider network has been modified to include an additional resistor R_3 in parallel with a back-to-back zener diode arrangement. When dc power is first applied,



 (a) Loop gain greater than 1 causes output to build up.



(b) Loop gain of 1 causes a sustained constant output.

 FIGURE 10-9 Oscillator start-up conditions.**FIGURE 10-10** Self-starting Wien-bridge oscillator using back-to-back zener diodes.

both zener diodes appear as opens. This places R_3 in series with R_1 , thus increasing the closed-loop gain of the amplifier as follows ($R_1 = 2R_2$):

$$A_{cl} = \frac{R_1 + R_2 + R_3}{R_2} = \frac{3R_2 + R_3}{R_2} = 3 + \frac{R_3}{R_2}$$

Initially, a small positive feedback signal develops from noise or turn-on transients. The lead-lag network permits only a signal with a frequency equal to f_r to appear in phase on the noninverting input. This feedback signal is amplified and continually reinforced, resulting in a buildup of the output voltage. When the output signal reaches the zener breakdown voltage, the zeners conduct and effectively short out R_3 . This lowers the amplifier's closed-loop gain to 3. At this point the total loop gain is 1 and the output signal levels off and the oscillation is sustained. All practical methods to achieve stability for feedback oscillators require the gain to be self-adjusting. This requirement is a form of automatic gain control (AGC). The zener diodes in this example limit the gain at the onset of a nonlinearity, in this case, zener conduction.

Although the zener feedback network is simple, it suffers from the fact that nonlinearity must occur to control gain; hence, it is difficult to achieve a clean sinusoidal waveform. Another method to control the gain uses a JFET as a voltage-controlled resistor in a negative feedback path. This method can produce an excellent sinusoidal waveform that is stable. Recall from Section 4-2 that a JFET operating with a small or zero V_{DS} is operating in the ohmic region. As the gate voltage increases, the drain-source resistance increases. If the JFET is placed in the negative feedback path, automatic gain control can be achieved because of this voltage-controlled resistance.

A JFET stabilized Wien-bridge oscillator is shown in Figure 10-11. The gain of the op-amp is controlled by the components shown in the shaded box, which include the JFET.

The JFET's drain-source resistance depends on the gate voltage. With no output signal, the gate is at zero volts, causing the drain-source resistance to be at the minimum. With this condition, the loop gain is greater than 1. Oscillations begin and rapidly build to a large output signal. Negative excursions of the output signal forward-bias D_1 , causing capacitor C_3 to charge to a negative voltage. This voltage increases the drain-source resistance of the JFET and reduces the gain (and hence the output). This is classic negative feedback at work. With the proper selection of components, the gain can be stabilized at the required level. You can explore this circuit further in Experiment 27 of the laboratory manual that accompanies this text. The following example illustrates a JFET stabilized oscillator.

 


FIGURE 10-11 Self-starting Wien-bridge oscillator using a JFET in the negative feedback loop.

EXAMPLE 10-1

Determine the frequency for the Wien-bridge oscillator in Figure 10-12. Also, calculate the setting for R_f assuming the internal drain-source resistance, r'_{ds} , of the JFET is $500\ \Omega$ when oscillations are stable.

 


FIGURE 10-12

SOLUTION

For the lead-lag network, $R_1 = R_2 = R = 10\ \text{k}\Omega$ and $C_1 = C_2 = C = 0.01\ \mu\text{F}$. The frequency is

$$f_r = \frac{1}{2\pi RC} = \frac{1}{2\pi(10\ \text{k}\Omega)(0.01\ \mu\text{F})} = \mathbf{1.59\ \text{kHz}}$$

The closed-loop gain must be 3.0 for oscillations to be sustained. For an inverting amplifier, the gain is that of a noninverting amplifier.

$$A_v = \frac{R_f}{R_i} + 1$$

R_i is composed of R_3 (the source resistor) and r'_{ds} . Substituting,

$$A_v = \frac{R_f}{R_3 + r'_{ds}} + 1$$

Rearranging and solving for R_f ,

$$R_f = (A_v - 1)(R_3 + r'_{ds}) = (3 - 1)(1.0 \text{ k}\Omega + 500 \Omega) = \mathbf{3.0 \text{ k}\Omega}$$

PRACTICE EXERCISE*

What happens to the oscillations if the setting of R_f is too high? What happens if the setting is too low?

*Answers are at the end of the chapter.

MULTISIM



Open file F10-12 found on the companion website. This simulation demonstrates the value of the feedback resistor affects the operation of a Wien-bridge.

SYSTEM EXAMPLE 10-1

TONE GENERATOR

High quality audio oscillators are often used in systems requiring a precise frequency standard. The system in this example is used by a musical instrument manufacturer to check the frequency of middle C, which is 261.625 Hz. The system is portable and uses two 9-V batteries. The overall system consists of a Wien-bridge oscillator, a voltage amplifier, a power amplifier, and a speaker. To avoid noise, distortion, and drift, the Wien-bridge and voltage amplifier are constructed with precision components and located in a separate enclosure. Figure SE10-1 shows the block diagram of the system. The focus of this example is the Wien-bridge oscillator and the voltage amplifier.

 
 


FIGURE SE10-1 Basic block diagram of an audio oscillator system.

The Wien-bridge oscillator and voltage amplifier circuit is shown in Figure SE10-2. It uses the AD822 op-amp, which is a dual-precision, low-power and low-noise FET input op-amp. The first half of the op-amp is used for the Wien-bridge oscillator; the second half is for the voltage amplifier. The AD822 has very low offset drift over its specified temperature range (maximum input bias current drift of 10 pA for B Grade). It uses very low power, making it an excellent choice for a battery powered circuit. Notice that the rheostats trim the frequency and are ganged. Assuming the rheostats are both set to 184 Ω of resistance, the frequency of the Wien-bridge is

$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi(59 \text{ k}\Omega + 184 \Omega)(0.1 \mu\text{F})} = 261.6 \text{ Hz}$$

The output of the bridge is isolated by the voltage amplifier, which helps prevent any loading effects on the bridge circuit. In a low-level application, the voltage amplifier could directly be connected to the speaker. In this system a power amplifier is used to increase the signal strength.

MULTISIM



Open file SE10-2 found on the companion website. This simulation allows you to fine tune the frequency of the Wien-bridge.

 


FIGURE SE10-2 Wien-bridge oscillator circuit and amplifier.

The Phase-Shift Oscillator

A type of sinusoidal feedback oscillator called the **phase-shift oscillator** is shown in Figure 10-13. Each of the three RC networks in the feedback loop can provide a maximum phase shift approaching 90°. Oscillation occurs at the frequency where the total phase shift through the three RC networks is 180°. The inversion of the op-amp itself provides the additional 180° to meet the requirement for oscillation of a 360° (or 0°) phase shift around the feedback loop.

 


FIGURE 10-13 Op-amp phase-shift oscillator.

The attenuation B of the three-section RC feedback network is


$$B = \frac{1}{29} \tag{10-3}$$

where $B = R_3/R_f$. The derivation of this unusual result is given in Appendix A. To meet the greater-than-unity loop gain requirement, the closed-loop voltage gain of the op-amp must be greater than 29 (set by R_f and R_3). The frequency of oscillation is also derived in Appendix A and stated in the following equation, where $R_1 = R_2 = R_3 = R$ and $C_1 = C_2 = C_3 = C$.

$$f_r = \frac{1}{2\pi\sqrt{6}RC} \tag{10-4}$$

EXAMPLE 10-2

- (a) Determine the value of R_f necessary for the circuit in Figure 10-14 to operate as an oscillator.
- (b) Determine the frequency of oscillation.

 
FIGURE 10-14
SOLUTION

- (a) $A_{cl} = 29$, and $B = \frac{1}{29} = \frac{R_3}{R_f}$. Therefore,

$$\frac{R_f}{R_3} = 29$$

$$R_f = 29R_3 = 29(10 \text{ k}\Omega) = \mathbf{290 \text{ k}\Omega}$$

- (b) $R_1 = R_2 = R_3 = R$ and $C_1 = C_2 = C_3 = C$. Therefore,

$$f_r = \frac{1}{2\pi\sqrt{6}RC} = \frac{1}{2\pi\sqrt{6}(10 \text{ k}\Omega)(0.001 \mu\text{F})} \cong \mathbf{6.5 \text{ kHz}}$$


PRACTICE EXERCISE

- (a) If R_1 , R_2 , and R_3 in Figure 10-14 are changed to $8.2 \text{ k}\Omega$, what value must R_f be for oscillation?
- (b) What is the value of f_r ?

MULTISIM


Open file F10-14 found on the companion website. This simulation demonstrates the instability of the phase shift oscillator.

In Chapter 9 you were introduced to the state-variable filter. These filters can be configured to act as state-variable oscillators by introducing positive feedback from the output of the third stage to the input of the first. If you refer back to Figure 9-20 you will see that the state-variable filter is comprised of an inverting amplifier and two integrators. The inverting amplifier introduces 180° of phase shift and each integrator adds 90° . This provides the 360° (0°) of phase shift required for positive feedback. State-variable oscillators are preferred in many types of systems because they have a more reliable start-up than single-stage RC oscillators. They also have low settling time and are reasonably immune to stray capacitance.

 SYSTEM NOTE


Twin-T Oscillator

Another type of RC feedback oscillator is called the *twin-T* because of the two T-type RC filters used in the feedback loop, as shown in Figure 10-15(a). One of the twin-T filters has a low-pass response, and the other has a high-pass response. The combined parallel filters

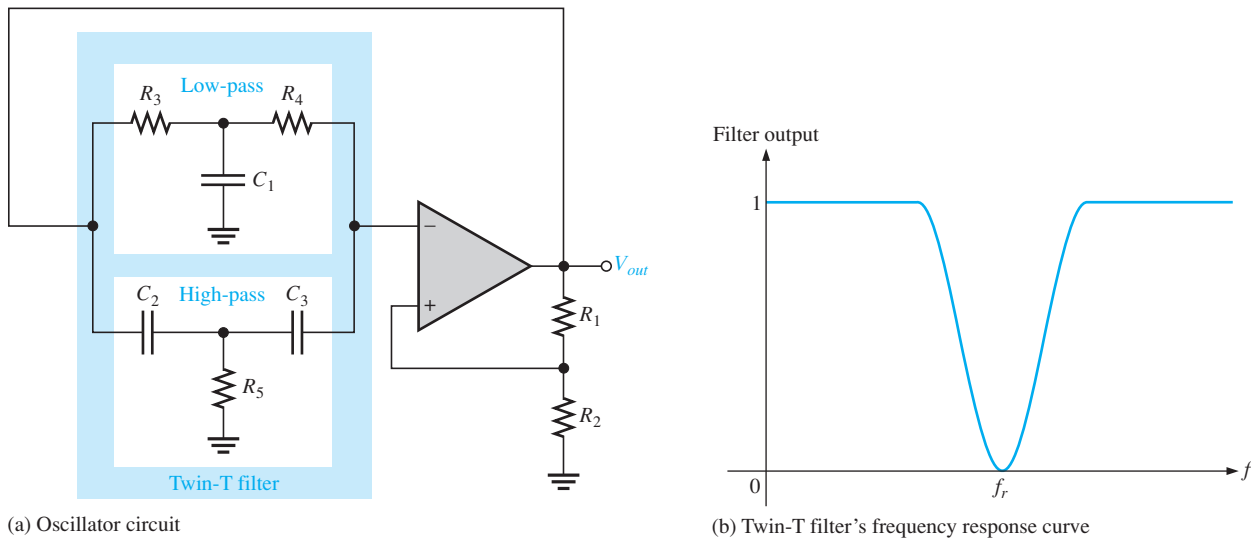


FIGURE 10-15 Twin-T oscillator and twin-T filter response.


produce a band-stop or notch response with a center frequency equal to the desired frequency of oscillation, f_r , as shown in Figure 10-15(b).

Oscillation cannot occur at frequencies above or below f_r because of the negative feedback through the filters. At f_r , however, there is negligible negative feedback; thus, the positive feedback through the voltage divider (R_1 and R_2) allows the circuit to oscillate.

In the previous System Note an oscillator using a state-variable filter was discussed. These circuits are often used in systems that use sensors to convert capacitive or resistive sensor outputs into a sinusoidal voltage. A comparator is added as a fourth stage to convert the sinusoidal output from the state-variable oscillator into digital pulses, which are able to be analyzed by a computer. The Texas Instruments UAF42 universal active filter IC is one choice because it includes a fourth op-amp that can be configured as a comparator. The spec sheet for the UAF42 can be found at www.ti.com. Here is how this system would work.

Suppose you want to monitor the fluid level in an oil tank. The fluid level sensors are actually capacitors that are formed as hollow tubes so that the oil can form some or all of the dielectric of the capacitor, depending on how much air is displaced within the tubes as the fluid level rises and falls. As the fluid level changes, the capacitance of the sensors changes because the dielectric has changed. These capacitive sensors are used in the feedback circuits of the two integrators in the state-variable oscillator. The output frequency of the oscillator changes because of the change in capacitance.

 A microcontroller then compares the output frequency from the comparator to a high-frequency clock signal. It counts the number of clock pulses in the time window determined by the period of the pulses from the comparator. Using a look-up table, the computer can convert the output from a capacitive sensor to a fluid level for display.



SYSTEM NOTE

SECTION 10-3 CHECKUP

- There are two feedback loops in the Wien-bridge oscillator. What is the purpose of each?
- A certain lead-lag network has $R_1 = R_2$ and $C_1 = C_2$. An input voltage of 5 V rms is applied. The input frequency equals the resonant frequency of the network. What is the rms output voltage?
- Why is the phase shift through the RC feedback network in a phase-shift oscillator equal to 180° ?
- What is the gain of the voltage amplifier in Figure SE10-2?

10–4 OSCILLATORS WITH *LC* FEEDBACK CIRCUITS

Although the *RC* feedback oscillators, particularly the Wien bridge, are generally suitable for frequencies up to about 1 MHz, *LC* feedback elements are normally used in oscillators that require higher frequencies of oscillation. Also, because of the frequency limitation (lower unity-gain frequency) of most op-amps, discrete transistors (BJT or FET) are often used as the gain element in *LC* oscillators. This section introduces several types of resonant *LC* feedback oscillators: the Colpitts, Clapp, Hartley, Armstrong, and crystal-controlled oscillators.


After completing this section, you should be able to

- Describe and analyze the operation of *LC* feedback oscillators
 - Identify and analyze a Colpitts oscillator
 - Identify and analyze a Clapp oscillator
 - Identify and analyze a Hartley oscillator
 - Identify and analyze an Armstrong oscillator
 - Describe the operation of crystal-controlled oscillators

The Colpitts Oscillator

One basic type of resonant circuit feedback oscillator is the Colpitts, named after its inventor—as are most of the others we cover here. As shown in Figure 10–16, this type of oscillator uses an *LC* circuit in the feedback loop to provide the necessary phase shift and to act as a resonant filter that passes only the desired frequency of oscillation.

FIGURE 10–16 A basic Colpitts oscillator with a BJT as the gain element.

 

The approximate frequency of oscillation is the resonant frequency of the *LC* circuit and is established by the values of C_1 , C_2 , and L according to this familiar formula:

$$f_r \cong \frac{1}{2\pi\sqrt{LC_T}} \quad (10-5)$$

where C_T is the total capacitance. Because the capacitors effectively appear in series around the tank circuit, the total capacitance (C_T) is

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

CONDITIONS FOR OSCILLATION AND START-UP The attenuation, B , of the resonant feedback circuit in the **Colpitts oscillator** is basically determined by the values of C_1 and C_2 .

Figure 10–17 shows that the tank voltage is divided between C_1 and C_2 (they are effectively in series). The voltage developed across C_2 is the oscillator's output voltage (V_{out}) and the voltage developed across C_1 is the feedback voltage (V_f), as indicated. The expression for the attenuation (B) is

$$B = \frac{V_f}{V_{out}} \cong \frac{IX_{C1}}{IX_{C2}} = \frac{X_{C1}}{X_{C2}} = \frac{1/(2\pi f_r C_1)}{1/(2\pi f_r C_2)}$$

Cancelling the $2\pi f_r$ terms gives

$$B = \frac{C_2}{C_1}$$


As you know, a condition for oscillation is $A_v B = 1$. Since $B = C_2/C_1$,

$$A_v = \frac{C_1}{C_2} \quad (10-6)$$

where A_v is the voltage gain of the amplifier, which is represented by the triangle in Figure 10–17. With this condition met, $A_v B = (C_1/C_2)(C_2/C_1) = 1$. Actually, for the oscillator to be self-starting, $A_v B$ must be greater than 1 (that is, $A_v B > 1$). Therefore, the voltage gain must be made slightly greater than C_1/C_2 .

$$A_v > \frac{C_1}{C_2}$$

FIGURE 10–17 The attenuation of the tank circuit is the output of the tank (V_f) divided by the input to the tank (V_{out}). $B = V_f/V_{out} = C_2/C_1$. For $A_v B > 1$, A_v must be greater than C_1/C_2 .

 

LOADING OF THE FEEDBACK CIRCUIT AFFECTS THE FREQUENCY OF OSCILLATION

As indicated in Figure 10–18, the input impedance of the amplifier acts as a load on the resonant feedback circuit and reduces the Q of the circuit. The resonant frequency of a parallel resonant circuit depends on the Q , according to the following formula:

$$f_r = \frac{1}{2\pi\sqrt{LC_T}} \sqrt{\frac{Q^2}{Q^2 + 1}} \quad (10-7)$$

As a rule of thumb, for a Q greater than 10, the frequency is approximately $1/(2\pi\sqrt{LC_T})$, as stated in Equation 10–5. When Q is less than 10, however, f_r is reduced significantly.

 


FIGURE 10-18 Z_{in} of the amplifier loads the feedback circuit and lowers its Q , thus lowering the resonant frequency.

A FET can be used in place of a BJT, as shown in Figure 10-19, to minimize the loading effect of the transistor’s input impedance. Recall that FETs have much higher input impedances than do bipolar junction transistors. Also, when an external load is connected to the oscillator output, as shown in Figure 10-20(a), f_r may decrease, again because of a reduction in Q . This happens if the load resistance is too small. In some cases, one way to eliminate the effects of a load resistance is by transformer coupling, as indicated in Figure 10-20(b). It is also very common to use an RF choke in place of a collector or drain resistor in high-frequency Colpitts oscillators.



 


FIGURE 10-19 A basic FET Colpitts oscillator.

 

 (a) A load capacitively coupled to oscillator output can reduce circuit Q and f_r .




(b) Transformer coupling of load can reduce loading effect by impedance transformation.

FIGURE 10-20 Oscillator loading.

EXAMPLE 10-3

- (a) Determine the frequency for the oscillator in Figure 10-21. Assume there is negligible loading on the feedback circuit and that its Q is greater than 10.
- (b) Find the frequency if the oscillator is loaded to a point where the Q drops to 8.

FIGURE 10-21

 

SOLUTION

$$(a) C_T = \frac{C_1 C_2}{C_1 + C_2} = \frac{(0.1 \mu\text{F})(0.01 \mu\text{F})}{0.11 \mu\text{F}} = 0.0091 \mu\text{F}$$

$$f_r \cong \frac{1}{2\pi\sqrt{LC_T}} = \frac{1}{2\pi\sqrt{(50 \text{ mH})(0.0091 \mu\text{F})}} = 7.46 \text{ kHz}$$

$$(b) f_r = \frac{1}{2\pi\sqrt{LC_T}} \sqrt{\frac{Q^2}{Q^2 + 1}} = (7.46 \text{ kHz})(0.9923) = 7.40 \text{ kHz}$$

PRACTICE EXERCISE

What frequency does the oscillator in Figure 10-21 produce if it is loaded to a point where $Q = 4$?

MULTISIM



Open file F10-21 found on the companion website. This simulation demonstrates the operation of a Colpitts oscillator with an RF choke in the collector circuit.

The Clapp Oscillator

The **Clapp oscillator** is a variation of the Colpitts. The basic difference is an additional capacitor, C_3 , in series with the inductor in the resonant feedback circuit, as shown in Figure 10-22. Since C_3 is in series with C_1 and C_2 around the tank circuit, the total capacitance is

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

and the approximate frequency of oscillation ($Q > 10$) is

$$f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

 


FIGURE 10-22 A basic Clapp oscillator.

If C_3 is much smaller than C_1 and C_2 , then C_3 almost entirely controls the resonant frequency ($f_r \cong 1/(2\pi\sqrt{LC_3})$). Since C_1 and C_2 are both connected to ground at one end, the junction capacitance of the transistor and other stray capacitances appear in parallel with C_1 and C_2 to ground, altering their effective values. C_3 is not affected, however, and thus provides a more accurate and stable frequency of oscillation.

The Hartley Oscillator

The **Hartley oscillator** is similar to the Colpitts except that the feedback circuit consists of two series inductors and a parallel capacitor as shown in Figure 10-23.

 


FIGURE 10-23 A basic Hartley oscillator.

MULTISIM



Open file F10-23 found on the companion website. This simulation demonstrates the operation of a Hartley oscillator with an RF choke in the collector circuit.

In this circuit, the frequency of oscillation for $Q > 10$ is

$$f_r \cong \frac{1}{2\pi\sqrt{L_T C}}$$

where $L_T = L_1 + L_2$. The inductors act in a role similar to C_1 and C_2 in the Colpitts to determine the attenuation, B , of the feedback circuit.

$$B \cong \frac{L_1}{L_2}$$

To assure start-up of oscillation, A_v must be greater than $1/B$.

$$A_v \cong \frac{L_2}{L_1} \quad (10-8)$$

Loading of the tank circuit has the same effect in the Hartley as in the Colpitts; that is, the Q is decreased and thus f_r decreases.

The Armstrong Oscillator

This type of LC feedback oscillator uses transformer coupling to feed back a portion of the signal voltage, as shown in Figure 10–24. It is sometimes called a “tickler” oscillator in reference to the transformer secondary or “tickler coil” that provides the feedback to keep the oscillation going. The Armstrong is less common than the Colpitts, Clapp, and Hartley, mainly because of the disadvantage of transformer size and cost. The frequency of oscillation is set by the inductance of the primary winding (L_{pri}) in parallel with C_1 .

$$f_r = \frac{1}{2\pi\sqrt{L_{pri}C_1}} \quad (10-9)$$

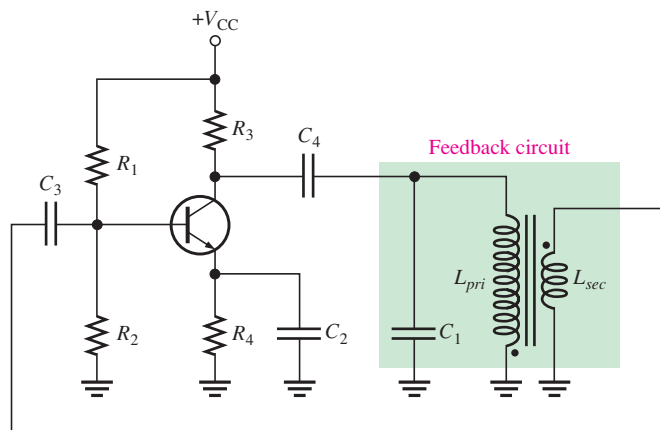


FIGURE 10–24 A basic Armstrong oscillator.

Crystal-Controlled Oscillators

The most stable and accurate type of feedback oscillator uses a piezoelectric **crystal** in the feedback loop to control the frequency.

THE PIEZOELECTRIC EFFECT Quartz is one type of crystalline substance found in nature that exhibits a property called the **piezoelectric effect**. When a changing mechanical stress is applied across the crystal to cause it to vibrate, a voltage develops at the frequency of mechanical vibration. Conversely, when an ac voltage is applied across the crystal, it vibrates at the frequency of the applied voltage. The greatest vibration occurs at the crystal’s natural resonant frequency, which is determined by the physical dimensions and by the way the crystal is cut.

Crystals used in electronic applications typically consist of a quartz wafer mounted between two electrodes and enclosed in a protective “can” as shown in Figure 10–25(a)

 


FIGURE 10-25 A quartz crystal.

and (b). A schematic symbol for a crystal is shown in Figure 10-25(c), and an equivalent *RLC* circuit for the crystal appears in Figure 10-25(d). As you can see, the crystal’s equivalent circuit is a series-parallel *RLC* circuit and can operate in either series resonance or parallel resonance. At the series resonant frequency, the inductive reactance is cancelled by the reactance of C_s . The remaining series resistor, R_s , determines the impedance of the crystal. Parallel resonance occurs when the inductive reactance and the reactance of the parallel capacitance, C_p , are equal. The parallel resonant frequency is usually at least 1 kHz higher than the series resonant frequency. A great advantage of the crystal is that it exhibits a very high *Q* (*Q*s with values of several thousand are typical).

An oscillator that uses a crystal as a series resonant tank circuit is shown in Figure 10-26(a). The impedance of the crystal is minimum at the series resonant frequency, thus providing maximum feedback. The crystal tuning capacitor, C_C , is used to “fine tune” the oscillator frequency by “pulling” the resonant frequency of the crystal slightly up or down.

A modified Colpitts configuration is shown in Figure 10-26(b) with a crystal acting as a parallel resonant tank circuit. The impedance of the crystal is maximum at parallel resonance, thus developing the maximum voltage across the capacitors. The voltage across C_1 is fed back to the input.

 


FIGURE 10-26 Basic crystal oscillators.

MODES OF OSCILLATION IN THE CRYSTAL Piezoelectric crystals can oscillate in either of two modes—fundamental or overtone. The fundamental frequency of

a crystal is the lowest frequency at which it is naturally resonant. The fundamental frequency depends on the crystal's mechanical dimensions, type of cut, and other factors, and is inversely proportional to the thickness of the crystal slab. Because a slab of crystal cannot be cut too thin without fracturing, there is an upper limit on the fundamental frequency. For most crystals, this upper limit is less than 20 MHz. For higher frequencies, the crystal must be operated in the overtone mode. Overtones are approximate integer multiples of the fundamental frequency. The overtone frequencies are usually, but not always, odd multiples (3, 5, 7, . . .) of the fundamental. Many crystal oscillators are available in integrated circuit packages.

SECTION 10-4 CHECKUP

1. What is the basic difference between the Colpitts and the Hartley oscillators?
2. What is the advantage of a FET amplifier in a Colpitts or Hartley oscillator?
3. How can you distinguish a Colpitts oscillator from a Clapp oscillator?

10-5 RELAXATION OSCILLATOR PRINCIPLES

The second major category of oscillators is the relaxation oscillator. Relaxation oscillators use an RC timing circuit and a device that changes states to generate a periodic waveform. In this section, you will learn about several circuits that are used to produce nonsinusoidal waveforms.

After completing this section, you should be able to

- Describe and analyze the operation of basic relaxation oscillators
- Discuss the operation of basic triangular-wave oscillators
- Discuss the operation of a voltage-controlled oscillator (VCO)
- Discuss the operation of a square-wave relaxation oscillator

A Triangular-Wave Oscillator

The op-amp integrator covered in Chapter 8 can be used as the basis for a triangular-wave generator. The basic idea is illustrated in Figure 10-27(a) where a dual-polarity, switched input is used. We use the switch only to introduce the concept; it is not a practical way to implement this circuit. When the switch is in position 1, the negative voltage is applied,

 


FIGURE 10-27 Basic triangular-wave generator.

and the output is a positive-going ramp. When the switch is thrown into position 2, a negative-going ramp is produced. If the switch is thrown back and forth at fixed intervals, the output is a triangular wave consisting of alternating positive-going and negative-going ramps, as shown in Figure 10-27(b).

A PRACTICAL TRIANGULAR-WAVE OSCILLATOR One practical implementation of a triangular-wave generator utilizes an op-amp comparator to perform the switching function, as shown in Figure 10-28. The operation is as follows. To begin, assume that the output voltage of the comparator is at its maximum negative level. This output is connected to the inverting input of the integrator through R_1 , producing a positive-going ramp on the output of the integrator. When the ramp voltage reaches the upper trigger point (UTP), the comparator switches to its maximum positive level. This positive level causes the integrator ramp to change to a negative-going direction. The ramp continues in this direction until the lower trigger point (LTP) of the comparator is reached. At this point, the comparator output switches back to the maximum negative level and the cycle repeats. This action is illustrated in Figure 10-29.

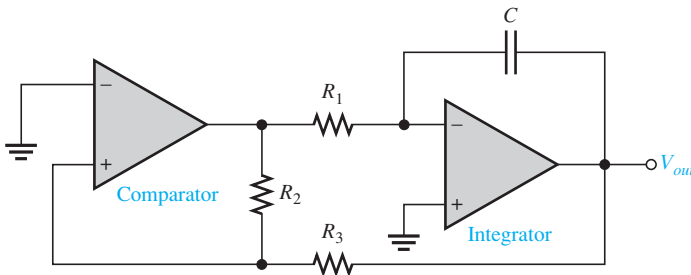


FIGURE 10-28 A triangular-wave generator using two op-amps.

 


FIGURE 10-29 Waveforms for the circuit in Figure 10-28.

Since the comparator produces a square-wave output, the circuit in Figure 10-28 can be used as both a triangular-wave generator and a square-wave generator. Devices of this type are commonly known as *function generators* because they produce more than one output function. The output amplitude of the square wave is set by the output swing of the comparator, and resistors R_2 and R_3 set the amplitude of the triangular output by establishing the UTP and LTP voltages according to the following formulas:

$$V_{\text{UTP}} = +V_{\text{max}} \left(\frac{R_3}{R_2} \right)$$

$$V_{\text{LTP}} = -V_{\text{max}} \left(\frac{R_3}{R_2} \right)$$

where the comparator output levels, $+V_{\text{max}}$ and $-V_{\text{max}}$, are equal. The frequency of both waveforms depends on the R_1C time constant as well as the amplitude-setting resistors, R_2

and R_3 . By varying R_1 , the frequency of oscillation can be adjusted without changing the output amplitude.

$$f = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right) \quad (10-10)$$

EXAMPLE 10-4

Determine the frequency of the circuit in Figure 10-30. To what value must R_1 be changed to make the frequency 20 kHz?

 


FIGURE 10-30

SOLUTION

$$f = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right) = \left(\frac{1}{4(10 \text{ k}\Omega)(0.01 \text{ }\mu\text{F})} \right) \left(\frac{33 \text{ k}\Omega}{10 \text{ k}\Omega} \right) = 8.25 \text{ kHz}$$

To make $f = 20 \text{ kHz}$,

$$R_1 = \frac{1}{4fC} \left(\frac{R_2}{R_3} \right) = \left(\frac{1}{4(20 \text{ kHz})(0.01 \text{ }\mu\text{F})} \right) \left(\frac{33 \text{ k}\Omega}{10 \text{ k}\Omega} \right) = 4.13 \text{ k}\Omega$$

PRACTICE EXERCISE

What is the amplitude of the triangular wave in Figure 10-30 if the comparator output is $\pm 10 \text{ V}$?

A Voltage-Controlled Sawtooth Oscillator (VCO)

The **voltage-controlled oscillator (VCO)** is a relaxation oscillator whose frequency can be changed by a variable dc control voltage. VCOs can be either sinusoidal or nonsinusoidal. One way to build a voltage-controlled sawtooth oscillator is with an op-amp integrator that uses a switching device (PUT) in parallel with the feedback capacitor to terminate each ramp at a prescribed level and effectively “reset” the circuit. Figure 10-31(a) shows the implementation.

The PUT is a programmable unijunction transistor with an anode, a cathode, and a gate terminal. The gate is always biased positively with respect to the cathode. When the anode voltage exceeds the gate voltage by approximately 0.7 V, the PUT turns on and acts as a forward-biased diode. When the anode voltage falls below this level, the PUT turns off. Also, the current must be above the holding value to maintain conduction.

The operation of the sawtooth generator begins when the negative dc input voltage, $-V_{IN}$, produces a positive-going ramp on the output. During the time that the ramp is increasing, the circuit acts as a regular integrator. The PUT triggers on when the output ramp (at the anode) exceeds the gate voltage by 0.7 V. The gate is set to the approximate

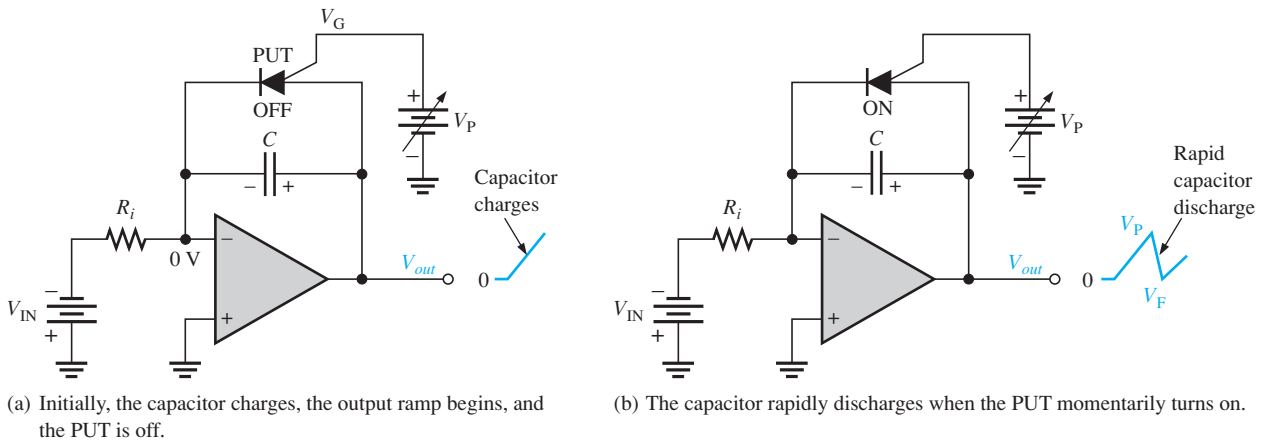


FIGURE 10-31 Voltage-controlled sawtooth oscillator operation.

desired sawtooth peak voltage. When the PUT turns on, the capacitor rapidly discharges, as shown in Figure 10-31(b). The capacitor does not discharge completely to zero because of the PUT's forward voltage, V_F . Discharge continues until the PUT current falls below the holding value. At this point, the PUT turns off and the capacitor begins to charge again, thus generating a new output ramp. The cycle continually repeats, and the resulting output is a repetitive sawtooth waveform, as shown. The sawtooth amplitude and period can be adjusted by varying the PUT gate voltage.

The frequency is determined by the R_iC time constant of the integrator and the peak voltage set by the PUT. Recall that the charging rate of the capacitor is V_{IN}/R_iC . The time it takes the capacitor to charge from V_F to V_P is the period, T , of the sawtooth (neglecting the rapid discharge time).

$$T = \frac{V_P - V_F}{|V_{IN}|/R_iC}$$

From $f = 1/T$,

$$f = \frac{|V_{IN}|}{R_iC} \left(\frac{1}{V_P - V_F} \right) \tag{10-11}$$

EXAMPLE 10-5

- (a) Find the peak-to-peak amplitude and frequency of the sawtooth output in Figure 10-32. Assume that the forward PUT voltage, V_F , is approximately 1 V.
- (b) Sketch the output waveform.

 


FIGURE 10-32

SOLUTION

- (a) First, find the gate voltage in order to establish the approximate voltage at which the PUT turns on.

$$V_G = \frac{R_4}{R_3 + R_4} (+V) = \frac{10 \text{ k}\Omega}{20 \text{ k}\Omega} (+15 \text{ V}) = 7.5 \text{ V}$$

This voltage sets the approximate maximum peak value of the sawtooth output (neglecting the 0.7 V).

$$V_P \cong 7.5 \text{ V}$$

The minimum peak value (low point) is

$$V_F \cong 1 \text{ V}$$

So the peak-to-peak amplitude is

$$V_{pp} = V_P - V_F = 7.5 \text{ V} - 1 \text{ V} = \mathbf{6.5 \text{ V}}$$

The frequency is determined as follows:

$$V_{IN} = \frac{R_2}{R_1 + R_2} (-V) = \frac{10 \text{ k}\Omega}{78 \text{ k}\Omega} (-15 \text{ V}) = -1.92 \text{ V}$$

$$f = \frac{|V_{IN}|}{R_i C} \left(\frac{1}{V_P - V_F} \right) = \left(\frac{1.92 \text{ V}}{(100 \text{ k}\Omega)(0.005 \mu\text{F})} \right) \left(\frac{1}{7.5 \text{ V} - 1 \text{ V}} \right) \cong \mathbf{591 \text{ Hz}}$$

- (b) The output waveform is shown in Figure 10–33. The period is

$$T = \frac{1}{f} = \frac{1}{591 \text{ Hz}} = 1.69 \text{ ms}$$

 


FIGURE 10–33 Output of the circuit in Figure 10–32.

PRACTICE EXERCISE

If R_i is changed to 56 k Ω in Figure 10–32, what is the frequency?

A Square-Wave Oscillator

The basic square-wave oscillator shown in Figure 10–34 is a type of relaxation oscillator because its operation is based on the charging and discharging of a capacitor. Notice that the op-amp's inverting (–) input is the capacitor voltage and the noninverting (+) input is a portion of the output fed back through resistors R_2 and R_3 . When the circuit is first turned on, the capacitor is uncharged, and thus the inverting input is at 0 V. This makes the output a positive maximum, and the capacitor begins to charge toward V_{out} through R_1 . When the capacitor voltage (V_C) reaches a value equal to the feedback voltage (V_f) on the noninverting input, the op-amp switches to the maximum negative state. At this point, the capacitor begins to discharge from $+V_f$ toward $-V_f$. When the capacitor voltage reaches $-V_f$, the op-amp switches back to the maximum positive state. This action continues to repeat, as shown in Figure 10–35, and a square-wave output voltage is obtained.

 


FIGURE 10-34 A square-wave relaxation oscillator.

 


FIGURE 10-35 Waveforms for the square-wave relaxation oscillator.

Very high-frequency systems including cellular phone systems and radar frequently use specialized bandpass filters to provide the feedback filtering necessary for stable oscillation. One type of filter used in microwave oscillators is the surface acoustic wave (SAW) filter. The resonant frequency is determined, to some degree, by its physical dimensions rather than its electrical properties.

SAW oscillators were first introduced in 1969, though the concept of a surface acoustic wave was first theorized in 1885. A SAW filter contains two electrode transducers (input and output) of interlaced fingers deposited on a piezoelectric substrate. The construction of a SAW filter is illustrated in Figure SN10-1.

The spacing between the fingers on one side is approximately equal to the wavelength of the filter center frequency as illustrated in Figure SN10-1. An RF signal applied to the input transducer sets up an acoustic wave traveling along the surface of the device at a frequency determined by the finger spacing. This surface acoustic wave is coupled into the fingers of the output transducer and converted back into electrical energy through the piezoelectric effect. The number of fingers, their length and shape, and the relative number of fingers between the input and output electrodes determines the response characteristics of the filter. SAW filters are limited to frequencies below about 10 GHz, though new construction technologies are pushing this boundary.


 


FIGURE SN10-1 A SAW filter.

SYSTEM NOTE

 

SECTION 10-5 CHECKUP

1. What is a VCO, and basically what does it do?
2. Upon what principle does a relaxation oscillator operate?
3. What is a SAW filter?

10–6 THE 555 TIMER AS AN OSCILLATOR

The 555 timer is a versatile integrated circuit with many applications. In this section, you will see how the 555 is configured as an astable or free-running multivibrator, which is essentially a square-wave oscillator. The use of the 555 timer as a voltage-controlled oscillator (VCO) is also discussed. The data sheet for the LM555 can be found at www.national.com.

After completing this section, you should be able to

- Use a 555 timer in an oscillator application
- Discuss astable operation of the 555 timer
- Explain how to use the 555 timer as a VCO

Astable Operation

A 555 timer connected to operate as an **astable multivibrator**, which is a free-running nonsinusoidal oscillator that produces a pulse waveform on its output, is shown in Figure 10–36. Notice that the threshold input (THRESH) is now connected to the trigger input (TRIG). The external components R_1 , R_2 , and C_{ext} form the timing network that sets the frequency of oscillation. The $0.01\ \mu\text{F}$ capacitor connected to the control input (CONT) is strictly for decoupling and has no effect on the operation.

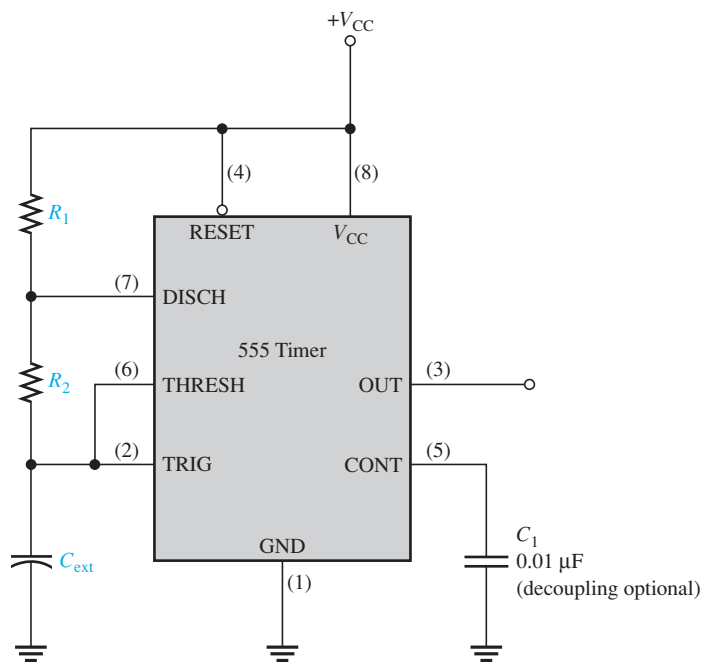


FIGURE 10–36 The 555 timer connected as an astable multivibrator.

The frequency of oscillation is given by Equation (10–12), or it can be found using the graph in Figure 10–37.

$$f = \frac{1.44}{(R_1 + 2R_2)C_{\text{ext}}} \quad (10-12)$$

By selecting R_1 and R_2 , the duty cycle of the output can be adjusted. Since C_{ext} charges through $R_1 + R_2$ and discharges only through R_2 , duty cycles approaching a minimum of 50 percent can be achieved if $R_2 \gg R_1$ so that the charging and discharging times are approximately equal.

 


FIGURE 10-37 Frequency of oscillation (free-running frequency) of a 555 timer in the astable mode as a function of C_{ext} and $R_1 + 2R_2$. The sloped lines are values of $R_1 + 2R_2$.

A formula to calculate the duty cycle is developed as follows. The time that the output is high (t_H) is expressed as

$$t_H = 0.693(R_1 + R_2)C_{ext}$$

The time that the output is low (t_L) is expressed as

$$t_L = 0.693R_2C_{ext}$$

The period, T , of the output waveform is the sum of t_H and t_L .

$$T = t_H + t_L = 0.693(R_1 + 2R_2)C_{ext}$$

This is the reciprocal of f in Equation (10-12). Finally, the percent duty cycle is

$$\text{Duty cycle} = \left(\frac{t_H}{T}\right)100\% = \left(\frac{t_H}{t_H + t_L}\right)100\%$$

$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2}\right)100\% \tag{10-13}$$

To achieve duty cycles of less than 50 percent, the circuit in Figure 10-36 can be modified so that C_{ext} charges through only R_1 and discharges through R_2 . This is achieved with a diode, D_1 , placed as shown in Figure 10-38. The duty cycle can be made less than

 


FIGURE 10-38 The addition of diode D_1 allows the duty cycle of the output to be adjusted to less than 50 percent by making $R_1 < R_2$.

50 percent by making R_1 less than R_2 . Under this condition, the formula for the percent duty cycle is

$$\text{Duty cycle} = \left(\frac{R_1}{R_1 + R_2} \right) 100\% \quad (10-14)$$

EXAMPLE 10-6

A 555 timer configured to run in the astable mode (oscillator) is shown in Figure 10-39. Determine the frequency of the output and the duty cycle.

 


FIGURE 10-39

SOLUTION

$$f = \frac{1.44}{(R_1 + 2R_2)C_{\text{ext}}} = \frac{1.44}{(2.2 \text{ k}\Omega + 9.4 \text{ k}\Omega)0.022 \text{ }\mu\text{F}} = 5.64 \text{ kHz}$$

$$\text{Duty cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% = \left(\frac{2.2 \text{ k}\Omega + 4.7 \text{ k}\Omega}{2.2 \text{ k}\Omega + 9.4 \text{ k}\Omega} \right) 100\% = 59.5\%$$

PRACTICE EXERCISE

Determine the duty cycle in Figure 10-39 if a diode is connected across R_2 as indicated in Figure 10-38.

Operation as a Voltage-Controlled Oscillator (VCO)

A 555 timer can be set up to operate as a VCO by using the same external connections as for astable operation, with the exception that a variable control voltage is applied to the CONT input (pin 5), as indicated in Figure 10-40.

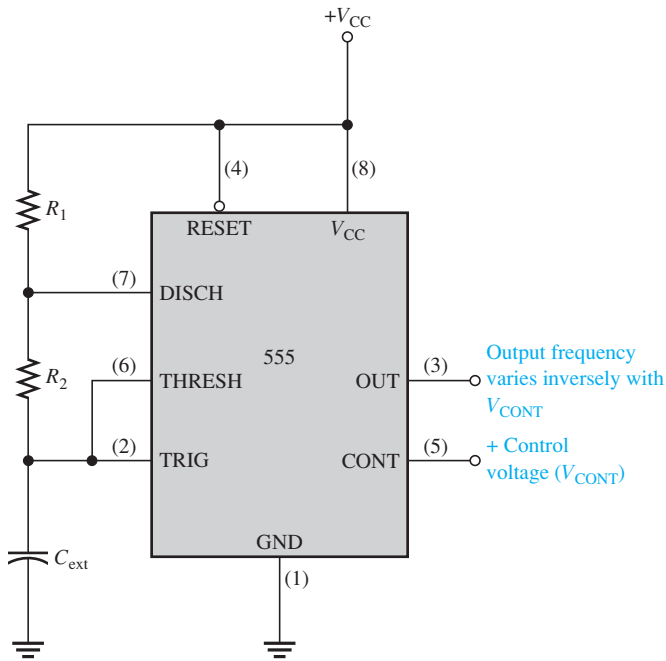


FIGURE 10-40 The 555 timer connected as a voltage-controlled oscillator (VCO). Note the variable control voltage input on pin 5.

For the capacitor voltage, as shown in Figure 10-41, the upper value is V_{CONT} and the lower value is $\frac{1}{2} V_{\text{CONT}}$. When the control voltage is varied, the output frequency also varies. An increase in V_{CONT} increases the charging and discharging time of the external capacitor and causes the frequency to decrease. A decrease in V_{CONT} decreases the charging and discharging time of the capacitor and causes the frequency to increase.

 



FIGURE 10-41 The VCO output frequency varies inversely with V_{CONT} because the charging and discharging time of C_{ext} is directly dependent on the control voltage.

An interesting application of the VCO is in phase-locked loops, which are used in various types of communications receivers to track variations in the frequency of incoming signals. You will learn about the basic operation of a phase-locked loop in Chapter 13.

SYSTEM EXAMPLE 10-2

AN ASK TEST GENERATOR

 In System Example 9-1 an RFID reader circuit was introduced. In order to test the reader, a circuit that will provide an ASK modulated output will simulate the signal from an RFID tag. This system example will incorporate two circuits covered in this chapter—an LC feedback oscillator and a free-running multivibrator.



Recall that the RFID tag transmits a 125 kHz ASK (amplitude shift keyed) signal modulated with coded information represented by a digital waveform. As a review, the basic block diagram of an RFID system is shown in Figure SE10–3.

 


FIGURE SE10–3 Block diagram of an RFID system.

The ASK Test Generator

In this system example, a circuit that can be used as a signal source for testing the RFID reader circuit board is developed. The test generator must produce a 125 kHz signal that is modulated with a 10 kHz pulse signal to simulate the RFID tag. An oscillator is used to generate the 125 kHz carrier signal, and a 555 timer produces the modulating pulse signal. The modulator is an analog switch that allows the carrier signal to be turned on and off by the modulating pulse signal. A basic block diagram of this circuit is shown in Figure SE10–4.

 


FIGURE SE10–4 Block diagram of the ASK test generator.

The 125 kHz Oscillator

The first step is to design and construct the 125 kHz oscillator circuit. A Colpitts oscillator built around a BJT is chosen for this design, but a FET could be used, or an op-amp-based Wien-bridge oscillator. Note the variable resistor R_{E1} and the precision tuning capacitor C_5 . R_{E1} allows for gain adjustment and C_5 allows for fine tuning the output frequency of the oscillator.

The 10 kHz Pulse Oscillator

For this test circuit, a 10 kHz square wave will be the modulating signal. A 555 timer configured in astable mode with a 50% duty cycle will be used to generate the 10 kHz square wave. Note the switching diode connected across R_B . The diode is required in order to produce a duty cycle of 50%. By adding the diode in parallel with R_B , C_{ext} charges only through R_A and discharges only through R_B . Since $R_A = R_B$ the duty cycle is 50%.

The Analog Switch

The final component that allows the 10 kHz square wave to turn the 125 kHz carrier on and off is an analog switch. When the 555 timer output is low, the analog switch turns on and the carrier signal is coupled to the ASK output. When the timer output is high, the analog switch turns off and the signal is blocked. A potentiometer at the output allows the test signal to be adjusted so that it matches the input requirements of the RFID reader.

SECTION 10-6 CHECKUP

1. When the 555 timer is configured as an astable multivibrator, how is the duty cycle determined?
2. When the 555 timer is used as a VCO, how is the frequency varied?

10-7 THE 555 TIMER AS A ONE-SHOT

A **one-shot** is a monostable multivibrator that produces a single output pulse for each input trigger pulse. The term *monostable* means that the device has only one stable state. When a one-shot is triggered, it temporarily goes to its unstable state but it always returns to its stable state. The time that it remains in its unstable state establishes the width of the output pulse and is set by the values of an external resistor and capacitor.

After completing this section, you should be able to

- Use a 555 timer as a one-shot device
- Discuss monostable operation
- Explain how to set the output pulse width

A 555 timer connected for **monostable** operation is shown in Figure 10-42. Compare this configuration to the one used for **astable** operation in Figure 10-36 and note the difference in the external circuit.

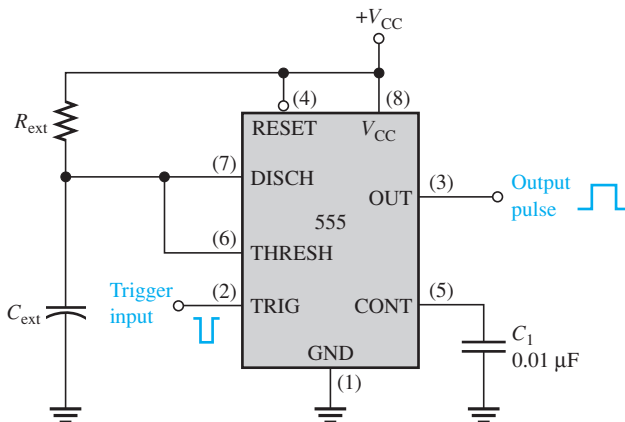


FIGURE 10-42 The 555 timer connected as a monostable multivibrator (one-shot).

Monostable Operation


A negative-going input trigger pulse produces a single output pulse with a predetermined width. Once triggered, the one-shot cannot be retriggered until it completely times out; that is, it completes a full output pulse. Once it times out, the one-shot can

then be triggered again to produce another output pulse. A low level on the reset input (RESET) can be used to prematurely terminate the output pulse. The width of the output pulse is determined by the following formula:

$$t_W = 1.1R_{\text{ext}}C_{\text{ext}} \quad (10-15)$$

The graph in Figure 10–43 shows various combinations of R_{ext} and C_{ext} and the associated output pulse widths. This graph can be used to select component values for a desired pulse width.

FIGURE 10–43 555 one-shot timing.

 

EXAMPLE 10–7

A 555 timer is connected as a one-shot with $R_{\text{ext}} = 10 \text{ k}\Omega$ and $C_{\text{ext}} = 0.1 \text{ }\mu\text{F}$. What is the pulse width of the output?


SOLUTION

You can determine the pulse width in two ways. You can use either Equation (10–15) or the graph in Figure 10–43. Using the formula,

$$t_W = 1.1R_{\text{ext}}C_{\text{ext}} = 1.1(10 \text{ k}\Omega)(0.1 \text{ }\mu\text{F}) = \mathbf{1.1 \text{ ms}}$$

To use the graph, move along the $C = 0.1 \text{ }\mu\text{F}$ line until it intersects with the sloped line corresponding to $R = 10 \text{ k}\Omega$. At that point, project down to the horizontal axis and you get a pulse width of 1.1 ms as illustrated in Figure 10–44.

FIGURE 10–44

 

PRACTICE EXERCISE

To what value must R_{ext} be changed to increase the one-shot's output pulse width to 5 ms?

Using One-Shots for Time Delay

In many applications, it is necessary to have a fixed time delay between certain events. Figure 10-45(a) shows two 555 timers connected as one-shots. The output of the first goes to the input of the second. When the first one-shot is triggered, it produces an output pulse whose width establishes a time delay. At the end of this pulse, the second one-shot is triggered. Therefore, we have an output pulse from the second one-shot that is delayed from the input trigger to the first one-shot by a time equal to the pulse width of the first one-shot, as indicated in the timing diagram in Figure 10-45(b).

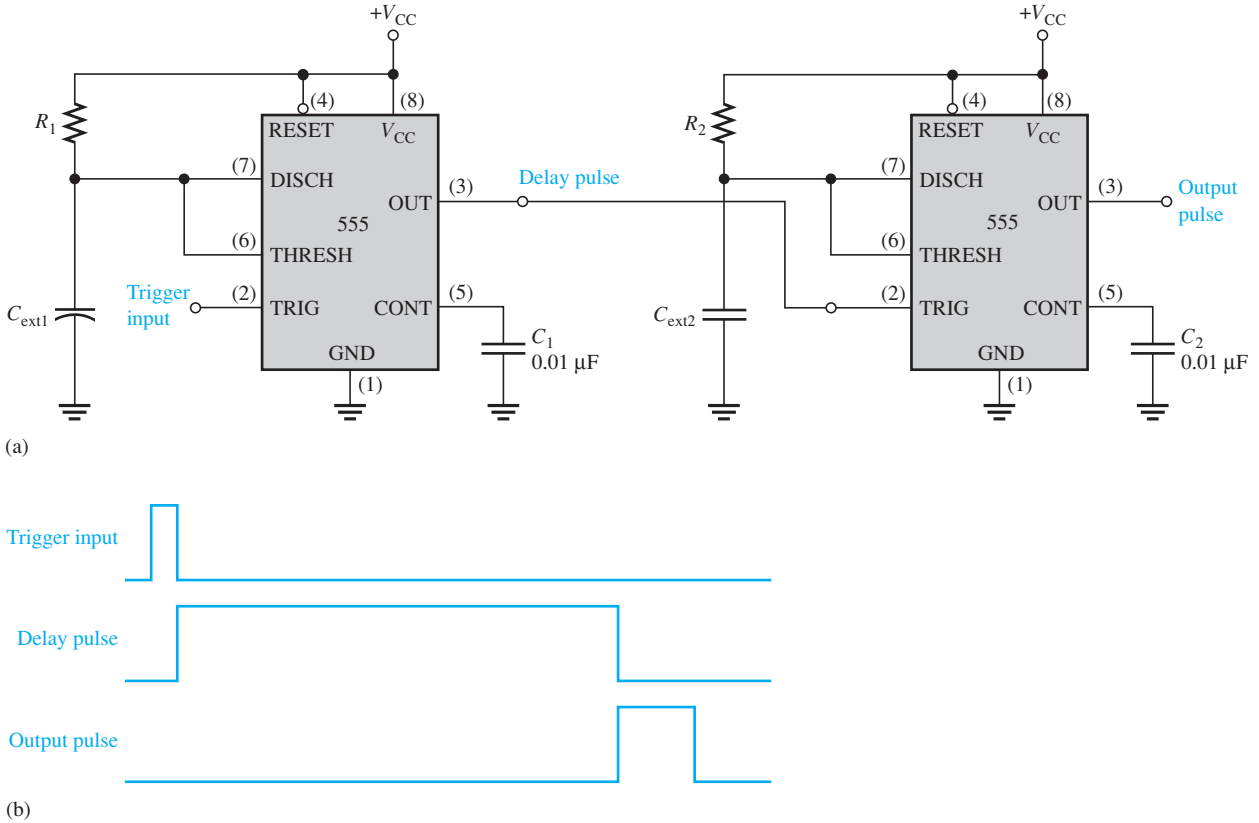


FIGURE 10-45 Two one-shots produce a delayed output pulse.

EXAMPLE 10-8

Determine the pulse widths and show the timing diagram (relationships of the input and output pulses) for the circuit in Figure 10-46.

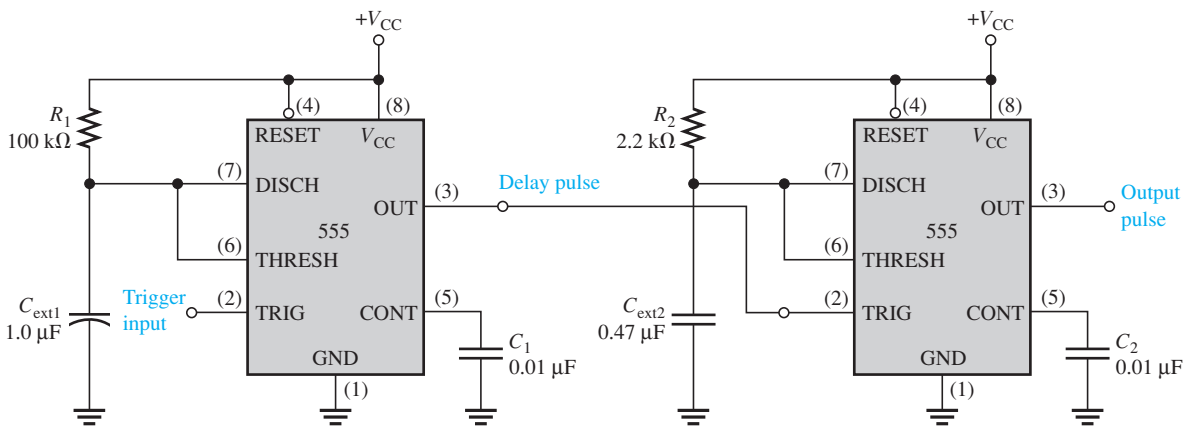


FIGURE 10-46

SOLUTION

The time relationship of the inputs and outputs are shown in Figure 10–47. The pulse widths for the two one-shots are

$$t_{W1} = 1.1R_1C_{\text{ext}1} = 1.1(100 \text{ k}\Omega)(1.0 \text{ }\mu\text{F}) = \mathbf{110 \text{ ms}}$$

$$t_{W2} = 1.1R_2C_{\text{ext}2} = 1.1(2.2 \text{ k}\Omega)(0.47 \text{ }\mu\text{F}) = \mathbf{1.14 \text{ ms}}$$

 


FIGURE 10–47

PRACTICE EXERCISE

Suggest a way that the circuit in Figure 10–46 can be modified so that the delay can be made adjustable from 10 ms to 200 ms.

SECTION 10–7 CHECKUP

1. How many stable states does a one-shot have?
2. A certain 555 one-shot circuit has a time constant of 5 ms. What is the output pulse width?
3. How can you decrease the pulse width of a one-shot?

SUMMARY

- Feedback oscillators operate with positive feedback.
- The two conditions for positive feedback are the phase shift around the feedback loop must be 0° and the voltage gain around the feedback loop must equal 1.
- For initial start-up, the voltage gain around the feedback loop must be greater than 1.
- Sinusoidal *RC* oscillators include the Wien-bridge, phase-shift, and twin-T.
- Sinusoidal *LC* oscillators include the Colpitts, Clapp, Hartley, Armstrong, and crystal-controlled.
- The feedback signal in a Colpitts oscillator is derived from a capacitive voltage divider in the *LC* circuit.
- The Clapp oscillator is a variation of the Colpitts with an extra capacitor added in series with the inductor in the feedback circuit.
- The feedback signal in a Hartley oscillator is derived from an inductive voltage divider in the *LC* circuit.
- The feedback signal in an Armstrong oscillator is derived by transformer coupling.
- Crystal-controlled oscillators are the most stable type of feedback oscillators.
- A relaxation oscillator uses an *RC* timing circuit and a device that changes states to generate a periodic waveform.
- The frequency in a voltage-controlled oscillator (VCO) can be varied with a dc control voltage.
- The 555 timer is an integrated circuit that can be used as an oscillator or as a one-shot by proper connection of external components.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Armstrong oscillator A type of LC feedback oscillator that uses transformer coupling in the feedback circuit.

Astable multivibrator A type of circuit that can operate as an oscillator and produces a pulse waveform output.

Clapp oscillator A variation of the Colpitts oscillator with an added capacitor in series with the inductor in the feedback circuit.

Colpitts oscillator A type of LC feedback oscillator that uses two series capacitors in the feedback circuit.

Feedback oscillator A type of oscillator that returns a fraction of output signal to the input with no net phase shift resulting in a reinforcement of the output signal.

Hartley oscillator A type of LC feedback oscillator that uses two series inductors in the feedback circuit.

One-shot A monostable multivibrator that produces a single output pulse for each input trigger pulse.

Phase-shift oscillator A type of sinusoidal feedback oscillator that uses three RC networks in the feedback loop.

Piezoelectric effect The property exhibited by a material where it produces a voltage at the frequency at which it vibrates due to changing mechanical stress.

Positive feedback A condition where an in-phase portion of the output voltage is fed back to the input.

Relaxation oscillator A type of oscillator that uses an RC timing circuit to generate a nonsinusoidal waveform.

Voltage-controlled oscillator A type of relaxation oscillator whose frequency can be changed by a variable dc voltage; also known as a VCO.

Wien-bridge oscillator A type of sinusoidal feedback oscillator that uses an RC lead-lag network in the feedback loop.

KEY FORMULAS

$$(10-1) \quad \frac{V_{out}}{V_{in}} = \frac{1}{3} \quad \text{Wien-bridge positive feedback attenuation}$$

$$(10-2) \quad f_r = \frac{1}{2\pi RC} \quad \text{Wien-bridge frequency}$$

$$(10-3) \quad B = \frac{1}{29} \quad \text{Phase-shift feedback attenuation}$$

$$(10-4) \quad f_r = \frac{1}{2\pi\sqrt{6RC}} \quad \text{Phase-shift oscillator frequency}$$

$$(10-5) \quad f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

$$(10-6) \quad A_v = \frac{C_1}{C_2}$$

$$(10-7) \quad f_r \cong \frac{1}{2\pi\sqrt{LC_T}} \sqrt{\frac{Q^2}{Q^2 + 1}}$$

$$(10-8) \quad A_v \cong \frac{L_2}{L_1}$$

$$(10-9) \quad f_r \cong \frac{1}{2\pi\sqrt{L_{pri}C_1}}$$

$$(10-10) \quad f = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right) \quad \text{Triangular wave generator frequency}$$

- (10-11) $f = \frac{|V_{IN}|}{R_f C} \left(\frac{1}{V_P - V_F} \right)$ Sawtooth VCO frequency
- (10-12) $f = \frac{1.44}{(R_1 + 2R_2)C_{ext}}$ 555 astable frequency
- (10-13) Duty cycle = $\left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\%$ 555 astable (duty cycle $\geq 50\%$)
- (10-14) Duty cycle = $\left(\frac{R_1}{R_1 + R_2} \right) 100\%$ 555 astable (duty cycle $< 50\%$)
- (10-15) $t_W = 1.1R_{ext}C_{ext}$ 555 one-shot pulse width

SELF-TEST


Answers are at the end of the chapter.

- An oscillator differs from an amplifier because it
 - has more gain
 - requires no input signal
 - requires no dc supply
 - always has the same output
- Wien-bridge oscillators are based on
 - positive feedback
 - negative feedback
 - the piezoelectric effect
 - high gain
- One condition for oscillation is a
 - phase shift around the feedback loop of 180°
 - gain around the feedback loop of one-third
 - phase shift around the feedback loop of 0°
 - gain around the feedback loop of less than one
- A second condition for oscillation is
 - no gain around the feedback loop
 - a gain of one around the feedback loop
 - the attenuation of the feedback network must be one-third
 - the feedback network must be capacitive
- In a certain oscillator, $A_v = 50$. The attenuation of the feedback network must be
 - 1
 - 0.01
 - 10
 - 0.02
- For an oscillator to properly start, the gain around the feedback loop must initially be
 - 1
 - less than 1
 - greater than 1
 - equal to B
- In a Wien-bridge oscillator, if the resistances in the feedback circuit are decreased, the frequency
 - decreases
 - increases
 - remains the same
- The Wien-bridge oscillator's positive feedback circuit is a(n)
 - RL network
 - LC network
 - voltage divider
 - lead-lag network
- A phase-shift oscillator has
 - three RC networks
 - three LC networks
 - a T-type network
 - a π -type network
- Colpitts, Clapp, and Hartley are names that refer to
 - types of RC oscillators
 - inventors of transistors
 - types of LC oscillators
 - types of active filters
- The main feature of a crystal oscillator is
 - economy
 - reliability
 - stability
 - wide bandwidth
- An oscillator whose frequency is changed by a variable dc voltage is known as a(n)
 - Wien-bridge oscillator
 - VCO
 - phase-shift oscillator
 - astable multivibrator

13. Which one of the following is not an input or output of the 555 timer?
- (a) Threshold (b) Control voltage
(c) Clock (d) Trigger
(e) Discharge (f) Reset
14. An astable multivibrator is
- (a) an oscillator (b) a one-shot
(c) a time-delay circuit (d) characterized by having no stable states
(e) answers (a) and (d)
15. The output frequency of a 555 timer connected as an oscillator is determined by
- (a) the supply voltage (b) the frequency of the trigger pulses
(c) the external RC time constant (d) the internal RC time constant
(e) answers (a) and (d)
16. The term *monostable* means
- (a) one output (b) one frequency
(c) one time constant (d) one stable state
17. A 555 timer connected as a one-shot has $R_{\text{ext}} = 2.0 \text{ k}\Omega$ and $C_{\text{ext}} = 2.0 \text{ }\mu\text{F}$. The output pulse has a width of
- (a) 1.1 ms (b) 4 ms
(c) 4 μs (d) 4.4 ms

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

 

Refer to Figure 10–48.

- If D_1 suddenly opens,
 1. The closed-loop gain will
(a) increase (b) decrease (c) not change
 2. The output amplitude will
(a) increase (b) decrease (c) not change
- If D_2 has a 5.1 V breakdown voltage instead of the specified 4.7 V,
 3. The output voltage will
(a) increase (b) decrease (c) not change
 4. The frequency of oscillation will
(a) increase (b) decrease (c) not change

Refer to Figure 10–49.

- If the capacitors are 0.01 μF instead of 0.02 μF ,
 5. The frequency of oscillation will
(a) increase (b) decrease (c) not change

Refer to Figure 10–50.

- If the op-amp dc supply voltage decreases,
 6. The frequency of oscillation will
(a) increase (b) decrease (c) not change
 7. The amplitude of the triangular output will
(a) increase (b) decrease (c) not change

Refer to Figure 10–52.

- If R_2 is less than the specified value,
 8. The frequency of the output will
(a) increase (b) decrease (c) not change
 9. The duty cycle of the output will
(a) increase (b) decrease (c) not change

- If C_1 is open,
 10. The frequency of the output will
 - (a) increase
 - (b) decrease
 - (c) not change
 11. The duty cycle will
 - (a) increase
 - (b) decrease
 - (c) not change
 12. The amplitude of the output will
 - (a) increase
 - (b) decrease
 - (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 10-1 The Oscillator

1. What type of input is required for an oscillator?
2. What are the basic components of an oscillator circuit?

SECTION 10-2 Feedback Oscillator Principles

3. If the voltage gain of the amplifier portion of an oscillator is 75, what must be the attenuation of the feedback circuit to sustain the oscillation?
4. Generally describe the change required in the oscillator of Problem 3 in order for oscillation to begin when the power is initially turned on.

SECTION 10-3 Sinusoidal Oscillators with RC Feedback Circuits

5. A certain lead-lag network has a resonant frequency of 3.5 kHz. What is the rms output voltage if an input signal with a frequency equal to f_r and with an rms value of 2.2 V is applied to the input?
6. Calculate the resonant frequency of a lead-lag network with the following values:
 $R_1 = R_2 = 6.2 \text{ k}\Omega$, and $C_1 = C_2 = 0.02 \text{ }\mu\text{F}$.
7. Determine the necessary value of R_2 in Figure 10-48 so that the circuit will oscillate. Neglect the forward resistance of the zener diodes. (*Hint*: The total gain of the circuit must be 3 when the zener diodes are conducting.)
8. Explain the purpose of R_3 in Figure 10-48.

 


FIGURE 10-48

9. For the Wien-bridge in Figure 10–49, calculate the setting for R_f , assuming the internal drain-source resistance, r'_{ds} , of the JFET is $350\ \Omega$ when oscillations are stable.

 


FIGURE 10–49

10. Find the frequency of oscillation for the Wien-bridge oscillator in Figure 10–49.
 11. What value of R_f is required in Figure 10–50? What is f_r ?

 


FIGURE 10–50

SECTION 10–4 Oscillators with LC Feedback Circuits

12. Calculate the frequency of oscillation for each circuit in Figure 10–51 and identify the type of oscillator. Assume $Q > 10$ in each case.

 


FIGURE 10–51

13. Determine what the gain of the amplifier stage must be in Figure 10–52 in order to have sustained oscillation.

 


FIGURE 10-52

SECTION 10-5 Relaxation Oscillator Principles

14. What type of signal does the circuit in Figure 10–53 produce? Determine the frequency of the output.
15. Show how to change the frequency of oscillation in Figure 10–53 to 10 kHz.

 


FIGURE 10-53

16. Determine the amplitude and frequency of the output voltage in Figure 10–54. Use 1 V as the forward PUT voltage.

 


FIGURE 10-54

17. Modify the sawtooth generator in Figure 10–54 so that its peak-to-peak output is 4 V.
18. A certain sawtooth generator has the following parameter values: $V_{IN} = 3\text{ V}$, $R = 4.7\text{ k}\Omega$, $C = 0.001\text{ }\mu\text{F}$, and V_F for the PUT is 1.2 V. Determine its peak-to-peak output voltage if the period is $10\text{ }\mu\text{s}$.

SECTION 10–6 The 555 Timer as an Oscillator

19. What are the two comparator reference voltages in a 555 timer when $V_{CC} = 10\text{ V}$?
20. Determine the frequency of oscillation for the 555 astable oscillator in Figure 10–55.
21. To what value must C_{ext} be changed in Figure 10–55 to achieve a frequency of 25 kHz?
22. In an astable 555 configuration, the external resistor $R_1 = 3.3\text{ k}\Omega$. What must R_2 equal to produce a duty cycle of 75 percent?

 


FIGURE 10–55

SECTION 10–7 The 555 Timer as a One-Shot

23. A 555 timer connected in the monostable configuration has a $56\text{ k}\Omega$ external resistor and a $0.22\text{ }\mu\text{F}$ external capacitor. What is the pulse width of the output?
24. The output pulse width of a certain 555 one-shot is 12 ms. If $C_{ext} = 2.2\text{ }\mu\text{F}$, what is R_{ext} ?
25. Suppose that you need to hook up a 555 timer as a one-shot in the lab to produce an output pulse with a width of $100\text{ }\mu\text{s}$. Select the appropriate values for the external components.
26. Devise a circuit to produce two sequential $50\text{ }\mu\text{s}$ pulses. The first pulse must occur 100 ms after an initial trigger and the second pulse must occur 300 ms after the first pulse.

MULTISIM TROUBLESHOOTING PROBLEMS

MULTISIM



27. Open file P10-27 and determine the fault.
28. Open file P10-28 and determine the fault.
29. Open file P10-29 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 10-1

1. An oscillator is a circuit that produces a repetitive output waveform with only the dc supply voltage as an input.
2. Positive feedback
3. The feedback network provides attenuation and phase shift.

SECTION 10-2

1. Zero phase shift and unity voltage gain around the closed feedback
2. Positive feedback is when a portion of the output signal is fed back to the input of the amplifier such that it reinforces itself.
3. Loop gain greater than 1

SECTION 10-3

1. The negative feedback loop sets the closed-loop gain; the positive feedback loop sets the frequency of oscillation.
2. 1.67 V
3. The three RC networks contribute a total of 180° and the inverting amplifier contributes 180° for a total of 360° around the loop.
4. 3.4

SECTION 10-4

1. The Colpitts uses two series capacitors in parallel with an inductor in the feedback circuit. The Hartley uses two series inductors in parallel with a capacitor.
2. The FET has higher input resistance than a BJT and does not load the resonant circuit as much.
3. The Clapp has an extra capacitor in series with the inductor in the feedback circuit.

SECTION 10-5

1. A voltage-controlled oscillator exhibits a frequency that can be varied with a dc control voltage.
2. The basis of a relaxation oscillator is the charging and discharging of a capacitor.
3. A special high-frequency bandpass filter that can be used at microwave frequencies

SECTION 10-6

1. The duty cycle is set by the external resistors and the external capacitor.
2. The frequency of a VCO is varied by changing V_{CONT} .

SECTION 10-7

1. A one-shot has one stable state.
2. $t_W = 5.5$ ms
3. The pulse width can be decreased by decreasing the external resistance or capacitance.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

10-1 If R_f is too large, the output is distorted. If R_f is too small, oscillations cease.

10-2 (a) 238 k Ω (b) 7.92 kHz

10-3 7.24 kHz

10-4 6.06 V peak-to-peak

10-5 1055 Hz

10-6 31.9%

10-7 45.5 k Ω

10-8 Replace R_1 with a potentiometer with a maximum resistance of at least 182 k Ω .

ANSWERS TO SELF-TEST

- | | | | | | |
|---------|---------|---------|---------|---------|---------|
| 1. (b) | 2. (a) | 3. (c) | 4. (b) | 5. (d) | 6. (c) |
| 7. (b) | 8. (d) | 9. (a) | 10. (c) | 11. (c) | 12. (b) |
| 13. (c) | 14. (e) | 15. (c) | 16. (d) | 17. (d) | |

ANSWERS TO TROUBLESHOOTER'S QUIZ

- | | | | |
|-------------|----------------|----------------|----------------|
| 1. increase | 2. increase | 3. increase | 4. not change |
| 5. increase | 6. not change | 7. decrease | 8. increase |
| 9. increase | 10. not change | 11. not change | 12. not change |

CHAPTER 11

VOLTAGE REGULATORS

OUTLINE

- 11-1 Voltage Regulation
- 11-2 Basic Series Regulators
- 11-3 Basic Shunt Regulators
- 11-4 Basic Switching Regulators
- 11-5 Integrated Circuit Voltage Regulators
- 11-6 Applications of IC Voltage Regulators

OBJECTIVES

- Describe line and load regulation
- Discuss the principles of series voltage regulators
- Discuss the principles of shunt voltage regulators
- Discuss the principles of switching regulators
- Discuss integrated circuit voltage regulators
- Discuss applications of IC voltage regulators

KEY TERMS

Line regulation

Load regulation

Linear regulator

Switching regulator

INTRODUCTION

A voltage **regulator** provides a constant dc output voltage that is practically independent of the input voltage, output load current, and temperature. The voltage regulator is one part of a power supply. Its input voltage comes from the filtered output of a rectifier derived from an ac voltage or from a battery in the case of portable systems.

Most voltage regulators fall into two broad categories—linear regulators and switching regulators. In the linear regulator category, two general types are the linear series regulator and the linear shunt regulator. These are normally available for either positive or negative output voltages. A dual regulator provides both positive and negative outputs. In the switching regulator category, three general configurations are step-down, step-up, and inverting.

Many types of integrated circuit (IC) regulators are available. The most popular types of linear regulator are the three-terminal fixed voltage regulator and the three-terminal adjustable voltage regulator. Switching regulators are also widely used in computer systems. In this chapter, specific IC devices are introduced as representative of the wide range of available devices.

VISIT THE WEBSITE

Study aids for this chapter are available at

<http://pearsonhighered.com/floyd>

11-1 VOLTAGE REGULATION

The requirement for a reliable source of constant voltage in virtually all electronic systems has led to many advances in power supply design. Designers have used feedback and operational amplifiers, as well as pulse circuit techniques to develop reliable constant-voltage (and constant-current) power supplies. The heart of any regulated supply is the ability to establish a constant-voltage reference. In this section, you will learn more about line and load regulation (introduced in Section 2-6).

After completing this section, you should be able to

- Describe line and load voltage regulation
 - Express line regulation as either a percentage or as a percentage per volt
 - Calculate line regulation
 - Express load regulation as either a percentage or as a percentage per milliamp
 - Calculate load regulation from either voltage data or resistance data

Line Regulation

Line regulation was introduced in Section 2-6 and is reviewed here. **Line regulation** is a measure of the ability of a power supply to maintain a constant output for changes in the input voltage. It is typically defined as a ratio of a change in output for a corresponding change in the input and expressed as a percentage.

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\% \quad (11-1)$$

This equation was given earlier as Equation (2-3). Some specification sheets show line regulation differently. It can be specified as a percentage change in the output voltage per volt divided by change in the input voltage. In this case, line regulation is defined and expressed as a percentage as

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}/V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\% \quad (11-2)$$

Because this definition is different, you need to be sure which definition is used when reading specifications. The key in a specification sheet is to look at the units. If the specification is a ratio of mV/V or other pure number, then Equation (11-1) is the defining equation. If the units are shown as %/mV or %/V, then Equation (11-2) is the defining equation.

EXAMPLE 11-1

When the input to a particular voltage regulator decreases by 5 V, the output decreases by 0.25 V. The nominal output is 15 V. Determine the line regulation expressed as a percentage and in units of %/V.

SOLUTION

From Equation (11-1), the percent line regulation is

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\% = \left(\frac{0.25 \text{ V}}{5 \text{ V}} \right) 100\% = 5\%$$

From Equation (11-2), the percent line regulation is

$$\text{Line regulation} = \left(\frac{\Delta V_{\text{OUT}}/V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\% = \left(\frac{0.25 \text{ V}/15 \text{ V}}{5 \text{ V}} \right) 100\% = 0.33\%/V$$

PRACTICE EXERCISE*

The input of a certain regulator increases by 3.5 V. As a result, the output voltage increases by 0.42 V. The nominal output is 20 V. Determine the regulation expressed as a percentage and in units of %/V.

*Answers are at the end of the chapter.

Load Regulation

Load regulation was introduced in Section 2–6 and is reviewed here. When the amount of current through a load changes due to a varying load resistance, the voltage regulator must maintain a nearly constant output voltage across the load. The percent load regulation specifies how much change occurs in the output voltage over a certain range of load current values, usually from minimum current (no load, NL) to maximum current (full load, FL). Ideally, the percent load regulation is 0%. It can be calculated and expressed as a percentage with the following formula:

$$\text{Load regulation} = \left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) 100\% \quad (11-3)$$

where V_{NL} is the output voltage with no load, and V_{FL} is the output voltage with full (maximum) load. This equation was given earlier as Equation (2–4). Equation (11–3) is expressed as a change due only to changes in load conditions; all other factors (such as input voltage and operating temperature) must remain constant. Normally, the operating temperature is specified as 25 °C.

 


FIGURE 11-1 Thevenin equivalent circuit for a power supply with a load resistor.

Sometimes power supply manufacturers specify the equivalent output resistance of a power supply (R_{OUT}) instead of its load regulation. Recall (Section 1–3) that an equivalent Thevenin circuit can be drawn for any two-terminal linear circuit. Figure 11–1 shows the equivalent Thevenin circuit for a power supply with a load resistor. The Thevenin voltage is the voltage from the supply with no load (V_{NL}), and the Thevenin resistance is the specified output resistance, R_{OUT} . Ideally, R_{OUT} is zero, corresponding to 0% load regulation, but in practical power supplies R_{OUT} is a small value. With the load resistor in place, the output voltage is found by applying the voltage-divider rule:

$$V_{\text{OUT}} = V_{\text{NL}} \left(\frac{R_L}{R_{\text{OUT}} + R_L} \right)$$

If we let R_{FL} equal the smallest-rated load resistance (largest-rated current), then the full-load output voltage (V_{FL}) is

$$V_{\text{FL}} = V_{\text{NL}} \left(\frac{R_{\text{FL}}}{R_{\text{OUT}} + R_{\text{FL}}} \right)$$

By rearranging and substituting into Equation (11–3),

$$\begin{aligned} V_{\text{NL}} &= V_{\text{FL}} \left(\frac{R_{\text{OUT}} + R_{\text{FL}}}{R_{\text{FL}}} \right) \\ \text{Load regulation} &= \frac{V_{\text{FL}} \left(\frac{R_{\text{OUT}} + R_{\text{FL}}}{R_{\text{FL}}} \right) - V_{\text{FL}}}{V_{\text{FL}}} \times 100\% = \left(\frac{R_{\text{OUT}} + R_{\text{FL}}}{R_{\text{FL}}} - 1 \right) 100\% \end{aligned}$$

$$\text{Load regulation} = \left(\frac{R_{\text{OUT}}}{R_{\text{FL}}} \right) 100\% \quad (11-4)$$

Equation (11–4) is a useful way of finding the percent load regulation when the output resistance and minimum load resistance are specified.

Alternately, the load regulation can be expressed as a percentage change in output voltage for each mA change in load current. For example, a load regulation of 0.01%/mA means that the output voltage changes 0.01 percent when the load current increases or decreases by 1 mA.

EXAMPLE 11-2

A certain voltage regulator has a +12.1 V output when there is no load ($I_L = 0$) and has a rated output current of 200 mA. With maximum current, the output voltage drops to +12.0 V. Determine the percentage load regulation and find the percent load regulation per mA change in load current.

SOLUTION

The no-load output voltage is

$$V_{NL} = 12.1 \text{ V}$$

The full-load output voltage is

$$V_{FL} = 12.0 \text{ V}$$

The percent load regulation is

$$\text{Load regulation} = \left(\frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\% = \left(\frac{12.1 \text{ V} - 12.0 \text{ V}}{12.0 \text{ V}} \right) 100\% = \mathbf{0.83\%}$$

The load regulation can also be expressed as

$$\text{Load regulation} = \frac{0.83\%}{200 \text{ mA}} = \mathbf{0.0042\%/mA}$$

PRACTICE EXERCISE

Prove that the results of this example are consistent with a specified output resistance of 0.5 Ω .

SECTION 11-1 CHECKUP*

1. Define *line regulation*.
2. Define *load regulation*.
3. The input of a certain regulator increases by 3.5 V. As a result, the output voltage increases by 0.042 V. The nominal output is 20 V. Determine the line regulation in both % and in %/V.
4. If a 5.0 V power supply has an output resistance of 80 m Ω and a specified maximum output current of 1.0 A, what is the load regulation? Give the result as a % and as a %/mA.

*Answers are at the end of the chapter.

11–2 BASIC SERIES REGULATORS

The fundamental classes of voltage regulators are linear regulators and switching regulators. Both of these are available in integrated circuit form. There are two basic types of linear regulator. One is the series regulator and the other is the shunt regulator. In this section, we will look at the series regulator. The shunt and switching regulators are covered in the next two sections.

After completing this section, you should be able to

- Discuss the principles of series voltage regulators
- Explain regulating action
- Calculate output voltage of an op-amp series regulator
- Discuss overload protection and explain how to use current limiting
- Describe a regulator with fold-back current limiting

A simple representation of a series type of **linear regulator** is shown in Figure 11–2(a), and the basic components are shown in the block diagram in Figure 11–2(b). Notice that the control element is in series with the load between input and output. The output sample circuit senses a change in the output voltage. The error detector compares the sample voltage with a reference voltage and causes the control element to compensate in order to maintain a constant output voltage.

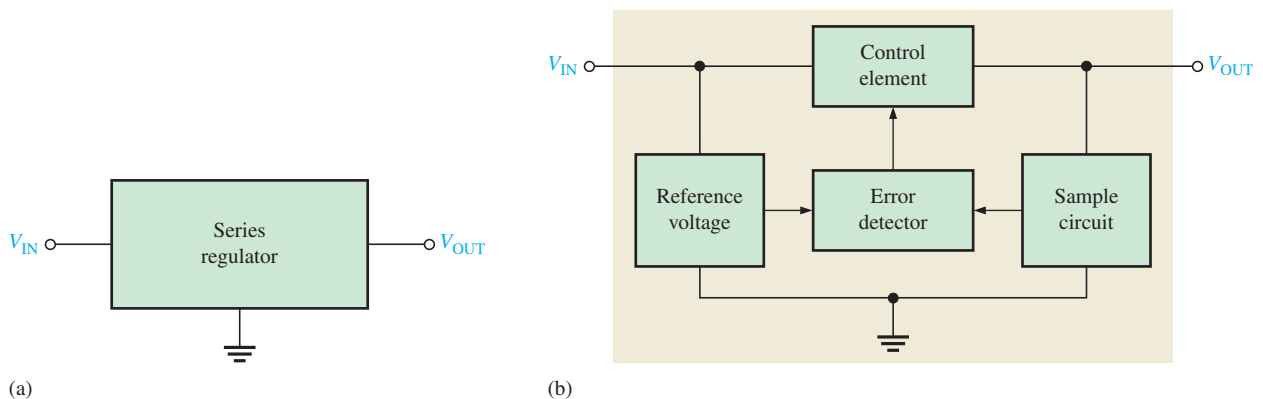


FIGURE 11–2 Simple series voltage regulator block diagram.

Voltage References

The ability of a voltage regulator to provide a constant output is dependent on the stability of a voltage reference to maintain a constant voltage for any change in temperature or other condition. Traditionally zener diodes (discussed in Section 2–8) were used as references. Zeners are designed to break down at a specific voltage and maintain a fairly constant voltage if the current in the zener is constant and the temperature does not change. The drawback to zener diodes is they tend to be noisy and the zener voltage may change slightly as the zener ages (this is called *drift*). An even more serious effect is that the zener voltage is sensitive to temperature changes; the zener voltage can change hundreds of parts per million (ppm) for a change of just 1 °C in temperature. This temperature effect varies widely among different types of zeners.

An alternative to the zener diode is the voltage reference IC. Voltage references are special low-noise ICs that provide precise initial accuracy and very low temperature drift. For example, the National Instruments LM4140 series voltage reference has an initial accuracy of 0.1% and a temperature coefficient (tempco) as low as 3 ppm/°C. The LM4030 shunt regulator has a better initial accuracy of 0.05% but its tempco is not quite as good at 10 ppm/°C. The LM4140 series reference comes as an 8-pin IC and is connected as shown

in Figure 11-3(a). The shunt reference LM4030 is a 5-pin IC and is connected as shown in Figure 11-3(b). As you can see, the schematic symbol for the shunt voltage reference is the same as for a zener diode. Wherever you see this symbol used in any of the voltage regulator circuits in this chapter, either a zener or a voltage reference IC can be used, depending on the accuracy required.

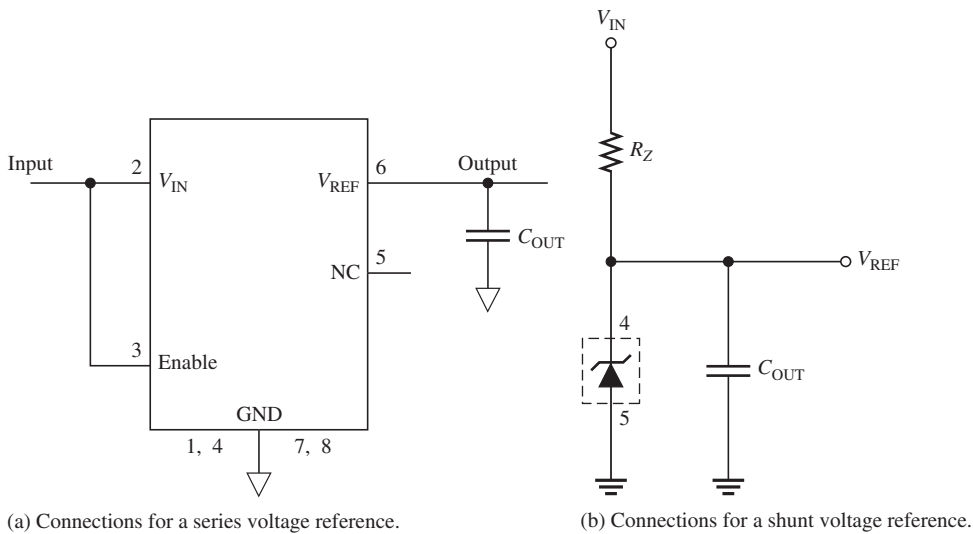



FIGURE 11-3

It should also be noted that voltage references are used in many other applications besides voltage regulators. They are commonly used in high-precision ADCs and DACs as well as low-noise references for sensor conditioners, voltage monitors, current limiters, and programmable current sources. The data sheets for the LM4030 and the LM4140 series of regulators can be found at www.national.com.

In any electronic system, device failure will eventually occur. We tend to think of device failure in terms of catastrophic failures, such as shorts or opens, but any device will change its characteristics over time. This is of special concern when dealing with precision devices such as a voltage reference IC. For example, the LM4030 shunt voltage reference has a long-term stability rating of 40 ppm for 1000 hours of use. This spec is based upon a temperature of 25 °C over the 1000 hours of use.

The concept of device fatigue is something that a technician or technologist must be aware of when working with precision circuits. Each device in the system may appear to be fully functional, but some devices must be replaced simply due to the fact that they have drifted from their original specifications over time. When troubleshooting a system that is performing outside its original design specs, device fatigue is something that needs to be considered.

SYSTEM NOTE


 


Regulating Action

A basic op-amp series regulator circuit is shown in Figure 11-4. The operation of the series regulator is illustrated in Figure 11-5. The resistive voltage divider formed by R_2 and R_3 senses any change in the output voltage.


Figure 11-5(a) illustrates what happens when the output tries to decrease because of a decrease in V_{IN} or because of a change in load current. A proportional voltage decrease is applied to the op-amp's inverting input by the voltage divider. Since the zener diode (D_1) holds the other op-amp input at a nearly fixed reference voltage, V_{REF} , a small difference voltage (error voltage) is developed across the op-amp's inputs. This difference voltage is

FIGURE 11-4 Basic op-amp series regulator.

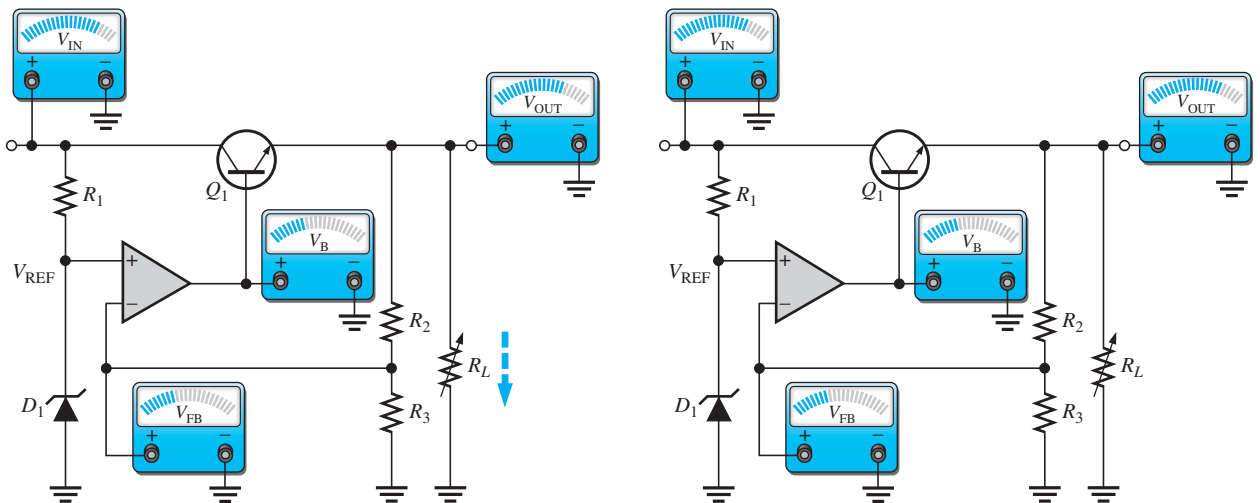 

(a) When V_{IN} or R_L decreases, V_{OUT} attempts to decrease. The feedback voltage, V_{FB} , also attempts to decrease, and as a result, the op-amp's output voltage V_B attempts to increase, thus compensating for the attempted decrease in V_{OUT} by increasing the Q_1 emitter voltage. Changes in V_{OUT} are exaggerated for illustration.

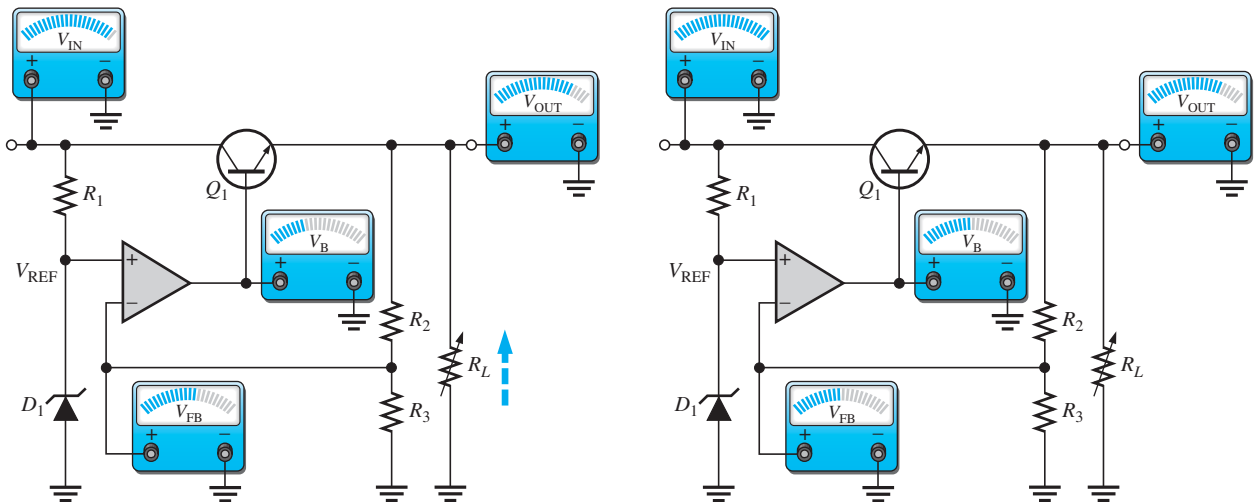(b) When V_{IN} (or R_L) stabilizes at its new lower value, the voltages return to their original values, thus keeping V_{OUT} constant as a result of the negative feedback.



(c) When V_{IN} or R_L increases, V_{OUT} attempts to increase. The feedback voltage, V_{FB} , also attempts to increase, and as a result, V_B , applied to the base of the control transistor, attempts to decrease, thus compensating for the attempted increase in V_{OUT} by decreasing the Q_1 emitter voltage.

(d) When V_{IN} (or R_L) stabilizes at its new higher value, the voltages return to their original values, thus keeping V_{OUT} constant as a result of the negative feedback.

FIGURE 11-5 Illustration of series regulator action that keeps V_{OUT} constant when V_{IN} or R_L changes.

amplified, and the op-amp's output voltage increases. For highest accuracy, D_1 is replaced with an IC reference. This increase is applied to the base of Q_1 , causing the emitter voltage V_{OUT} to increase until the voltage to the inverting input again equals the reference (zener) voltage. This action offsets the attempted decrease in output voltage, thus keeping it nearly constant, as shown in part (b). The power transistor, Q_1 , is used with a heat sink because it must handle all of the load current.

The opposite action occurs when the output tries to increase, as indicated in Figure 11-5(c) and (d). The op-amp in the series regulator is actually connected as a noninverting amplifier where the reference voltage V_{REF} is the input at the noninverting terminal, and the R_2/R_3 voltage divider forms the negative feedback network. The closed-loop voltage gain is

$$A_{cl} = 1 + \frac{R_2}{R_3}$$

Therefore, the regulated output voltage of the series regulator is

$$V_{OUT} \cong \left(1 + \frac{R_2}{R_3}\right)V_{REF} \quad (11-5)$$

From this analysis, you can see that the output voltage is determined by the zener voltage (V_{REF}) and the feedback ratio of R_2/R_3 . It is relatively independent of the input voltage, and therefore regulation is achieved (as long as the input voltage and load current are within specified limits).

EXAMPLE 11-3

Determine the output voltage for the regulator in Figure 11-6 and the base voltage of Q_1 .

 


FIGURE 11-6

SOLUTION

$V_{REF} = 5.1$ V, the zener voltage. The regulated output voltage is therefore

$$V_{OUT} = \left(1 + \frac{R_2}{R_3}\right)V_{REF} = \left(1 + \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega}\right)5.1 \text{ V} = (2)5.1 \text{ V} = \mathbf{10.2 \text{ V}}$$

The base voltage of Q_1 is

$$V_B = 10.2 \text{ V} + V_{BE} = 10.2 \text{ V} + 0.7 \text{ V} = \mathbf{10.9 \text{ V}}$$

PRACTICE EXERCISE

The following changes are made in the circuit in Figure 11-6: A 3.3 V zener replaces the 5.1 V zener, $R_1 = 1.8$ k Ω , $R_2 = 22$ k Ω , and $R_3 = 18$ k Ω . What is the output voltage?

MULTISIM




Open file F11-06 found on the companion website. This simulation demonstrates the operation and line regulation of a basic op-amp series regulator.

Short-Circuit or Overload Protection

If an excessive amount of load current is drawn, the series-pass transistor can be quickly damaged or destroyed. Most regulators use some type of current-limiting mechanism. Figure 11–7 shows one method of current limiting to prevent overloads called *constant-current limiting*. The current-limiting circuit consists of transistor Q_2 and resistor R_4 .

FIGURE 11–7 Series regulator with constant-current limiting.

 

The load current through R_4 produces a voltage from base to emitter of Q_2 . When I_L reaches a predetermined maximum value, the voltage drop across R_4 is sufficient to forward-bias the base-emitter junction of Q_2 , thus causing it to conduct. Enough Q_1 base current is diverted into the collector of Q_2 so that I_L is limited to its maximum value $I_{L(\max)}$. Since the base-to-emitter voltage of Q_2 cannot exceed about 0.7 V, the voltage across R_4 is held to this value, and the load current is limited to

$$I_{L(\max)} = \frac{0.7 \text{ V}}{R_4} \quad (11-6)$$

EXAMPLE 11–4

Determine the maximum current that the regulator in Figure 11–8 can provide to a load.

 


FIGURE 11–8

SOLUTION

$$I_{L(\max)} = \frac{0.7 \text{ V}}{R_4} = \frac{0.7 \text{ V}}{1.0 \Omega} = 0.7 \text{ A}$$

PRACTICE EXERCISE

If the output of the regulator in Figure 11–8 is shorted to ground, what is the current?

MULTISIM



Open file F11-08 found on the companion website. This simulation illustrates the short-circuit protection provided by adding a current-limiting transistor to the series regulator.

Regulator with Fold-Back Current Limiting

In the previous current-limiting technique, the current is restricted to a maximum constant value. **Fold-back current limiting** is a method used particularly in high-current regulators whereby the output current under overload conditions drops to a value well below the peak load current capability to prevent excessive power dissipation.

BASIC IDEA The basic concept of fold-back current limiting is as follows, with reference to Figure 11-9. The circuit is similar to the constant current-limiting arrangement in Figure 11-7, with the exception of resistors R_5 and R_6 . The voltage drop developed across R_4 by the load current must not only overcome the base-emitter voltage required to turn on Q_2 , but it must also overcome the voltage across R_5 . That is, the voltage across R_4 must be

$$V_{R4} = V_{R5} + V_{BE}$$

 


FIGURE 11-9 Series regulator with fold-back current limiting.

In an overload or short-circuit condition, the load current increases to a value, $I_{L(max)}$, that is sufficient to cause Q_2 to conduct. At this point the current can increase no further. The decrease in output voltage results in a proportional decrease in the voltage across R_5 ; thus less current through R_4 is required to maintain the forward-biased condition of Q_1 . So, as V_{OUT} decreases, I_L decreases, as shown in the graph of Figure 11-10.

The advantage of this technique is that the regulator is allowed to operate with peak load current up to $I_{L(max)}$; but when the output becomes shorted, the current drops to a lower value to prevent overheating of the device.

 


FIGURE 11-10 Fold-back current limiting (output voltage versus load current).

SECTION 11-2 CHECKUP

1. What are the basic components in a series regulator?
2. A certain series regulator has an output voltage of 8 V. If the op-amp's closed loop gain is 4, what is the value of the reference voltage?
3. What is the typical symptom of fatigue failure?

11-3 BASIC SHUNT REGULATORS

The second basic type of linear voltage regulator is the shunt regulator. As you have learned, the control element in the series regulator is the series-pass transistor. In the shunt regulator, the control element is a transistor in parallel (shunt) with the load.

After completing this section, you should be able to

- Discuss the principles of shunt voltage regulators
- Describe the operation of a basic op-amp shunt regulator
- Compare series and shunt regulators

A simple representation of a shunt type of linear regulator is shown in Figure 11-11(a), and the basic components are shown in the block diagram in part (b) of the figure.

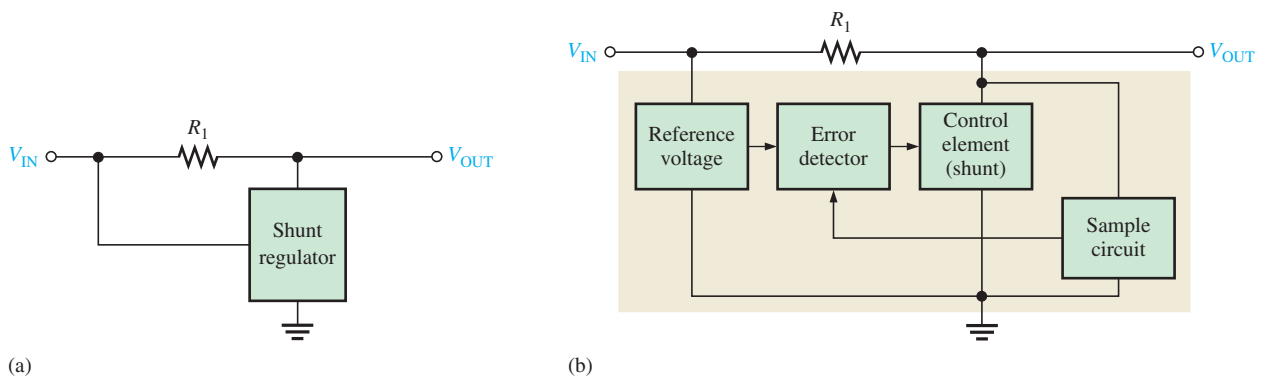


FIGURE 11-11 Simple shunt regulator and block diagram.

In the basic shunt regulator, the control element is a transistor, Q_1 , in parallel with the load, as shown in Figure 11-12. A resistor, R_1 , is in series with the load. The operation of the circuit is similar to that of the series regulator, except that regulation is achieved by controlling the current through the parallel transistor Q_1 .

 
 
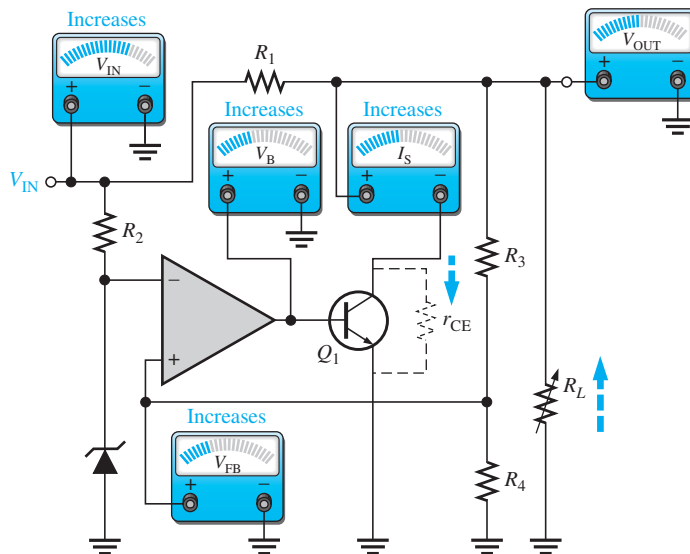


FIGURE 11-12 Basic op-amp shunt regulator.

When the output voltage tries to decrease due to a change in input voltage or load current caused by a change in load resistance, as shown in Figure 11-13(a), the attempted decrease is sensed by R_3 and R_4 and is applied to the op-amp's noninverting input. The resulting difference voltage reduces the op-amp's output (V_B), driving Q_1 less, thus reducing its collector current (shunt current) and increasing its internal collector-to-emitter


 (a) Response to a decrease in V_{IN} or R_L

 (b) Response to an increase in V_{IN} or R_L
FIGURE 11-13 Sequence of responses when V_{OUT} tries to decrease as a result of a decrease in R_L or V_{IN} (opposite responses for an attempted increase).

resistance r_{CE} . Since r_{CE} acts as a voltage divider with R_1 , this action offsets the attempted decrease in V_{OUT} and maintains it at an almost constant level.

The opposite action occurs when the output tries to increase, as indicated in Figure 11-13(b). With I_L and V_{OUT} constant, a change in the input voltage produces a change in shunt current (I_S) as follows:

$$\Delta I_S = \frac{\Delta V_{IN}}{R_1}$$

With a constant V_{IN} and V_{OUT} , a change in load current causes an opposite change in shunt current.

$$\Delta I_S = -\Delta I_L$$

This formula says that if I_L increases, I_S decreases, and vice versa. The shunt regulator is less efficient than the series type but offers inherent short-circuit protection. If the output is

shorted ($V_{OUT} = 0$), the load current is limited by the series resistor R_1 to a maximum value as follows ($I_S = 0$).

$$I_{L(\max)} = \frac{V_{IN}}{R_1} \quad (11-7)$$

EXAMPLE 11-5

In Figure 11-14, what power rating must R_1 have if the maximum input voltage is 12.5 V?

 


FIGURE 11-14

SOLUTION

The worst-case power dissipation in R_1 occurs when the output is short-circuited. $V_{OUT} = 0$, and when $V_{IN} = 12.5$ V, the voltage dropped across R_1 is $V_{IN} - V_{OUT} = 12.5$ V. The power dissipation in R_1 is

$$P_{R1} = \frac{V_{R1}^2}{R_1} = \frac{(12.5 \text{ V})^2}{22 \Omega} = 7.1 \text{ W}$$

Therefore, a resistor with at least a **10 W** rating should be used.

PRACTICE EXERCISE

In Figure 11-14, R_1 is changed to 33Ω . What must be the power rating of R_1 if the maximum input voltage is 24 V?

MULTISIM



Open file F11-14 found on the companion website. This simulation demonstrates the load regulation of the shunt regulator.

SECTION 11-3 CHECKUP

- How does the control element in a shunt regulator differ from that in a series regulator?
- What is one advantage of a shunt regulator over a series type? What is a disadvantage?

11–4 BASIC SWITCHING REGULATORS

The two types of linear regulators—series and shunt—have control elements (transistors) that are conducting all the time, with the amount of conduction varied as demanded by changes in the output voltage or current. The switching regulator is different; the control element operates as a switch.

After completing this section, you should be able to

- Discuss the principles of switching regulators
 - Describe the step-down configuration of a switching regulator
 - Determine the output voltage of the step-down configuration
 - Describe the step-up configuration of a switching regulator
 - Determine the output voltage of the step-up configuration
 - Describe the voltage-inverter configuration
-


A much greater efficiency can be realized with a switching type of voltage regulator than with linear types because, as the transistor switches on and off, it dissipates power only when it is on. In a linear regulator, the transistor is always on and constantly dissipates power because the transistor looks like a variable resistor. This causes heat to be generated and wastes power. In a **switching regulator**, the transistor operates only on the ends of the load line, except during the very short switching time, so its resistance is either very high (cutoff) or very low (saturated). As a result, efficiencies can be greater than 90%. Switching regulators are particularly useful where efficiency is important, such as for computers or tablets. An efficient regulator avoids excessive heat, which can destroy electronic components, and increases battery life.

Switching regulators are designed for various power levels. They range in power levels from less than one watt for some battery-operated portable equipment to hundreds and thousands of watts in high-power applications. The requirements for the application determine the particular design, but all switching regulators require feedback to control the on-off time for the switch. Three basic configurations of switching regulators are step-down, step-up, and inverting. In some cases, such as a laptop computer, all three types may be employed for various parts of the system; for example, the display typically will use an inverting type, the microprocessor may use a step-down type, and the disk drive may use a step-up type.


Step-Down Configuration

In the step-down configuration (also called a buck converter), the output voltage is always less than the input voltage. A basic step-down switching regulator is shown in Figure 11–15(a), and its simplified equivalent is shown in Figure 11–15(b). Transistor Q_1 is used to switch the input voltage at a duty cycle that is based on the regulator's load requirement. MOSFET transistors can switch faster than BJTs, so they have become the preferred type of switching device, assuming that the off-state voltage is not too high. Depending on the application, BJTs are still used, and in some cases thyristors (covered in Chapter 15) are used as the switching device. The LC filter is then used to average the switched voltage. Since Q_1 is either *on* (saturated) or *off*, the power lost in the control element is relatively small. Therefore, the switching regulator is useful primarily in higher power applications or in applications such as computers where efficiency is of utmost concern.

The on and off intervals of Q_1 are shown in the waveform of Figure 11–16(a). The capacitor charges during the on-time (t_{on}) and discharges during the off-time (t_{off}). When the on-time is increased relative to the off-time, the capacitor charges more, thus increasing the output voltage, as indicated in Figure 11–16(b). When the on-time is decreased relative to the off-time, the capacitor discharges more, thus decreasing the output voltage, as in Figure 11–16(c). Therefore, by adjusting the duty cycle, $t_{on}/(t_{on} + t_{off})$, of Q_1 , the output voltage can be varied. The inductor further smooths the fluctuations of the output voltage caused by the charging and discharging action.

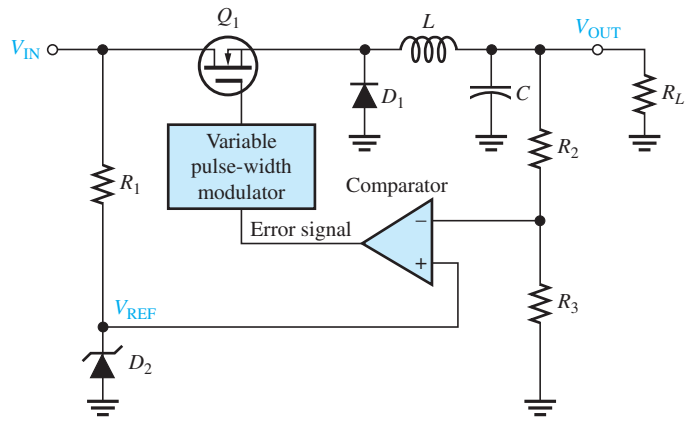


(a) Typical circuit

 


(b) Simplified equivalent circuit


FIGURE 11-15 Basic step-down switching regulator.

 

(a) V_{OUT} depends on the duty cycle.

 

 (b) Increase the duty cycle and V_{OUT} increases.



(c) Decrease the duty cycle and V_{OUT} decreases.

FIGURE 11-16 Switching regulator waveforms. The V_C waveform is shown for no inductive filtering to illustrate the charge and discharge action (ripple). L and C smooth V_C to a nearly constant level, as indicated by the dashed line for V_{OUT} .

Ideally, the output voltage is expressed as


$$V_{\text{OUT}} = \left(\frac{t_{\text{on}}}{T} \right) V_{\text{IN}} \quad (11-8)$$

T is the period of the on-off cycle of Q_1 and is related to the frequency by $T = 1/f$. The period is the sum of the on-time and the off-time.


$$T = t_{\text{on}} + t_{\text{off}}$$

The ratio t_{on}/T is called the *duty cycle*.

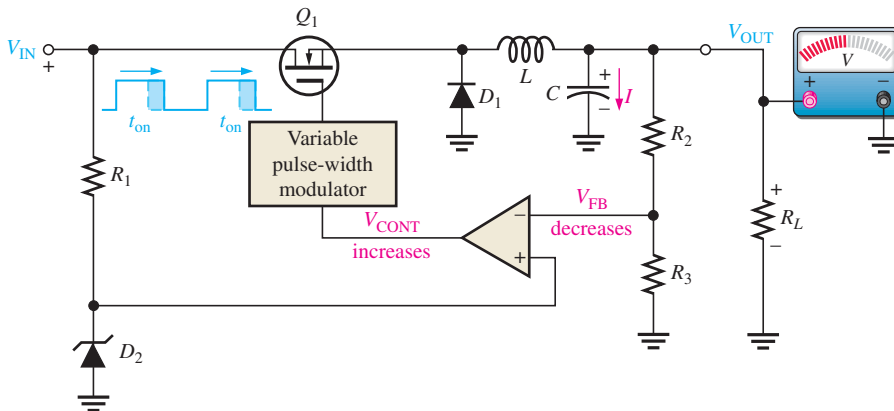The regulating action is as follows and is illustrated in Figure 11-17. When V_{OUT} tries to decrease, the on-time of Q_1 is increased, causing an additional charge on the capacitor, C , to offset the attempted decrease. When V_{OUT} tries to increase, the on-time of Q_1 is decreased, causing C to discharge enough to offset the attempted increase.



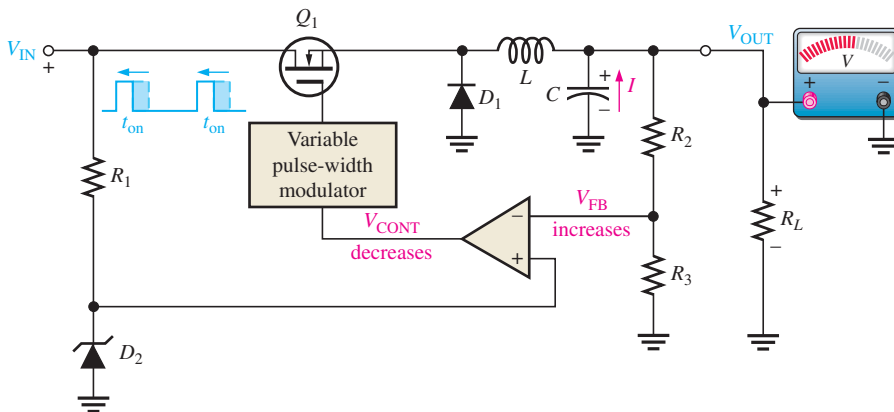(a) When V_{OUT} attempts to decrease, the on-time of Q_1 increases.



(b) When V_{OUT} attempts to increase, the on-time of Q_1 decreases.

FIGURE 11-17 Basic regulating action of a step-down switching regulator.

Step-Up Configuration

A basic step-up type of switching regulator (sometimes called a boost converter) is shown in Figure 11-18, where transistor Q_1 operates as a switch to ground.

The switching action is illustrated in Figures 11-19 and 11-20. When Q_1 turns on, a voltage equal to approximately V_{IN} is induced across the inductor with a polarity as indicated in Figure 11-19. During the on-time (t_{on}) of Q_1 , the inductor voltage, V_L , decreases

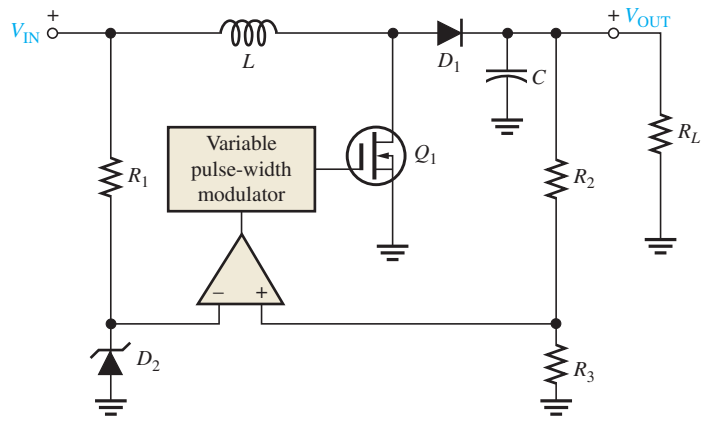


FIGURE 11-18 Basic step-up switching regulator.

 


FIGURE 11-19 Basic action of a step-up regulator when Q_1 is on.

 


FIGURE 11-20 Basic switching action of a step-up regulator when Q_1 turns off.

from its initial maximum and diode D_1 is reverse-biased. The longer Q_1 is on, the smaller V_L becomes. During the on-time, the capacitor only discharges an extremely small amount through the load.

When Q_1 turns off, as indicated in Figure 11-20, the inductor voltage suddenly reverses polarity and adds to V_{IN} , forward-biasing diode D_1 and allowing the capacitor to charge. The output voltage is equal to the capacitor voltage and can be larger than V_{IN} because the capacitor is charged to V_{IN} plus the voltage induced across the inductor during the off-time of Q_1 .

The longer the on-time of Q_1 , the more the inductor voltage will decrease and the greater the magnitude of the voltage when the inductor reverses polarity at the instant Q_1 turns off. As you have seen, this reverse polarity voltage is what charges the capacitor above V_{IN} . The output voltage is dependent on both the inductor's magnetic field action (determined by t_{on}) and the charging of the capacitor (determined by t_{off}).

Voltage regulation is achieved by the variation of the on-time of Q_1 (within certain limits) as related to changes in V_{OUT} due to changing load or input voltage. If V_{OUT} tries to increase, the on-time of Q_1 will decrease, which results in a decrease in the amount that C will charge. If V_{OUT} tries to decrease, the on-time of Q_1 will increase, which results in an increase in the amount that C will charge. This regulating action maintains V_{OUT} at an essentially constant level.

Voltage-Inverter Configuration

A third type of switching regulator produces an output voltage that is opposite in polarity to the input. A basic diagram is shown in Figure 11-21. This circuit is sometimes called a buck-boost converter.


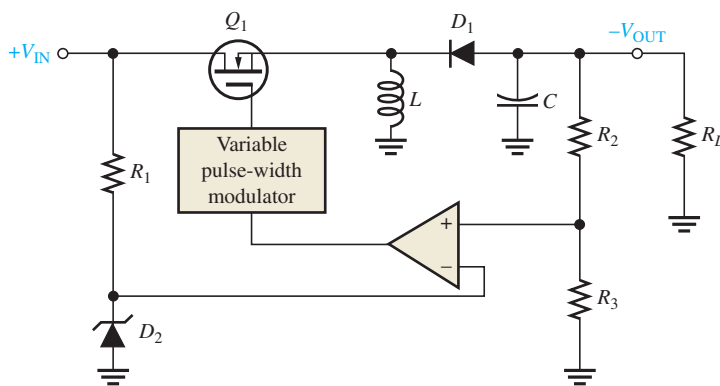


FIGURE 11-21 Basic inverting switching regulator.


When Q_1 turns on, the inductor voltage jumps to approximately V_{IN} and the magnetic field rapidly expands, as shown in Figure 11-22(a). While Q_1 is on, the diode is reverse-biased and the inductor voltage decreases from its initial maximum. When Q_1 turns off, the magnetic field collapses and the inductor's polarity reverses, as shown in Figure 11-22(b). This forward-biases the diode, charges C , and produces a negative output voltage, as indicated. The repetitive on-off action of Q_1 produces a repetitive charging and discharging that is smoothed by the LC filter action.

As with the step-up regulator, the less time Q_1 is on, the greater the output voltage is, and vice versa. This regulating action is illustrated in Figure 11-23. As stated earlier, switching regulator efficiencies can be greater than 90 percent.

FIGURE 11-22 Basic inverting action of an inverting switching regulator.

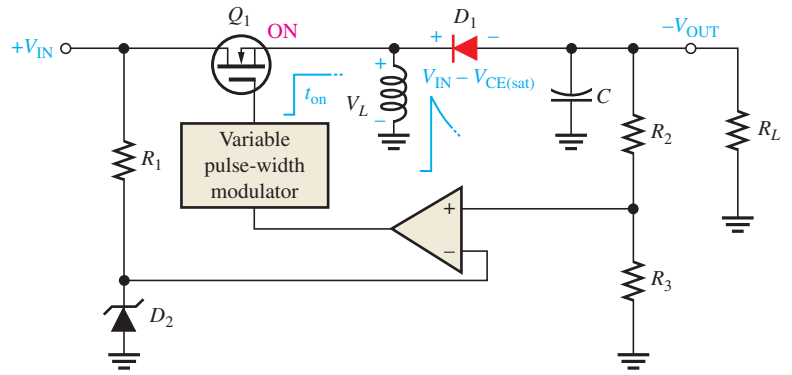


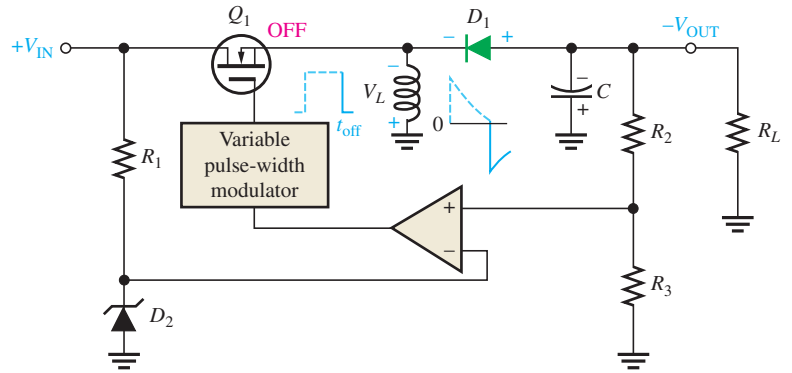(a) When Q_1 is on, D_1 is reverse-biased.




(b) When Q_1 turns off, D_1 forward biases.

FIGURE 11-23 Basic regulating action of an inverting switching regulator.

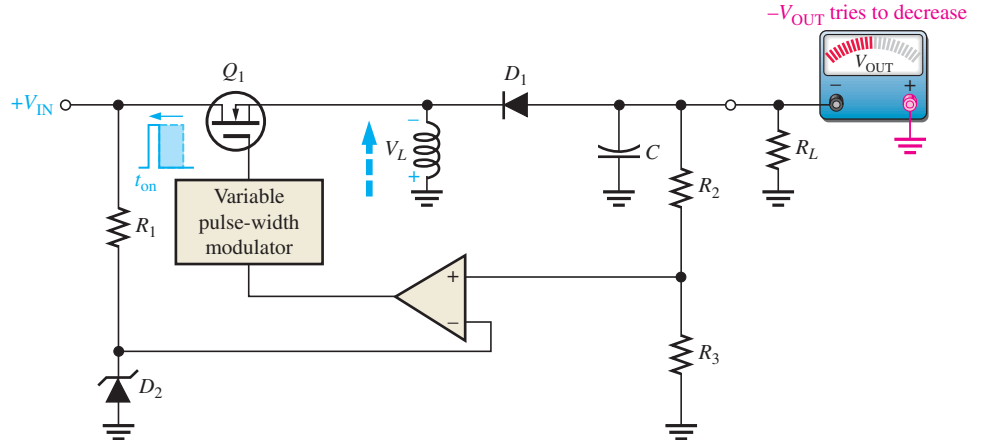

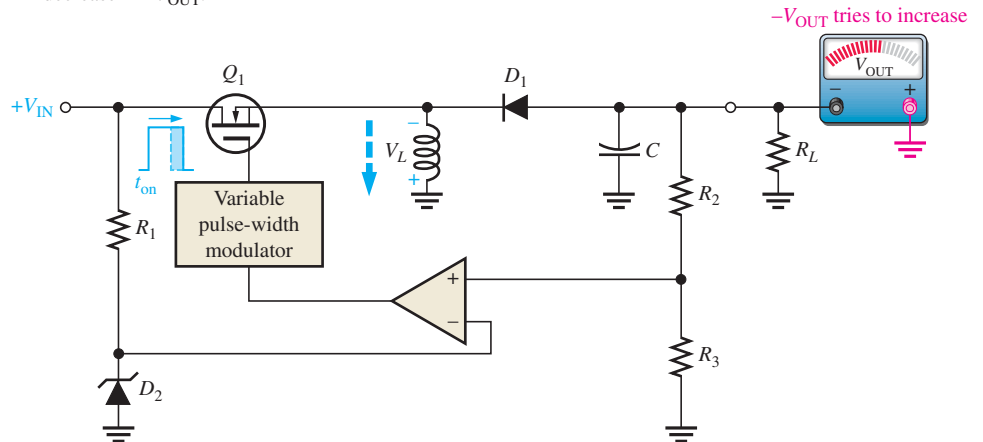(a) When $-V_{OUT}$ tries to decrease, t_{on} decreases, causing V_L to increase. This compensates for the attempted decrease in $-V_{OUT}$.



(b) When $-V_{OUT}$ tries to increase, t_{on} increases, causing V_L to decrease. This compensates for the attempted increase in $-V_{OUT}$.

SECTION 11-4 CHECKUP

1. What are three types of switching regulators?
2. What is the primary reason switching regulators are used in computer systems?
3. How are changes in output voltage compensated for in the switching regulator?

11-5 INTEGRATED CIRCUIT VOLTAGE REGULATORS

In the previous sections, the basic voltage regulator configurations were presented. Several types of both linear and switching regulators are available in integrated circuit (IC) form. Generally, the linear regulators are three-terminal devices that provide either positive or negative output voltages that can be either fixed or adjustable. Three-terminal regulators were introduced in Section 2-6. In this section, typical linear and switching IC regulators are covered in more detail.

After completing this section, you should be able to

- Discuss integrated circuit voltage regulators
 - Describe the 7800 series of positive regulators
 - Describe the 7900 series of negative regulators
 - Describe the LM317 adjustable positive regulator
 - Describe the LM337 adjustable negative regulator
 - Describe IC switching regulators

Fixed Positive Linear Voltage Regulators

Although many types of IC regulators are available, the 7800 series of IC regulators is representative of three-terminal devices that provide a fixed positive output voltage. The three terminals are input, output, and ground as indicated in the standard fixed voltage configuration in Figure 11-24(a). The last two digits in the part number designate the output voltage. For example, the 7805 is a +5.0 V regulator. Other available output voltages are given in Figure 11-24(b). (Common IC regulator packages were shown in Figure 2-26(c).)

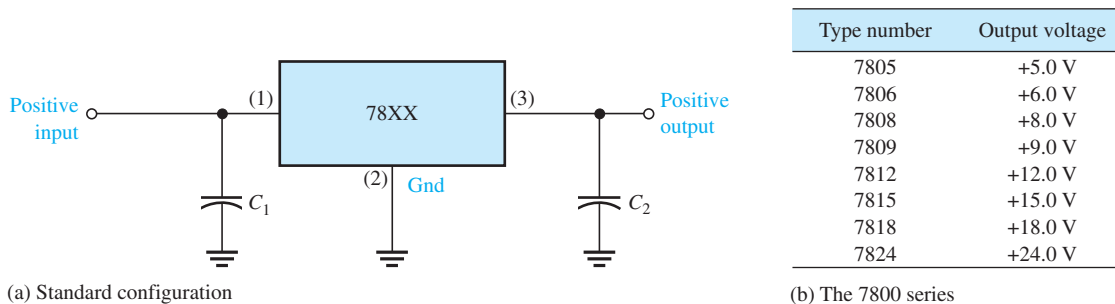


FIGURE 11-24 The 7800 series three-terminal fixed positive voltage regulators.

Capacitors are used on the input and output as indicated. The output capacitor acts basically as a line filter to improve transient response. The input capacitor is used to prevent unwanted oscillations when the regulator is some distance from the power supply filter such that the line has a significant inductance.


The 7800 series can produce output currents up to in excess of 1 A when used with an adequate heat sink. The input voltage must be at least 2 V above the output voltage in order to maintain regulation. The circuits have internal thermal overload protection and short-circuit current-limiting features.

Thermal overload occurs when the internal power dissipation becomes excessive and the temperature of the device exceeds a certain value. Thermal overload is a problem if inadequate heat sinking is provided or if the regulator is not properly secured to the heat sink. Almost all applications of regulators require a heat sink. Heat generated by the regulator must move to the heat sink and then to the surrounding air. A good heat sink is massive and has fins (to increase area). A regulator that is too hot may show symptoms of drift, excess ripple, or the output may fall out of regulation. The spec sheets for the 78XX series can be found at www.onsemi.com.

Voltage regulators have a specification called the dropout voltage. The dropout voltage of a regulator is the difference between the input voltage and the output voltage at which the device can no longer maintain voltage regulation. For example, 78XX and 79XX voltage regulator ICs have a dropout voltage rating of 2 V. This means that for a 7812, if the input voltage drops below 14 V, voltage regulation is lost. Regulation is usually assumed to be lost when the output voltage drops 100 mV below its rated value.

With the increase in the number of portable devices, such as laptops and tablets, this can present a problem. For example, a lithium ion battery has an output voltage of 4.2 V when fully charged, but drops to about 2.7 V when almost discharged. This concern has led to the development of low-dropout regulators.

Low-dropout (LDO) regulators maintain regulation with much lower input-to-output voltage differentials, usually between 100 mV and 200 mV. One example is the ADP1710/ADP1711 series of CMOS linear regulators from Analog Devices. Both devices are available in 16 fixed output voltage options, and the 1710 is available in an adjustable version (0.8 V to 5 V) as well. Each of these devices has a dropout rating of 150 mV at 150 mA load current. Their spec sheets can be found at www.analog.com.

 

SYSTEM NOTE

Fixed Negative Linear Voltage Regulators

The 7900 series is typical of three-terminal IC regulators that provide a fixed negative output voltage. This series is the negative-voltage counterpart of the 7800 series and shares most of the same features and characteristics. Figure 11–25 indicates the standard configuration and part numbers with corresponding output voltages that are available. Be aware that the pins on the 7900 series regulators do not have the same function as the 7800 series pins. The spec sheets for the 79XX series can be found at www.onsemi.com.

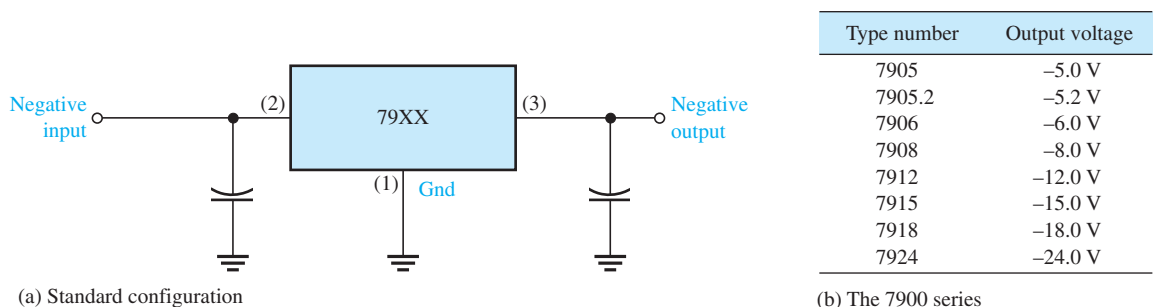


FIGURE 11–25 The 7900 series three-terminal fixed negative voltage regulators.

Adjustable Positive Linear Voltage Regulators

The LM317 is an example of a three-terminal positive regulator with an adjustable output voltage. A data sheet for this device is given in Appendix A. The standard configuration is shown in Figure 11-26. Input and output capacitors, C_1 and C_3 , respectively, are used for the reasons discussed previously. The capacitor, C_2 , at the adjustment terminal also acts as a filter to improve transient response. Notice that there is an input, an output, and an adjustment terminal. The external fixed resistor, R_1 , and the external variable resistor, R_2 , provide the output voltage adjustment. V_{OUT} can be varied from 1.2 V to 37 V depending on the resistor values. The LM317 can provide over 1.5 A of output current to a load.

 


FIGURE 11-26 The LM317 three-terminal adjustable positive voltage regulator.

The LM317 is operated as a “floating” regulator because the adjustment terminal is not connected to dc ground but floats to whatever voltage is across R_2 . This allows the output voltage to be much higher than that of a fixed-voltage regulator.

BASIC OPERATION As indicated in Figure 11-27, a constant 1.25 V reference voltage (V_{REF}) is maintained by the regulator between the output terminal and the adjustment terminal. This constant reference voltage produces a constant current (I_{REF}) through R_1 , regardless of the value of R_2 . I_{REF} is also through R_2 .

$$I_{REF} = \frac{V_{REF}}{R_1} = \frac{1.25 \text{ V}}{R_1}$$

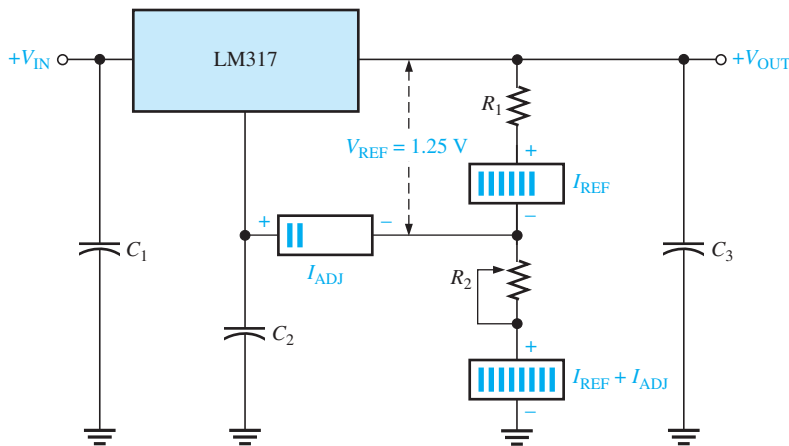


FIGURE 11-27 Operation of the LM317 adjustable voltage regulator.

In addition, there is a very small constant current into the adjustment terminal of approximately $50 \mu\text{A}$ called I_{ADJ} , which is through R_2 . A formula for the output voltage is as follows:

$$V_{OUT} = V_{REF} \left(1 + \frac{R_2}{R_1} \right) + I_{ADJ} R_2 \quad (11-9)$$

MULTISIM




Open file F11-27 found on the companion website. This simulation demonstrates the operation of an adjustable voltage regulator.

As you can see, the output voltage is a function of both R_1 and R_2 . Once the value of R_1 is set, the output voltage is adjusted by varying R_2 .

EXAMPLE 11-6

Determine the minimum and maximum output voltages for the voltage regulator in Figure 11-28. Assume $I_{\text{ADJ}} = 50 \mu\text{A}$.

FIGURE 11-28

 

SOLUTION

$$V_{R1} = V_{\text{REF}} = 1.25 \text{ V}$$

When R_2 is set at its minimum of 0Ω ,

$$V_{\text{OUT}(\text{min})} = V_{\text{REF}} \left(1 + \frac{R_2}{R_1} \right) + I_{\text{ADJ}} R_2 = 1.25 \text{ V}(1) = \mathbf{1.25 \text{ V}}$$

When R_2 is set at its maximum of $5.0 \text{ k}\Omega$,

$$\begin{aligned} V_{\text{OUT}(\text{max})} &= V_{\text{REF}} \left(1 + \frac{R_2}{R_1} \right) + I_{\text{ADJ}} R_2 = 1.25 \text{ V} \left(1 + \frac{5.0 \text{ k}\Omega}{220 \Omega} \right) + (50 \mu\text{A}) 5.0 \text{ k}\Omega \\ &= 29.66 \text{ V} + 0.25 \text{ V} = \mathbf{29.9 \text{ V}} \end{aligned}$$

PRACTICE EXERCISE

What is the output voltage of the regulator if R_2 is set at $2.0 \text{ k}\Omega$?

Adjustable Negative Linear Voltage Regulators

The LM337 is the negative output counterpart of the LM317 and is a good example of this type of IC regulator. Like the LM317, the LM337 requires two external resistors for output voltage adjustment as shown in Figure 11-29. The output voltage can be adjusted from -1.2 V to -37 V , depending on the external resistor values. The spec sheets for the LM317 and LM337 can be found at www.national.com.


 


FIGURE 11-29 The LM337 three-terminal adjustable negative voltage regulator.

Most standard adjustable regulators are designed to work from relatively low input voltages. For example, the maximum input-output voltage differential for the LM117 and LM317 is 40 V. In some systems it is more practical to work with input voltages that are much higher. It is for these types of applications that high-voltage linear regulators have been developed.

The LR8 and LR12 three-terminal ICs are two examples of high-voltage regulators. Both these regulators are designed to work directly off the rectified ac mains of a system. The LR8 can accept input voltages up to 450 V and still provide a regulated output voltage as low as 12 V. This device is compatible with rectified 120 V or 240 V line voltages. The LR12 has a maximum input voltage rating of 100 V for a 12 V output, making it compatible with 48 V telecom line voltages. Both devices can provide regulated outputs as low as 1.2 V with lower input voltages. The output voltage is set by a voltage divider between the output and the adjust input, just like for the LM117/LM317. Both devices require a minimum 12 V input-to-output voltage differential and 500 μA of output current for proper operation. The spec sheet for these devices can be found at www.supertex.com.

SYSTEM NOTE

 

Troubleshooting Three-Terminal Regulators

Three-terminal regulators are very reliable devices. When problems occur, the indication is usually an incorrect voltage, high ripple, noisy or oscillating output, or drift. Troubleshooting a regulator circuit is best done with an oscilloscope as problems such as excessive ripple or noise won't show up using a DMM. Before starting, it is useful to review the possible causes of a failure (analysis) and plan measurements that will point to the failure.

If the output voltage is too low, the input voltage should be checked; the problem may be in the circuit preceding the regulator. Also check the load resistor: Does the problem go away when the load is removed? If so, it may be that the load draws too much current. A high output can occur with adjustable regulators if the feedback resistors are the wrong value or open. If there is ripple or noise on the output, check the capacitors for an open, for a wrong value, or whether they are installed with the proper polarity. A useful quick check of a capacitor is to place another capacitor of the same or larger size in parallel with the capacitor to be tested. If the output is oscillating, has high ripple, or is drifting, check that the regulator is not too hot or supplying more than its rated current. If heat is a problem, make sure the regulator is firmly secured to the heat sink.

Switching Voltage Regulators

As an example of an IC switching voltage regulator, let's look at the LM78S40. This is a universal device that can be used with external components to provide step-up, step-down, and inverting operation.

The internal circuitry of the 78S40 is shown in Figure 11-30. This circuit can be compared to the basic switching regulators that were covered in Section 11-4. For example, look back at Figure 11-15(a). The oscillator and comparator functions are directly comparable. The gate and flip-flop, which are digital devices, were not included in the basic circuit of Figure 11-15(a), but they provide additional regulating action. Transistors Q_1 and Q_2 effectively perform the same function as Q_1 in the basic circuit. The 1.25 V reference block in the 78S40 has the same purpose as the zener diode in the basic circuit, and diode D_1 in the 78S40 corresponds to D_1 in the basic circuit.

The 78S40 also has an "uncommitted" op-amp thrown in for good measure. It is not used in any of the regulator configurations. External circuitry is required to make this device operate as a regulator, as you will see in Section 11-6. The spec sheet for the LM78S40 can be found at www.national.com.


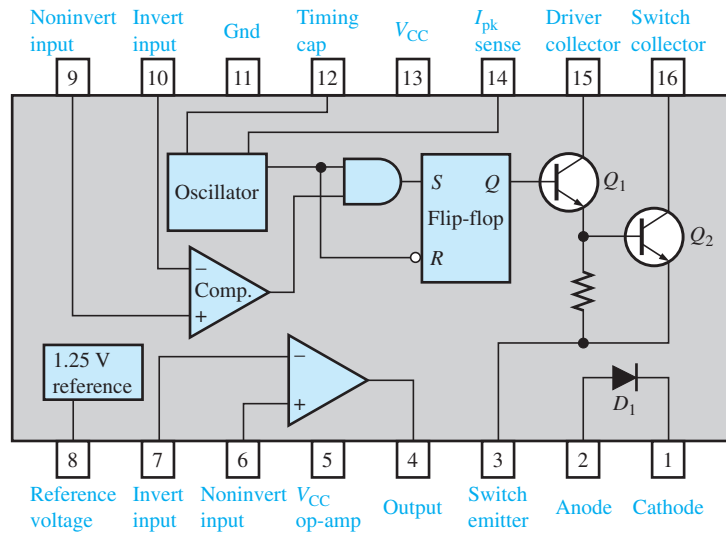


FIGURE 11-30 The 78S40 switching regulator.

SYSTEM EXAMPLE 11-1

 

A WIND TURBINE

A wind turbine is a transducer. It first converts the wind's kinetic energy into mechanical energy by forcing the rotor blades to turn. This mechanical energy is then used to rotate the armature of an ac generator (alternator) converting mechanical energy into electrical energy.

Wind velocity is constantly changing. This means that both the frequency and the amplitude of the turbine generator output are also constantly changing. For this reason the varying generator output is first converted into a varying dc voltage. Then a voltage regulator, similar to those covered in this chapter, is used to produce a constant dc voltage. Finally the regulated dc voltage is converted back into an ac voltage with a constant amplitude and frequency. Without the voltage regulator, this would not be possible.

Wind Turbine Basics

Three key elements in a wind turbine are the rotor blades, the ac generator, and the ac-to-dc converter. The converter contains a rectifier circuit and a voltage regulator. In many wind turbines, electronic circuits sense the wind direction and speed and adjust the orientation and pitch of the blades to maximize the energy collected from the wind. The generator produces a varying ac voltage that depends on the rotational speed of the blades. Since the frequency and amplitude of the generator output varies with wind speed, the ac output is converted to dc and then back to 60 Hz ac with an inverter. Like a solar power system, the energy can be stored in batteries using a charge controller.

Figure SE11-1 shows a basic diagram of a horizontal-axis wind turbine (HAWT) for small power applications, such as home use. Note that the voltage regulator is part of the ac-to-dc converter block. A typical wind turbine has three blades and is mounted on a very high support tower. Wind energy is converted to mechanical energy by the rotating blades. As shown in Figure SE11-1, the blade rotation is applied to a shaft, which is geared up to turn the ac generator shaft at a higher rate than the blades are rotating. The generator rotation produces an ac voltage output with a frequency that depends on the rate of rotation. Since it is a variable frequency and amplitude output, as previously mentioned, the ac is converted to dc by the ac-to-dc converter. The dc is sent to a charge controller that charges storage batteries. The battery output is applied to an inverter where it is converted to a 120 V, 60 Hz ac voltage for individual consumer use. The wind vane and yaw bearing assembly are used on small turbines to keep the blades pointed into the wind. An anemometer senses the

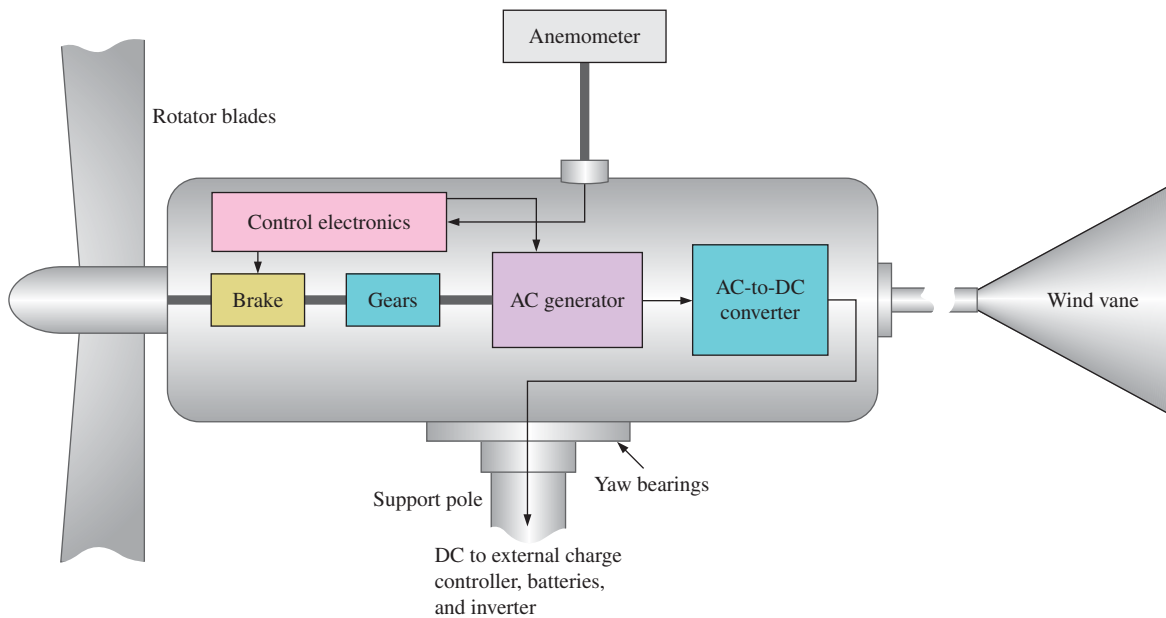


FIGURE SE11-1 Basic small HAWT system operation.

wind speed in order to brake the blades when the wind reaches a specified speed. This prevents mechanical damage if the wind speed is too high.

The AC-to-DC Converter

Because of the variable frequency of the ac from the generator, it must first be converted to dc for the charge controller. A rectifier and voltage regulator are used for the conversion, as illustrated in Figure SE11-2. The ac voltage from the generator varies in amplitude and frequency as a function of wind speed. The filtered rectifier changes the varying ac to a varying dc voltage, which is then applied to a voltage regulator to produce a specified constant dc voltage, as shown. The constant dc output from the regulator allows the external inverter to produce an ac voltage with a stable amplitude and frequency.

 


FIGURE SE11-2 AC-to-DC converter block diagram.

SECTION 11-5 CHECKUP

1. What are the three terminals of a fixed-voltage regulator?
2. What is the output voltage of a 7809? Of a 7915?
3. What are the three terminals of an adjustable-voltage regulator?
4. What external components are required for a basic LM317 configuration?

11-6 APPLICATIONS OF IC VOLTAGE REGULATORS

REGULATORS

In the last section, you saw several devices that are representative of the general types of IC voltage regulators. Now, several different ways these devices can be modified with external circuitry to improve or alter their performance are examined.

After completing this section, you should be able to

- Discuss applications of IC voltage regulators
 - Explain the use of an external pass transistor
 - Explain the use of current limiting
 - Explain how to use a voltage regulator as a constant-current source
 - Discuss some application considerations for switching regulators

The External Pass Transistor

As you know, an IC voltage regulator is capable of delivering only a certain amount of output current to a load. For example, the 7800 series regulators can handle a peak output current of 1.3 A (more under certain conditions). If the load current exceeds the maximum allowable value, there will be thermal overload and the regulator will shut down. A thermal overload condition means that there is excessive power dissipation inside the device.

If an application requires more than the maximum current that the regulator can deliver, an external pass transistor can be used. Figure 11-31 illustrates a three-terminal regulator with an external pass transistor for handling currents in excess of the output current capability of the basic regulator.


 


FIGURE 11-31 A 7800-series three-terminal regulator with an external pass transistor.


The value of the external current-sensing resistor R_{ext} determines the value of current at which Q_{ext} begins to conduct because it sets the base-to-emitter voltage of the transistor. As long as the current is less than the value set by R_{ext} , the transistor Q_{ext} is off, and the regulator operates normally as shown in Figure 11-32(a). This is because the voltage drop across R_{ext} is less than the 0.7 V base-to-emitter voltage required to turn Q_{ext} on. R_{ext} is determined by the following formula, where I_{max} is the highest current that the voltage regulator is to handle internally.

$$R_{\text{ext}} = \frac{0.7 \text{ V}}{I_{\text{max}}}$$

When the current is sufficient to produce at least a 0.7 V drop across R_{ext} , the external pass transistor Q_{ext} turns on and conducts any current in excess of I_{max} , as indicated in Figure 11-32(b). Q_{ext} will conduct more or less, depending on the load requirements. For example, if the total load current is 3 A and I_{max} was selected to be 1 A, the external pass transistor will conduct 2 A, which is the excess over the internal regulator current I_{max} .

 

 (a) When the regulator current is less than I_{max} , the external pass transistor is off and the regulator is handling all of the current.



(b) When the load current exceeds I_{max} , the drop across R_{ext} turns Q_{ext} on and the transistor conducts the excess current.

FIGURE 11-32 Operation of the regulator with an external pass transistor.

EXAMPLE 11-7

What value is R_{ext} if the maximum current to be handled internally by the voltage regulator in Figure 11-31 is set at 700 mA?

SOLUTION

$$R_{\text{ext}} = \frac{0.7\text{ V}}{I_{\text{max}}} = \frac{0.7\text{ V}}{0.7\text{ A}} = 1\ \Omega$$

PRACTICE EXERCISE

If R_{ext} is changed to $1.5\ \Omega$, at what current value will Q_{ext} turn on?

The external pass transistor is typically a power transistor with heat sink that must be capable of handling a maximum power of

$$P_{\text{ext}} = I_{\text{ext}}(V_{\text{IN}} - V_{\text{OUT}})$$

EXAMPLE 11-8

What must be the minimum power rating for the external pass transistor used with a 7824 regulator in a circuit such as that shown in Figure 11-31? The input voltage is 30 V and the load resistance is $10\ \Omega$. The maximum internal current is to be 700 mA. Assume that there is no heat sink for this calculation. Keep in mind that the use of a heat sink increases the effective power rating of the transistor and you can use a lower-rated transistor.

SOLUTION

The load current is

$$I_L = \frac{V_{\text{OUT}}}{R_L} = \frac{24 \text{ V}}{10 \Omega} = 2.4 \text{ A}$$

The current through Q_{ext} is

$$I_{\text{ext}} = I_L - I_{\text{max}} = 2.4 \text{ A} - 0.7 \text{ A} = 1.7 \text{ A}$$

The power dissipated by Q_{ext} is

$$P_{\text{ext}(\text{min})} = I_{\text{ext}}(V_{\text{IN}} - V_{\text{OUT}}) = 1.7 \text{ A}(30 \text{ V} - 24 \text{ V}) = 1.7 \text{ A}(6 \text{ V}) = \mathbf{10.2 \text{ W}}$$

For a safety margin, choose a power transistor with a rating greater than 10.2 W, say, at least 15 W.

PRACTICE EXERCISE

Rework this example using a 7815 regulator.

Current Limiting

A drawback of the circuit in Figure 11–31 is that the external transistor is not protected from excessive current, such as would result from a shorted output. An additional current-limiting network (Q_{lim} and R_{lim}) can be added as shown in Figure 11–33 to protect Q_{ext} from excessive current and possible burnout.


 



FIGURE 11–33 Regulator with current limiting.

The following describes the way the current-limiting network works. The current-sensing resistor R_{lim} sets the V_{BE} of transistor Q_{lim} . The base-to-emitter voltage of Q_{ext} is now determined by $V_{R_{\text{ext}}} - V_{R_{\text{lim}}}$ because they have opposite polarities. So, for normal operation, the drop across R_{ext} must be sufficient to overcome the opposing drop across R_{lim} . If the current through Q_{ext} exceeds a certain maximum ($I_{\text{ext}(\text{max})}$) because of a shorted output or a faulty load, the voltage across R_{lim} reaches 0.7 V and turns Q_{lim} on. Q_{lim} now conducts current away from Q_{ext} and through the regulator, forcing a thermal overload to occur and shut down the regulator. Remember, the IC regulator is internally protected from thermal overload as part of its design.

This action is shown in Figure 11–34. In part (a), the circuit is operating normally with Q_{ext} conducting less than the maximum current that it can handle with Q_{lim} off. Part (b) shows what happens when there is a short across the load. The current through Q_{ext} suddenly increases and causes the voltage drop across R_{lim} to increase, which turns Q_{lim} on. The current is now diverted through the regulator, which causes it to shut down due to thermal overload.

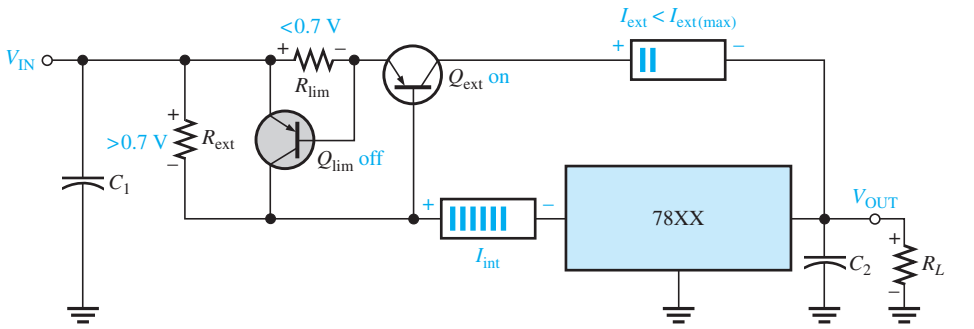

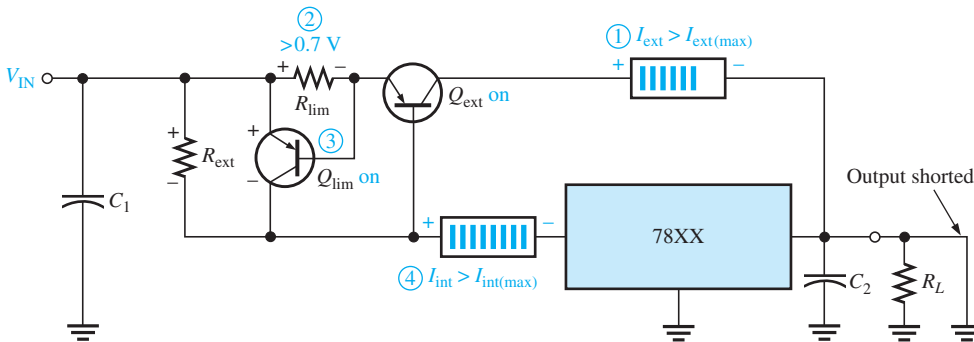(a) During normal operation, when the load current is not excessive, Q_{lim} is off.



(b) When a short occurs ①, the external current becomes excessive and the voltage across R_{lim} increases ② and turns on Q_{lim} ③, which then conducts current away from Q_{ext} and routes it through the regulator, causing the internal regulator current to become excessive ④ and to force the regulator into thermal shut down.

FIGURE 11-34 The current-limiting action of the regulator circuit.

A Current Regulator

The three-terminal regulator can be used as a current source when an application requires that a constant current be supplied to a variable load. The basic circuit is shown in Figure 11-35 where R_1 is the current-setting resistor. The regulator provides a fixed constant voltage, V_{OUT} , between the ground terminal (not connected to ground in this case) and the output terminal. This determines the constant current supplied to the load.

$$I_L = \frac{V_{OUT}}{R_1} + I_G$$

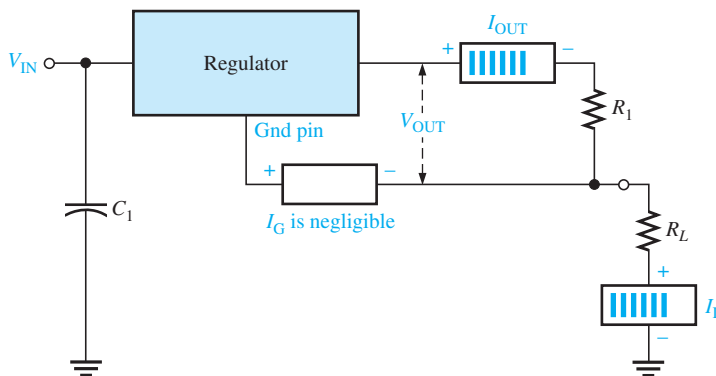


FIGURE 11-35 The three-terminal regulator as a current source.

The current, I_G , from the ground terminal is very small compared to the output current and can often be neglected.

EXAMPLE 11-9

What value of R_1 is necessary in a 7805 regulator to provide a constant current of 1 A to a variable load that can be adjusted from 0–10 Ω ?

SOLUTION

First, 1 A is within the limits of the 7805's capability (remember, it can handle at least 1.3 A without an external pass transistor).

The 7805 produces 5 V between its ground terminal and its output terminal. Therefore, if you want 1 A of current, the current-setting resistor must be (neglecting I_G)

$$R_1 = \frac{V_{\text{OUT}}}{I_L} = \frac{5 \text{ V}}{1 \text{ A}} = 5.0 \Omega$$

The circuit is shown in Figure 11-36.

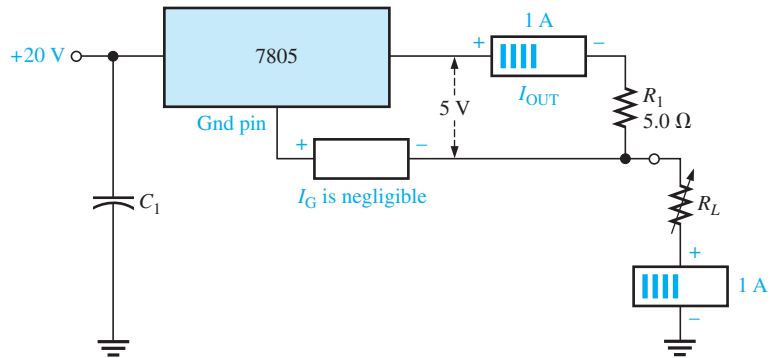


FIGURE 11-36 A 1 A constant-current source.

PRACTICE EXERCISE

If a 7808 regulator is used instead of the 7805, to what value would you change R_1 to maintain a constant current of 1 A?

SYSTEM EXAMPLE 11-2**A VARIABLE DUAL-POLARITY POWER SUPPLY**

In this system example a variable dual-polarity power supply is discussed. Rather than use a variable regulator like the LM117, the same type of fixed-value regulator that was used in System Example 2-2 will be employed, but configured so that can function as a variable regulator.

The Circuit

Refer to the schematic shown in Figure SE11-3. This circuit is designed to produce output voltages of $\pm 12 \text{ V}$ to $\pm 30 \text{ V}$, from a standard 120 V/60 Hz line voltage. The positive and negative voltages are individually variable. Maximum load current is stated to be 500 mA maximum for either side of the dual supply. Fusing will be on the primary side of the transformer.

The Voltage Regulators

A 7812 fixed-value regulator is used for the positive supply and a 7912 for the negative supply. Per the manufacturer's instructions, $0.33 \mu\text{F}$ capacitors are installed from the input of each regulator to ground, and $0.1 \mu\text{F}$ caps from the output to ground have been added. The large input filtering capacitors of $6800 \mu\text{F}$ produce excellent ripple rejection. Note that the

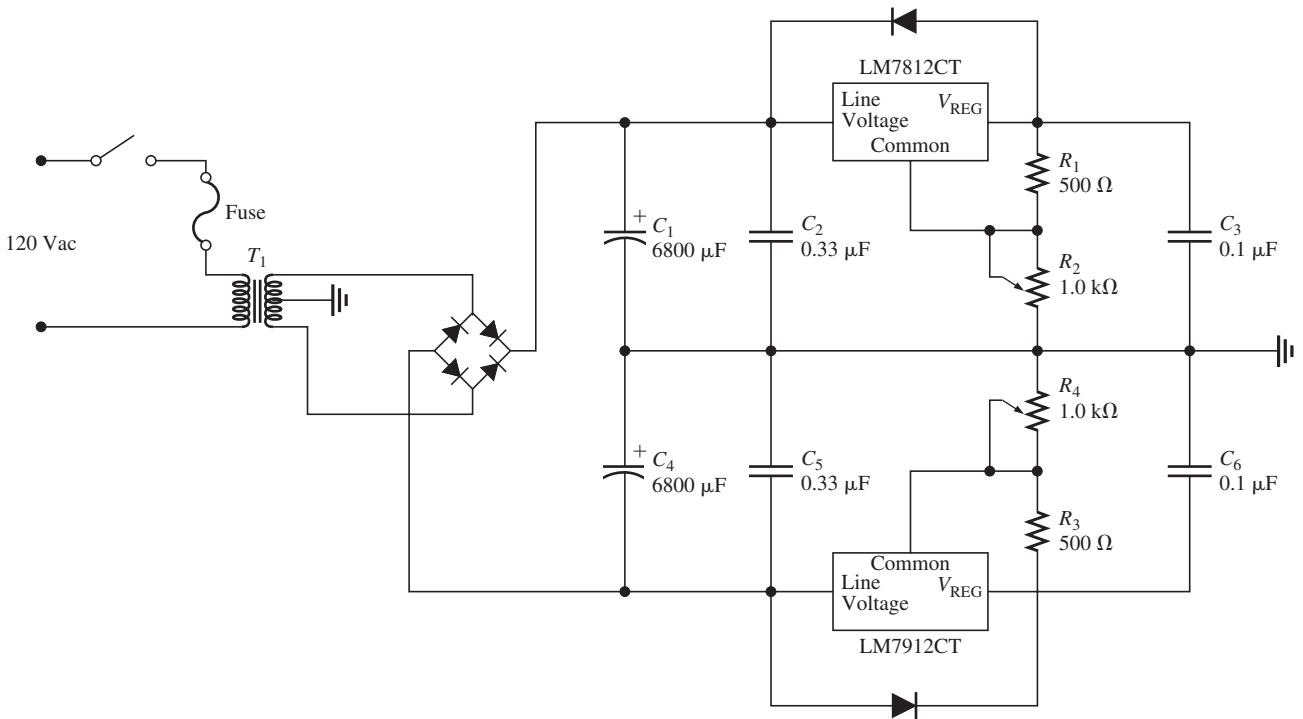


FIGURE SE11-3 Schematic of variable dual-polarity power supply.

positive terminal of the 6800 μF capacitor at the input to the 7912 is connected to ground because of the negative supply voltage.

Installing small-value capacitors in parallel with large-value capacitors may seem unnecessary, but there is a good reason for it. Large electrolytic capacitors have relatively high internal equivalent resistance and some internal inductance as well. Installing the low-value capacitors in parallel improves transient response and decreases the possibility of high-frequency oscillation.

The diodes across each regulator are installed as protection devices. If for any reason the output voltage should be greater than the input voltage, the diodes will conduct and protect the regulator. This could be the result of counter EMF of an inductive load.

Notice the voltage divider connected between the output and the reference terminals of the positive regulator. The voltage between these two pins (V_{R1}) will always have a differential of approximately 12 V. This means that V_{R2} must be 24 V since it has twice the resistance. If we set the reference voltage at some value greater than 0 V, then the output voltage will be equal to 12 V plus the value of the reference voltage. For example, assume that R_2 is adjusted to half its maximum value. This means that the voltage at the reference terminal of the regulator is 12 V, so the actual voltage to ground at the output of the regulator is 24 V. The same principle applies to the negative regulator except for the polarity of the voltages.

MULTISIM



Open file SE11-03 found on the companion website. This simulation demonstrates the operation of a variable dual-polarity dc power supply.

Switching Regulator Configurations

In Section 11-5, the LM78S40 was introduced as an example of an IC switching voltage regulator. Figure 11-37 shows the external connections for a step-down configuration where the output voltage is less than the input voltage, and Figure 11-38 shows a step-up configuration in which the output voltage is greater than the input voltage. An inverting configuration is also possible, but it is not shown here.

The timing capacitor, C_T , controls the pulse width and frequency of the oscillator and thus establishes the on-time of transistor Q_2 . The voltage across the current-sensing resistor R_{CS} is used internally by the oscillator to vary the duty cycle based on the desired peak load current. The voltage divider, made up of R_1 and R_2 , reduces the output voltage to a nominal value equal to the reference voltage. If V_{OUT} exceeds its set value, the output of

FIGURE 11-37 The step-down configuration of the 78S40 switching regulator.


 


FIGURE 11-38 The step-up configuration of the 78S40 switching regulator.

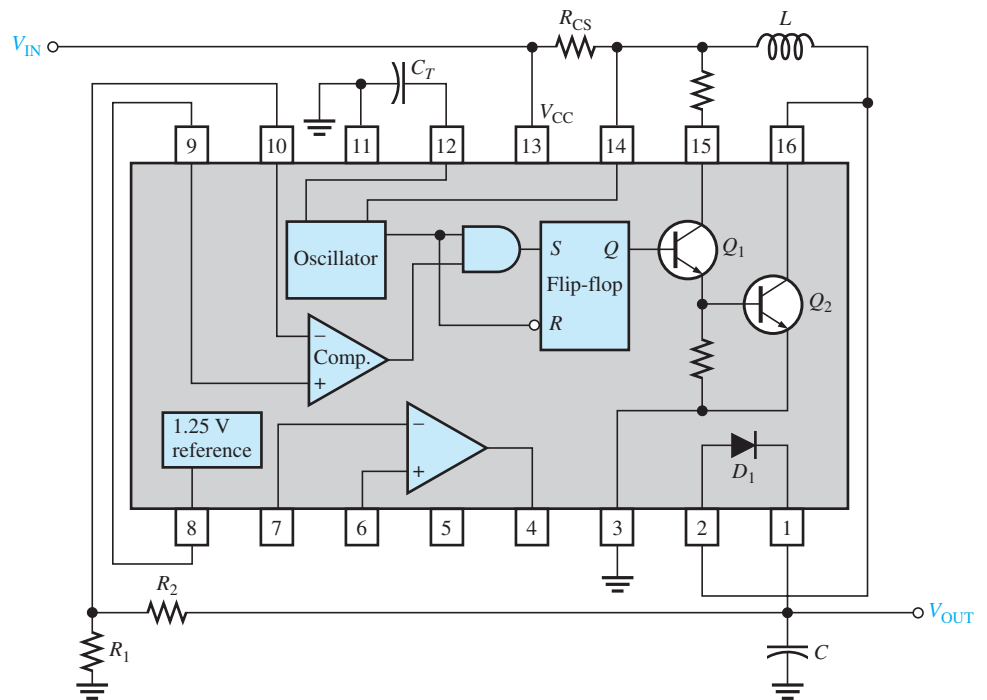

the comparator switches to its low state, disabling the gate to turn Q_2 off until the output decreases. This regulating action is in addition to that produced by the duty cycle variation of the oscillator as described in Section 11-4 in relation to the basic switching regulator.

SECTION 11-6 CHECKUP

1. What is the purpose of using an external pass transistor with an IC voltage regulator?
2. What is the advantage of current limiting in a voltage regulator?
3. How can you configure a three-terminal regulator as a current source?
4. Why is a small value capacitor placed in parallel with a large value capacitor in some power supplies?

SUMMARY

- Voltage regulators keep a constant dc output voltage when the input or load varies within limits.
- A basic voltage regulator consists of a reference voltage source, an error detector, a sampling element, and a control device. Protection circuitry is also found in most regulators.
- Two basic categories of voltage regulators are linear and switching.
- Two basic types of linear regulators are series and shunt.
- In a series linear regulator, the control element is a transistor in series with the load.
- In a shunt linear regulator, the control element is a transistor in parallel with the load.
- Three configurations for switching regulators are step-down, step-up, and inverting.
- Switching regulators are more efficient than linear regulators and are particularly useful in low-voltage, high-current applications.
- Three-terminal linear IC regulators are available for either fixed output or variable output voltages of positive or negative polarities.
- An external pass transistor increases the current capability of a regulator.
- The 7800 series are three-terminal IC regulators with fixed positive output voltage.
- The 7900 series are three-terminal IC regulators with fixed negative output voltage.
- The LM317 is a three-terminal IC regulator with a positive variable output voltage.
- The LM337 is a three-terminal IC regulator with a negative variable output voltage.
- The M78S40 is a switching voltage regulator.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Linear regulator A voltage regulator in which the control element operates in the linear region.

Line regulation The percentage change in output voltage for a given change in line (input) voltage.

Load regulation The percentage change in output voltage for a given change in load current.

Switching regulator A voltage regulator in which the control element is a switching device.

KEY FORMULAS

- (11-1) **Line regulation** $= \left(\frac{\Delta V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\%$ Percent line regulation
- (11-2) **Line regulation** $= \left(\frac{\Delta V_{\text{OUT}}/V_{\text{OUT}}}{\Delta V_{\text{IN}}} \right) 100\%$ Percent line regulation per volt
- (11-3) **Load regulation** $= \left(\frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \right) 100\%$ Percent load regulation
- (11-4) **Load regulation** $= \left(\frac{R_{\text{OUT}}}{R_{\text{FL}}} \right) 100\%$ Percent load regulation given output resistance and minimum load resistance
- (11-5) $V_{\text{OUT}} \cong \left(1 + \frac{R_2}{R_3} \right) V_{\text{REF}}$ Series regulator output
- (11-6) $I_{\text{L(max)}} = \frac{0.7 \text{ V}}{R_4}$ Constant current limiting
- (11-7) $I_{\text{L(max)}} = \frac{V_{\text{IN}}}{R_1}$ Maximum load current for a shunt regulator
- (11-8) $V_{\text{OUT}} = \left(\frac{t_{\text{on}}}{T} \right) V_{\text{IN}}$ Output voltage for step-down switching regulator
- (11-9) $V_{\text{OUT}} = V_{\text{REF}} \left(1 + \frac{R_2}{R_1} \right) + I_{\text{ADJ}} R_2$ Output voltage for IC voltage regulator


SELF-TEST

Answers are at the end of the chapter.

- In the case of line regulation, when the
 - temperature varies, the output voltage stays constant
 - output voltage changes, the load current stays constant
 - input voltage changes, the output voltage stays constant
 - load changes, the output voltage stays constant
- In the case of load regulation, when the
 - temperature varies, the output voltage stays constant
 - input voltage changes, the load current stays constant
 - load changes, the load current stays constant
 - load changes, the output voltage stays constant
- All of the following are parts of a basic voltage regulator *except*
 - control element
 - sampling circuit
 - voltage follower
 - error detector
 - reference voltage
- The basic difference between a series regulator and a shunt regulator is the
 - amount of current that can be handled
 - position of the control element
 - type of sample circuit
 - type of error detector
- In a basic series regulator, V_{OUT} is determined by
 - the control element
 - the sample circuit
 - the reference voltage
 - answers (b) and (c)
- The main purpose of current limiting in a regulator is
 - protection of the regulator from excessive current
 - protection of the load from excessive current
 - to keep the power supply transformer from burning up
 - to maintain a constant output voltage
- In a linear regulator, the control transistor is conducting
 - a small part of the time
 - half the time
 - all of the time
 - only when the load current is excessive
- In a switching regulator, the control transistor is conducting
 - part of the time
 - all of the time
 - only when the input voltage exceeds a set limit
 - only when there is an overload
- The LM317 is an example of an IC
 - three-terminal negative voltage regulator
 - fixed positive voltage regulator
 - switching regulator
 - linear regulator
 - variable positive voltage regulator
 - answers (b) and (d) only
 - answers (d) and (e) only
- An external pass transistor is used for
 - increasing the output voltage
 - improving the regulation
 - increasing the current that the regulator can handle
 - short-circuit protection

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

 

Refer to Figure 11–41.

- If D_1 is mistakenly replaced with a 4.7 V zener,
 1. The output voltage will
 - (a) increase (b) decrease (c) not change
 2. The voltage across Q_1 from collector to emitter will
 - (a) increase (b) decrease (c) not change

Refer to Figure 11–42.

- If the output current is much less than maximum and the emitter of Q_2 is open,
 3. The output voltage will
 - (a) increase (b) decrease (c) not change
 4. The maximum current that can be supplied to a load will
 - (a) increase (b) decrease (c) not change
- If R_2 is shorted,
 5. The output voltage will
 - (a) increase (b) decrease (c) not change

Refer to Figure 11–43.

- If R_1 is open,
 6. The output voltage will
 - (a) increase (b) decrease (c) not change

Refer to Figure 11–44.

- If C is open,
 7. The ripple voltage on the output will
 - (a) increase (b) decrease (c) not change
- If the duty cycle of the oscillator increases,
 8. The output voltage will
 - (a) increase (b) decrease (c) not change

Refer to Figure 11–46.

- If R_1 is smaller than the specified value,
 9. The output voltage will
 - (a) increase (b) decrease (c) not change
 10. The line regulation will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 11–1 Voltage Regulation

1. The nominal output voltage of a certain regulator is 8 V. The output changes 2 mV when the input voltage goes from 12 V to 18 V. Determine the line regulation and express it as a percentage change.
2. Express the line regulation found in Problem 1 in units of %/V.

3. A certain regulator has a no-load output voltage of 10 V and a full-load output voltage of 9.90 V. What is the percent load regulation?
4. In Problem 3, if the full-load current is 250 mA, express the load regulation in %/mA.

SECTION 11-2 Basic Series Regulators

5. Label the functional blocks for the voltage regulator in Figure 11-39.

 


FIGURE 11-39

6. Determine the output voltage for the regulator in Figure 11-40.

 


FIGURE 11-40

7. Determine the output voltage for the series regulator in Figure 11-41.

 


FIGURE 11-41

8. If R_3 in Figure 11-41 is increased to 4.7 k Ω , what happens to the output voltage?
9. If the zener voltage is 2.7 V instead of 2.4 V in Figure 11-41, what is the output voltage?

10. A series voltage regulator with constant current limiting is shown in Figure 11–42. Determine the value of R_4 if the load current is to be limited to a maximum value of 250 mA. What power rating must R_4 have?
11. If the R_4 determined in Problem 10 is halved, what is the maximum load current?

 


FIGURE 11–42

SECTION 11–3 Basic Shunt Regulators

12. In the shunt regulator of Figure 11–43, when the current through R_L increases, does Q_1 conduct more or less? Why?
13. Assume the current through R_L remains constant and V_{IN} changes by 1 V in Figure 11–43. What is the change in the collector current of Q_1 ?

 


FIGURE 11–43

14. With a constant input voltage of 17 V, the load resistance in Figure 11–43 is varied from 1.0 kΩ to 1.2 kΩ. Neglecting any change in output voltage, how much does the shunt current through Q_1 change?
15. If the maximum allowable input voltage in Figure 11–43 is 25 V, what is the maximum possible output current when the output is short-circuited? What power rating should R_1 have?

SECTION 11–4 Basic Switching Regulators

16. A basic switching regulator is shown in Figure 11–44. If the switching frequency of the transistor is 10 kHz with an off-time of 6 μs, what is the output voltage?
17. What is the duty cycle of the transistor in Problem 16?
18. When does the diode D_1 in Figure 11–45 become forward-biased?
19. If the on-time of Q_1 in Figure 11–45 is decreased, does the output voltage increase or decrease?

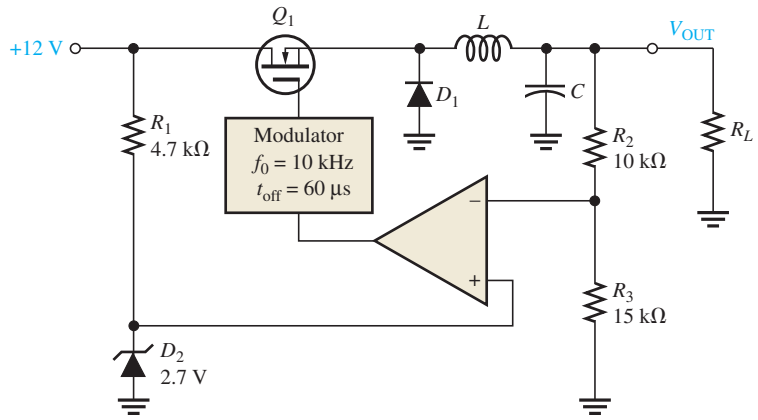


FIGURE 11-44

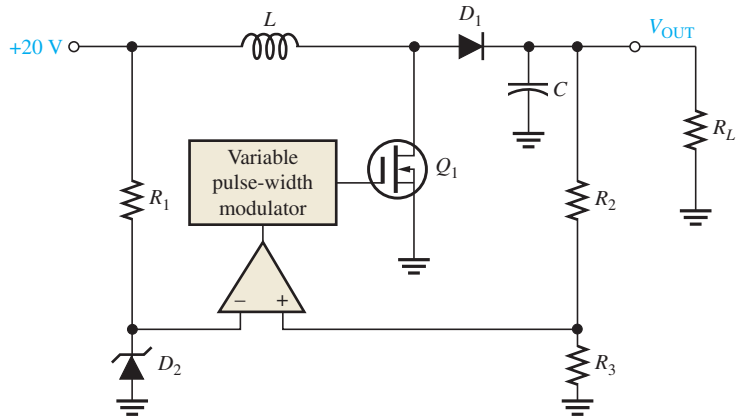


FIGURE 11-45

SECTION 11-5 Integrated Circuit Voltage Regulators

20. What is the output voltage of each of the following IC regulators?
 (a) 7806 (b) 7905.2 (c) 7818 (d) 7924
21. Determine the output voltage of the regulator in Figure 11-46. $I_{ADJ} = 50 \mu\text{A}$.

 


FIGURE 11-46

22. Determine the minimum and maximum output voltages for the circuit in Figure 11-47. $I_{ADJ} = 50 \mu\text{A}$.

 


FIGURE 11-47

23. With no load connected, how much current is there through the regulator in Figure 11–46? Neglect the adjustment terminal current.
24. Select the values for the external resistors to be used in an LM317 circuit that is required to produce an output voltage of 12 V with an input of 18 V. The maximum regulator current with no load is to be 2 mA. There is no external pass transistor.

SECTION 11–6 Applications of IC Voltage Regulators

25. In the regulator circuit of Figure 11–48, determine R_{ext} if the maximum internal regulator current is to be 250 mA.
26. Using a 7812 voltage regulator and a $10\ \Omega$ load in Figure 11–48, how much power will the external pass transistor have to dissipate? The maximum internal regulator current is set at 500 mA by R_{ext} .

 


FIGURE 11–48

27. Show how to include current limiting in the circuit of Figure 11–48. What should the value of the limiting resistor be if the external current is to be limited to 2 A?
28. Using an LM317, design a circuit that will provide a constant current of 500 mA to a load.
29. Repeat Problem 28 using a 7908.
30. If a 78S40 switching regulator is to be used to regulate a 12 V input down to a 6 V output, calculate the values of the external voltage-divider resistors.

MULTISIM TROUBLESHOOTING PROBLEMS

MULTISIM



31. Open file P11-31 and determine the fault.
32. Open file P11-32 and determine the fault.
33. Open file P11-33 and determine the fault.
34. Open file P11-34 and determine the fault.
35. Open file P11-35 and determine the fault.
36. Open file P11-36 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 11–1

1. The percentage change in the output voltage for a given change in input voltage.
2. The percentage change in output voltage for a given change in load current.
3. 1.2%; 0.06%/V
4. 1.6%; 0.0016%/mA

SECTION 11–2

1. Control element, error detector, sampling element, reference source
2. 2 V
3. The symptom of fatigue failure is generally that a system is operating outside its design specification.

SECTION 11-3

1. In a shunt regulator, the control element is in parallel with the load rather than in series.
2. A shunt regulator has inherent current limiting. A disadvantage is that a shunt regulator is less efficient than a series regulator.

SECTION 11-4

1. Step-down, step-up, inverting
2. Switching regulators operate at a higher efficiency so they add less heat to the system. A side benefit is less cooling is required.
3. The duty cycle varies to regulate the output.

SECTION 11-5

1. Input, output, and ground
2. A 7809 has a +9 V output; a 7915 has a -15 V output.
3. Input, output, adjustment
4. A two-resistor voltage divider

SECTION 11-6

1. A pass transistor increases the current that can be handled.
2. Current limiting prevents excessive current and prevents damage to the regulator.
3. See Figure 11-35.
4. A small value capacitor can improve the transient response and decrease the possibility of high frequency oscillation.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

11-1 12%, 0.6%/V

11-2 The voltage drop of $12.1\text{ V} - 12.0\text{ V} = 0.1\text{ V}$ is across the specified output resistance. Since $I = 0.2\text{ A}$ at 12.0 V , $0.1/0.2 = 0.5\ \Omega$.

11-3 7.33 V

11-4 0.7 A

11-5 17.5 W

11-6 12.7 V

11-7 467 mA

11-8 12 W dissipated; choose a larger practical value (e.g., 20 W).

11-9 $8\ \Omega$

ANSWERS TO SELF-TEST

1. (c)
2. (d)
3. (c)
4. (b)
5. (d)
6. (a)
7. (c)
8. (a)
9. (g)
10. (c)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. increase
2. decrease
3. not change
4. increase
5. decrease
6. decrease
7. increase
8. increase
9. increase
10. not change

CHAPTER 12

SPECIAL-PURPOSE AMPLIFIERS

OUTLINE

- 12-1 Instrumentation Amplifiers
- 12-2 Isolation Amplifiers
- 12-3 Operational Transconductance Amplifiers (OTAs)
- 12-4 Log and Antilog Amplifiers

OBJECTIVES

- Understand and explain the operation of an instrumentation amplifier (IA)
- Understand and explain the operation of an isolation amplifier
- Understand and explain the operation of an operational transconductance amplifier (OTA)
- Understand and explain the operation of log and antilog amplifiers

KEY TERMS

Instrumentation amplifier Logarithm
Isolation amplifier Antilog
Operational
transconductance
amplifier

INTRODUCTION

A general-purpose op-amp, such as the 741, is an extremely versatile and widely used device. However, many specialized IC amplifiers have been designed with certain types of systems in mind or with certain special features or characteristics. Most of these devices are actually derived from the basic op-amp. These special amplifiers include the *instrumentation amplifier* (IA) that is used in high-noise environments and data acquisition systems, the *isolation amplifier* that is used in high-voltage and medical systems, the *operational transconductance amplifier* (OTA) that is used as a voltage-to-current amplifier, and the *logarithmic amplifier* that are used for linearizing certain types of inputs and for mathematical operations. In this chapter, you will learn about each of these devices and some of their basic applications.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

12–1 INSTRUMENTATION AMPLIFIERS

An instrumentation amplifier is a differential voltage-gain device that amplifies the difference between the voltages existing at its two input terminals. The main purpose of an instrumentation amplifier is to amplify small signals that are riding on large common-mode voltages. The key characteristics are high input impedance, high common-mode rejection, low output offset, and low output impedance. A basic instrumentation amplifier is made up of three op-amps and several resistors. The voltage gain is set with an external resistor. Instrumentation amplifiers (IAs) are commonly used in environments with high common-mode noise such as in data acquisition systems where remote sensing of input variables is required.

After completing this section, you should be able to

- Understand and explain the operation of an instrumentation amplifier (IA)
- Explain how op-amps are connected to form an IA
- Describe how the voltage gain is set
- Discuss a system application
- Describe the features of the AD622 instrumentation amplifier

The Basic Instrumentation Amplifier

One of the most common problems in measuring systems is the contamination of the signal from a transducer with unwanted noise (such as 60 Hz power line interference). Transducers typically produce a small differential signal carrying the desired information. Noise that is added to both signal conductors in the same amount is called a common-mode noise (discussed in Section 6–2). Ideally, the differential signal should be amplified and the common-mode noise should be rejected.

A second problem for measuring systems is that many transducers have a high output impedance and can easily be loaded down when connected to an amplifier. An amplifier for small transducer signals needs to have a very high input impedance to avoid this loading effect.

The solution to these measurement problems is the **instrumentation amplifier (IA)**, a specially designed differential amplifier with ultra-high input impedance and extremely good common-mode rejection (up to 130 dB) as well as the ability to achieve high, stable gains. Instrumentation amplifiers can faithfully amplify low-level signals in the presence of high common-mode noise. They are used in a variety of signal-processing applications where accuracy is important and where low drift, low bias currents, precise gain, and very high CMRR are required.

Figure 12–1 shows a basic instrumentation amplifier (IA) constructed from three op-amps. Op-amps A1 and A2 are modified voltage-followers, each containing a feedback resistor (R_1 and R_2). The feedback resistors have no effect in this circuit (and could be left out) but will be used when the circuit is modified in the next step. The voltage-followers

 


FIGURE 12–1 The basic instrumentation amplifier using three op-amps.

provide high input impedance with a gain of 1. Op-amp A3 is a differential amplifier that amplifies the difference between V_{out1} and V_{out2} . Although this circuit has the advantage of high input impedance, it requires extremely high precision matching of the gain resistors to achieve a high CMRR (R_3 must match R_4 and R_5 must match R_6). Further, it still has two resistors that must be changed if variable gain is desired (typically R_3 and R_4), and they must track each other with high precision over the operating temperature range.

A clever alternate configuration which solves the difficulties of the circuit in Figure 12-1 and provides high gain is the three op-amp IA shown in Figure 12-2. The inputs are buffered by op-amp A1 and op-amp A2, providing a very high input impedance. Op-amps A1 and A2 can now provide gain. The entire assembly (except for R_G) is contained in a single IC. In this design, the common-mode gain still depends on very precisely matched resistors. However, these resistors can be critically matched during manufacture (by laser trimming) within the IC. Resistors R_3 , R_4 , R_5 , and R_6 are generally set by the manufacturer for a gain of 1.0 for the differential amplifier. Resistors R_1 and R_2 are precision-matched resistors set equal to each other. This means the overall differential gain can be controlled by the size of just resistor R_G , supplied by the user. Appendix A derives the following equation for the output voltage:

$$V_{out} = \left(1 + \frac{2R}{R_G}\right)(V_{in2} - V_{in1}) \quad (12-1)$$

where the closed-loop gain is

$$A_{cl} = 1 + \frac{2R}{R_G}$$

and where $R_1 = R_2 = R$. The last equation shows that the gain of the instrumentation amplifier can be set by the value of the external resistor R_G when R_1 and R_2 have known fixed values.

 


FIGURE 12-2 The instrumentation amplifier with the external gain-setting resistor R_G . Differential and common-mode signals are indicated.

The external gain-setting resistor R_G can be calculated for a desired voltage gain by using the following formula:

$$R_G = \frac{2R}{A_{cl} - 1} \quad (12-2)$$

Instrumentation amplifiers in which the gain is set to specific values using a binary input instead of a resistor are also available.

EXAMPLE 12-1

Determine the value of the external gain-setting resistor R_G for a certain IC instrumentation amplifier with $R_1 = R_2 = 25 \text{ k}\Omega$. The voltage gain is to be 500.

MULTISIM



Open file F12-02 found on the companion website. This simulation demonstrates how the feedback resistors and resistor R_G affect the voltage gain of an instrumentation amplifier.

SOLUTION

$$R_G = \frac{2R}{A_{cl} - 1} = \frac{50 \text{ k}\Omega}{500 - 1} \cong 100 \Omega$$

PRACTICE EXERCISE*

What value of external gain-setting resistor is required for an instrumentation amplifier with $R_1 = R_2 = 39 \text{ k}\Omega$ to produce a gain of 325?

*Answers are at the end of the chapter.

Applications

As mentioned in the introduction to this section, the instrumentation amplifier is normally used to measure small differential signal voltages that are superimposed on a common-mode noise voltage that is often much larger than the signal voltage. Applications include situations where a quantity is sensed by a remote device, such as a temperature- or pressure-sensitive transducer, and the resulting small electrical signal is sent over a long line subject to electrical noise that produces common-mode voltages in the line. The instrumentation amplifier at the end of the line must amplify the small signal from the remote sensor and reject the large common-mode voltage. Figure 12–3 illustrates this.

MULTISIM

Open file F12-03 found on the companion website. This simulation demonstrates the high common-mode rejection characteristics of the instrumentation amplifier.

 



FIGURE 12–3 Illustration of the rejection of large common-mode voltages and the amplification of smaller signal voltages by an instrumentation amplifier.

Instrumentation amplifiers are often used to amplify the signal from some type of sensor. The sensor may measure temperature, strain, pressure, or some other parameter, but in any case, the signal coming from the sensor is usually very low in magnitude. Further, the environment in which the instrumentation amplifier is operating can often be very noisy with long cable runs from the sensor to the amplifier inputs. Shielded coaxial cables are often used to minimize the coupling of external noise into the system. Unfortunately, coaxial cables can also impair the common-mode rejection of the instrumentation amplifier.

In any shielded coax cable there are stray capacitances distributed along the length of the cable between the two signal lines and the shield. Since the stray capacitances between each signal line and the shield are not equal, this can result in a phase shift between any waveforms on the signal lines, especially at high frequencies. This phase shift means that any noise on the two signal lines is no longer truly common-mode and noise rejection is compromised.

One solution to this problem is a technique called *shield guarding*. Guarding uses a voltage follower to feed the common-mode signal back to the shield. This balances any voltage differences between the signal lines and the shield which reduces leakage current and cancels the effects of the distributed capacitances. This technique is used in System Example 12–1.

 Some instrumentation amplifiers have a built-in shield guard driver. One example is the AD522. This is a precision instrumentation amplifier specifically designed for data acquisition in worst-case environments. This device has a “data guard” output terminal that is connected to the cable shield. The data sheet for the AD522 can be found at www.analog.com.



SYSTEM NOTE

A Specific Instrumentation Amplifier

Now that you have the basic idea of how an instrumentation amplifier works, let's look at two specific devices. The first is a low-cost device, the AD622, is shown in Figure 12-4. An IC package pin diagram is shown for reference. This instrumentation amplifier is based on the classic design using three op-amps as previously discussed.

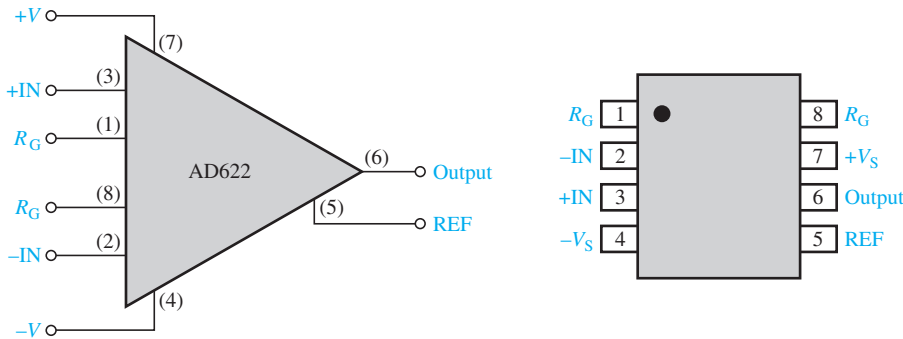


FIGURE 12-4 The AD622 instrumentation amplifier.

Some of the features of the AD622 are as follows. The voltage gain can be adjusted from 2 to 1000 with an external resistor R_G . There is unity gain with no external resistor. The input impedance is 10 G Ω . The common-mode rejection ratio (CMRR') has a minimum value of 66 dB. Recall that a higher CMRR' means better rejection of common-mode voltages. The AD622 has a bandwidth of 800 kHz at a gain of 10 and a slew rate of 1.2 V/ μ s. The data sheet for the AD622 can be found at www.analog.com.

SETTING THE VOLTAGE GAIN For the AD622, an external resistor must be used to achieve a voltage gain greater than unity, as indicated in Figure 12-5. Resistor R_G is connected between the R_G terminals (pins 1 and 8). No resistor is required for unity gain. R_G is selected for the desired gain based on the following formula:

$$R_G = \frac{50.5 \text{ k}\Omega}{A_v - 1} \tag{12-3}$$

Notice that this formula is the same as Equation (12-2) for the classic three-op-amp configuration where the internal resistors R_1 and R_2 are each 25.25 k Ω .

GAIN VERSUS FREQUENCY The graph in Figure 12-6 shows how the gain varies with frequency for gains of 1, 10, 100, and 1000. As you can see, the bandwidth decreases as the gain increases.

 


FIGURE 12-5 The AD622 with a gain-setting resistor.

 


FIGURE 12-6 Gain versus frequency for the AD622 instrumentation amplifier.

EXAMPLE 12-2

Calculate the gain and determine the approximate bandwidth using the graph in Figure 12-6 for the instrumentation amplifier in Figure 12-7.

 


FIGURE 12-7

SOLUTION

The voltage gain is determined as follows:

$$R_G = \frac{50.5 \text{ k}\Omega}{A_v - 1}$$

$$A_v - 1 = \frac{50.5 \text{ k}\Omega}{R_G}$$

$$A_v = \frac{50.5 \text{ k}\Omega}{510 \Omega} + 1 = \mathbf{100}$$

The approximate bandwidth is determined from the graph.

$$BW \cong \mathbf{60 \text{ kHz}}$$

PRACTICE EXERCISE


Modify the circuit in Figure 12-7 for a gain of approximately 45.

In systems that have a sensitive transducer and a longer cable run, a precision IA may be required. An example of a precision IA is the AD624. The AD624 is designed specifically for low-level transducers such as load cells, strain gauges, and certain pressure transducers. The AD624 has a combination of low noise, high gain accuracy, low gain temperature coefficient, and high linearity. It has very high CMRR at 60 Hz, making it an excellent choice for noisy industrial systems. The AD624C version can reduce common-mode power line interference by 110 dB at a gain of 100 and even more for higher gains. In other words, a 1 V common-mode interference signal will be reduced to about 3 μV for a CMRR of 110 dB, which is lower than almost all sensitive transducer signals. In System Example 12-2, this IA is shown in an application. The complete data sheet can be found at www.analog.com.

SYSTEM EXAMPLE 12-1

A LIQUID LEVEL CONTROL SYSTEM

 The system in this example is designed to maintain a constant liquid level in a tank. The level is kept constant by an electric pump and a pressure sensor (transducer) that detects a change in the level of the liquid by sensing the pressure in a tube.



Level-Sensing Method

A tube with both ends open is placed vertically in a liquid so that one end is above the surface of the liquid. The level of liquid in the tube will be the same as the level in the tank. Now, if the upper end is closed, the pressure of the air trapped in the tube will vary in proportion to a change in the level of the liquid. For example, if the liquid is water and it rises in the tank by 20 mm, then the pressure in the tube will increase by 20 mm of water. A pressure sensor is placed on the upper end of the tube when the liquid is at its reference level, and the other side is exposed to atmospheric pressure. When the water level decreases, a negative change in pressure is measured by the pressure sensor and a small proportional voltage is produced. The voltage from the pressure sensor is connected to an instrumentation amplifier, which amplifies the small voltage to drive a comparator with hysteresis (Schmitt trigger). The hysteresis enables the system to have two trigger levels and prevents cycling the pump too often. The comparator reference voltage is adjusted to the desired values and when the level falls below the lower reference, the comparator turns the pump *on* to refill the tank to the upper reference level. The pressure sensor detects when the upper reference level of the liquid is reached, and the comparator turns the pump *off*. A basic diagram of the system is shown in Figure SE12-1.

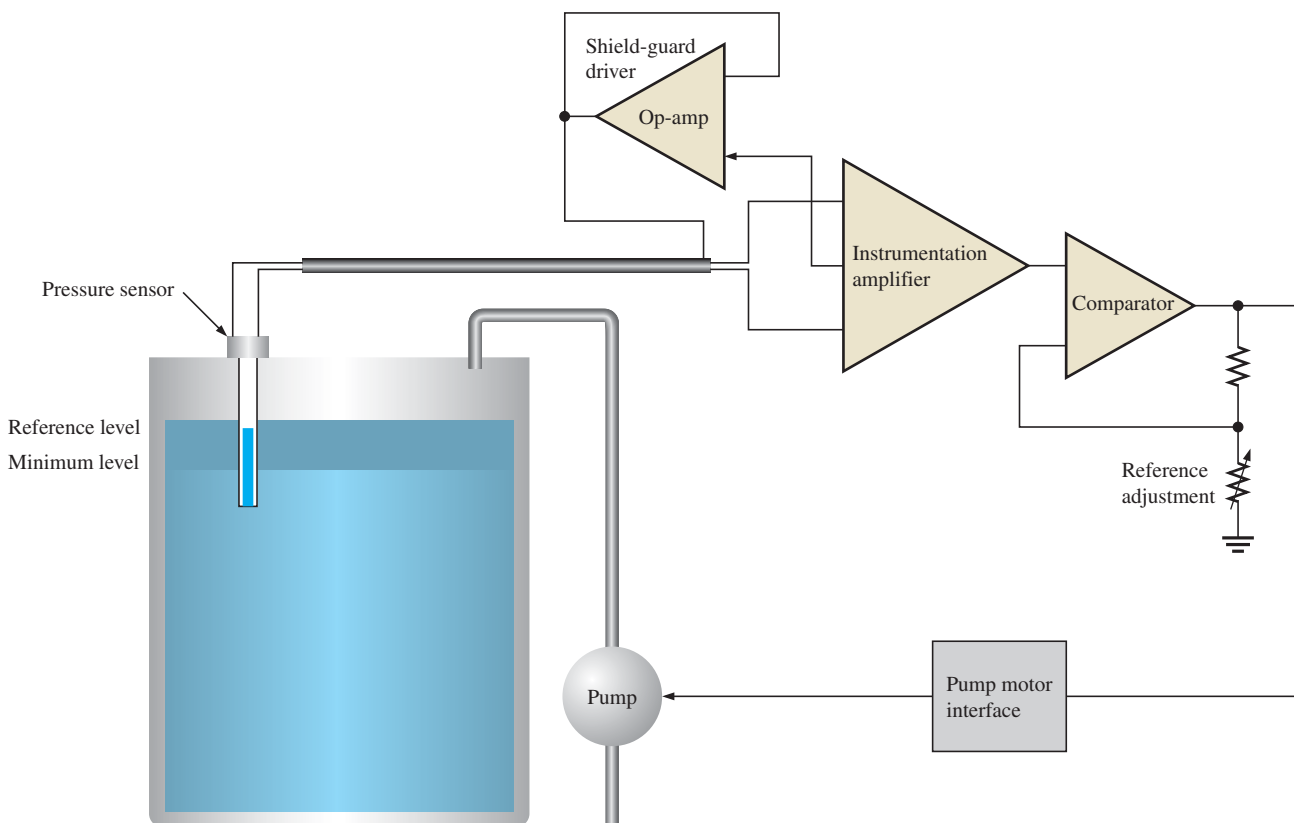


FIGURE SE12-1 Block diagram of the liquid-level control system.

The Circuit

This system will operate in an industrial environment with exposure to mostly 60 Hz electrical noise. Also, the circuit will be located some distance from the tank and connected to the pressure sensor with a long coaxial cable. The output voltage of the pressure sensor is very small ($100\ \mu\text{V} - 200\ \mu\text{V}$). For these reasons, a shield-guard driver is incorporated to minimize the effects of noise on the small signal. The AD624 instrumentation amplifier is used to drive an LM111 comparator with hysteresis controlled by a rheostat in the feedback circuit. An AD711 op-amp connected as a voltage-follower is used for the guard driver. The circuit diagram is shown in Figure SE12-2. Power supply connections are omitted to simplify the drawing. Resistors R_1 and R_2 provide a return path for bias currents to prevent output drift, R_3 is a pull-up resistor for the comparator output, and R_4 and R_5 provide for the adjustable reference levels by varying the hysteresis. R_6 provides a resistance in series with the shield-guard driver to limit current.

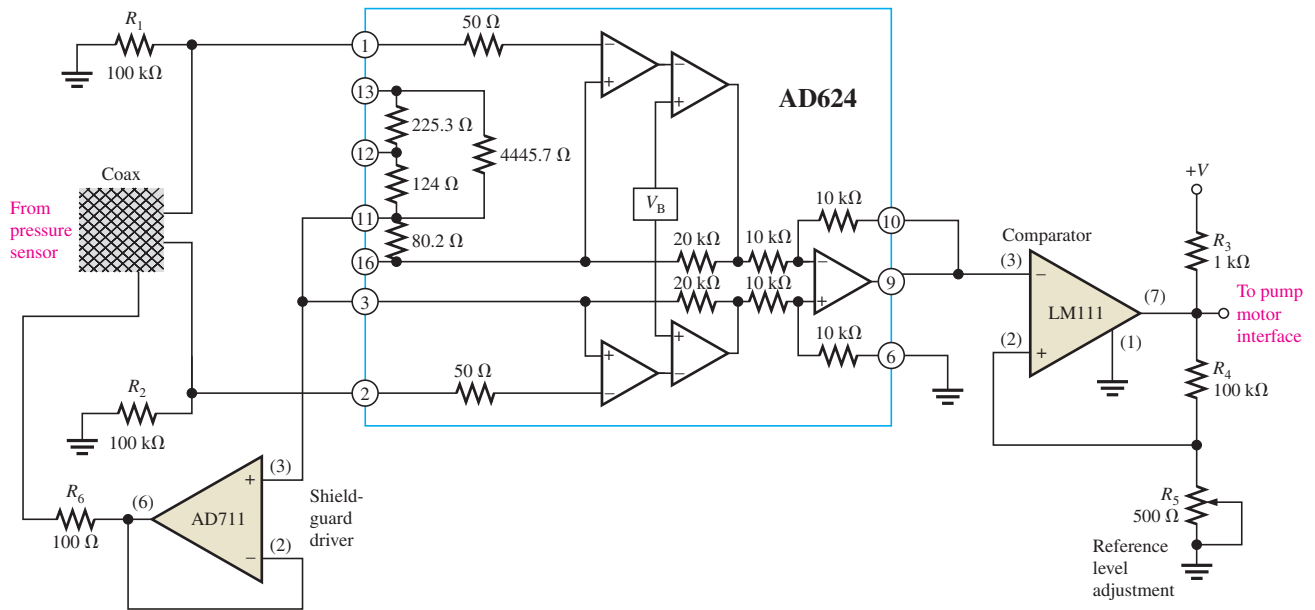


FIGURE SE12-2 Schematic diagram of the liquid-level control circuit.

As the liquid level in the tank decreases, the pressure in the tube decreases. This decrease in pressure is translated into a proportional decrease in voltage by the pressure sensor. This decrease in voltage is processed by the circuit to trigger the comparator to its HIGH state to turn the pump *on* when a desired minimum level is reached. An increase in level occurs while the pump is running, causing a proportional increase in pressure. When the maximum level is reached, the circuit triggers the comparator to its LOW state to turn the pump *off*. This process is illustrated in Figure SE12-3.

 


FIGURE SE12-3 System operation.

SECTION 12-1 CHECKUP*

1. What is the main purpose of an instrumentation amplifier and what are three of its key characteristics?
2. What components do you need to construct a basic instrumentation amplifier?
3. How is the gain determined in a basic instrumentation amplifier?
4. In a certain AD622 configuration, $R_G = 10\text{ k}\Omega$. What is the voltage gain?
5. Why do some systems use a shield guard driver?

*Answers are at the end of the chapter.

12-2 ISOLATION AMPLIFIERS

An isolation amplifier provides dc isolation between input and output. It is used for the protection of human life or sensitive equipment in those applications where hazardous power-line leakage or high-voltage transients are possible. The principal areas of application are in medical instrumentation, power plant instrumentation, industrial processing, and automated testing.

After completing this section, you should be able to

- Explain and analyze the operation of an isolation amplifier
- Describe and discuss the features of the ISO124 as an example of a capacitor-coupled isolation amplifier
- Describe and discuss the features of the 3656KG as an example of a transformer-coupled isolation amplifier
- Describe a system that uses a three-port isolation amplifier, the AD210.

A Basic Capacitor-Coupled Isolation Amplifier

An **isolation amplifier** is a device that consists of two electrically isolated stages. The input stage and the output stage are separated from each other by an isolation barrier so that a signal must be processed in order to be coupled across the isolation barrier. Some isolation amplifiers use optical coupling or transformer coupling to provide isolation between the stages. However, many modern isolation amplifiers use capacitive coupling for isolation. Each stage has separate supply voltages and grounds so that there are no common electrical paths between them. A simplified block diagram for a typical isolation amplifier is shown in Figure 12-8. Notice two different ground symbols are used to reinforce the concept of stage separation.

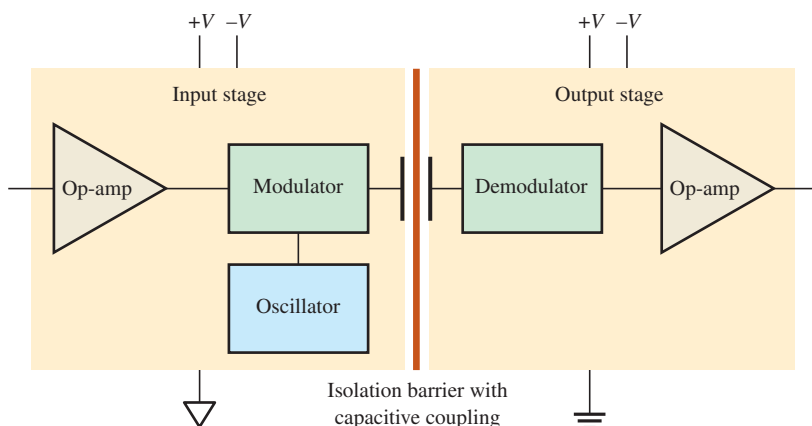


FIGURE 12-8 Simplified block diagram of a typical isolation amplifier.

The input stage consists of an amplifier, an oscillator, and a modulator. **Modulation** is the process of allowing a signal containing information to modify a characteristic of another signal, such as amplitude, frequency, or pulse width, so that the information in the first signal is also contained in the second. In this case, the modulator uses a high-frequency square-wave oscillator to modify the original signal. A small-value capacitor in the isolation barrier is used to couple the lower-frequency modulated signal or dc voltage from the input to the output. Without modulation, prohibitively high-value capacitors would be necessary with a resulting degradation in the isolation between the stages.

The output stage consists of a demodulator that extracts the original input signal from the modulated signal so that the original signal from the input stage is back to its original form.

The high-frequency oscillator output in Figure 12–8 can be either amplitude or pulse-width modulated by the signal from the input amplifier. In amplitude modulation, the amplitude of the oscillator output is varied corresponding to the variations of the input signal, as indicated in Figure 12–9(a), which uses one cycle of a sine wave for illustration. In pulse-width modulation, the duty cycle of the oscillator output is varied by changing the pulse width corresponding to the variations of the input signal. An isolation amplifier using pulse-width modulation is represented in Figure 12–9(b).

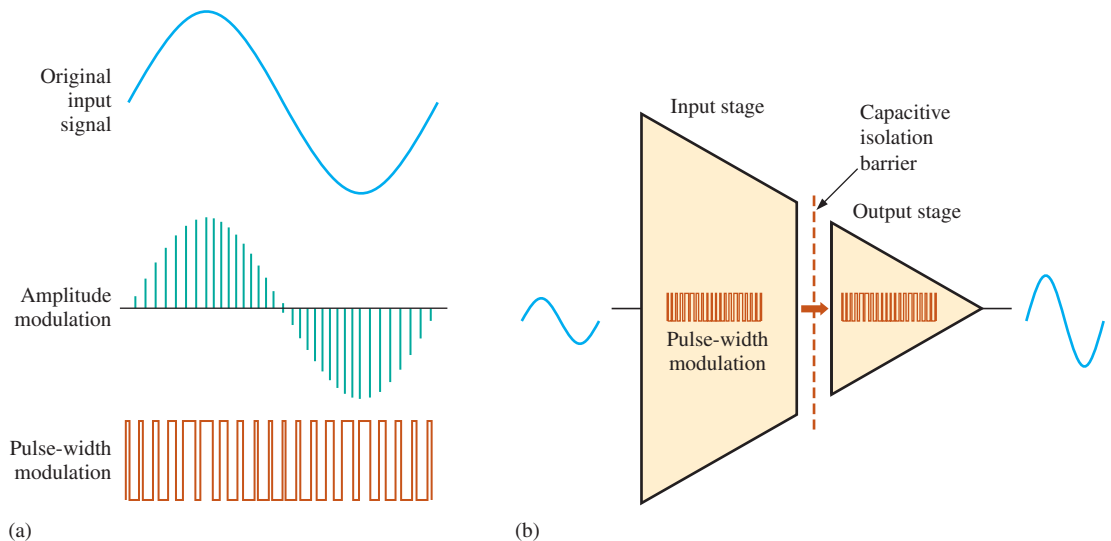


FIGURE 12–9 Modulation.

Although it uses a relatively complex process internally, the isolation amplifier is still just an amplifier and is simple to use. When separate dc supply voltages and an input signal are applied, an amplified output signal is the result. The isolation function itself is an unseen process.

EXAMPLE 12–3

The ISO124 is an integrated circuit isolation amplifier. It has a voltage gain of 1 and operates on positive and negative dc supply voltages for both stages. This device uses pulse-width modulation (sometimes called duty cycle modulation) with a frequency of 500 kHz. It is recommended that the supply voltages be decoupled with external capacitors to reduce noise. Show the appropriate connections.

SOLUTION

The manufacturer recommends a 1 μF tantalum capacitor (for low leakage) from each dc power supply pin to ground. This is shown in Figure 12–10 where the supply voltages are $\pm 15\text{ V}$.

 


FIGURE 12-10 Basic signal and power connections for an ISO124 isolation amplifier.

PRACTICE EXERCISE

The output signal may have some ripple introduced by the demodulation process. How could this ripple be removed?

A Transformer-Coupled Isolation Amplifier

The Texas Instruments (Burr-Brown) 3656KG is an example of an isolation amplifier that uses transformer coupling to isolate the two stages. Unlike the ISO124, which has a fixed unity gain, the 3656KG provides for external gain adjustment of both stages. A diagram of the 3656KG with external gain resistors and decoupling capacitors is shown in Figure 12-11.

 


FIGURE 12-11 The 3656KG isolation amplifier.

The voltage gains of both the input stage and the output stage can be set with external resistors connected as shown in the figure. The gain of the input stage is

$$A_{v1} = \frac{R_{f1}}{R_{i1}} + 1 \quad (12-4)$$

The gain of the output stage is

$$A_{v2} = \frac{R_{f2}}{R_{i2}} + 1 \quad (12-5)$$

The total amplifier gain is the product of the gains of the input and output stages.

$$A_{v(\text{tot})} = A_{v1}A_{v2}$$

EXAMPLE 12-4

Determine the total voltage gain of the 3656KG isolation amplifier in Figure 12-12.

SOLUTION

The voltage gain of the input stage is

$$A_{v1} = \frac{R_{f1}}{R_{i1}} + 1 = \frac{22 \text{ k}\Omega}{2.2 \text{ k}\Omega} + 1 = 10 + 1 = 11$$

The voltage gain of the output stage is

$$A_{v2} = \frac{R_{f2}}{R_{i2}} + 1 = \frac{47 \text{ k}\Omega}{10 \text{ k}\Omega} + 1 = 4.7 + 1 = 5.7$$

 


FIGURE 12-12

The total voltage gain of the isolation amplifier is

$$A_{v(\text{tot})} = A_{v1}A_{v2} = (11)(5.7) = \mathbf{62.7}$$


PRACTICE EXERCISE

Select resistor values in Figure 12-12 that will produce a total voltage gain of approximately 100.

Isolation amplifiers may use inductive, capacitive, or optical coupling between the input and output stages. Which type of isolation amplifier is chosen depends on the type of system application—different isolators have differing performance characteristics and different costs.

Transformer-coupled isolation amplifiers are the most common. They can have analog accuracy of 12–16 bits and bandwidth values in the hundreds of kHz. They are usually limited to maximum voltage levels of 10 kV and often much lower. They also tend to be expensive. Capacitively coupled isolation amplifiers are cheaper but they have lower analog accuracy (perhaps 12 bits), lower bandwidth, and lower voltage ratings. Optical isolators are fast and cheap, and can have voltage ratings in the tens of kilovolts. Unfortunately they have poor analog linearity and cannot be used in applications where precision is required.

SYSTEM NOTE

 

Applications

As previously mentioned, the isolation amplifier is used in applications that require no common grounds between a transducer and the processing circuits where interfacing to sensitive equipment is required. In chemical, nuclear, and metal-processing industries, for example, millivolt signals typically exist in the presence of large common-mode voltages that can be in the kilovolt range. In this type of environment, the isolation amplifier can amplify small signals from very noisy equipment and provide a safe output to sensitive equipment such as computers.

Another important application is in various types of medical equipment. In medical applications where body functions such as heart rate and blood pressure are monitored, the very small monitored signals are combined with large common-mode signals, such as 60 Hz power-line pickup from the skin. In these situations, without isolation, dc leakage or equipment failure could be fatal. Figure 12-13 shows a simplified diagram of an isolation amplifier in a cardiac-monitoring application. In this situation, heart signals, which are very small, are combined with much larger common-mode signals caused by muscle noise, electrochemical noise, residual electrode voltage, and 60 Hz power-line pickup from the skin.


 


FIGURE 12-13 Fetal heartbeat monitoring using an isolation amplifier.

The monitoring of the fetal heartbeat, as illustrated, is the most demanding type of cardiac monitoring because, in addition to the fetal heartbeat that typically generates $50\ \mu\text{V}$, there is also the mother's heartbeat that typically generates 1 mV. The common-mode voltages can run from about 1 mV to about 100 mV. The CMR (common-mode rejection) of the isolation amplifier separates the signal of the fetal heartbeat from that of the mother's heartbeat and from those common-mode signals. Therefore, the signal from the fetal heartbeat is essentially all that the amplifier sends to the monitoring equipment.

In medical applications like a fetal heart monitor, it is obvious why isolation of the heart monitor sensor from the rest of the system is critical. As mentioned, a system failure could have fatal results for the patient. There are some medical applications where isolation of the test equipment from the sensor is also important.

For example, assume a patient suffering from chest pains is connected to an electrocardiograph (ECG) machine and then suddenly goes into cardiac arrest. One possible response by medical personnel could be to use a defibrillator to restart the patient's heart. A defibrillator can produce voltages of 7.5 kV or higher. The ECG must be protected from these dangerous voltage levels, so isolation of the ECG from the sensors is also critical.

 


SYSTEM NOTE

A Wideband Three-Port Isolation Amplifier

The AD210 is a second example of an instrumentation amplifier. The AD210 is a wide-band, three-port isolation amplifier. A three-port isolation amplifier has the input and output ports but also includes a power port. The power port supplies isolated power to both the input and output side of the isolation barrier using internal transformer coupling. The AD210 can also supply isolated external power to operate ICs on the input or output side. This provides additional system protection should a fault occur in the power source. On the input side, the isolated power is labeled as $\pm V_{ISS}$; on the output side it is $\pm V_{OSS}$. In addition, the AD210 has an uncommitted op-amp on the input side so as to allow buffering or gain as required by the user. The following system example shows an application of the AD210 and its power port as well as the AD622 instrumentation amplifier that was introduced earlier.

SYSTEM EXAMPLE 12-2

 

MOTOR CONTROL SYSTEM

In many industrial systems, a high-power or high-voltage application is controlled by a computer or programmable logic controller that operates from a low dc voltage. The high power portion of the system needs to be isolated from the digital portion to provide protection to the sensitive control circuits. In this system example, both an instrumentation amplifier and an isolation amplifier are key components to sensing motor current for a large industrial motor. Figure SE12-4 shows the block diagram of the sensor and isolation portion of the system.

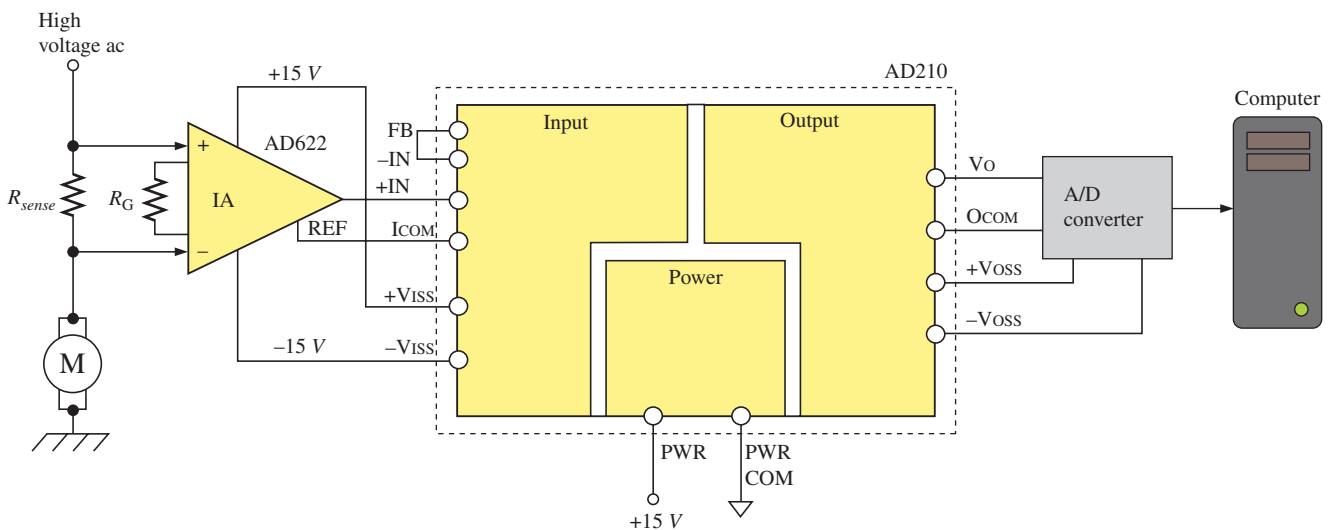


FIGURE SE12-4 Current sensor and isolation circuits for a motor control system.

The current to the motor is sensed by a very small sense resistor, which is amplified by the AD622 instrumentation amplifier (gain determined by R_G). Isolated power for the IA is taken from the input side of the AD210. The signal from the IA is a voltage that represents the motor current. This signal is buffered by the internal op-amp of the AD210 (done with a jumper from $-IN$ to FB , the feedback input). The signal modulates a carrier on the input side and the carrier is demodulated on the output side, recovering the original signal. The signal is buffered at the output and sent to the A/D converter and the computer. (Analog-to-digital converters are covered in Chapter 14.) Notice that isolated power for the A/D converter is from the output side of the isolation amplifier. The computer uses the current information to control the motor speed according to the system requirements.

SECTION 12-2 CHECKUP

1. In what types of applications are isolation amplifiers used?
2. What are the two stages in a typical isolation amplifier and what is the purpose of having two stages?
3. How are the stages in an isolation amplifier connected?
4. What is the purpose of the oscillator in an isolation amplifier?
5. What is the purpose of the third port in a three-port isolation amplifier?

12-3 OPERATIONAL TRANSCONDUCTANCE AMPLIFIERS (OTAs)

Conventional op-amps are, as you know, primarily voltage amplifiers in which the output voltage equals the gain times the input voltage. The OTA is primarily a voltage-to-current amplifier in which the output current equals the gain times the input voltage.

After completing this section, you should be able to

- Understand and explain the operation of an operational transconductance amplifier (OTA)
- Identify the OTA symbol
- Discuss the relationship between transconductance and bias current
- Describe the features of the LM13700 OTA
- Discuss OTA applications

Figure 12-14 shows the symbol for an **operational transconductance amplifier (OTA)**. The double circle symbol at the output represents an output current source that is dependent on a bias current. Like the conventional op-amp, the OTA has two differential input terminals, a high input impedance, and a high CMRR. Unlike the conventional op-amp, the OTA has a bias-current input terminal, a high output impedance, and no fixed open-loop voltage gain.

 


FIGURE 12-14 Symbol for an operational transconductance amplifier (OTA).

The Transconductance Is the Gain of an OTA

In general, the **transconductance** of an electronic device is the ratio of the output current to the input voltage. For an OTA, voltage is the input variable and current is the output variable;

therefore, the ratio of output current to input voltage is its gain. Consequently, the voltage-to-current gain of an OTA is the transconductance, g_m .

$$g_m = \frac{I_{out}}{V_{in}}$$

In an OTA, the transconductance is dependent on a constant (K) times the bias current (I_{BIAS}) as indicated in Equation (12–6). The value of the constant is dependent on the internal circuit design.

$$g_m = KI_{BIAS} \quad (12-6)$$

The output current is controlled by the input voltage and the bias current as shown by the following formula:

$$I_{out} = g_m V_{in} = KI_{BIAS} V_{in}$$

The Transconductance Is a Function of Bias Current

The relationship of the transconductance and the bias current in an OTA is an important characteristic. The graph in Figure 12–15 illustrates a typical relationship. Notice that the transconductance increases linearly with the bias current. The constant of proportionality, K , is the slope of the line and has a value of approximately $16 \mu\text{S}/\mu\text{A}$.

 


FIGURE 12-15 Example of a transconductance versus bias current graph for a typical OTA.

EXAMPLE 12-5

If an OTA has a $g_m = 1000 \mu\text{S}$, what is the output current when the input voltage is 50 mV?

SOLUTION

$$I_{out} = g_m V_{in} = (1000 \mu\text{S})(50 \text{ mV}) = 50 \mu\text{A}$$

PRACTICE EXERCISE

Based on $K \cong 16 \mu\text{S}/\mu\text{A}$, calculate the bias current required to produce $g_m = 1000 \mu\text{S}$.

Basic OTA Circuits

Figure 12-16 shows the OTA used as an inverting amplifier with fixed-voltage gain. The voltage gain is set by the transconductance and the load resistance as follows.

$$V_{out} = I_{out}R_L$$

 


FIGURE 12-16 An OTA as an inverting amplifier with a fixed-voltage gain.

Dividing both sides by V_{in} ,


$$\frac{V_{out}}{V_{in}} = \left(\frac{I_{out}}{V_{in}} \right) R_L$$

Since V_{out}/V_{in} is the voltage gain and $I_{out}/V_{in} = g_m$,

$$A_v = g_m R_L$$

The transconductance of the amplifier in Figure 12-16 is determined by the amount of bias current, which is set by the dc supply voltages and the bias resistor R_{BIAS} .

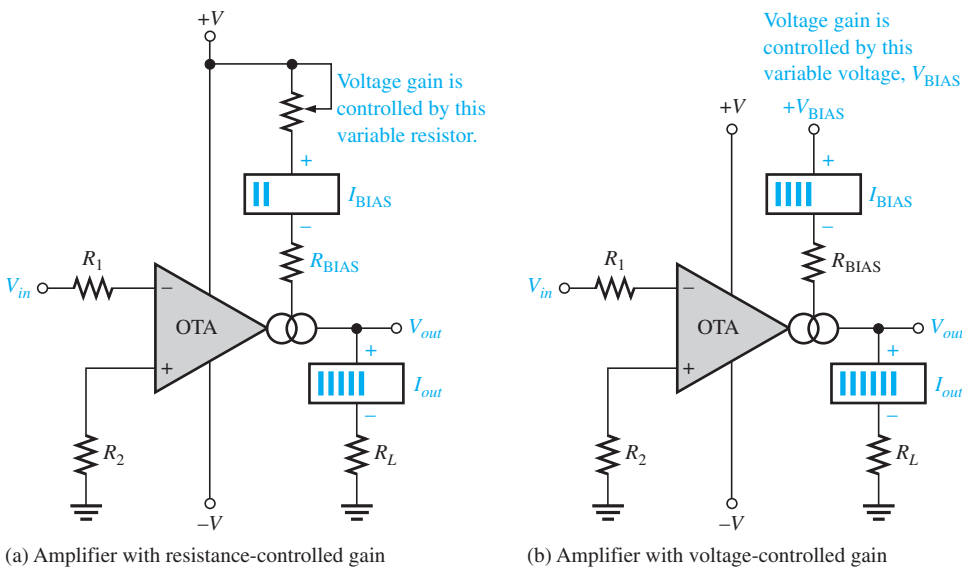One of the most useful features of an OTA is that the voltage gain can be controlled by the amount of bias current. This can be done manually, as shown in Figure 12-17(a), by using a variable resistor in series with R_{BIAS} in the circuit of Figure 12-16. By changing



(a) Amplifier with resistance-controlled gain

(b) Amplifier with voltage-controlled gain

FIGURE 12-17 An OTA as an inverting amplifier with a variable-voltage gain.

the resistance, you can produce a change in I_{BIAS} , which changes the transconductance. A change in the transconductance changes the voltage gain. The voltage gain can also be controlled with an externally applied variable voltage as shown in Figure 12–17(b). A variation in the applied bias voltage causes a change in the bias current.

A Specific OTA

The LM13700 is a typical OTA and serves as a representative device. The LM13700 is a dual-device package containing two OTAs and buffer circuits. Figure 12–18 shows the pin configuration using a single OTA in the package. The maximum dc supply voltages are $\pm 18\text{ V}$, and its transconductance characteristic happens to be the same as indicated by the graph in Figure 12–15. The data sheet for the LM13700 can be found at www.national.com.

For an LM13700, the bias current is determined by the following formula:

$$I_{\text{BIAS}} = \frac{+V_{\text{BIAS}} - (-V) - 1.4\text{V}}{R_{\text{BIAS}}} \quad (12-7)$$

 


FIGURE 12–18 An LM13700 OTA. There are two in an IC package. The buffer transistors are not shown. Pin numbers for both OTAs are given in parentheses.

The 1.4 V is due to the internal circuit where a base-emitter junction and a diode connect the external R_{BIAS} with the negative supply voltage ($-V$). The positive bias voltage may be obtained from the positive supply voltage.

Not only does the transconductance of an OTA vary with bias current, but so does the input and output resistances. Both the input and output resistances decrease as the bias current increases, as shown in Figure 12–19.

 


FIGURE 12–19 Example of input and output resistances versus bias current.

EXAMPLE 12-6

The OTA in Figure 12-20 is connected as an inverting fixed-gain amplifier. Determine the voltage gain.

 


FIGURE 12-20

SOLUTION

Calculate the bias current as follows:

$$I_{\text{BIAS}} = \frac{+V_{\text{BIAS}} - (-V) - 1.4 \text{ V}}{R_{\text{BIAS}}} = \frac{9 \text{ V} - (-9 \text{ V}) - 1.4 \text{ V}}{33 \text{ k}\Omega} = 503 \mu\text{A}$$

Using $K \cong 16 \mu\text{S}/\mu\text{A}$ from the graph in Figure 12-14, the value of transconductance corresponding to $I_{\text{BIAS}} = 503 \mu\text{A}$ is approximately

$$g_m = KI_{\text{BIAS}} \cong (16 \mu\text{S}/\mu\text{A})(503 \mu\text{A}) = 8.05 \times 10^3 \mu\text{S}$$

Using this value of g_m , calculate the voltage gain.

$$A_v = g_m R_L \cong (8.05 \times 10^3 \mu\text{S})(10 \text{ k}\Omega) = \mathbf{80.5}$$

PRACTICE EXERCISE

If the OTA in Figure 12-20 is operated with dc supply voltages of $\pm 12 \text{ V}$, will this change the voltage gain and, if so, to what value?

Two OTA Applications

AMPLITUDE MODULATOR Figure 12-21 illustrates an OTA connected as an amplitude modulator. The voltage gain is varied by applying a modulation voltage to the bias input. When a constant-amplitude input signal is applied, the amplitude of the output signal will vary according to the modulation voltage on the bias input. The gain is dependent on bias current, and bias current is related to the modulation voltage by the following relationship:

$$I_{\text{BIAS}} = \frac{V_{\text{mod}} - (-V) - 1.4 \text{ V}}{R_{\text{BIAS}}}$$

This modulating action is shown in Figure 12-21 for a higher frequency sinusoidal input voltage and a lower frequency sinusoidal modulating voltage.

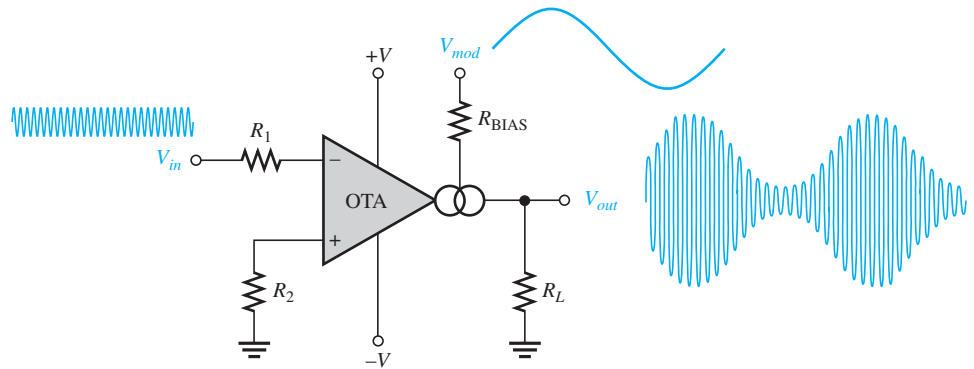


FIGURE 12-21 The OTA as an amplitude modulator.

EXAMPLE 12-7

The input to the OTA amplitude modulator in Figure 12-22 is a 50 mV peak-to-peak, 1 MHz sine wave. Determine the output signal, given the modulation voltage shown is applied to the bias input.

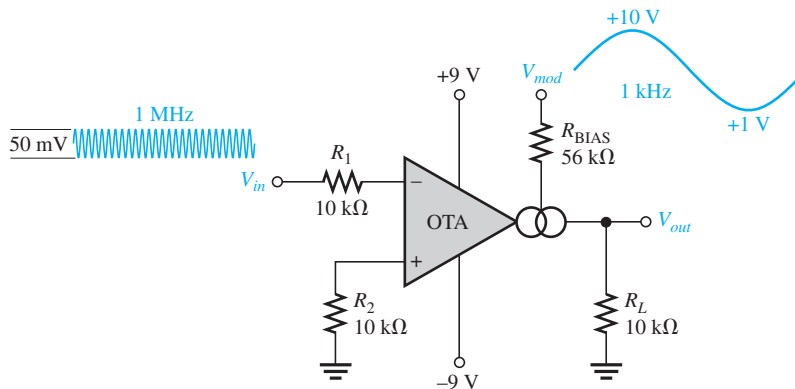


FIGURE 12-22

SOLUTION

The maximum voltage gain is when I_{BIAS} , and thus g_m , is maximum. This occurs at the maximum peak of the modulating voltage, V_{mod} .

$$I_{\text{BIAS(max)}} = \frac{V_{\text{mod(max)}} - (-V) - 1.4 \text{ V}}{R_{\text{BIAS}}} = \frac{10 \text{ V} - (-9 \text{ V}) - 1.4 \text{ V}}{56 \text{ k}\Omega} = 314 \mu\text{A}$$

From the graph in Figure 12-15, the constant K is approximately $16 \mu\text{S}/\mu\text{A}$.

$$g_m = KI_{\text{BIAS(max)}} = (16 \mu\text{S}/\mu\text{A})(314 \mu\text{A}) = 5.02 \text{ mS}$$

$$A_{v(\text{max})} = g_m R_L = (5.02 \text{ mS})(10 \text{ k}\Omega) = 50.2$$

$$V_{\text{out(max)}} = A_{v(\text{min})} V_{\text{in}} = (50.2)(50 \text{ mV}) = 2.51 \text{ V}$$

The minimum bias current is

$$I_{\text{BIAS(min)}} = \frac{V_{\text{mod(min)}} - (-V) - 1.4 \text{ V}}{R_{\text{BIAS}}} = \frac{1 \text{ V} - (-9 \text{ V}) - 1.4 \text{ V}}{56 \text{ k}\Omega} = 154 \mu\text{A}$$

$$g_m = KI_{\text{BIAS(min)}} = (16 \mu\text{S}/\mu\text{A})(154 \mu\text{A}) = 2.46 \text{ mS}$$

$$A_{v(\text{min})} = g_m R_L = (2.46 \text{ mS})(10 \text{ k}\Omega) = 24.6$$

$$V_{\text{out(min)}} = A_{v(\text{min})} V_{\text{in}} = (24.6)(50 \text{ mV}) = 1.23 \text{ V}$$

The resulting output voltage is shown in Figure 12-23.

 


FIGURE 12-23

PRACTICE EXERCISE

Repeat this example with the sinusoidal modulating signal replaced by a square wave with the same maximum and minimum levels and a bias resistor of 39 kΩ.

SCHMITT TRIGGER Figure 12-24 shows an OTA used in a Schmitt-trigger configuration. (Refer to Section 8-1.) Basically, a Schmitt trigger is a comparator with hysteresis where the input voltage drives the device into either positive or negative saturation. When the input voltage exceeds a certain threshold value or trigger point, the device switches to one of its saturated output states. When the input falls back below another threshold value, the device switches back to its other saturated output state.

In the case of the OTA Schmitt trigger, the threshold levels are set by the current through resistor R_1 . The maximum output current in an OTA equals the bias current. Therefore, in the saturated output states, $I_{out} = I_{BIAS}$. The maximum positive output voltage is $I_{out}R_1$, and this voltage is the positive threshold value or upper trigger point. When the input voltage exceeds this value, the output switches to its maximum negative voltage, which is $-I_{out}R_1$. Since $I_{out} = I_{BIAS}$, the trigger points can be controlled by the bias current. Figure 12-25 illustrates this operation.

 


FIGURE 12-24 The OTA as a Schmitt trigger.

 


FIGURE 12-25 Basic operation of the OTA Schmitt trigger.

SYSTEM EXAMPLE 12–3



SYNTHESIZED SINE-WAVE GENERATOR

A synthesized sine-wave generator is shown in block diagram form in SE12–5. A synthesized sine-wave generator is a test instrument that can generate a sine wave with a very accurate frequency for testing circuit responses. To generate the sine wave, the user enters the desired parameters into a digital controller. The controller stores the information and passes along data to a sequence generator. This portion of the circuit generates numbers representing amplitude values along the wave at the desired interval and stores the values in a read-only memory. The memory is clocked at a certain interval that depends on the desired frequency and the digital steps are converted to a sine wave by the digital-to-analog converter (covered in Chapter 14). The conversion process produces unwanted higher frequencies components, which are removed with a low-pass filter that is set to pass the desired sine wave but not the higher harmonics. Here is where a transconductance amplifier (OTA) is very useful—the transconductance amplifier can be configured as a voltage-controlled variable cutoff low-pass filter. If the user decides to change frequencies, the low-pass filter is reconfigured by the controller to a new cutoff frequency by sending a certain voltage to it. Voltage-controlled low-pass circuits have other applications (electronic music for example). The circuit description for a variable low-pass filter is available in the manufacturer’s specification sheet (see www.national.com for the LM13700 for example).

 


FIGURE SE 12–5 A synthesized sine-wave generator

SECTION 12–3 CHECKUP

1. What does OTA stand for?
2. If the bias current in an OTA is increased, does the transconductance increase or decrease?
3. What happens to the voltage gain if the OTA is connected as a fixed-voltage amplifier and the supply voltages are increased?
4. What happens to the voltage gain if the OTA is connected as a variable-gain voltage amplifier and the voltage at the bias terminal is decreased?

12–4 LOG AND ANTILOG AMPLIFIERS

A logarithmic (log) amplifier produces an output that is proportional to the logarithm of the input. Log amplifiers are used in applications that require compression of analog input data, linearization of transducers that have exponential outputs, optical density measurements and more. An antilogarithmic (antilog) amplifier takes the antilog or inverse log of the input. In this section, the principles of these amplifiers are discussed.

After completing this section, you should be able to

- Understand and explain the operation of log and antilog amplifiers
- Define *logarithm* and *natural logarithm*
- Describe the feedback configurations
- Discuss signal compression with logarithmic amplifiers

Logarithms

A **logarithm** (log) is basically a power. It is defined as the power to which a base, b , must be raised to yield a particular number, N . The defining formula for a logarithm is

$$b^x = N$$

In this formula, x represents the log of N . For example, you know that $10^2 = 100$. In this example, 2 is the power of ten that yields the number 100. In other words, 2 is the log of 100 (with base ten implied).

There are two practical bases used for logarithms. Base ten is used for what are called common logs because our counting system is base ten. The abbreviation *log* in a mathematical expression or on your calculator implies base ten. Sometimes the subscript 10 is included with the abbreviation as \log_{10} . The second base is derived from an important mathematical series which gives the number 2.71828.¹ This number is represented by the letter e (mathematicians use ϵ). Base e is used because it is part of mathematical equations that describe natural phenomena such as the charging and discharging of a capacitor and the relationship between voltage and current in certain semiconductor devices. Logarithms that use base e are said to be **natural logarithms** and are shown with the abbreviation *ln* in mathematical expressions and on your calculator.

A useful conversion between the two bases is given by the equation

$$\ln x = 2.303 \log_{10} x$$

The Basic Logarithmic Amplifier

A log amp produces an output that is proportional to the logarithm of the input voltage. The key element in a basic log amplifier is a semiconductor pn junction in the form of either a diode or the base-emitter junction of a bipolar transistor. A pn junction exhibits a natural logarithmic current for many decades of input voltage. Figure 12–26(a) shows this characteristic for a typical small-signal diode, plotted as a linear plot; Figure 12–26(b) shows the same characteristic plotted as a log plot (the y -axis is logarithmic). I_D is the forward diode current and V_D is the forward diode voltage. The logarithmic relationship between diode current and voltage is clearly seen in the plot in part (b). Although the plot only shows four decades of data, the actual logarithmic relationship for a diode extends over seven decades! The relationship between the current and voltage is expressed by the following general equation for a diode:

$$V_D = K \ln \left(\frac{I_D}{I_R} \right)$$

In this equation, K is a constant that is determined by several factors including the temperature and is approximately 0.025 V at 25°C. I_R , the reverse leakage current, is a constant for a given diode.

¹The series is $e = \lim_{n \rightarrow \infty} \left(1 + \frac{1}{n} \right)^n$.

 



FIGURE 12-26 The characteristic curve for a typical diode.

LOG AMPLIFIER WITH A DIODE When the feedback resistor in an inverting amplifier is replaced with a diode, the result is a basic log amp, as shown in Figure 12-27. The output voltage, V_{out} , is equal to $-V_D$. Because of the virtual ground, the input current can be expressed as V_{in}/R_1 . By substituting these quantities into the diode equation, the output voltage is

$$V_{out} \cong -(0.025 \text{ V}) \ln\left(\frac{V_{in}}{I_R R_1}\right) \tag{12-8}$$

From Equation (12-8), you can see that the output voltage is the negative of a logarithmic function of the input voltage. The value of the output is controlled by the value of the input voltage and the value of the resistor R_1 .


FIGURE 12-27 A basic log amplifier using a diode as the feedback element.

 

EXAMPLE 12-8

Determine the output voltage for the log amplifier in Figure 12-28. Assume $I_R = 50 \text{ nA}$.

FIGURE 12-28

 

SOLUTION

The input voltage and the resistor value are given in Figure 12-28.

$$\begin{aligned} V_{\text{OUT}} &= -(0.025 \text{ V}) \ln\left(\frac{V_{\text{in}}}{I_{\text{R}}R_1}\right) = -(0.025 \text{ V}) \ln\left(\frac{2 \text{ V}}{(50 \text{ nA})(100 \text{ k}\Omega)}\right) \\ &= -(0.025 \text{ V}) \ln(400) = -(0.025 \text{ V})(5.99) = \mathbf{-0.150 \text{ V}} \end{aligned}$$

PRACTICE EXERCISE

Calculate the output voltage of the log amplifier with a +4 V input.

LOG AMPLIFIER WITH A BJT The base-emitter junction of a bipolar transistor exhibits the same type of natural logarithmic characteristic as a diode because it is also a *pn* junction. A log amplifier with a BJT connected in a common-base form in the feedback loop is shown in Figure 12-29. Notice that V_{out} with respect to ground is equal to $-V_{\text{BE}}$.

The analysis for this circuit is the same as for the diode log amplifier except that $-V_{\text{BE}}$ replaces V_{D} , I_{C} replaces I_{D} , and I_{EBO} replaces I_{R} . The emitter-to-base leakage current is I_{EBO} . The expression for the output voltage is

$$V_{\text{out}} = -(0.025 \text{ V}) \ln\left(\frac{V_{\text{in}}}{I_{\text{EBO}}R_1}\right) \quad (12-9)$$

 


FIGURE 12-29 A basic log amplifier using a transistor as the feedback element.

EXAMPLE 12-9

What is V_{out} for a transistor log amplifier with $V_{\text{in}} = 3 \text{ V}$ and $R_1 = 68 \text{ k}\Omega$? Assume $I_{\text{EBO}} = 40 \text{ nA}$.

SOLUTION

$$\begin{aligned} V_{\text{out}} &= -(0.025 \text{ V}) \ln\left(\frac{V_{\text{in}}}{I_{\text{EBO}}R_1}\right) = -(0.025 \text{ V}) \ln\left(\frac{3 \text{ V}}{(40 \text{ nA})(68 \text{ k}\Omega)}\right) \\ &= -(0.025 \text{ V}) \ln(1103) = \mathbf{-0.175 \text{ V}} \end{aligned}$$

PRACTICE EXERCISE

Calculate V_{out} if R_1 is changed to $33 \text{ k}\Omega$.

The Basic Antilog Amplifier

The antilog amplifier is the complement of a log amplifier. If you know the logarithm of a number, you know the power the base is raised to. To obtain the **antilog**, you must take the *exponential* of the logarithm.


$$x = e^{\ln x}$$

This is equivalent to saying the antilog_{*e*} of $\ln x$ is just x . (Notice that the antilog is base e in this statement.) On many calculators the antilog of a base 10 logarithm is labelled $\overline{10^x}$ and in some cases $\overline{\text{INV LOG}}$. The antilog of a base e logarithm is labelled $\overline{e^x}$ or $\overline{\text{INV LN}}$.

The basic antilog amplifier is formed by reversing the position of the transistor (or diode) with the resistor in the log amp circuit. The antilog circuit is shown in Figure 12–30 using a transistor base-emitter junction as the input element and a resistor as the feedback element. The relationship between the current and voltage for a diode still applies.

$$V_D = K \ln\left(\frac{I_D}{I_R}\right)$$

FIGURE 12–30 A basic anti-log amplifier.

 

For the antilog amplifier, V_D is the negative input voltage and I_D represents the current in the feedback resistor, which by Ohm's law is V_{out}/R_F . Since a transistor is used, $I_R = I_{EBO}$. Making these substitutions in the diode equation,

$$V_{in} = -K \ln\left(\frac{V_{out}}{I_{EBO}R_F}\right)$$

Rearranging,

$$V_{out} = -I_{EBO}R_F e^{V_{in}/K}$$


Substituting $K \cong 0.025$ V and clearing the exponent,

$$V_{out} \cong -I_{EBO}R_F \text{antilog}_e\left(\frac{V_{in}}{25 \text{ mV}}\right) \quad (12-10)$$

EXAMPLE 12–10

For the antilog amplifier in Figure 12–31, find the output voltage. Assume $I_{EBO} = 40$ nA.

FIGURE 12–31

 

SOLUTION

First of all, notice that the input voltage in Figure 12-31 is the inverted output voltage of the log amplifier in Example 12-9. In this case, the antilog amplifier reverses the process and produces an output that is proportional to the antilog of the input. So the output voltage of the antilog amplifier in Figure 12-31 should have the same magnitude as the input voltage of the log amplifier in Example 12-9 because all the constants are the same. Let's see if it does.

$$\begin{aligned} V_{\text{OUT}} &\cong -I_{\text{EBO}}R_{\text{Fantilog}}e^{\left(\frac{V_{\text{in}}}{25 \text{ mV}}\right)} = -(40 \text{ nA})(68 \text{ k}\Omega)\text{antilog}_e\left(\frac{0.175 \text{ V}}{25 \text{ mV}}\right) \\ &= -(40 \text{ nA})(68 \text{ k}\Omega)(1100) = -3 \text{ V} \end{aligned}$$

PRACTICE EXERCISE

Determine V_{OUT} for the amplifier in Figure 12-31 if the feedback resistor is changed to 100 k Ω .

IC Log, Log-Ratio, and Antilog Amplifiers


Several factors make the basic log amp and the basic antilog amp circuit with a diode and op-amp unsatisfactory for many applications. The basic circuit is temperature sensitive and tends to have error at very low diode currents; also, components need to be precisely matched, and the output level is not a convenient value. These problems are difficult to address with off-the-shelf components; however, manufacturers have designed precision integrated circuit logarithmic and log-ratio amplifiers with temperature compensation, low bias currents, and high accuracy that require no user adjustments. Log-ratio measurements produce an output that is proportional to the log ratio of *two* inputs.

The LOG102 is an example of a log, log-ratio, and antilog amplifier in one 14-pin IC. It has a maximum accuracy specification of 0.15% at full-scale output (FSO) and a six-decade range of input current (1 nA to 1 mA). With a few external resistors, the user can connect the amplifier as either a log, a log-ratio, or an antilog amplifier. Scaling of the output voltage can be done by simply selecting an appropriate output pin. As with most log amps, the input will function with only one polarity of input current. The data sheet for the LOG102 can be found at www.ti.com.

Signal Compression with Logarithmic Amplifiers

In certain applications, a signal may be too large in magnitude for a particular system to handle. The term *dynamic range* is often used to describe the range of voltages contained in a signal. In these cases, the signal voltage must be scaled down by a process called **signal compression** so that it can be properly handled by the system. If a linear circuit is used to scale a signal down in amplitude, the lower voltages are reduced by the same percentage as the higher voltages. Linear signal compression often results in the lower voltages becoming obscured by noise and difficult to accurately distinguish, as illustrated in Figure 12-32(a). To overcome this problem, a signal with a large dynamic range can be compressed using a logarithmic response, as shown in Figure 12-32(b). In logarithmic signal compression, the higher voltages are reduced more than the lower voltages, thus keeping the lower voltage signals from being lost in noise. A log amplifier preceding an 8-bit ADC can replace a more expensive 20-bit ADC because of signal compression.

FIGURE 12–32 The basic concept of signal compression with a logarithmic amplifier.

 

A Basic Multiplier with Log and Antilog Amps

Multipliers are based on the fundamental logarithmic relationship that states that the product of two terms equals the sum of the logarithms of each term. This relationship is shown in the following formula:

$$\ln(a \times b) = \ln a + \ln b$$

This formula shows that two signal voltages are effectively multiplied if the logarithms of the signal voltages are added.

You know how to get the logarithm of a signal voltage by using a log amplifier. By summing the outputs of two log amplifiers, you get the logarithm of the product of the two original input voltages. Then, by taking the antilogarithm, you get the product of the two input voltages as indicated in the following equations:

$$\ln V_1 + \ln V_2 = \ln(V_1 V_2)$$

$$\text{antilog}_e[\ln(V_1 V_2)] = V_1 V_2$$

The block diagram in Figure 12–33 shows how the functions are connected to multiply two input voltages. Constant terms are omitted for simplicity. The electronic circuit version of this operation will have three inversions for each signal.

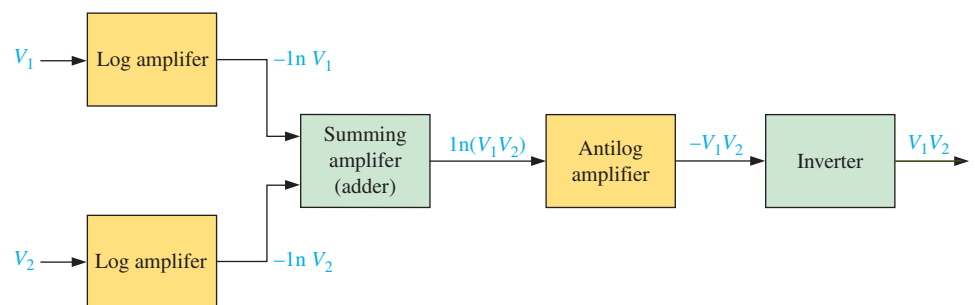


FIGURE 12–33 Basic block diagram of an analog multiplier.

Figure 12-34 shows the basic multiplier circuitry. The outputs of the log amplifiers are stated as follows:

$$V_{out(log1)} = -K_1 \ln\left(\frac{V_{in1}}{K_2}\right)$$

$$V_{out(log2)} = -K_1 \ln\left(\frac{V_{in2}}{K_2}\right)$$

where $K_1 = 0.025 \text{ V}$, $K_2 = RI_{EBO}$, and $R = R_1 = R_2 = R_6$. The two output voltages from the log amplifiers are added and inverted by the unity-gain summing amplifier to produce the following result:

$$V_{out(sum)} = K_1 \ln\left[\left(\frac{V_{in1}}{K_2}\right) + \ln\left(\frac{V_{in2}}{K_2}\right)\right] = K_1 \ln\left(\frac{V_{in1}V_{in2}}{K_2^2}\right)$$

This expression is then applied to the antilog amplifier; the expression for the multiplier output voltage is as follows:

$$V_{out(antilog)} = -K_2 \text{antilog}_e\left(\frac{V_{out(sum)}}{K_1}\right) = -K_2 \text{antilog}_e\left[\frac{K_1 \ln\left(\frac{V_{in1}V_{in2}}{K_2^2}\right)}{K_1}\right]$$

$$= -K_2 \left(\frac{V_{in1}V_{in2}}{K_2^2}\right) = -\frac{V_{in1}V_{in2}}{K_2}$$

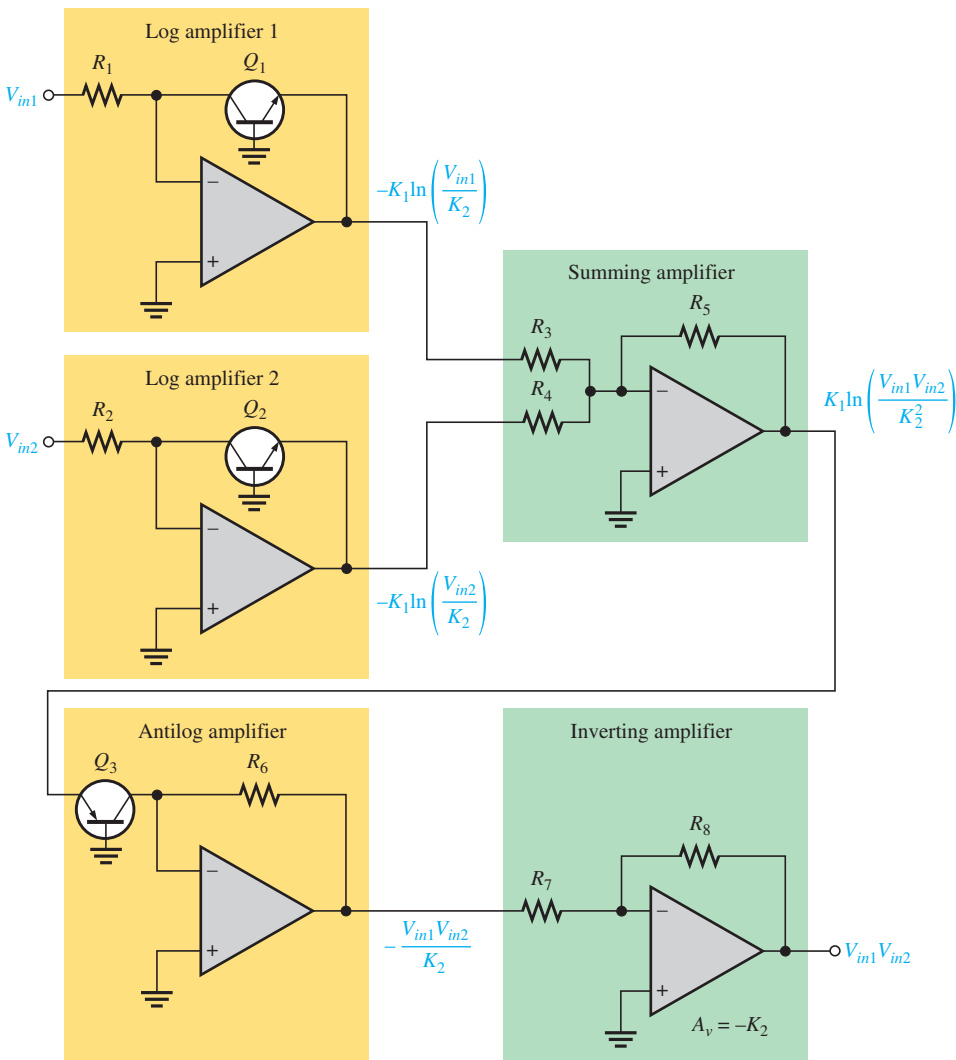


FIGURE 12-34 A basic multiplier.

As you can see, the output of the antilog amplifier is a constant ($1/K_2$) times the *product* of the input voltages. The final output is developed by an inverting amplifier with a voltage gain of $-K_2$.

$$V_{out} = -K_2 \left(-\frac{V_{in1}V_{in2}}{K_2} \right)$$

$$V_{out} = V_{in1}V_{in2} \quad (12-11)$$

As in the case of log amps, analog multipliers are available in IC form. These are covered in Chapter 13.

SECTION 12-4 CHECKUP

1. What purpose does the diode or transistor perform in the feedback loop of a log amplifier?
2. Why is the output of a basic log amplifier limited to about 0.7 V?
3. What are the factors that determine the output voltage of a basic log amplifier?
4. In terms of implementation, how does a basic antilog amplifier differ from a basic log amplifier?
5. What circuits make up a basic analog multiplier?
6. Why does the basic multiplier circuit in Figure 12-34 include an inverter at the end?

SUMMARY

- A basic instrumentation amplifier is formed by three op-amps and seven resistors, including the gain-setting resistor, R_G .
- An instrumentation amplifier has high input impedance, high CMRR, low output offset, and low output impedance.
- The voltage gain of a basic instrumentation amplifier is set by a single external resistor.
- An instrumentation amplifier is useful in applications where small signals are embedded in large common-mode noise.
- A basic isolation amplifier has three electrically isolated parts: input, output, and power.
- Most isolation amplifiers use transformer coupling for isolation.
- Isolation amplifiers are used to interface sensitive equipment with high-voltage environments and to provide protection from electrical shock in certain medical applications.
- The operational transconductance amplifier (OTA) is a voltage-to-current amplifier.
- The output current of an OTA is the input voltage times the transconductance.
- In an OTA, transconductance varies with bias current; therefore, the gain of an OTA can be varied with a bias voltage or a variable resistor.
- The operation of log and antilog amplifiers is based on the nonlinear (logarithmic) characteristic of a pn junction.
- A log amplifier has a BJT in the feedback loop.
- An antilog amplifier has a BJT in series with the input.
- Logarithmic amplifiers are used for signal compression, analog multiplication, and log-ratio measurements.
- An analog multiplier is based on the mathematical principle that states the logarithm of the product of two variables equals the sum of the logarithms of the variables.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Antilog The number corresponding to a given logarithm.

Instrumentation amplifier A differential voltage-gain device that amplifies the differences between the voltages existing at its two input terminals.

Isolation amplifier An amplifier in which the input and output stages are not electrically connected.

Logarithm An exponent; the logarithm of a quantity is the exponent or power to which a given number called the base must be raised in order to equal the quantity.

Operational transconductance amplifier An amplifier in which the output current is the gain times the input voltage.

KEY FORMULAS

INSTRUMENTATION AMPLIFIER

$$(12-1) \quad V_{out} = \left(1 + \frac{2R}{R_G}\right)(V_{in2} - V_{in1})$$

$$(12-2) \quad R_G = \frac{2R}{A_{cl} - 1}$$

$$(12-3) \quad R_G = \frac{50.5 \text{ k}\Omega}{A_v - 1} \quad (\text{for the AD622})$$

ISOLATION AMPLIFIER

$$(12-4) \quad A_{v1} = \frac{R_{f1}}{R_{i1}} + 1$$

$$(12-5) \quad A_{v2} = \frac{R_{f2}}{R_{i2}} + 1$$

OPERATIONAL TRANSCONDUCTANCE AMPLIFIER (OTA)

$$(12-6) \quad g_m = KI_{BIAS}$$

$$(12-7) \quad I_{BIAS} = \frac{+V_{BIAS} - (-V) - 1.4 \text{ V}}{R_{BIAS}} \quad (\text{for the LM13700})$$

LOGARITHMIC AMPLIFIER

$$(12-8) \quad V_{out} \cong -(0.025 \text{ V}) \ln\left(\frac{V_{in}}{I_R R_1}\right)$$

$$(12-9) \quad V_{out} = -(0.025 \text{ V}) \ln\left(\frac{V_{in}}{I_{EBO} R_1}\right)$$

$$(12-10) \quad V_{out} \cong -I_{EBO} R_F \text{antilog}_e\left(\frac{V_{in}}{25 \text{ mV}}\right)$$

$$(12-11) \quad V_{out} = V_{in1} V_{in2}$$

SELF-TEST


Answers are at the end of the chapter.

- To make a basic instrumentation amplifier, it takes
 - one op-amp with a certain feedback arrangement
 - two op-amps and seven resistors
 - three op-amps and seven capacitors
 - three op-amps and seven resistors
- Typically, an instrumentation amplifier has an external resistor used for
 - establishing the input impedance
 - setting the voltage gain
 - setting the current gain
 - interfacing with an instrument

3. Instrumentation amplifiers are used primarily in
 - (a) high-noise environments
 - (b) medical equipment
 - (c) test instruments
 - (d) filter circuits
4. Isolation amplifiers are used primarily in
 - (a) remote, isolated locations
 - (b) systems that isolate a single signal from many different signals
 - (c) applications where there are high voltages and sensitive equipment
 - (d) applications where human safety is a concern
 - (e) answers (c) and (d)
5. The three parts of a basic isolation amplifier are
 - (a) amplifier, filter, and power
 - (b) input, output, and coupling
 - (c) input, output, and power
 - (d) gain, attenuation, and offset
6. The stages of most isolation amplifiers are connected by
 - (a) copper strips
 - (b) transformers
 - (c) microwave links
 - (d) current loops
7. The characteristic that allows an isolation amplifier to amplify small signal voltages in the presence of much greater noise voltages is its
 - (a) CMRR
 - (b) high gain
 - (c) high input impedance
 - (d) magnetic coupling between input and output
8. The term *OTA* means
 - (a) operational transistor amplifier
 - (b) operational transformer amplifier
 - (c) operational transconductance amplifier
 - (d) output transducer amplifier
9. In an OTA, the transconductance is controlled by
 - (a) the dc supply voltage
 - (b) the input signal voltage
 - (c) the manufacturing process
 - (d) a bias current
10. The voltage gain of an OTA circuit is set by
 - (a) a feedback resistor
 - (b) the transconductance only
 - (c) the transconductance and the load resistor
 - (d) the bias current and supply voltage
11. An OTA is basically a
 - (a) voltage-to-current amplifier
 - (b) current-to-voltage amplifier
 - (c) current-to-current amplifier
 - (d) voltage-to-voltage amplifier
12. The operation of a logarithmic amplifier is based on
 - (a) the nonlinear operation of an op-amp
 - (b) the logarithmic characteristic of a *pn* junction
 - (c) the reverse breakdown characteristic of a *pn* junction
 - (d) the logarithmic charge and discharge of an *RC* circuit
13. If the input to a log amplifier is x , the output is proportional to
 - (a) e^x
 - (b) $\ln x$
 - (c) $\log_{10}x$
 - (d) $2.3 \log_{10}x$
 - (e) answers (a) and (c)
 - (f) answers (b) and (d)
14. If the input to an antilog amplifier is x , the output is proportional to
 - (a) $e^{\ln x}$
 - (b) e^x
 - (c) $\ln x$
 - (d) e^{-x}
15. The logarithm of the product of two numbers is equal to the
 - (a) sum of the two numbers
 - (b) sum of the logarithms of each of the numbers
 - (c) difference of the logarithms of each of the numbers
 - (d) ratio of the logarithms of the numbers

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

 

Refer to Figure 12–35.

- If R_5 opens,
 1. The output signal voltage will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the output of op-amp 3 opens,
 2. The output signal voltage will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 12–36.

- If R_G opens,
 3. The voltage gain will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the value of R_G is larger than the specified value,
 4. The bandwidth will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 12–37(a).

- If there is a short across the 18 k Ω resistor,
 5. The voltage gain will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the 150 k Ω resistor shorts,
 6. The output signal voltage will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the capacitor between pins 19 and 20 is open,
 7. The gain will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 12–38.

- If the value of R_{BIAS} is less than the specified value,
 8. The output voltage will
 - (a) increase
 - (b) decrease
 - (c) not change

- If the negative dc supply voltage decreases (less negative),
 9. The output voltage will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the positive supply voltage increases,
 10. The transconductance will
 - (a) increase
 - (b) decrease
 - (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 12-1 Instrumentation Amplifiers

1. Determine the voltage gains of op-amps A1 and A2 for the instrumentation amplifier configuration in Figure 12-35.
2. Find the overall voltage gain of the instrumentation amplifier in Figure 12-35.
3. The following voltages are applied to the instrumentation amplifier in Figure 12-35. $V_{in1} = 5$ mV, $V_{in2} = 10$ mV, and $V_{cm} = 225$ mV. Determine the final output voltage.
4. What value of R_G must be used to change the gain of the instrumentation amplifier in Figure 12-35 to 1000?
5. What is the voltage gain of the AD622 instrumentation amplifier in Figure 12-36?
6. Determine the approximate bandwidth of the amplifier in Figure 12-36 if the voltage gain is set to 10. Use the graph in Figure 12-6.
7. Specify what you must do to change the gain of the amplifier in Figure 12-36 to approximately 24.
8. Determine the value of R_G in Figure 12-36 for a voltage gain of 20.

 


FIGURE 12-35

 


FIGURE 12-36

SECTION 12-2 Isolation Amplifiers

9. The op-amp in the input stage of a certain isolation amplifier has a voltage gain of 30. The output stage is set for a gain of 10. What is the overall voltage gain of this device?
10. Determine the overall voltage gain of each 3656KG in Figure 12-37.

 


FIGURE 12-37

11. Specify how you would change the overall gain of the amplifier in Figure 12-37(a) to approximately 100 by changing only the gain of the input stage.
12. Specify how you would change the overall gain in Figure 12-37(b) to approximately 440 by changing only the gain of the output stage.
13. Specify how you would connect each amplifier in Figure 12-37 for unity gain.

SECTION 12-3 Operational Transconductance Amplifiers (OTAs)

14. A certain OTA has an input voltage of 10 mV and an output current of 10 μ A. What is the transconductance?
15. A certain OTA with a transconductance of 5000 μ S has a load resistance of 10 k Ω . If the input voltage is 100 mV, what is the output current? What is the output voltage?
16. The output voltage of a certain OTA with a load resistance is determined to be 3.5 V. If its transconductance is 4000 μ S and the input voltage is 100 mV, what is the value of the load resistance?
17. Determine the voltage gain of the OTA in Figure 12-38. Assume $K = 16 \mu$ S/ μ A for the graph in Figure 12-39.
18. If a 10 k Ω rheostat is added in series with the bias resistor in Figure 12-38, what are the minimum and maximum voltage gains?

 


FIGURE 12-38

 


FIGURE 12-39

19. The OTA in Figure 12–40 functions as an amplitude modulation circuit. Determine the output voltage waveform for the given input waveforms assuming $K = 16 \mu\text{S}/\mu\text{A}$.

 


FIGURE 12–40

20. Determine the trigger points for the Schmitt-trigger circuit in Figure 12–41.
21. Determine the output voltage waveform for the Schmitt trigger in Figure 12–41 in relation to a 1 kHz sine wave with peak values of $\pm 10 \text{ V}$.

 


FIGURE 12–41

SECTION 12–4 Log and Antilog Amplifiers

22. Using your calculator, find the natural logarithm (\ln) of each of the following numbers:
- 0.5
 - 2
 - 50
 - 130
23. Repeat Problem 22 for \log_{10} .
24. What is the antilog of 1.6?
25. Explain why the output of a log amplifier is limited to approximately 0.7 V.
26. What is the output voltage of a certain log amplifier with a diode in the feedback path when the input voltage is 3 V? The input resistor is $82 \text{ k}\Omega$ and the reverse leakage current is 100 nA.
27. Determine the output voltage for the amplifier in Figure 12–42. Assume $I_{EBO} = 60 \text{ nA}$.
28. Determine the output voltage for the amplifier in Figure 12–43. Assume $I_{EBO} = 60 \text{ nA}$.

 


FIGURE 12-42

 


FIGURE 12-43

29. Signal compression is one application of logarithmic amplifiers. Suppose an audio signal with a maximum voltage of 1 V and a minimum voltage of 100 mV is applied to the log amplifier in Figure 12-42. What will be the maximum and minimum output voltages? What conclusion can you draw from this result?

MULTISIM TROUBLESHOOTING PROBLEMS

MULTISIM



30. Open file P12-30 and determine the fault.
31. Open file P12-31 and determine the fault.
32. Open file P12-32 and determine the fault.
33. Open file P12-33 and determine the fault.

ANSWERS TO SECTION CHECKUPS

SECTION 12-1

1. The main purpose of an instrumentation amplifier is to amplify small signals that occur on large common-mode voltages. The key characteristics are high input impedance, high CMRR, low output impedance, and low output offset.
2. Three op-amps and seven resistors are required to construct a basic instrumentation amplifier (see Figure 12-2).
3. The gain is set by the external resistor R_G .
4. $A_v \cong 6$
5. A shield guard driver can reduce leakage current and reduce the effects of distributed capacitance between signal conductors and the shield.

SECTION 12-2

1. Isolation amplifiers are used in medical equipment, power plant instrumentation, industrial processing, and automated testing.
2. The two stages of an isolation amplifier are input and output.
3. The stages are connected by transformer coupling.
4. The oscillator acts as a dc to ac converter so that the dc power can be ac coupled to the input and output stages.
5. The third port sends isolated power to the input and output sides.

SECTION 12-3

1. OTA stands for operational transconductance amplifier.
2. Transconductance increases with bias current.
3. Assuming that the bias input is connected to the supply voltage, the voltage gain increases when the supply voltage is increased because this increases the bias current.
4. The gain decreases as the bias voltage decreases.

SECTION 12-4

1. A diode or transistor in the feedback loop provides the exponential (nonlinear) characteristic.
2. The output of a basic log amplifier is limited to the barrier potential of the pn junction (about 0.7 V).
3. The output voltage is determined by the input voltage, the input resistor, and the emitter-to-base leakage current.
4. The transistor in an antilog amplifier is in series with the input rather than in the feedback loop.
5. A multiplier is made of two log amplifiers, a summing amplifier, an antilog amplifier, and an inverting amplifier.
6. Each signal has been inverted three times in processing. A 4th inversion restores the sign.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

12-1 240 Ω

12-2 Make $R_G = 1.1 \text{ k}\Omega$.

12-3 Adding an output filter capacitor will attenuate the ripple.

12-4 Many combinations are possible. Here is one: $R_{f1} = 10 \text{ k}\Omega$, $R_{i1} = 1.0 \text{ k}\Omega$, $R_{f2} = 10 \text{ k}\Omega$, $R_{i2} = 1.0 \text{ k}\Omega$

12-5 62.5 μA . Note the scale is logarithmic.

12-6 Yes. Approximately 110.

12-7 $V_{out(max)} = 3.61 \text{ V}$; $V_{out(min)} = 1.76 \text{ V}$

12-8 -0.167 V

12-9 -0.193 V

12-10 -4.4 V

ANSWERS TO SELF-TEST

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (d) | 2. (b) | 3. (a) | 4. (e) | 5. (c) |
| 6. (b) | 7. (a) | 8. (c) | 9. (d) | 10. (c) |
| 11. (a) | 12. (b) | 13. (f) | 14. (b) | 15. (b) |

ANSWERS TO TROUBLESHOOTER'S QUIZ

- | | | | | |
|-------------|---------------|-------------|-------------|--------------|
| 1. increase | 2. decrease | 3. decrease | 4. increase | 5. decrease |
| 6. decrease | 7. not change | 8. increase | 9. decrease | 10. increase |

CHAPTER 13

COMMUNICATIONS CIRCUITS

OUTLINE

- 13-1 Basic Receivers
- 13-2 The Linear Multiplier
- 13-3 Amplitude Modulation
- 13-4 The Mixer
- 13-5 AM Demodulation
- 13-6 IF and Audio Amplifiers
- 13-7 Frequency Modulation
- 13-8 The Phase-Locked Loop (PLL)
- 13-9 Fiber Optics

OBJECTIVES

- Describe basic superheterodyne receivers
- Discuss the function of a linear multiplier
- Discuss the fundamentals of amplitude modulation
- Discuss the basic function of a mixer
- Describe AM demodulation
- Describe IF and audio amplifiers
- Describe frequency modulation
- Describe the phase-locked loop (PLL)
- Discuss fiber optics

KEY TERMS

Amplitude modulation (AM)

Frequency modulation (FM)

Four-quadrant multiplier

Balanced modulation Mixer

Voltage-controlled oscillator (VCO)

Phase-locked loop (PLL)

Modem

Fiber optics

Critical angle

INTRODUCTION

Communications electronics encompasses a wide range of systems, including both analog (linear) and digital. Any system that sends information from one point to another over relatively long distances can be classified as a communications system. Some of the categories of communications systems are radio (broadcast, ham, CB, marine), television, telephony, radar, navigation, satellite, data (digital), and telemetry.

Many communications systems use either amplitude modulation (AM) or frequency modulation (FM) to send information. Other modulation methods include pulse modulation, phase modulation, and frequency shift keying (FSK) as well as more specialized techniques. By necessity, the scope of this chapter is limited and is intended to introduce you to basic AM and FM communications systems and circuits and to fiber optics.

VISIT THE WEBSITE

Study aids for this chapter are available at

<http://pearsonhighered.com/floyd>

13–1 BASIC RECEIVERS

Receivers based on the superheterodyne principle are standard in one form or another in most types of analog communications systems and are found in familiar systems such as standard broadcast radio, stereo, and television. This section provides a basic introduction to amplitude modulation and frequency modulation and an overview of the complete AM and FM receiver.

After completing this section, you should be able to

- Describe basic superheterodyne receivers
- Define *AM* and *FM*
- Discuss the major functional blocks of an AM receiver
- Discuss the major functional blocks of an FM receiver

Amplitude Modulation (AM)

Amplitude modulation (AM) is a method for sending audible information, such as voice and music, by electromagnetic waves that are broadcast through the atmosphere. In AM, the amplitude of a signal with a specific frequency (f_c), called the *carrier*, is varied according to a modulating signal, which can be an audio signal (such as voice or music), as shown in Figure 13–1. The carrier frequency permits the receiver to be tuned to a specific known frequency. The resulting AM waveform contains the carrier frequency, an upper-side frequency equal to the carrier frequency plus the modulation frequency ($f_c + f_m$), and a lower-side frequency equal to the carrier frequency minus the modulation frequency ($f_c - f_m$). Harmonics of these frequencies are also present. For example, if a 1 MHz carrier is amplitude modulated with a 5 kHz audio signal, the frequency components in the AM waveform are 1 MHz (carrier), $1\text{ MHz} + 5\text{ kHz} = 1,005,000\text{ Hz}$ (upper side), and $1\text{ MHz} - 5\text{ kHz} = 995,000\text{ Hz}$ (lower side).

 


FIGURE 13–1 An example of an amplitude modulated signal. In this case, the higher-frequency carrier is modulated by a lower-frequency sinusoidal signal.

The frequency band for AM broadcast receivers is 540 kHz to 1640 kHz. This means that an AM receiver can be tuned to pick up a specific carrier frequency that lies in the broadcast band. Each AM radio station transmits at a specific carrier frequency that is different from any other station in the area, so you can tune the receiver to pick up any desired station.

The Superheterodyne AM Receiver

A block diagram of a superheterodyne AM receiver is shown in Figure 13–2. The receiver shown consists of an antenna, an RF (radio frequency) amplifier, a mixer, a local oscillator

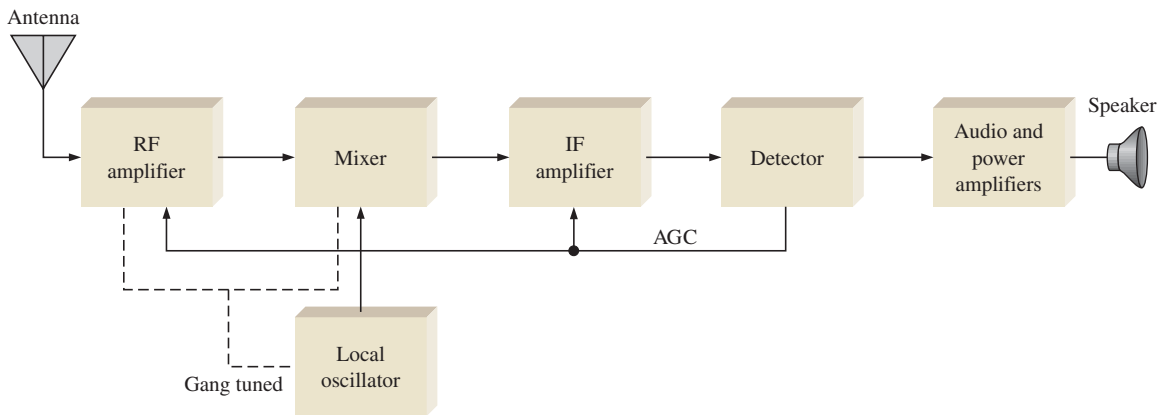


FIGURE 13-2 Superheterodyne AM receiver block diagram.

(LO), an IF (intermediate frequency) amplifier, a detector, an audio amplifier and a power amplifier, and a speaker.

ANTENNA The antenna picks up all radiated signals and feeds them into the RF amplifier. These signals are very small (usually only a few microvolts).

RF AMPLIFIER This circuit can be adjusted (tuned) to select and amplify any frequency within the AM broadcast band. Only the selected frequency and its two side bands pass through the amplifier. (Some AM receivers do not have a separate RF amplifier stage.)

LOCAL OSCILLATOR This circuit generates a steady sine wave at a frequency 455 kHz above the selected RF frequency.

MIXER This circuit accepts two inputs, the amplitude modulated RF signal from the output of the RF amplifier (or the antenna when there is no RF amplifier) and the sinusoidal output of the local oscillator. These two signals are then “mixed” by a nonlinear process called *heterodyning* to produce sum and difference frequencies. For example, if the RF carrier has a frequency of 1000 kHz, the LO frequency is 1455 kHz and the sum and difference frequencies out of the mixer are 2455 kHz and 455 kHz, respectively. The difference frequency is always 455 kHz no matter what the RF carrier frequency.

IF AMPLIFIER The input to the IF amplifier is the 455 kHz AM signal, a replica of the original AM carrier signal except that the frequency has been lowered to 455 kHz. The IF amplifier significantly increases the level of this signal.

DETECTOR This circuit recovers the modulating signal (audio signal) from the 455 kHz IF. At this point the IF is no longer needed, so the output of the detector consists of only the audio signal.

AUDIO AND POWER AMPLIFIERS This circuit amplifies the detected audio signal and drives the speaker to produce sound.

AGC The automatic gain control (AGC) provides a dc level out of the detector that is proportional to the strength of the received signal. This level is fed back to the IF amplifier, and sometimes to the mixer and RF amplifier, to adjust the gains and thus maintain constant signal levels throughout the system over a wide range of incoming carrier signal strengths.

SYSTEM EXAMPLE 13–1



AM RECEIVER SIGNAL FLOW

Figure SE13–1 shows the signal flow through an AM superheterodyne receiver. The receiver can be tuned to accept any frequency in the AM band. The RF amplifier, mixer, and local oscillator are tuned simultaneously so that the LO frequency is always 455 kHz above the incoming RF signal frequency. This is called *gang tuning*.


 


FIGURE SE13–1

Frequency Modulation (FM)

In this method of **modulation**, the modulating signal (audio) varies the frequency of a carrier as opposed to the amplitude, as in the case of AM. Figure 13–3 illustrates basic **frequency modulation (FM)**. The standard FM broadcast band consists of carrier frequencies from

FIGURE 13–3 An example of frequency modulation.

 

88 MHz to 108 MHz, which is significantly higher than AM. The FM receiver is similar to the AM receiver in many ways, but there are several differences.

The Superheterodyne FM Receiver

A block diagram of a superheterodyne FM receiver is shown in Figure 13-4. Notice that it includes an RF amplifier, mixer, local oscillator, and IF amplifier just as in the AM receiver. These circuits must operate, however, at higher frequencies than in the AM system. A significant difference in FM is the way the audio signal must be recovered from the modulated IF. This is accomplished by the limiter, discriminator, and de-emphasis network.

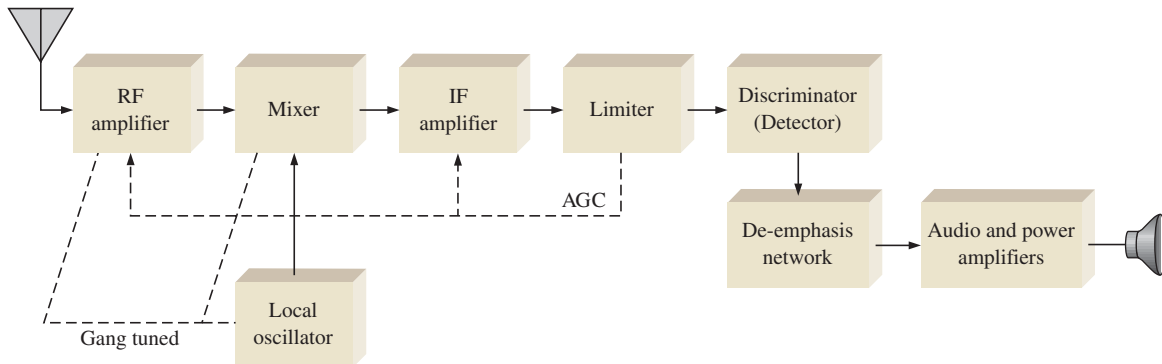


FIGURE 13-4 Superheterodyne FM receiver block diagram.

RF AMPLIFIER This circuit must be capable of amplifying any frequency between 88 MHz and 108 MHz. It is highly selective so that it passes only the selected carrier frequency and significant side-band frequencies that contain the **audio**.

LOCAL OSCILLATOR This circuit produces a sine wave at a frequency 10.7 MHz above the selected RF frequency.

MIXER This circuit performs the same function as in the AM receiver, except that its output is a 10.7 MHz FM signal regardless of the RF carrier frequency.

IF AMPLIFIER This circuit amplifies the 10.7 MHz FM signal.

LIMITER The limiter removes any unwanted variations in the amplitude of the FM signal as it comes out of the IF amplifier and produces a constant amplitude FM output at the 10.7 MHz intermediate frequency.

DISCRIMINATOR This circuit performs the equivalent function of the detector in an AM system and is often called a detector rather than a discriminator. The **discriminator** recovers the audio from the FM signal.

DE-EMPHASIS NETWORK For certain reasons, the higher modulating frequencies are amplified more than the lower frequencies at the transmitting end of an FM system by a process called *preemphasis*. The de-emphasis circuit in the FM receiver brings the high-frequency audio signals back to the proper amplitude relationship with the lower frequencies.

AUDIO AND POWER AMPLIFIERS This circuit is the same as in the AM system and can be shared when there is a dual AM/FM configuration.

SYSTEM EXAMPLE 13–2



FM RECEIVER SIGNAL FLOW

Figure SE13–2 shows the signal flow through an FM superheterodyne receiver. The receiver can be tuned to accept any frequency in the FM band. The RF amplifier, mixer, and local oscillator are tuned simultaneously so that the LO frequency is always 10.7 MHz above the incoming RF signal frequency.

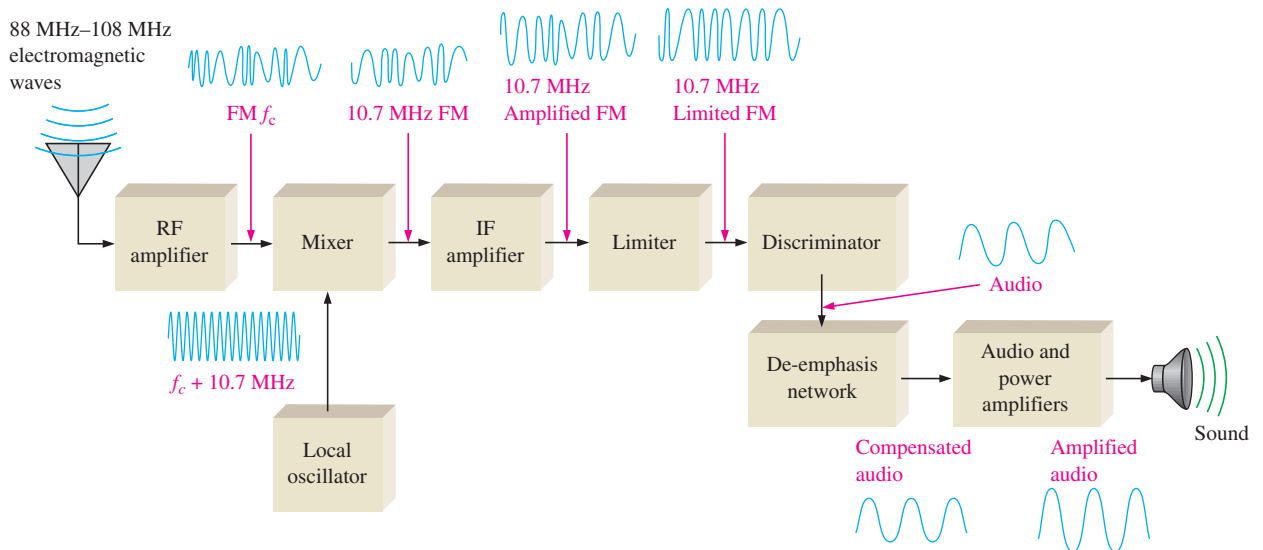


FIGURE SE13–2

SECTION 13–1 CHECKUP*

1. What do *AM* and *FM* mean?
2. How do *AM* and *FM* differ?
3. What are the standard broadcast frequency bands for *AM* and *FM*?

*Answers are at the end of the chapter.

13–2 THE LINEAR MULTIPLIER

The linear multiplier is a key circuit in many types of communications systems. In this section, you will examine the basic principles of IC linear multipliers. In the following sections, we will concentrate on multiplier applications in *AM* and *FM* systems.

After completing this section, you should be able to

- Discuss the function of a linear multiplier
- Describe multiplier quadrants
- Discuss linear multiplier scale factor
- Discuss the transfer function of a linear multiplier

Multiplier Quadrants

There are one-quadrant, two-quadrant, and **four-quadrant multipliers**. The quadrant classification indicates the number of input polarity combinations that the multiplier can handle. A graphical representation of the quadrants is shown in Figure 13-5. A four-quadrant multiplier can accept any of the four possible input polarity combinations and produce an output with the corresponding polarity.

 


FIGURE 13-5 Four-quadrant polarities and their products.

The AD532 Linear Multiplier

Modern linear multiplier ICs like the AD532 contain all of the components necessary to multiply two input signals. Refer to the AD532 block diagram shown in Figure 13-6. As you can see, the X and Y inputs can be viewed as differential inputs to two operational amplifiers. These inputs can also be connected single-ended simply by connecting one of the X or Y inputs to ground.

 


FIGURE 13-6 Block diagram of an AD532 linear multiplier IC.

All resistors are laser-trimmed thin-film components deposited directly on the substrate of the chip. This results in multiplication accuracy of up to $\pm 1\%$ at full scale. In older linear multiplier ICs external resistors were required. This resulted in more complex circuitry with the associated larger footprint, higher current draw and lower efficiency, and increased noise.

The input op-amps are connected to the multiplier cell where the product of the inputs is generated. Depending on the magnitude of the inputs, and how they are connected to the inverting and noninverting inputs, either a positive or negative output can be achieved. Also note the output op-amp. Again, in older linear multipliers external op-amps were often required. The on-board output op-amp provides low output impedance, allowing the multiplier to drive low-impedance loads.

Transfer Function and Scale Factor

The *transfer function* for a linear multiplier defines the output signal for a given set of inputs. For the AD532 the transfer function is

$$V_{out} = \frac{(X_1 - X_2)(Y_1 - Y_2)}{10 \text{ V}}$$

Note the 10 V value in the denominator of the transfer function. This value is referred to as the *scale factor* (SF) for the device. As you can imagine, multiplying voltages can result in large magnitudes, so a scale factor is built into each linear multiplier to allow for larger magnitude inputs. In some literature you will see the scale factor represented by the letter K and stated as the inverse of SF. For the AD532, $K = 0.1$, so the output will be one-tenth the product of the inputs. An SF value of 10 V ($K = 0.1$) is a very common value for linear multipliers.

Connecting the AD532 as a Multiplier

Figure 13–7 shows the pin-out for the AD532 in a 14-pin DIP package. It is also available in a 20-lead leadless chip carrier package. Figure 13–8 shows how the AD532 should be connected so that it operates as a linear multiplier. First of all note that the Z input is connected to the output. Referring back to Figure 13–6 you can see that this closes the feedback loop of the output op-amp.

 


FIGURE 13–7 14-pin DIP pin-out for the AD532.

 


FIGURE 13–8 AD532 multiplier connection.

Also note the potentiometer connected between the supply inputs, with its wiper connected to the V_{OS} input. This is an optional connection and is used to compensate for any possible output offset. The device is laser-trimmed for a 0 V offset during production, so in many cases a compensation circuit is not necessary. For precision work, all inputs are grounded and the compensation potentiometer is adjusted so that the output is 0 V. It can also be used to compensate for offsets introduced by other components in the system. When a compensation network is not required, the V_{OS} pin is tied to ground.

The AD532 is a four-quadrant multiplier so any combination of input polarities can be accepted. Its inputs can be connected single-ended or as differential inputs, and the output can be either a positive or negative value. These characteristics are illustrated in the following examples.

EXAMPLE 13-1

Assume an AD532 is connected as a multiplier. The inputs are $X_1 = 3\text{ V}$, $X_2 = 1.4\text{ V}$, and $Y_1 = 5.3\text{ V}$, and $Y_2 = 1.8\text{ V}$. Determine the output voltage.

SOLUTION

The output voltage is found as

$$V_{out} = \frac{(X_1 - X_2)(Y_1 - Y_2)}{10\text{ V}} = \frac{(3\text{ V} - 1.4\text{ V})(5.3\text{ V} - 1.8\text{ V})}{10\text{ V}} = \frac{5.6\text{ V}^2}{10\text{ V}} = 560\text{ mV}$$

PRACTICE EXERCISE*

Find V_{OUT} if all the inputs in Example 13-1 have their polarity reversed.

*Answers are at the end of the chapter.

EXAMPLE 13-2

Assume an AD532 is connected as a multiplier and the inputs are single-ended. $X_1 = 4.15\text{ V}$ and $Y_1 = -1.51\text{ V}$. Determine the output voltage.

SOLUTION

The output voltage is found as

$$V_{out} = \frac{(X_1 - 0\text{ V})(Y_1 - 0\text{ V})}{10\text{ V}} = \frac{(4.15\text{ V})(-1.51\text{ V})}{10\text{ V}} = \frac{-6.27\text{ V}^2}{10\text{ V}} = -627\text{ mV}$$

PRACTICE EXERCISE

Find V_{OUT} if the Y_1 input is grounded and -1.51 V is applied to Y_2 .

Other Multiplier Applications

The focus of this chapter is on AM and FM communication systems. In later sections you will be shown how the linear multiplier is an important component in modulation, demodulation, and mixer circuits. In all of these applications it is configured as a multiplier, but these devices have other applications, especially in instrumentation. The AD532 can also be configured as a two-quadrant divider, a squaring circuit, a square root circuit, and a difference of squares circuit. A full discussion of these applications is beyond the scope of this text, but more information on these circuits, and the spec sheet for the AD532, can be found at www.analog.com.

SECTION 13-2 CHECKUP

1. Compare a four-quadrant multiplier to a one-quadrant multiplier in terms of the inputs that can be handled.
2. What does SF stand for and what is its value for the AD532?
3. What does the transfer function of a linear multiplier define?

13–3 AMPLITUDE MODULATION

Amplitude modulation (AM) is an important method for transmitting information. Of course, the AM superheterodyne receiver is designed to receive transmitted AM signals. In this section, we further define amplitude modulation and show how the linear multiplier can be used as an amplitude-modulated device.

After completing this section, you should be able to

- Discuss the fundamentals of amplitude modulation
- Explain how AM is basically a multiplication process
- Describe sum and difference frequencies
- Discuss balanced modulation
- Describe the frequency spectra
- Explain standard AM

As you learned in Section 13–1, amplitude modulation is the process of varying the amplitude of a signal of a given frequency (carrier) with another signal of much lower frequency (modulating signal). One reason that the higher-frequency carrier signal is necessary is because audio or other signals with relatively low frequencies cannot be transmitted with antennas of a practical size. The basic concept of standard amplitude modulation is illustrated in Figure 13–9.

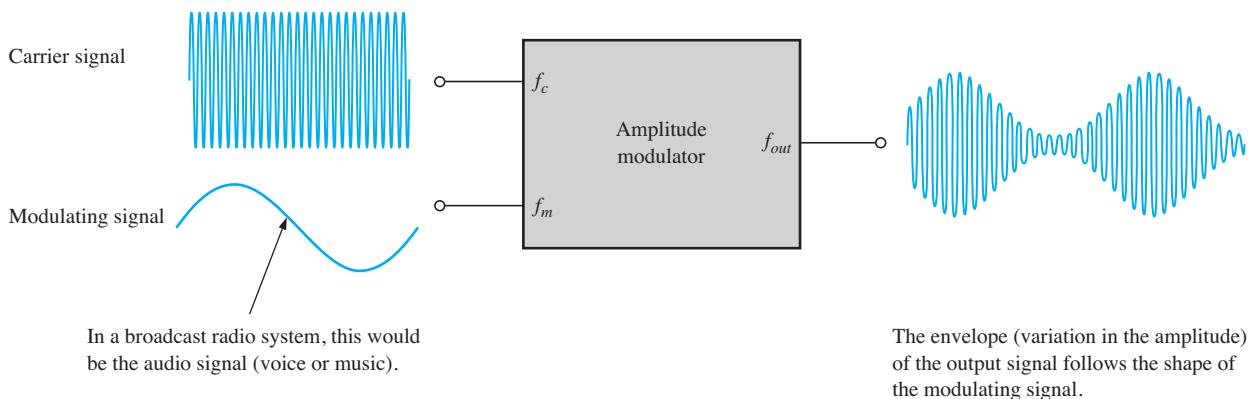


FIGURE 13–9 Basic concept of amplitude modulation.

A Multiplication Process

If a signal is applied to the input of a variable-gain device, the resulting output is an amplitude-modulated signal because $V_{out} = A_v V_{in}$. The output voltage is the input voltage multiplied by the voltage gain. For example, if the gain of an amplifier is made to vary sinusoidally at a certain frequency and an input signal is applied at a higher frequency, the output signal will have the higher frequency. However, its amplitude will vary according to the variation in gain as illustrated in Figure 13–10. Amplitude modulation is basically a multiplication process (input voltage multiplied by a variable gain).

Sum and Difference Frequencies

If the expressions for two sinusoidal signals of different frequencies are multiplied mathematically, a term containing both the difference and the sum of the two frequencies is produced. Recall from ac circuit theory that a sinusoidal voltage can be expressed as

$$v = V_p \sin 2\pi ft$$

 


FIGURE 13-10 The amplitude of the output voltage varies according to the gain and is the product of voltage gain and input voltage.

where V_p is the peak voltage and f is the frequency. Two different sinusoidal signals can be expressed as follows:

$$v_1 = V_{1(p)} \sin 2\pi f_1 t$$

$$v_2 = V_{2(p)} \sin 2\pi f_2 t$$

Multiplying these two sinusoidal wave terms,

$$\begin{aligned} v_1 v_2 &= (V_{1(p)} \sin 2\pi f_1 t)(V_{2(p)} \sin 2\pi f_2 t) \\ &= V_{1(p)} V_{2(p)} (\sin 2\pi f_1 t)(\sin 2\pi f_2 t) \end{aligned}$$

The basic trigonometric identity for the product of two sinusoidal functions is

$$(\sin A)(\sin B) = \frac{1}{2} [\cos(A - B) - \cos(A + B)]$$

Applying this identity to the previous formula for $v_1 v_2$,

$$\begin{aligned} v_1 v_2 &= \frac{V_{1(p)} V_{2(p)}}{2} [(\cos 2\pi f_1 t - 2\pi f_2 t) - (\cos 2\pi f_1 t + 2\pi f_2 t)] \\ &= \frac{V_{1(p)} V_{2(p)}}{2} [(\cos 2\pi(f_1 - f_2)t) - (\cos 2\pi(f_1 + f_2)t)] \end{aligned}$$

$$v_1 v_2 = \frac{V_{1(p)} V_{2(p)}}{2} \cos 2\pi(f_1 - f_2)t - \frac{V_{1(p)} V_{2(p)}}{2} \cos 2\pi(f_1 + f_2)t \quad (13-1)$$

You can see in Equation (13-1) that the product of the two sinusoidal voltages V_1 and V_2 contains a difference frequency ($f_1 - f_2$) and a sum frequency ($f_1 + f_2$). The fact that the product terms are cosine simply indicates a 90° phase shift in the multiplication process.

Balanced Modulation

Since amplitude modulation is simply a multiplication process, the preceding analysis is now applied to carrier and modulating signals. The expression for the sinusoidal carrier signal can be written as

$$v_c = V_{c(p)} \sin 2\pi f_c t$$

Assuming a sinusoidal modulating signal, it can be expressed as

$$v_m = V_{m(p)} \sin 2\pi f_m t$$

Substituting these two signals in Equation (13–1),

$$v_c v_m = \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi(f_c - f_m)t - \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi(f_c + f_m)t$$

An output signal described by this expression for the product of two sinusoidal signals is produced by a linear multiplier. Notice that there is a difference frequency term ($f_c - f_m$) and a sum frequency term ($f_c + f_m$), but the original frequencies, f_c and f_m , do not appear alone in the expression. Thus, the product of two sinusoidal signals contains no signal with the carrier frequency, f_c , or with the modulating frequency, f_m . This form of amplitude modulation is called **balanced modulation** because there is no carrier frequency in the output. The carrier frequency is “balanced out.”

The Frequency Spectra of a Balanced Modulator

A graphical picture of the frequency content of a signal is called its frequency spectrum (see Sec. 1–2). A frequency spectrum shows voltage on a frequency base rather than on a time base as a waveform diagram does. The frequency spectra of the product of two sinusoidal signals are shown in Figure 13–11. Part (a) shows the two input frequencies and part (b) shows the output frequencies. In communications terminology, the sum frequency is called the *upper-side frequency* and the difference frequency is called the *lower-side frequency* because the frequencies appear on each side of the missing carrier frequency.

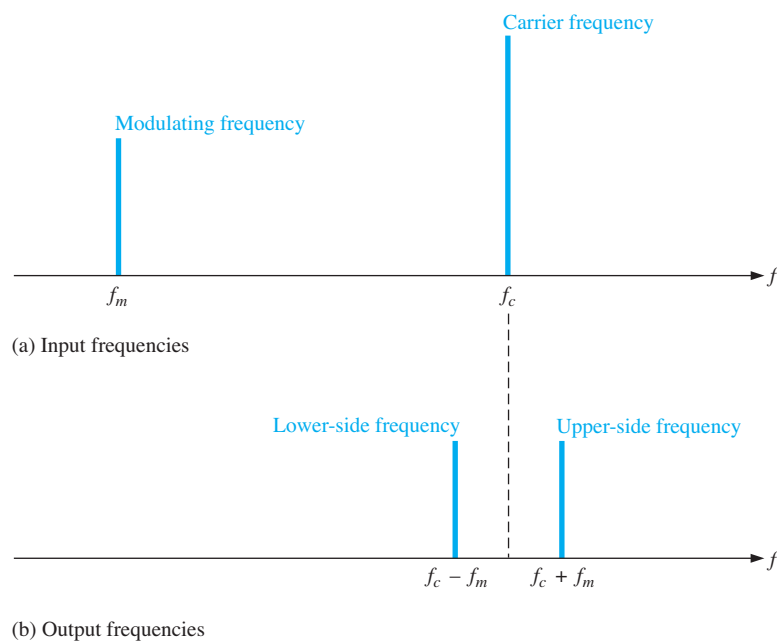


FIGURE 13–11 Illustration of the input and output frequency spectra for a linear multiplier.

The Linear Multiplier as a Balanced Modulator

As mentioned, the linear multiplier acts as a balanced modulator when a carrier signal and a modulating signal are applied to its inputs, as illustrated in Figure 13–12. A balanced modulator produces an upper-side frequency and a lower-side frequency, but it does not produce a carrier frequency. Since there is no carrier signal, balanced modulation is sometimes known as *suppressed-carrier modulation*. Balanced modulation is used in certain types of communications such as single side-band systems, but it is not used in standard AM broadcast systems.

 


FIGURE 13-12 The linear multiplier as a balanced modulator.

EXAMPLE 13-3

Determine the frequencies contained in the output signal of the balanced modulator in Figure 13-13.

 


FIGURE 13-13

SOLUTION

The upper-side frequency is

$$f_c + f_m = 5 \text{ MHz} + 10 \text{ kHz} = \mathbf{5.01 \text{ MHz}}$$

The lower-side frequency is

$$f_c - f_m = 5 \text{ MHz} - 10 \text{ kHz} = \mathbf{4.99 \text{ MHz}}$$

PRACTICE EXERCISE

Explain how the separation between the side frequencies can be increased using the same carrier frequency.

Standard Amplitude Modulation (AM)

In standard AM systems, the output signal contains the carrier frequency as well as the sum and difference side frequencies. Standard amplitude modulation is illustrated by the frequency spectrum in Figure 13-14.

 


FIGURE 13-14 The output frequency spectrum of a standard amplitude modulator.

The expression for a standard amplitude-modulated signal is

$$V_{out} = V_{c(p)}^2 \sin 2\pi f_c t + \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi (f_c - f_m) t - \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi (f_c + f_m) t$$

Notice in Equation (13–2) that the first term is for the carrier frequency and the other two terms are for the side frequencies. Let's see how the carrier-frequency term gets into the equation.

If a dc voltage equal to the peak of the carrier voltage is added to the modulating signal before the modulating signal is multiplied by the carrier signal, a carrier-signal term appears in the final result as shown in the following steps. Add the peak carrier voltage to the modulating signal, and you get the following expression:

$$V_{c(p)} + V_{m(p)}\sin 2\pi f_m t$$

Multiply by the carrier signal.

$$\begin{aligned} V_{out} &= (V_{c(p)}\sin 2\pi f_c t)(V_{c(p)} + V_{m(p)}\sin 2\pi f_m t) \\ &= \underbrace{V_{c(p)}^2\sin 2\pi f_c t}_{\text{carrier term}} + \underbrace{V_{c(p)}V_{m(p)}(\sin 2\pi f_c t)(\sin 2\pi f_m t)}_{\text{product term}} \end{aligned}$$

Apply the basic trigonometric identity to the product term.

$$V_{out} = V_{c(p)}^2\sin 2\pi f_c t + \frac{V_{c(p)}V_{m(p)}}{2}\cos 2\pi(f_c - f_m)t - \frac{V_{c(p)}V_{m(p)}}{2}\cos 2\pi(f_c + f_m)t$$

This result shows that the output of the multiplier contains a carrier term and two side-frequency terms. Figure 13–15 illustrates how a standard amplitude modulator can be implemented by a summing circuit followed by a linear multiplier. Figure 13–16 shows a possible implementation of the summing circuit.

 


FIGURE 13–15 Basic block diagram of an amplitude modulator.

 


FIGURE 13–16 Implementation of the summing circuit in the amplitude modulator.

EXAMPLE 13–4

A carrier frequency of 1200 kHz is modulated by a sinusoidal wave with a frequency of 25 kHz by a standard amplitude modulator. Determine the output frequency spectrum.

SOLUTION

The lower-side frequency is

$$f_c - f_m = 1200 \text{ kHz} - 25 \text{ kHz} = \mathbf{1175 \text{ kHz}}$$

The upper-side frequency is

$$f_c + f_m = 1200 \text{ kHz} + 25 \text{ kHz} = \mathbf{1225 \text{ kHz}}$$

The output contains the carrier frequency and the two side frequencies as shown in Figure 13-17.

 


FIGURE 13-17

PRACTICE EXERCISE

Compare the output frequency spectrum in this example to that of a balanced modulator having the same inputs.

Amplitude Modulation with Voice or Music

To this point in our discussion, we have considered the modulating signal to be a pure sinusoidal signal just to keep things fairly simple. If you receive an AM signal modulated by a pure sinusoidal signal in the audio frequency range, you will hear a single tone from the receiver's speaker.

A voice or music signal consists of many sinusoidal components within a range of frequencies from about 20 Hz to 20 kHz. For example, if a carrier frequency is amplitude modulated with voice or music with frequencies from 100 Hz to 10 kHz, the frequency spectrum is as shown in Figure 13-18. Instead of one lower-side and one upper-side frequency, as in the case of a single-frequency modulating signal, a band of lower-side frequencies, and a band of upper-side frequencies correspond to the sum and difference frequencies of each sinusoidal component of the voice or music signal.

 


FIGURE 13-18 Example of a frequency spectrum for a voice or music signal.

SECTION 13–3 CHECKUP

1. What is amplitude modulation?
2. What is the difference between balanced modulation and standard AM?
3. What two input signals are used in amplitude modulation? Explain the purpose of each signal.
4. What are the upper-side frequency and the lower-side frequency?
5. How can a balanced modulator be changed to a standard amplitude modulator?

13–4 THE MIXER

The mixer in the receiver system discussed in Section 13–1 can be implemented with a linear multiplier as you will see in this section. The basic principles of linear multiplication of sinusoidal signals are covered, and you will see how sum and difference frequencies are produced. The difference frequency is a critical part of the operation of many types of receiver systems.

After completing this section, you should be able to

- Discuss the basic function of a mixer
- Explain why a mixer is a linear multiplier
- Describe the frequencies in the mixer and IF portion of a receiver

The **mixer** is basically a frequency converter because it changes the frequency of a signal to another value. The mixer in a receiver system takes the incoming modulated RF signal (which is sometimes amplified by an RF amplifier and sometimes not) along with the signal from the local oscillator and produces a modulated signal with a frequency equal to the difference of its two input frequencies (RF and LO). The mixer also produces a frequency equal to the sum of the input frequencies. The mixer function is illustrated in Figure 13–19.

 


FIGURE 13–19 The mixer function.

The Mixer Is a Linear Multiplier

In the case of receiver applications, the mixer must produce an output that has a frequency component equal to the difference of its input frequencies. From the mathematical analysis in Section 13–3, you can see that if two sinusoidal signals are multiplied, the product contains the difference frequency and the sum frequency. Thus, the mixer is actually a linear multiplier as indicated in Figure 13–20.

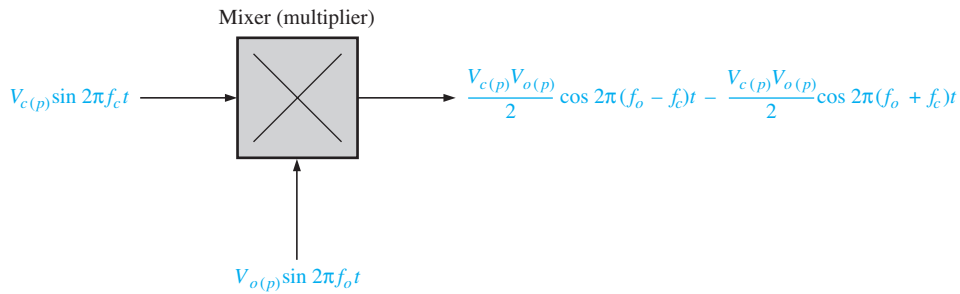


FIGURE 13-20 The mixer as a linear multiplier.

EXAMPLE 13-5

Determine the output expression for a multiplier with one sinusoidal input having a peak voltage of 5 mV and a frequency of 1200 kHz and the other input having a peak voltage of 10 mV and a frequency of 1655 kHz.

SOLUTION

The two input expressions are

$$v_1 = (5 \text{ mV})\sin 2\pi(1200 \text{ kHz})t$$

$$v_2 = (10 \text{ mV})\sin 2\pi(1655 \text{ kHz})t$$

Multiplying,

$$v_1v_2 = (5 \text{ mV})(10 \text{ mV})[\sin 2\pi(1200 \text{ kHz})t][\sin 2\pi(1655 \text{ kHz})t]$$

Applying the trigonometric identity, $(\sin A)(\sin B) = \frac{1}{2}[\cos(A - B) - \cos(A + B)]$,

$$V_{out} = \frac{(5 \text{ mV})(10 \text{ mV})}{2} \cos 2\pi(1655 \text{ kHz} - 1200 \text{ kHz})t \\ - \frac{(5 \text{ mV})(10 \text{ mV})}{2} \cos 2\pi(1655 \text{ kHz} + 1200 \text{ kHz})t$$

$$V_{out} = (25 \mu\text{V})\cos 2\pi(455 \text{ kHz})t - (25 \mu\text{V})\cos 2\pi(2855 \text{ kHz})t$$

PRACTICE EXERCISE

What is the value of the peak amplitude and frequency of the difference frequency component in this example?

In the receiver system, both the sum and difference frequencies from the mixer are applied to the IF (intermediate frequency) amplifier. The IF amplifier is actually a tuned amplifier that is designed to respond to the difference frequency while rejecting the sum frequency. You can think of the IF amplifier section of a receiver as a band-pass filter plus an amplifier because it uses resonant circuits to provide the frequency selectivity. This is illustrated in Figure 13-21.

 
 


FIGURE 13-21 Example of frequencies in the mixer and IF portion of a receiver.

EXAMPLE 13–6

Determine the output frequency of the IF amplifier for the conditions shown in Figure 13–22.

**FIGURE 13–22****SOLUTION**

The IF amplifier produces only the difference frequency signal on its output.

$$f_{out} = f_{diff} = f_o - f_c = 1035 \text{ kHz} - 580 \text{ kHz} = \mathbf{455 \text{ kHz}}$$

PRACTICE EXERCISE

Based on your basic knowledge of the superheterodyne receiver from Section 13–1, determine the IF output frequency when the incoming RF signal changes to 1550 kHz.

SECTION 13–4 CHECKUP

1. What is the purpose of the mixer in a superheterodyne receiver?
2. How does the mixer produce its output?
3. If a mixer has 1000 kHz on one input and 350 kHz on the other, what frequencies appear on the output?

13–5 AM DEMODULATION

The linear multiplier can be used to demodulate or detect an AM signal as well as to perform the modulation process that was discussed in Section 13–3. *Demodulation* can be thought of as reverse modulation. The purpose is to get back the original modulating signal (voice or music in the case of standard AM receivers). The detector in the AM receiver can be implemented using a multiplier, although another method using peak envelope detection is common.

After completing this section, you should be able to

- Describe AM demodulation
- Discuss a basic AM demodulator
- Discuss the frequency spectra

The Basic AM Demodulator

An AM demodulator can be implemented with a linear multiplier followed by a low-pass filter, as shown in Figure 13–23. The critical frequency of the filter is the highest audio frequency that is required for a given application (15 kHz, for example).

 


FIGURE 13-23 Basic AM demodulator.

Operation in Terms of the Frequency Spectra

Let's assume a carrier modulated by a single tone with a frequency of 10 kHz is received and converted to a modulated intermediate frequency of 455 kHz, as indicated by the frequency spectra in Figure 13-24. Notice that the upper-side and lower-side frequencies are separated from both the carrier and the IF by 10 kHz.

 


FIGURE 13-24 An AM signal converted to IF.

When the modulated output of the IF amplifier is applied to the demodulator along with the IF, sum and difference frequencies for each input frequency are produced as shown in Figure 13-25. Only the 10 kHz audio frequency is passed by the filter. A drawback to this type of AM detection is that a pure IF must be produced to mix with the modulated IF.

 


FIGURE 13-25 Example of demodulation.

SECTION 13-5 CHECKUP

1. What is the purpose of the filter in the linear multiplier demodulator?
2. If a 455 kHz IF modulated by a 1 kHz audio frequency is demodulated, what frequency or frequencies appear on the output of the demodulator?

13–6 IF AND AUDIO AMPLIFIERS

In this section, IC amplifiers for intermediate and audio frequencies are introduced. As you have learned, the IF amplifier in a communications receiver provides amplification of the modulated IF signal out of the mixer before it is applied to the detector. After the audio signal is recovered by the detector, it goes to the audio preamp where it is amplified and applied to the power amplifier that drives the speaker.

After completing this section, you should be able to

- Describe IF and audio amplifiers
- Discuss the function of an IF amplifier
- Explain how the local oscillator and mixer operate with the IF amplifier
- State the purpose of the audio amplifier
- Discuss the LM386 audio power amplifier

The Basic Function of the IF Amplifier

The IF amplifier in a receiver is a tuned amplifier with a specified bandwidth operating at a center frequency of 455 kHz for AM and 10.7 MHz for FM. The IF amplifier is one of the key features of a superheterodyne receiver because it is set to operate at a single resonant frequency that remains the same over the entire band of carrier frequencies that can be received. Figure 13–26 illustrates the basic function of an IF amplifier in terms of the frequency spectra.

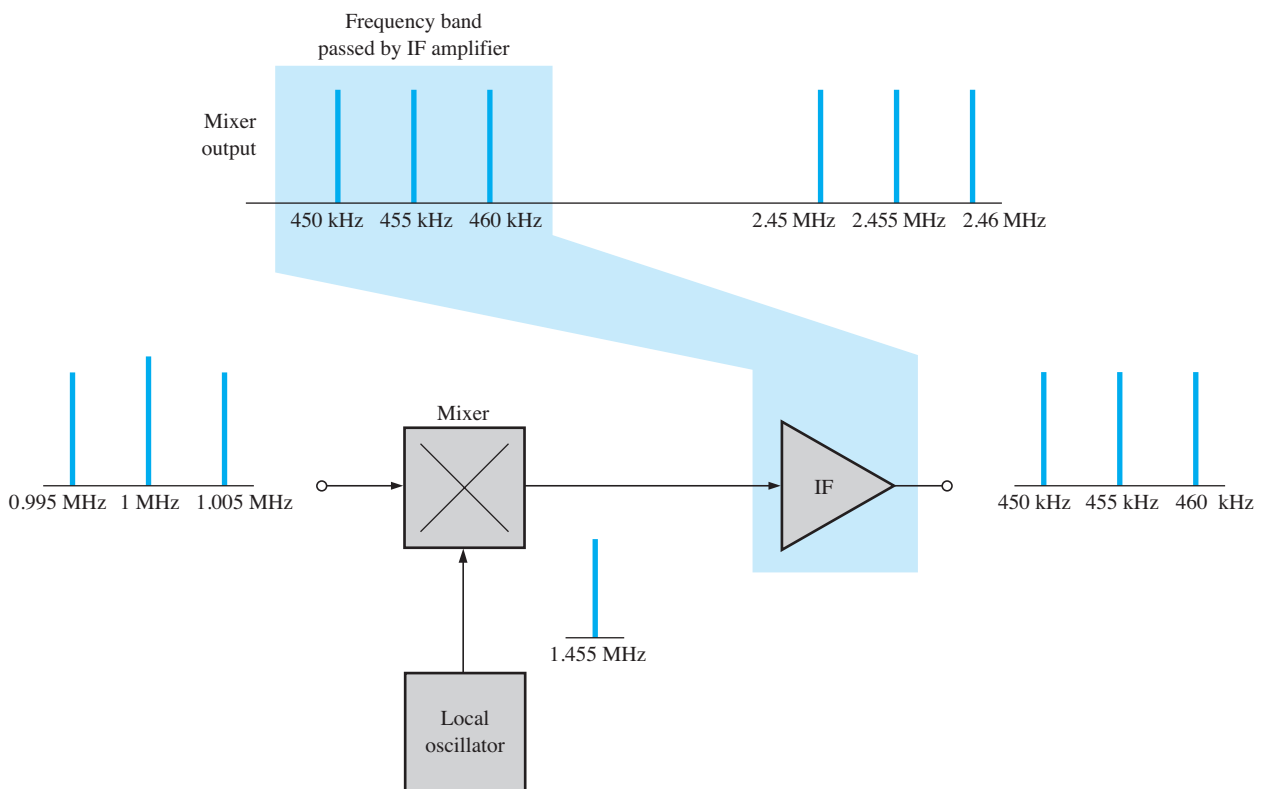


FIGURE 13–26 An illustration of the basic function of the IF amplifier in an AM receiver.

Assume, for example, that the received carrier frequency of $f_c = 1$ MHz is modulated by an audio signal with a maximum frequency of $f_m = 5$ kHz, indicated in Figure 13–26 by the frequency spectrum on the input to the mixer. For this frequency, the local oscillator is at a frequency of

$$f_o = 1 \text{ MHz} + 455 \text{ kHz} = 1.455 \text{ MHz}$$

The mixer produces the following sum and difference frequencies as indicated in Figure 13-26.

$$\begin{aligned}f_o + f_c &= 1.455 \text{ MHz} + 1 \text{ MHz} = 2.455 \text{ MHz} \\f_o - f_c &= 1.455 \text{ MHz} - 1 \text{ MHz} = 455 \text{ kHz} \\f_o + (f_c + f_m) &= 1.455 \text{ MHz} + 1.005 \text{ MHz} = 2.46 \text{ MHz} \\f_o + (f_c - f_m) &= 1.455 \text{ MHz} + 0.995 \text{ MHz} = 2.45 \text{ MHz} \\f_o - (f_c + f_m) &= 1.455 \text{ MHz} - 1.005 \text{ MHz} = 450 \text{ kHz} \\f_o - (f_c - f_m) &= 1.455 \text{ MHz} - 0.995 \text{ MHz} = 460 \text{ kHz}\end{aligned}$$

Since the IF amplifier is a frequency-selective circuit, it responds only to 455 kHz and any side frequencies lying in the 10 kHz band centered at 455 kHz. So all of the frequencies out of the mixer are rejected except the 455 kHz IF, all lower-side frequencies down to 450 kHz, and all upper-side frequencies up to 460 kHz. This frequency spectrum is the audio modulated IF.

A Basic IF Amplifier

Although the detailed circuitry of the IF amplifier may differ from one system to another, it always has a tuned (resonant) circuit on the input or on the output or on both. Figure 13-27(a) shows a basic IF amplifier with tuned transformer coupling at the input and output. The general frequency response curve is shown in Figure 13-27(b).

 


FIGURE 13-27 A basic IF amplifier with a tuned circuit on the input and output.

AGC IN IF AMPLIFIERS IF amplifiers can be used in either AM or FM systems. Figure 13-28 shows a typical circuit diagram for an application in an AM receiver. This configuration has a single-tuned transformer-coupled output. The AGC input is normally fed back from the detector in an AM receiver and is used to keep the IF gain at a constant level so that variations in the strength of the incoming RF signal do not cause the audio output to vary significantly. Signal strength can vary for a number of reasons, but atmospheric factors are the most common, assuming the receiver is stationary. If the receiver is mobile, then any number of environmental factors can affect the strength of the signal at the receiver. When the AGC voltage increases, the IF gain decreases; when the AGC voltage decreases, the IF gain increases.


 


FIGURE 13-28 A typical circuit configuration for an IF amplifier.

Although Figure 13–27 shows tuned *LC* circuits at the input and output of the IF amplifier, crystal filters are commonly used. Remember that a crystal can be modeled as a series or parallel resonant *LC* circuit. Crystal filters have a much higher *Q* than discrete *LC* filters, resulting in more selectivity and a much smaller footprint.

The filter used at the front end of the IF amplifier is often referred to as a *roofing filter*. In some literature this term is misinterpreted to mean that a roofing filter is only used in systems where the IF frequency is higher, or above, the highest RF frequency. This is simply not the case. The term “*roofing*” means protection. The roofing filter at the front end of an IF amplifier protects later stages, like mixers and signal processing subsystems farther downstream.

 

SYSTEM NOTE

Audio Amplifiers

Audio amplifiers are used in a receiver system following the detector to provide amplification of the recovered audio signal and audio power to drive the speaker(s), as indicated in Figure 13–29. Audio amplifiers typically have bandwidths of 3 kHz to 15 kHz or more depending on the requirements of the system. High quality audio systems will cover the range of human hearing, which is usually stated as 20 Hz to 20 kHz. For strictly voice communications a 3 kHz bandwidth is reasonable and represents the bandwidth of a typical telephone system. IC audio amplifiers are available with a range of capabilities. Previously, in Section 5–7, the fixed-gain, LM384 IC power amplifier was introduced. To complete the radio, the more versatile LM386 is selected here. The data sheet for the LM386 can be found at www.national.com.

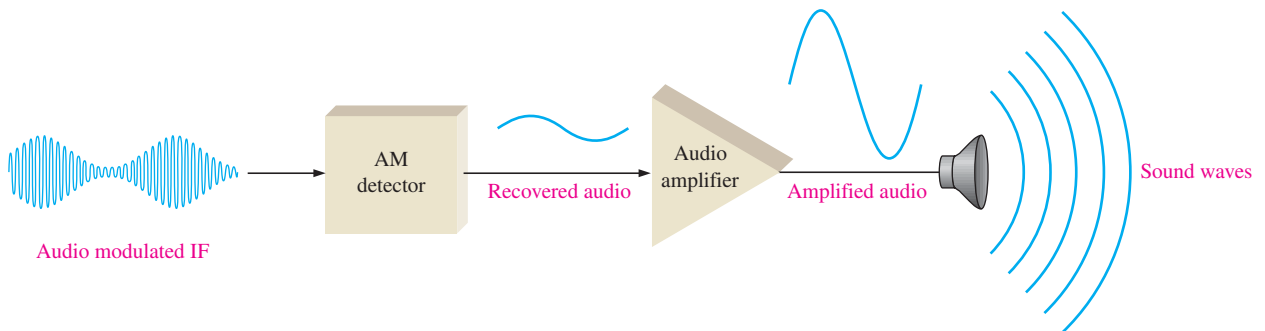


FIGURE 13–29 The audio amplifier in a receiver system.

THE LM386 AUDIO-POWER AMPLIFIER This device is an example of a low-power audio power amplifier that is capable of providing several hundred milliwatts to an 8 Ω speaker. The LM386 is specified for much higher frequencies than just audio frequencies. It operates from any dc supply voltage in the 4 V to 12 V range, making it a good choice for systems that are battery powered. The pin configuration of the LM386 is shown in Figure 13–30(a). The voltage gain is 20 without external connections to the gain terminals, as shown in Figure 13–30(b). A voltage gain of 200 is achieved by connecting a 10 μF capacitor from pin 1 to pin 8, as shown in Figure 13–30(c). Voltage gains between

 


FIGURE 13–30 Pin configuration and gain connections for the LM386 audio amplifier.

20 and 200 can be realized by a resistor (R_G) and capacitor (C_G) connected in series from pin 1 to pin 8 as shown in Figure 13-30(d). These external components are effectively placed in parallel with an internal gain-setting resistor.

A typical application of the LM386 as a power amplifier in a radio receiver is shown in Figure 13-31. Here the detected AM signal is fed to the inverting input through the volume control potentiometer, R_1 , and resistor R_2 . C_1 is the input coupling capacitor and C_2 is the power supply decoupling capacitor. R_2 and C_3 filter out any residual RF or IF signal that may be on the output of the detector. R_3 and C_6 provide additional filtering before the audio signal is applied to the speaker through the coupling capacitor C_7 .

 


FIGURE 13-31 The LM386 as an AM audio power amplifier.

SECTION 13-6 CHECKUP

1. What is the purpose of the IF amplifier in an AM receiver?
2. What is the center frequency of an AM IF amplifier?
3. Why is the bandwidth of an AM receiver IF amplifier 10 kHz?
4. Why must the audio amplifier follow the detector in a receiver system?
5. Compare the frequency response of the IF amplifier to that of the audio amplifier.

13-7 FREQUENCY MODULATION

As you have seen, modulation is the process of varying a parameter of a carrier signal with an information signal. Recall that in amplitude modulation the parameter of amplitude is varied. In frequency modulation (FM), the frequency of a carrier is varied above and below its normal or at-rest value by a modulating signal. This section provides a basic introduction to FM and discusses the differences between an AM and an FM receiver.

After completing this section, you should be able to

- Describe frequency modulation
 - Discuss the voltage-controlled oscillator
 - Explain frequency demodulation

In a frequency-modulated (FM) signal, the carrier frequency is increased or decreased according to the modulating signal. The amount of deviation above or below the carrier frequency depends on the amplitude of the modulating signal. The rate at which the frequency deviation occurs depends on the frequency of the modulating signal.

Figure 13–32 illustrates both a square wave and a sine wave modulating the frequency of a carrier. The carrier frequency is highest when the modulating signal is at its maximum positive amplitude and is lowest when the modulating signal is at its maximum negative amplitude.

 


FIGURE 13–32 Examples of frequency modulation.

A Basic Frequency Modulator

Frequency modulation is achieved by varying the frequency of an oscillator with the modulating signal. A **voltage-controlled oscillator (VCO)** is typically used for this purpose, as illustrated in Figure 13–33.


 


FIGURE 13–33 Frequency modulation with a voltage-controlled oscillator.

Generally, a variable-reactance type of voltage-controlled oscillator is used in FM applications. The variable-reactance VCO uses the varactor diode as a voltage-variable capacitance, as illustrated in Figure 13–34, where the capacitance is varied with the modulating voltage, V_m .


FIGURE 13–34 Basic variable-reactance VCO.

 

Noise is a concern in voltage-controlled oscillators. A perfect oscillator would have an infinitesimally narrow frequency spectrum, but no such device has yet been manufactured. Noise can result in amplitude or frequency modulation of the oscillator; remember that varactors are nonlinear devices so modulation can occur if a modulating signal (the noise) is applied.

Noise can come from many sources, such as harmonics on the supply lines or even mechanical vibrations. It can also be the result of thermal vibrations or flicker ($1/f$) noise within the device. Commonsense steps can be taken to limit noise. Basic considerations like using shielded cables and maintaining proper grounding will lower noise levels. The oscillator should be isolated from any digital circuitry and separate power supplies should be used whenever possible. Also, capacitive decoupling of the power supply lines can reduce noise.

SYSTEM NOTE

 

An Integrated Circuit FM Transmitter

There are a number of integrated circuit low-power FM transmitters in a single IC that can be used in portable systems such as cordless phones and FM communication equipment. One IC that can be used as the heart of an FM transmitter is the MAXIM MAX2605 to MAX2609 series of voltage-controlled oscillators (VCOs). These are sophisticated circuits with 158 internal transistors, but easy to implement in various circuits.

The VCO is contained in a six pin SOT23 case, so it is small and easily works in a portable, battery-powered device (V_{CC} is specified from +2.7 V to +5.5 V). Figure 13-35 shows the pin diagram for the series. Each increase in part number corresponds to a higher frequency range; the series covers the range from 45 MHz to 650 MHz. Tuning is accomplished by applying a DC voltage to the TUNE pin, which is connected internally to a varactor diode. Only an external inductor between the IND pin and GND (ground) is required for the oscillator to operate. The output is an open-collector differential output between pins 4 and 6. The spec sheet is available www.maxim-ic.com.

With only a few external components, any of the MAX2605-MAX2609 series can be configured as an FM transmitter for short distance communication.

The circuit is shown in Figure 13-36, using a MAX2606 (70-150 MHz). The oscillator frequency is set by L_1 . For the MAX2606, an inductance of 430 μH will produce a rest frequency of approximately 100 MHz. This frequency can be tuned over a limited range by adjusting the voltage to the internal varactor using R_1 to set a dc level. The frequency

 


FIGURE 13-35 Pin diagram for the MAX2605-MAX2609.

 


FIGURE 13-36 FM transmitter using the MAX2606 VCO.

increases and decreases in proportion to the dc level on the internal varactor. The input audio level is set by R_2 and causes the varactor voltage to follow the audio signal, hence introduces frequency modulation. The outputs of the MAX2606 are open collector, meaning there is no internal collector resistor. Resistors R_7 and R_8 are pull-up resistors connected between collector outputs of the differential amplifier to V_{CC} . These resistors provide DC bias for the output amplifier. As shown, the output power is very low (only about $100 \mu\text{W}$) but the addition of a power amplifier can easily increase the power.

FM Demodulation

Except for the higher frequencies, the standard broadcast FM receiver is basically the same as the AM receiver up through the IF amplifier. The main difference between an FM receiver and an AM receiver is the method used to recover the audio signal from the modulated IF.

There are several methods for demodulating an FM signal. These include slope detection, phase-shift discrimination, ratio detection, quadrature detection, and phase-locked loop demodulation. Most of these methods are covered in detail in communications courses. However, because of its importance in many systems, the next section is devoted to the phase-locked loop (PLL) including FM demodulation.

SECTION 13–7 CHECKUP

1. How does an FM signal carry information?
2. What does VCO stand for?
3. On what principle are most VCOs used in FM based?

13–8 THE PHASE-LOCKED LOOP (PLL)

In the last section, the PLL was mentioned as a way to demodulate an FM signal. In addition to FM demodulation, PLLs are used in a wide variety of communications applications, which include TV receivers, tone decoders, telemetry receivers, modems, and data synchronizers, to name a few. Many of these applications are covered in an electronic communications course. In fact, entire books have been written on the finer points of PLL operation, analysis, and applications. The approach in this section is intended only to present the basic concept and give you an intuitive idea of how PLLs work and how they are used in FM demodulation.

After completing this section, you should be able to

- Describe the phase-locked loop (PLL)
- Draw a basic block diagram for the PLL
- Discuss the phase detector and state its purpose
- State the purpose of the VCO
- State the purpose of the low-pass filter
- Explain lock range and capture range
- Explain how a PLL can be used as an FM demodulator

The Basic PLL Concept

The **phase-locked loop (PLL)** is a feedback circuit consisting of a phase detector, a low-pass filter, and a voltage-controlled oscillator (VCO). Some PLLs also include an amplifier in the loop, and in some applications the filter is not used.

The PLL is capable of locking onto or synchronizing with an incoming signal. When the phase of the incoming signal changes, indicating a change in frequency, the phase detector's output increases or decreases just enough to keep the VCO frequency the same as the frequency of the incoming signal. A basic PLL block diagram is shown in Figure 13-37.

 


FIGURE 13-37 Basic PLL block diagram.

The general operation of the PLL is as follows. The phase detector compares the phase difference between the incoming signal, V_i , and the VCO signal, V_o . When the frequency of the incoming signal, f_i , is different from that of the VCO frequency, f_o , the phase angle between the two signals is also different. The output of the phase detector and the filter is proportional to the phase difference of the two signals. This proportional voltage is fed to the VCO, forcing its frequency to move toward the frequency of the incoming signal until the two frequencies are equal. At this point, the PLL is locked onto the incoming frequency. If f_i changes, the phase difference also changes, forcing the VCO to track the incoming frequency.

The Phase Detector

The phase-detector circuit in a PLL is basically a linear multiplier. The following analysis illustrates how it works in a PLL application. The incoming signal, V_i , and the VCO signal, V_o , applied to the phase detector can be expressed as

$$v_i = V_i \sin(2\pi f_i t + \theta_i)$$

$$v_o = V_o \sin(2\pi f_o t + \theta_o)$$

where θ_i and θ_o are the relative phase angles of the two signals. The phase detector multiplies these two signals and produces a sum and difference frequency output, V_d , as follows:

$$V_d = V_i \sin(2\pi f_i t + \theta_i) \times V_o \sin(2\pi f_o t + \theta_o)$$

$$= \frac{V_i V_o}{2} \cos[(2\pi f_i t + \theta_i) - (2\pi f_o t + \theta_o)] - \frac{V_i V_o}{2} \cos[(2\pi f_i t + \theta_i) + (2\pi f_o t + \theta_o)]$$

When the PLL is locked,

$$f_i = f_o$$

and

$$2\pi f_i t = 2\pi f_o t$$

Therefore, the detector output voltage is

$$V_d = \frac{V_i V_o}{2} [\cos(\theta_i - \theta_o) - \cos(4\pi f_i t + \theta_i + \theta_o)]$$

The second cosine term in the above equation is a second harmonic term ($2 \times 2\pi f_i t$) and is filtered out by the low-pass filter. The control voltage on the output of the filter is expressed as

$$V_c = \frac{V_i V_o}{2} \cos \theta_e \quad (13-3)$$

where $\theta_e = \theta_i - \theta_o$, where θ_e is the *phase error*. The filter output voltage is proportional to the phase difference between the incoming signal and the VCO signal and is used as the control voltage for the VCO. This operation is illustrated in Figure 13–38.

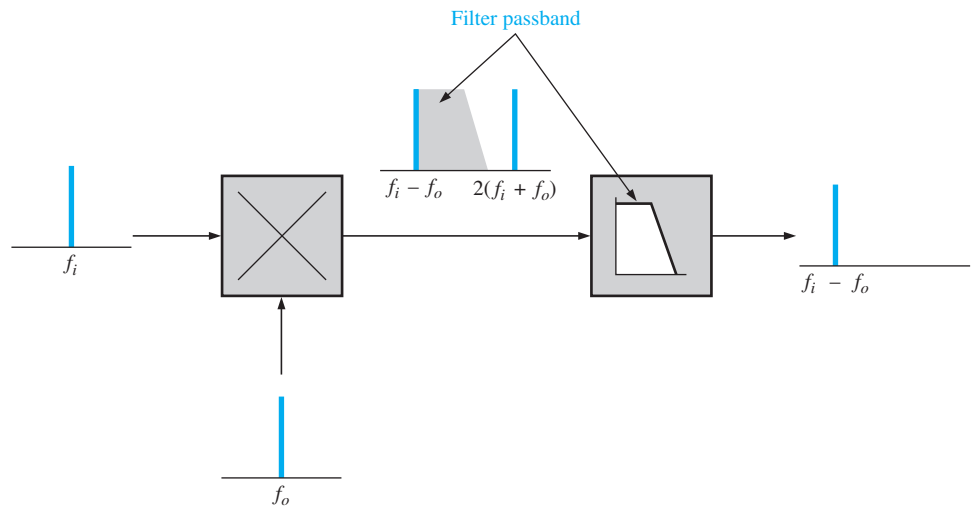


FIGURE 13–38 Basic phase detector/filter operation.

EXAMPLE 13–7

A PLL is locked onto an incoming signal with a frequency of 1 MHz at a phase angle of 50° . The VCO signal is at a phase angle of 20° . The peak amplitude of the incoming signal is 0.5 V and that of the VCO output signal is 0.7 V.

- What is the VCO frequency?
- What is the value of the control voltage being fed back to the VCO at this point?

SOLUTION

- Since the PLL is in lock, $f_i = f_o = 1 \text{ MHz}$.
- $\theta_e = \theta_i - \theta_o = 50^\circ - 20^\circ = 30^\circ$

$$V_c = \frac{V_i V_o}{2} \cos \theta_e = \frac{(0.5 \text{ V})(0.7 \text{ V})}{2} \cos 30^\circ = (0.175 \text{ V}) \cos 30^\circ = \mathbf{0.152 \text{ V}}$$

PRACTICE EXERCISE

If the phase angle of the incoming signal changes instantaneously to 30° , indicating a change in frequency, what is the instantaneous VCO control voltage?

The Voltage-Controlled Oscillator (VCO)

Voltage-controlled oscillators can take many forms. A VCO can be some type of *LC* or crystal oscillator, as was shown in Section 13–7, or it can be some type of *RC* oscillator or multivibrator. No matter the exact type, most VCOs employed in PLLs operate on the principle of *variable reactance* using the varactor diode as a voltage-variable capacitor.

The capacitance of a varactor diode varies inversely with reverse-bias voltage. The capacitance decreases as reverse voltage increases, and vice versa.

In a PLL, the control voltage fed back to the VCO is applied as a reverse-bias voltage to the varactor diode within the VCO. The frequency of oscillation is inversely related to capacitance for an RC type oscillator by the formula

$$f_o = \frac{1}{2\pi RC}$$

and for an LC type oscillator by the formula

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

These formulas show that frequency increases as capacitance decreases and vice versa.

Capacitance decreases as reverse voltage (control voltage) increases. Therefore, an increase in control voltage to the VCO causes an increase in frequency and vice versa. Basic VCO operation is illustrated in Figure 13-39. The graph in part (b) shows that at the nominal control voltage, $V_{c(nom)}$, the oscillator is running at its nominal or free-running frequency, $f_{o(nom)}$. An increase in V_c above the nominal value forces the oscillator frequency to increase, and a decrease in V_c below the nominal value forces the oscillator frequency to decrease. There are, of course, limits on the operation as indicated by the minimum and maximum points. The transfer function or conversion gain, K , of the VCO is normally expressed as a certain frequency deviation per unit change in control voltage.

$$K = \frac{\Delta f_o}{\Delta V_c}$$

 


FIGURE 13-39 Basic VCO operation.

EXAMPLE 13-8

The output frequency of a certain VCO changes from 50 kHz to 65 kHz when the control voltage increases from 0.5 V to 1 V. What is the conversion gain, K ?

SOLUTION

$$K = \frac{\Delta f_o}{\Delta V_c} = \frac{65 \text{ kHz} - 50 \text{ kHz}}{1 \text{ V} - 0.5 \text{ V}} = \frac{15 \text{ kHz}}{0.5 \text{ V}} = \mathbf{30 \text{ kHz/V}}$$

PRACTICE EXERCISE

If the conversion gain of a certain VCO is 20 kHz/V, how much frequency deviation does a change in control voltage from 0.8 V to 0.5 V produce? If the VCO frequency is 250 kHz at 0.8 V, what is the frequency at 0.5 V?

Basic PLL Operation

When the PLL is locked, the incoming frequency, f_i , and the VCO frequency, f_o , are equal. However, there is always a phase difference between them called the *static phase error*. The phase error, θ_e , is the parameter that keeps the PLL locked in. As you have seen, the filtered voltage from the phase detector is proportional to θ_e (Equation (13-3)). This voltage controls the VCO frequency and is always just enough to keep $f_o = f_i$.

Figure 13-40 shows the PLL and two sinusoidal signals of the same frequency but with a phase difference, θ_e . For this condition the PLL is in lock and the VCO control voltage is constant. If f_i decreases, θ_e increases to θ_{e1} as illustrated in Figure 13-41. This

 


FIGURE 13-40 PLL in lock under static condition ($f_o = f_i$ and constant θ_e).

 


FIGURE 13-41 PLL action when f_i decreases.

increase in θ_e is sensed by the phase detector causing the VCO control voltage to decrease, thus decreasing f_o until $f_o = f_i$ and keeping the PLL in lock. If f_i increases, θ_e decreases to θ_{e1} as illustrated in Figure 13-42. This decrease in θ_e causes the VCO control voltage to increase, thus increasing f_o until $f_o = f_i$ and keeping the PLL in lock.


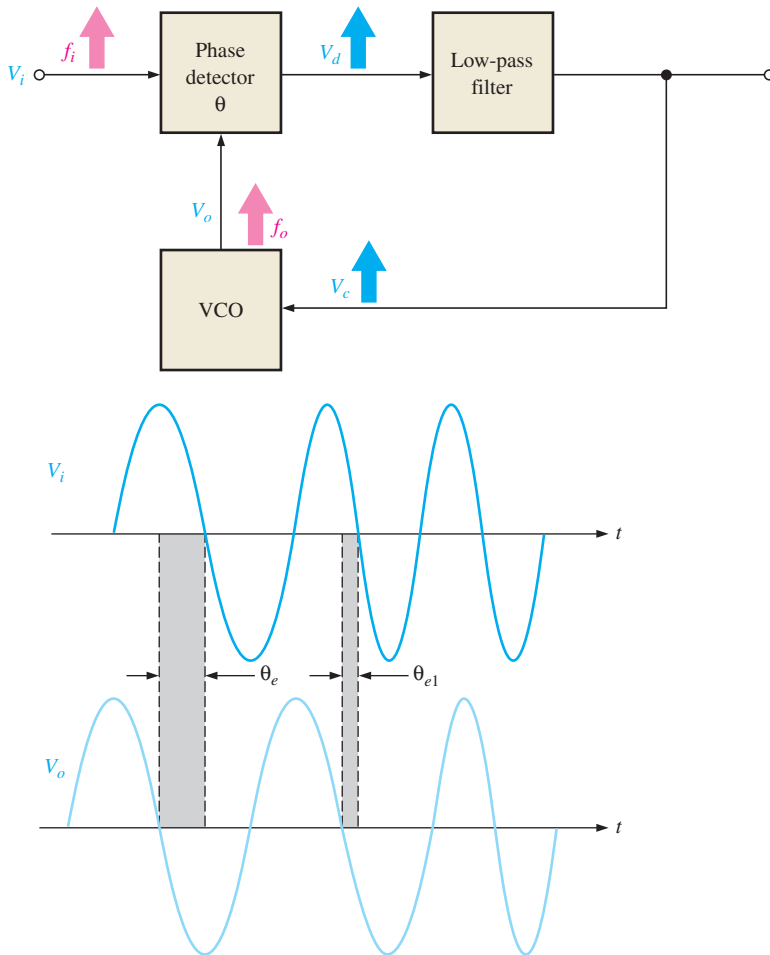



FIGURE 13-42 PLL action when f_i increases.

LOCK RANGE Once the PLL is locked, it will track frequency changes in the incoming signal. The range of frequencies over which the PLL can maintain lock is called the *lock* or *tracking range*. Limitations on the hold-in range are the maximum frequency deviations of the VCO and the output limits of the phase detector. The hold-in range is independent of the bandwidth of the low-pass filter because, when the PLL is in lock, the difference frequency ($f_i - f_o$) is zero or a very low instantaneous value that falls well within the bandwidth. The hold-in range is usually expressed as a percentage of the VCO frequency.

CAPTURE RANGE Assuming the PLL is not in lock, the range of frequencies over which it can acquire lock with an incoming signal is called the *capture range*. Two basic conditions are required for a PLL to acquire lock. First, the difference frequency ($f_o - f_i$) must be low enough to fall within the filter's bandwidth. This means that the incoming frequency must not be separated from the nominal or free-running frequency of the VCO by more than the bandwidth of the low-pass filter. Second, the maximum deviation, Δf_{max} , of the VCO frequency must be sufficient to allow f_o to increase or decrease to a value equal to f_i . These conditions are illustrated in Figure 13-43; and when these conditions exist, the PLL will “pull” the VCO frequency toward the incoming frequency until $f_o = f_i$.

 


(a)

 

(b) $f_i - f_o$ decreases as f_o deviates towards f_i .

FIGURE 13-43 Illustration of the conditions for a PLL to acquire lock.

SYSTEM EXAMPLE 13-3

 

A DATA COMMUNICATIONS SYSTEM USING AN FSK MODEM

Digital data, consisting of a series of binary digits (1s and 0s), can be sent from one device to another over the telephone lines. Two voltage levels are used to represent the two types of bits, a high-voltage level (1) and a low voltage level (0). The data stream is made up of time intervals when the voltage has a constant high value or a constant low value with very fast transitions from one level to the other. In other words, the data stream contains very low frequencies (constant-voltage intervals) and very high frequencies (transitions). Since the standard telephone system has a bandwidth of approximately 3000 Hz, it cannot handle the very low and the very high frequencies that make up a typical data stream without losing most of the information. Because of the bandwidth limitation of the telephone system, it is necessary to modify digital data before they are sent out. One method of doing this is with frequency shift keying (FSK), which is a form of frequency modulation.

A simplified block diagram of a digital communication system for interfacing digital terminal equipment (DTE) to the telephone network is shown in Figure SE13-3. The system FSK modulates digital data before they are transmitted over the phone line and demodulates FSK signals received from another DTE. Because its basic function is to *modulate* and *demodulate*, it is called a *modem*. Although the modem performs many associated functions, as indicated by the different blocks, in this system example our focus will be on the modulation and demodulation circuits.

 


FIGURE SE13-3 A data communications system.

The FSK **modem** interfaces digital terminal equipment with the telephone network so that digital data can be transmitted and received over regular phone lines, thus allowing DTEs to communicate with each other. Figure SE13-3 shows a block diagram of a simple data communications system in which a modem at each end of the phone line provides interfacing for the two DTEs.

The modem (DCE) consists of three basic functional blocks as shown in Figure SE13-4: the FSK modem circuits, the phone line interface circuits, and the timing and control circuits. The dual polarity power supply is not shown. Although the focus of this system application is the FSK modem, we will briefly look at each of the other parts to give you a basic idea of the overall system function.

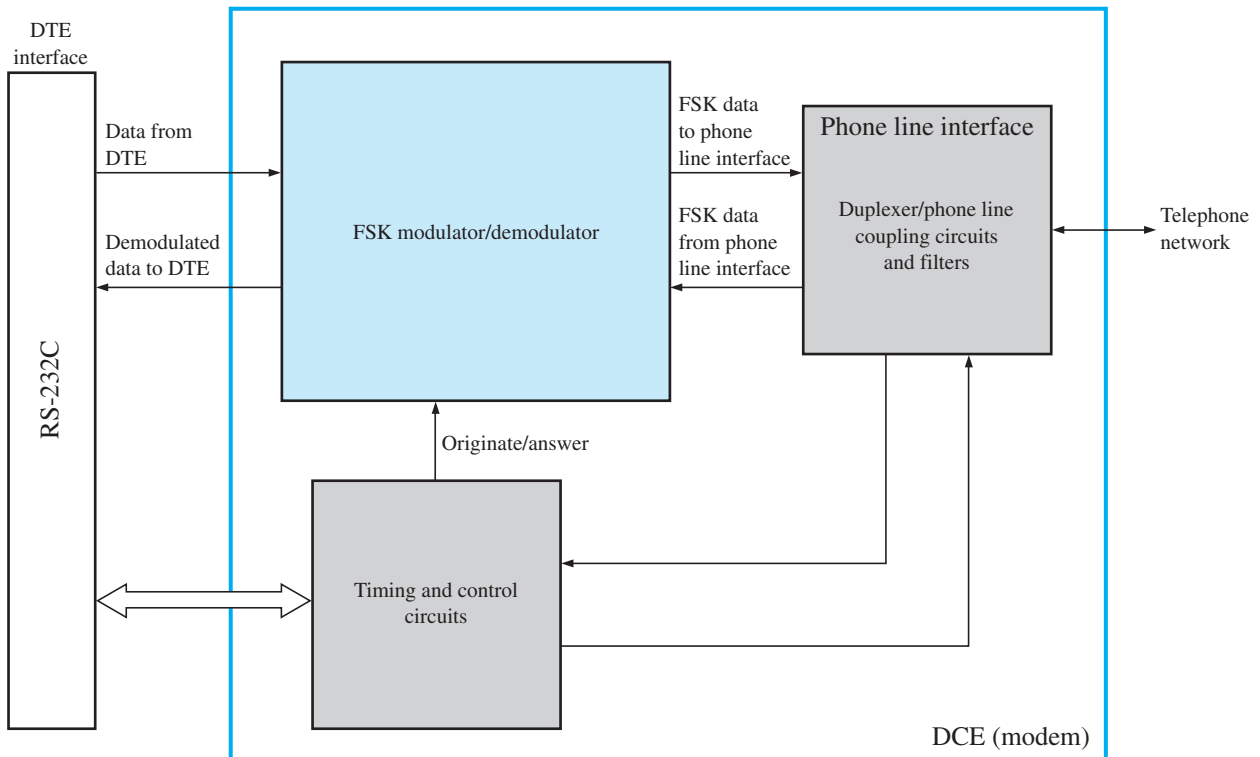


FIGURE SE13-4 Basic block diagram of a modem.

THE PHONE LINE INTERFACE The main purposes of this circuitry are to couple the phone line to the modem by proper impedance matching, to provide necessary filtering, and to accommodate full-duplex transmission of data. *Full-duplex* means essentially that information can be going both ways on a single phone line at the same time. This allows a DTE connected to a modem to be sending data and receiving data simultaneously without the transmitted data interfering with the received data. Full-duplexing is implemented by assigning the transmitted data one bandwidth and the received data another separate bandwidth within the 300 Hz to 3 kHz overall bandwidth of the phone network.

TIMING AND CONTROL One basic function of the timing and control circuits is to determine the proper mode of operation for the modem. The two modes are the originate mode and the answer mode. Another function is to provide a standard interface (such as RS-232C) with the DTE. The RS-232C standard requires certain defined command and control signals, data signals, and voltage levels for each signal.


FREQUENCY-SHIFT KEYING (FSK) FSK is one method used to overcome the bandwidth limitation of the telephone system so that digital data can be sent over the phone lines. The basic idea of FSK is to represent 1s and 0s by two different frequencies within

the telephone bandwidth. By the way, any frequency within the telephone bandwidth is an audible tone. The standard frequencies for a full-duplex 300 baud modem in the originate mode are 1070 Hz for a 0 (called a space) and 1270 Hz for a 1 (called a mark). In the answer mode, 2025 Hz is a 0 and 2225 Hz is a 1.

An example of a digital data stream converted to FSK by a modem is shown in Figure SE13–5.



(a) Data stream

 

(b) Corresponding FSK signal (frequency relationships are not exact)

FIGURE SE13–5 Example of FSK data.

SECTION 13–8 CHECKUP

- List the three basic components in a phase-locked loop.
- What is another circuit used in some PLLs other than the three listed in Question 1?
- What is the basic function of a PLL?
- What is the difference between the lock range and the capture range of a PLL?
- Basically, how does a PLL track the incoming frequency?

13–9 FIBER OPTICS

Fiber optic cables are replacing copper wire as a means of sending signals over long distances in many types of communications systems. Fiber optics is used by cable television, telephone, and electric utility companies, among others.

After completing this section, you should be able to

- Discuss fiber optic cables
- Describe how signals are sent through a fiber optic cable
- Define the basic types of fiber optic cable

Instead of using electrical pulses to transmit information through copper lines, **fiber optics** uses light pulses to transmit information through fiber optic cables about the diameter of a human hair, which is about 100 microns (one millionth of a meter). Fiber optic systems have several advantages over systems using copper wire. These include faster speed, higher signal capacity, longer transmission distances without amplification, less susceptibility to interference, and they are more economical to maintain.

Basic Operation

When light is introduced into one end of a fiber optic cable, it “bounces” along until it emerges from the other end. The fiber is generally made of pure glass or plastic that is surrounded by a highly reflective cladding that acts essentially as a mirrored surface but actually uses a physics phenomenon called *total internal reflection* to produce an almost lossless reflection. Think of a fiber optic cable as a pipe lined inside with a mirror. As the light moves along the fiber, it is reflected off the cladding so that it can move around bends in the fiber with essentially no loss. A fiber optic cable consists of the core, which is the glass fiber itself, the cladding that surrounds the fiber and provides the reflective surface, and the outer coating or jacket that provides protection. Other layers may be added for strengthening. The basic structure of a single fiber optic cable is illustrated in Figure 13-44(a), and the propagation of light along a fiber with a bend is shown in part (b). It doesn't matter whether the fiber is straight or bent; the light still travels through it but with higher loss when the bend angle is high.

 


FIGURE 13-44 Simplified structure and operation of a fiber optic cable.

When a light ray enters the fiber optic cable, it strikes the reflective surface of the cladding at an angle called the **angle of incidence**, θ_i . If the angle of incidence is greater than a parameter known as the **critical angle**, θ_c , the light ray is then reflected back into the core at an angle called the *angle of reflection*, θ_r , as shown in Figure 13-45(a). The angle of incidence is always equal to the angle of reflection. If the angle of incidence is less than the critical angle, the light ray is refracted and passes into the cladding, causing energy to be lost, as shown in Figure 13-45(b). This is called *scattering* and any refracted light represents a loss or attenuation as a light ray is propagated through the fiber optic cable. Another cause of attenuation of light in a fiber optic cable is called *absorption*, which is caused by the interactions of the light photons and the molecules of the core.

 


FIGURE 13-45 Critical angle in a fiber optic cable.

The core material and the cladding material each have a parameter known as the **index of refraction**, which determines the critical angle. The critical angle is defined by the formula

$$\theta_c = \cos^{-1}\left(\frac{n_2}{n_1}\right) \quad (13-4)$$

where n_1 is the index of refraction of the core and n_2 is the index of refraction of the cladding.

EXAMPLE 13–9

A certain fiber optic cable has a core index of refraction of 1.35 and a cladding index of refraction of 1.30. Determine the critical angle.

SOLUTION

$$\theta_c = \cos^{-1}\left(\frac{n_2}{n_1}\right) = \cos^{-1}\left(\frac{1.30}{1.35}\right) = 15.6^\circ$$

RELATED PROBLEM

Calculate the critical angle if $n_1 = 1.67$ and $n_2 = 1.59$.

Modes of Light Propagation

Three basic modes of light propagation in fiber optic cables are multimode step index, single-mode step index, and multimode graded index.

MULTIMODE STEP INDEX Figure 13–46 shows a fiber optic cable in which the diameter of the core is fairly large relative to the diameter of the cladding. As shown, there is a sharp transition in the index of refraction going from the core to the cladding, thus the term *step*. Light entering the cable will tend to propagate through the core in multiple rays or modes, as indicated. Some of the rays will go straight down the core, while others will bounce back and forth as they propagate. Still others will scatter due to their small angle of incidence, causing attenuation in the light energy. As a result of the multiple modes, the light will encounter time dispersion; that is, all the light rays will not arrive at the end of the cable at exactly the same time.

 


FIGURE 13–46 Multimode step index fiber optic cable.

SINGLE-MODE STEP INDEX Figure 13–47 shows a fiber optic cable in which the diameter core is very small relative to the diameter of the cladding. There is a sharp transition in the index of refraction going from the core to the cladding. Light entering the cable tends to propagate through the core in a single ray or mode. This results in much less attenuation and, ideally, no time dispersion compared to the multimode cable.



FIGURE 13–47 Single-mode step index fiber optic cable.

MULTIMODE GRADED INDEX Figure 13-48 shows a fiber optic cable in which the diameter of the core is fairly large relative to the diameter of the cladding. There is a gradual or graded transition in the index of refraction going from the center of the core into the cladding. Light rays will be more curved as they bounce through the gradually changing indices of refraction, resulting in less attenuation and time dispersion than in the multimode step index cable.

 


FIGURE 13-48 Multimode graded index fiber optic cable.

A Fiber Optic Data Communications Link

A simplified block diagram of a fiber optic data communications link is shown in Figure 13-49. The source provides the electrical signal that is to be transmitted. This electrical signal is converted to a light signal and coupled to the fiber optic cable by the transmitter. At the receiving end, the light signal is coupled out of the cable into the receiver, which converts it to an electrical signal. This signal is then processed and connected to the end user.

The electrical signal modulates the light intensity and produces a light signal that carries the same information as the electrical signal. A special connector then couples the light signal into the fiber optic cable. At the other end the receiver demodulates the light signal and converts it back into the original electrical signal.


 


FIGURE 13-49 Basic block diagram of a fiber optic data communication link.

Fiber optic systems are preferred over wired and wireless systems for a number of reasons. Bandwidth is certainly one major advantage. The full bandwidth capability of fiber optics has not been fully realized even today. The fact that a fiber optic signal can travel over 60 miles before it needs to be regenerated is another major advantage. Also light is not subject to outside interference sources like EMI, RFI, lightning, or electromagnetic pulses (EMPs) so data are less likely to be corrupted. There are no grounding or shorting issues and there is no crosstalk between channels.

Another advantage of fiber optics is security. Intelligence on a wired system can be tapped fairly easily using electromagnetic induction techniques. Wireless data is also easy to steal. Although data in a fiber optic system is still susceptible to security breaches, it is much more difficult to access without detection than traditional systems.

SYSTEM NOTE

 

SECTION 13-9 CHECKUP

1. Generally, what is a fiber optic cable made of?
2. Typically, what is the approximate diameter of a fiber optic cable?
3. Name three basic parts of a fiber optic cable.
4. What is the difference between the critical angle and the angle of incidence?
5. List three types of fiber optic cables.

SUMMARY

- In amplitude modulation (AM), the amplitude of a higher-frequency carrier signal is varied by a lower-frequency modulating signal (usually an audio signal).
- A basic superheterodyne AM receiver consists of an RF amplifier (not always), a mixer, a local oscillator, an IF (intermediate frequency) amplifier, an AM detector, and audio and power amplifiers.
- The IF in a standard AM receiver is 455 kHz.
- The AGC (automatic gain control) in a receiver tends to keep the signal strength constant within the receiver to compensate for variations in the received signal.
- In frequency modulation (FM), the frequency of a carrier signal is varied by a modulating signal.
- A superheterodyne FM receiver is basically the same as an AM receiver except that it requires a limiter to keep the IF amplitude constant, a different kind of detector or discriminator, and a deemphasis network. The IF is 10.7 MHz.
- A four-quadrant linear multiplier can handle any combination of voltage polarities on its inputs.
- Amplitude modulation is basically a multiplication process.
- The multiplication of sinusoidal signals produces sum and difference frequencies.
- The output spectrum of a balanced modulator includes upper-side and lower-side frequencies, but no carrier frequency.
- The output spectrum of a standard amplitude modulator includes upper-side and lower-side frequencies and the carrier frequency.
- A linear multiplier is used as the mixer in receiver systems.
- A mixer converts the RF signal down to the IF signal. The radio frequency varies over the AM or FM band. The intermediate frequency is constant.
- One type of AM demodulator consists of a multiplier followed by a low-pass filter.
- The audio and power amplifiers boost the output of the detector or discriminator and drive the speaker.
- A voltage-controlled oscillator (VCO) produces an output frequency that can be varied by a control voltage. Its operation is based on a variable reactance.
- A VCO is a basic frequency modulator when the modulating signal is applied to the control voltage input.
- A phase-locked loop (PLL) is a feedback circuit consisting of a phase detector, a low-pass filter, a VCO, and sometimes an amplifier.
- The purpose of a PLL is to lock onto and track incoming frequencies.
- A linear multiplier can be used as a phase detector.
- A modem is a modulator/demodulator.
- DTE stands for digital terminal equipment.
- DCE stands for digital communications equipment.
- Fiber optics provides a light path from a light-emitting device to a light-activated device.
- The three parts of a fiber optic cable are the core, the cladding and the jacket.
- Light rays bounce off the core boundary at the angle of incidence greater than the critical angle in order to be reflected. If the angle is less than the critical angle, the light rays are refracted into the cladding.
- The three types of cable are multimode step index, single-mode step index, and multimode graded index.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Amplitude modulation (AM) A communication method in which a lower-frequency signal modulates (varies) the amplitude of a higher-frequency signal (carrier).

Balanced modulation A form of amplitude modulation in which the carrier is suppressed; sometimes known as *suppressed-carrier modulation*.

Critical angle The angle above which full reflection occurs in a fiber optic cable.

Fiber optics The use of light pulses to transmit information through a fiber optic cable.

Four-quadrant multiplier A linear device that produces an output voltage proportional to the product of two input voltages.

Frequency modulation (FM) A communication method in which a lower-frequency intelligence-carrying signal modulates (varies) the frequency of a higher-frequency signal.

Mixer A device for down-converting frequencies in a receiver system.

Modem A device that converts signals produced by one type of device to a form compatible with another; *modulator/demodulator*.

Phase-locked loop (PLL) A device for locking onto and tracking the frequency of an incoming signal.

Voltage-controlled oscillator (VCO) An oscillator for which the output frequency is dependent on a controlling input voltage.

KEY FORMULAS

- (13-1) $V_{\text{OUT}} = KV_X V_Y$ Multiplier output voltage
- (13-2)
$$v_1 v_2 + \frac{V_{1(p)} V_{2(p)}}{2} \cos 2\pi(f_1 - f_2)t$$

$$- \frac{V_{1(p)} V_{2(p)}}{2} \cos 2\pi(f_1 + f_2)t$$
 Sum and difference frequencies
- (13-3)
$$V_{\text{out}} = V_{c(p)}^2 \sin 2\pi f_c t$$

$$+ \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi(f_c - f_m)t$$

$$- \frac{V_{c(p)} V_{m(p)}}{2} \cos 2\pi(f_c + f_m)t$$
 Standard AM
- (13-4) $\theta_c = \cos^{-1}\left(\frac{n_2}{n_1}\right)$ Critical angle of fiber optic cable

SELF-TEST

Answers are at the end of the chapter.

- In amplitude modulation, the pattern produced by the peaks of the carrier signal is called the
 - index
 - envelope
 - audio signal
 - upper-side frequency
- Which of the following is not a part of an AM superheterodyne receiver?
 - Mixer
 - IF amplifier
 - DC restorer
 - Detector
 - Audio amplifier
 - Local oscillator
- In an AM receiver, the local oscillator always produces a frequency that is above the incoming RF by
 - 10.7 kHz
 - 455 MHz
 - 10.7 MHz
 - 455 kHz
- An FM receiver has an IF frequency that is
 - in the 88 MHz to 108 MHz range
 - in the 540 kHz to 1640 kHz range
 - 455 kHz
 - greater than the IF in an AM receiver
- The detector or discriminator in an AM or an FM receiver
 - detects the difference frequency from the mixer
 - changes the RF to IF
 - recovers the audio signal
 - maintains a constant IF amplitude

6. In order to handle all combinations of input voltage polarities, a multiplier must have
 - (a) four-quadrant capability
 - (b) three-quadrant capability
 - (c) four inputs
 - (d) dual-supply voltages
7. The internal attenuation of a multiplier is called the
 - (a) transconductance
 - (b) scale factor
 - (c) reduction factor
8. If the X_2 input of a linear multiplier is grounded, the X_1 input is operating as a(n)
 - (a) difference input
 - (b) differential input
 - (c) single-ended input
 - (d) averaging input
9. Amplitude modulation is basically a
 - (a) summing of two signals
 - (b) multiplication of two signals
 - (c) subtraction of two signals
 - (d) nonlinear process
10. The frequency spectrum of a balanced modulator contains
 - (a) a sum frequency
 - (b) a difference frequency
 - (c) a carrier frequency
 - (d) answers (a), (b), and (c)
 - (e) answers (a) and (b)
 - (f) answers (b) and (c)
11. The IF in a receiver is the
 - (a) sum of the local oscillator frequency and the RF carrier frequency
 - (b) local oscillator frequency
 - (c) difference of the local oscillator frequency and the carrier RF frequency
 - (d) difference of the carrier frequency and the audio frequency
12. When a receiver is tuned from one RF frequency to another,
 - (a) the IF changes by an amount equal to the LO (local oscillator) frequency
 - (b) the IF stays the same
 - (c) the LO frequency changes by an amount equal to the audio frequency
 - (d) both the LO and the IF frequencies change
13. The output of the AM detector goes directly to the
 - (a) IF amplifier
 - (b) mixer
 - (c) audio amplifier
 - (d) speaker
14. If the control voltage to a VCO increases, the output frequency
 - (a) decreases
 - (b) does not change
 - (c) increases
15. A PLL maintains lock by comparing the
 - (a) phase of two signals
 - (b) frequency of two signals
 - (c) amplitude of two signals
16. The attenuation in a fiber optic cable as a result of photons interacting with the molecules of the core is called
 - (a) scattering
 - (b) absorption
 - (c) cladding
 - (d) incidence

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 13–59.

- If the R_1 potentiometer is 20 k Ω instead of 10 k Ω ,
 1. The output signal range will
 - (a) increase
 - (b) decrease
 - (c) not change
- If C_3 opens,
 2. A low-frequency output signal voltage will
 - (a) increase
 - (b) decrease
 - (c) not change

- 3. A high-frequency cutoff will
 - (a) increase (b) decrease (c) not change
- If C_2 opens,
 - 4. The amplifier gain will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 13-1 Basic Receivers

1. Label each block in the AM receiver in Figure 13-50.
2. Label each block in the FM receiver in Figure 13-51.

 


FIGURE 13-50

 


FIGURE 13-51

3. An AM receiver is tuned to a transmitted frequency of 680 kHz. What is the local oscillator (LO) frequency?
4. An FM receiver is tuned to a transmitted frequency of 97.2 MHz. What is the LO frequency?
5. The LO in an FM receiver is running at 101.9 MHz. What is the incoming RF? What is the IF?

SECTION 13-2 The Linear Multiplier

6. Calculate the output from an AD532 linear multiplier for the following differential input voltages.
 - (a) $X_1 = 2.75 \text{ V}, X_2 = -4.32 \text{ V}, Y_1 = 2.26 \text{ V}, Y_2 = 6.67 \text{ V}$
 - (b) $X_1 = -3.33 \text{ V}, X_2 = 9.31 \text{ V}, Y_1 = 4.42 \text{ V}, Y_2 = -5.15 \text{ V}$
 - (c) $X_1 = -2.75 \text{ V}, X_2 = -4.32 \text{ V}, Y_1 = 2.26 \text{ V}, Y_2 = -6.67 \text{ V}$
 - (d) $X_1 = -3.33 \text{ V}, X_2 = 9.31 \text{ V}, Y_1 = -4.42 \text{ V}, Y_2 = 5.15 \text{ V}$

7. Calculate the output from an AD532 linear multiplier for the following differential input voltages.
 - (a) $X_1 = -6.22 \text{ V}$, $X_2 = -1.15 \text{ V}$, $Y_1 = 4.33 \text{ V}$, $Y_2 = -4.85 \text{ V}$
 - (b) $X_1 = 7.43 \text{ V}$, $X_2 = -5.55 \text{ V}$, $Y_1 = -4.86 \text{ V}$, $Y_2 = -9.11 \text{ V}$
 - (c) $X_1 = 11.6 \text{ V}$, $X_2 = 650 \text{ mV}$, $Y_1 = 880 \text{ mV}$, $Y_2 = 2.35 \text{ V}$
 - (d) $X_1 = -750 \text{ mV}$, $X_2 = 875 \text{ mV}$, $Y_1 = -12.2 \text{ V}$, $Y_2 = 4.66 \text{ V}$
8. Calculate the output from an AD532 linear multiplier for the following single-ended input voltages. Assume that the X_2 and Y_2 inputs are tied to ground.
 - (a) $X = 18.6 \text{ V}$, $Y = 1.65 \text{ V}$ (b) $X = -2.44 \text{ V}$, $Y = 22.6 \text{ V}$
 - (c) $X = 12.1 \text{ V}$, $Y = -4.2 \text{ V}$ (d) $X = -750 \text{ mV}$, $Y = -44 \text{ V}$
9. Calculate the output from an AD532 linear multiplier for the following single-ended input voltages. Assume that the X_1 and Y_1 inputs are tied to ground.
 - (a) $X = 450 \text{ mV}$, $Y = -15.5 \text{ V}$ (b) $X = -2.75 \text{ V}$, $Y = -15.4 \text{ V}$
 - (c) $X = -22.1 \text{ V}$, $Y = 800 \text{ mV}$ (d) $X = 40 \text{ V}$, $Y = 85 \text{ mV}$

SECTION 13-3 Amplitude Modulation

10. If a 100 kHz signal and a 30 kHz signal are applied to a balanced modulator, what frequencies will appear on the output?
11. What are the frequencies on the output of the balanced modulator in Figure 13-52?
12. If a 1000 kHz signal and a 3 kHz signal are applied to a standard amplitude modulator, what frequencies will appear on the output?
13. What are the frequencies on the output of the standard amplitude modulator in Figure 13-53?

 


FIGURE 13-52

 


FIGURE 13-53

14. The frequency spectrum in Figure 13-54 is for the output of a standard amplitude modulator. Determine the carrier frequency and the modulating frequency.
15. The frequency spectrum in Figure 13-55 is for the output of a balanced modulator. Determine the carrier frequency and the modulating frequency.

 


FIGURE 13-54

 


FIGURE 13-55

16. A voice signal ranging from 300 Hz to 3 kHz amplitude modulates a 600 kHz carrier. Develop the frequency spectrum.

SECTION 13-4 The Mixer

17. Determine the output expression for a multiplier with one sinusoidal input having a peak voltage of 0.2 V and a frequency of 2200 kHz and the other input having a peak voltage of 0.15 V and a frequency of 3300 kHz.
18. Determine the output frequency of the IF amplifier for the frequencies shown in Figure 13-56.

 


FIGURE 13-56

SECTION 13-5 AM Demodulation

19. The input to a certain AM receiver consists of a 1500 kHz carrier and two side frequencies separated from the carrier by 20 kHz. Determine the frequency spectrum at the output of the mixer amplifier.
20. For the same conditions stated in Problem 19, determine the frequency spectrum at the output of the IF amplifier.
21. For the same conditions stated in Problem 19, determine the frequency spectrum at the output of the AM detector (demodulator).

SECTION 13-6 IF and Audio Amplifiers

22. For a carrier frequency of 1.2 MHz and a modulating frequency of 8.5 kHz, list all of the frequencies on the output of the mixer in an AM receiver.
23. In a certain AM receiver, one amplifier has a passband from 450 kHz to 460 kHz and another has a passband from 10 Hz to 5 kHz. Identify these amplifiers.
24. Determine the maximum and minimum output voltages for the audio power amplifier in Figure 13-57.

 


FIGURE 13-57

SECTION 13-7 Frequency Modulation

25. Explain how a VCO is used as a frequency modulator.
26. How does an FM signal differ from an AM signal?
27. Explain how an audio signal is converted to frequency modulation in the MAX2606 in Figure 13-36?

SECTION 13–8 The Phase-Locked Loop (PLL)

28. Label each block in the PLL diagram of Figure 13–58.

 


FIGURE 13–58

29. A PLL is locked onto an incoming signal with a peak amplitude of 250 mV and a frequency of 10 MHz at a phase angle of 30° . The 400 mV peak VCO signal is at a phase angle of 15° .
- What is the VCO frequency?
 - What is the value of the control voltage being fed back to the VCO at this point?
30. What is the conversion gain of a VCO if a 0.5 V increase in the control voltage causes the output frequency to increase by 3.6 kHz?
31. If the conversion gain of a certain VCO is 1.5 kHz per volt, how much does the frequency change if the control voltage increases 0.67 V?
32. Name two conditions for a PLL to acquire lock.

SECTION 13–9 Fiber Optics

33. A certain fiber-optic cable has a core index of refraction of 1.43 and a cladding index of refraction of 1.40. Determine the critical angle.
34. A certain fiber-optic cable has a core index of refraction of 1.55 and a cladding index of refraction of 1.35. If a light ray strikes the core/cladding boundary at an angle of 28.2° , will it be reflected or refracted?

ANSWERS TO SECTION CHECKUPS**SECTION 13–1**

- AM is amplitude modulation. FM is frequency modulation.
- In AM, the modulating signal varies the amplitude of a carrier. In FM, the modulating signal varies the frequency of a carrier.
- AM: 540 kHz to 1640 kHz; FM: 88 MHz to 108 MHz

SECTION 13–2

- A four-quadrant multiplier can handle any combination (4) of positive and negative inputs. A one-quadrant multiplier can only handle two positive inputs, for example.
- SF stands for scale factor. $SF = 10\text{ V}$ for the AD532.
- The transfer function of a linear multiplier defines the output for a given set of inputs.

SECTION 13–3

- Amplitude modulation is the process of varying the amplitude of a carrier signal with a modulating signal.
- Balanced modulation produces no carrier frequency on the output, whereas standard AM does.

3. The carrier signal is the modulated signal and has a sufficiently high frequency for transmission. The modulating signal is a lower-frequency signal that contains information and varies the carrier amplitude according to its waveshape.
4. The upper-side frequency is the sum of the carrier frequency and the modulating frequency. The lower-side frequency is the difference of the carrier frequency and the modulating frequency.
5. By summing the peak carrier voltage and the modulating signal before mixing with the carrier signal.

SECTION 13-4

1. The mixer produces (among other frequencies) a signal representing the difference between the incoming carrier frequency and the local oscillator frequency. This is called the intermediate frequency.
2. The mixer multiplies the carrier and the local oscillator signals.
3. $1000 \text{ kHz} + 350 \text{ kHz} = 1350 \text{ kHz}$, $1000 \text{ kHz} - 350 \text{ kHz} = 650 \text{ kHz}$

SECTION 13-5

1. The filter removes all frequencies except the audio.
2. Only the 1 kHz

SECTION 13-6

1. To amplify the 455 kHz amplitude modulated IF coming from the mixer.
2. The IF center frequency is 455 kHz.
3. The 10 kHz bandwidth allows the upper-side and lower-side frequencies that contain the information to pass.
4. The audio amplifier follows the detector because the detector is the circuit that recovers the audio from the modulated IF.
5. The IF has a response of approximately $455 \text{ kHz} \pm 5 \text{ kHz}$. The typical audio amplifier has a maximum bandwidth from tens of hertz up to about 15 kHz, although for many amplifiers, the bandwidth can be much less than this typical maximum.

SECTION 13-7

1. The frequency variation of an FM signal bears the information.
2. VCO is voltage-controlled oscillator.
3. VCOs are based on the principle of voltage-variable reactance.

SECTION 13-8

1. Phase detector, low-pass filter, and VCO
2. Sometimes a PLL uses an amplifier in the loop.
3. A PLL locks onto and tracks a variable incoming frequency.
4. The lock range specifies how much a lock-on frequency can deviate without the PLL losing lock. The capture range specifies how close the incoming frequency must be from the free-running VCO frequency in order for the PLL to lock.
5. The PLL detects a change in the phase of the incoming signal compared to the VCO signal that indicates a change in frequency. The positive feedback then causes the VCO frequency to change along with the incoming frequency.

SECTION 13-9

1. Fiber is made from pure glass or plastic.
2. Fiber optic cables have a diameter of approximately 100 microns.
3. A fiber optic cable is composed of a core, the cladding, and a protective outer jacket.
4. The angle of incidence is the angle at which light rays strike the surface of the cladding. If the angle of incidence is less than the critical angle, light is refracted rather than being reflected, light enters the cladding and energy is lost.
5. Multimode step index, single-mode step index, and multimode graded index.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 13-1 The output does not change. $V_{\text{out}} = 560 \text{ mV}$.
13-2 627 mV
13-3 Modulate the carrier with a higher-frequency signal.
13-4 The balanced modulator output has the same side frequencies but does not have a carrier frequency.
13-5 $V_p = 0.025 \text{ mV}, f = 455 \text{ kHz}$
13-6 455 kHz
13-7 0.172 V
13-8 A decrease of 6 kHz; 244 kHz
13-9 17.8°

ANSWERS TO SELF-TEST

1. (b) 2. (c) 3. (d) 4. (d) 5. (c) 6. (a) 7. (b)
8. (c) 9. (b) 10. (e) 11. (c) 12. (b) 13. (c) 14. (c)
15. (a) 16. (b)

ANSWERS TO TROUBLESHOOTER'S QUIZ

1. not change 2. not change 3. increase 4. not change

CHAPTER 14

DATA CONVERSION

OUTLINE

- 14-1 Analog Switches
- 14-2 Sample-and-Hold Amplifiers
- 14-3 Interfacing the Analog and Digital Worlds
- 14-4 Digital-to-Analog (D/A) Conversion
- 14-5 Basic Concepts of Analog-to-Digital (A/D) Conversion
- 14-6 Analog-to-Digital (A/D) Conversion Methods
- 14-7 Voltage-to-Frequency (V/F) and Frequency-to-Voltage (F/V) Converters
- 14-8 Troubleshooting

OBJECTIVES

- Explain analog switches and identify each type
- Discuss the operation of sample-and-hold amplifiers
- Discuss analog and digital quantities and general interfacing considerations
- Describe the operation of digital-to-analog converters (DACs)
- Describe A/D conversion
- Discuss the operation of analog-to-digital converters (ADCs)
- Discuss the basic operation of V/F converters and F/V converters
- Troubleshoot DACs and ADCs

KEY TERMS

Analog switch	Resolution
Sample-and-hold	Quantization
Acquisition time	Flash
Analog-to-digital converter (ADC)	Successive approximation
Digital-to-analog converter (DAC)	

INTRODUCTION

Data conversion circuits make interfacing between analog and digital systems possible. Most things in nature occur in analog form. For example, your voice is analog, time is analog, temperature and pressure are analog, and the speed of your vehicle is analog. These quantities and others are first sensed or measured with analog (linear) circuits and are then frequently converted to digital form to facilitate storage, processing, or display.

Also, in many applications, information in digital form must be converted back to analog form. An example of this is digitized music that is stored on a CD. Before you can hear the sounds, the digital information must be converted to its original analog form.

In this chapter, you will study several basic types of circuits found in applications that require data conversion.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

14–1 ANALOG SWITCHES

Analog switches are important in many types of electronic systems where it is necessary to switch signals on and off electronically. Major applications of analog switches are in signal selection, routing, and processing. Analog switches usually incorporate a FET as the basic switching element.

After completing this section, you should be able to

- Explain analog switches and identify each type
- Identify a single-pole–single-throw analog switch
- Identify a single-pole–double-throw analog switch
- Identify a double-pole–single-throw analog switch
- Describe the ADG1212 analog switch IC
- Discuss multiple-channel analog switches

Types of Analog Switches

Three basic types of **analog switches** in terms of their functional operation are

- Single pole–single throw (SPST)
- Single pole–double throw (SPDT)
- Double pole–single throw (DPST)

Figure 14–1 illustrates these three basic types of analog switches. Most analog switches use MOSFETs as the switching device. As you can see, the analog switch consists of a control element and one or more input-to-output paths called *switch channels*.

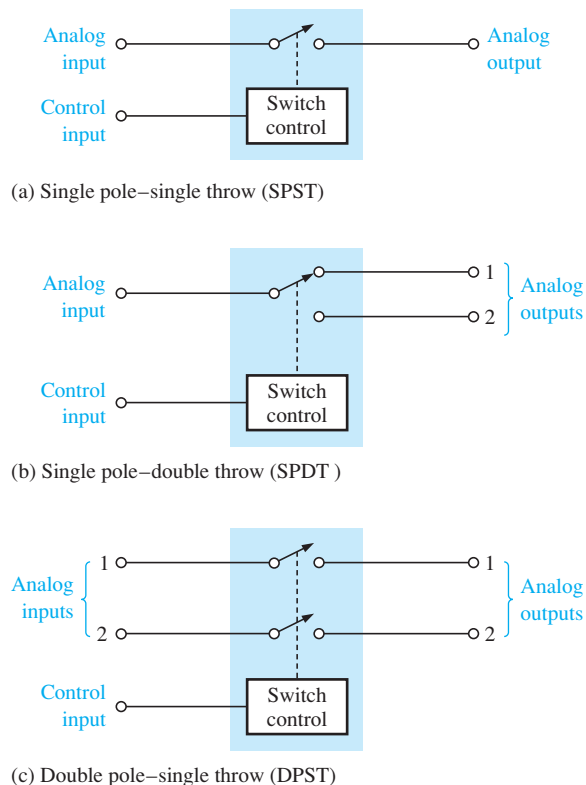


FIGURE 14–1 Basic types of analog switches.

An example of an analog switch is the ADG1212. This IC device has four independently operated SPST switches as shown in Figure 14–2(a). Typical packages are shown in Figure 14–2(b).

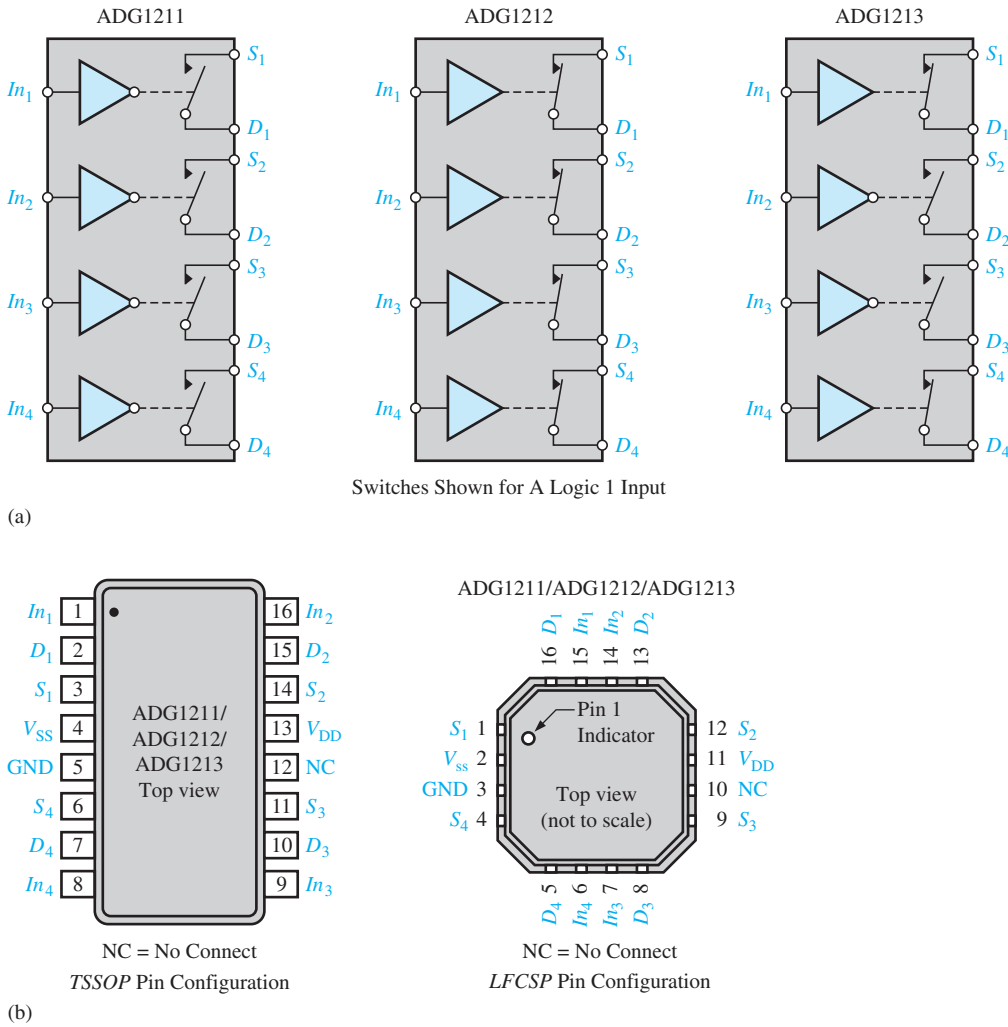


FIGURE 14-2 The ADG12XX family of Quad SPST switches.

The only difference between the ADG1212 and the other two devices in this family is how they respond to input control logic. Refer to Figure 14-2(a), which illustrates how each device responds to a high input control signal. The switches in the ADG1212 close when the input control is at a high logic level and open when the input is low. The ADG1211 control logic is inverted—the switches are closed for a low input and open for a high. The ADG1213 exhibits *break-before-make* switching. Switches 1 and 4 are closed for a high and open for a low. Switches 2 and 3 are open for a high and closed for a low. When used in multiplexer applications, the control inputs to switches 1 and 2 and switches 3 and 4 are tied together. This means that a single high input closes one switch and opens the other. This family of analog switches is 3 V logic compatible with a minimum high voltage of 2.0 V and maximum low of 0.8 V. The data sheet for this family of switches can be found at www.analog.com.

EXAMPLE 14-1

Determine the output waveform of the analog switch in Figure 14-3(a) for the control voltage and analog input voltage shown. Assume the switch closes when the control voltage is high.

 


FIGURE 14-3

SOLUTION

When the control voltage is high, the switch is closed and the analog input passes through to the output. When the control voltage is low, the switch is open and there is no output voltage. The output waveform is shown in Figure 14-3(b) in relation to the other voltages.

PRACTICE EXERCISE*

What will be the output waveform in Figure 14-3 if the frequency of the control voltage is doubled but you keep the same duty cycle?

*Answers are at the end of the chapter.

Multiple-Channel Analog Switches

In data acquisition systems where inputs from several different sources must be independently converted to digital form for processing, a technique called *multiplexing* is used. A separate analog switch is used for each analog source as illustrated in Figure 14-4 for a four-channel system. In this type of application, all of the outputs of the analog switches are connected together to form a common output and only one switch can be closed at a given time. The common switch outputs are connected to the input of a voltage-follower as indicated.

 


FIGURE 14-4 A four-channel analog multiplexer.

An example of an IC analog multiplexer is the AD9300 shown in Figure 14-5. This device contains four analog switches that are controlled by a channel decoder. The inputs A_0 and A_1 determine which one of the four switches is on. If A_0 and A_1 are both low, input In_1 is selected. If A_0 is high and A_1 is low, input In_2 is selected. If A_0 is low and A_1 is high, input In_3 is selected. If A_0 and A_1 are both high, input In_4 is selected. The Enable input controls

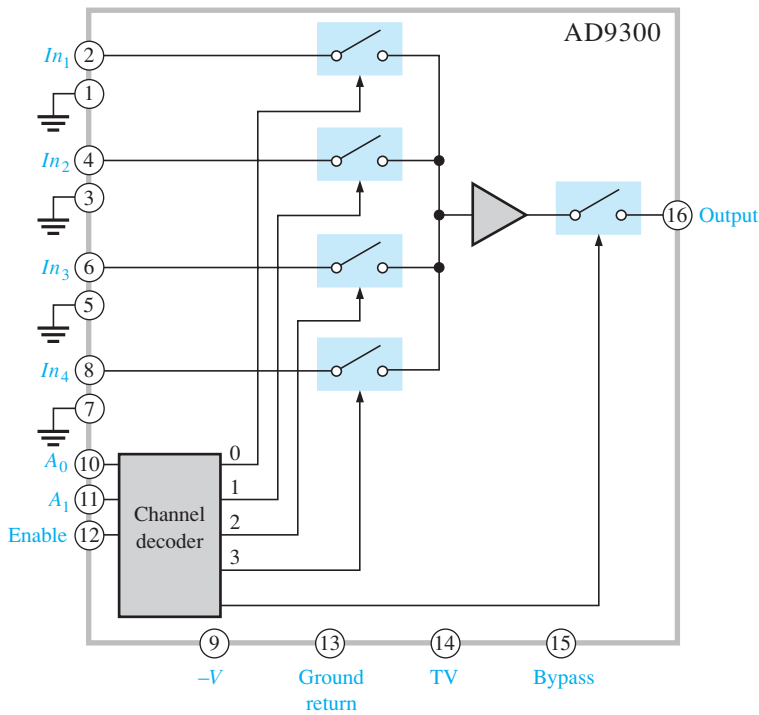


FIGURE 14-5 The AD9300 analog multiplexer.

the switch that connects or disconnects the output. The output is in a high-impedance state when the chip is not enabled, allowing more than one device to be connected together. This idea is shown in System Example 14-1. The AD9300 is capable of switching 4 channels of video for applications including video routing, medical imaging, radar systems, and data acquisition systems. The data sheet for the AD9300 can be found at www.analog.com.

EXAMPLE 14-2

Determine the output waveform of the analog multiplexer in Figure 14-6 for the control inputs and the analog inputs shown.

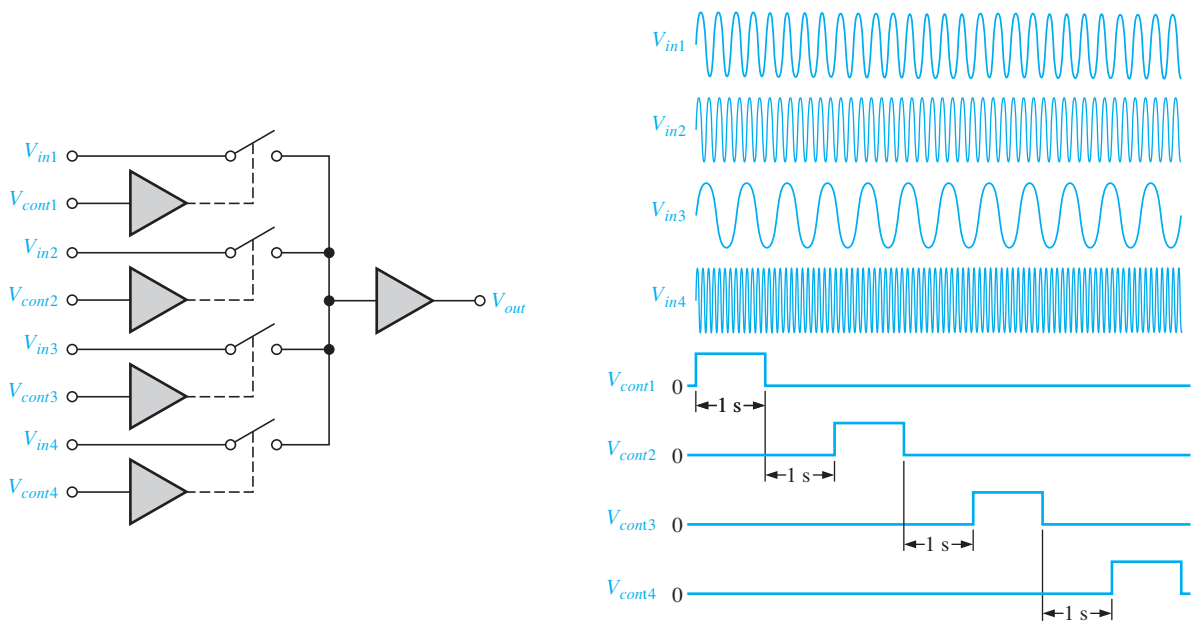



FIGURE 14-6

SOLUTION

When a control input is a high level, the corresponding switch is closed and the analog voltage on its input is switched through to the output. Notice that only one control voltage is high at a time. The inputs to the switches are sinusoidal waves, each having a different frequency. The resulting output is a sequence of different sinusoidal waves that last for one second and that are separated by a one-second interval, as indicated in Figure 14–7.


**PRACTICE EXERCISE**

How is the output waveform in Figure 14–7 affected if the time interval between the control voltage pulses is decreased?

 SYSTEM EXAMPLE 14-1**A Solar Tracking System**

The solar panel control system in this system example shares some of the basic elements of the one introduced in Chapter 4. In this system, there are four solar panels to control, and the system uses stepper motors rather than dc motors. The panels are mounted on an alt-azimuth mounting that moves horizontally and vertically using stepper motors to track the sun, and potentiometers to relay position information to the controller. The control circuitry maintains each solar panel at approximately a 90° angle with respect to the sun's rays. An alt-azimuth arrangement for very large panels is common, because it is mechanically stable and the panels do not need to be mounted as high for ground clearance. Figure SE14–1 shows the basic arrangement of each panel, showing the stepper motors and the position potentiometers.

FIGURE SE14-1 A solar panel with position controls and sensors for azimuth and elevation.

 

A digital controller containing pre-programmed position information for the sun will control all eight stepper motors. Figure SE14–2 shows the block diagram of the control circuits. Our focus in this system is the analog control board and specifically the AD9300 IC, which is the analog multiplexer (MUX). The ADC9300 accepts altitude and elevation voltages from each potentiometer on all four panels and routes the information to an analog-to-digital converter, which changes the analog signals into digital signals for processing.


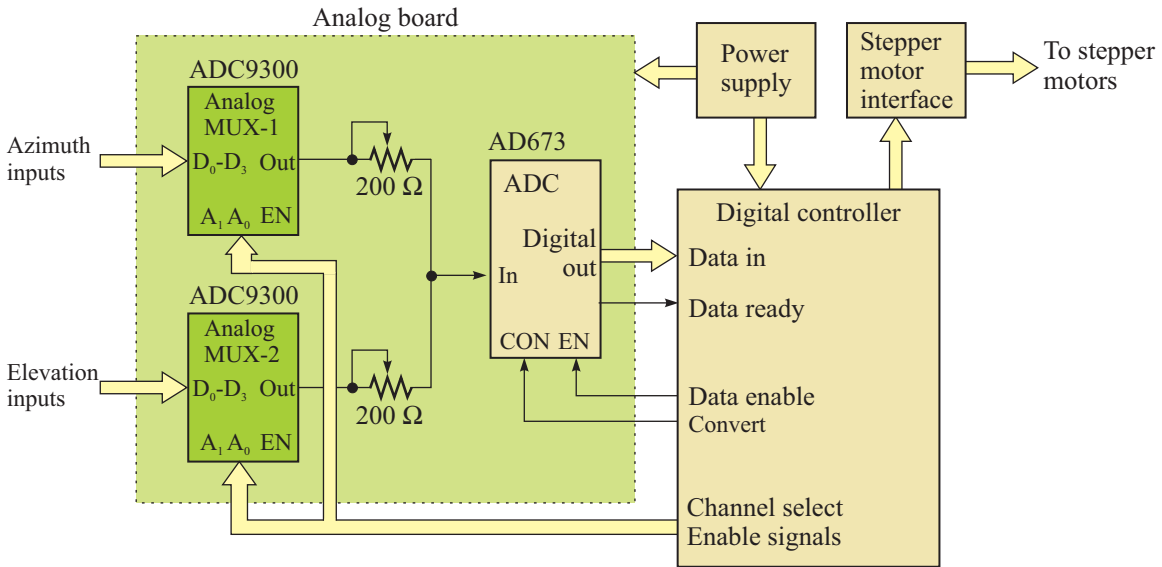


FIGURE SE14-2 Block diagram of the solar panel control system.

Obviously, a solar tracking system requires only occasional adjustments in position to track the sun across the sky. In this system, the controller is mostly idle, but every eight minutes, it wakes up, reads the data, and adjusts all of the trackers. At this time, various signals are generated by the digital controller to read the data. One MUX is enabled and puts the data for one of the potentiometers on its Out line. The analog-to-digital converter converts it to a digital signal for the controller. The controller continues to rapidly generate select and enable signals for the multiplexers, reading the four azimuth and the four elevation position voltages, one at a time. Each resulting digital code is processed by comparing the angle it represents to angular information about solar position based on time of day and date that is stored in the digital controller's memory. Based on its computations, the digital controller issues the proper control signal to the appropriate stepping motor to realign the solar panel for maximum solar energy production.

Figure SE14-3 shows the timing signals for the system. As you can see, the controller generates all of the timing signals necessary to read the position information from the panels. First one analog MUX is enabled and address signals are sent to select a potentiometer to read. A short time later, the controller requests the ADC to do a conversion. After the ADC completes the conversion, it sends a Data ready signal to the controller and the data is then transferred to the controller. The process repeats for the second MUX.

 

A series of A/D conversions occurs every eight minutes.

FIGURE SE14-3 Timing diagram for the solar tracking sequence.

SECTION 14-1 CHECKUP*

1. What is the purpose of an analog switch?
2. What is the basic function of an analog multiplexer?
3. In Figure SE14-2, the outputs of two AD9300s are shown connected through potentiometers to a common input on the ADC. Why is this a valid connection?

*Answers are at the end of the chapter.

14-2 SAMPLE-AND-HOLD AMPLIFIERS

A sample-and-hold amplifier samples an analog input voltage at a certain point in time and retains or holds the sampled voltage for an extended time after the sample is taken. The sample-and-hold process keeps the sampled analog voltage constant for the length of time necessary to allow an analog-to-digital converter (ADC) to convert the voltage to digital form.


After completing this section, you should be able to

- Discuss the operation of sample-and-hold amplifiers
- Describe tracking in a sample-and-hold amplifier
- Define *aperture time*, *aperture jitter*, *acquisition time*, *droop*, and *feedthrough*
- Describe the AD585 sample-and-hold amplifier

A Basic Sample-and-Hold Circuit


A basic **sample-and-hold** circuit consists of an analog switch, a capacitor, and input and output buffer amplifiers as shown in Figure 14-8. The analog switch samples the analog input voltage through the input buffer amplifier, the capacitor (C_H) stores or holds the sampled voltage for a period of time, and the output buffer amplifier provides a high input impedance to prevent the capacitor from discharging quickly.

FIGURE 14-8 A basic sample-and-hold circuit.

 

As illustrated in Figure 14-9, a relatively narrow control voltage pulse closes the analog switch and allows the capacitor to charge to the value of the input voltage. The switch

FIGURE 14-9 Basic action of a sample-and-hold.

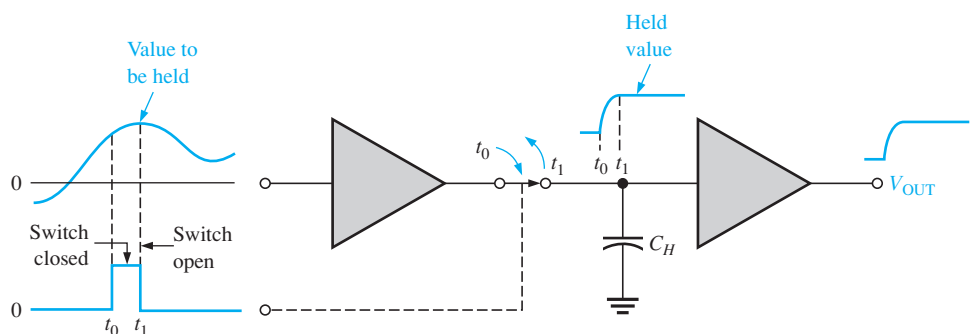

then opens, and the capacitor holds the voltage for a relatively long period of time because of the very high impedance discharge path through the op-amp input. So basically, the sample-and-hold circuit converts an instantaneous value of the analog input voltage to a dc voltage.

Tracking During Sample Time

Perhaps a more appropriate designation for a sample-and-hold amplifier is sample/track-and-hold because the circuit actually tracks the input voltage during the sample interval. As indicated in Figure 14-10, the output follows the input during the time that the control voltage is high; and when the control voltage goes low, the last voltage is held until the next sample interval.


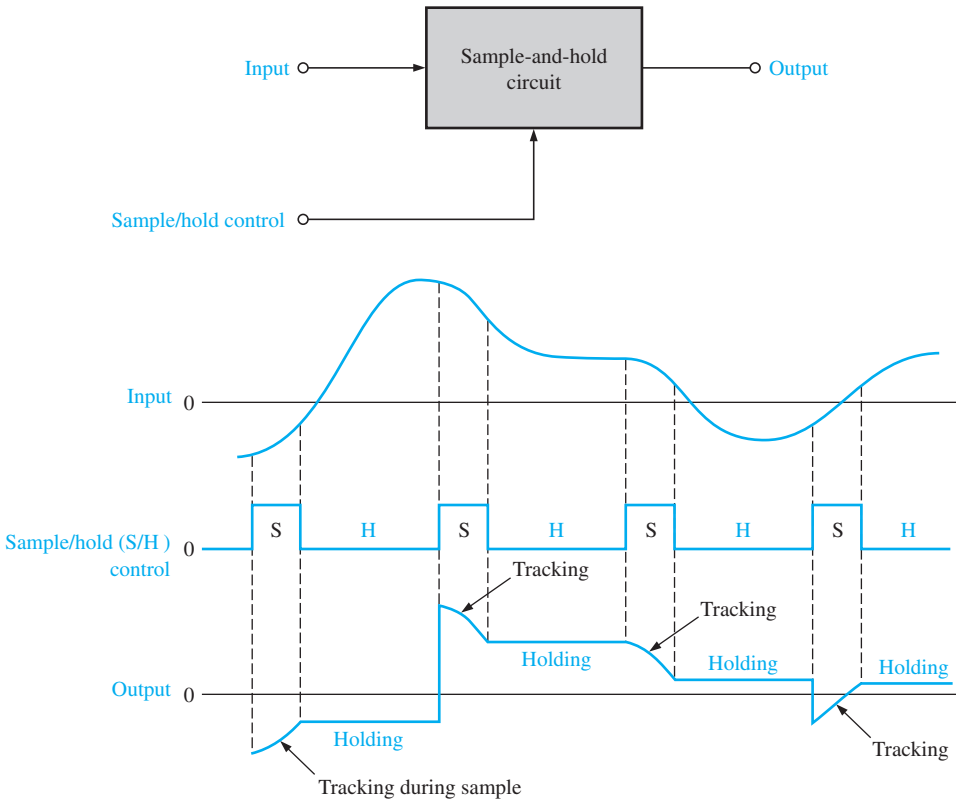


FIGURE 14-10 Example of tracking during a sample-and-hold sequence.

EXAMPLE 14-3

Determine the output voltage waveform for the sample/track-and-hold amplifier in Figure 14-11, given the input and control voltage waveforms.

FIGURE 14-11

 

SOLUTION

During the time that the control voltage is high, the analog switch is closed and the circuit is tracking the input. When the control voltage goes low, the analog switch opens; the last voltage value is held at a constant level until the next time the control voltage goes high. This is shown in Figure 14-12.

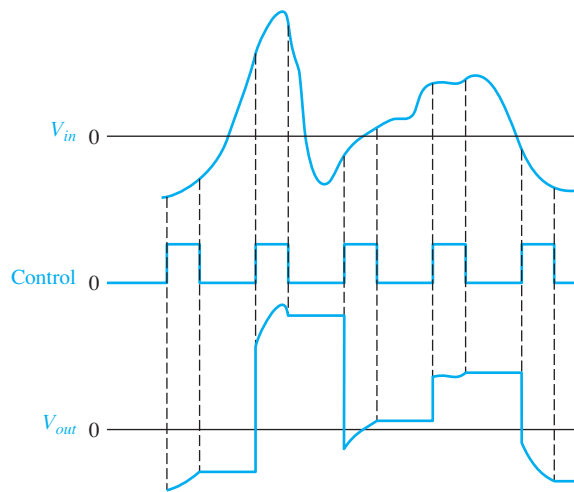


FIGURE 14-12

PRACTICE EXERCISE

Sketch the output voltage waveform for Figure 14-11 if the control voltage frequency is reduced by half.

Performance Specifications


In addition to specifications similar to those of a closed-loop op-amp that were discussed in Chapter 6, several specifications are peculiar to sample-and-hold amplifiers. These include the aperture time, aperture jitter, **acquisition time**, droop, and feedthrough.

- **Aperture time**—the time for the analog switch to fully open after the control voltage switches from its sample level to its hold level. Aperture time produces a delay in the effective sample point.
- **Aperture jitter**—the uncertainty in the aperture time.
- **Acquisition time**—the time required for the device to reach its final value when the control voltage switches from its hold level to its sample level.
- **Droop**—the change in voltage from the sampled value during the hold interval because of charge leaking off the hold capacitor.
- **Feedthrough**—the component of the output voltage that follows the input signal after the analog switch is opened. The inherent capacitance from the input to the output of the switch causes feedthrough.

Each of these parameters is illustrated in Figure 14-13 for an example input voltage waveform.

Sample-and-hold circuits are used in systems requiring analog-to-digital conversion, such as analog data collection systems where various transducers provide the inputs. The sample time of a sample-and-hold circuit is primarily a function of the value of the holding capacitor. In order for the holding capacitor to be fully charged during a short sample time, a low-value holding capacitor is necessary. On the other hand, to achieve a long accurate hold time, a high-value holding capacitor is necessary. It would appear that a sample-and-hold circuit capable of sampling very short samples with long accurate hold times is not possible.

By cascading two sample-and-hold circuits, long hold times of short duration samples can be realized. The first stage has a low-value holding capacitor providing the short sample time. The second stage has a large-value holding capacitor, which allows for longer hold times. In this way both objectives can be achieved.

 

 


FIGURE 14-13 Sample-and-hold amplifier specifications. The effects are exaggerated for clarity. The black curve is the input voltage waveform. The colored curve is output voltage.

A Specific Device

An example of a basic sample-and-hold amplifier is the AD585. The circuit and pin configuration are shown in Figure 14-14. As shown in the figure, this particular device consists of two buffer amplifiers and an analog switch that is controlled by a logic gate. The internal hold capacitor has a value of 100 pF. An additional capacitor can be connected externally in parallel, if necessary, between pins 7 and 8.


 



FIGURE 14-14 The AD585 sample-and-hold amplifier.

The control voltage for establishing the sample/hold intervals is applied between pins 14 and 13 or pins 12 and 13. The input signal to be sampled is applied to pin 2. A potentiometer for nulling out the offset voltage can be connected between pins 3 and 5, and the overall gain of the device can be set to pin 1 or pin 2 without external feedback connections. Two typical configurations are shown in Figure 14-15. Other values of gain can be achieved using external resistors. The data sheet for the AD585 can be found at www.analog.com.

FIGURE 14–15 Two possible configurations of the AD585 sample-and-hold amplifier.

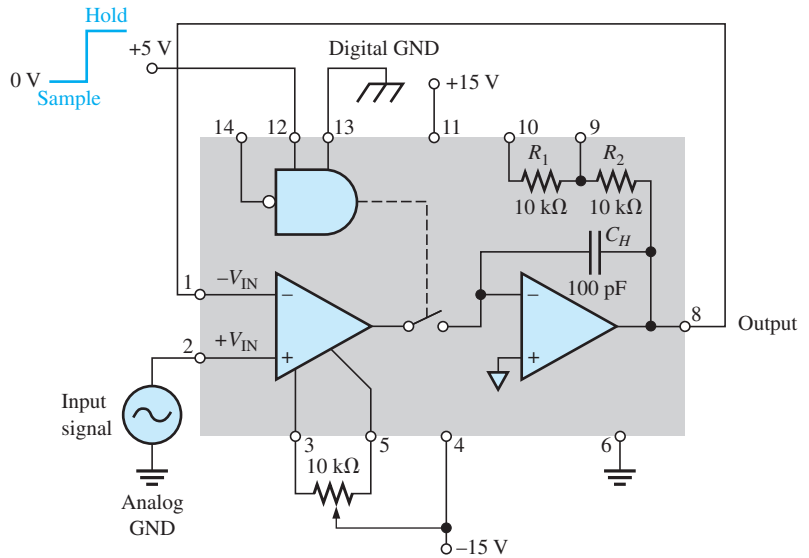

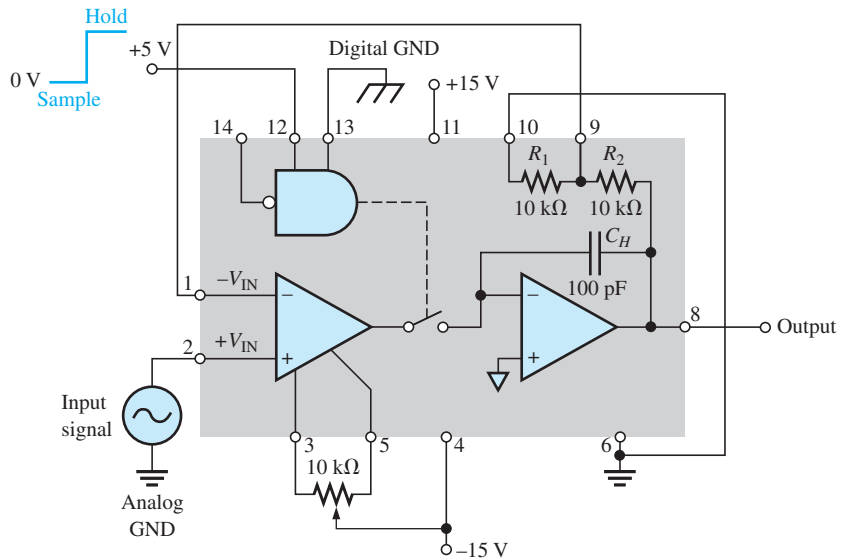(a) Sample and hold with $A_v = +1$ and an optional offset null adjustment



(b) Sample and hold with $A_v = +2$ ($A_v = R_2/R_1 + 1 = 10\text{ k}\Omega/10\text{ k}\Omega + 1 = 2$).

SECTION 14–2 CHECKUP

1. What is the basic function of a sample-and-hold amplifier?
2. In reference to the output of a sample-and-hold amplifier, what does droop mean?
3. Define *aperture time*.
4. What is acquisition time?

14-3 INTERFACING THE ANALOG AND DIGITAL WORLDS

Analog quantities are sometimes called real-world quantities because most physical quantities are analog in nature. Many systems have analog inputs representing quantities, such as temperature, speed, position, pressure, and force. The analog quantity is converted to digital for processing and control, thus it is important to have a basic understanding of the interface between analog and digital quantities. A basic familiarity with the binary number system is assumed for this and the next sections.

After completing this section, you should be able to

- Discuss digital and analog quantities and general interfacing considerations
- Describe an analog quantity
- Describe a digital quantity
- Discuss examples of real-world analog/digital interfacing

Digital and Analog Signals

An analog quantity is one that has a continuous set of values over a given range, as contrasted with discrete values for the digital case. Almost any measurable quantity is analog in nature, such as temperature, pressure, speed, and time. To further illustrate the difference between an analog and a digital representation of a quantity, let's take the case of a voltage that varies over a range from 0 V to +15 V. The analog representation of this quantity takes in all values between 0 and +15 V, of which there is an infinite number.

In a *digital* representation using a 4-bit binary code, only sixteen values can be defined. More values between 0 and +15 can be represented by using more bits in the digital code. So an analog quantity can be represented to a high degree of accuracy with a digital code that specifies discrete values within the range. This concept is illustrated in Figure 14-16, where the analog function shown is a smoothly changing curve that takes on values between 0 V and +15 V. If a 4-bit code is used to represent this curve, each binary number represents a discrete point on the curve.

In Figure 14-16 the voltage on the analog curve is measured, or sampled, at each of thirty-five equal intervals. The voltage at each of these intervals is represented by a 4-bit code as indicated. At this point, we have a series of binary numbers representing various voltage values along the analog curve. This is the basic idea of analog-to-digital (A/D) conversion.

 


FIGURE 14-16 Discrete (digital) points on an analog curve.

An approximation of the analog function in Figure 14–16 can be reconstructed from the sequence of digital numbers that has been generated. Obviously, there will be some error in the reconstruction because only certain values are represented (thirty-six in this example) and not the continuous set of values. If the digital values at all of the thirty-six points are graphed as shown in Figure 14–17, we have a reconstructed function. As you can see, the graph only approximates the original curve because values between the points are not known.


 


FIGURE 14–17 A rough digital reproduction of an analog curve.

To interface between the digital and analog worlds, two basic processes are required. These are analog-to-digital (A/D) conversion and digital-to-analog (D/A) conversion. Analog-to-digital conversion is accomplished by a special integrated circuit called an **analog-to-digital converter (ADC)**. Basically an ADC converts an analog signal into a sequence of digital codes. The codes are input to a computer or other digital device for processing. The following two system examples illustrate the application of these conversion processes.

SYSTEM EXAMPLE 14–2

 

AN ELECTRONIC THERMOSTAT

A simplified block diagram of a digital controller based electronic thermostat is shown in Figure SE14–4. The room temperature sensor produces an analog voltage that is proportional to the temperature. This voltage is increased by the linear amplifier and applied to the analog-to-digital converter (ADC), where it is converted to a digital code and periodically sampled by the controller. For example, suppose the room temperature is 67°F. A specific voltage value corresponding to this temperature appears on the ADC input and is converted to an 8-bit binary number, 0100011.

Internally, the digital controller compares this binary number with a binary number representing the desired temperature (say, 01001000 for 72°F). This desired value has been previously entered from the keypad and stored in a register. The comparison shows that the actual room temperature is less than the desired temperature. As a result, the controller instructs the unit control circuit to turn the furnace on. As the furnace runs, the controller continues to monitor the actual temperature via the ADC. When the actual temperature equals or exceeds the desired temperature, the controller turns the furnace off. The system will have two thresholds (hysteresis) to avoid cycling the furnace too quickly.

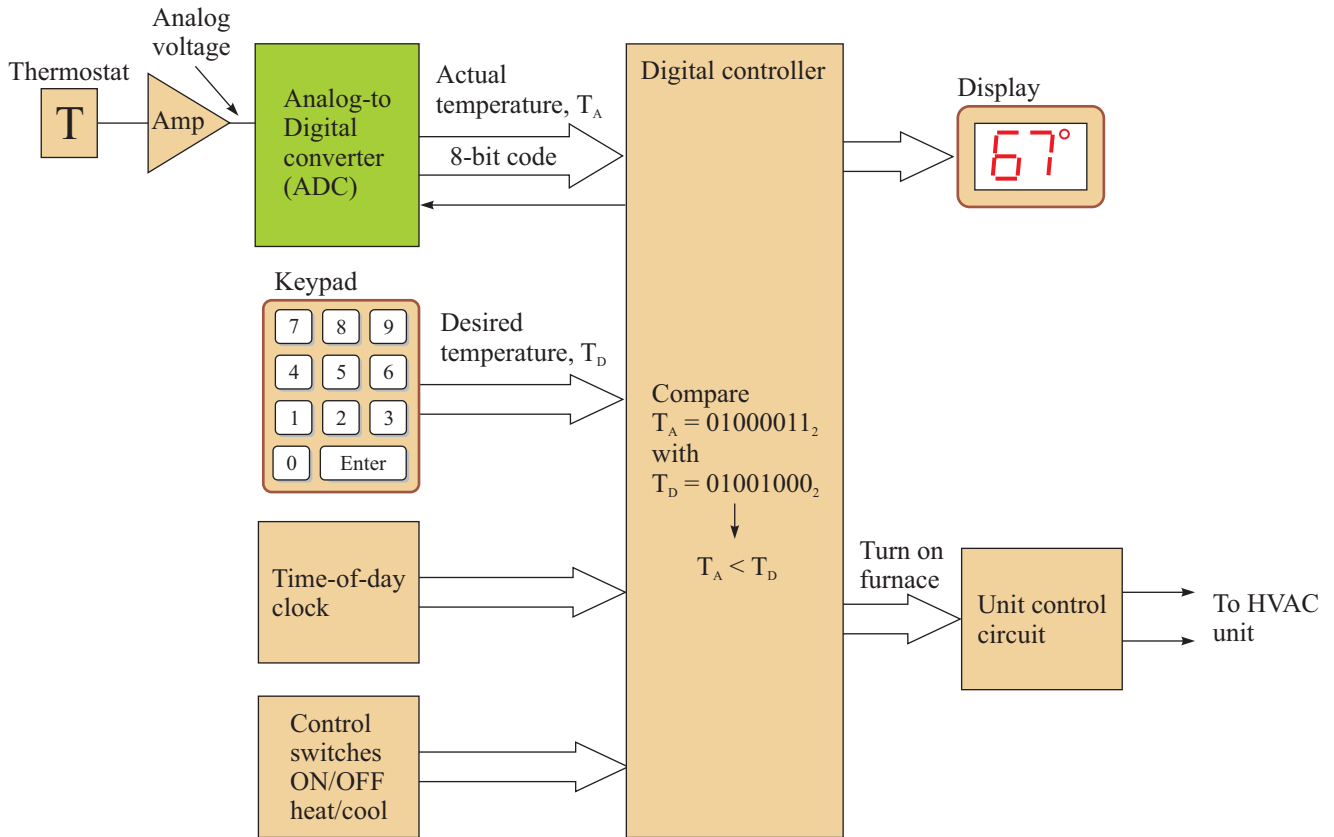


FIGURE SE14-4 An electronic thermostat that uses an ADC.


Some systems require both A/D and D/A conversion. D/A conversion is accomplished by a special integrated circuit called a **digital-to-analog converter (DAC)**. A DAC is defined as a device in which information in digital form is converted to an analog form. The following system example is one with both a ADC and a DAC.

SYSTEM EXAMPLE 14-3

THE ADC AND DAC IN A CELLULAR PHONE

Figure SE14-5 shows a simplified block diagram of a digital cell phone. Our focus is the ADC and DAC necessary to convert between the analog voice signal and a digital voice format and back. The voice **codec** (codec is the abbreviation for coder/decoder) contains, among other functions, the ADC and DAC. For transmission, the voice signal from the microphone is converted to digital form by the ADC in the codec and then it goes to a digital signal processor (DSP) for processing. Digital Signal Processors are basically specialized computers designed to run a built-in set of instructions in real time. From the DSP, the digital signal goes to the rf (radio frequency) section where it is modulated and changed to the radio frequency for transmission to a cell phone relay point (tower).

When there is an incoming message, the rf signal containing voice data is picked up by the antenna, demodulated, and changed to a digital signal. The digital signal is then applied to the DSP for processing, after which it goes to the codec for conversion back to the original voice signal by the DAC. It is then amplified and applied to the speaker.

 

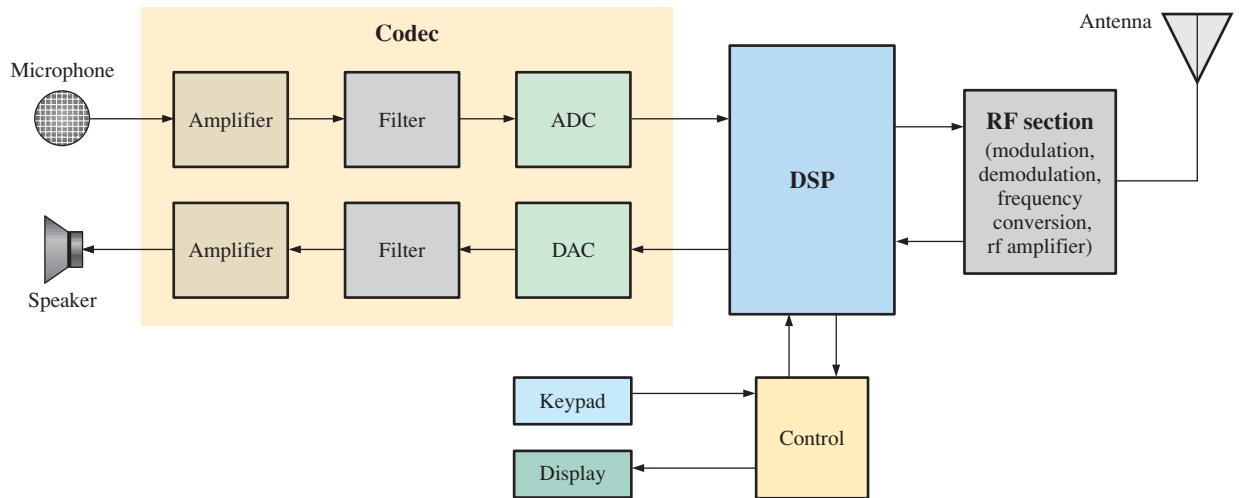


FIGURE SE14-5 Simplified block diagram of a digital cellular phone.

SECTION 14-3 CHECKUP

1. In what form do quantities appear naturally?
2. Explain the basic purpose of A/D conversion.
3. Explain the basic purpose of D/A conversion.

14-4 DIGITAL-TO-ANALOG (D/A) CONVERSION

A **digital-to-analog converter** is a device in which information in digital form is converted to analog form. D/A conversion is an important part of many systems. In this section, we will examine two basic types of digital-to-analog converters (DACs) and learn about their performance characteristics. The binary-weighted-input DAC was introduced in Chapter 8 as an example of a scaling adder application and is covered more thoroughly in this section. Also, a more commonly used configuration called the $R/2R$ ladder DAC is introduced.

After completing this section, you should be able to

- Describe the operation of digital-to-analog converters (DACs)
- Describe the binary-weighted-input DAC
- Describe the $R/2R$ ladder DAC
- Discuss resolution, accuracy, linearity, monotonicity, and settling time

Binary-Weighted-Input Digital-to-Analog Converter

The binary-weighted-input DAC uses a resistor network with resistance values that represent the binary weights of the input bits of the digital code. Figure 14-18 shows a 4-bit DAC of this type. Each of the input resistors will either have current or have no current, depending on the input voltage level. If the input voltage is zero (binary 0), the current is also zero. If the input voltage is high (binary 1), the amount of current depends on the input resistor value and is different for each input resistor, as indicated by the meters.

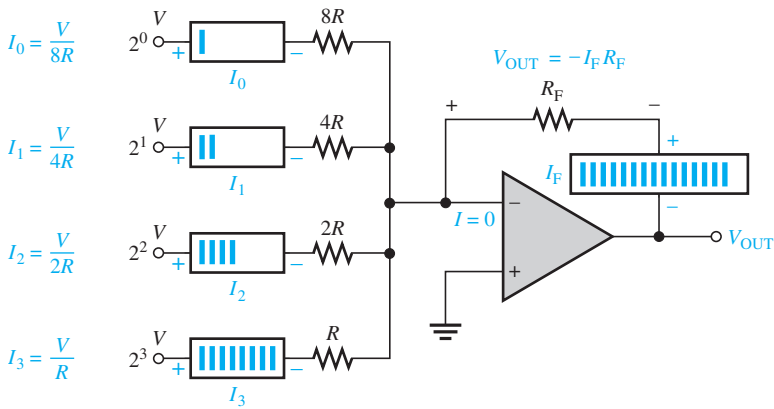


FIGURE 14-18 A 4-bit DAC with binary-weighted inputs.

Since there is practically no current at the op-amp inverting ($-$) input, all of the input currents sum together and go through R_F . Since the inverting input is at 0 V (virtual ground), the drop across R_F is equal to the output voltage, so $V_{OUT} = -I_F R_F$. Notice that V_{OUT} is negative because of inversion.

The values of the input resistors are chosen to be inversely proportional to the binary weights of the corresponding input bits. The lowest-value resistor (R) corresponds to the highest binary-weighted input (2^3). The other resistors are multiples of R (that is, $2R$, $4R$, and $8R$) and correspond to the binary weights 2^2 , 2^1 , and 2^0 , respectively. The input currents are also proportional to the binary weights. Thus, the output voltage is proportional to the sum of the binary weights because the sum of the currents is through R_F .

One of the disadvantages of this type of DAC is the number of different resistor values. For example, an 8-bit converter requires eight resistors, ranging from some value of R to $128R$ in binary-weighted steps. This range of resistors requires tolerances of one part in 255 (less than 0.5%) to accurately convert the input, making this type of DAC more difficult to mass-produce.

EXAMPLE 14-4

Determine the output of the DAC in Figure 14-19(a) if the waveforms representing a sequence of 4-bit binary numbers in Figure 14-19(b) are applied to the inputs. Input D_0 is the least significant bit (LSB).

 


FIGURE 14-19

SOLUTION

First, determine the current for each of the weighted inputs. Since the inverting ($-$) input of the op-amp is at 0 V (virtual ground) and a binary 1 corresponds to +5 V, the current through any of the input resistors is 5 V divided by the resistance value.

$$I_0 = \frac{5\text{ V}}{40\text{ k}\Omega} = 0.125\text{ mA}$$

$$I_1 = \frac{5\text{ V}}{20\text{ k}\Omega} = 0.25\text{ mA}$$

$$I_2 = \frac{5 \text{ V}}{10 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$I_3 = \frac{5 \text{ V}}{5 \text{ k}\Omega} = 1.0 \text{ mA}$$

There is essentially no current at the inverting op-amp input because of its extremely high impedance. Therefore, assume that all of the current goes through the feedback resistor R_F . Since one end of R_F is at 0 V (virtual ground), the drop across R_F equals the output voltage, which is negative with respect to virtual ground.

$$V_{\text{OUT}(D_0)} = (1.0 \text{ k}\Omega)(-0.125 \text{ mA}) = -0.125 \text{ V}$$


$$V_{\text{OUT}(D_1)} = (1.0 \text{ k}\Omega)(-0.25 \text{ mA}) = -0.25 \text{ V}$$

$$V_{\text{OUT}(D_2)} = (1.0 \text{ k}\Omega)(-0.5 \text{ mA}) = -0.5 \text{ V}$$

$$V_{\text{OUT}(D_3)} = (1.0 \text{ k}\Omega)(-1.0 \text{ mA}) = -1.0 \text{ V}$$

From Figure 14–19(b), the first binary input code is 0000, which produces an output voltage of 0 V. The next input code is 0001, which produces an output voltage of -0.125 V . The next code is 0010, which produces an output voltage of -0.25 V . The next code is 0011, which produces an output voltage of $-0.125 \text{ V} + -0.25 \text{ V} = -0.375 \text{ V}$. Each successive binary code increases the output voltage by -0.125 V , so for this particular straight binary sequence on the inputs, the output is a stairstep waveform going from 0 V to -1.875 V in -0.125 V steps. This is shown in Figure 14–20.

FIGURE 14–20 Output of the DAC in Figure 14–19.

 

PRACTICE EXERCISE

What size are the output steps of the DAC if the feedback resistance is changed to $2.0 \text{ k}\Omega$?



The $R/2R$ Ladder Digital-to-Analog Converter

Another method of D/A conversion is the $R/2R$ ladder, as shown in Figure 14–21 for four bits. It overcomes one of the problems in the binary-weighted-input DAC in that it requires only two resistor values.


Start by assuming that the D_3 input is at a high level ($+5 \text{ V}$) and the others are at a low level (ground, 0 V). This condition represents the binary number 1000. A circuit analysis will show that this reduces to the equivalent form shown in Figure 14–22(a). Essentially no current goes through the $2R$ equivalent resistance because the inverting input is at virtual ground. Thus, all of the current ($I = 5 \text{ V}/2R$) through R_7 also goes through R_F , and the output voltage is -5 V .

Figure 14–22(b) shows the equivalent circuit when the D_2 input is at $+5 \text{ V}$ and the others are at ground. This condition represents 0100. If we thevenize looking from R_8 , we


FIGURE 14–21 An $R/2R$ ladder DAC.

 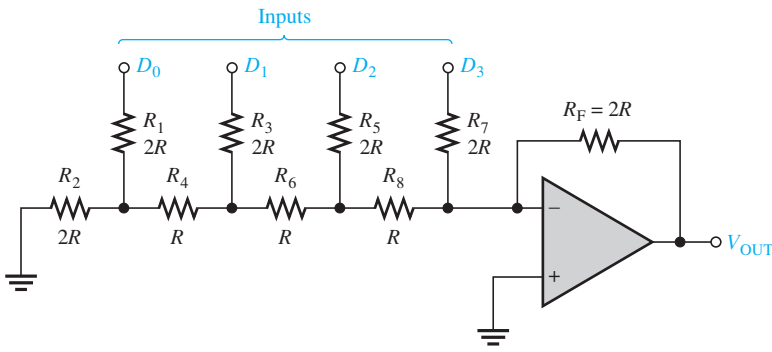

 
(a) Equivalent circuit for $D_3 = 1$, $D_2 = 0$, $D_1 = 0$, $D_0 = 0$



 (b) Equivalent circuit for $D_3 = 0$, $D_2 = 1$, $D_1 = 0$, $D_0 = 0$



 (c) Equivalent circuit for $D_3 = 0$, $D_2 = 0$, $D_1 = 1$, $D_0 = 0$



(d) Equivalent circuit for $D_3 = 0$, $D_2 = 0$, $D_1 = 0$, $D_0 = 1$

FIGURE 14–22 Analysis of the $R/2R$ ladder DAC.

get 2.5 V in series with R , as shown in part (b).¹ This results in a current through R_F of $I = -2.5 \text{ V}/2R$, which gives an output voltage of -2.5 V . Keep in mind that there is no current at the op-amp inverting input and that there is no current through the equivalent resistance to ground because it has 0 V across it, due to the virtual ground.


Figure 14–22(c) shows the equivalent circuit when the D_1 input is at +5 V and the others are at ground. Again thevenizing looking from R_8 , we get 1.25 V in series with R as shown. This results in a current through R_F of $I = -1.25 \text{ V}/2R$, which gives an output voltage of -1.25 V .

In part (d) of Figure 14–22, the equivalent circuit representing the case where D_0 is at +5 V and the other inputs are at ground is shown. Thevenizing from R_8 gives an equivalent of 0.625 V in series with R as shown. The resulting current through R_F is $I = -0.625 \text{ V}/2R$, which gives an output voltage of -0.625 V .

Notice that each successively lower-weighted input produces an output voltage that is halved, so that the output voltage is proportional to the binary weight of the input bits.

In systems that use an $R/2R$ ladder, a monolithic IC is almost always used. The actual value of the resistors in an $R/2R$ ladder does not affect the accuracy of the circuit; however, resistor ratios should be matched as closely as possible. Constructing the ladder network on a monolithic IC provides much better matching of the R and $2R$ values, in the same way that transistor arrays provide better device matching than individual discrete devices. Thin-film monolithic $R/2R$ networks constructed on the same substrate are significantly superior to systems produced using discrete resistors.

There is another source of system inaccuracy in $R/2R$ networks that is often overlooked. The inputs applied to the $2R$ input resistors are switched between the reference voltage and ground. The resistance of the switch itself can be significant enough to affect the accuracy of the ladder network. By using automated laser trimming techniques, the $2R$ legs of the ladder can be trimmed to compensate for switch resistance, thus improving network accuracy.

 

SYSTEM NOTE

Performance Characteristics of Digital-to-Analog Converters

The performance characteristics of a DAC include resolution, accuracy, linearity, monotonicity, and settling time, each of which is discussed in the following list:

- **Resolution.** The resolution of a DAC is the reciprocal of the maximum number of discrete steps in the output. Resolution, of course, is dependent on the number of input bits. For example, a 4-bit DAC has a resolution of one part in $2^4 - 1$ (one part in fifteen). Expressed as a percentage, this is $(1/15)100 = 6.67\%$. The total number of discrete steps equals $2^n - 1$, where n is the number of bits. Resolution can also be expressed as the number of bits that are converted.
- **Accuracy.** Accuracy is a comparison of the actual output of a DAC with the expected output. It is expressed as a percentage of a full-scale, or maximum, output voltage. For example, if a converter has a full-scale output of 10 V and the accuracy is $\pm 0.1\%$, then the maximum error for any output voltage is $(10 \text{ V})(0.001) = 10 \text{ mV}$. Ideally, the accuracy should be no worse than $\pm 1/2$ of a least significant bit (LSB). For an 8-bit converter, the least significant bit is 0.39% of full scale. The accuracy should be approximately $\pm 0.2\%$.
- **Linearity.** A linear error is a deviation from the ideal straight-line output of a DAC. A special case is an offset error, which is the amount of output voltage when the input bits are all zeros.
- **Monotonicity.** A DAC is monotonic if it does not miss any steps when it is sequenced over its entire range of input bits.

¹Section 1–3 describes the Thevenin equivalent circuit and how to thevenize.

- **Settling time.** Settling time is normally defined as the time it takes a DAC to settle within $\pm 1/2$ LSB of its final value when a change occurs in the input code.

EXAMPLE 14-5

Determine the resolution, expressed as a percentage, of (a) an 8-bit DAC and (b) a 12-bit DAC.

SOLUTION

(a) For the 8-bit converter,

$$\frac{1}{2^8 - 1} \times 100 = \frac{1}{255} \times 100 = \mathbf{0.392\%}$$

(b) For the 12-bit converter,

$$\frac{1}{2^{12} - 1} \times 100 = \frac{1}{4095} \times 100 = \mathbf{0.0244\%}$$

PRACTICE EXERCISE

Determine the percent resolution for an 18-bit converter.

SECTION 14-4 CHECKUP

1. What is the disadvantage of the DAC with binary-weighted inputs?
2. What is the resolution of a 4-bit DAC?
3. What is the advantage of a monolithic IC over a discrete circuit for an R/2R ladder?

14-5 BASIC CONCEPTS OF ANALOG-TO-DIGITAL (A/D) CONVERSION

As you have seen, analog-to-digital conversion is the process by which an analog quantity is converted to digital form. A/D conversion is necessary when measured quantities must be in digital form for processing in a computer or for display or storage. Basic concepts of A/D conversion including resolution, conversion time, sampling theory, and quantization error are introduced in this section.

After completing this section, you should be able to

- Describe A/D conversion
- Define *resolution*
- Explain conversion time
- Discuss sampling theory
- Define *quantization error*

Resolution

An analog-to-digital converter (ADC) translates a continuous analog signal into a series of binary numbers. Each binary number represents the value of the analog signal at the time of

conversion. The **resolution** of an ADC can be expressed as the number of bits (binary digits) used to represent each value of the analog signal. A 4-bit ADC can represent sixteen different values of an analog signal because $2^4 = 16$. An 8-bit ADC can represent 256 different values of an analog signal because $2^8 = 256$. A 12-bit ADC can represent 4096 different values of the analog signal because $2^{12} = 4096$. The more bits, the more accurate is the conversion and the greater is the resolution because more values of a given analog signal can be represented.

Resolution is basically illustrated in Figure 14–23 using the analog voltage ramp in part (a). For the case of 3-bit resolution as shown in part (b), only eight values of the voltage ramp can be represented by binary numbers. D/A reconstruction of the ramp using the eight binary values results in the stair-step approximation shown. For the case of 4-bit resolution as shown in part (c), sixteen values can be represented, and D/A reconstruction results in a more accurate 16-step approximation as shown. For the case of 5-bit resolution as shown in part (d), D/A reconstruction produces an even more accurate 32-step approximation of the ramp.

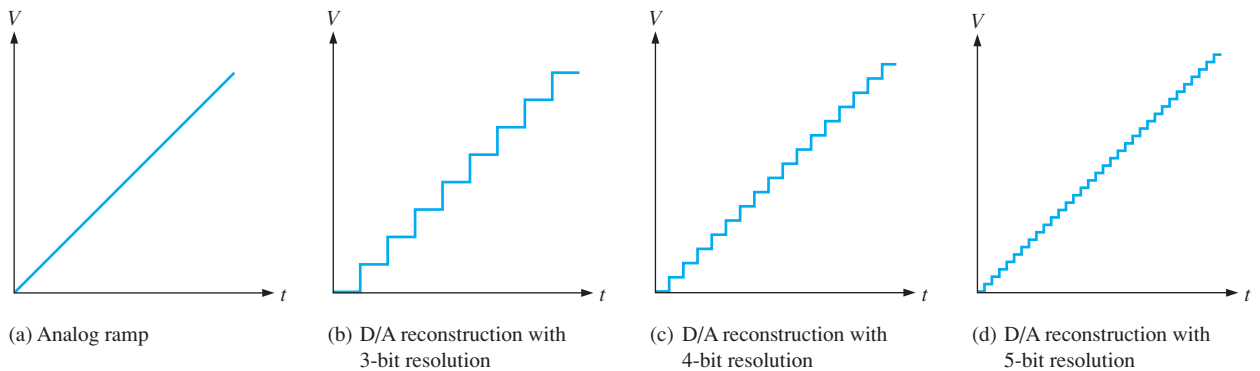


FIGURE 14–23 Illustration of the effect of resolution on the representation of an analog signal (a ramp in this case).

Conversion Time

In addition to resolution, another important characteristic of ADCs is conversion time. The conversion of a value on an analog waveform into a digital quantity is not an instantaneous event, but it is a process that takes a certain amount of time. The conversion time can range from microseconds for fast converters to milliseconds for slower devices. Conversion time is illustrated in a basic way in Figure 14–24. As you can see, the value of the analog voltage to be converted occurs at time t_0 but the conversion is not complete until time t_1 .

 


FIGURE 14–24 An illustration of A/D conversion time.

Sampling Theory

In A/D conversion, an analog waveform is sampled at a given point and the sampled value is then converted to a binary number. Since it takes a certain interval of time to accomplish the conversion, the number of samples of an analog waveform during a given period of time is limited. For example, if a certain ADC can make one conversion in 1 ms, it can make 1000 conversions in one second. That is, it can convert 1000 different analog values to digital form in a one-second interval.

In order to represent an analog waveform, the minimum sample rate must be greater than twice the maximum frequency component of the analog signal. This minimum sampling rate is known as the **Nyquist rate**. At the Nyquist rate, an analog signal is sampled and converted more than two times per cycle, which establishes the fundamental frequency of the analog signal. Filtering can be used to obtain a facsimile of the original signal after D/A conversion. Obviously, a greater number of conversions per cycle of the analog signal results in a more accurate representation of the analog signal. This is illustrated in Figure 14-25 for two different sample rates. The lower waveforms are the D/A reconstructions for various sample rates.

 


FIGURE 14-25 Illustration of two sampling rates.

Quantization Error

The term **quantization** in this context refers to determining a value for an analog quantity. Ideally, we would like to determine a value at a given instant and convert it immediately to digital form. This is, of course, impossible because of the conversion time of ADCs. Since an analog signal may change during a conversion time, its value at the end of the conversion time may not be the same as it was at the beginning (unless the input is a constant dc). This change in the value of the analog signal during the conversion time produces what is called the **quantization error**, as illustrated in Figure 14-26.

One way to avoid or at least minimize quantization error is to use a sample-and-hold circuit at the input to the ADC. As you learned in Section 14-2, a sample-and-hold amplifier quickly samples the analog input and then holds the sampled value for a certain time. When used in conjunction with an ADC, the sample-and-hold is held constant for the duration of the conversion time. This allows the ADC to convert a constant value to digital form and avoids the quantization error. A basic illustration of this process is shown in Figure 14-27. When compared to the conversion in Figure 14-26, you can see that a more accurate representation of the analog input at the desired sample point is achieved.

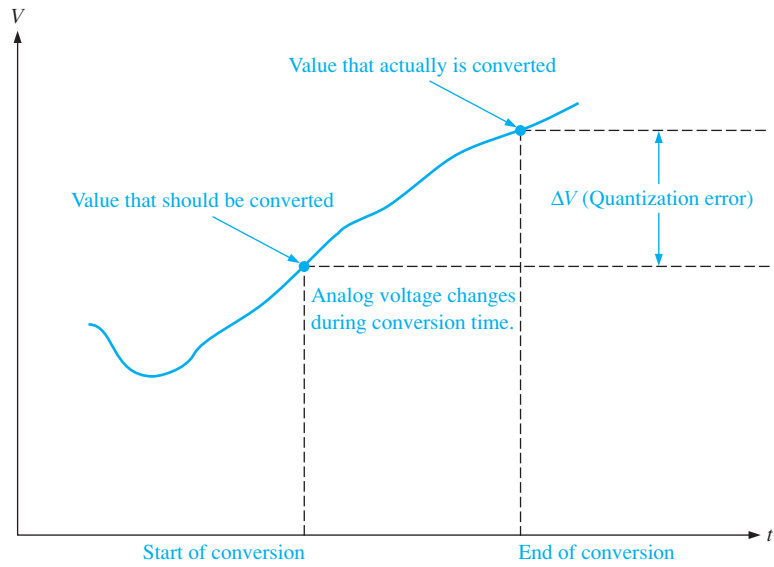


FIGURE 14-26 Illustration of quantization error in A/D conversion.

 


FIGURE 14-27 Using a sample-and-hold amplifier to avoid quantization error.

SECTION 14-5 CHECKUP

1. What is conversion time?
2. According to sampling theory, what is the minimum sampling rate for a 100 Hz sine wave?
3. Basically, how does a sample-and-hold circuit avoid quantization error in A/D conversion?

14-6 ANALOG-TO-DIGITAL (A/D) CONVERSION METHODS

Now that you are familiar with some basic A/D conversion concepts, we will look at several methods for A/D conversion. These methods are flash (simultaneous), staircase ramp, tracking, single-slope, dual-slope, and successive approximation. The flash and dual-slope methods were introduced in Chapter 8 as examples of op-amp applications. Some of that material is reviewed and expanded upon in this section.

After completing this section, you should be able to

- Discuss the operation of analog-to-digital converters (ADCs)
- Describe the flash ADC
- Describe the staircase-ramp ADC
- Describe the tracking ADC
- Describe the single-slope ADC
- Describe the dual-slope ADC
- Describe the successive-approximation ADC

Flash (Simultaneous) Analog-to-Digital Converter

The **flash** (simultaneous) method utilizes comparators that compare reference voltages with the analog input voltage. When the analog voltage exceeds the reference voltage for a given comparator, a high-level output is generated. Figure 14-28 shows a 3-bit converter

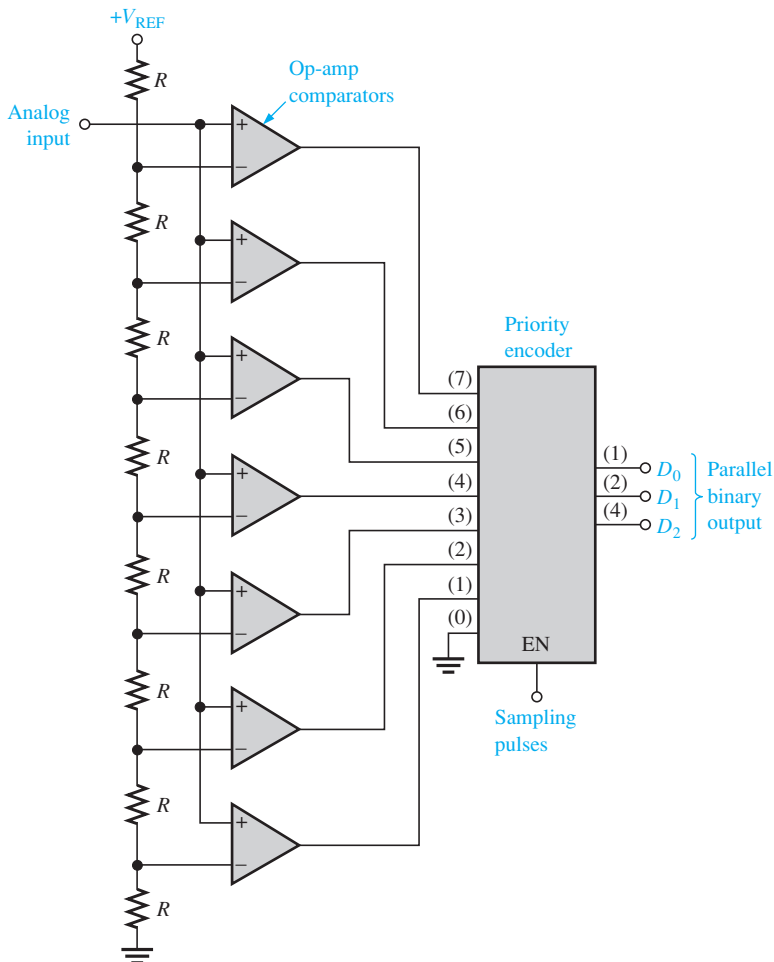


FIGURE 14-28 A 3-bit flash ADC.

that uses seven comparator circuits; a comparator is not needed for the all-0s condition. A 4-bit converter of this type requires fifteen comparators. In general, $2^n - 1$ comparators are required for conversion to an n -bit binary code. The large number of comparators necessary for a reasonable-sized binary number is one of the disadvantages of the flash ADC. Its chief advantage is that it provides a fast conversion time.

The reference voltage for each comparator is set by the resistive voltage-divider network. The output of each comparator is connected to an input of the priority encoder. The encoder is sampled by a pulse on the Enable input, and a 3-bit binary code representing the value of the analog input appears on the encoder's outputs. The binary code is determined by the highest-order input having a high level.

The sampling rate determines the accuracy with which the sequence of digital codes represents the analog input of the ADC. The more samples taken in a given unit of time, the more accurately the analog signal is represented in digital form.

The following example illustrates the basic operation of the flash ADC in Figure 14-28.

EXAMPLE 14-6

Determine the binary code output of the 3-bit flash ADC for the analog input signal in Figure 14-29 and the sampling pulses (encoder Enable) shown. For this example, $V_{REF} = +8\text{ V}$.

 


FIGURE 14-29 Sampling of values on an analog waveform for conversion to digital form.

SOLUTION

The resulting A/D output sequence is listed as follows and shown in the waveform diagram of Figure 14-30 in relation to the sampling pulses.

100, 110, 111, 110, 100, 010, 000, 001, 011, 101, 110, 111

 


FIGURE 14-30 Resulting digital outputs for sampled values. Output D_0 is the least significant bit (LSB).

PRACTICE EXERCISE

If the amplitude of the analog voltage in Figure 14-29 is reduced by half, what will the A/D output sequence be?

Stairstep-Ramp Analog-to-Digital Converter

The stairstep-ramp method of A/D conversion is also known as the *digital-ramp* or the *counter* method. It employs a DAC and a binary counter to generate the digital value of an analog input. Figure 14-31 shows a diagram of this type of converter.

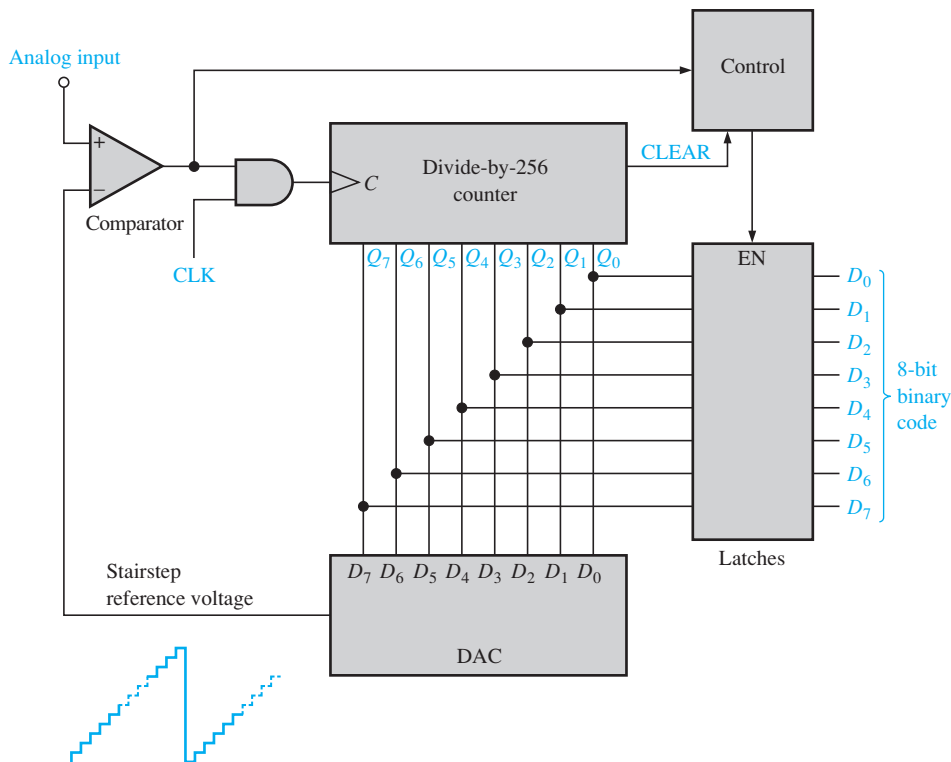


FIGURE 14-31 Stairstep-ramp ADC (8 bits).

Assume that the counter begins in the reset state (all 0s) and the output of the DAC is zero. Now assume that an analog voltage is applied to the input. When it exceeds the reference voltage (output of DAC), the comparator switches to a high-level output state and enables the AND gate. The clock pulses begin advancing the counter through its binary states, producing a stairstep reference voltage from the DAC. The counter continues to advance from one binary state to the next, producing successively higher steps in the reference voltage. When the stairstep reference voltage reaches the analog input voltage, the comparator output will go to its low level and disable the AND gate, thus cutting off the clock pulses to stop the counter. The binary state of the counter at this point equals the number of steps in the reference voltage required to make the reference equal to or greater than the analog input. This binary number, of course, represents the value of the analog input. The control logic loads the binary count into the latches and resets the counter, thus beginning another count sequence to sample the input value.

The stairstep-ramp method is slower than the flash method because, in the worst case of maximum input, the counter must sequence through its maximum number of states before a conversion occurs. For an 8-bit conversion, this means a maximum of 256 counter

states. Figure 14–32 illustrates a conversion sequence for a 4-bit conversion. Notice that for each sample, the counter must count from zero up to the point at which the staircase reference voltage reaches the analog input voltage. The conversion time varies, depending on the analog voltage.

 


FIGURE 14–32 Example of a 4-bit conversion, showing an analog input and the staircase reference voltage.

Tracking Analog-to-Digital Converter

The tracking method uses an up/down counter (a counter that can go either way in a binary sequence) and is faster than the staircase-ramp method because the counter is not reset after each sample, but rather tends to track the analog input. Figure 14–33 shows a typical 8-bit tracking ADC.

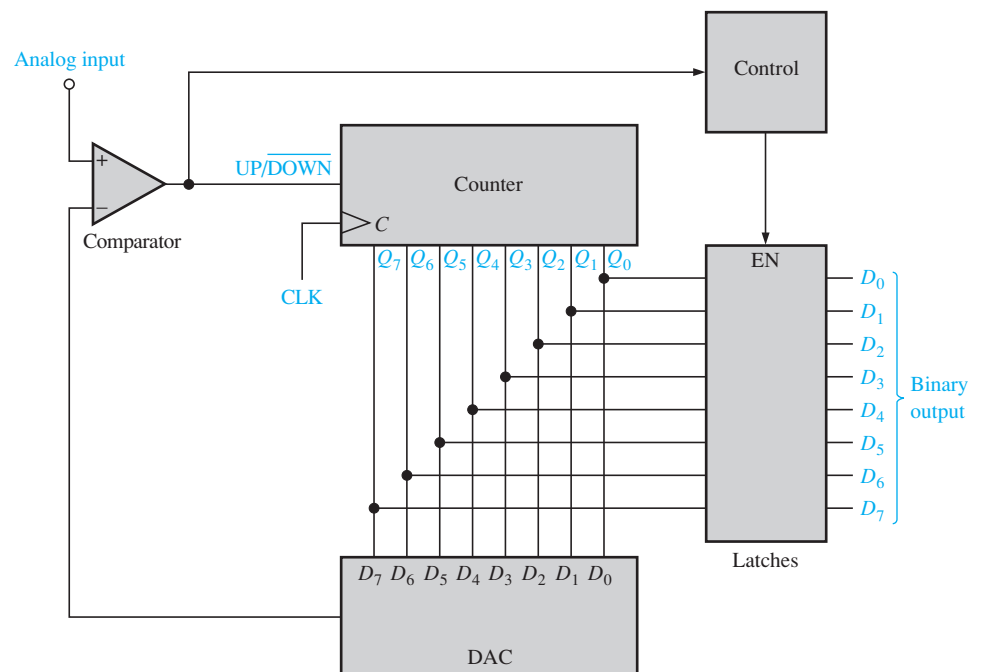


FIGURE 14–33 An 8-bit tracking ADC.

As long as the DAC reference voltage is less than the analog input, the comparator output level is high, putting the counter in the UP mode, which causes it to produce an up

sequence of binary counts. This causes an increasing stairstep reference voltage out of the DAC, which continues until the stairstep reaches the value of the input voltage.

When the reference voltage equals the analog input, the comparator's output switches to its low level and puts the counter in the DOWN mode, causing it to back up one count. If the analog input is decreasing, the counter will continue to back down in its sequence and effectively track the input. If the input is increasing, the counter will back down one count after the comparison occurs and then will begin counting up again. When the input is constant, the counter backs down one count when a comparison occurs. The reference output is now less than the analog input, and the comparator output goes to its high level, causing the counter to count up. As soon as the counter increases one state, the reference voltage becomes greater than the input, switching the comparator to its low-output state. This causes the counter to back down one count. This back-and-forth action continues as long as the analog input is a constant value, thus causing an oscillation between two binary states in the ADC output. This is a disadvantage of this type of converter.

Figure 14-34 illustrates the tracking action of this type of ADC for a 4-bit conversion.

 


FIGURE 14-34 Tracking action of an ADC.

Single-Slope Analog-to-Digital Converter

Unlike the previous two methods, the single-slope converter does not require a DAC. It uses a linear ramp generator to produce a constant-slope reference voltage. A diagram is shown in Figure 14-35.

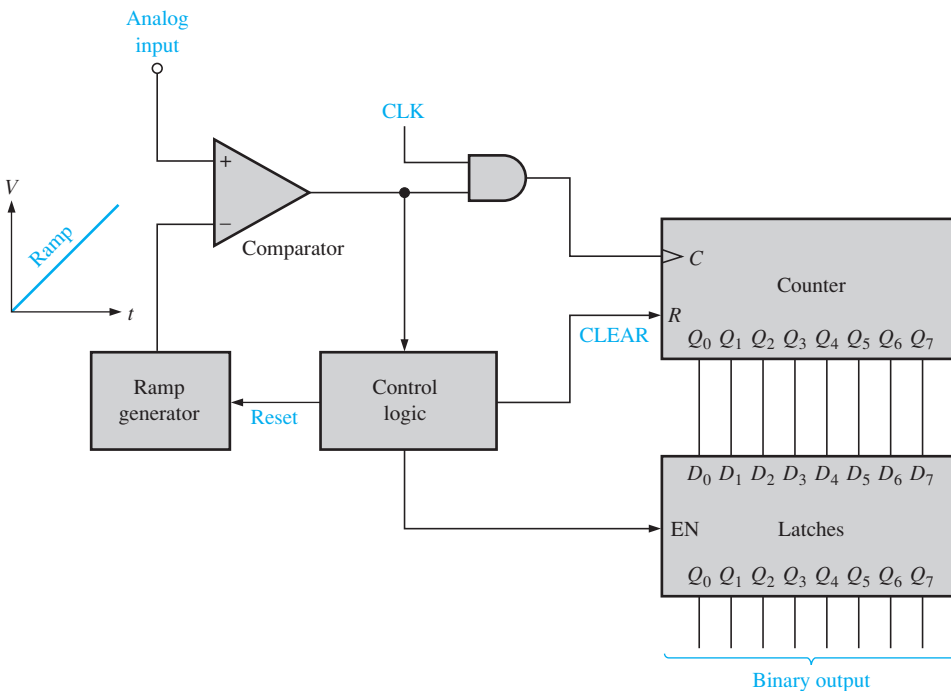


FIGURE 14-35 Single-slope ADC.

At the beginning of a conversion cycle, the counter is in the reset state and the ramp generator output is 0 V. The analog input is greater than the reference voltage at this point and therefore produces a high-level output from the comparator. This high level enables the clock to the counter and starts the ramp generator.

Assume that the slope of the ramp is 1 V/ms. The ramp will increase until it equals the analog input; at this point the ramp is reset, and the binary count is stored in the latches by the control logic. Let's assume that the analog input is 2 V at the point of comparison. This means that the ramp is also 2 V and has been running for 2 ms. Since the comparator output has been at its high level for 2 ms, 200 clock pulses have been allowed to pass through the gate to the counter (assuming a clock frequency of 100 kHz). At the point of comparison, the counter is in the binary state that represents decimal 200. With proper scaling and decoding, this number can be displayed as 2.00 V. This basic concept is used in some digital voltmeters.

Dual-Slope Analog-to-Digital Converter

The operation of the dual-slope ADC is similar to that of the single-slope type except that a variable-slope ramp and a fixed-slope ramp are both used. This type of converter is common in digital voltmeters.

A ramp generator (integrator), A1, is used to produce the dual-slope characteristic. A block diagram of a dual-slope ADC is shown in Figure 14–36 for reference.

 


FIGURE 14–36 Dual-slope ADC.

Figure 14–37 illustrates dual-slope conversion. Let's assume that the counter is reset and the output of the integrator is zero. Now assume that a positive input voltage is applied to the input through the switch (SW) as selected by the control logic. Since the inverting (–) input of A1 is at virtual ground, and assuming that V_{in} is constant for a period of time, there will be constant current through the input resistor R and therefore through the capacitor C . Capacitor C will charge linearly because the current is constant and, as a result, there will be a negative-going linear voltage ramp on the output of A1, as illustrated in Figure 14–37(a).

When the counter reaches a specified count, it will be reset, and the control logic will switch the negative reference voltage ($-V_{REF}$) to the input of A1, as shown in Figure 14–37(b). At this point the capacitor is charged to a negative voltage ($-V$) proportional to the input analog voltage.

Now the capacitor discharges linearly because of the constant current from the $-V_{REF}$, as shown in Figure 14–37(c). This linear discharge produces a positive-going ramp on the A1 output, starting at $-V$ and having a constant slope that is independent of the

 


FIGURE 14-37 Dual-slope conversion.

charge voltage. As the capacitor discharges, the counter advances from its reset state. The time it takes the capacitor to discharge to zero depends on the initial voltage $-V$ (proportional to V_{in}) because the discharge rate (slope) is constant. When the integrator (A1) output voltage reaches zero, the comparator (A2) switches to its low state and disables the clock to the counter. The binary count is latched, thus completing one conversion cycle. The binary count is proportional to V_{in} because the time it takes the capacitor to discharge depends only on $-V$, and the counter records this interval of time.

Successive-Approximation Analog-to-Digital Converter

Perhaps the most widely used method of A/D conversion is **successive approximation**. It has a much faster conversion time than the other methods with the exception of the flash method. It also has a fixed conversion time that is the same for any value of the analog input.

Figure 14–38 shows a basic block diagram of a 4-bit successive-approximation ADC. It consists of a DAC, a successive-approximation register (SAR), and a comparator. The basic operation is as follows. The bits of the DAC are enabled one at a time, starting with the most significant bit (MSB). As each bit is enabled, the comparator produces an output that indicates whether the analog input voltage is greater or less than the output of the DAC. If the DAC output is greater than the analog input, the comparator's output is low, causing the bit in the register to reset. If the DAC output is less than the analog input, the bit is retained in the register. The system does this with the MSB first, then the next most significant bit, then the next, and so on. After all the bits of the DAC have been tried, the conversion cycle is complete.

In order to better understand the operation of the successive-approximation ADC, let's take a specific example of a 4-bit conversion. Figure 14–39 illustrates the step-by-step conversion of a given analog input voltage (5 V in this

case). Let's assume that the DAC has the following output characteristic: $V_{OUT} = 8\text{ V}$ for the 2^3 bit (MSB), $V_{OUT} = 4\text{ V}$ for the 2^2 bit, $V_{OUT} = 2\text{ V}$ for the 2^1 bit, and $V_{OUT} = 1\text{ V}$ for the 2^0 bit (LSB).

Figure 14–39(a) shows the first step in the conversion cycle with the MSB = 1. The output of the DAC is 8 V. Since this is greater than the analog input of 5 V, the output of the comparator is low, causing the MSB in the SAR to be reset to a 0.

Figure 14–39(b) shows the second step in the conversion cycle with the 2^2 bit equal to a 1. The output of the DAC is 4 V. Since this is less than the analog input of 5 V, the output of the comparator switches to its high level, causing this bit to be retained in the SAR.

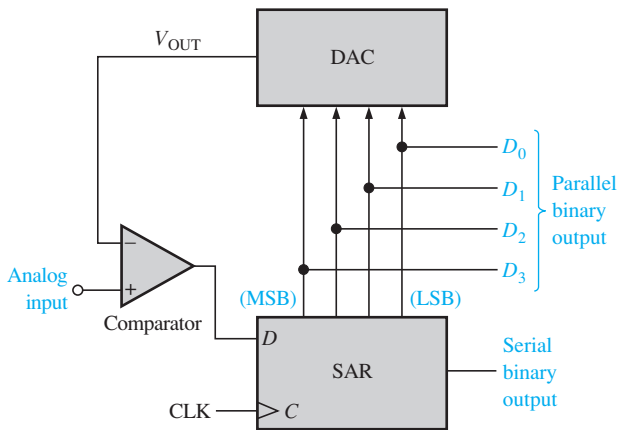


FIGURE 14–38 Successive-approximation ADC.

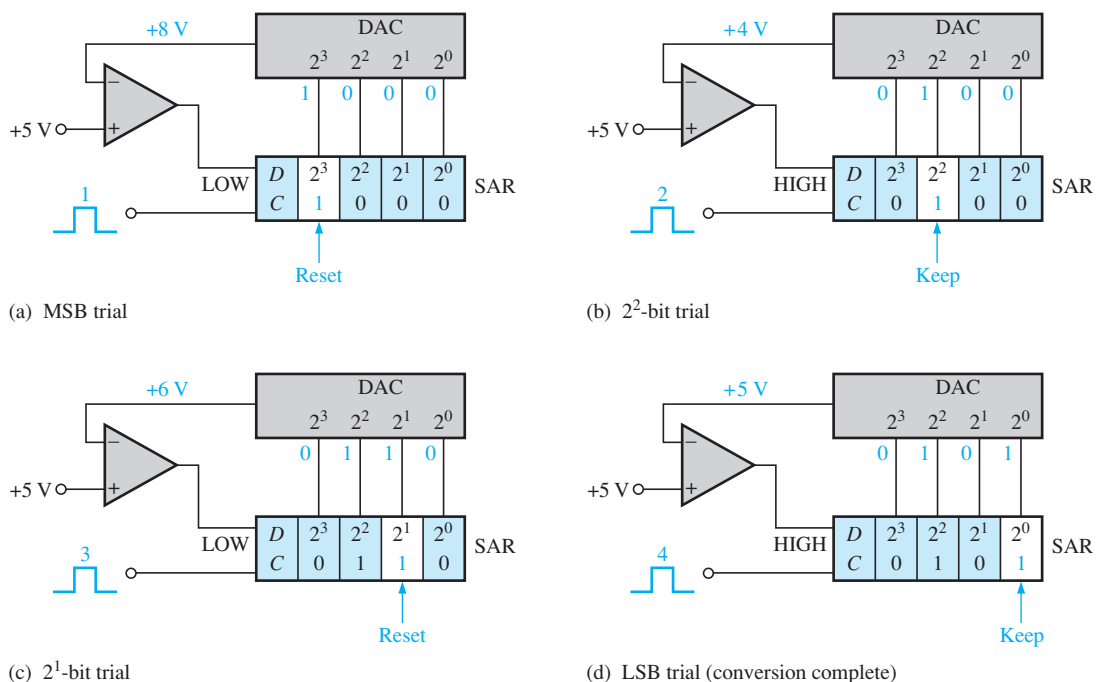


FIGURE 14–39 Successive-approximation conversion process.

Figure 14-39(c) shows the third step in the conversion cycle with the 2^1 bit equal to a 1. The output of the DAC is 6 V because there is a 1 on the 2^2 bit input and on the 2^1 bit input; $4\text{ V} + 2\text{ V} = 6\text{ V}$. Since this is greater than the analog input of 5 V, the output of the comparator switches to its low level, causing this bit to be reset to a 0.

Figure 14-39(d) shows the fourth and final step in the conversion cycle with the 2^0 bit equal to a 1. The output of the DAC is 5 V because there is a 1 on the 2^2 bit input and on the 2^0 bit input; $4\text{ V} + 1\text{ V} = 5\text{ V}$.

The four bits have all been tried, thus completing the conversion cycle. At this point the binary code in the register is 0101, which is the binary value of the analog input of 5 V. Another conversion cycle now begins, and the basic process is repeated. The SAR is cleared at the beginning of each cycle.

A Specific Analog-to-Digital Converter

The ADC0804 is an example of a successive-approximation ADC. The data sheet for this device can be found at www.national.com. A block diagram is shown in Figure 14-40. This device operates from a +5 V supply and has a resolution of eight bits with a conversion time of $100\ \mu\text{s}$. Also, it has guaranteed monotonicity and an on-chip clock generator. The data outputs are tristate so that they can be interfaced with a microprocessor bus system.

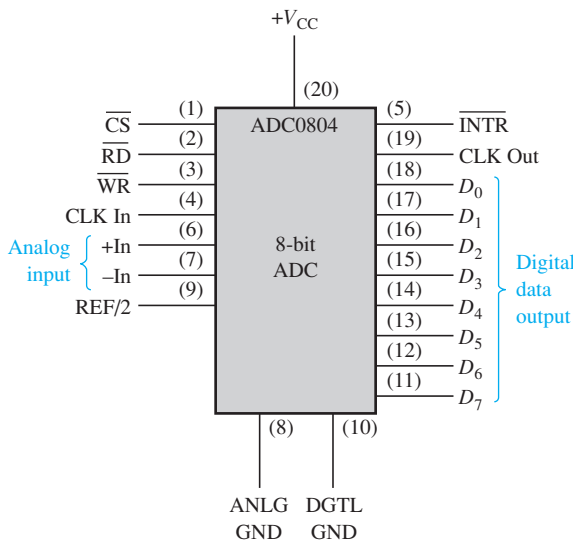


FIGURE 14-40 The ADC0804 analog-to-digital converter.

A detailed logic diagram of the ADC0804 is shown in Figure 14-41, and the basic operation of the device is as follows. The ADC0804 contains the equivalent of a 256-resistor DAC network. The successive-approximation logic sequences the network to match the analog differential input voltage ($+V_{\text{IN}} - (-V_{\text{IN}})$) with an output from the resistive network. The MSB is tested first. After eight comparisons (sixty-four clock periods), an 8-bit binary code is transferred to an output latch, and the interrupt ($\overline{\text{INTR}}$) output goes low. The device can be operated in a free-running mode by connecting the $\overline{\text{INTR}}$ output to the write ($\overline{\text{WR}}$) input and holding the conversion start ($\overline{\text{CS}}$) low. To ensure start-up under all conditions, a low $\overline{\text{WR}}$ input is required during the power-up cycle. Taking $\overline{\text{CS}}$ low anytime after that will interrupt the conversion process.

When the $\overline{\text{WR}}$ input goes low, the internal successive-approximation register (SAR) and the 8-bit shift register are reset. As long as both $\overline{\text{CS}}$ and $\overline{\text{WR}}$ remain low, the analog-to-digital converter remains in a reset state. Conversion starts one to eight clock periods after $\overline{\text{CS}}$ or $\overline{\text{WR}}$ makes a low-to-high transition.

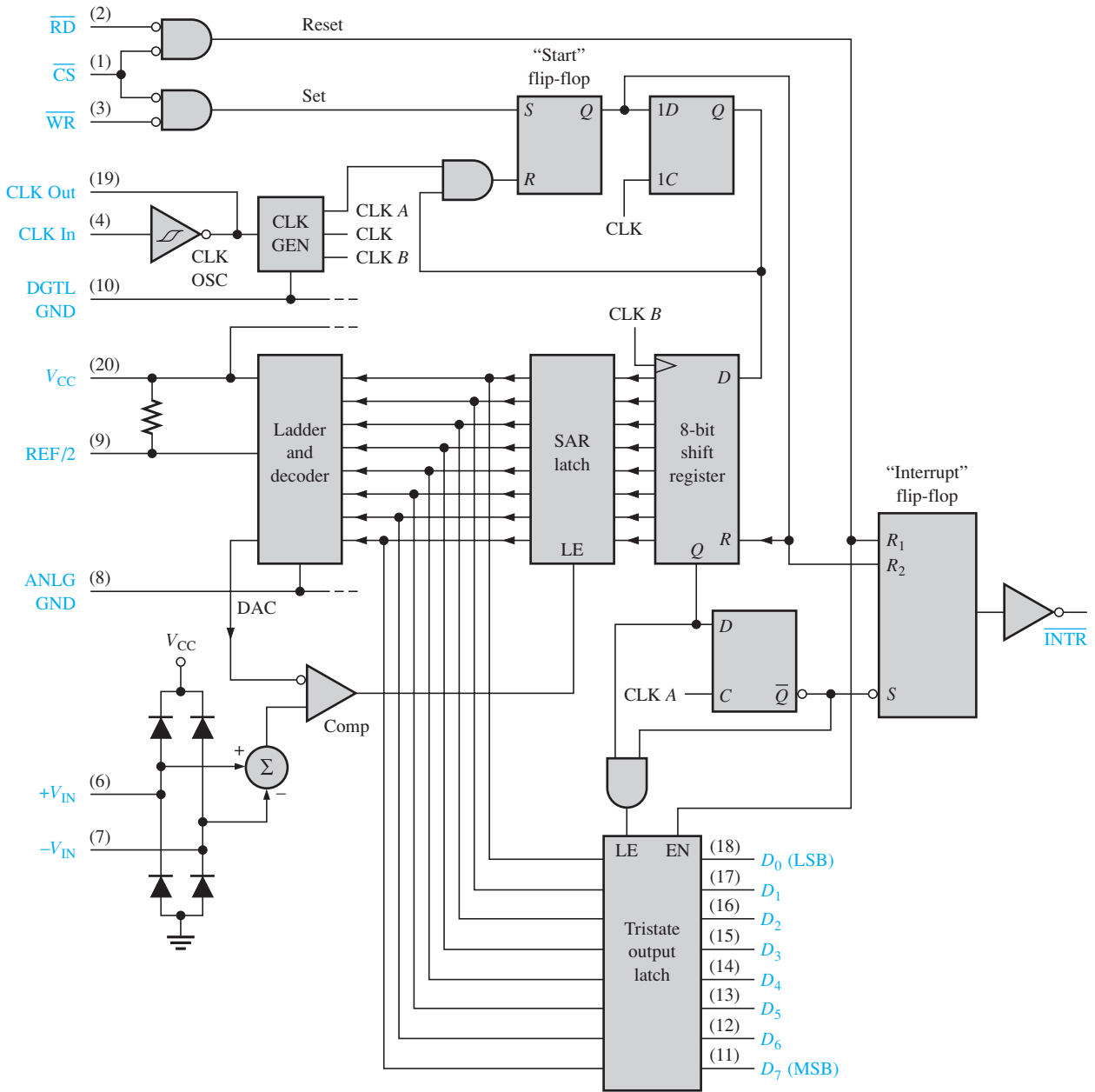


FIGURE 14-41 Logic diagram of the ADC0804 ADC.

When the \overline{CS} and \overline{WR} inputs are low, the start flip-flop is set, and the interrupt flip-flop and 8-bit register are reset. The high is ANDed with the next clock pulse, which puts a high on the reset input of the start flip-flop. If either \overline{CS} or \overline{WR} has gone high, the set signal to the start flip-flop is removed, causing it to be reset. A high is placed on the **D** input of the 8-bit shift register, and the conversion process is started. If the \overline{CS} and \overline{WR} inputs are still low, the start flip-flop, the 8-bit shift register, and the SAR remain reset. This action allows for wide \overline{CS} and \overline{WR} inputs, with conversion starting from one to eight clock periods after one of the inputs has gone high.

When the high input has been clocked through the 8-bit shift register, completing the SAR search, it is applied to an AND gate controlling the output latches and to the **D** input of a flip-flop. On the next clock pulse, the digital word is transferred to the tristate output latches, and the interrupt flip-flop is set. The output of the interrupt flip-flop is inverted to provide an \overline{INTR} output that is high during conversion and low when conversion is complete.

When a low is at both the \overline{CS} and \overline{RD} inputs, the tristate output latch is enabled, the output code is applied to the D_0 through D_7 lines, and the interrupt flip-flop is reset. When either the \overline{CS} or the \overline{RD} input returns to a high, the D_0 through D_7 outputs are disabled. The interrupt flip-flop remains reset.

A few additional IC analog-to-digital converters are listed in Table 14-1.

TABLE 14-1 • Several popular ADCs.

DEVICE	DESCRIPTION	RESOLUTION	CONVERSION TIME	SUPPLY VOLTAGES
AD673 ¹	Successive Approximation	8 bits	20 μ s	+5 V, -12 V
AD9220 ¹	Successive Approximation	12 bits	100 ns	+5 V
ADC0802N ²	Successive Approximation	8 bits	100 μ s	+5 V
ADC0803N ²	Successive Approximation	8 bits	100 μ s	+5 V
HI7191 ³	Sigma Delta	24 bits	—	\pm 5 V
TLC5510 ⁴	Flash Conversion	8 bits	25 ns	+5 V
ADS1216 ⁴	Sigma Delta	24 bits	—	2.7 V to 5.25 V

¹Data sheet available at www.analog.com

²Data sheet available at www.national.com

³Data sheet available at www.intersil.com

⁴Data sheet available at www.ti.com

SECTION 14-6 CHECKUP

1. What is the fastest method of analog-to-digital conversion?
2. Which A/D conversion method uses an up/down counter?
3. The successive-approximation converter has a fixed conversion time. (True or false)

14-7 VOLTAGE-TO-FREQUENCY (V/F) AND FREQUENCY-TO-VOLTAGE (F/V) CONVERTERS

Voltage-to-frequency converters convert an analog input voltage to a pulse stream or square wave in such a way that there is a linear relationship between the analog voltage and the frequency of the pulse stream. Frequency-to-voltage converters perform the inverse operation by converting a pulse stream to a voltage that is proportional to the pulse stream frequency. Actually, V/F and F/V converters can be used as ADCs and DACs in certain applications. In other applications, V/F and F/V converters are used, for example, in high-noise immunity digital transmission and in digital voltmeters.

After completing this section, you should be able to

- Discuss the basic operation of V/F and F/V converters
 - Describe the AD650 V/F converter
 - Discuss V/F and F/V applications

A Basic Voltage-to-Frequency Converter

The concept of voltage-to-frequency converters is shown in Figure 14–42. An analog voltage on the input is converted to a pulse signal with a frequency that is directly proportional to the amplitude of the input voltage. There are several ways to implement a V/F converter. For example, the VCO (voltage-controlled oscillator) with which you are already familiar can be used as one type of V/F converter. In this section, we will look at a relatively common implementation called the *charge-balance V/F converter*.

 


FIGURE 14–42 The basic V/F concept.

Figure 14–43 shows the diagram of a basic charge-balance V/F converter. It consists of an integrator, a comparator, a one-shot, a current source, and an electronic switch. The input resistor R_{in} , the integration capacitor C_{int} , and the one-shot timing capacitor C_{os} are components whose values are selected based on desired performance.



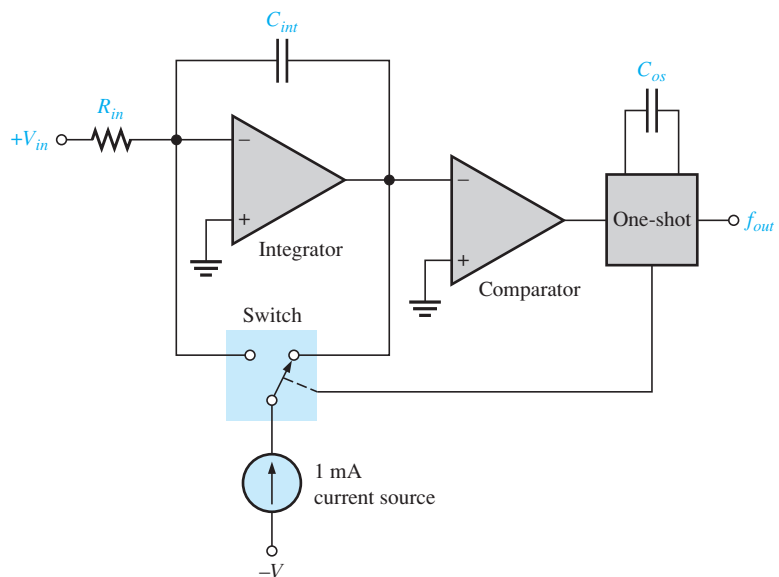


FIGURE 14–43 A basic voltage-to-frequency converter.

The basic operation of the V/F converter in Figure 14–46 is as follows. A positive input voltage produces an input current ($I_{in} = V_{in}/R_{in}$) that charges the capacitor C_{int} , as indicated in Figure 14–44(a). During this integrate mode, the integrator output voltage is a downward ramp, as shown. When the integrator output voltage reaches zero, the comparator triggers the one-shot. The one-shot produces a pulse with a fixed width, t_{os} , that switches the 1 mA current source to the input of the integrator and initiates the reset mode.

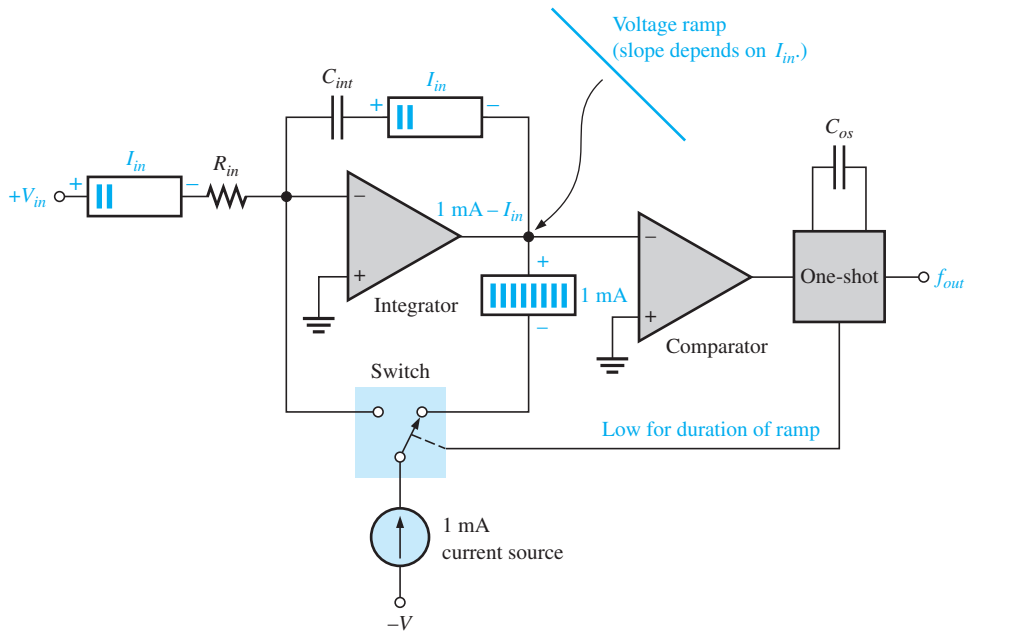

(a) V/F converter in the integrate mode

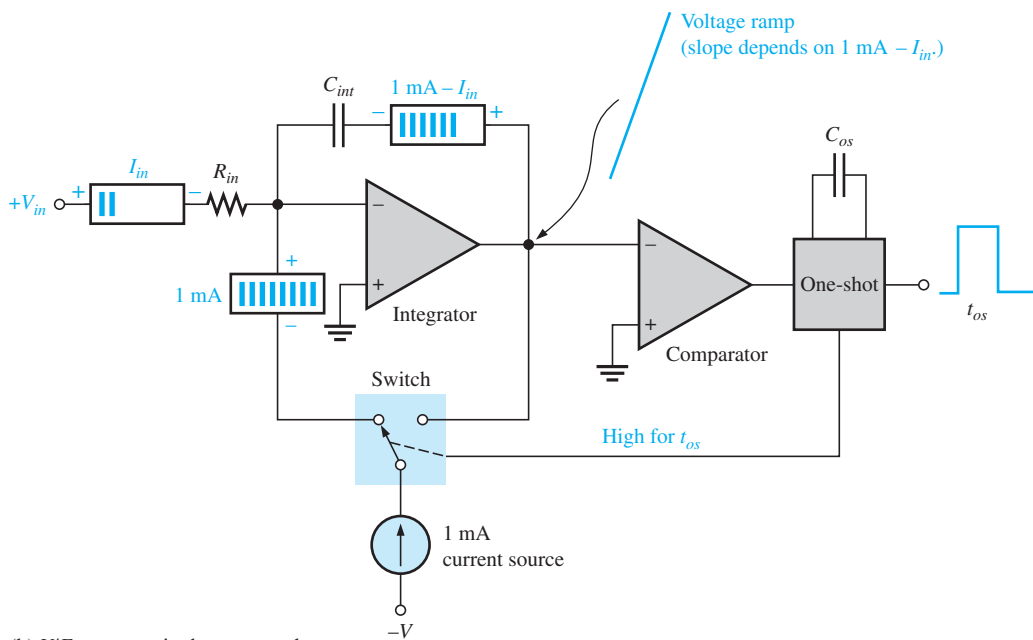


(b) V/F converter in the reset mode

FIGURE 14-44 Basic operation of a V/F converter for a constant input voltage.

During the reset mode, current through the capacitor is in the opposite direction from the integrate mode, as indicated in Figure 14-44(b). This produces an upward ramp on the integrator output as indicated. After the one-shot times out, the current source is switched back to the integrator output, initiating another integrate mode, and the cycle repeats.


If the input voltage is held constant, the output waveform of the integrator is as shown in Figure 14-45(a), where the amplitude and the integrate time remain constant. The final output of the V/F converter is taken off the one-shot, as indicated in Figure 14-44. As long as the input voltage is constant, the output pulse stream has a constant frequency as indicated in Figure 14-45(b).

FIGURE 14-45 V/F converter waveforms for a constant input voltage.

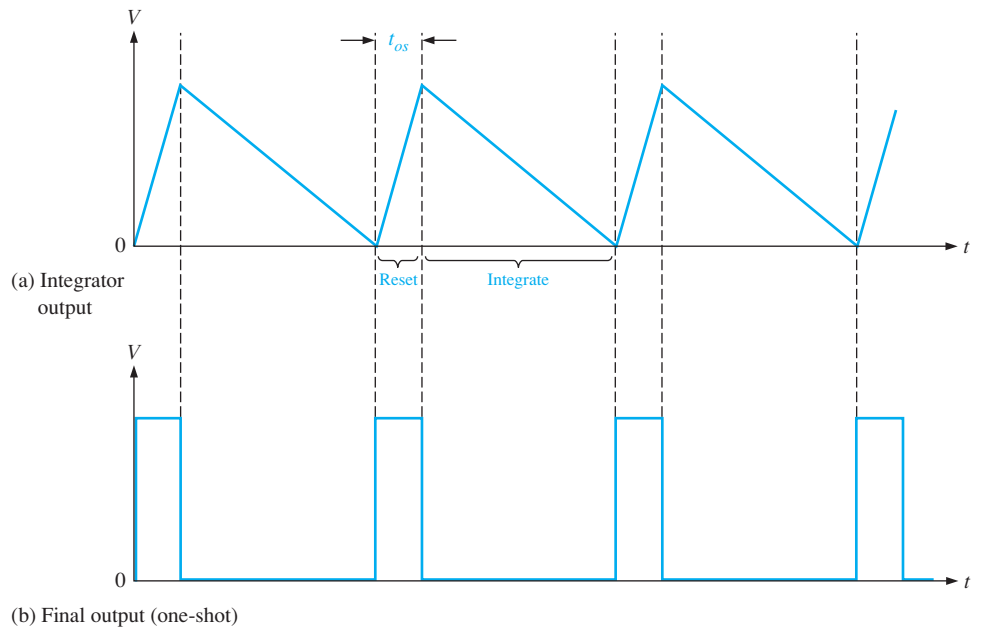

WHEN THE INPUT VOLTAGE INCREASES An increase in the input voltage, V_{in} , causes the input current, I_{in} , to increase. In the basic relationship $I_C = (V_C/t)C$, the term V_C/t is the slope of the capacitor voltage. If the current increases, V_C/t also increases since C is constant. As applied to the V/F converter, this means that if the input current (I_{in}) increases, then the slope of the integrator output during the integrate mode will also increase and reduce the period of the final output voltage. Also, during the reset mode, the opposite current through the capacitor, $1 \text{ mA} - I_{in}$, is smaller, thus decreasing the slope of the upward ramp and reducing the amplitude of the integrator output voltage. This is illustrated in the waveform diagram of Figure 14-46 where the input voltage, and thus the

FIGURE 14-46 The output frequency increases when the input voltage increases.

 

input current, takes a step increase from one value to another. Notice that during reset, the positive-going slope of the integrator voltage is less, so it reaches a smaller amplitude during the time t_{os} . Remember, t_{os} does not change. Notice also that during integration, the negative-going slope of the integrator voltage is greater, so it reaches zero quicker. The net result of this increase in input voltage is that the output frequency increases an amount proportional to the increase in the input voltage. So, as the input voltage varies, the output frequency varies proportionally.

The AD650 Integrated Circuit V/F Converter

The AD650 is a good example of a V/F converter very similar to the basic device we just discussed. The data sheet for the AD650 can be found at www.analog.com. The main differences in the AD650 are the output transistor and the comparator threshold voltage of -0.6 V instead of ground, as shown in Figure 14-47. The input resistor, integrating capacitor, one-shot capacitor, and the output pull-up resistor are external components, as indicated.

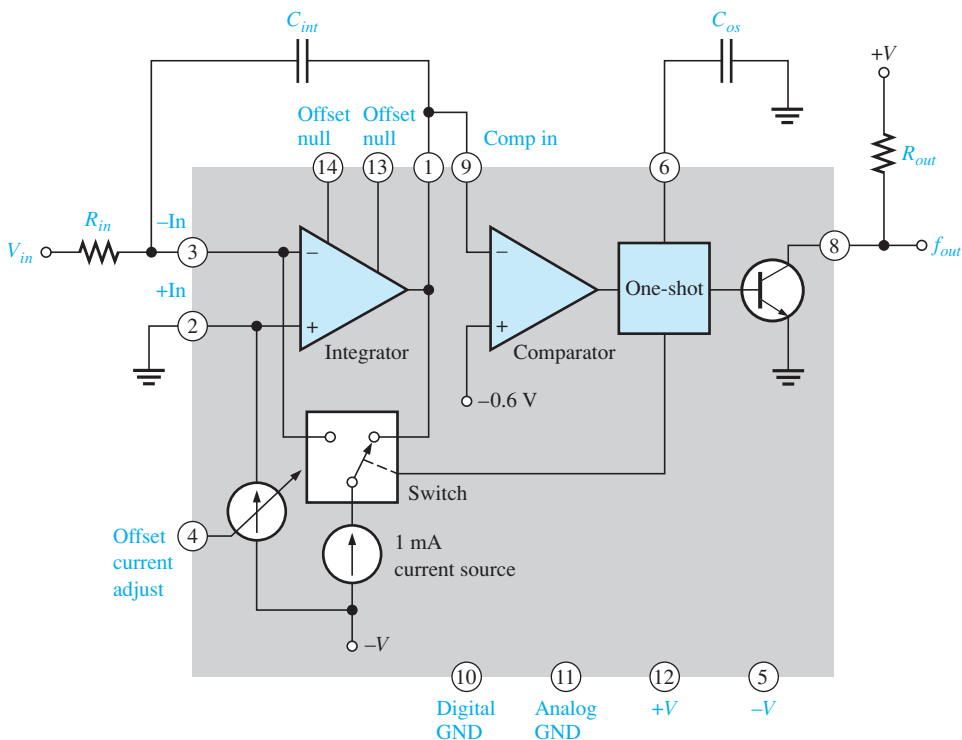


FIGURE 14-47 The AD650 V/F converter.

The values of the external components determine the operating characteristics of the device. The pulse width of the one-shot output is set by the following formula:

$$t_{os} = C_{os}(6.8 \times 10^3 \text{ s/F}) + 3 \times 10^{-7} \text{ s} \quad (14-1)$$

During the reset interval, the integrator output voltage increases by an amount expressed as

$$\Delta V = \frac{(1 \text{ mA} - I_{in})t_{os}}{C_{int}} \quad (14-2)$$

The duration of the integrate interval when the integrator output is sloping downward is

$$t_{int} = \frac{\Delta V}{I_{in}/C_{int}} = \frac{t_{os}(1 \text{ mA} - I_{in})/C_{int}}{I_{in}/C_{int}}$$

$$t_{int} = \left(\frac{1 \text{ mA}}{I_{in}} - 1 \right) t_{os} \tag{14-3}$$

The period of a full cycle consists of the reset interval plus the integrate interval.

$$T = t_{os} + t_{int} = t_{os} + \left(\frac{1 \text{ mA}}{I_{in}} - 1 \right) t_{os} = \left(1 + \frac{1 \text{ mA}}{I_{in}} - 1 \right) t_{os} = \left(\frac{1 \text{ mA}}{I_{in}} \right) t_{os}$$

Therefore, the output frequency can be expressed as

$$f_{out} = \frac{I_{in}}{t_{os}(1 \text{ mA})} \tag{14-4}$$

As you can see in Equation (14-4), the output frequency is directly proportional to the input current; and since $I_{in} = V_{in}/R_{in}$, it is also directly proportional to the input voltage and inversely proportional to the input resistance. The output frequency is also inversely proportional to t_{os} , which depends on the value of C_{os} .

EXAMPLE 14-7

Determine the output frequency for the AD650 V/F converter in Figure 14-48 when a constant input voltage of 5 V is applied.

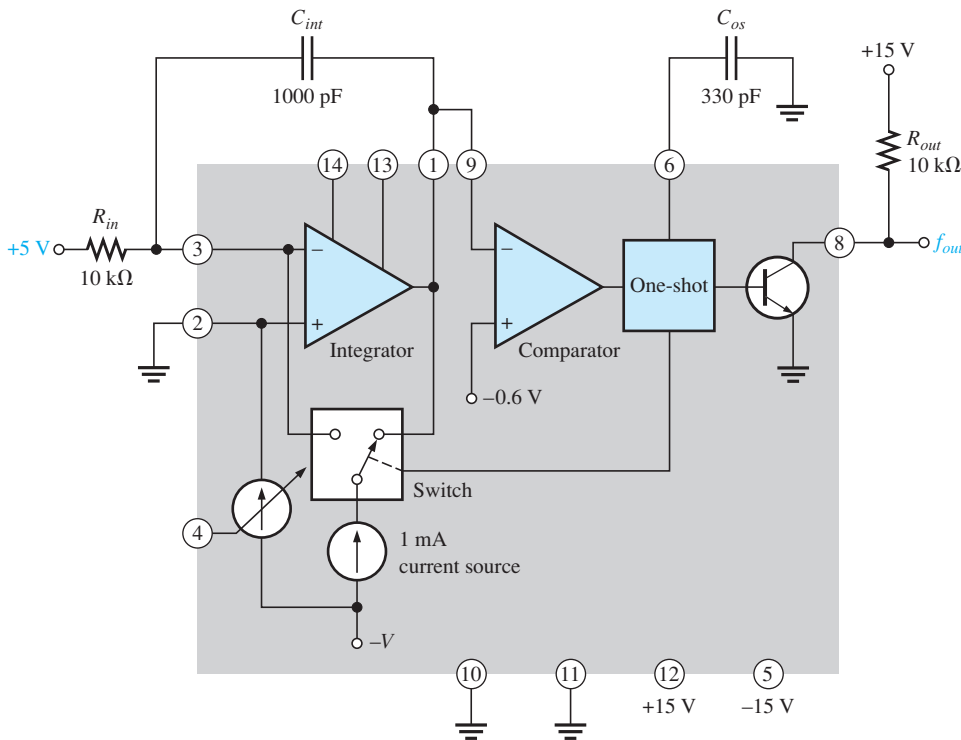


FIGURE 14-48

SOLUTION

$$\begin{aligned}
 t_{os} &= C_{os}(6.8 \times 10^3 \text{ s/F}) + 3 \times 10^{-7} \text{ s} \\
 &= 330 \text{ pF}(6.8 \times 10^3 \text{ s/F}) + 3 \times 10^{-7} \text{ s} = 2.5 \mu\text{s} \\
 I_{in} &= \frac{V_{in}}{R_{in}} = \frac{5 \text{ V}}{10 \text{ k}\Omega} = 500 \mu\text{A} \\
 f_{out} &= \frac{I_{in}}{t_{os}(1 \text{ mA})} = \frac{500 \mu\text{A}}{(2.5 \mu\text{s})(1 \text{ mA})} = \mathbf{200 \text{ kHz}}
 \end{aligned}$$

PRACTICE EXERCISE

What are the minimum and maximum output frequencies for the V/F converter in Figure 14-48 when a triangular wave with a minimum peak value of 1 V and a maximum peak value of 6 V is applied to the input?

A Basic F/V Converter

Figure 14-49 shows a basic frequency-to-voltage converter. The elements are the same as those in the voltage-to-frequency converter of Figure 14-43, but they are connected differently.

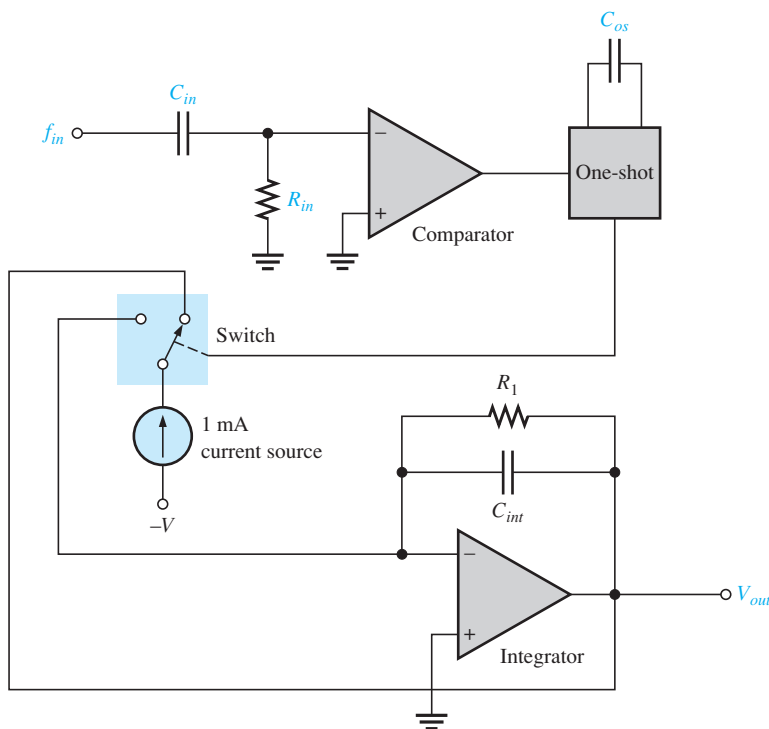


FIGURE 14-49 A basic frequency-to-voltage (F/V) converter.

When an input frequency is applied to the comparator input, it triggers the one-shot, which produces a fixed pulse width (t_{os}) determined by C_{os} . This switches the 1 mA current source to the integrator input and C_{int} charges. Between one-shot pulses, C_{int} discharges through R_1 . The higher the input frequency, the closer the one-shot pulses are together and the less C_{int} discharges. This causes the integrator output to increase as input frequency increases and to decrease as the input frequency decreases. The integrator output is the final voltage output of the F/V converter. F/V conversion action is illustrated by the waveforms in Figure 14-50. C_{int} and R_1 act as a filter and tend to smooth out the ripples on the integrator output as indicated by the dashed curve.

Figure 14-51 shows the AD650 connected to function as a frequency-to-voltage converter. Compare this configuration with the voltage-to-frequency connection in Figure 14-47.

FIGURE 14-50 An example of frequency-to-voltage conversion.


 


FIGURE 14-51 The AD650 connected as a frequency-to-voltage (F/V) converter.

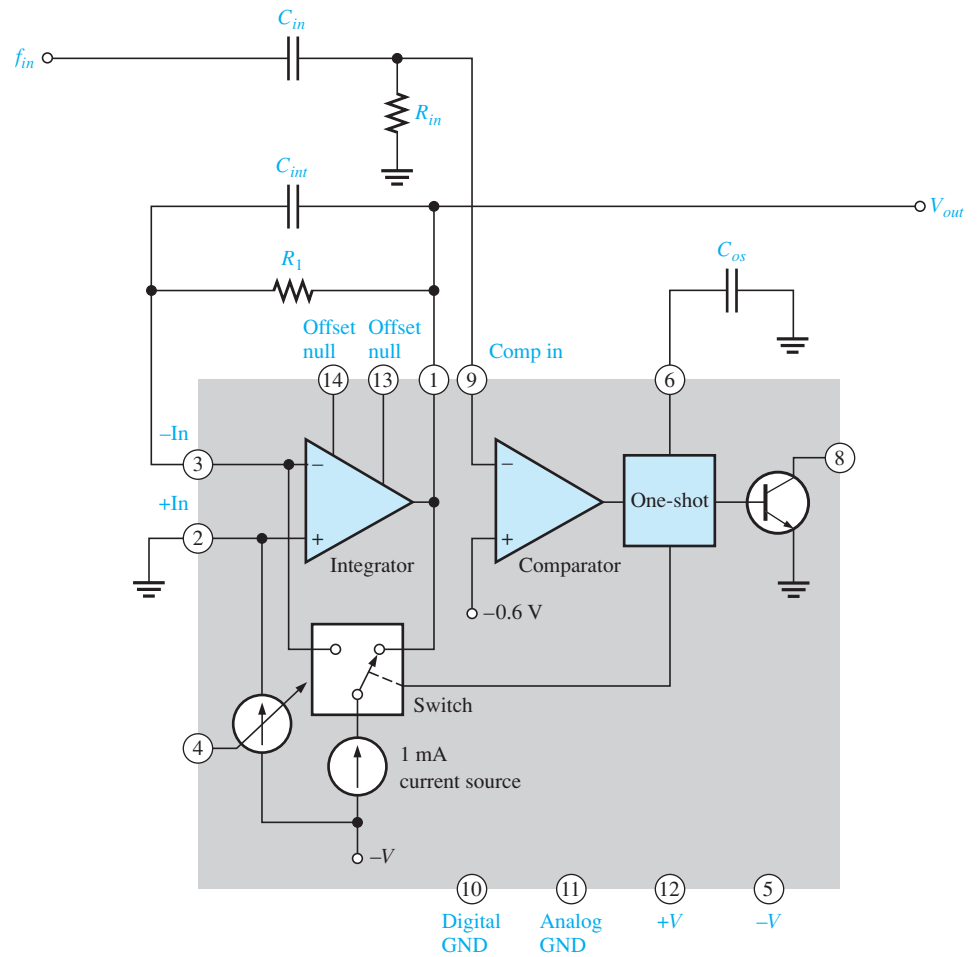


Frequency-to-voltage converters are often used in systems where a rotating device or machine is monitored. One example would be the tachometer in an automobile. A timing gear or flywheel is used to generate pulses based on engine rpm. The number of teeth in the gear determines the pulses per rotation (ppr). The pulses are applied to the input of the F/V converter and a proportional output voltage is produced. This is then digitized by an ADC and processed by the car's on-board computer.

For example, suppose a flywheel with 250 teeth is used as a timing device and engine rpm ranges from 800 rpm at idle to a maximum of 6000 rpm at red line. At idle the flywheel produces $(800 \text{ rpm} \div 60 \text{ s/m}) \times (250 \text{ ppr}) = 3333$ pulses per second (3.33 kHz). The output frequency is 25 kHz at red line.

This is just one simple example, but F/V converters can be used in any system where the speed of a rotating device must be monitored. In some applications variations in rotational speed can result in serious problems. Suppose the speed of a dc motor is being monitored. If the rotational speed of the motor should vary outside some predetermined window, the applied voltage to the motor could be changed to compensate for the change in motor speed. This is especially important in dc motors since the speed of a dc motor is inversely proportional to load. If the load should be totally removed (a belt or drive chain should break), then the motor would speed out of control and eventually destroy itself.

SYSTEM NOTE

 

A Remote Sensing Application

One application of V/F and F/V converters is in the remote sensing of a quantity (temperature, pressure, level) that is converted to an analog voltage by a transducer. The analog voltage is then converted to a pulse frequency by a V/F converter, which is then transmitted by some method (radio link, fiber-optical link, telemetry) to a base unit receiver that includes an F/V converter. This basic application of V/F and F/V conversion is illustrated in Figure 14-52.

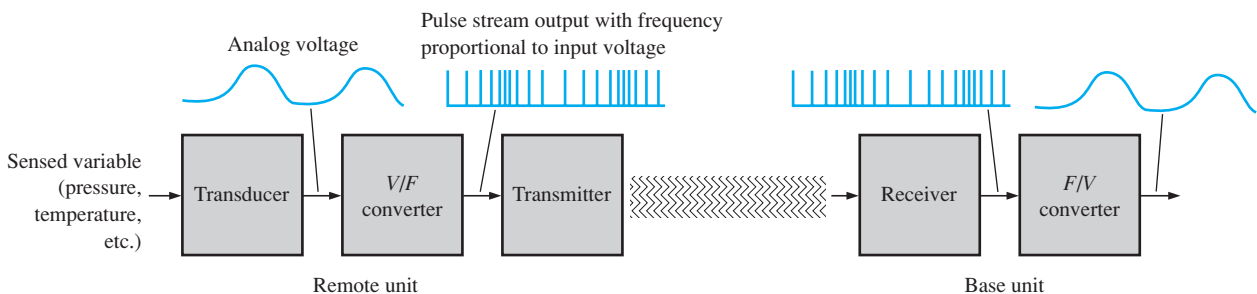


FIGURE 14-52 Basic application of V/F and F/V conversion.

SECTION 14-7 CHECKUP

- List the basic components in a typical V/F converter.
- In a V/F converter, if the input voltage changes from 1 V to 6.5 V, what happens to the output?
- Describe the basic differences between a V/F and a F/V converter in terms of inputs and outputs.
- Assume a flywheel with 150 teeth is rotating at 2000 rpm. What is the output frequency of the pulses?

14–8 TROUBLESHOOTING

Basic testing of DACs and ADCs includes checking their performance characteristics, such as monotonicity, offset, linearity, and gain, and checking for missing or incorrect codes. In this section, the fundamentals of testing these analog interfaces are introduced.

After completing this section, you should be able to

- Troubleshoot DACs and ADCs
- Identify D/A conversion errors
- Identify A/D conversion errors

Testing Digital-to-Analog Converters

The concept of DAC testing is illustrated in Figure 14–53. In this basic method, a sequence of binary codes is applied to the inputs, and the resulting output is observed. The binary code sequence extends over the full range of values from 0 to $2^n - 1$ in ascending order, where n is the number of bits.

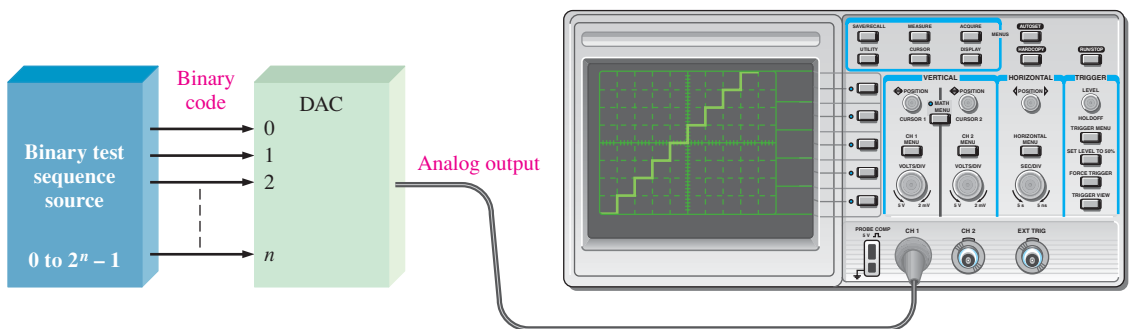


FIGURE 14–53 Basic test setup for a DAC.


The ideal output is a straight-line staircase as indicated. As the number of bits in the binary code is increased, the resolution is improved. That is, the number of discrete steps increases, and the output approaches a straight-line linear ramp.

D/A Conversion Errors


Several D/A conversion errors to be checked for are shown in Figure 14–54, which uses a 4-bit conversion for illustration purposes. A 4-bit conversion produces fifteen discrete steps. Each graph in the figure includes an ideal staircase ramp for comparison with the faulty outputs.

NONMONOTONICITY The step reversals in Figure 14–54(a) indicate **nonmonotonic** performance, which is a form of nonlinearity. In this particular case, the error occurs because the 2^1 bit in the binary code is interpreted as a constant 0. That is, a short is causing the bit input line to be stuck in the low state.

 
DIFFERENTIAL NONLINEARITY Figure 14–54(b) illustrates differential nonlinearity in which the step amplitude is less than it should be for certain input codes. This particular output could be caused by the 2^2 bit having an insufficient weight, perhaps




(a) Nonmonotonic output (green)

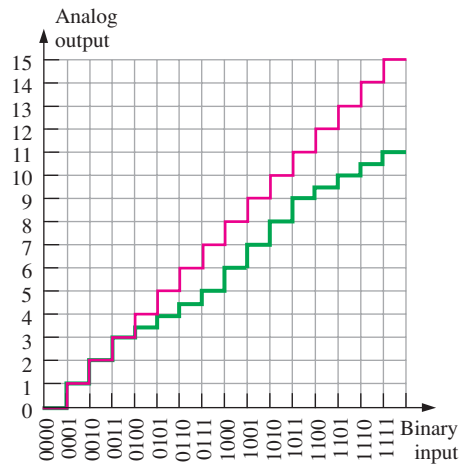

(b) Differential nonlinearity (green)

 

(c) High and low gains (green)

 

(d) Offset error (green)

FIGURE 14-54 Illustrations of several D/A conversion errors.

because of a faulty input resistor. We could also see steps with amplitudes greater than normal if a particular binary weight were greater than it should be.

LOW OR HIGH GAIN Output errors caused by low or high gain are illustrated in Figure 14-54(c). In the case of low gain, all of the step amplitudes are less than ideal. In the case of high gain, all of the step amplitudes are greater than ideal. This situation may be caused by a faulty feedback resistor in the op-amp circuit.

OFFSET ERROR An offset error is illustrated in Figure 14-54(d). Notice that when the binary input is 0000, the output voltage is nonzero and that this amount of offset is the same for all steps in the conversion. A faulty op-amp may be the culprit in this situation.

EXAMPLE 14-8

The DAC output in Figure 14-55 is observed when a straight 4-bit binary sequence is applied to the inputs. Identify the type of error, and suggest an approach to isolate the fault.

 


FIGURE 14-55

SOLUTION

The DAC in this case is nonmonotonic. Analysis of the output reveals that the device is converting the following sequence, rather than the actual binary sequence applied to the inputs.

0010, 0011, 0010, 0011, 0110, 0111, 0110, 0111, 1010, 1011, 1010,
1011, 1110, 1111, 1110, 1111

Apparently, the 2^1 bit (second from right) is stuck in the high (1) state. To find the problem, first monitor the bit input pin of the device. If it is changing states, the fault is internal, most likely an open. If the external pin is not changing states and is always high, check for an external short to +V that may be caused by a solder bridge somewhere on the circuit board. If no problem is found here, disconnect the source output from the DAC input pin, and see if the output signal is correct. If these checks produce no results, the fault is most likely internal to the DAC, perhaps a short to the supply voltage.

PRACTICE EXERCISE

Graph the output of a DAC if a straight 4-bit binary sequence is applied to the inputs and the most significant bit input of the DAC is stuck high.

Testing Analog-to-Digital Converters

One method for testing ADCs is shown in Figure 14-56. A DAC is used as part of the test setup to convert the ADC output back to analog form for comparison with the test input.

A test input in the form of a linear ramp is applied to the input of the ADC. The resulting binary output sequence is then applied to the DAC test unit and converted to a staircase ramp. The input and output ramps are compared for any deviation.

A/D Conversion Errors

Again, a 4-bit conversion is used to illustrate the principles. Let's assume that the test input is an ideal linear ramp.

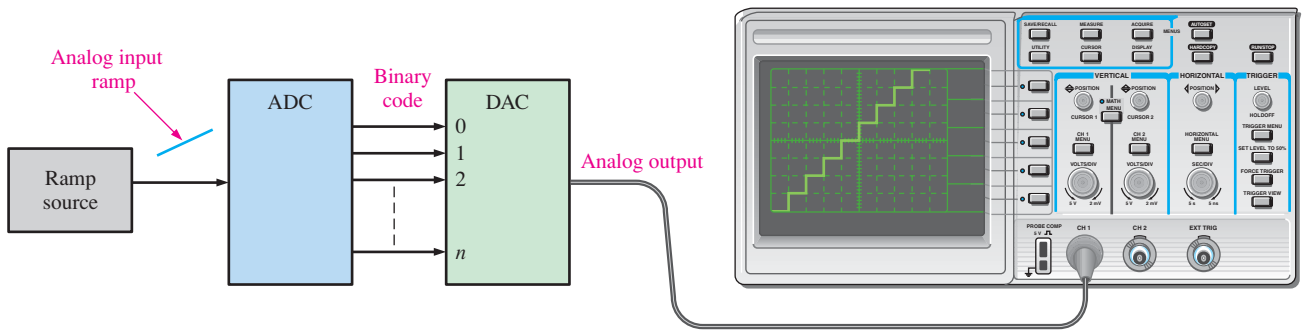


FIGURE 14-56 A method for testing ADCs.

MISSING CODE The staircase output in Figure 14-57(a) indicates that the binary code 1001 does not appear on the output of the ADC. Notice that the 1000 value stays for two intervals and then the output jumps to the 1010 value.

In a flash ADC, for example, a failure of one of the comparators can cause a missing-code error.

 


FIGURE 14-57 Illustrations of A/D conversion errors.

INCORRECT CODES The staircase output in Figure 14-57(b) indicates that several of the binary code words coming out of the ADC are incorrect. Analysis indicates that the 2^1 -bit line is stuck in the low state in this particular case.

OFFSET Offset conditions are shown in 14-57(c). In this situation, the ADC interprets the analog input voltage as greater than its actual value. This error is probably due to a faulty comparator circuit.

EXAMPLE 14-9

A 4-bit flash ADC is shown in Figure 14-58(a). It is tested with a setup like the one in Figure 14-56. The resulting reconstructed analog output is shown in Figure 14-58(b). Identify the problem and the most probable fault.

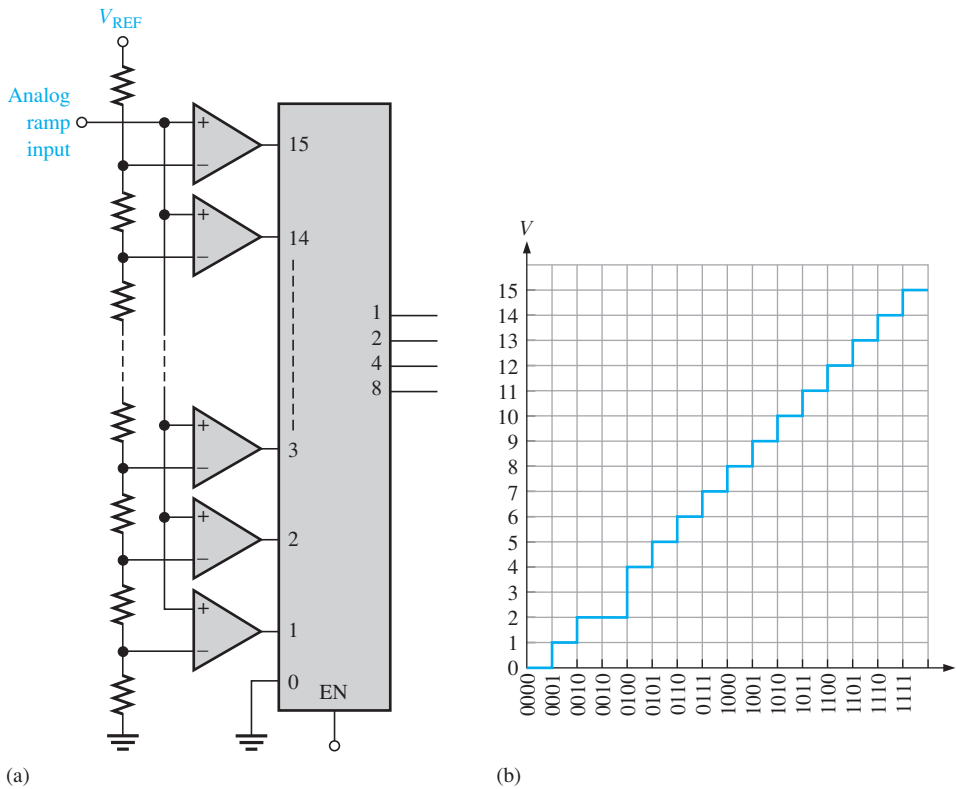


FIGURE 14-58

SOLUTION

The binary code 0011 is missing from the ADC output, as indicated by the missing step. Most likely, the output of comparator 3 is stuck in its inactive state (low).

PRACTICE EXERCISE

If the output of comparator 15 is stuck in the high state, what will be the reconstructed analog output when the ADC is tested in a setup like the one in Figure 14-56?

SECTION 14-8 CHECKUP

1. How do you detect nonmonotonic behavior in a DAC?
2. What effect does low gain have on a DAC output?
3. Name two types of output errors in an ADC.

SUMMARY

- There are three basic types of analog switches: single pole–single throw (SPST), single pole–double throw (SPDT), and double pole–single throw (DPST).
- An analog switch is typically a MOSFET that is opened or closed with a control input.
- A sample-and-hold amplifier samples a voltage at a certain point in time and retains or holds that voltage for an interval of time.
- An analog quantity is one that has a continuous set of values over time.

- A digital quantity is one that has a set of discrete values over time.
- Two basic types of digital-to-analog converters (DACs) are the binary-weighted-input converter and the $R/2R$ ladder converter.
- The $R/2R$ ladder DAC is easier to implement because only two resistor values are required compared to a different value for each input in the binary-weighted-input DAC.
- The number of bits in an analog-to-digital converter (ADC) determines its resolution.
- The minimum sampling rate for A/D conversion is twice the maximum frequency component of the analog signal.
- The flash or simultaneous method of A/D conversion is the fastest.
- The successive-approximation method of A/D conversion is the most widely used.
- Other common methods of A/D conversion are single-slope, dual-slope, tracking, and staircase ramp (counter method).
- In a voltage-to-frequency converter (V/F), the output frequency is directly proportional to the amplitude of the analog input voltage.
- In a frequency-to-voltage converter (F/V), the amplitude of the output voltage is directly proportional to the input frequency.
- Types of D/A conversion errors include nonmonotonicity, differential nonlinearity, low or high gain, and offset error.
- Types of A/D conversion errors include missing code, incorrect code, and offset.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Acquisition time In an analog switch, the time required for the device to reach its final value when switched from hold to sample.

Analog switch A type of semiconductor switch that connects an analog signal from input to output with a control input.

Analog-to-digital converter (ADC) A device used to convert an analog signal to a sequence of digital codes.

Digital-to-analog converter (DAC) A device in which information in digital form is converted to an analog form.

Flash A method of A/D conversion.

Quantization The determination of a value for an analog quantity.

Resolution In relation to DACs or ADCs, the number of bits involved in the conversion. Also, for DACs, the reciprocal of the maximum number of discrete steps in the output.

Sample-and-hold The process of taking the instantaneous value of a quantity at a specific point in time and storing it on a capacitor.

Successive approximation A method of A/D conversion.

KEY FORMULAS

V/F CONVERTERS

$$(14-1) \quad t_{os} = C_{os}(6.8 \times 10^3 \text{ s/F}) + 3 \times 10^{-7} \text{ s} \quad \text{One-shot time}$$

$$(14-2) \quad \Delta V = \frac{(1 \text{ mA} - I_{in})t_{os}}{C_{int}} \quad \text{Integrator output increase in reset interval}$$

$$(14-3) \quad t_{int} = \left(\frac{1 \text{ mA}}{I_{in}} - 1 \right) t_{os} \quad \text{Integrate interval}$$

$$(14-4) \quad f_{out} = \frac{I_{in}}{t_{os}(1 \text{ mA})} \quad \text{Output frequency}$$

SELF-TEST

Answers are at the end of the chapter.

1. An analog switch
 - (a) changes an analog signal to digital
 - (b) connects or disconnects an analog signal to the output
 - (c) stores the value of an analog voltage at a certain point
 - (d) combines two or more analog signals onto a single line
2. An analog multiplexer
 - (a) produces the sum of several analog voltages on an output line
 - (b) connects two or more analog signals to an output at the same time
 - (c) connects two or more analog signals to an output one at a time in sequence
 - (d) distributes two or more analog signals to different outputs in sequence
3. A basic sample-and-hold circuit contains an
 - (a) analog switch and an amplifier
 - (b) analog switch, a capacitor, and an amplifier
 - (c) analog multiplexer and a capacitor
 - (d) analog switch, a capacitor, and input and output buffer amplifiers
4. In a sample/track-and-hold amplifier,
 - (a) the voltage at the end of the sample interval is held
 - (b) the voltage at the beginning of the sample interval is held
 - (c) the average voltage during the sample interval is held
 - (d) the output follows the input during the sample interval
 - (e) answers (a) and (d)
5. In an analog switch, the aperture time is the time it takes for the switch to
 - (a) fully open after the control switches from hold to sample
 - (b) fully close after the control switches from sample to hold
 - (c) fully open after the control switches from sample to hold
 - (d) fully close after the control switches from hold to sample
6. In a binary-weighted-input digital-to-analog converter (DAC),
 - (a) all of the input resistors are of equal value
 - (b) there are only two input resistor values required
 - (c) the number of different input resistor values equals the number of inputs
7. In a 4-bit binary-weighted-input DAC, if the lowest-valued-input resistor is 1.0 k Ω , the highest-valued input resistor is
 - (a) 2 k Ω
 - (b) 4 k Ω
 - (c) 8 k Ω
 - (d) 16 k Ω
8. The advantage of an $R/2R$ ladder DAC is
 - (a) it is more accurate
 - (b) it uses only two resistor values
 - (c) it uses only one resistor value
 - (d) it can handle more inputs
9. In a DAC, monotonicity means that
 - (a) the accuracy is within one-half of a least significant bit
 - (b) there are no missing steps in the output
 - (c) there is one bit missing from the input
 - (d) there are no linear errors
10. An 8-bit analog-to-digital converter (ADC) can represent
 - (a) 144 discrete values of an analog input
 - (b) 4096 discrete values of an analog input
 - (c) a continuous set of values of an analog input
 - (d) 256 discrete values of an analog input
11. An analog signal must be sampled at a minimum rate greater than
 - (a) twice the maximum frequency
 - (b) twice the minimum frequency
 - (c) the maximum frequency
 - (d) the minimum frequency
12. Quantization error in an ADC is due to
 - (a) poor resolution
 - (b) nonlinearity of the input
 - (c) a missing bit in the output
 - (d) a change in the input voltage during the conversion time

13. Quantization error can be avoided by
 (a) using a higher resolution ADC (b) using a sample-and-hold prior to the ADC
 (c) shortening the conversion time (d) using a flash ADC
14. The type of ADC with the fastest conversion time is the
 (a) dual-slope (b) single-slope
 (c) simultaneous (d) successive-approximation
15. The output of a V/F converter
 (a) has an amplitude proportional to the frequency of the input
 (b) is a digital reproduction of the input voltage
 (c) has a frequency that is inversely proportional to the amplitude of the input
 (d) has a frequency that is directly proportional to the amplitude of the input
16. An element not found in the typical V/F converter is a(n)
 (a) linear amplifier (b) one-shot
 (c) integrator (d) comparator

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 14–63(a).

- If the gate input from pin 12 is stuck high,
 1. The output voltage will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the external capacitor $C_{H(\text{ext})}$ opens,
 2. The sampling rate will
 - (a) increase
 - (b) decrease
 - (c) not change
 3. The device's ability to hold the sampled value will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 14–63(b).

- If the external 10 k Ω resistor opens,
 4. The voltage gain will
 - (a) increase
 - (b) decrease
 - (c) not change
 5. The offset voltage compensation will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 14–65.

- If the 10 k Ω resistor opens,
 6. The magnitude of the output signal voltage will
 - (a) increase
 - (b) decrease
 - (c) not change

7. The amplifier open-loop gain will
 - (a) increase
 - (b) decrease
 - (c) not change

Refer to Figure 14–69.

- If R_1 has a value smaller than specified,
 8. The output frequency will
 - (a) increase
 - (b) decrease
 - (c) not change
- If C_2 is larger than its specified value,
 9. The output frequency will
 - (a) increase
 - (b) decrease
 - (c) not change
- If the positive dc supply voltage increases,
 10. The amplitude of the output voltage will
 - (a) increase
 - (b) decrease
 - (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 14–1 Analog Switches

1. Determine the output waveform for the analog switch in Figure 14–59(a) for each set of waveforms in parts (b), (c), and (d).

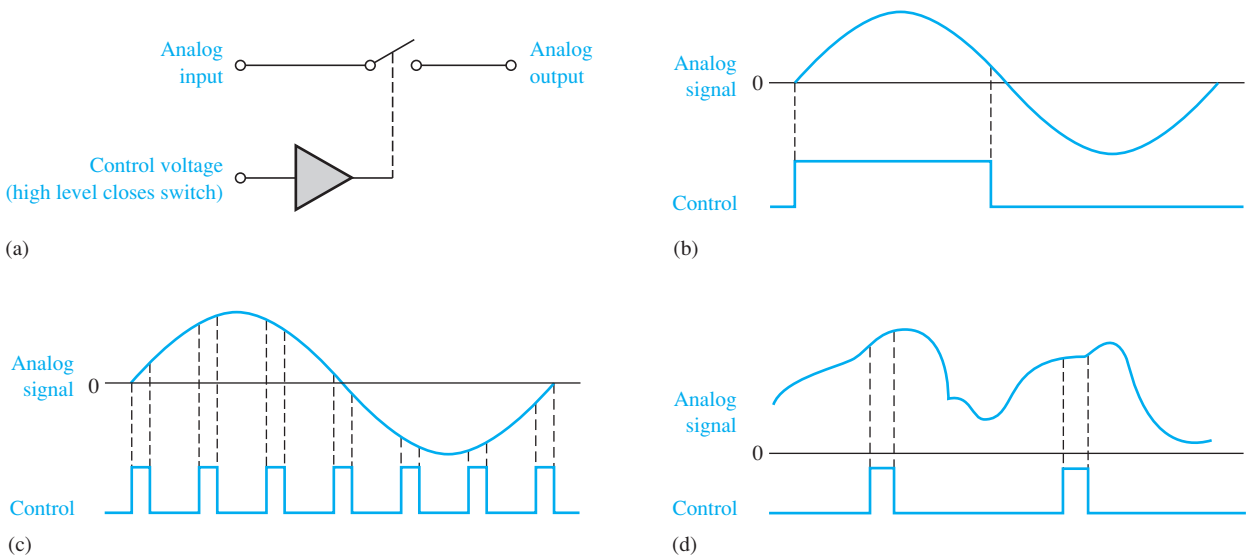


FIGURE 14–59

2. Determine the output of the 4-channel analog multiplexer in Figure 14-60 for the signal and control inputs shown. Assume each switch closes with a high input.

 


FIGURE 14-60

SECTION 14-2 Sample-and-Hold Amplifiers

3. Determine the output voltage waveform for the sample/track-and-hold amplifier in Figure 14-61 given the analog input and the control voltage waveforms shown. Sample is the high control level.

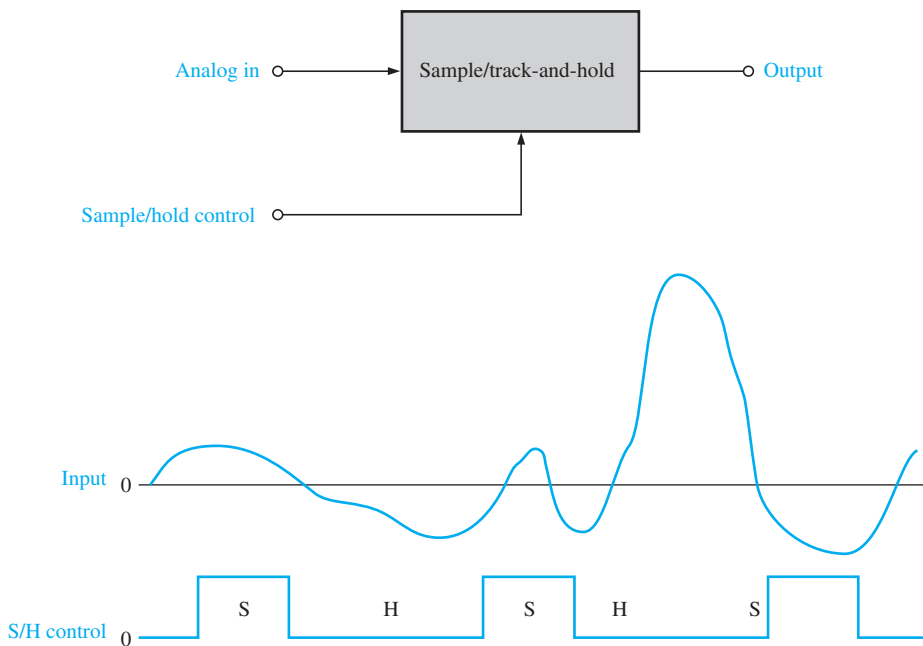


FIGURE 14-61

4. Repeat Problem 3 for the waveforms in Figure 14-62.



 


FIGURE 14-62

 5. Determine the gain of each AD585 sample-and-hold amplifier in Figure 14-63.



(a)

 

(b)

FIGURE 14-63

SECTION 14-3 Interfacing the Analog and Digital Worlds

6. The analog signal in Figure 14-64 is sampled at 2 ms intervals. Represent the signal by a series of 4-bit binary numbers.
7. Sketch the digital reproduction of the analog curve represented by the series of binary numbers developed in Problem 6.
8. Graph the analog signal represented by the following sequence of binary numbers: 1111, 1110, 1101, 1100, 1010, 1001, 1000, 0111, 0110, 0101, 0100, 0101, 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1100, 1011, 1010, 1010.

 


FIGURE 14-64

SECTION 14-4 Digital-to-Analog (D/A) Conversion

9. In a certain 4-bit DAC, the lowest-weighted resistor has a value of 10 kΩ. What should the values of the other input resistors be?
10. Determine the output of the DAC in Figure 14-65(a) if the sequence of 4-bit numbers in part (b) is applied to the inputs.

 


FIGURE 14-65

11. Repeat Problem 10 for the inputs in Figure 14-66.
12. Determine the resolution expressed as a percentage for each of the following DACs:
 - (a) 3-bit
 - (b) 10-bit
 - (c) 18-bit

 


 
FIGURE 14-66

SECTION 14–5 Basic Concepts of Analog-to-Digital (A/D) Conversion

 
13. How many discrete values of an analog signal can each of the following ADCs represent?
(a) 4-bit (b) 5-bit (c) 8-bit (d) 16-bit
14. Determine the Nyquist rate for sinusoidal voltages with each of the following periods:
(a) 10 s (b) 1 ms (c) 30 μs (d) 1000 ns
15. What is the quantization error expressed in volts of an ADC with a sample-and-hold input for a sampled value of 3.2 V if the sample-and-hold has a droop of 100 mV/s? Assume that the conversion time of the ADC is 10 ms.

SECTION 14–6 Analog-to-Digital (A/D) Conversion Methods

16. Determine the binary output sequence of a 3-bit flash ADC for the analog input signal in Figure 14–67. The sampling rate is 100 kHz and $V_{\text{REF}} = 8 \text{ V}$.

**FIGURE 14–67**

17. Repeat Problem 16 for the analog waveform in Figure 14–68.
18. For a certain 4-bit successive-approximation ADC, the maximum ladder output is +8 V. If a constant +6 V is applied to the analog input, determine the sequence of binary states for the SAR.

**FIGURE 14–68****SECTION 14–7 Voltage-to-Frequency (V/F) and Frequency-to-Voltage (F/V) Converters**

19. The analog input to a V/F converter increases from 0.5 V to 3.5 V. Does the output frequency increase, decrease, or remain unchanged?
20. Assume that when the input to a certain V/F converter is 0 V, there is no output signal (0 Hz). Also, when a constant +2 V is applied to the input, the corresponding output frequency is 1 kHz. Now, if the input takes a step up to +4 V, what is the output frequency?
21. Calculate the value of the timing capacitor required to produce a 5 μs pulse width in an AD650 V/F converter.

22. Determine the increase in the integrator output voltage during the reset interval in the AD650 shown in Figure 14–69.

 


FIGURE 14–69

23. Determine the minimum and maximum output frequencies of the AD650 in Figure 14–69 for the portion of the input voltage shown within the shaded area in Figure 14–70.

 


FIGURE 14–70

SECTION 14–8 Troubleshooting

24. A 4-bit DAC has failed in such a way that the MSB is stuck at 0. Draw the analog output when a straight binary sequence is applied to the inputs.
25. A straight binary sequence is applied to a 4-bit DAC and the output in Figure 14–71 is observed. What is the problem?
26. An ADC produces the following sequence of binary numbers when a certain analog signal is applied to its input: 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 0110, 0101, 0100, 0011, 0010, 0001, 0000.
- (a) Reconstruct the input from the digital codes as a DAC would.
- (b) If the ADC failed so that the code 0111 were missing from the output, what would the reconstructed output look like?

 


FIGURE 14-71

ANSWERS TO SECTION CHECKUPS

SECTION 14-1

1. To switch analog signals on or off electronically.
2. An analog multiplexer switches analog voltages from several lines onto a common output line in a time sequence.
3. The outputs of the AD9300 are in a high-impedance state when the chip is not enabled, allowing more than one output to be connected together.

SECTION 14-2

1. A sample-and-hold retains the value of an analog signal taken at a given point.
2. Droop is the decrease in the held voltage due to capacitor leakage.
3. Aperture time is the time required for an analog switch to fully open at the end of a sample pulse.
4. Acquisition time is the time required for the device to reach final value at the start of the sample pulse.

SECTION 14-3

1. Natural quantities are in analog form.
2. A/D conversion changes an analog quantity into digital form.
3. D/A conversion changes a digital quantity into analog form.

SECTION 14-4

1. Each input resistor must have a different value.
2. 6.67%
3. Resistor ratios can be much more precisely matched in a monolithic IC and switch resistance can be compensated for.

SECTION 14-5

1. The time for a sampled analog value to be converted to digital is the conversion time.
2. Greater than 200 Hz.
3. The sample-and-hold keeps the sampled value constant during conversion.

SECTION 14-6

1. Flash is the fastest method of A/D conversion.
2. Tracking A/D conversion uses an up-down counter.
3. True

SECTION 14-7

1. V/F components: integrator, comparator, one-shot, current source, and switch
2. The output frequency increases proportionally.
3. The V/F converter has a voltage input and a frequency output. The F/V converter has a frequency input and a voltage output.
4. 5.0 kHz

SECTION 14-8

1. Nonmonotonicity is indicated by a step reversal.
2. Step amplitudes are less than ideal.
3. Missing code, incorrect code, offset (any two)

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

14-1 See Figure 14-72.

 


FIGURE 14-72

14-2 The same tones will be closer together.

14-3 See Figure 14-73.

 


FIGURE 14-73

- 14-4 0.25 V
- 14-5 0.00038%
- 14-6 010, 011, 011, 011, 010, 001, 000, 000, 001, 010, 011, 011
- 14-7 $f_{min} = 40 \text{ kHz}, f_{max} = 240 \text{ kHz}$
- 14-8 See Figure 14-74.
- 14-9 A constant 15 V output.

 


FIGURE 14-74

ANSWERS TO SELF-TEST

- 1. (b)
- 2. (c)
- 3. (d)
- 4. (e)
- 5. (c)
- 6. (c)
- 7. (c)
- 8. (b)
- 9. (b)
- 10. (d)
- 11. (a)
- 12. (d)
- 13. (b)
- 14. (c)
- 15. (d)
- 16. (a)

ANSWERS TO TROUBLESHOOTER'S QUIZ

- 1. decrease
- 2. not change
- 3. decrease
- 4. decrease
- 5. not change
- 6. increase
- 7. not change
- 8. increase
- 9. decrease
- 10. increase

CHAPTER 15

MEASUREMENT AND CONTROL

OUTLINE

- 15-1 RMS-to-DC Converters
- 15-2 Angle Measurement
- 15-3 Temperature Measurement
- 15-4 Strain Measurement, Pressure Measurement, and Motion Measurement
- 15-5 Power Control

OBJECTIVES

- Describe the basic operation of rms-to-dc converters
- Discuss angle measurement using a synchro
- Discuss the operation of three types of temperature-measuring circuits
- Describe methods of measuring strain, pressure, and motion
- Describe how power to a load is controlled

KEY TERMS

Root mean square
Transducer
Synchro
Resolver
Synchro-to-digital
converter (SDC)
Resolver-to-digital
converter (RDC)
Thermocouple

Resistance temperature
detector (RTD)
Thermistor
Strain gage
Thyristor
Silicon-controlled
rectifier (SCR)
Triac
Zero-voltage switching

INTRODUCTION

This chapter introduces several types of transducers and related circuits for measuring basic physical analog parameters such as angular position, temperature, strain, pressure, and flow rate.

A transducer is a device that converts a physical parameter into another form. Transducers can be used at the input (a microphone) or output (a speaker) of a system. With electronic-measuring systems, the input transducer converts a quantity to be measured (temperature, humidity, flow rate, weight) into an electrical parameter (voltage, current, resistance, capacitance) that can be processed by an electronic instrument or system.

Transducers and their associated circuits are important in many systems. The measurement of angular position is critical in robotics, radar, and industrial machine control. Temperature-measuring and pressure-measuring systems are used in industry for monitoring temperatures and pressures of various fluids or gases in tanks and pipes, and they are used in automotive applications for measuring temperatures and pressures in various parts of the automobile. Strain measurement is important for testing the strength of materials under stress in such areas as aircraft design. Also, the silicon-controlled rectifier, triac, and zero-voltage switch, which are important power control applications, are introduced in this chapter.

VISIT THE WEBSITE

Study aids for this chapter are available at
<http://pearsonhighered.com/floyd>

15-1 RMS-TO-DC CONVERTERS

One important application of rms-to-dc converters is in noise measurement for determining thermal noise, transistor, and switch contact noise. Another application is in the measurement of signals from mechanical phenomena such as strain, vibration, and expansion or contraction. RMS-to-dc converters are also useful for accurate measurements of low-frequency, low duty-cycle pulse trains.

After completing this section, you should be able to

- Describe the basic operation of rms-to-dc converters
- Define *rms*
- Explain the rms-to-dc conversion process
- List the basic circuits in an rms-to-dc converter
- Discuss the difference between explicit and implicit rms-to-dc converters
- Give examples of rms-to-dc converter applications

Definition of RMS

RMS stands for **root mean square** and is related to the amplitude of an ac signal. In practical terms, the rms value of an ac voltage is equal to the value of a dc voltage required to produce the same heating effect in a resistance. For this reason, it is sometimes called the *effective* value of an ac voltage. For example, an ac voltage with an rms value of 1 V produces the same amount of heat in a given resistor as a 1 V dc voltage. Mathematically, the rms value is found by taking the square root of the average (**mean**) of the signal voltage squared, as expressed in the following formula:

$$V_{rms} = \sqrt{\text{avg}(V_{in}^2)} \quad (15-1)$$

RMS-to-DC Conversion

RMS-to-dc converters are electronic circuits that continuously compute the square of the input signal voltage, average it, and take the square root of the result. The output of an rms-to-dc converter is a dc voltage that is proportional to the rms value of the input signal. The block diagram in Figure 15-1 illustrates the basic conversion process.


 


FIGURE 15-1 The rms-to-dc conversion process.

THE SQUARING CIRCUIT The squaring circuit is generally a linear multiplier with the signal applied to both inputs as shown in Figure 15-2. Linear multipliers were introduced in Chapter 13.

FIGURE 15-2 The squaring circuit is a linear multiplier.

 

THE AVERAGING CIRCUIT The simplest type of averaging circuit is a single-pole low-pass filter on the input of an op-amp voltage-follower, as shown in Figure 15-3.

 


FIGURE 15-3 A basic averaging circuit.

The RC filter passes only the dc component (average value) of the squared input voltage. The overbar designates an average value.

THE SQUARE ROOT CIRCUIT A square root circuit uses a linear multiplier in an op-amp feedback loop as shown in Figure 15-4. Note that the op-amp output signal is applied to both inputs of the linear multiplier.

 


FIGURE 15-4 A square root circuit.

A Complete RMS-to-DC Converter

Figure 15-5 shows the three functional circuits combined to form an rms-to-dc converter. This combination is often referred to as an *explicit* rms-to-dc converter because of the straightforward method used in determining the rms value.

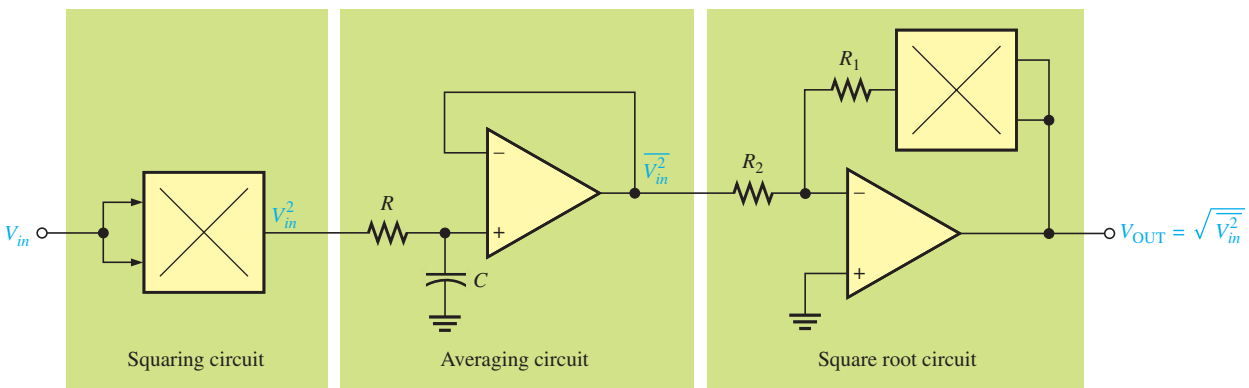


FIGURE 15-5 Explicit type of rms-to-dc converter.

Another method for achieving rms-to-dc conversion, sometimes called the *implicit* method, uses feedback to perform the square root operation. A basic circuit is shown in Figure 15-6. The first block squares the input voltage and divides by the output voltage. The averaging circuit produces the final dc output voltage, which is fed back to the squarer/divider circuit.

 


FIGURE 15-6 Implicit type of rms-to-dc converter.

The operation of the circuit in Figure 15-6 can be understood better by going through the mathematical steps performed by the circuit as follows. The expression for the output of the squarer/divider is

$$\frac{\overline{V_{in}^2}}{V_{OUT}}$$

The voltage at the noninverting (+) input to the voltage-follower is

$$V_{in(NI)} = \frac{\overline{V_{in}^2}}{V_{OUT}}$$

where the overbar indicates average value. The final output voltage is

$$V_{OUT} = \frac{\overline{V_{in}^2}}{V_{OUT}}$$

$$V_{OUT}^2 = \overline{V_{in}^2}$$

$$V_{OUT} = \sqrt{\overline{V_{in}^2}} \tag{15-2}$$

The AD637 IC RMS-to-DC Converter

As an example of a specific IC device, let’s look at the AD637 rms-to-dc converter. The data sheet for this device can be found at www.analog.com. This device is essentially an implicit type of converter except that it has an absolute value circuit at the input and it uses an inverting low-pass filter for averaging, remember that the overbar represents an average value, as indicated in Figure 15-7. The averaging capacitor, C_{avg} , is an external component that can be selected to provide a minimum averaging error under various input conditions.

 


FIGURE 15-7 Basic diagram of the AD637 rms-to-dc converter.

The absolute value circuit in the first block is simply a full-wave rectifier that changes all the negative portions of an input voltage to positive. The squarer/divider circuit is actually implemented with log and antilog circuits as shown in Figure 15-8.

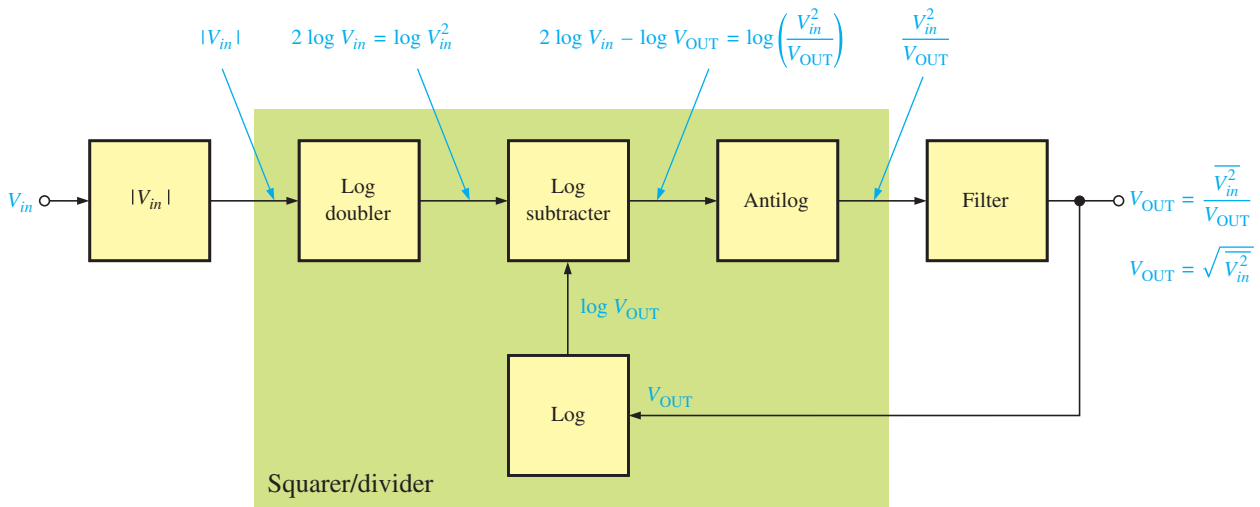


FIGURE 15-8 Internal function diagram of the AD637.

Notice that the second block in Figure 15-8 produces the log of the square of the input by taking the log of V_{in} and then multiplying it by two.

$$2 \log V_{in} = \log V_{in}^2$$

This equation is based on the fundamental rule of logarithms that states the log of a variable squared is equal to twice the log of the variable. The third block is a subtracter that subtracts the logarithm of the output voltage from the log of the input squared.


$$2 \log V_{in} - \log V_{OUT} = \log V_{in}^2 - \log V_{OUT} = \log\left(\frac{V_{in}^2}{V_{OUT}}\right)$$

This equation is based on the fundamental rule of logarithms that states that the difference of two logarithmic terms equals the logarithm of the quotient of the two terms. The antilog circuit takes the antilog of $\log(V_{in}^2/V_{OUT})$ and produces an output equal to V_{in}^2/V_{OUT} , as indicated in the figure. The low-pass filter averages the output of the antilog circuit and produces the final output.

All ac-to-dc converters introduce some amount of error, and these errors come from a variety of sources. Low-frequency or *static errors* are comprised of offset errors, scale factor (gain) errors, and nonlinearity errors. Static errors apply only to waveforms below 1 kHz. In modern ac-to-dc converters, static errors are extremely low. Static error ratings are usually designated as the sum of a constant plus a percentage of the reading. For example, the AD8436 is rated at $\pm 10 \mu\text{V} \pm 0.5\%$ of reading. This means that the maximum static error will be no greater than 0.5% of the true rms value plus 10 μV .

At higher frequencies, or for complex waveforms that have high harmonic content, other sources of error are introduced. One common way to define a complex waveform is its crest factor. The *crest factor* of a waveform is the ratio of its peak value to its effective (rms) value. For example, a dc signal has a crest factor of 1, while a pure sine wave, or a full-wave rectified sine wave, has a crest factor of 1.414. As a rule, the higher the crest factor, the higher the harmonic content. This is especially a concern when trying to convert high amplitude pulse trains with low duty cycles. The high amplitude can cause overload problems, while the low duty cycle requires high resolution. The AD8436 is rated for accurate conversions for crest factors up to 10. The data sheet for the AD8436 can be found at www.analog.com.

SYSTEM NOTE

 


Examples of RMS-to-DC Converter Applications

In addition to the measurement applications mentioned in the section introduction, rms-to-dc converters are used in a variety of system applications. A couple of typical applications are in automatic gain control (AGC) circuits and rms voltmeters. Let's look at each of these in a general way.


AGC CIRCUITS Figure 15–9 shows a general diagram of an AGC circuit that incorporates an rms-to-dc converter. AGC circuits are used in audio systems to keep the output amplitude constant when the input signal level varies over a certain range. They are also used in signal generators to keep the output amplitude constant with variations in waveform, duty cycle, and frequency.

FIGURE 15–9 A simplified AGC circuit using an rms-to-dc converter.

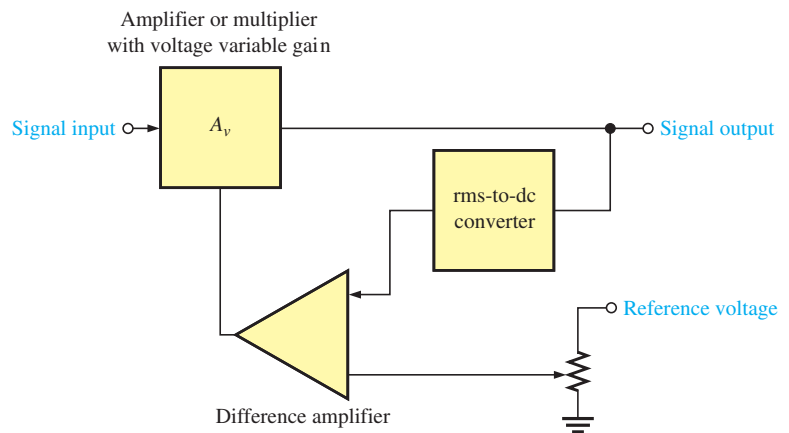

RMS VOLTMETERS Figure 15–10 basically illustrates the rms-to-dc converter in an rms voltmeter. The rms-to-dc converter produces a dc output that is equivalent to the rms value of the input signal. This dc value is then converted to digital form by an ADC and displayed.

FIGURE 15–10 A simplified rms voltmeter.

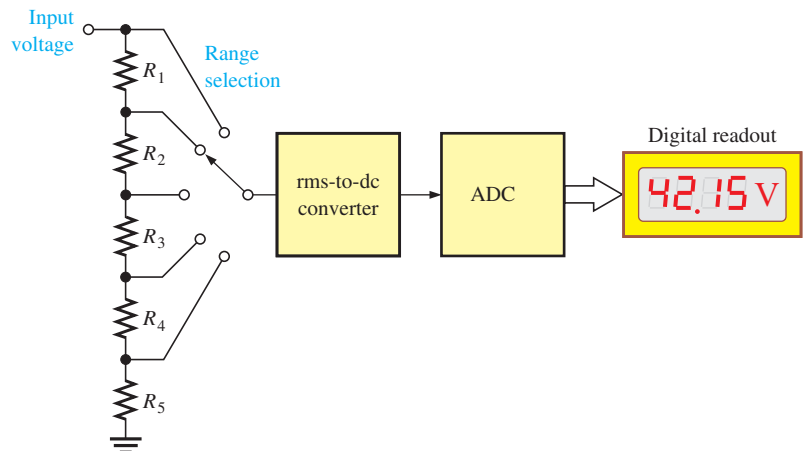

SECTION 15–1 CHECKUP*

1. What is the basic purpose of an rms-to-dc converter?
2. What are the three internal functions performed by an rms-to-dc converter?

15–2 ANGLE MEASUREMENT

In many applications, the angular position of a shaft or other mechanical mechanism must be measured and converted to an electrical signal for processing or display. Examples of this mechanical-to-electrical interfacing are found in radar and satellite antennas, wind vanes, solar systems, industrial machines including robots, and military fire control systems, to name a few. In this section, the circuits for interfacing angular position transducers, called synchros, are introduced. **Transducers**, in general, are devices that convert a physical parameter from one form to another. Before we get into the circuits used in angular measurements, a brief introduction to synchros will provide some background.

After completing this section, you should be able to

- Discuss angle measurement using a synchro
 - Define *synchro* and explain the basic operation
 - Define *resolver* and explain the basic operation
 - Discuss synchro-to-digital converters and resolver-to-digital converters
 - Describe the basic operation of an RDC
 - Show how angles can be represented by digital codes
 - Discuss an RDC application

Synchros

A **synchro** is an electromechanical transducer used for shaft angle measurement and positioning. There are several different types of synchros, but all can be thought of basically as rotating transformers. In physical appearance, a synchro resembles a small ac motor, as shown in Figure 15–11(a), with a diameter ranging from about 0.5 in. to about 4 in.

 


FIGURE 15–11 A typical synchro and its basic winding structure.

The basic synchro consists of a **rotor**, which can revolve within a fixed **stator** assembly. A shaft is connected to the rotor so that when the shaft rotates, the rotor also rotates. In most synchros, there is a rotor winding and three stator windings. The stator windings are connected as shown in Figure 15–11(b) and are separated by 120° around the stator. The windings are brought out to a terminal block at one end of the housing.

SYNCHRO VOLTAGES When a reference sinusoidal voltage is applied across the rotor winding, the voltage induced across any one of the stator windings is proportional to the sine of the angle (θ) between the rotor winding and the stator winding. The angle θ is dependent on the shaft position.

The voltage induced across any two stator windings (between any two stator terminals) is the sum or difference of the two stator voltages. These three voltages, called *synchro format voltages*, are represented in Figure 15–12 and are derived using a basic trigonometric identity. The important thing is that each of the three synchro format voltages is a function of

 


FIGURE 15-12 Synchro format voltages with a reference voltage applied to the rotor.

the shaft angle, θ , and can be used to determine the angular position at any time. As the shaft rotates, the format voltages change proportionally.

Resolvers

The **resolver** is a particular type of synchro that is often used in rotational systems to transduce the angular position. Resolvers differ from regular synchros in that the rotor and two stator windings are separated from each other by 90° rather than by 120° . The basic winding configuration of a simple resolver is shown in Figure 15-13.

 


FIGURE 15-13 Simple resolver winding configuration.

RESOLVER VOLTAGES If a reference sinusoidal voltage is applied to the rotor winding, the resulting voltages across the stator windings are as given in Figure 15-14. These voltages are a function of the shaft angle θ and are called *resolver format voltages*. One of the voltages is proportional to the sine of θ and the other voltage is proportional to the cosine of θ . Notice that the resolver has a four-terminal output compared to the three-terminal output of the standard synchro.

 


FIGURE 15-14 Resolver format voltages with a reference voltage applied to the rotor.

Basic Operation of Synchro-to-Digital and Resolver-to-Digital Converters

Synchro-to-digital converters (SDCs) and **resolver-to-digital converters (RDCs)** are electronic circuits used to convert the format voltages from a synchro or resolver to a digital format. These devices may be considered a very specialized form of analog-to-digital converter.

All converters, both SDCs and RDCs, operate internally with resolver format voltages. Therefore, the output format voltages of a synchro must first be transformed into resolver format by a special type of transformer called the *Scott-T transformer*, as illustrated in Figure 15-15.

 


FIGURE 15-15 Inputs and outputs of a Scott-T transformer.

Some SDCs have internal Scott-T transformers, but others require a separate transformer. Other than the transformer, the basic operation and internal circuitry of SDCs and RDCs are the same, so let's focus on RDCs. A simplified block diagram of a tracking RDC is shown in Figure 15-16.

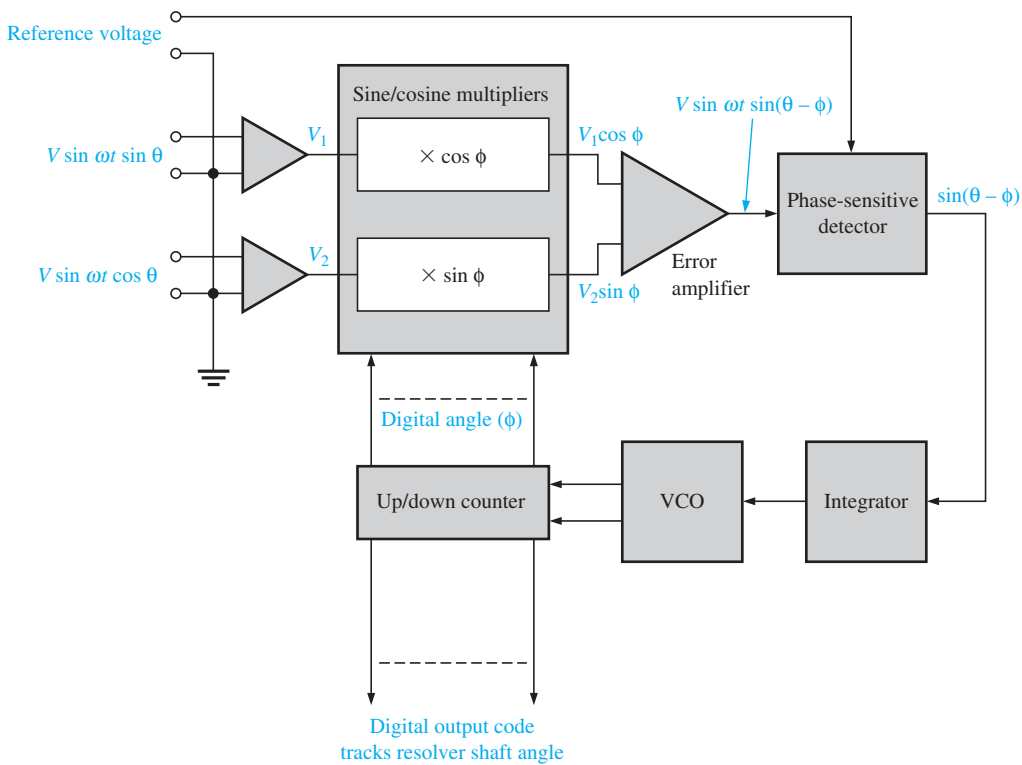


FIGURE 15-16 Simplified diagram of a resolver-to-digital converter (RDC).

The two resolver format voltages, $V_1 = V \sin \omega t \sin \theta$ and $V_2 = V \sin \omega t \cos \theta$, are applied to the RDC inputs as indicated in Figure 15-16 (θ is the current shaft angle of the resolver). These resolver voltages go through buffers to special multiplier circuits. Let's assume that the current state of the up/down counter represents some angle, ϕ . The digital code representing ϕ is applied to the multiplier circuits along with the resolver voltages. The cosine multiplier takes the cosine of ϕ and multiplies it times the resolver voltage V_1 . The resulting output of the cosine multiplier is

$$V_1 \cos \phi = V \sin \omega t \sin \theta \cos \phi$$

The resulting output of the sine multiplier is

$$V_2 \sin \phi = V \sin \omega t \cos \theta \sin \phi$$

These two voltages are subtracted by the error amplifier to produce the following error voltage:

$$V \sin \omega t \sin \theta \cos \phi - V \sin \omega t \cos \theta \sin \phi = V \sin \omega t (\sin \theta \cos \phi - \cos \theta \sin \phi)$$

A basic trigonometric identity reduces the error voltage expression to

$$V \sin \omega t \sin(\theta - \phi)$$

The phase-sensitive detector produces a dc error voltage proportional to $\sin(\theta - \phi)$, which is applied to the integrator. The output of the integrator drives a voltage-controlled oscillator (VCO), which provides clock pulses to the up/down counter. When the counter reaches the value of the current shaft angle θ , then $\phi = \theta$ and

$$\sin(\theta - \phi) = 0$$

If the sine is zero, then the difference of the angles is 0° .

$$\theta - \phi = 0^\circ$$

At this point, the angle stored in the counter equals the resolver shaft angle.

$$\phi = \theta$$

When the shaft angle changes, the counter will count up or down until its count equals the new shaft angle. Therefore, the RDC will continuously track the resolver shaft angle and produce an output digital code that equals the angle at all times.

Representation of Angles with a Digital Code

The most common method of representing an angular measurement with a digital code is given in Table 15–1 for word lengths up to 16 bits. A binary 1 in any bit position means that

TABLE 15–1 • Bit weights for resolver-to-digital conversion.

BIT POSITION	ANGLE (DEGREES)
1 (MSB)	180.00000
2	90.00000
3	45.00000
4	22.50000
5	11.25000
6	5.62500
7	2.81250
8	1.40625
9	0.70313
10	0.35156
11	0.17578
12	0.08790
13	0.04395
14	0.02197
15	0.01099
16	0.00549

the corresponding angle is included, and a 0 means that the corresponding angle is not included.

EXAMPLE 15-1

A certain RDC has an 8-bit digital output. What is the angle being measured if the output code is 01001101? The left-most bit is the MSB.

SOLUTION

BIT POSITION	BIT	ANGLE (DEGREES)
1	0	0
2	1	90.00000
3	0	0
4	0	0
5	1	11.25000
6	1	5.62500
7	0	0
8	1	1.40625

To get the angle represented, add all the included angles (as indicated by the presence of a 1 in the output code).

$$90.00000^\circ + 11.25000^\circ + 5.62500^\circ + 1.40625^\circ = \mathbf{108^\circ}$$

Although more digits are carried in the calculation to show the process, the answer is rounded to the nearest degree.

PRACTICE EXERCISE*

What is the angular shaft position measured by a 12-bit RDC when it has a binary code of 100000100001 on its outputs?

* Answers are at the end of the chapter.

A Specific Resolver-to-Digital Converter

To illustrate a typical IC device, let's look at the AD2S90, which is a 12-bit converter. The data sheet for the AD2S90 can be found at www.analog.com. The diagram for this device is shown in Figure 15-17, and as you can see, it is basically the same as the general RDC in Figure 15-16 with some additions. Additional circuits include the latch and serial interface for controlling the data transfer to and interfacing with other digital systems. These additional circuits do not affect the conversion process.

Additional outputs include the Direction (DIR) output, which indicates the direction of rotation of the resolver shaft. The Velocity output is proportional to the rate of change of the input angle.


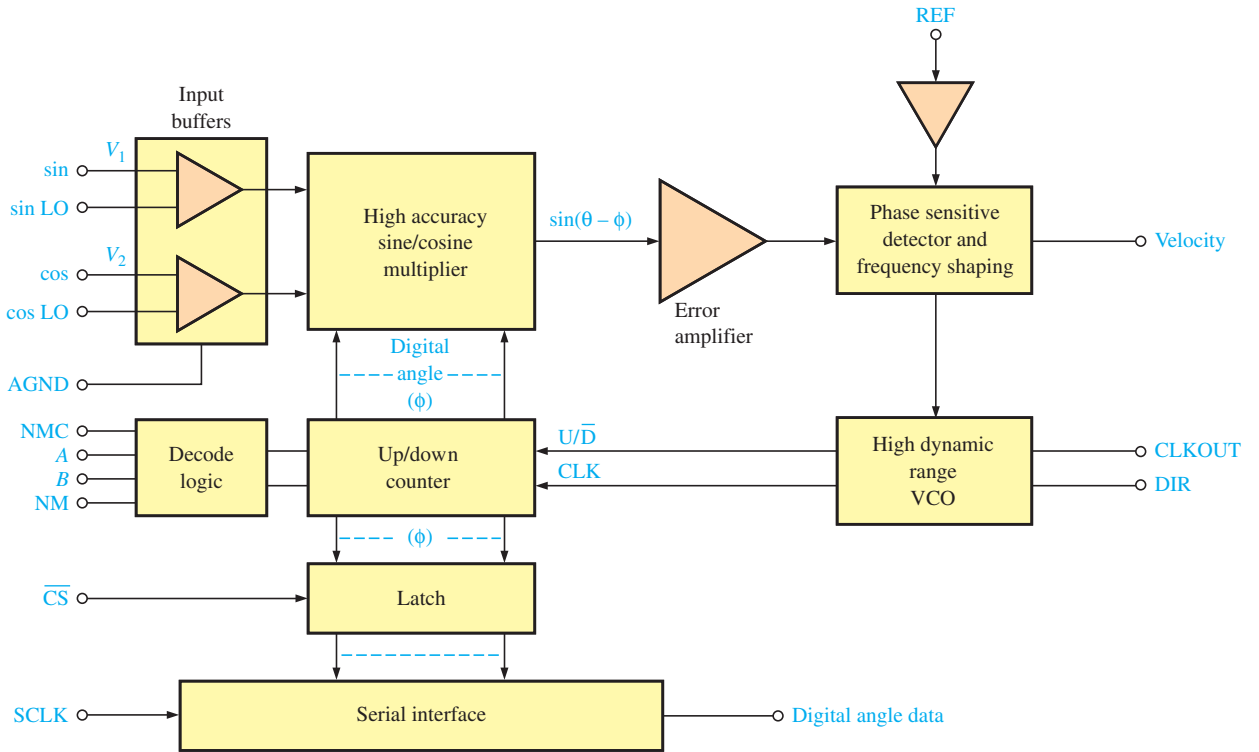


FIGURE 15-17 Diagram of the AD2S90 resolver-to-digital converter.

SYSTEM EXAMPLE 15-1

 

A WIND-DIRECTION SYSTEM

The measurement of wind direction is one example of how an RDC can be used. As shown in Figure SE15-1, a wind vane is fixed to the shaft of a resolver. As the wind vane moves to align with the direction of the wind, the resolver shaft rotates and its angle indicates the wind direction. The resolver output is applied to an RDC and the resulting digital output code, which represents the wind direction, drives a digital readout.

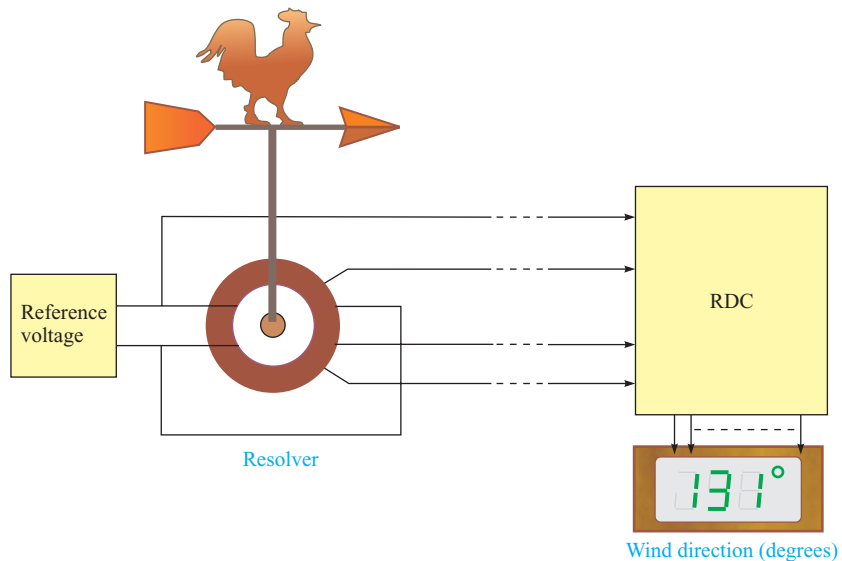


FIGURE SE15-1

A more sophisticated wind-measuring system would include an instrument to measure wind speed. Basically, a propeller-type flow meter in which the blades revolve past a magnetic sensor, producing a series of pulses. The faster the wind blows, the faster the blades revolve and the more pulses are received. The AD650 frequency-to-voltage converter was introduced in Chapter 14. As you can see, this is a simple way to sense wind speed. You might want to think about how you would complete the implementation of this system.

SECTION 15-2 CHECKUP

1. What is a transducer that converts a mechanical shaft position into electrical signals called?
2. What type of input does an RDC accept?
3. What type of output does an RDC produce?
4. What is the function of an RDC?

15-3 TEMPERATURE MEASUREMENT

Temperature is perhaps the most common physical parameter that is measured and converted to electrical form. Several types of temperature sensors respond to temperature and produce a corresponding indication by a change or alteration in a physical characteristic that can be detected by an electronic circuit. Common types of temperature sensors are thermocouples, resistance temperature detectors (RTDs), and thermistors. In this section, we will look at each of these sensors and at signal conditioning circuits that are required to interface the transducers to electronic equipment.

After completing this section, you should be able to

- Discuss the operation of three types of temperature-measuring circuits
- Describe the thermocouple and how to interface it with an electronic circuit
- Describe the resistance temperature detector (RTD) and circuit interfacing
- Describe the thermistor and circuit interfacing

The Thermocouple

The **thermocouple** is formed by joining two dissimilar metals. A small voltage, called the *Seebeck voltage*, is produced across the junction of the two metals when heated, as illustrated in Figure 15-18. The amount of voltage produced is dependent on the types of metals and is directly proportional to the temperature of the junction (positive temperature coefficient); however, this voltage is generally much less than 100 mV. Measurement systems often use an instrumentation amplifier as a means of avoiding noise with thermocouple measurements. The voltage versus temperature characteristic of thermocouples is somewhat nonlinear, but the amount of nonlinearity is predictable. Thermocouples are widely used in certain industries because they have a wide temperature range and can be used to measure very high temperatures.

Some common metal combinations used in commercial thermocouples are chromel-alumel (chromel is a nickel-chromium alloy and alumel is a nickel-aluminum alloy), iron-constantan (constantan is a copper-nickel alloy), chromel-aluminum, tungsten-rhenium alloys, and platinum-10% Rh/Pt. Each of these

 


FIGURE 15-18 A voltage proportional to temperature is generated when a thermocouple is heated.

types of thermocouple has a different temperature range, coefficient, and voltage characteristic and is designated by the letter *E*, *J*, *K*, *W*, and *S*, respectively. The overall temperature range covered by thermocouples is from -250°C to 2000°C . Each type covers a different portion of this range, as shown in Figure 15–19.

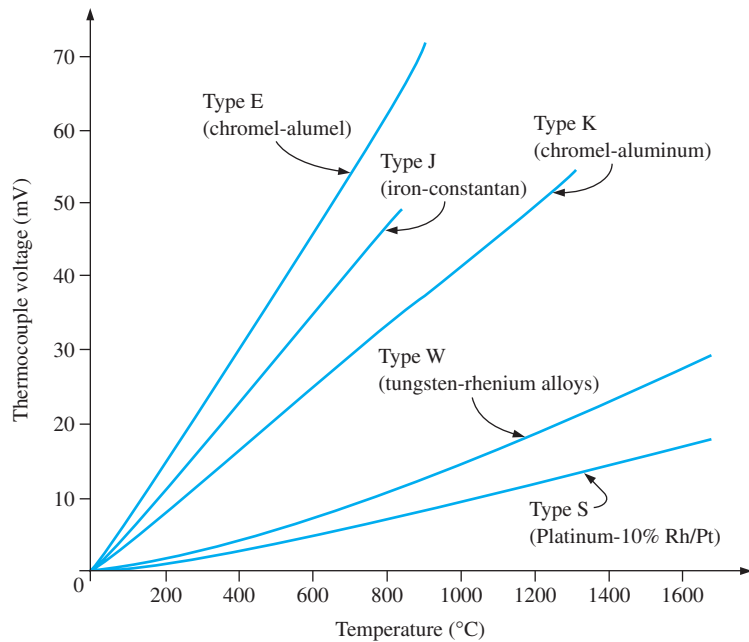


FIGURE 15–19 Output of some common thermocouples with 0°C as the reference temperature.

THERMOCOUPLE-TO-ELECTRONICS INTERFACE When a thermocouple is connected to a signal-conditioning circuit, as illustrated in Figure 15–20, an *unwanted* thermocouple is effectively created at the point(s) where one or both of the thermocouple wires connect to the circuit terminals made of a dissimilar metal. The unwanted thermocouple junction is sometimes referred to as a **cold junction** in some references because it is normally at a significantly lower temperature than that being measured by the measuring thermocouple. These unwanted thermocouples can have an unpredictable effect on the overall voltage that is sensed by the circuit because the voltage produced by the unwanted thermocouple opposes the measured thermocouple voltage and its value depends on ambient temperature.

 


FIGURE 15–20 Creation of an unwanted thermocouple in a thermocouple-to-electronics interface.

EXAMPLE OF A THERMOCOUPLE-TO-ELECTRONICS INTERFACE

As shown in Figure 15-21, a copper/constantan thermocouple (known as type T) is used, in this case, to measure the temperature in an industrial temperature chamber. The copper thermocouple wire is connected to a copper terminal on the circuit board and the constantan wire is also connected to a copper terminal on the circuit board. The copper-to-copper connection is no problem because the metals are the same. The constantan-to-copper connection acts as an unwanted thermocouple that will produce a voltage in opposition to the thermocouple voltage because the metals are dissimilar.

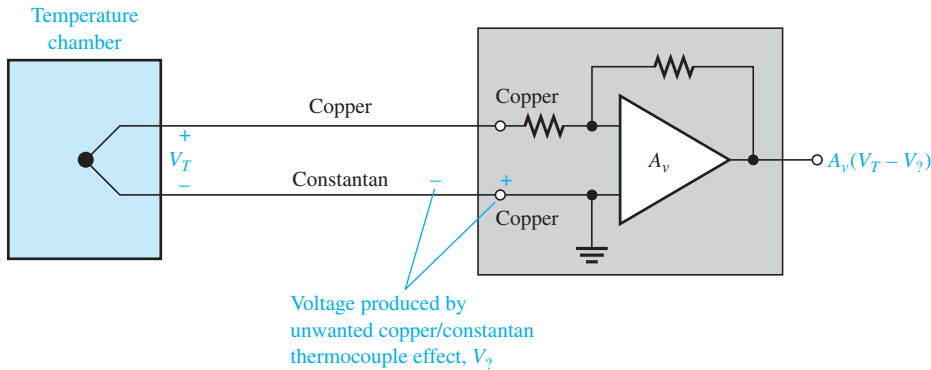


FIGURE 15-21 A simplified temperature-measuring circuit with an unwanted thermocouple at the junction of the constantan wire and the copper terminal.

Since the unwanted thermocouple connection is not at a fixed temperature, its effects are unpredictable and it will introduce inaccuracy into the measured temperature. One method for eliminating an unwanted thermocouple effect is to add a reference thermocouple at a constant known temperature (usually 0°C). Figure 15-22 shows that by using a reference thermocouple that is held at a constant known temperature, the unwanted thermocouple at the circuit terminal is eliminated because both contacts to the circuit terminals are now copper-to-copper. The voltage produced by the reference thermocouple is a known constant value and can be compensated for in the circuitry.

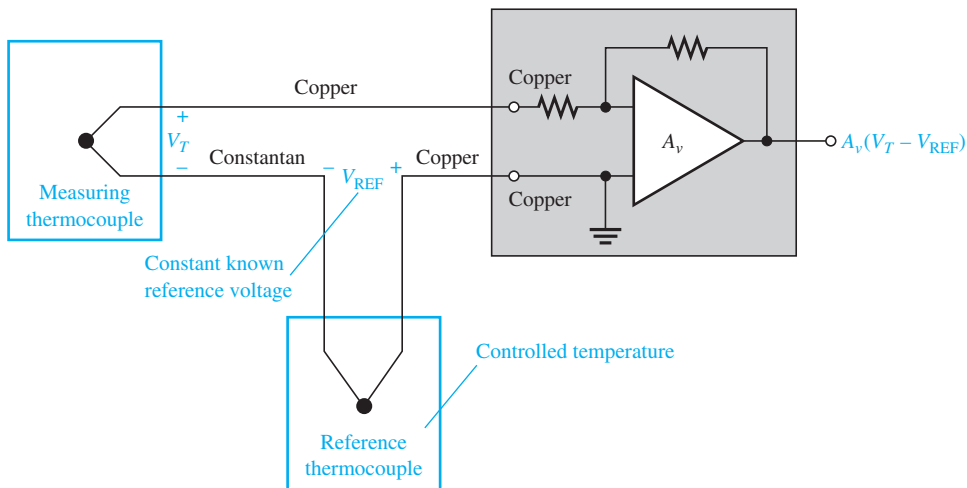


FIGURE 15-22 Using a reference thermocouple in a temperature-measuring circuit.

EXAMPLE 15–2

Suppose the thermocouple in Figure 15–21 is measuring 200°C in an industrial oven. The circuit board is in an area where the ambient temperature can vary from 15°C to 35°C. Using Table 15–2 for a type-*T* (copper/constantan) thermocouple, determine the voltage across the circuit input terminals at the ambient temperature extremes. What is the maximum percent error in the voltage at the circuit input terminals?

TEMPERATURE (°C)	OUTPUT (mV)
–200	–5.603
–100	–3.378
0	0.000
+100	4.277
+200	9.286
+300	14.860
+400	20.869

SOLUTION

From Table 15–2, you know that the measuring thermocouple is producing 9.286 mV. To determine the voltage that the unwanted thermocouple is creating at 15°C, you must interpolate from the table. Since 15°C is 15% of 100°C, a linear interpolation gives the following voltage:

$$0.15(4.277 \text{ mV}) = 0.642 \text{ mV}$$

Since 35°C is 35% of 100°C, the voltage is

$$0.35(4.277 \text{ mV}) = 1.497 \text{ mV}$$

The voltage across the circuit input terminals at 15°C is

$$9.286 \text{ mV} - 0.642 \text{ mV} = \mathbf{8.644 \text{ mV}}$$

The voltage across the circuit input terminals at 35°C is

$$9.286 \text{ mV} - 1.497 \text{ mV} = \mathbf{7.789 \text{ mV}}$$

The maximum percent error in the voltage at the circuit input terminals is

$$\left(\frac{9.286 \text{ mV} - 7.789 \text{ mV}}{9.286 \text{ mV}} \right) 100\% = \mathbf{16.1\%}$$

You can never be sure how much it is off because you have no control over the ambient temperature. Also, the linear interpolation may or may not be accurate depending on the linearity of the temperature characteristic of the unwanted thermocouple.

PRACTICE EXERCISE

In the case of the circuit in Figure 15–21, if the temperature being measured goes up to 300°C, what is the maximum percent error in the voltage across the circuit input terminals?

EXAMPLE 15-3

Refer to the thermocouple circuit in Figure 15-22. Suppose the thermocouple is measuring 200°C . Again, the circuit board is in an area where the ambient temperature can vary from 15°C to 35°C . The reference thermocouple is held at exactly 0°C . Determine the voltage across the circuit input terminals at the ambient temperature extremes.

SOLUTION

From Table 15-2 in Example 15-2, the thermocouple voltage is 0 V at 0°C . Since the reference thermocouple produces no voltage at 0°C and is completely independent of ambient temperature, there is no error in the measured voltage over the ambient temperature range. Therefore, the voltage across the circuit input terminals at both temperature extremes equals the measuring thermocouple voltage, which is **9.286 mV** .

PRACTICE EXERCISE

If the reference thermocouple were held at -100°C instead of 0°C , what would be the voltage across the circuit input terminals if the measuring thermocouple were at 400°C ?

COMPENSATION It is bulky and expensive to maintain a reference thermocouple at a fixed temperature (usually an ice bath is required). Another approach is to compensate for the unwanted thermocouple effect by adding a compensation circuit as shown in Figure 15-23. This is sometimes referred to as *cold-junction compensation*. The compensation circuit consists of a resistor and an integrated circuit temperature sensor with a temperature coefficient that matches that of the unwanted thermocouple.

 


FIGURE 15-23 Simplified circuit for compensation of unwanted thermocouple effect.

The current source in the temperature sensor produces a current that creates a voltage drop, V_c , across the compensation resistor, R_c . The resistance is adjusted so that this voltage drop is equal and opposite the voltage produced by the unwanted thermocouple at a given temperature. When the ambient temperature changes, the current changes proportionally, so that the voltage across the compensation resistor is always approximately equal to the unwanted thermocouple voltage. Since the compensation voltage, V_c , is opposite in polarity to the unwanted thermocouple voltage, the unwanted voltage is effectively cancelled.

The functions shown in the circuit of Figure 15-23 plus others are available in IC packages and hybrid modules known as *thermocouple signal conditioners*. The AD8496, 1B51, and 3B47 are examples of this type of circuit. They are designed for interfacing a thermocouple with various types of electronic systems and provide gain, compensation, isolation, common-mode rejection, and other features in one package. The data sheets for these three signal conditioners can be found at www.analog.com.

In some systems, it is necessary to measure the temperature of a small volume. This can present some unique challenges. Suppose that you are using a thermocouple to measure the temperature of a liquid in a test tube. Since all thermocouples have some mass, heating the thermocouple means that the temperature of the liquid will drop. Also, heat will travel along the thermocouple wire and be dissipated in the atmosphere. This is referred to as *thermal shunting*. In both of these cases, the smaller the liquid sample and the higher the temperature difference between the liquid and the thermocouple, the greater the impact on the accuracy of the measurement.

Thermal shunting can be reduced by choosing a thermocouple with thinner wires. The thinner wires will result in a steeper temperature gradient at the junction of the liquid and the ambient air. Unfortunately, thinner wire introduces another set of problems. Thinner wire means higher resistance, which in turn means a greater susceptibility to noise. One possible solution is to use thermocouple extension wire for the run to the measuring instrument. Extension wire is of a lower gage, has lower resistance, and thus increases noise immunity.




SYSTEM NOTE

Resistance Temperature Detectors (RTDs)

A second major type of temperature transducer is the **resistance temperature detector (RTD)**. The RTD is a resistive device in which the resistance changes directly with temperature (positive temperature coefficient). The RTD is more nearly linear than the thermocouple. RTDs are constructed in either a wire-wound configuration or by a metal-film technique. The most common RTDs are made of either platinum, nickel, or nickel alloys. Platinum RTD sensors are one of the most accurate temperature sensors available. They are capable of achieving accuracies of $\pm 0.02^\circ\text{C}$, but only if precise signal processing is applied. They also cover a relatively wide range of temperatures, typically -200°C to $+850^\circ\text{C}$.

Generally, RTDs are used to sense temperature in two basic ways. First, as shown in Figure 15–24(a), the RTD is driven by a current source and, since the current is constant, the change in voltage across it is proportional (by Ohm's law) to the change in its resistance with temperature. Second, as shown in Figure 15–24(b), the RTD is connected in a 3-wire bridge circuit, and the bridge output voltage is used to sense the change in the RTD resistance and, thus, the temperature.

 


(a) A change in temperature, ΔT , produces a change in voltage, ΔV , across the RTD proportional to the change in RTD resistance when the current is constant.

(b) A change in temperature, ΔT , produces a change in bridge output voltage, ΔV , proportional to the change in RTD resistance.


FIGURE 15–24 Basic methods of employing an RTD in a temperature-sensing circuit.

THEORY OF THE 3-WIRE BRIDGE To avoid subjecting the three bridge resistors to the same temperature that the RTD is sensing, the RTD is usually remotely located to the point where temperature variations are to be measured and connected to the rest of the bridge by long wires. The resistance of the three bridge resistors must remain constant. The long extension wires to the RTD have resistance that can affect the accurate operation of the bridge.

Figure 15–25(a) shows the RTD connected in the bridge with a 2-wire configuration. Notice that the resistance of both of the long connecting wires appear in the same leg of the

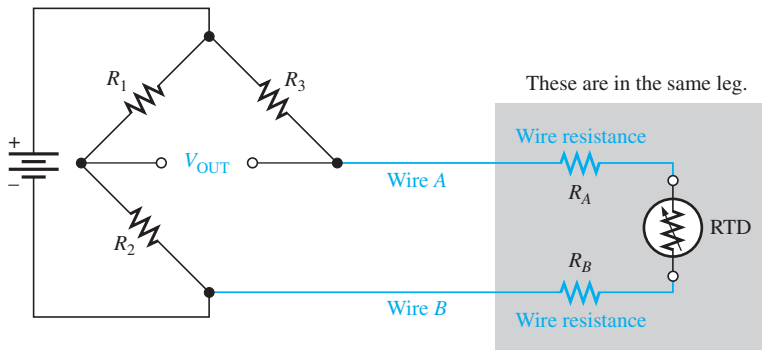

(a) Two-wire bridge connection

 

(b) Three-wire bridge connection

FIGURE 15-25 Comparison of 2-wire and 3-wire bridge connections in an RTD circuit.

bridge as the RTD. Recall from your study of basic circuits that $V_{\text{OUT}} = 0 \text{ V}$ and the bridge is balanced when $R_{\text{RTD}} = R_3$ if $R_1 = R_2$. The wire resistances will throw the bridge off balance when $R_{\text{RTD}} = R_3$ and will cause an error in the output voltage for any value of the RTD resistance because they are in series with the RTD in the same leg of the bridge.

The 3-wire configuration in Figure 15-25(b) overcomes the wire resistance problem. By connecting a third wire to one end of the RTD as shown, the resistance of wire A is now placed in the same leg of the bridge as R_3 and the resistance of wire B is placed in the same leg of the bridge as the RTD. Because the wire resistances are now in opposite legs of the bridge, their effects will cancel if both wire resistances are the same (equal lengths of the same type of wire). The resistance of the third wire has no effect; essentially no current goes through it because the output terminals of the bridge are open or are connected across a very high impedance. The balance condition is expressed as

$$R_{\text{RTD}} + R_B = R_3 + R_A$$

If $R_A = R_B$, then they cancel in the equation and the balance condition is completely independent of the wire resistances.

$$R_{\text{RTD}} = R_3$$

The method described here is important in many measurements that use a sensitive transducer and a bridge. It is often used in strain-gage measurements (described in Section 15-4).

BASIC RTD TEMPERATURE-SENSING CIRCUITS Two simplified RTD measurement circuits are shown in Figure 15-26. The circuit in part (a) is one implementation of an RTD driven by a constant current. The operation is as follows. From your study of basic op-amp circuits, recall that the input current and the current through the feedback path are essentially equal because the input impedance of the op-amp is ideally infinite. Therefore, the constant current through the RTD is set by the constant input voltage, V_{IN} , and the input resistance, R_1 , because the inverting input is at virtual ground. The RTD is in the feedback path and, therefore, the output voltage of the op-amp is equal to the voltage across the RTD. As the resistance of the RTD changes with temperature, the voltage across the RTD also changes because the current is constant.

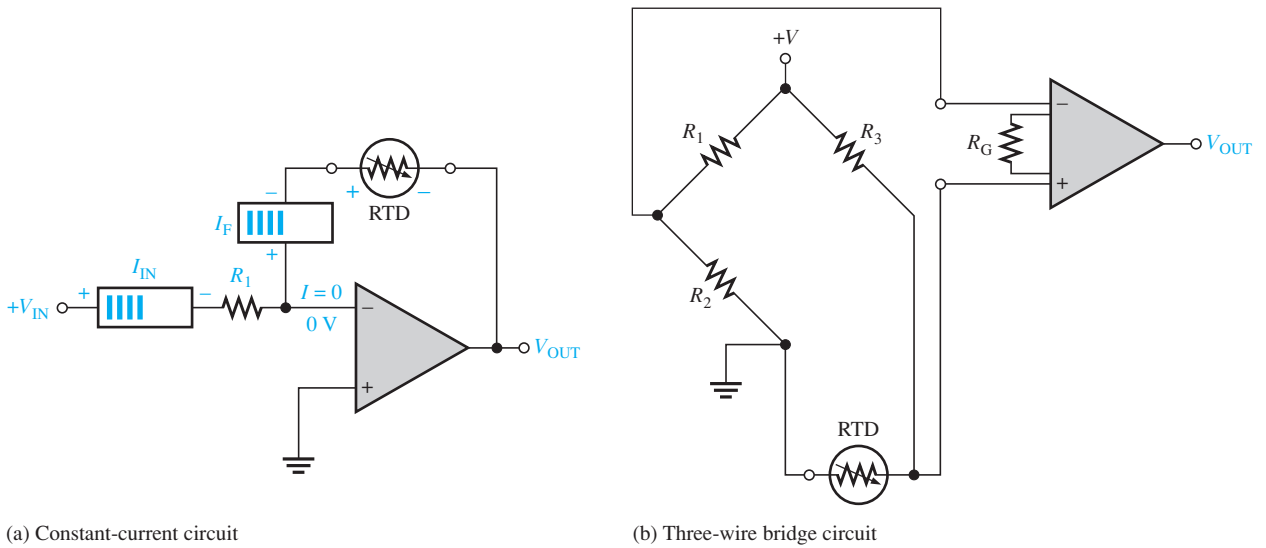



FIGURE 15-26 Basic RTD temperature-measuring circuits.

The circuit in Figure 15-26(b) shows a basic circuit in which an instrumentation amplifier is used to amplify the voltage across the 3-wire bridge circuit. The RTD forms one leg of the bridge, and as its resistance changes with temperature, the bridge output voltage also changes proportionally. The bridge is adjusted for balance ($V_{OUT} = 0 \text{ V}$) at some reference temperature, say, 0°C . This means that R_3 is selected to equal the resistance of the RTD at this reference temperature.

EXAMPLE 15-4

Determine the output voltage of the instrumentation amplifier in the RTD circuit in Figure 15-27 if the resistance of the RTD is 1320Ω at the temperature being measured.

FIGURE 15-27

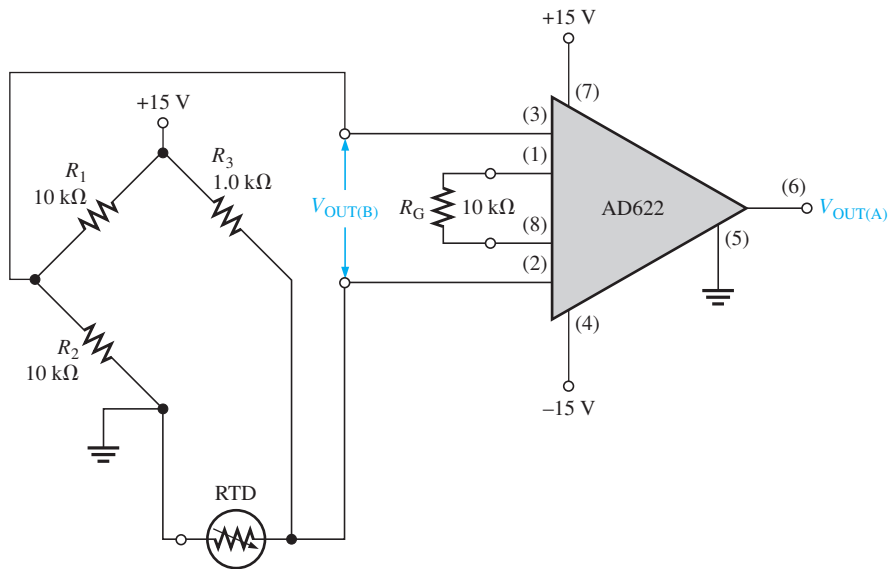

SOLUTION

The bridge output voltage is

$$\begin{aligned}
 V_{OUT(B)} &= \left(\frac{R_{RTD}}{R_3 + R_{RTD}} \right) 15 \text{ V} - \left(\frac{R_2}{R_1 + R_2} \right) 15 \text{ V} = \left(\frac{1320 \Omega}{2320 \Omega} \right) 15 \text{ V} - \left(\frac{10 \text{ k}\Omega}{20 \text{ k}\Omega} \right) 15 \text{ V} \\
 &= 8.53 \text{ V} - 7.5 \text{ V} = 1.03 \text{ V}
 \end{aligned}$$

From Equation (12-3), the voltage gain of the AD622 instrumentation amplifier is

$$R_G = \frac{50.5 \text{ k}\Omega}{A_v - 1}$$

$$A_v = \frac{50.5 \text{ k}\Omega}{R_G} + 1 = 5.05 + 1 = 6.05$$

The output voltage from the amplifier is

$$V_{\text{OUT(A)}} = (6.05)(1.03 \text{ V}) = \mathbf{6.23 \text{ V}}$$

PRACTICE EXERCISE

Solve for the nominal resistance of the RTD in Figure 15-27 that will balance the bridge at 25°C. What is the amplifier output voltage when the bridge is balanced?

Depending on the application, some modern systems use a dedicated RTD converter IC, called a microconverter. One example of a microconverter family is the ADuC8xx series from Analog Devices.

The technique used by these devices is illustrated in Figure SE15-2. A reference current source is applied to the RTD, which is connected in series with a precision reference resistor. This produces an RTD voltage and reference voltage. The RTD voltage is amplified and then digitized by an ADC. A microcontroller uses software to convert the RTD resistance to a temperature, based upon the voltage across the reference resistance. All the necessary active components are part of the microconverter, including the reference current source, differential input stages, gain stages, the ADC, and the microcontroller. For more information on microconverters refer to application note AN-709 at www.analog.com.

 


FIGURE SN15-1 Block diagram of an RTD converter.

SYSTEM NOTE

Thermistors

A third major type of temperature transducer is the **thermistor**, which is a resistive device made from a semiconductive material such as nickel oxide or cobalt oxide. Thermistors can have either a negative temperature coefficient (NTC) or a positive temperature coefficient (PTC). The resistance of an NTC thermistor decreases with temperature, while the resistance of a PTC device increases with temperature. NTC thermistors are the more common of the two. The temperature characteristic for thermistors is more nonlinear than that for thermocouples or RTDs; in fact, a thermistor's temperature characteristic is essentially logarithmic. Also, like the RTD, the temperature range of a thermistor is more limited than that of a thermocouple. Thermistors have the advantage of a greater sensitivity than either thermocouples or RTDs and are generally less expensive. This means that their change in resistance per degree change in temperature is greater. They also have a low thermal mass, which results in fast response times. Since they are both variable-resistance devices, the thermistor and the RTD can be used in similar circuits.

Like the RTD, thermistors can be used in constant-current-driven configurations or in bridges. In Figure 15–28, the general response of an NTC thermistor in a constant-current op-amp circuit is compared to that of an RTD in a similar circuit. Both the RTD and the thermistor are exposed to the same temperature environment as indicated. It is assumed that at some reference temperature, the RTD and the thermistor have the same resistance and produce the same output voltage. In the RTD circuit, as the temperature increases from the reference value, the op-amp’s output voltage increases from the reference value because the resistance of the RTD increases. In the NTC thermistor circuit, as the temperature increases, the op-amp’s output voltage decreases from the reference value because the thermistor’s resistance decreases due to its negative temperature coefficient. Also, for the same temperature change, the change in the output voltage of the thermistor circuit is greater than the corresponding change in the output voltage of the RTD circuit because of the greater sensitivity of the thermistor.


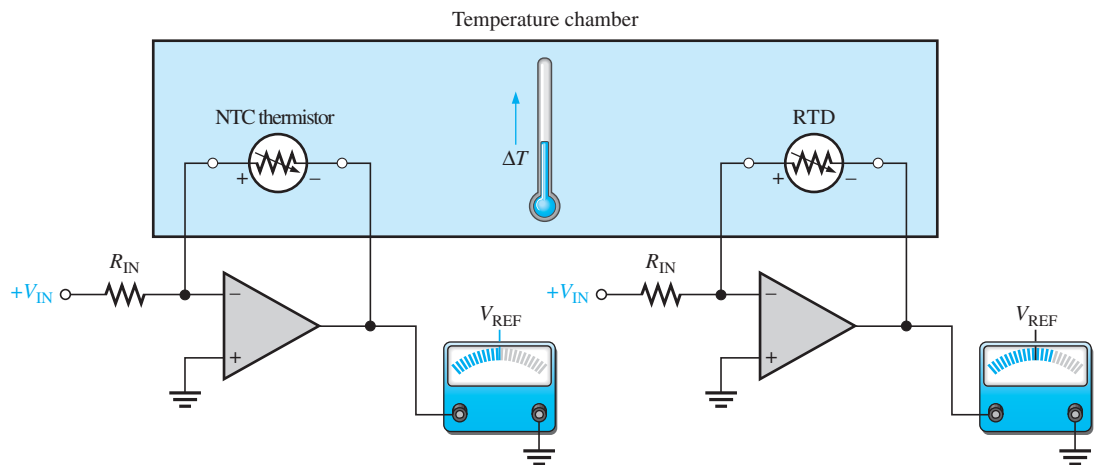


FIGURE 15–28 General comparison of the responses of an NTC thermistor circuit to a similar RTD circuit.

Thermistors are used in a variety of systems. Temperature monitoring is critical in some systems such as automotive systems. In a typical automotive system, thermistors monitor coolant temperature, passenger compartment air temperature, outside air temperature and transmission fluid temperature. If the auto is equipped with a liquid crystal display (LCD), you may find a thermistor used to monitor temperature and vary the driving current to the display. The fluid used in LCD modules is very temperature sensitive—at higher temperatures display contrast improves and at lower temperatures it degrades. This means that if a constant voltage is used to power an LCD module, it will either be too high or too low, depending on the ambient temperature. Thermistors are commonly used in the supply circuits of mobile devices to help maintain a bright, easily read screen without sacrificing efficiency. They provide a higher driving current in cold weather and a lower, more efficient current in warmer weather. In any battery operated device, efficiency is always a concern.

SYSTEM NOTE

 

SECTION 15–5 CHECKUP

1. What is a thermocouple?
2. How can temperature be measured with a thermocouple?
3. What is an RTD and how does its operation differ from a thermocouple?
4. What is the primary operational difference between an RTD and a thermistor?
5. Of the three devices introduced in this section, which one would most likely be used to measure extremely high temperatures?
6. Name three applications for thermistors in automobiles.

15-4 STRAIN MEASUREMENT, PRESSURE MEASUREMENT, AND MOTION MEASUREMENT

In this section, methods of measuring three types of force-related parameters (strain, pressure, and motion) are examined. A variety of applications require the measurement of these three parameters. Also, other parameters, such as the flow rate of a fluid, can be measured indirectly by measuring strain, pressure, or motion.

After completing this section, you should be able to


- Describe methods of measuring strain, pressure, and motion
 - Explain how a strain gage operates
 - Discuss strain gage circuits
 - Explain how pressure transducers work
 - Discuss pressure-measuring circuits
 - List several pressure transducer applications
 - Explain displacement transducers, velocity transducers, and acceleration transducers

The Strain Gage

Strain is the deformation, either expansion or compression, of a material due to a force acting on it. For example, a metal rod or bar will lengthen slightly when an appropriate force is applied as illustrated in Figure 15-29(a). Also, if a metal plate is bent, there is an expansion of the upper surface, called *tensile strain*, and a compression of the lower surface, called *compressive strain*, as shown in Figure 15-29(b).



 (a) Strain occurs as length changes from L to $L + \Delta L$ when force is applied.



(b) Strain occurs when the flat plate is bent, causing the upper surface to expand and the lower surface to contract.

FIGURE 15-29 Examples of strain.

Strain gages are based on the principle that the resistance of a material increases if its length increases and decreases if its length decreases. This is expressed by the following formula (which you should recall from your dc/ac circuits course).

$$R = \frac{\rho L}{A} \quad (15-3)$$

This formula states that the resistance of a material, such as a length of wire, depends directly on the resistivity (ρ) and the length (L) and inversely on the cross-sectional area (A).

A **strain gage** is basically a long, very thin strip of resistive material that is bonded to the surface of an object on which strain is to be measured, such as a wing or tail section of an airplane under test. When a force acts on the object to cause a slight elongation, the strain gage also lengthens proportionally and its resistance increases. Most strain gages are formed in a pattern similar to that in Figure 15–30(a) to achieve enough length for a sufficient resistance value in a smaller area. It is then placed along the line of strain as indicated in Figure 15–30(b).

 


FIGURE 15–30 A simple strain gage and its placement.

As shown in Figure 15–30, a strain gage is mounted along the line of force that causes the strain. Ideally, the resistance of the gage will only change as a result of strain, but in reality, materials under test also change in shape due to changes in temperature (thermal expansion). Strain gage manufacturers attempt to minimize sensitivity to temperature by processing the gage material to compensate for the thermal expansion of the specimen material for which the gage is intended. Compensated gages reduce thermal sensitivity, but they do not completely eliminate it.


 


FIGURE SN15–2 Using a dummy gage to compensate for temperature.

Another method of compensating for thermal expansion is to use a second *dummy gage*. The dummy gage is applied at right angles (transverse) to the line of strain, as illustrated in Figure SN15–2. This means that strain has little effect on the dummy gage. But since materials expand or contract in all directions due to changes in temperature, the resistance change of the dummy gage due to thermal expansion is the same as the active gage. This provides a reference value from which thermal expansion can be factored out.

 

SYSTEM NOTE

THE GAGE FACTOR OF A STRAIN GAGE An important characteristic of strain gages is the **gage factor (GF)**, which is defined as the ratio of the fractional change in resistance to the fractional change in length along the axis of the gage. For metallic

strain gages, the GF s are typically around 2. The concept of gage factor is illustrated in Figure 15-31 and expressed in Equation (15-4) where R is the nominal resistance and ΔR is the change in resistance due to strain. The fractional change in length ($\Delta L/L$) is designated strain (ϵ) and is usually expressed in parts per million, called *microstrain* (designated $\mu\epsilon$).

$$GF = \frac{\Delta R/R}{\Delta L/L} \quad (15-4)$$

 


FIGURE 15-31 Illustration of gage factor. The ohmmeter symbol is not intended to represent a practical method for measuring ΔR .

EXAMPLE 15-5

A certain material being measured under stress undergoes a strain of 5 parts per million ($5 \mu\epsilon$). The strain gage has a nominal (unstrained) resistance of 320Ω and a gage factor of 2.0. Determine the resistance change in the strain gage.

SOLUTION

$$GF = \frac{\Delta R/R}{\Delta L/L} = \frac{\Delta R/R}{\epsilon}$$

$$\Delta R = (GF)(R)(\epsilon) = 2.0(320 \Omega)(5 \times 10^{-6}) = \mathbf{3.2 \text{ m}\Omega}$$

PRACTICE EXERCISE

If the strain in this example is $8 \mu\epsilon$, how much does the resistance change?

Basic Strain Gage Circuits

Because a strain gage exhibits a resistance change when the quantity it is sensing changes, it is typically used in circuits similar to those used for RTDs. The basic difference is that strain instead of temperature is being measured. Therefore, strain gages are usually applied in bridge circuits or in constant-current-driven circuits, as shown in Figure 15-32. They can be used in applications in the same way as RTDs and thermistors. The 1B31 is an example of a strain gage signal conditioner. Its data sheet can be found at www.analog.com.

 


FIGURE 15-32 Basic strain-measuring circuits.

Pressure Transducers

Pressure transducers are devices that exhibit a change in resistance proportional to a change in pressure. Basically, pressure sensing is accomplished using a strain gage bonded to a flexible diaphragm as shown in Figure 15-33(a). Figure 15-33(b) shows the diaphragm with no net pressure exerted on it. When a net positive pressure exists on one side of the diaphragm, as shown in Figure 15-33(c), the diaphragm is pushed upward and its surface expands. This expansion causes the strain gage to lengthen and its resistance to increase.

 


FIGURE 15-33 A simplified pressure sensor constructed with a strain gage bonded to a flexible diaphragm.

Pressure transducers typically are manufactured using a foil strain gage bonded to a stainless steel diaphragm or by integrating semiconductor strain gages (resistors) in a silicon diaphragm. Either way, the basic principle remains the same.

Pressure transducers come in three basic configurations in terms of relative pressure measurement. The absolute pressure transducer measures applied pressure relative to a vacuum as illustrated in Figure 15-34(a). The gage pressure transducer measures applied pressure relative to the pressure of the surroundings (ambient pressure) as illustrated in Figure 15-34(b). The differential pressure transducer measures one applied pressure


 


FIGURE 15-34 Three basic types of pressure transducers.

relative to another applied pressure as shown in Figure 15-34(c). Some transducer configurations include circuitry such as bridge completion circuits and op-amps within the same package as the sensor itself, as indicated.

Pressure-Measuring Circuits

Because pressure transducers are devices in which the resistance changes with the quantity being measured, they are usually in a bridge configuration as shown by the basic op-amp bridge circuit in Figure 15-35(a). In some cases, the complete circuitry is built into the transducer package, and in other cases the circuitry is external to the sensor. The symbols in parts (b) through (d) of Figure 15-35 are sometimes used to represent the complete pressure transducer with an amplified output. The symbol in part (b) represents the absolute pressure transducer, the symbol in part (c) represents the gage pressure transducer, and the symbol in part (d) represents the differential pressure transducer.

 

(a) Basic bridge circuit

 


FIGURE 15-35 A basic pressure transducer circuit and symbols.

FLOW RATE MEASUREMENT One common method of measuring the flow rate of a fluid through a pipe is the differential-pressure method. A flow restriction device such as a Venturi section (or other type of restriction such as an orifice) is placed in the flow stream. The Venturi section is formed by a narrowing of the pipe, as indicated in Figure 15–36. Although the velocity of the fluid increases as it flows through the narrow channel, the volume of fluid per minute (volumetric flow rate) is constant throughout the pipe.

 


FIGURE 15–36 A basic method of flow rate measurement.

Because the velocity of the fluid increases as it goes through the restricted area, the pressure also increases. If pressure is measured at a wide point and at a narrow point, the flow rate can be determined because flow rate is proportional to the square root of the differential pressure, as shown in Figure 15–36.

PRESSURE TRANSDUCER APPLICATIONS Pressure transducers are used anywhere there is a need to determine the pressure of a substance. In medical systems, pressure transducers are used for blood pressure measurement; in aircraft, pressure transducers are used for altitude pressure, cabin pressure, and hydraulic pressure; in automobiles, pressure transducers are used for fuel flow, oil pressure, brake line pressure, manifold pressure, and steering system pressure, to name a few.

Motion-Measuring Circuits

DISPLACEMENT TRANSDUCERS *Displacement* is a quantity that indicates the change in position of a body or point. Angular displacement refers to a rotation that can be measured in degrees or radians. Displacement transducers can be either contacting or noncontacting.

Contacting transducers typically use a sensing shaft with a coupling device to follow the position of the measured quantity. A contacting type of displacement sensor that relates a change in inductance to displacement is the linear variable differential transformer (LVDT). The sensing shaft is connected to a moving magnetic core inside a specially wound transformer. A typical LVDT is shown in Figure 15–37. The primary of the transformer is in line and located between two identical secondaries. The primary winding is excited with ac (usually in the range of 1 to 5 kHz). When the core is centered, the voltage induced in each secondary is equal. As the core moves off center, the voltage in one secondary will be greater than the other. With the demodulator circuit shown, the polarity of the output changes as the core passes the center position. The transducer has excellent sensitivity, linearity, and repeatability.

 


FIGURE 15–37 LVDT displacement transducers.

Noncontacting displacement transducers include optical and capacitive transducers. Photocells can be arranged to observe light through holes in an encoding disk or to count fringes painted on the surface to be measured. Optical systems are fast; but noise, including

background light sources, can produce spurious signals in optical sensors. It is useful to build hysteresis into the system if noise is a problem (see Section 8-1).

Fiber-optic sensors make excellent proximity detectors for close ranges. Reflective sensors use two fiber bundles, one for transmitting light and the other for receiving light from a reflective surface, as illustrated in Figure 15-38. Light is transmitted in the fiber bundle without any significant attenuation. When it leaves the transmitting fiber bundle, it forms a spot on the target that is inversely proportional to the square of the distance. The receiving bundle is aimed at the spot and collects the reflected light to an optical sensor. The light intensity detected by the receiving bundle depends on the physical size and arrangement of the fibers as well as the distance to the spot and the reflecting surface, but the technique can respond to distances approaching 1 microinch. The major disadvantage is limited dynamic range.

Capacitive sensors can be made into very sensitive displacement and proximity transducers. The capacitance is varied by moving one of the plates of a capacitor with respect to the second plate. The moving plate can be any metallic surface such as the diaphragm of a capacitive microphone or a surface that is being measured. The capacitor can be used to control the frequency of a resonant circuit and thus convert the capacitive change into a usable electrical output. (Experiment 37 of the lab book shows an example.)

 


FIGURE 15-38 Fiber-optic proximity detector.

VELOCITY TRANSDUCERS *Velocity* is defined as the rate of change of displacement. It follows that velocity can be determined indirectly with a displacement sensor and measuring the time between two positions. A direct measurement of velocity is possible with certain transducers that have an output proportional to the velocity to be measured. These transducers can respond to either linear or angular velocity. Linear velocity transducers can be constructed using a permanent magnet inside a concentric coil, forming a simple motor by generating an emf proportional to the velocity. Either the coil or the magnet can be fixed and the other moved with respect to the fixed component. The output is taken from the coil.

There are a variety of transducers that are designed to measure angular velocity. Tachometers, a class of angular velocity transducers, provide a dc or ac voltage output. A dc tachometer is basically a small generator with a coil that rotates in a constant magnetic field. A voltage is induced in the coil as it rotates in the magnetic field. The average value of the induced voltage is proportional to the speed of rotation, and the polarity is indicative of the direction of rotation, an advantage with dc tachometers. AC tachometers can be designed as generators that provide an output frequency that is proportional to the rotational speed.

Another technique for measuring angular velocity is to rotate a shutter over a photo-sensitive element. The shutter interrupts a light source from reaching the photocells, causing the output of the photocells to vary at a rate proportional to the rotational speed.

ACCELERATION TRANSDUCERS Acceleration is usually measured by use of a spring-supported seismic mass, mounted in a suitable enclosure as shown in Figure 15-39.

 


FIGURE 15-39 A basic accelerometer. Motion is converted to a voltage by the variable resistor.

Damping is provided by a dashpot, which is a mechanical device to reduce the vibration. The relative motion between the case and the mass is proportional to the acceleration. A secondary transducer such as a resistive displacement transducer or an LVDT is used to convert the relative motion to an electrical output. Ideally, the mass does not move when the case accelerates because of its inertia; in practice, it does because of forces applied to it through the spring. The accelerometer has a natural frequency, the period of which should be shorter than the time required for the measured acceleration to change. Accelerometers used to measure vibration should also be used at frequencies less than the natural frequency.

An accelerometer that uses the basic principle of the LVDT can be constructed to measure vibration. The mass is made from a magnet that is surrounded with a coil. Voltage induced in the coil is a function of the acceleration.

Another type of accelerometer uses a piezoelectric crystal in contact with the seismic mass. The crystal generates an output voltage in response to forces induced by the acceleration of the mass. Piezoelectric crystals are small in size and have a natural frequency that is very high; they can be used to measure high-frequency vibration. The drawback to piezoelectric crystals is that the output is very low and the impedance of the crystal is high, making it subject to problems from noise.

SECTION 15–4 CHECKUP

1. Describe a basic strain gage.
2. Describe a basic pressure gage.
3. List three types of pressure gages.
4. (a) What is an LVDT?
(b) What does it measure?

15–5 POWER CONTROL

A useful application of electronic circuits is to control power to a load. In this section, you will learn about two devices that are widely used in power control applications—the SCR and the triac. These devices are members of a class of devices known as thyristors, which are widely used in industrial controls for motors, heaters, phase controls, and many other applications. A thyristor can be thought of as an electronic switch that can rapidly turn on or off a large current to a load. Integrated circuits are frequently used to determine the time to turn on or off the SCR or triac.

After completing this section, you should be able to

- Describe how power to a load is controlled
- Describe the SCR and triac
- Explain how to turn an SCR on or off
- Explain the term *zero-voltage switching*
- Define *microcontroller*

The Silicon-Controlled Rectifier

A **thyristor** is a semiconductor switch composed of four or more layers of alternating *pnpn* material. There are various types of thyristors; the type principally depends on the number of layers and the particular connections to the layers. When a connection is made to the first, second, and fourth layer of a four-layer thyristor, a form of gated diode known as a **silicon-controlled rectifier (SCR)** is formed. This is one of the most important devices in

the thyristor family because it acts like a diode that can be turned on when required. The basic structure and schematic symbol for an SCR is shown in Figure 15-40. For an SCR, the three connections are labeled the anode (A), cathode (K), and gate (G) as shown.

The characteristic curve for an SCR is shown in Figure 15-41(a) for a gate current of zero. There are a total of four regions of the characteristic curve of interest. The reverse characteristic (plotted in quadrant 3) is the same as a normal diode with regions called the reverse-blocking region and a reverse-avalanche region. The reverse-blocking region is equivalent to an open switch. The reverse voltage that must be applied to an SCR to drive it into the avalanche region is typically several hundred volts or more. SCRs are normally not operated in the reverse-avalanche region.



 


FIGURE 15-40 The silicon-controlled rectifier (SCR).

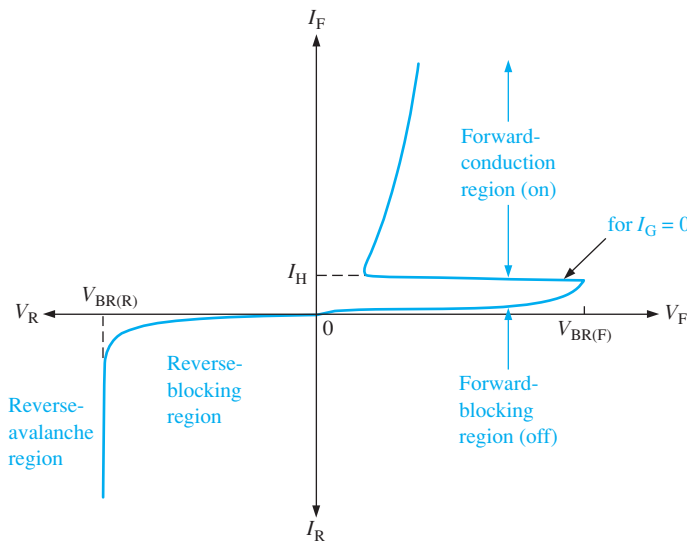

 (a) When $I_G = 0$, $V_{BR(F)}$ must be exceeded to move into the conduction region.



(b) I_G controls the value of $V_{BR(F)}$ required for turn on.

FIGURE 15-41 SCR characteristic curves.

The forward characteristic (plotted in quadrant 1) is divided into two regions. There is a forward-blocking region, where the SCR is basically off and the very high resistance between the anode and cathode can be approximated by an open switch. The second region is the forward-conduction region, where anode current occurs as in a normal diode. To move an SCR into this region, the forward-breakover voltage, $V_{BR(F)}$, must be exceeded. When an SCR is operated in the forward conduction region, it approximates a closed

switch between anode and cathode. Notice the similarity to a normal diode characteristic (see Figure 2–10) except for the forward-blocking region.

TURNING THE SCR ON There are two ways to move an SCR into the forward-conduction region. In both cases, the anode to cathode must be forward-biased; that is, the anode must be positive with respect to the cathode. The first method has already been mentioned and requires the application of forward voltage that exceeds the forward breakover voltage, $V_{BR(F)}$. Breakover voltage triggering is not normally used as a triggering method. The second method requires a positive pulse of current (trigger) on the gate. This pulse reduces the forward-breakover voltage, as shown in Figure 15–41(b) and the SCR conducts. The greater the gate current, the lower the value of $V_{BR(F)}$. This is the normal method for turning on an SCR.

Once the SCR is turned on, the gate loses control. In effect, the SCR is latched and will continue to approximate a closed switch as long as anode current is maintained. When the anode current drops below a value of current called the holding current, the SCR will drop out of conduction. The holding current is indicated in Figure 15–41.

TURNING THE SCR OFF There are two basic methods for turning off an SCR: anode current interruption and forced commutation. The anode current can be interrupted by opening the path in the anode circuit, causing the anode current to drop to zero and turning off the SCR. One common “automatic” method to interrupt the anode current is to connect the SCR in an ac circuit. The negative cycle of the ac waveform will turn off the SCR.

The forced commutation method requires momentarily forcing current through the SCR in the direction opposite to the forward conduction so that forward current is reduced below the holding value. This can be implemented by various circuits. Probably the simplest is to electronically switch a charged capacitor across the SCR in the reverse direction.

The Triac

The **triac** is a thyristor with the ability to pass current bidirectionally and is therefore an ac power control device. Although it is one device, its performance is equivalent to two SCRs connected in parallel in opposite directions but with a common gate terminal. The basic characteristic curves for a triac are illustrated in Figure 15–42. Because a triac is like two back-to-back SCRs, there is no reverse characteristic.

 


FIGURE 15–42 Triac characteristic curves.

As in the case of the SCR, gate triggering is the usual method for turning on a triac. Application of current to the triac gate initiates the latching mechanism discussed in the previous section. Once conduction has been initiated, the triac will conduct on with either polarity; hence it is useful as an ac controller. A triac can be triggered such that ac power is supplied to the load for a portion of the ac cycle. This enables the triac to provide more or less power to the load depending on the trigger point. This basic operation is illustrated with the circuit in Figure 15-43.

The Zero-Voltage Switch

One problem that arises with triggering an SCR or triac when it is switched on during the ac cycle is generation of RFI (radio frequency interference) due to switching transients. If the SCR or triac is suddenly switched on near the peak of the ac cycle, for example, there would be a sudden inrush of current to the load. When there is a sudden transition of voltage or current, many high-frequency components are generated. These high-frequency components can radiate into sensitive electronic circuits, creating serious disturbances, even catastrophic failures. By switching the SCR or triac on when the voltage across it is zero, the sudden increase in current is prevented because the current will increase sinusoidally with the ac voltage. **Zero-voltage switching** also prevents thermal shock to the load, which, depending on the type of load, may shorten its life.

Not all applications can use zero-voltage switching, but when it is possible, noise problems are greatly reduced. For example, the load might be a resistive heating element, and the power is typically turned on for several cycles of the ac and then turned off for several cycles to maintain a certain temperature. The zero-voltage switch uses a sensing circuit to determine when to turn power on. The idea of zero-voltage switching is illustrated in Figure 15-44.



 


FIGURE 15-43 Basic triac phase control. The timing of the gate trigger determines the portion of the ac cycle passed to the load.

 

 (a) Zero-voltage switching of load current



(b) Nonzero switching of load current produces current transients that cause RFI.

FIGURE 15-44 Comparison of zero-voltage switching to nonzero switching of power to a load.

A basic circuit that can provide a trigger as the ac waveform crosses the zero axis in the positive direction is shown in Figure 15–45. Resistor R_1 and diodes D_1 and D_2 protect the input of the comparator from excessive voltage swings. The output voltage level of the comparator is a square wave. C_1 and R_2 form a differentiating circuit to convert the square wave output to trigger pulses. Diode D_3 limits the output to positive triggers only.

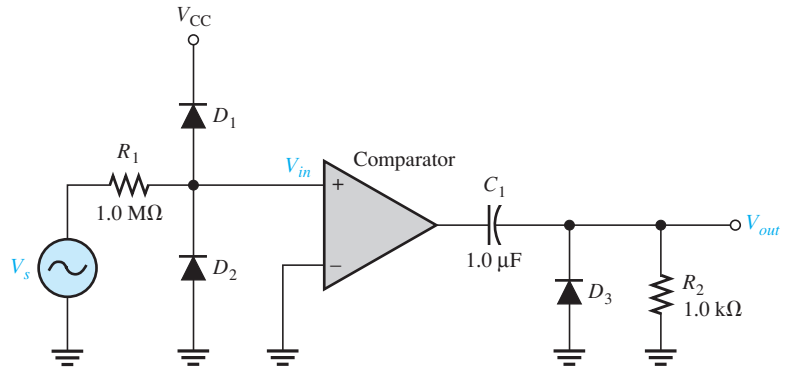


FIGURE 15–45 A circuit that can provide triggers when the ac waveform crosses the zero axis in the positive direction.

Microcontrollers

SCRs and triacs are often used in systems that have many additional requirements. For instance, a system as basic as a washing machine requires timing functions, speed or torque regulation, motor protection, sequence generation, display control, and so on. Systems like this can be controlled by a special class of computers called **microcontrollers**. A microcontroller is constructed as a single integrated circuit with all of the basic features found in a microprocessor, with special input/output (I/O) circuits, ADCs (analog-to-digital converters), counters, timers, oscillators, memory, and other features. Microcontrollers can be configured for a specific system and offer an inexpensive alternative to older methods for providing a trigger to an SCR or triac.

A specific microcontroller is the Texas Instruments MSP430. Its data sheet can be found at www.ti.com. The MSP430 is a low-cost 16-bit controller with a reduced instruction set (RISC). It can operate at high speed with extremely low power consumption. It can perform all of the control functions required in a small system and can be used to directly drive the gate of a small triac or SCR. It is possible to build a zero-crossing input for the MSP430. Essentially, the same input protection circuit shown in Figure 15–45 is connected to one of the input ports of the MSP430.

SECTION 15–5 CHECKUP

- How does an SCR differ from a triac in terms of delivering power to a load?
- Explain the basic purpose in zero-voltage switching.
- In what type of system would you expect to find an SCR or triac?

SUMMARY

- An rms-to-dc converter performs three basic functions: squaring, averaging, and taking the square root.
- Squaring is usually implemented with a linear multiplier.
- A simple averaging circuit is a low-pass filter that passes only the dc component of the input.

- A square root circuit utilizes a linear multiplier in the feedback loop of an op-amp.
- A synchro is a shaft angle transducer having three stator windings.
- A resolver is a type of synchro that, in its simplest form, has two stator windings.
- The output voltages of a synchro or resolver are called *format voltages* and are proportional to the shaft angle.
- A resolver-to-digital converter (RDC) converts resolver format voltages to a digital code that represents the angular position of the shaft.
- A thermocouple is a type of temperature transducer formed by the junction of two dissimilar metals.
- When the thermocouple junction is heated, a voltage is generated across the junction that is proportional to the temperature.
- Thermocouples can be used to measure very high temperatures.
- The resistance temperature detector (RTD) is a temperature transducer in which the resistance changes directly with temperature. It has a positive temperature coefficient.
- RTDs are typically used in bridge circuits or in constant-current circuits to measure temperature. They have a more limited temperature range than thermocouples.
- The thermistor is a temperature transducer in which the resistance changes with temperature. They can have either a positive or a negative temperature coefficient, but NTC thermistors are more common.
- Thermistors are more sensitive than RTDs or thermocouples, but their temperature range is limited.
- The strain gage is based on the fact that the resistance of a material increases when its length increases.
- The gage factor of a strain gage is the fractional change in resistance to the fractional change in length.
- Pressure transducers are constructed with strain gages bonded to a flexible diaphragm.
- An absolute pressure transducer measures pressure relative to a vacuum.
- A gage pressure transducer measures pressure relative to ambient pressure.
- A differential pressure transducer measures one pressure relative to another pressure.
- The flow rate of a liquid can be measured using a differential pressure gage.
- A zero-voltage switch generates pulses at the zero crossings of an ac voltage for triggering a thyristor used in power control.
- Motion-measuring circuits include LVDT displacement transducers, velocity transducers, and accelerometers.
- The SCR and triac are two types of thyristors used in power control circuits.

KEY TERMS

Key terms and other bold terms in the chapter are defined in the end-of-book glossary.

Resolver A type of synchro.

Resolver-to-digital converter (RDC) An electronic circuit that converts resolver voltages to a digital format that represents the angular position of the rotor shaft.

Root mean square (rms) The value of an ac voltage that corresponds to a dc voltage that produces the same heating effect in a resistance.

Resistance temperature detector (RTD) A type of temperature transducer in which resistance is directly proportional to temperature.

Transducer A device that converts a physical parameter into an electrical quantity.

Silicon-controlled rectifier (SCR) A type of three-terminal thyristor that conducts current when triggered on and remains on until the anode current falls below a specific value.

Strain gage A transducer formed by a resistive material in which a lengthening or shortening due to stress produces a proportional change in resistance.

Synchro An electromechanical transducer used for shaft angle measurement and control.

Synchro-to-digital converter (SDC) An electronic circuit that converts synchro voltages to a digital format that represents the angular position of the rotor shaft.

Thermistor A type of temperature transducer in which device resistance changes proportional to temperature. They can have either a positive temperature coefficient (PTC) or a negative temperature coefficient (NTC).

Thermocouple A type of temperature transducer formed by the junction of two dissimilar metals that produces a voltage proportional to temperature.

Thyristor A class of four-layer (*pnpn*) semiconductor devices.

Triac A three-terminal thyristor that can conduct current in either direction when properly activated.

Zero-voltage switching The process of switching power to a load at the zero crossings of an ac voltage to minimize RF noise generation.

KEY FORMULAS

$$(15-1) \quad V_{rms} = \sqrt{\text{avg}(V_{in}^2)} \quad \text{Root-mean-square value}$$

$$(15-2) \quad V_{OUT} = \sqrt{V_{in}^2} \quad \text{RMS-to-dc converter output}$$

$$(15-3) \quad R = \frac{\rho L}{A} \quad \text{Resistance of a material}$$

$$(15-4) \quad GF = \frac{\Delta R/R}{\Delta L/L} \quad \text{Gage factor of a strain gage}$$

SELF-TEST

Answers are at the end of the chapter.

- The rms value of an ac signal is equal to
 - the peak value
 - the dc value that produces the same heating effect
 - the square root of the average value
 - answers (b) and (c)
- An explicit type of rms-to-dc converter contains
 - a squaring circuit
 - an averaging circuit
 - a square root circuit
 - a squarer/divider circuit
 - all of the above
 - answers (a), (b), and (c) only
- A synchro produces
 - three format voltages
 - two format voltages
 - one format voltage
 - one reference voltage
- A resolver produces
 - three format voltages
 - two format voltages
 - one format voltage
 - none of these
- A Scott-T transformer is used for
 - coupling the reference voltage to a synchro or resolver
 - changing resolver format voltages to synchro format voltages
 - changing synchro format voltages to resolver format voltages
 - isolating the rotor winding from the stator windings
- The output of an RDC is a
 - sine wave with an amplitude proportional to the angular position of the resolver shaft
 - digital code representing the angular position of the stator housing
 - digital code representing the angular position of the resolver shaft
 - sine wave with a frequency proportional to the angular position of the resolver shaft
- A thermocouple
 - produces a change in resistance for a change in temperature
 - produces a change in voltage for a change in temperature
 - is made of two dissimilar metals
 - answers (b) and (c)

8. In a thermocouple circuit, where each of the thermocouple wires is connected to a copper circuit board terminal,
- (a) an unwanted thermocouple is produced
 - (b) compensation is required
 - (c) a reference thermocouple must be used
 - (d) answers (a), (b), and (c)
 - (e) answers (a) and (c)
9. A thermocouple signal conditioner is designed to provide
- (a) gain
 - (b) compensation
 - (c) isolation
 - (d) common-mode rejection
 - (e) all of the answers
10. An RTD
- (a) produces a change in resistance for a change in temperature
 - (b) has a negative temperature coefficient
 - (c) has a wider temperature range than a thermocouple
 - (d) all of these
11. The purpose of a 3-wire bridge is to eliminate
- (a) nonlinearity of an RTD
 - (b) the effects of wire resistance in an RTD circuit
 - (c) noise from the RTD resistance
 - (d) none of these
12. A thermistor has
- (a) less sensitivity than an RTD
 - (b) a greater temperature range than a thermocouple
 - (c) a logarithmic response to changes in temperature
 - (d) a more linear response than an RTD
13. Both RTDs and thermistors are used in
- (a) circuits that measure resistance
 - (b) circuits that measure temperature
 - (c) bridge circuits
 - (d) constant-current-driven circuits
 - (e) answers (b), (c), and (d)
 - (f) answers (b) and (c) only
14. When the length of a strain gage increases,
- (a) it produces more voltage
 - (b) its resistance increases
 - (c) its resistance decreases
 - (d) it produces an open circuit
15. A higher gage factor indicates that the strain gage is
- (a) less sensitive to a change in length
 - (b) more sensitive to a change in length
 - (c) has more total resistance
 - (d) made of a physically larger conductor
16. Many types of pressure transducers are made with
- (a) thermistors
 - (b) RTDs
 - (c) strain gages
 - (d) none of these
17. Gage pressure is measured relative to
- (a) ambient pressure
 - (b) a vacuum
 - (c) a reference pressure
18. The flow rate of a liquid can be measured with a(n)
- (a) string
 - (b) temperature sensor
 - (c) absolute pressure transducer
 - (d) differential pressure transducer
19. Zero-voltage switching is commonly used in
- (a) determining thermocouple voltage
 - (b) SCR and triac power control circuits
 - (c) in balanced bridge circuits
 - (d) RFI generation
20. A major disadvantage of nonzero switching of power to a load is
- (a) lack of efficiency
 - (b) possible damage to the thyristor
 - (c) RF noise generation

TROUBLESHOOTER'S QUIZ

Answers are at the end of the chapter.

Refer to Figure 15–46.

- If the 220 k Ω resistor opens,
 1. The closed-loop gain will
 - (a) increase (b) decrease (c) not change

Refer to Figure 15–47.

- If the bridge is balanced and the dc supply voltage is disconnected,
 2. The output voltage will
 - (a) increase (b) decrease (c) not change
- If the RTD opens,
 3. The magnitude of the voltage across the output terminals will
 - (a) increase (b) decrease (c) not change

Refer to Figure 15–49.

- If R_G is larger than specified,
 4. The amplifier output voltage will
 - (a) increase (b) decrease (c) not change
 5. The bridge output voltage will
 - (a) increase (b) decrease (c) not change

Refer to Figure 15–51.

- If the gate of the SCR opens and the input does not exceed the breakover voltage,
 6. The output voltage will
 - (a) increase (b) decrease (c) not change
- If R opens,
 7. The output voltage will
 - (a) increase (b) decrease (c) not change
- If the gate trigger voltage V_G increases in amplitude,
 8. The output voltage will
 - (a) increase (b) decrease (c) not change

Refer to Figure 15–52.

- If the input voltage increases in amplitude,
 9. The output voltage will
 - (a) increase (b) decrease (c) not change
- If D_3 is open,
 10. The amplitude of the positive triggers will
 - (a) increase (b) decrease (c) not change
- If D_3 is reversed,
 11. The amplitude of the positive triggers will
 - (a) increase (b) decrease (c) not change

PROBLEMS

Answers to odd-numbered problems are at the end of the book.

SECTION 15–1 RMS-to-DC Converters

1. A 5 V dc voltage is applied across a 1.0 k Ω resistor. To achieve the same power in the 1.0 k Ω resistor as produced by the dc voltage, what must be the rms value of a sinusoidal voltage?

- Based on the fundamental definition of rms, determine the rms value for a symmetrical square wave with an amplitude of ± 1 V.

SECTION 15-2 Angle Measurement

- A certain RDC has an 8-bit digital output. What is the angle that is being measured if the output code is 10000111?
- Repeat Problem 3 for an RDC output code of 00010101.
- How many bits does the latch hold in an AD2S90 RDC?
- Explain the Direction and Velocity outputs on an AD2S90 RDC.

SECTION 15-3 Temperature Measurement

- Three identical thermocouples are each exposed to a different temperature as follows: Thermocouple *A* is exposed to 450°C , thermocouple *B* is exposed to 420°C , and thermocouple *C* is exposed to 1200°C . Which thermocouple produces the most voltage?
- You have two thermocouples. One is a *K* type and the other is a *T* type. In general, what do these letter designations tell you?
- Determine the output voltage of the op-amp in Figure 15-46 if the thermocouple is measuring a temperature of 400°C and the circuit itself is at 25°C . Refer to Table 15-2.

 


FIGURE 15-46

- What should be the output voltage in Problem 9 if the circuit is properly compensated?
- At what resistance value of the RTD will the bridge circuit in Figure 15-47 be balanced if the wires running to the RTD each have a resistance of $10\ \Omega$?

 


FIGURE 15-47

- At what resistance value of the RTD will the bridge circuit in Figure 15-48 be balanced if the wires running to the RTD each have a resistance of $10\ \Omega$?

 


FIGURE 15-48

13. Explain the difference in the results of Problems 11 and 12.
14. Determine the output voltage of the instrumentation amplifier in Figure 15–49 if the resistance of the RTD is $697\ \Omega$ at the temperature being measured.

 


FIGURE 15–49

SECTION 15–4 Strain Measurement, Pressure Measurement, and Motion Measurement

15. A certain material being measured undergoes a strain of 3 parts per million. The strain gage has a nominal resistance of $600\ \Omega$ and a gage factor of 2.5. Determine the resistance change in the strain gage.
16. Explain how a strain gage can be used to measure pressure.
17. Identify and compare the three symbols in Figure 15–50.

 


FIGURE 15–50

SECTION 15–5 Power-Control

18. Name two ways an SCR can be placed in the forward-conduction region.
19. Sketch the V_R waveform for the circuit in Figure 15–51, given the indicated relationship of the input waveforms.
20. For the circuit in Figure 15–52, sketch the waveform at the output of the comparator and at the output of the circuit in relation to the input. Assume the input is a $115\ \text{V rms}$ sine wave and the comparator and the power supply voltages for the comparator are $\pm 10\ \text{V}$.
21. What change to the circuit in Figure 15–52 would you make if you wanted to have positive triggers on the negative slope of the input waveform?

 


FIGURE 15-51

 


FIGURE 15-52

ANSWERS TO SECTION CHECKUPS

SECTION 15-1

1. An rms-to-dc converter produces a dc output voltage that is equal to the rms value of the ac input voltage.
2. Internally, an rms-to-dc converter squares, averages, and takes the square root.

SECTION 15-2

1. Synchro
2. An RDC accepts resolver format voltages on its inputs.
3. An RDC produces a digital code representing the angular shaft position of the resolver.
4. An RDC converts the angular shaft position of a resolver into a digital code.

SECTION 15-3

1. A thermocouple is a temperature transducer formed by the junction of two dissimilar metals.
2. A voltage proportional to the temperature is produced across the junction of two dissimilar metals.
3. An RTD is a resistance temperature detector in which the resistance is proportional to the temperature, whereas the thermocouple produces a voltage.
4. An RTD has a positive temperature coefficient, and a thermistor can have either a positive or a negative temperature coefficient.
5. The thermocouple has a greater temperature range than the RTD or thermistor.
6. Coolant temperature, air temperature, and transmission fluid temperature measurements.

SECTION 15-4

1. Basically, a strain gage is a resistive element whose dimensions can be altered by an applied force to produce a change in resistance.
2. Basically, a pressure gage is a strain gage bonded to a flexible diaphragm.
3. Absolute, gage, and differential
4. (a) A linear variable differential transformer
(b) Displacement

SECTION 15-5

1. An SCR is unidirectional and therefore allows current through the load only during half of the ac cycle. A triac is bidirectional and allows current during the complete cycle.
2. Zero-voltage switching eliminates fast transitions in the current to a load, thus reducing RFI emissions and thermal shock to the load element.
3. In a system in which power is controlled.

ANSWERS TO PRACTICE EXERCISES FOR EXAMPLES

- 15-1 183°
 15-2 10.1%
 15-3 24.247 mV
 15-4 1.0 k Ω ; 0 V
 15-5 5.12 m Ω

ANSWERS TO SELF-TEST

- | | | | | |
|---------|---------|---------|---------|---------|
| 1. (b) | 2. (f) | 3. (a) | 4. (b) | 5. (c) |
| 6. (c) | 7. (d) | 8. (d) | 9. (e) | 10. (a) |
| 11. (b) | 12. (c) | 13. (e) | 14. (b) | 15. (b) |
| 16. (c) | 17. (a) | 18. (d) | 19. (b) | 20. (c) |

ANSWERS TO TROUBLESHOOTER'S QUIZ

- | | | | |
|---------------|----------------|--------------|---------------|
| 1. increase | 2. not change | 3. increase | 4. decrease |
| 5. not change | 6. decrease | 7. decrease | 8. not change |
| 9. not change | 10. not change | 11. decrease | |

APPENDIX

Derivations of Selected Equations

Equation (3–9)

The Shockley equation for the base-emitter pn junction is

$$I_E = I_R(e^{VQ/kT} - 1)$$

where I_E = the total forward current across the base-emitter junction

I_R = the reverse saturation current

V = the voltage across the depletion region

Q = the charge on an electron

k = a number known as Boltzmann's constant

T = the absolute temperature

At ambient temperature, $Q/kT \cong 40$, so

$$I_E = I_R(e^{40V} - 1)$$

Differentiating,

$$\frac{dI_E}{dV} = 40I_R e^{40V}$$

Since $I_R e^{40V} = I_E + I_R$,

$$\frac{dI_E}{dV} = 40(I_E + I_R)$$

Assuming $I_R \ll I_E$,

$$\frac{dI_E}{dV} \cong 40I_E$$

The ac resistance r'_e of the base-emitter junction can be expressed as dV/dI_E .

$$r'_e = \frac{dV}{dI_E} \cong \frac{1}{40I_E} \cong \frac{25 \text{ mV}}{I_E}$$

Equation (4–10)

The gain of a CD amplifier is

$$A_v = \frac{R_s}{r'_s} + R_s$$

Substituting $1/g_m$ for r'_s gives

$$A_v = \frac{R_s}{\frac{1}{g_m} + R_s} = \frac{g_m R_s}{1 + g_m R_s}$$

Equation (7–4)

The formula for open-loop gain in Equation (7–2) can be expressed in complex notation as

$$A_{ol} = \frac{A_{ol(mid)}}{1 + jf/f_{c(ol)}}$$

Substituting the above expression into the equation $A_{cl} = A_{ol}/(1 + BA_{ol})$, we get a formula for the total closed-loop gain.

$$A_{cl} = \frac{A_{ol(mid)}/(1 + jf/f_{c(ol)})}{1 + BA_{ol(mid)}/(1 + jf/f_{c(ol)})}$$

Multiplying the numerator and denominator by $1 + jf/f_{c(ol)}$ yields

$$A_{cl} = \frac{A_{ol(mid)}}{1 + BA_{ol(mid)} + jf/f_{c(ol)}}$$

Dividing the numerator and denominator by $1 + BA_{ol(mid)}$ gives

$$A_{cl} = \frac{A_{ol(mid)}/(1 + BA_{ol(mid)})}{1 + j[f/(f_{c(ol)}(1 + BA_{ol(mid)}))]}$$

The above expression is of the form of the first equation

$$A_{cl} = \frac{A_{cl(mid)}}{1 + jf/f_{c(cl)}}$$

where $f_{c(cl)}$ is the closed-loop critical frequency. Thus,

$$f_{c(cl)} = f_{c(ol)}(1 + BA_{ol(mid)})$$

Equation (9–7)

The center frequency equation is

$$f_0 = \frac{1}{2\pi\sqrt{(R_1 \parallel R_3)R_2C_1C_2}}$$

Substituting C for C_1 and C_2 and rewriting $R_1 \parallel R_3$ as the product-over-sum produces

$$f_0 = \frac{1}{2\pi C \sqrt{\left(\frac{R_1 R_3}{R_1 + R_3}\right) R_2}}$$

Rearranging,

$$f_0 = \frac{1}{2\pi C} \sqrt{\left(\frac{R_1 + R_3}{R_1 R_2 R_3}\right)}$$

Equation (10–1)

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{R(-jX)/(R-jX)}{(R-jX) + R(-jX)/(R-jX)} \\ &= \frac{R(-jX)}{(R-jX)^2 - jRX} \end{aligned}$$

Multiplying the numerator and denominator by j ,

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{RX}{j(R - jX)^2 + RX} \\ &= \frac{RX}{RX + j(R^2 - j2RX - X^2)} \\ &= \frac{RX}{RX + jR^2 + 2RX - jX^2} \\ \frac{V_{out}}{V_{in}} &= \frac{RX}{3RX + j(R^2 - X^2)}\end{aligned}$$

For a 0° phase angle there can be no j term. Recall from complex numbers in ac theory that a *nonzero* angle is associated with a complex number having a j term. Therefore, at f_r the j term is 0.

$$R^2 - X^2 = 0$$

Thus,

$$\frac{V_{out}}{V_{in}} = \frac{RX}{3RX}$$

Cancelling,

$$\frac{V_{out}}{V_{in}} = \frac{1}{3}$$

Equation (10-2)

From the derivation of Equation (10-1),

$$\begin{aligned}R^2 - X^2 &= 0 \\ R^2 &= X^2 \\ R &= X\end{aligned}$$

Since $X = \frac{1}{2\pi f_r C}$,

$$\begin{aligned}R &= \frac{1}{2\pi f_r C} \\ f_r &= \frac{1}{2\pi RC}\end{aligned}$$

Equations (10-3) and (10-4)

The feedback network in the phase-shift oscillator consists of three RC stages, as shown in Figure A-1. An expression for the attenuation is derived using the mesh analysis method for the loop assignment shown. All R s are equal in value, and all C s are equal in value.

 


FIGURE A-1

$$\begin{aligned}(R - j1/2\pi fC)I_1 - RI_2 + 0I_3 &= V_{in} \\ -RI_1 + (2R - j1/2\pi fC)I_2 - RI_3 &= 0 \\ 0I_1 - RI_2 + (2R - j1/2\pi fC)I_3 &= 0\end{aligned}$$

In order to get V_{out} , we must solve for I_3 using determinants:

$$\begin{aligned}I_3 &= \frac{\begin{vmatrix} (R - j1/2\pi fC) & -R & V_{in} \\ -R & (2R - j1/2\pi fC) & 0 \\ 0 & -R & 0 \end{vmatrix}}{\begin{vmatrix} (R - j1/2\pi fC) & -R & 0 \\ -R & (2R - j1/2\pi fC) & -R \\ 0 & -R & (2R - j1/2\pi fC) \end{vmatrix}} \\ I_3 &= \frac{R^2 V_{in}}{(R - j1/2\pi fC)(2R - j1/2\pi fC)^2 - R^2(2R - j1/2\pi fC) - R^2(R - j1/2\pi fC)} \\ \frac{V_{out}}{V_{in}} &= \frac{RI_3}{V_{in}} \\ &= \frac{R^3}{(R - j1/2\pi fC)(2R - j1/2\pi fC)^2 - R^3(2 - j1/2\pi fRC) - R^3(1 - j1/2\pi fRC)} \\ &= \frac{R^3}{R^3(1 - j1/2\pi fRC)(2 - j1/2\pi fRC)^2 - R^3[(2 - j1/2\pi fRC) - (1 - j1/2\pi fRC)]} \\ &= \frac{R^3}{R^3(1 - j1/2\pi fRC)(2 - j1/2\pi fRC)^2 - R^3(3 - j1/2\pi fRC)} \\ &= \frac{1}{(1 - j1/2\pi fRC)(2 - j1/2\pi fRC)^2 - (3 - j1/2\pi fRC)}\end{aligned}$$

Expanding and combining the real terms and the j terms separately,

$$\frac{V_{out}}{V_{in}} = \frac{1}{\left(1 - \frac{5}{4\pi^2 f_r^2 R^2 C^2}\right) - j\left(\frac{6}{2\pi fRC} - \frac{1}{(2\pi f)^3 R^3 C^3}\right)}$$

For oscillation in the phase-shift amplifier, the phase shift through the RC network must equal 180° . For this condition to exist, the j term must be 0 at the frequency of oscillation f_r .

$$\begin{aligned}\frac{6}{2\pi f_r RC} - \frac{1}{(2\pi f_r)^3 R^3 C^3} &= 0 \\ \frac{6(2\pi)^2 f_r^2 R^2 C^2 - 1}{(2\pi)^3 f_r^3 R^3 C^3} &= 0 \\ 6(2\pi)^2 f_r^2 R^2 C^2 - 1 &= 0 \\ f_r^2 &= \frac{1}{6(2\pi)^2 R^2 C^2} \\ f_r &= \frac{1}{2\pi\sqrt{6}RC}\end{aligned}$$

Since the j term is 0,

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{1}{1 - \frac{5}{4\pi^2 f_r^2 R^2 C^2}} = \frac{1}{1 - \frac{5}{\left(\frac{1}{\sqrt{6}RC}\right)^2 R^2 C^2}} \\ &= \frac{1}{1 - 30} = -\frac{1}{29}\end{aligned}$$

The negative sign results from the 180° inversion. Thus, the value of attenuation for the feedback network is

$$B = \frac{1}{29}$$

Equation (12-1)

The output voltage of the upper op-amp is called V_{out1} and the output voltage of the lower op-amp is called V_{out2} . The difference in these two voltages sets up a current in the two feedback resistors, R , and R_G , given by Ohm's law.

$$i = \frac{V_{out1} - V_{out2}}{2R + R_G}$$

Because of negative feedback, ideally, the input voltage is across R_G (no voltage drop across the op-amp inputs). Applying Ohm's law again,

$$i = \frac{V_{in1} - V_{in2}}{R_G}$$

The current in the feedback resistors (R) and the gain resistor (R_G) are the same, since the op-amp inputs (ideally) draw no current. Equating the currents,

$$\frac{V_{out1} - V_{out2}}{R_G + 2R} = \frac{V_{in1} - V_{in2}}{R_G}$$

The third op-amp is set up as a unity-gain differential amplifier. Its output is

$$V_{out} = -(V_{out1} - V_{out2})$$

Substituting this result into the previous equation,

$$\frac{-V_{out}}{R_G + 2R} = \frac{V_{in1} - V_{in2}}{R_G}$$

Rearranging, changing signs, and simplifying,

$$V_{out} = \left(1 + \frac{2R}{R_G}\right)(V_{in2} - V_{in1})$$


This page intentionally left blank

ANSWERS TO ODD-NUMBERED PROBLEMS

Chapter 1


1. $45.4 \mu\text{S}$
3. Answers vary depending on the triangle used. For a 100-mV change, the resistance used is $\frac{\Delta V}{\Delta I} = \frac{0.75 - 0.65 \text{ V}}{8 - 3.2 \text{ mA}} \approx 21 \Omega$
5. (a) $V_p = 100 \text{ V}$, $V_{\text{avg}} = 63.7 \text{ V}$, $\omega = 200 \text{ rad/s}$
(b) 79.6 V
7. 37 kHz
9. 1.11
11. Odd harmonics
13. Voltage across $1.0 \text{ k}\Omega$ load = 1.65 V ;
Voltage across $2.7 \text{ k}\Omega$ load = 3.25 V ;
Voltage across $3.6 \text{ k}\Omega$ load = 3.79 V

FIGURE ANS-1

 

15. See Figure ANS-1.

FIGURE ANS-2

 

17. See Figure ANS-2.
19. 4.0 V
21. 51 dB
23. -60 dB
25. (a) -10 dB (b) 10 V
27. The supply is common to both channels, so it is not the problem. Start by reversing the channels at the input of the amplifier. If Channel 2 is still bad, the problem is most likely the amplifier or the Ch-2 speaker. Speakers can be tested by reversing them.
If the problem changes channels when the first test is done, the problem is before the amplifier inputs and could be the A_2 microphone or a problem in wiring, including the


battery lead at the microphone. Test by changing SW to the B microphones. If this corrects the problem, check the A_2 microphone; otherwise look for continuity to the switch and check the switch itself.

29. Use a static-safe wrist strap (and static-free work station, if possible).

Chapter 2

1. See Figure ANS-3.

FIGURE ANS-3

 

3. (a) Full-wave rectifier
(b) 28.3 V (total)
(c) 14.1 V (reference is center tap)
(d) See Figure ANS-4 (offset approximation).
(e) 13.4 mA (offset approximation)
(f) 28.3 V (ideal approximation)

 


FIGURE ANS-4

5. $V_p = 50 \text{ V}/0.637 = 78.5 \text{ V}$; $\text{PIV} = 78.5 \text{ V}$
7. $60 \mu\text{V}$
9. 11.94 V
11. 9.06 V
13. See Figure ANS-5.

 


FIGURE ANS-5

15. See Figure ANS-6.

 


FIGURE ANS-6

- 17. 2.6%
- 19. 2.0 V. Note: since the plot is logarithmic, 25 pF is 70% of the linear distance between 20 pF and 30 pF.
- 21. 2.0 V
- 23. Dark current
- 25. $V_{RRM} = 400$ V
- 27. DMM1 is correct but DMM2 is reading the rectified average voltage rather than the peak voltage that it would show if the capacitor was in the circuit. DMM3, indicating no voltage, implies an open circuit between the bridge and the output. The most likely cause is an open path along the output line between the bridge and the filter capacitor.
- 29. (a) Readings are correct.
 (b) Open zener diode
 (c) Open switch or fuse blown
 (d) Open capacitor
 (e) Open transformer winding (less likely: more than one diode open)
- 31. See Figure ANS-7. The output voltages are $V_{OUT1} = 6.8$ V and $V_{OUT2} = 24$ V.
- 33. A turns ratio of $N_{pri}:N_{sec} = 5:1$ is a reasonable choice based on the 24 V output.
- 35. D_2 is open.
- 37. C_1 is shorted.

 


FIGURE ANS-7

Chapter 3

- 1. 5.29 mA
- 3. 29.4 mA
- 5. $I_B = 0.276$ mA; $I_C = 20.7$ mA; $V_C = 15.1$ V
- 7. $I_B = 13.6$ μA; $I_C = 3.4$ mA; $V_C = 6.6$ V
- 9. $I_C = 3.67$ mA (saturation current); $V_{CE} = 0.1$ V
- 11. (a) decrease (to zero) (b) remain the same
 (c) increase (d) increase (e) increase
- 13. $I_C \cong I_E = 0.92$ mA; $V_{CE} = 8.34$ V
- 15. $I_{C(sat)} = 5.52$ mA; $V_{CE(cutoff)} = 15$ V
- 17. $P = (36.2$ mA)(9.23 V) = 334 mW
- 19. (a) $I_C = 36.2$ mA; $V_{CE} = 7.1$ V
 (b) $P_{RC} = 432$ mW
 (c) $P_D = 256$ mW
- 21. $V_B = 2.64$ V; $V_E = 1.94$ V; $V_C = 10.0$ V
- 23. $A_{v(max)} = 123$; $A_{v(min)} = 2.9$
- 25. $R_{in(tot)} = 5.44$ kΩ; $A_i = 5.44$
- 27. $I_{c(sat)(ac)} = 32.1$ mA; $V_{ce(cutoff)(ac)} = 13.0$ V
- 29. Low input resistance
- 31. 45 Ω
- 33. $I_{C(sat)(Q1)} = 1.19$ mA; $I_{C(sat)(Q2)} \cong 10$ mA
- 35. See Figure ANS-8.

 


FIGURE ANS-8

- 37. With the positive probe on the emitter and negative probe on the base, the reading is an open (or extremely high resistance). With the leads reversed, the reading is much lower.

- 39. (a) 27.8 (b) 109
- 41. C_1 is open.
- 43. R_1 is shorted
- 45. The collector terminal is open.

Chapter 4

- 1. JFETs
- 3. (a) Depletion region widens (creating a narrower channel)
 - (b) Increase
 - (c) Less
- 5. +5.0 V
- 7. (a) 10 mA (b) 4 GΩ (c) R_{IN} drops
- 9. (a) Approximately +4 V
 - (b) Approximately 2.5 mA
 - (c) Approximately +15.8 V
- 11. (a) +2.1 V (b) 2.1 mA (c) +5.97 V
- 13. (a) $V_{DS} = +6.3$ V; $V_{GS} = -1.0$ V
 - (b) $V_{DS} = +7.29$ V; $V_{GS} = -0.3$ V
 - (c) $V_{DS} = -1.65$ V; $V_{GS} = +2.35$ V

- 25. $A_v = -21.9$
- 27. $A_{v(min)} = 0.64$; $A_{v(max)} = 0.9$
- 29. Q_1 or Q_2 open, R_E open, no negative supply voltage, open path between transistors
- 31. 0.953 mA
- 33. (a) $I_D = 4.85$ mA; $V_{DS} = 9.3$ V (b) $A_v = -3.5$
- 35. It is a resistance that appears to be in series with the signal and indicates how much the FET departs from ideal.
- 37. 37. In a CMOS switch the transistors are in series and one of them is always off. This means the switch draws almost no current from the supply, except for the brief moments when it is changing states.
- 39. R_L is shorted
- 41. Q_2 gate terminal is open
- 43. D_1 is shorted

Chapter 5

- 1. $A_{v(overall)} = 38.4$; $R_{in} \cong 1.0$ MΩ; $R_{out} = 2.7$ kΩ
- 3. $A_{v(overall)} = 812$; $A'_{v(overall)} = 58.2$ dB
- 5. (a) See Figure ANS-10.
 - (b) $A_{v(overall)} = 6000$
 - (c) $A_{v(overall)} = 3600$

 


FIGURE ANS-10

- 15. $I_D = 0.514$ mA; $V_D = +6.86$ V
- 17. The gate is separated from the channel by a silicon-dioxide insulating layer.
- 19. +3 V
- 21. (a) Since $V_{GS} > V_{GS(th)}$, the device is on.
 - (b) Since $V_{GS} < V_{GS(th)}$, the device is off.
- 23. See Figure ANS-9.

- 7. Since it increases the input resistance of stage 2, gain will be larger.
- 9. To prevent reflections from affecting the signal
- 11. An increase in the input signal will cause it to move over a larger portion of the load line. At the upper end, the transconductance is higher, thus the gain is higher. At the lower end, the opposite is true. The overall effect is increased distortion.
- 13. 10 kΩ
- 15. See Figure ANS-11.

FIGURE ANS-9


 
 


FIGURE ANS-11

 17. $Q = 79$; $A_{v(NL)} = 415$; $BW = 5.75$ kHz
 19. (a) $I_{C(Q2)} = 5.3$ mA; $V_{B(Q3)} = +0.7$ V; $I_{C(Q3)} = 120$ mA;
 $V_{E(Q3)} = 0$ V
 (b) 0.25 W
 21. See Figure ANS-12.



23. (a) None
 (b) Gain increases to 101
 (c) No noticeable effect
 25. (a) $I_{CQ} = 68.4$ mA; $V_{CEQ} = 5.14$ V.
 (b) $A_v = 11.7$; $A_p = 263$
 27. The changes are shown in Figure ANS-13. The advantage of this arrangement is that the load resistor is referenced to ground.

 


FIGURE ANS-13

29. (a) $V_{B(Q1)} = +0.7$ V; $V_{B(Q2)} = -0.7$ V; $V_E = 0$ V;
 $I_{CQ} = 8.3$ mA; $V_{CEQ(Q1)} = +9$ V; $V_{CEQ(Q2)} = -9$ V
 (b) 0.5 W
 31. (a) $V_{B(Q1)} = +8.2$ V; $V_{B(Q2)} = +6.8$ V; $V_E = 7.5$ V;
 $I_{CQ} = 6.8$ mA; $V_{CEQ(Q1)} = +7.5$ V; $V_{CEQ(Q2)} = -7.5$ V
 (b) $P_L = 167$ mW
 33. (a) C_2 open or Q_2 open
 (b) power supply off, open R_1 , Q_1 base shorted to ground
 (c) Q_1 has collector-to-emitter short
 (d) one or both diodes shorted
 35. $C = 1.76$ nF added in series
 37. 2 W
 39. R_2 is open
 41. R_F is shorted

43. D_1 is shorted
 45. C_4 is open

Chapter 6

1. *Practical op-amp*: High open-loop gain, high input impedance, low output impedance, large bandwidth, high CMRR. *Ideal op-amp*: Infinite open-loop gain, infinite input impedance, zero output impedance, infinite bandwidth, infinite CMRR.
3. (a) Single-ended input; differential output
 (b) Single-ended input; single-ended output
 (c) Differential input; single-ended output
 (d) Differential input; differential output
5. V1: differential output voltage
 V2: noninverting input voltage
 V3: single-ended output voltage
 V4: differential input voltage
 A1: bias current
7. 8.1 μ A
9. 107.96 dB
11. 0.3
13. 40 μ s
15. $V_f = 49.5$ mV, $B = 0.0099$
17. (a) 11 (b) 101 (c) 47.81 (d) 23
19. (a) 1.0 (b) -1.0 (c) 22.3 (d) -10
21. (a) 0.45 mA (b) 0.45 mA
 (c) -10 V (d) -10
23. (a) $Z_{in(VF)} = 1.32 \times 10^{12} \Omega$; $Z_{out(VF)} = 0.455$ m Ω
 (b) $Z_{in(VF)} = 5 \times 10^{11} \Omega$; $Z_{out(VF)} = 0.6$ m Ω
 (c) $Z_{in(VF)} = 40,000$ M Ω ; $Z_{out(VF)} = 1.5$ m Ω
25. (a) R_1 open or op-amp faulty (b) R_2 open
27. The closed-loop gain will become a fixed -100.
29. R_E is shorted
31. R_i is shorted
33. R_L is shorted

Chapter 7

1. 70 dB
3. 1.67 k Ω
5. (a) 79,603 (b) 56,569 (c) 7960 (d) 80
7. (a) -0.67° (b) -2.69° (c) -5.71°
 (d) -45° (e) -71.22° (f) -84.29°
9. (a) 0 dB/decade (b) -20 dB/decade
 (c) -40 dB/decade (d) -60 dB/decade
11. (a) 29.8 dB; closed-loop
 (b) 23.9 dB; closed-loop
 (c) 0 dB; closed-loop
13. 21.14 MHz
15. Circuit (b) has smaller BW (97.5 kHz).
17. (a) 150° (b) 120° (c) 60° (d) 0° (e) -30°

19. (a) Unstable (b) Stable (c) Marginally stable
21. 25 Hz

Chapter 8

1. 24 V, with distortion
3. $V_{UTP} = +2.77$ V; $V_{LTP} = -2.77$ V
5. See Figure ANS-14.

 


FIGURE ANS-14

7. +8.57 V and -0.968 V
9. (a) -2.5 V (b) -3.52 V
11. 110 k Ω
13. $V_{OUT} = -3.57$ V; $I_f = -357$ μ A
15. -4.46 mV/ μ s
17. 1 mA
19. See Figure ANS-15.


 


FIGURE ANS-15

21. See Figure ANS-16.

FIGURE ANS-16

 

23. The output is not correct because the output should also be high when the input goes below +2 V. Possible faults:

Op-amp A2 bad, diode D_2 open, noninverting (+) input of op-amp A2 not properly set at +2 V, or V_{in} is not reaching inverting input.

25. Output is not correct. R_2 is open.
27. R_2 is open
29. R_1 is shorted
31. D_1 is open
33. R_f is open

Chapter 9

1. (a) Band pass (b) High pass
(c) Low pass (d) Band stop
3. 48.2 kHz; No
5. 700 Hz, 5.05
7. (a) 1, not Butterworth
(b) 1.44, approximate Butterworth
(c) 1st stage: 1.67
2nd stage: 1.67
Not Butterworth
9. (a) Chebyshev (b) Butterworth
(c) Bessel (d) Butterworth
11. 190 Hz
13. Add another identical stage and change the ratio of the feedback resistors to 0.068 for first stage, 0.586 for second stage, and 1.482 for third stage.
15. Exchange positions of resistors and capacitors in the filter network.
17. (a) Decrease R_1 and R_2 or C_1 and C_2 .
(b) Increase R_3 or decrease R_4 .
19. (a) $f_0 = 4.95$ kHz, $BW = 3.84$ kHz
(b) $f_0 = 449$ Hz, $BW = 96.5$ Hz
(c) $f_0 = 15.9$ kHz, $BW = 838$ Hz
21. Sum the low-pass and high-pass outputs with a two-input adder.
23. C_1 is open
25. R_1 is shorted
27. R_{A2} is shorted
29. R_6 is open

Chapter 10

1. An oscillator requires no input (other than dc power).
3. $1/75$
5. 733 mV
7. 50 k Ω
9. 2.34 k Ω
11. 136 k Ω ; 691 Hz
13. $A_v = 10$
15. Change R_1 to 3.54 k Ω
17. $R_4 = 65.8$ k Ω , $R_5 = 47$ k Ω
19. 3.33 V; 6.67 V
21. 0.0076 μ F

- 23. 13.6 ms
- 25. $0.01 \mu\text{F}$; $9.1 \text{ k}\Omega$
- 27. D_1 is shorted
- 29. R_2 is open

Chapter 11

- 1. 0.033%
- 3. 1.01%
- 5. See Figure ANS-17.

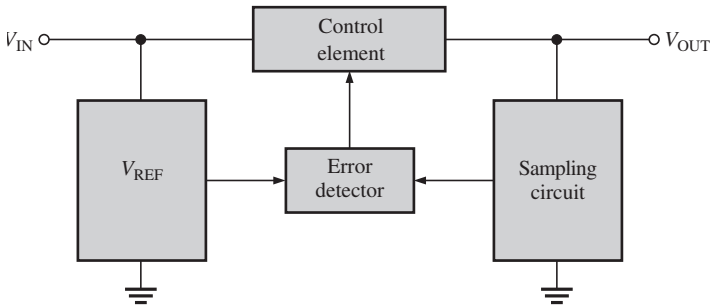


FIGURE ANS-17

- 7. 8.5 V
- 9. 9.57 V
- 11. 500 mA
- 13. 10 mA
- 15. $I_{L(\text{max})} = 250 \text{ mA}$, $P_{R1} = 6.25 \text{ W}$
- 17. 40%
- 19. Decreases
- 21. 14.25 V
- 23. 1.3 mA
- 25. 2.8Ω
- 27. $R_{\text{lim}} = 0.35 \Omega$
- 29. See Figure ANS-18.

 


FIGURE ANS-18

- 31. D_1 is open.
- 33. R_1 is shorted
- 35. R_1 is open

Chapter 12

- 1. $A_{v(1)} = A_{v(2)} = 101$
- 3. 1.005 V
- 5. 51.5
- 7. Change R_G to $2.2 \text{ k}\Omega$
- 9. 300
- 11. Change the $18 \text{ k}\Omega$ resistor to $68 \text{ k}\Omega$.
- 13. Connect output (pin 15) directly to pin 14, and connect pin 6 directly to pin 10 to make $R_F = 0$.

- 15. $500 \mu\text{A}$, 5 V
- 17. $A_v \cong 11.2$
- 19. See Figure ANS-19.

 


FIGURE ANS-19

- 21. See Figure ANS-20.

 


FIGURE ANS-20

- 23. (a) -0.301 (b) 0.301 (c) 1.699 (d) 2.114
- 25. The output of a log amplifier is limited to 0.7 V because of the transistor's pn junction.
- 27. -157 mV
- 29. $V_{out(max)} = -147\text{ mV}$, $V_{out(min)} = -89.2\text{ mV}$; the 1 V input peak is reduced 85% , whereas the 100 mV input peak is reduced only 10% .
- 31. R_1 is open.
- 33. R_G is open.

Chapter 13

- 1. See Figure ANS-21.

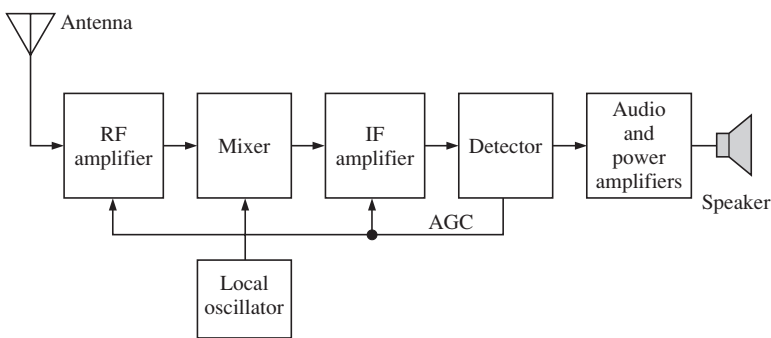


FIGURE ANS-21

- 3. 1135 kHz
- 5. RF: 91.2 MHz , IF: 10.7 MHz
- 7. (a) -4.65 V (b) 5.52 V (c) -1.61 V (d) 2.74 V
- 9. (a) -698 mV (b) 4.24 V
(c) -1.77 V (d) 340 mV
- 11. $f_{diff} = 8\text{ kHz}$, $f_{sum} = 10\text{ kHz}$
- 13. $f_{diff} = 1.7\text{ MHz}$, $f_{sum} = 1.9\text{ MHz}$, $f_1 = 1.8\text{ MHz}$
- 15. $f_c = 850\text{ kHz}$, $f_m = 3\text{ kHz}$
- 17. $V_{out} = 15\text{ mV} \cos[(1100\text{ kHz})2\pi t]$
 $- 15\text{ mV} \cos[(5500\text{ kHz})2\pi t]$
- 19. See Figure ANS-22.


 


FIGURE ANS-22

- 21. See Figure ANS-23.

FIGURE ANS-23

 

- 23. The IF amplifier has a 450 kHz – 460 kHz passband. The audio/power amplifiers have a 10 Hz – 5 kHz pass-band.
- 25. The modulating input signal is applied to the control terminal of the VCO. As the input signal amplitude varies, the output frequency of the VCO will vary proportionally.
- 27. The audio signal varies the voltage to an internal varactor, which changes the frequency of the VCO.
- 29. (a) 10 MHz
(b) 48.3 mV
- 31. 1005 Hz
- 33. 11.8°

Chapter 14

- 1. See Figure ANS-24.
- 3. See Figure ANS-25.
- 5. (a) 1 (b) 3


 
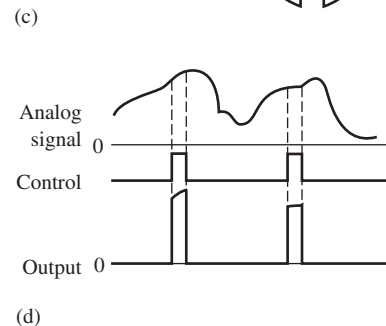


FIGURE ANS-24

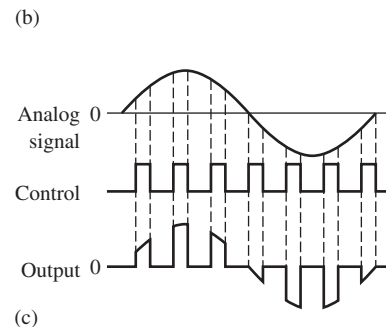


 


FIGURE ANS-25

7. See Figure ANS-26.

FIGURE ANS-26

 

9. 5 kΩ, 2.5 kΩ, 1.25 kΩ

11.

D_3	D_2	D_1	D_0	V_{OUT}
0	0	0	0	0 V
0	0	1	1	$-0.50 \text{ V} + (-0.25 \text{ V}) = -0.75 \text{ V}$
1	0	0	0	-2.00 V
1	1	1	1	$-2.00 \text{ V} + (-1.00 \text{ V}) + (-0.50 \text{ V}) + (-0.25 \text{ V}) = -3.75 \text{ V}$
1	1	1	0	$-2.00 \text{ V} + (-1.00 \text{ V}) + (-0.50 \text{ V}) = -3.50 \text{ V}$
0	1	0	0	-1.00 V
0	0	0	0	0 V
0	0	0	1	-0.25 V
1	0	1	1	$-2.00 \text{ V} + (-0.50 \text{ V}) + (-0.25 \text{ V}) = -2.75 \text{ V}$
1	1	1	0	$-2.00 \text{ V} + (-1.00 \text{ V}) + (-0.50 \text{ V}) = -3.50 \text{ V}$
1	1	0	1	$-2.00 \text{ V} + (-1.00 \text{ V}) + (-0.25 \text{ V}) = -3.25 \text{ V}$
0	1	0	0	-1.00 V
1	0	1	1	$-2.00 \text{ V} + (-0.50 \text{ V}) + (-0.25 \text{ V}) = -2.75 \text{ V}$
0	0	0	1	-0.25 V
0	0	1	1	$-0.50 + (-0.25 \text{ V}) = -0.75 \text{ V}$

13. (a) 16 (b) 32 (c) 256 (d) 65,536

15. 1 mV

17.

SAMPLING TIME (μS)	BINARY OUTPUT
0	000
10	000
20	001
30	100
40	110
50	101
60	100
70	011
80	010
90	001
100	001
110	011
120	110
130	111
140	111
150	111
160	111
170	111
180	111
190	111
200	100

19. f_{out} increases.
 21. 691 pF (use standard 680 pF)
 23. $f_{out(min)} = 26.2$ kHz, $f_{out(max)} = 80.9$ kHz
 25. The D_0 (LSB) is stuck high and the D_2 is stuck low.

Chapter 15

1. 5 V
 3. 189.84°
 5. 12 bits
 7. Thermocouple C
 9. -4.36 V
 11. 540Ω
 13. The effects of the wire resistances are cancelled in the 3-wire bridge.
 15. $\Delta R = 4.5$ m Ω
 17. (a) absolute pressure transducer
 (b) gage pressure transducer
 (c) differential pressure transducer

19. See Figure ANS-27.

 


FIGURE ANS-27

21. Reverse the comparator inputs.

This page intentionally left blank

GLOSSARY

ac beta (β_{ac}) The ratio of a change in collector current to a corresponding change in base current in a bipolar junction transistor.

Accuracy In relation to DACs or ADCs, a comparison of the actual output with the expected output, expressed as a percentage.

Acquisition time In an analog switch, the time required for the device to reach its final value when switched from hold to sample.

ac resistance The ratio of a small change in voltage divided by a corresponding change in current for a given device; also called *dynamic*, *small-signal*, or *bulk resistance*.

Active filter A frequency-selective circuit consisting of active devices such as transistors or op-amps coupled with reactive components.

A/D conversion A process whereby information in analog form is converted into digital form.

Amplification The process of producing a larger voltage, current, or power using a smaller input signal as a “pattern.”

Amplifier An electronic circuit having the capability of amplification and designed specifically for that purpose.

Amplitude modulation (AM) A communication method in which a lower-frequency signal modulates (varies) the amplitude of a higher-frequency signal (carrier).

Analog signal A signal that can take on a continuous range of values within certain limits.

Analog switch A type of semiconductor switch that connects an analog signal from input to output with a control input.

Analog-to-digital converter (ADC) A device used to convert an analog signal to a sequence of digital codes.

Anode (semiconductor diode definition) The terminal of a semiconductor diode that is more positive with respect to the other terminal when it is biased in the forward direction.

Antilog The number corresponding to a given logarithm.

Aperture jitter In an analog switch, the uncertainty in the aperture time.

Aperture time In an analog switch, the time to fully open after being switched from sample to hold.

Armstrong oscillator A type of *LC* feedback oscillator that uses transformer coupling in the feedback circuit.

Astable Characterized by having no stable states; a type of oscillator.

Astable multivibrator A type of circuit that can operate as an oscillator and produces a pulse waveform output.

Attenuation The reduction in the level of power, current, or voltage.

Audio Related to the range of frequencies that can be heard by the human ear and generally considered to be in the 20 Hz to 20 kHz range.

Automatic gain control (AGC) A feedback system that reduces the gain for larger signals and increases the gain for smaller signals.

Balanced modulation A form of amplitude modulation in which the carrier is suppressed; sometimes known as *suppressed-carrier modulation*.

Band-pass filter A type of filter that passes a range of frequencies lying between a certain lower frequency and a certain higher frequency.

Band-stop filter A type of filter that blocks or rejects a range of frequencies lying between a certain lower frequency and a certain higher frequency.

Bandwidth The characteristic of certain types of electronic circuits that specifies the usable range of frequencies that pass from input to output. It is the upper critical frequency minus the lower critical frequency.

Barrier potential The inherent voltage across the depletion region of a *pn* junction.

Base One of the semiconductor regions in a BJT.

Base bias A form of bias in which a single resistor is connected between a BJT’s base and V_{CC} .

Bessel A type of filter response having a linear phase characteristic and less than -20 dB/decade/pole roll-off.

Bias The application of dc voltage to a diode or other electronic device to produce a desired mode of operation.

Bipolar Characterized by two *pn* junctions.

Bipolar junction transistor (BJT) A transistor constructed with three doped semiconductor regions separated by two *pn* junctions.

Bounding The process of limiting the output range of an amplifier or other circuit.

Butterworth A type of filter response characterized by flatness in the passband and a -20 dB/decade/pole roll-off.

Bypass capacitor A capacitor connected in parallel with a resistor to provide the ac signal with a low impedance path.

Carrier The high frequency (RF) signal that carries modulated information in AM, FM, and other communications systems.

Cascode amplifier Common-source and common-gate amplifiers connected in series.

Cathode (semiconductor diode definition) The terminal of a diode that is more negative with respect to the other terminal when it is biased in the forward direction.

Center tap A connection at the midpoint of the secondary of a transformer.

Characteristic curve A plot that shows the relationship between two variable properties of a device. For most electronic devices, a characteristic curve refers to a plot of the current, I , plotted as a function of voltage, V .

Chebyshev A type of filter response characterized by ripples in the passband and a greater than -20 dB/decade/pole roll-off.

C_{iss} The common-source input capacitance of a FET as seen looking into the gate.

Clamper A circuit that adds a dc level to an ac signal; also called a *dc restorer*.

Clapp oscillator A variation of the Colpitts oscillator with an added capacitor in series with the inductor in the feedback circuit.

Class A An amplifier that operates in the active region at all times.

Class AB An amplifier that is biased into slight conduction. The Q-point is slightly above cutoff.

Class B An amplifier that has the Q-point located at cutoff, causing the output current to vary only during one-half of the input cycle.

Closed-loop An op-amp configuration in which the output is connected back to the input through a feedback circuit.

Closed-loop voltage gain The net voltage gain of an amplifier when negative feedback is included.

Coax A transmission line, principally used for high frequencies, in which a center conductor is surrounded by a tubular conducting shield.

Cold junction A reference thermocouple held at a fixed temperature and used for compensation in thermocouple circuits.

Collector One of the semiconductor regions in a BJT.

Collector characteristic curves A set of collector I - V curves that show how I_C varies with V_{CE} for a given base current.

Collector feedback bias A form of bias, used in CE and CB amplifiers, in which a single resistor is connected between a BJT's base and its collector.

Colpitts oscillator A type of LC feedback oscillator that uses two series capacitors in the feedback circuit.

Common-base (CB) A BJT amplifier configuration in which the base is the common terminal to an ac signal or ground.

Common-collector (CC) A BJT amplifier configuration in which the collector is the common terminal to an ac signal or ground.

Common-drain (CD) A FET amplifier configuration in which the drain is the grounded terminal to an ac signal or ground.

Common-emitter (CE) A BJT amplifier configuration in which the emitter is the common terminal to an ac signal or ground.

Common-gate (CG) A FET amplifier configuration in which the gate is the grounded terminal to an ac signal or ground.

Common mode A condition characterized by the presence of the same signal on both op-amp inputs.

Common-mode input impedance The ac resistance between each input and ground.

Common-mode input voltage range The range of input voltage, which, when applied to both inputs, will not cause clipping or other output distortion.

Common-mode rejection ratio (CMRR) The ratio of open-loop gain to common-mode gain; a measure of an op-amp's ability to reject common-mode signals.

Common-source (CS) A FET amplifier configuration in which the source is the grounded terminal.

Comparator A circuit that compares two input voltages and produces an output in either of two states indicating the greater than or less than relationship of the inputs.

Compensation The process of modifying the roll-off rate of an amplifier to ensure stability.

Complementary symmetry transistors These are a matching pair of npn/pnp BJTs or a matching pair of n -channel/ p -channel FETs.

Conduction electron An electron that has broken away from the valance band of the parent atom and is free to move from atom to atom within the atomic structure of a material; also called a *free electron*.

Constant-current region The region on the drain characteristic of a FET in which the drain current is independent of the drain-to-source voltage.

Constant-current source A circuit that delivers a load current that remains constant when the load resistance changes.

Coupling capacitor A capacitor connected in series with the ac signal and used to block dc voltages.

Covalent bond A type of chemical bond in which atoms share electron pairs.

Critical angle The angle above which full reflection occurs in a fiber optic cable.

Critical frequency The frequency that defines the end of the passband of a filter; also called *cutoff frequency*.

Crossover distortion Distortion in the output of a class B push-pull amplifier at the point where each transistor changes from the cutoff state to the on state.

Crystal A solid in which the particles form a regular, repeating pattern.

Current mirror A circuit that uses matching diode junctions to form a current source. The current in a diode junction is reflected as a matching current in the other junction (which is typically the base-emitter junction of a transistor). Current mirrors are commonly used to bias a push-pull amplifier.

Current-to-voltage converter A circuit that converts a variable input current to a proportional output voltage.

Cutoff The nonconducting state of a transistor.

Cycle The complete sequence of values that a waveform exhibits before another identical pattern occurs.

D/A conversion The process of converting a sequence of digital codes to an analog form.

Damping factor (DF) A filter characteristic that determines the type of response.

dBm Decibel power level when the reference is understood to be 1 mW (see Decibel).

dc beta (β_{DC}) The ratio of collector current to base current in a bipolar junction transistor.

Decibel A dimensionless quantity that is 10 times the logarithm of a power ratio or 20 times the logarithm of a voltage ratio.

Decoupling network A low-pass filter that provides a low-impedance path to ground for high-frequency signals.

Demodulation The process in which the information signal is recovered from the IF carrier signal; the reverse of modulation.

Depletion mode A class of FETs that is on with zero-gate voltage and is turned off by gate voltage. All JFETs and some MOSFETs are depletion-mode devices.

Depletion region The area near a pn junction on both sides that has no majority carriers.

Differential amplifier (diff-amp) An amplifier that produces an output voltage proportional to the difference of the two input voltages.

Differential input impedance The total resistance between the inverting and the noninverting inputs.

Differential mode The input condition of an op-amp in which opposite polarity signals are applied to the two inputs.

Differentiator A circuit that produces an inverted output that approximates the rate of change of the input function.

Digital signal A noncontinuous signal that has discrete numerical values assigned to the specific steps.

Digital-to-analog converter (DAC) A device in which information in digital form is converted to an analog form.

Diode An electronic device that permits current in only one direction.

Discrete device An individual electrical or electronic component that must be used in combination with other components to form a complete functional circuit.

Discriminator A type of FM demodulator.

Domain The values assigned to the independent variable. For example, frequency or time are typically used as the independent variable for plotting signals.

Doping The process of imparting impurities to an intrinsic semiconductive material in order to control its conduction characteristics.

Drain One of the three terminals of a field-effect transistor; it is one end of the channel.

Droop In an analog switch, the change in the sampled value during the hold interval.

Dynamic emitter resistance (r'_e) The ac resistance of the emitter; it is determined by the dc emitter current.

Efficiency (power) The ratio of the signal power supplied to the load to the power from the dc supply.

Electroluminescence The process of releasing light energy by the recombination of electrons in a semiconductor.

Electron The basic particle of negative electrical charge in matter.

Electrostatic discharge (ESD) The discharge of a high voltage through an insulating path that frequently destroys a device.

Emitter One of the three semiconductor regions in a BJT.

Emitter bias A very stable form of bias requiring two power supplies. The emitter is connected through a resistor to one supply; another resistor is connected between a BJT's base and ground.

Energy The ability to do work.

Enhancement mode A MOSFET in which the channel is formed (or enhanced) by the application of a gate voltage.

Feedback oscillator A type of oscillator that returns a fraction of output signal to the input with no net phase shift resulting in a reinforcement of the output signal.

Feedforward A method of frequency compensation in op-amp circuits.

Feedthrough In an analog switch, the component of the output voltage that follows the input voltage after the switch opens.

Fiber optics The use of light pulses to transmit information through a fiber optic cable.

Field-effect transistor (FET) A voltage-controlled device in which the voltage at the gate terminal controls the amount of current through the device.

Filter A type of electrical circuit that passes certain frequencies and rejects all others.

Flash A method of A/D conversion.

Floating point A point in the circuit that is not electrically connected to ground or a "solid" voltage.

Fold-back current limiting A method of current limiting in voltage regulators.

Forward bias The condition in which a *pn* junction conducts current.

Four-quadrant multiplier A linear device that produces an output voltage proportional to the product of two input voltages.

Frequency The number of repetitions per unit of time for a periodic waveform.

Frequency modulation (FM) A communication method in which a lower-frequency intelligence-carrying signal modulates (varies) the frequency of a higher-frequency signal.

Full-wave rectifier A circuit that converts an alternating sine wave into a pulsating dc voltage consisting of both halves of a sine wave for each input cycle.

Gage factor (GF) The ratio of the fractional change in resistance to the fractional change in length along the axis of the gage.

Gain The amount of amplification. Gain is a ratio of an output quantity to an input quantity (e.g., voltage gain is the ratio of the output voltage to the input voltage).

Gate One of the three terminals of a field-effect transistor. A voltage applied to the gate controls drain current.

Germanium A semiconductive material.

Half-wave rectifier A circuit that converts an alternating sine wave into a pulsating dc voltage consisting of one-half of a sine wave for each input cycle.

Harmonics Higher-frequency sinusoidal waves that are integer multiples of a fundamental frequency.

Hartley oscillator A type of *LC* feedback oscillator that uses two series inductors in the feedback circuit.

High-pass filter A type of filter that passes frequencies above a certain frequency while rejecting lower frequencies.

Hole A mobile vacancy in the electronic valence structure of a semiconductor. A hole acts like a positively charged particle.

Hysteresis The property that permits a circuit to switch from one state to the other at one voltage level and switch back to the original state at another lower voltage level.

I_{DSS} The drain current in a FET when the gate is shorted to the source. For JFETs, this is the maximum allowed current.

I_{GSS} The gate-reverse current in a FET. The value is based on a specified gate-to-source voltage.

Input bias current The average dc current required by the inputs of an op-amp to properly operate the device.

Input offset voltage (V_{OS}) The differential dc voltage required between the op-amp inputs to force the differential output to zero volts.

Input offset voltage drift A parameter that specifies how much change occurs in the input offset voltage for each degree change in temperature.

Instrumentation amplifier A differential voltage-gain device that amplifies the difference between the voltage existing at its two input terminals.

Insulated gate bipolar transistor A transistor that acts like a voltage-controlled BJT.

Integrated circuit (IC) A type of circuit in which all the components are constructed on a single chip of silicon.

Integrator A circuit that produces an inverted output that approximates the area under the curve of the input function.

Intermediate frequency A fixed frequency that is lower than the RF, produced by beating an RF signal with an oscillator frequency.

Intrinsic (pure) An intrinsic semiconductor is one in which the charge concentration is essentially the same as a pure crystal with relatively few free electrons.

Inverting amplifier An op-amp closed-loop configuration in which the input signal is applied to the inverting input.

Ion An atom or group of atoms that has gained or lost one or more valence electrons, resulting in a net positive or negative charge.

Isolation amplifier An amplifier in which the input and output stages are not electrically connected.

Junction field-effect transistor (JFET) A type of FET that operates with a reverse-biased *pn* junction to control current in a channel. It is a depletion-mode device.

Large-signal A signal that operates an amplifier over a significant portion of its load line.

Light-emitting diode (LED) A type of diode that emits light when there is forward current.

Limiting A circuit that removes part of a waveform above or below a specified level; also called a *clipper*.

Linear component A component in which an increase in current is proportional to the applied voltage.

Linearity A straight-line relationship. A linear error is a deviation from the ideal straight-line output of a DAC.

Linear regulator A voltage regulator in which the control element operates in the linear region.

Line regulation The change in output voltage for a given change in line (input) voltage, normally expressed as a percentage.

Load line A straight line plotted on a current versus voltage plot that represents all possible operating points for an external circuit.

Load regulation The change in output voltage for a given change in load current, normally expressed as a percentage.

Logarithm An exponent; the logarithm of a quantity is the exponent or power to which a given number called the base must be raised in order to equal the quantity.

Loop gain An op-amp's open-loop voltage gain times the attenuation of the feedback network.

Low-pass filter A type of filter that passes frequencies below a certain frequency while rejecting higher frequencies.

Mean Average value.

Microcontroller A specialized microprocessor designed for control functions.

Mixer A nonlinear circuit that combines two signals and produces the sum and difference frequencies; a device for down-converting frequencies in a receiver system.

Modem A device that converts signals produced by one type of device to a form compatible with another; *modulator/demodulator*.

Modulation The process in which a signal containing information is used to modify the amplitude, frequency, or phase of a much higher-frequency signal called the carrier.

Monostable Characterized by having one stable state.

Monotonicity In relation to DACs, the presence of all steps in the output when sequenced over the entire range of input bits.

MOSFET Metal-oxide semiconductor field-effect transistor; one of two major types of FET. It uses a SiO₂ layer to insulate the gate lead from the channel. MOSFETs can be either depletion mode or enhancement mode.

Natural logarithm The exponent to which the base *e* (*e* = 2.71828) must be raised in order to equal a given quantity.

Negative feedback The process of returning a portion of the output back to the input in a manner to cancel changes that may occur at the input.

Neutralization A method of preventing unwanted oscillations by adding negative feedback to just cancel the positive feedback caused by internal capacitances of an amplifier.

Noise An unwanted voltage or current fluctuation.

Noninverting amplifier An op-amp closed-loop configuration in which the input signal is applied to the noninverting input.

Nonmonotonicity In relation to DACs, a step reversal or missing step in the output when sequenced over the entire range of input bits.

Norton's theorem An equivalent circuit that replaces a complicated two-terminal linear network with a single current source and a parallel resistance.

Nyquist rate In sampling theory, the minimum rate at which an analog voltage can be sampled for A/D conversion. The sample rate must be more than twice the maximum frequency component of the input signal.

Ohmic region The region on the drain characteristic of a FET with low values of V_{DS} in which the channel resistance can be changed by the gate voltage; in this region the FET can be operated as a voltage-controlled resistor.

One-shot A monostable multivibrator that produces a single output pulse for each input trigger pulse.

Open-loop A condition in which an op-amp has no feedback.

Open-loop voltage gain The internal gain of an amplifier without external feedback.

Operational amplifier (op-amp) A type of amplifier that has very high voltage gain, very high input impedance, very low output impedance, and good rejection of common-mode signals.

Operational transconductance amplifier An amplifier in which the output current is the gain times the input voltage.

Order The number of poles in a filter.

Oscillator An electronic circuit that operates with positive feedback and produces a time-varying output signal without an external input signal.

Output impedance The ac resistance viewed from the output terminal of an op-amp.

Passband The region of frequencies that are allowed to pass through a filter with minimum attenuation.

Peak detector A circuit used to detect the peak of the input voltage and store that peak value on a capacitor.

Period (*T*) The time for one cycle of a repeating wave.

Periodic A waveform that repeats at regular intervals.

Phase angle (in radians) The fraction of a cycle that a waveform is shifted from a reference waveform of the same frequency.

Phase-locked loop (PLL) A device for locking onto and tracking the frequency of an incoming signal.

Phase margin The difference between the total phase shift through an amplifier and 180° ; the additional amount of phase shift that can be allowed before instability occurs.

Phase shift The relative angular displacement of a time-varying function relative to a reference.

Phase-shift oscillator A type of sinusoidal feedback oscillator that uses three RC networks in the feedback loop.

Photodiode A diode whose reverse resistance changes with incident light.

Piezoelectric effect The property exhibited by a material where it produces a voltage at the frequency at which it vibrates due to changing mechanical stress.

Pinch-off voltage The value of the drain-to-source voltage of a FET at which the drain current becomes constant when the gate-to-source voltage is zero.

PN junction The boundary between n -type and p -type materials.

Pole A network containing one resistor and one capacitor that contributes -20 dB/decade to a filter's roll-off rate.

Positive feedback A condition where an in-phase portion of the output voltage is fed back to the input.

Power gain The ratio of the power delivered to the load to the input power of an amplifier.

Power supply A device that converts ac or dc voltage into a voltage or current suitable for use in various applications to power electronic equipment. The most common form is to convert ac from the utility line to a constant dc voltage.

programmable gain amplifier (PGA) a type of op-amp that has its gain selected by a digital input. A PGA may have multiple channels. Typically, a microcontroller or computer selects the channel and sets the gain with a digital signal.

Push-pull A type of class B amplifier with two transistors in which one transistor conducts for one half-cycle and the other conducts for the other half-cycle.

Quality factor (Q) A dimensionless number that is the ratio of the maximum energy stored in a cycle to the energy lost in a cycle. The ratio of a band-pass filter's center frequency to its bandwidth.

Quantization The determination of a value for an analog quantity.

Quantization error The error resulting from the change in the analog voltage during the A/D conversion time.

Quantizing The process of assigning numbers to sampled data.

Quiescent point The point on a load line that represents the current and voltage conditions for a circuit with no signal (also called operating or Q-point). It is the intersection of a device characteristic curve with a load line.

Radio frequency interference (RFI) High frequencies produced when high values of current and voltage are rapidly switched on and off and causes unwanted signals in another circuit.

$r_{DS(on)}$ The resistance of the channel of a FET measured between the drain and the source when the FET is fully on and only a small voltage is between the drain and the source.

Recombination The process of a free electron in the conduction band falling into a hole in the valence band of an atom.

Rectifier An electronic circuit that converts ac into pulsating dc.

Regulator An electronic circuit that is connected to the output of a rectifier and maintains an essentially constant output voltage despite changes in the input, the load current, or the temperature.

Relaxation oscillator A type of oscillator that uses an RC timing circuit to generate a nonsinusoidal waveform.

Resistance temperature detector (RTD) A type of temperature transducer in which resistance is directly proportional to temperature.

Resolution In relation to DACs or ADCs, the number of bits involved in the conversion. Also, for DACs, the reciprocal of the maximum number of discrete steps in the output.

Resolver A type of synchro.

Resolver-to-digital converter (RDC) An electronic circuit that converts resolver voltages to a digital format that represents the angular position of the rotor shaft.

Reverse bias The condition in which a pn junction blocks current.

Ripple voltage The variation in the dc voltage on the output of a filtered rectifier caused by the slight charging and discharging action of the filter capacitor.

Roll-off The rate of decrease in gain, below or above the critical frequencies of a filter.

Root mean square (RMS) The value of an ac voltage that corresponds to a dc voltage that produces the same heating effect in a resistance.

Rotor The part of a synchro that is attached to the shaft and rotates.

Sample-and-hold The process of taking the instantaneous value of a quantity at a specific point in time and storing it on a capacitor.

Sampling The process of breaking the analog waveform into time "slices" that approximate the original wave.

Saturation The state of a BJT in which the collector current has reached a maximum and is independent of the base current.

Schmitt trigger A comparator with hysteresis.

Semiconductor A material that has a conductance value between that of a conductor and that of an insulator. Silicon and germanium are examples.

Settling time The time it takes a DAC to settle within $\pm 1/2$ LSB of its final value.

Shell An energy level in which electrons orbit the nucleus of an atom.

Signal compression The process of scaling down the amplitude of a signal voltage.

Silicon A semiconductive material used in diodes and transistors.

Silicon-controlled rectifier A type of three-terminal thyristor that conducts current when triggered on and remains on until the anode current falls below a specific value.

Single-ended mode The input condition of an op-amp in which one input is grounded and the signal voltage is applied only to the other input.

Skin effect The phenomenon at high frequencies that causes current to move to the outside surface of conductors.

Slew rate The rate of change of the output voltage of an op-amp in response to a step input.

Source One of the three terminals of a field-effect transistor; it is one end of the channel.

Spectrum A plot of amplitude versus frequency for a signal.

Stability A condition in which an amplifier circuit does not oscillate.

Stage Each transistor in a multistage amplifier that amplifies a signal.

Standing wave A stationary wave on a transmission line formed by the interaction of an incident and reflected wave.

Stator The part of a synchro that is fixed. The stator windings are located on the stator.

Strain The expansion or compression of a material caused by stress forces acting on it.

Strain gage A transducer formed by a resistive material in which a lengthening or shortening due to stress produces a proportional change in resistance.

Successive approximation A method of A/D conversion.

Summing amplifier A variation of a basic comparator circuit that is characterized by two or more inputs and an output voltage that is proportional to the magnitude of the algebraic sum of the input voltages.

Switch An electrical or electronic device for opening and closing a current path.

Switching regulator A voltage regulator in which the control element is a switching device.

Synchro An electromechanical transducer used for shaft angle measurement and control.

Synchro-to-digital converter (SDC) An electronic circuit that converts synchro voltages to a digital format that represents the angular position of the rotor shaft.

Terminal An external contact point on an electronic device.

Thermal overload A condition in a rectifier where the internal power dissipation of the circuit exceeds a certain maximum due to excessive current.

Thermistor A type of temperature transducer in which resistance is proportional to temperature. Thermistors can have either a positive or a negative temperature coefficient.

Thermocouple A type of temperature transducer formed by the junction of two dissimilar metals that produces a voltage proportional to temperature.

Thevenin's theorem An equivalent circuit that replaces a complicated two-terminal linear network with a single voltage source and a series resistance.

Thyristor A class of four-layer (*pnpn*) semiconductor devices, such as the silicon-controlled rectifier.

Transconductance The ratio of output current to input voltage; the gain of a FET; it is determined by a small change in drain

current divided by a corresponding change in gate-to-source voltage. It is measured in siemens or mhos.

Transducer A device that converts a physical quantity from one form to another; for example, a microphone converts sound into voltage.

Transfer curve A plot of the output of a circuit or system for a given input.

Transistor A semiconductor device used for amplification and switching applications in electronic circuits.

Triac A three-terminal thyristor that can conduct current in either direction when properly activated.

Trim To precisely adjust or fine-tune a value.

Uncompensated op-amp An op-amp with more than one critical frequency.

Valence electron An electron in the outermost shell or orbit of an atom.

Varactor A diode that is used as a voltage-variable capacitor.

Vector Any quantity that has both magnitude and direction.

$V_{GS(off)}$ The voltage applied between the gate and the source that is just sufficient to turn off a FET. The exact point is arbitrary; some manufacturers use a specific very small current to determine it.

Voltage-controlled oscillator A type of relaxation oscillator whose frequency can be changed by a variable dc voltage; also known as a VCO.

Voltage-divider bias A very stable form of bias in which a voltage divider is connected between V_{CC} and ground; the output of the divider supplies bias current to the base of a BJT.

Voltage-follower A closed-loop, noninverting op-amp with a voltage gain of one.

Voltage regulation The process of maintaining an essentially constant output voltage over variations in input voltage or load.

Voltage-to-current converter A circuit that converts a variable input voltage to a proportional output current.

Wien-bridge oscillator A type of sinusoidal feedback oscillator that uses an RC lead-lag network in the feedback loop.

Zener diode A type of diode that operates in reverse breakdown (called zener breakdown) to provide voltage regulation.

Zero-voltage switching The process of switching power to a load at the zero crossings of an ac voltage to minimize radio-frequency (RF) noise generation.

INDEX

- A**
- Absorption, 619
- ac beta, 749
- ac resistance, 3–4, 749
- Acceleration transducers, 719–720
- Accelerometers, 719–720
- Acceptors, 46
- Accuracy
- DAC, 650
 - defined, 749
- Acquisition time, 640, 749
- Active filters, 425–454. *See also* Filters
- advantages over passive filters, 434
 - all-pass, 430
 - band-pass, 442–448
 - band-pass response, 428–429
 - band-stop, 448–450
 - band-stop response, 429–430
 - Bessel characteristic, 432
 - Butterworth characteristic, 431
 - cascaded, 436–437
 - Chebyshev characteristic, 431
 - critical frequency, 433
 - damping factor, 432
 - defined, 425, 427, 749
 - devices, 425
 - discrete point measurement, 450
 - FM stereo receiver example, 451–453
 - high-pass, 439–442
 - high-pass response, 427–428
 - low-pass, 434–439
 - low-pass response, 426–427
 - response characteristics, 431–434
 - response measurements, 450–453
 - roll-off rate, 433
 - Sallen-Key, 435–436
 - single-pole, 434
 - swept frequency measurement, 450–451
 - switched-capacitor, 449
- Active FM antenna example, 244–245
- AD2590 resolver-to-digital converter, 701–702
- AD210 isolation amplifier, 560
- AD532 linear multiplier
- block diagram, 591
 - connecting, 592–593
 - defined, 591
 - as four-quadrant multiplier, 593
 - transfer function and scale factor, 592
- AD585 sample-and-hold amplifier, 641–642
- AD622 instrumentation amplifier
- defined, 551
 - gain versus frequency, 551–552
 - illustrated, 551
 - voltage gain, setting, 551
- AD624 instrumentation amplifier, 552
- AD637 rms-to-DC converter
- block diagram, 694
 - defined, 694
 - internal function diagram, 695
- AD650 IC V/F converter. *See also* Voltage-to-frequency (V/F) converters
- defined, 669
 - example, 670–671
 - full cycle period, 670
 - illustrated, 669
 - interval duration, 670
 - output frequency, 670
- AD8436 converter, 695
- AD9300 analog multiplexer, 634–635
- ADC0804 ADC
- defined, 663
 - illustrated, 663
 - logic diagram, 664
- ADCs. *See* Analog-to-digital converters
- ADG1212 analog switch, 632–633
- Adjustable negative linear regulators, 528
- Adjustable positive linear regulators. *See also* IC regulators
- defined, 527
 - LM317, 527–528
 - operation, 527–528
- AGC. *See* Automatic gain control
- All-pass filters, 430
- AM. *See* Amplitude modulation
- AM demodulators
- basic, 602–603
 - defined, 602
 - illustrated, 603
 - operation in terms of frequency spectra, 603
- AM receivers (superheterodyne)
- AGC, 587
 - antenna, 587
 - audio and power amplifiers, 587
 - block diagram, 587
 - defined, 586–587
 - detector, 587
 - IF amplifier, 587
 - local oscillator, 587
 - mixer, 587
 - RF amplifier, 587
 - signal flow, 588
- Amplification, 749
- Amplifiers, 18–29
- averaging, 398–399
 - capacitively coupled, 240–247
 - cascaded stages, 23–24
 - cascode, 213
 - common-base (CB), 147–152
 - common-collector (CC), 143–147
 - common-drain (CD), 209–212
 - common-emitter (CE), 136–142
 - common-gate (CG), 212–213
 - common-source (CS), 206–208
 - decibel power ratios, 25–28
 - decibel voltage ratios, 28–29
 - defined, 20, 749
 - direct-coupled, 259–265
 - efficiency, 270
 - IF, 256–257
 - instrumentation, 548–555
 - inverting, 328–329
 - isolation, 555–561
 - linear, 20–21
 - log and antilog, 569–571
 - model, 22–23
 - noninverting, 326–328
 - nonlinear, 21–22
 - operational, 307–342
 - operational transconductance (OTAs), 561–568
 - output, 23
 - RF, 247–252
 - sample-and-hold, 638–642
 - special-purpose, 547–576
 - summing, 396–402
 - switching, 21
 - transformer-coupled, 252–259
 - tuned, 250–251
 - waveshaping, 21
 - wide-band, 32–33
- Amplitude modulation (AM), 594–600
- balanced modulation, 595–596
 - concept illustration, 594
 - defined, 586, 594, 749
 - demodulation, 602–603
 - frequency spectra, 596
 - linear multiplier as balanced modulator, 596–597
 - multiplication process, 594
 - with music, 599
 - as OTA application, 565–567
 - signal conversion to IF, 603
 - signal example, 586
 - standard, 597–599
 - sum and difference frequencies, 594–595
 - with voice, 599
 - waveform, 586
- Analog electronics
- ac resistance, 3–4
 - conventional current, 4
 - electron flow, 4
 - linear equations, 2–3
- Analog multiplexers
- AD9300, 634–635
 - defined, 634
 - four-channel, 634
- Analog signals
- defined, 5, 749
 - digital signals and, 643–645
 - examples of, 7
 - frequency domain, 10–12
 - periodic, 10
 - time-domain, 10
 - types of, 5
- Analog switches, 632–638
- ADG1212, 632–633
 - applications, 632
 - in ASK test generator, 493
 - break-before-make switching, 633
 - defined, 749
 - multiple-channel, 634–636
 - solar panel control system example, 636–637
 - types of, 632–634
- Analog switches (MOSFET)
- analog multiplexer, 219
 - applications, 218–220
 - defined, 217

- Analog switches (MOSFET) (*continued*)
 example, 218
 operation of, 217
 sampling circuit, 218
 switched-capacitor circuit, 219–220
- Analog systems
 defined, 12
 examples of, 12–13
- Analog waveforms, 6
- Analog-to-digital (A/D) conversion
 concepts, 651–654
 defined, 644, 651, 749
 errors, 676–677
 example, 395–396
 incorrect code, 677
 methods, 655–665
 missing code, 677
 offset error, 677
- Analog-to-digital converters (ADCs)
 ADC0804, 663–665
 cell phone example, 645–646
 conversion time, 652
 defined, 644, 749
 dual-slope, 660–661
 flash (simultaneous), 655–657
 list of, 665
 method for testing, 677
 quantization error, 653–654
 resolution, 651–652
 sampling theory, 653
 single-slope, 659–660
 specific, 663–665
 staircase-ramp, 657–658
 successive approximation, 662–663
 testing, 676
 tracking, 658–659
- Angle measurement, 697–703
 digital code representation, 700–701
 RDC operation, 698–700
 resolvers, 698
 SDC operation, 698–700
 synchros, 697–698
- Angle of incidence, 619
- Angle of reflection, 619
- Anode terminal, 48, 749
- Antennas
 capacitively coupled amplifier, 244–245
 superheterodyne AM receiver, 587
- Antilog amplifiers. *See also* Special-purpose amplifiers
 defined, 572, 749
 feedback resistor current, 572
 IC, 573
 multipliers with, 574–576
 negative input voltage, 572
- Aperture jitter, 640, 749
- Aperture time, 640, 749
- Armstrong oscillators, 480, 749
- ASK test generator example
 analog switch, 493
 block diagram, 492
 defined, 491–492
 125kHz oscillator, 492
 10 kHz pulse oscillator, 492
- Astable, 749
- Astable multivibrators, 488–490, 749
- Attenuation
 defined, 749
 phase-shift oscillator, 749–751
- Audio, 749
- Audio amplifiers, 606–607
 defined, 606
 LM386, 606–607
 superheterodyne AM receiver, 589
 superheterodyne FM receivers, 589
- Automatic gain control (AGC)
 circuits, 696
 defined, 749
 feedback oscillators, 469
 IF amplifiers, 605
 RF amplifier input, 197
 superheterodyne AM receiver, 587
 tuned amplifier, 251
- Avalanche breakdown, 49
- Avalanche effect, 49
- Average value, sinusoidal wave, 8–9
- Averaging amplifier, 398–399
- Averaging circuits
 defined, 692
 illustrated, 693
- B**
- Balanced modulators
 defined, 595–596, 749
 frequency spectra of, 596
 linear multiplier as, 596–597
- Band-pass filters, 442–448. *See also* Active filters
 bandwidth, 428
 cascaded low-pass/high-pass filters and, 442–443
 critical frequencies, 429
 defined, 428, 749
 multiple-feedback, 443–444
 quality factor, 429
 response, 428–429
 for RFID reader, 445
 state-variable, 445–447
- Band-stop filters, 448–450. *See also* Active filters
 defined, 429, 749
 multiple-feedback, 448
 response, 429–430
 state-variable, 448–449
- Bandwidth
 defined, 357, 749
 negative feedback effect on, 363–364
 open-loop voltage gain, 357
 unity-gain, 357
- Barrier potential, 47, 749
- Base, 749
- Base bias
 circuit illustration, 122
 defined, 122, 749
 example, 123
- Baseball counting system example, 86
- Base-collector junction, 112
- Base-emitter junction, 112
- Bessel characteristic, 432, 749
- Bias
 BJT circuits, 121–131
 clamper, 287–288
 collector-feedback, 123–124
 defined, 749
 diode, 50–51
 D-MOSFET, 202–203
 emitter, 128–129
 E-MOSFET, 203–204
 forward, 48, 751
 forward-reverse, 113
 reverse, 49–50, 753
 stability, 260–263
 voltage-divider, 124–128, 190–191, 754
 zero, 202
- Bias current
 input/output resistances versus, 564
 transconductance as function of current, 562
- Biassing
 current sources, 192, 211–212
 graphical methods, 188–190
 JFET, 186–193
 push-pull amplifier, 274–275
 self, 186–188
- Binary-weighted-input DAC. *See also* Digital-to-analog converters (DACs)
 defined, 646
 disadvantages, 647
 example, 647–648
 illustrated, 647
- Bipolar, 749
- Bipolar junction transistors (BJTs), 111–167
 ac equivalent circuit, 135
 ac quantities, 131–132
 amplification, 136
 base, 112
 base bias, 122–123
 base-collector junction, 112
 base-emitter characteristic, 116
 base-emitter junction, 112
 bias circuits, 121–131
 bypass capacitor, 135–136
 characteristic curves, 116–118
 collector, 112
 collector characteristic, 116–118
 collector-feedback bias, 123–124
 common-base (CB) amplifier, 147–152
 common-collector (CC) amplifier, 143–147
 common-emitter (CE) amplifier, 136–142
 construction illustration, 112
 coupling capacitor, 135
 currents, 114
 cutoff, 118–119
 data sheet parameters, 130–136
 dc beta (β_{DC}), 114–115
 dc current gain, 133
 dc equivalent circuit, 135
 dc load line, 119–120
 dc power dissipation, 133
 dc quantities, 131–132
 defined, 112, 749
 electron flow, 114
 emitter, 112
 emitter bias, 128–129
 forward-reverse bias, 113
 gain measurement, 166
 general-purpose/small-signal, 158
 IV curve, 119
 leakage measurement, 166
 log amplifier with, 571
 maximum power dissipation curve, 133–134
 multiple-transistor packages, 159
 one-transistor switching circuit, 154–155
 operation of, 113–114
 power, 158–159
 Q-point, 121
 RF, 159–160
 saturation, 118–119

- structure of, 112–121
- summary, 166–167
- as a switch, 152–157
- symbols, 112
- temperature control system example, 129–130
- testers, 163–165
- testing, with DMM, 160–166
- transistor categories, 157–160
- troubleshooting, 160–166
- two-transistor switching circuit, 155
- voltage-divider bias, 124–128
- voltages, 115–116
- BJTs.** *See* Bipolar junction transistors
- Bonds**
 - covalent, 44–45
 - metallic, 44
- Bounding**
 - defined, 391, 749
 - output, 391–393
- Break-before-make switching,** 633
- Breakdown voltages, zener diode,** 78
- Bridge rectifiers**
 - functioning, 61–62
 - linear power supply example, 70
 - open diode effect in, 97
 - output voltage, 62
 - peak inverse voltage (PIV), 62
 - shorted diode effect, 98
- Butterworth characteristic,** 431, 749
- Bypass capacitors,** 135, 263, 749
- C**
 - Cable TV systems, 259
 - Capacitance**
 - junction field-effect transistors (JFETs), 185–186
 - varactor diode, 82
 - Capacitively coupled amplifiers,** 240–247
 - active FM antenna example, 244–245
 - analysis, 241
 - defined, 240
 - example, 243–244
 - input resistance, 242
 - isolation, 555–557
 - loading effects, 241–244
 - noise and, 245–246
 - oscillation and, 245–246
 - output resistance, 242
 - unloaded gain, 241
 - unwanted oscillation and noise, 245–246
 - voltage gain, 242
 - Capacitor-input filter**
 - defined, 63
 - leaky, 98–99
 - linear power supply example, 70–71
 - operation with, 64
 - ripple voltage, 63–64
 - surge current, 65
 - Capacitors**
 - bypass, 135, 263, 749
 - charging of, 403–404
 - coupling, 135, 750
 - integrator, 403–404
 - shorted, 98–99
 - voltage, 404
 - Capture range,** 615
 - Carriers,** 749
 - Cascaded filters**
 - band-pass response, 442–443
 - high-pass, 441
 - low-pass, 436–437
 - Cascaded stages, amplifier,** 23–24
 - Cascode amplifiers,** 213, 749
 - Cathode terminal,** 48, 749
 - Center tap,** 749
 - Center-tapped full-wave rectifier,** 59–60
 - Characteristic curves**
 - BJT, 116–118
 - collector, 750
 - collector characteristic, 116–118
 - defined, 3, 749
 - diode, 51
 - drain characteristic curve, 181
 - illustrated, 3
 - phase control, 723
 - plotting on oscilloscope, 51–52
 - silicon-controlled rectifiers (SCRs), 721
 - triacs, 722
 - turning on, 723
 - Characteristic impedance, transmission line,** 248
 - Chebyshev characteristic,** 431, 749
 - Circuit breakers, troubleshooting,** 96
 - Clamper bias**
 - action, 288
 - class C power amplifier, 287–288
 - Clampers**
 - defined, 76, 749
 - example, 77
 - negative, 77
 - positive, 76
 - Clapp oscillators.** *See also* LC feedback oscillators
 - defined, 478, 750
 - schematic, 479
 - Class A power amplifiers.** *See also* Power amplifiers
 - centered Q-point, 266–267
 - DC quiescent power, 268
 - defined, 265, 750
 - efficiency, 270–271
 - heat dissipation, 265–266
 - large-signal type, 265
 - maximum efficiency, 271
 - maximum output, 266
 - output power, 268–270
 - power gain, 267–268
 - Class AB power amplifiers,** 750
 - Class B power amplifiers,** 272–283. *See also* Power amplifiers
 - ac operation, 275–276
 - biasing, 274–275
 - complementary symmetry transistors, 273
 - crossover distortion, 273–274
 - current mirror, 274
 - defined, 272, 750
 - illustrated, 272
 - MOSFET, 278–281
 - PA system power amplifier example, 281–282
 - push-pull operation, 272–273
 - Q-point at cutoff, 272
 - single-supply operation, 276–277
 - transformer coupling, 273
 - Class C power amplifiers.** *See also* Power amplifiers
 - clamper bias, 287–288
 - defined, 283
 - example, 288–289
 - illustrated, 284
 - maximum output power, 287
 - operation of, 283–284
 - power dissipation, 284–285
 - resonant circuit action, 286
 - tank circuit, 287
 - tuned, illustrated, 285
 - tuned operation, 285–287
 - waveforms, 284
 - Class D power amplifiers.** *See also* Power amplifiers
 - block diagram, 289
 - complementary MOSFET stage, 291–292
 - defined, 283, 289
 - low-pass filter, 292
 - pulse-width modulation (PWM), 290–291
 - signal flow, 292
 - Clippers.** *See* Limiters
 - Closed-loop,** 750
 - Closed-loop gain**
 - defined, 355, 750
 - illustrated, 355
 - open-loop gain comparison, 364
 - open-loop gain intersection, 369
 - programmable gain amplifiers, 355
 - Closed-loop response (op-amp)**
 - defined, 363
 - gain-bandwidth product, 364–365
 - negative feedback effect, 363–364
 - CMOS**
 - advantages of, 220
 - digital switching application, 220–222
 - inverter, 221
 - NAND gate, 221
 - NOR gate, 221–222
 - CMRR.** *See* Common-mode rejection ratio
 - Coax,** 248, 750
 - Codecs,** 645
 - Cold junctions**
 - compensation, 707
 - defined, 704, 750
 - Collector,** 750
 - Collector characteristic curves,** 750
 - Collector-feedback bias**
 - circuit illustration, 123
 - collector current, 124
 - defined, 123, 750
 - example, 124
 - Colpitts oscillators.** *See also* LC feedback oscillators
 - conditions for oscillation, 476
 - defined, 475, 750
 - FET, 477
 - frequency of oscillation, 475
 - loading of, 476–478
 - RF choke, 477
 - schematic, 475
 - start-up conditions, 476
 - Common mode,** 750
 - Common-base (CB) amplifiers.** *See also* Bipolar junction transistors (BJTs)
 - ac parameters, 151–152
 - defined, 147, 750
 - equivalent circuit, 148
 - illustrated, 148
 - input resistance, 149
 - output resistance, 149–151
 - with swamping resistor, 148–149
 - voltage-divider bias, 148

- Common-collector (CC) amplifiers. *See also* Bipolar junction transistors (BJTs)
- ac parameters, 151–152
 - current gain, 144–145
 - darlington feedback regulator, 146–147
 - darlington pair, 146
 - defined, 143, 750
 - equivalent circuit, 143
 - illustrated, 143
 - input resistance, 144
 - output resistance, 144
 - voltage gain, 143–144
- Common-drain (CD) amplifiers
- with current-source biasing, 211–212
 - defined, 209, 750
 - example, 210–211
 - illustrated, 209
 - input resistance, 209–210
 - source-follower, 209
 - voltage gain, 209
 - voltage-divider bias, 210
- Common-emitter (CE) amplifiers, 136–142.
- See also* Bipolar junction transistors (BJTs)
 - ac equivalent circuit, 137–138
 - ac load line, 140–142
 - ac parameters, 151–152
 - collector ac circuit, 139
 - defined, 136, 750
 - dynamic emitter resistance, 138
 - emitter ac circuit, 138–139
 - illustrated, 137
 - input resistance, 139–140
 - output resistance, 139–140
 - Q-point, 140–141
 - total ac resistance, 138
 - two-stage, 240
 - voltage gain, 138–139, 148–149
- Common-gate (CG) amplifiers. *See also* FET linear amplifiers
- as cascode amplifier, 213
 - defined, 212, 750
 - JFET, 213
 - MOSFET, 213
- Common-mode input impedance, 750
- Common-mode input voltage range, 319, 750
- Common-mode operation (diff-amp), 313–314
- Common-mode rejection, 314
- Common-mode rejection ratio (CMRR)
- dB expression, 314
 - defined, 314, 750
 - example, 315–316
 - infinite, 320
 - op-amp, 320
- Common-source (CS) amplifiers. *See also* FET linear amplifiers
- defined, 206, 750
 - D-MOSFET, 206–207
 - E-MOSFET, 207
 - example, 208
 - input resistance, 207–208
 - JFET, 206
 - voltage gain, 207
- Communications circuits, 585–622
- AM demodulation, 602–603
 - amplitude modulation, 594–600
 - audio amplifier, 604–607
 - fiber optics, 618–621
 - frequency modulation (FM), 607–610
 - IF amplifiers, 604–607
 - introduction to, 585
 - linear multiplier, 590–593
 - mixer, 600–602
 - PLL, 610–618
 - receivers, 586–590
- Comparators, 386–396
- analog-to-digital (A/D) conversion
 - application, 395–396
 - bounded, 392
 - defined, 750
 - double-bounded, 392
 - external component failure symptoms, 411–412
 - input noise effect on, 388–389
 - noise effect reduction, 389–391
 - nonzero-level detection, 387–388
 - operation with hysteresis, 390
 - output bounding, 391–393
 - oven-temperature sensing circuit application, 394
 - Schmitt trigger, 390
 - troubleshooting, 411–413
 - window, 393–394
 - zero-level detection, 386
- Compensating network
- action, 372
 - critical frequency for, 372–373
 - example, 373–374
 - frequency response, 373
 - open-loop response change, 372
- Compensation. *See also* Operational amplifiers (op-amps)
- cold-junction, 707
 - defined, 750
 - extent of, 375
 - external, 372
 - feedforward, 377
 - internal, 372
 - phase lag, 371, 372
 - single-capacitor, 375–377
 - thermal expansion, 714
 - thermocouple, 707
- Complementary MOSFETs
- defined, 291
 - efficiency, 292
 - illustrated, 291
- Complementary symmetry transistors
- class B power amplifier, 273
 - defined, 272, 750
- Conduction band, 44
- Conduction electrons, 750
- Constant-current limiting, 514
- Constant-current region, 181, 750
- Constant-current source, 409, 750
- Conventional current, 4
- Conversion time, ADC, 652
- Coupling capacitors, 135, 750
- Covalent bonds, 44–45, 750
- Crest factor, 695
- Critical angle, 619, 750
- Critical frequency
- active filters, 433
 - defined, 750
- Crossover distortion
- class B power amplifier, 273–274
 - defined, 273, 750
 - illustrated, 274
 - transformer-coupled amplifier, 275
- Crystal, 750
- Crystal-controlled oscillators, 481
- defined, 480
 - fundamental frequency, 482
 - modes of oscillation, 481–482
 - piezoelectric effect, 480–481
 - schematics, 481
- Current gain
- BJT, 133
 - common-collector (CC) amplifier, 144–145
- Current limiting
- action illustration, 535
 - network functioning, 534
 - regulator with, 534
- Current mirror, 274, 750
- Current regulators, 535–536
- Current(s)
- bias, 562
 - input bias, 318
 - input offset, 319
 - integrator, 404
 - sources, 192
- Current-source biasing
- common-drain (CD) amplifier with, 211–212
 - defined, 192
 - examples of, 192–193
 - illustrated, 192
- Current-to-voltage converter. *See also* Op-amp circuits
- defined, 409, 750
 - illustrated, 410
- Cutoff
- BJT, 118–119
 - common-emitter (CE) amplifier, 141
 - defined, 750
 - JFET, 183
 - Q-point at, 272
 - Q-point closer to, 267
 - transistor switch, 153
- Cutoff voltage
- JFET, 182
 - pinch-off voltage versus, 182–183
- Cycle, 750
- Czocharlski method, 54
- ## D
- DACs. *See* Digital-to-analog converters
- Damping factor (DF), 432, 750
- Darlington feedback regulator example, 146–147
- Darlington pairs, 146
- Data communication system using FSK modem
- example
 - block diagram, 617
 - defined, 616
 - frequency-shift keying (FSK), 617–618
 - FSK data example, 618
 - illustrated, 616
 - phone line interface, 617
 - timing and control, 617
- Data conversion circuits, 631–679
- analog and digital interface, 643–646
 - analog switches, 632–638
 - A/D conversion, 651–665
 - D/A conversion, 646–651
 - F/V converters, 671–675
 - introduction to, 631
 - sample-and-hold amplifiers, 638–642
 - troubleshooting, 674–678
 - V/F converters, 666–671

- Data sheets
 - BJT, 132–135
 - defined, 91
 - diode, 91–95
 - JFET, 185
 - MOSFET, 197–198
 - op-amp, 317–323
 - power transistor, 280–281
 - dBm, 28, 750
 - dc beta (β_{DC}), 114–115, 750
 - dc quiescent power, 268
 - dc resistance, 4
 - dc restorers. *See* Clampers
 - dc voltages, testing, 33
 - Decibels (dB)
 - dBm, 28
 - defined, 24, 25, 750
 - as dimensionless quantity, 26
 - power ratios, 25–28
 - uses of, 27
 - voltage ratios, 28–29
 - Decoupling network, 750
 - De-emphasis network, 589
 - Demodulation
 - AM, 602–603
 - defined, 750
 - example, 603
 - FM, 610
 - Depletion mode, 750
 - Depletion MOSFETs (D-MOSFETs). *See also* Metal-oxide semiconductor FETs (MOSFETs)
 - bias, 202–203
 - common-source (CS) amplifier, 206–207
 - current-source biasing, 203
 - defined, 194
 - depletion mode, 194–195
 - enhancement mode, 195
 - modes, 194
 - source bias, 203
 - structure of, 194
 - symbols, 195
 - transfer characteristic, 195–196
 - voltage-divider with self-bias, 203
 - zero bias, 202
 - Depletion region, 750
 - Detectors
 - fiber optic proximity, 719
 - phase, 611–612
 - resistance temperature (RTDs), 708–711
 - superheterodyne AM receiver, 587
 - DF (damping factor), 432
 - Differential amplifiers (diff-amps). *See also* Operational amplifiers (op-amps)
 - circuit, 310
 - common-mode input, 313–314
 - common-mode rejection, 314
 - common-mode rejection ratio (CMRR), 314–316
 - current changes, 311
 - defined, 310, 750
 - differential input, 312–313
 - as input stage of op-amp, 316
 - internal arrangement of op-amp, 316
 - modes of single operation, 312–314
 - operation of, 310–312
 - output voltage, 317
 - single-ended input, 312
 - symbol, 310
 - voltage changes, 311
 - Differential input impedance, 750
 - Differential mode (diff-amp), 312–313, 751
 - Differential nonlinearity, 674–675
 - Differentiators (op-amp)
 - defined, 403, 751
 - example, 407–408
 - illustrated, 406
 - output, 407
 - with ramp input, 406
 - Digital codes, angle representation, 700–701
 - Digital electronics, 1
 - Digital multimeters (DMMs)
 - defective transistors and, 162–163
 - defined, 31–32
 - diode test position, 162
 - features, 32
 - illustrated, 32
 - nondefective transistors and, 162
 - testing transistors with, 161–163
 - Digital signals
 - analog signals and, 643–645
 - defined, 6, 751
 - examples of, 7
 - Digital storage oscilloscopes (DSOs), 33
 - Digital-to-analog (D/A) conversion, 646–651
 - defined, 644, 750
 - differential nonlinearity, 674–675
 - errors, 674–675
 - example, 400–401
 - low/high gain, 675
 - nonmonotonicity, 674
 - offset error, 675
 - Digital-to-analog converters (DACs)
 - accuracy, 650
 - binary-weighted-input, 646–648
 - cell phone example, 645–646
 - defined, 645, 646, 751
 - linearity, 650
 - monotonicity, 650
 - performance characteristics, 650–651
 - R/2R ladder, 648–650
 - resolution, 650
 - setting time, 651
 - test setup for, 674
 - testing, 674
 - Diode data sheet
 - defined, 91
 - electrical characteristics, 93
 - instantaneous voltage, 93
 - lead temperature, 94
 - maximum average value, 92
 - maximum current, 93
 - maximum forward voltage drop, 93
 - maximum peak value, 92
 - maximum reverse current, 94
 - maximum reverse dc voltage, 92
 - maximum reverse peak value, 92
 - maximum reverse peak voltage, 91
 - parameters, 91–94
 - ratings, 91, 92
 - Diode drop, 51
 - Diode models
 - ideal, 52
 - offset, 53
 - offset-resistance, 53–54
 - Diodes
 - bias circuits, 50–51
 - characteristic curve, 51–52
 - characteristics, 50–57
 - clampers, 76–77
 - defined, 751
 - IV characteristic curve, 4
 - light-emitting (LEDs), 84–89
 - limiters, 72–76
 - log amplifier with, 570–571
 - open, troubleshooting, 96–97
 - packages, 51
 - photodiodes, 89–91
 - shorted, 97–98
 - special-purpose, 78–91
 - symbol, 50–51
 - terminal identification, 51
 - testing, 52
 - varactor, 82–84
 - zener, 78–81
 - Direct coupling, 259
 - Direct-coupled amplifiers, 259–265
 - bias, 260
 - defined, 259
 - feedback voltage, 264
 - negative feedback for bias stability, 260–263
 - negative feedback for gain stability, 263–265
 - without feedback, 260
 - Direct-coupled preamps, 264
 - Discrete components, 307
 - Discrete devices, 751
 - Discrete point measurement, 450
 - Discriminators
 - defined, 751
 - superheterodyne FM receivers, 589
 - Displacement transducers, 718–719
 - Distortion
 - crossover, 273–275, 750
 - harmonic, 11
 - intermodulation (IMD), 11
 - DMMs. *See* Digital multimeters (DMMs)
 - Domain, 10, 751
 - Donors, 46
 - Doping, 46, 751
 - Double-ended operation (diff-amp), 312–313
 - Drain
 - characteristic curve, 181
 - defined, 751
 - voltage, 187
 - Drift, 510
 - Droop, 640, 751
 - Dropout voltage, 526
 - DSOs (digital storage oscilloscopes), 33
 - Dual-axis solar tracking, 226–227
 - Dual-gate MOSFETs, 197
 - Dual-slope ADC. *See also* Analog-to-digital converters (ADCs)
 - conversion, 661
 - counter, 660
 - defined, 660
 - illustrated, 660
 - Dummy gages, 714
 - Dynamic emitter resistance, 138, 751
 - Dynamic resistance, 4
- ## E
- Edge-emitting LEDs, 87
 - Efficiency
 - class A power amplifier, 270–271
 - complementary MOSFETs, 292
 - defined, 270, 751

- Electrocardiography (ECG), 246
 Electroluminescence, 84, 751
 Electromagnetic pulses (EMPs), 621
 Electromagnetic spectrum, 34
 Electron current, 45
 Electron flow, 4
 Electronic thermostat example, 644–645
 Electrons
 conduction, 43
 defined, 751
 energy, 43–46
 hole current and, 45
 orbits, 43
 valence, 43, 44, 754
 Electrostatic discharge (ESD), 278, 751
 Emitter, 751
 Emitter bias
 circuits illustration, 128
 defined, 128, 751
 example, 128–129
 Emitter-follower amplifiers. *See* Common-emitter (CE) amplifiers
 EMPs (electromagnetic pulses), 621
 Energy, 751
 Enhancement mode, 751
 Enhancement MOSFETs (E-MOSFETs). *See* also Metal-oxide semiconductor FETs (MOSFETs)
 bias, 203–204
 common-source (CS) amplifier, 207
 construction, 196
 defined, 196
 operation of, 196
 schematic symbols, 196, 197
 for switching applications, 216
 transfer characteristic, 197
 Equation derivations, 747–751
 base-emitter *pn* junction, 747
 CD amplifier gain, 747
 center frequency, 748
 feedback resistors current, 751
 open-loop gain, 748
 phase-shift oscillator attenuation, 749–751
 Equivalent circuits
 BJT, 135
 common-base (CB) amplifier, 148
 common-emitter (CE) amplifier, 137–138, 143
 transmission line, 248
 zener diode, 79–80
 ESD (electrostatic discharge), 278, 751
 External pass transistors
 heat sink, 533
 regulator operation, 533
 7800-series three-terminal regulator with, 532
- F**
 Far-infrared, 34
 Feedback oscillators, 464–482
 Armstrong, 480
 Clapp, 478–479
 Colpitts, 475–478
 conditions for oscillation, 465
 crystal-controlled, 480–482
 defined, 463, 751
 elements, 463
 Hartley, 479–480
 LC, 475–482
 phase-shift, 472–473
 positive feedback, 464
 RC, 466–474
 stability for, 469
 start-up conditions, 465–466
 twin-T, 473–474
 Wien-bridge, 466–472
 Feedback voltage, 264
 Feedforward compensation, 377, 751
 Feedthrough, 640
 FET Colpitts oscillator, 477
 FET linear amplifiers, 205–215
 common-drain (CD), 209–212
 common-gate (CG), 212–213
 common-source (CS), 206–208
 preamplifiers example, 214–215
 FET preamplifiers example
 defined, 214
 JFET preamp, 214–215
 MOSFET preamp, 215
 Fetal heartbeat monitors, 559
 Fiber optics
 absorption, 619
 angle of incidence, 619
 angle of reflection, 619
 critical angle, 619
 data communications link, 621
 defined, 618, 751
 index of refraction, 619
 modes of light propagation, 620–621
 multimode graded index, 621
 multimode step index, 620
 operation, 619
 scattering, 619
 single-mode step index, 620
 structure of, 619
 system preference, 621
 total internal reflection, 619
 Fiber-optic proximity detectors, 719
 Field-effect transistors (FETs), 177–229. *See* also FET linear amplifiers; Junction field-effect transistors (JFETs); Metal-oxide semiconductor FETs (MOSFETs)
 classification of, 179
 defined, 177, 178, 751
 electrical noise, 178
 family, 178–179
 input resistance, 178
 transconductance of, 205–206
 transfer characteristic, 205
 types of, 177
 Filters
 active, 425–454
 all-pass, 430
 band-pass, 428–429, 442–448
 band-stop, 429–430, 448–450
 cascaded, 436–437, 441
 defined, 425, 751
 high-pass, 427–428, 439–442
 low-pass, 426–427, 434–439, 752
 multiple-feedback, 443–444
 passband of, 426
 response characteristics, 431–434
 response measurements, 450–453
 Sallen-Key, 435–436, 440–441
 single-pole, 434, 439–440
 switched-capacitor, 449
 555 timers
 ASK test generator, 491–493
 astable operation, 488–490
 connected as astable multivibrators, 488
 monostable operation, 493–494
 as one-shots, 493–496
 operation as VCOs, 490–491
 as oscillators, 488–493
 Fixed negative linear regulators, 526
 Fixed positive linear regulators. *See* also IC regulators
 capacitors, 525
 defined, 525
 output currents, 526
 7800 series, 525–526
 thermal overload, 526
 Flash (simultaneous) ADC. *See* also Analog-to-digital converters (ADCs)
 defined, 655, 751
 example, 656–657
 illustrated, 655
 reference voltage, 656
 sampling rate, 656
 Floating point, 161, 751
 Flow rate measurement, 718
 FM. *See* Frequency modulation
 FM receivers (superheterodyne)
 audio and power amplifiers, 589
 block diagram, 589
 de-emphasis network, 589
 discriminator, 589
 limiter, 589
 local oscillator, 589
 mixer, 589
 RF amplifier, 589
 signal flow, 590
 FM stereo receiver example
 block diagram, 452
 channel separation circuits, 453
 defined, 451–452
 system description, 452
 FM transmitters, 609–610
 Fold-back current limiting
 defined, 515, 751
 regulator with, 515
 Forward bias, 49–50, 751
 Forward-reverse bias, 113
 Four-channel mixer/amplifier example
 defined, 401
 op-amps, 401–402
 schematic, 402
 XLR connectors, 401
 Fourier series, 11–12
 Fourier transform, 11
 Freescale Semiconductor MC34119, 295–296
 Frequencies, 751
 Frequency diversity, 447
 Frequency domain signals
 defined, 10
 Fourier series, 11–12
 harmonics, 10–11
 Frequency modulation (FM), 588–589, 607–610
 carrier frequency, 607
 defined, 607, 751
 demodulation, 610
 with VCO, 608
 Frequency response, op-amp, 322
 Frequency shifting, 259
 Frequency-shift keying (FSK), 617–618
 Frequency-to-voltage (*F/V*) converters

- AD650, 671–672
 applications, 665
 defined, 665, 671
 example illustration, 672
 illustrated, 671
 remote sensing application, 673
 in systems with rotating device, 673
 use of, 673
- FSK modems, 616–618
- Full-wave rectifiers
 center-tapped, 59–60
 defined, 59, 751
 example, 61
 illustrated, 59
 operation of, 62
 peak inverse voltage (PIV), 60
 turns ratio effect on, 60
- Fuses
 linear power supply example, 70
 open, troubleshooting, 96
- G**
- Gage factor (*GF*)
 defined, 714, 751
 illustrated, 715
 typical, 715
- Gain
 defined, 751
 measurement, 166
 power, 753
 stability, 263–265
- Gain-bandwidth product, 364–365
- Gate, 751
- General-purpose/small-signal transistors, 158
- Germanium, 44, 751
- H**
- Half-splitting, 31
- Half-wave rectifiers. *See also* Rectifiers
 defined, 57, 751
 example, 58–59
 operation, 58
- Harmonic distortion, 11
- Harmonics
 defined, 10, 751
 odd, 10–11
- Hartley oscillators
 defined, 479, 751
 frequency of oscillation, 479–480
 schematic, 479
 start-up conditions, 480
- Hazeltine neutralization, 251
- H-bridge motor control circuit, 227–228
- Heat dissipation, class A power amplifier, 265–266
- High-intensity LEDs. *See also* Light-emitting diodes (LEDs)
 in automotive lighting, 88
 displays, 88
 in home/business lighting applications, 88
 pixel formation, 88
 traffic lights, 87
 uses for, 86
- High-pass filters, 439–442. *See also* Active filters
 cascading, 441
 defined, 427, 751
 idealized curves, 428
 response, 427–428
- Sallen-Key, 440–441
 single-pole, 439–440
 sixth-order, 441
- Hole current, 45
- Holes, 751
- Hysteresis
 comparator operation with, 389–390
 defined, 389, 751
 example, 391
 positive feedback for, 389
- I**
- IC power amplifiers
 for audio applications, 293
 defined, 293
 LM384, 293–295
 MC34119, 295–296
- IC regulators. *See also* Regulators
 adjustable negative, 528
 adjustable positive, 527–528
 applications of, 532–538
 current limiting, 534–535
 current regulator, 535–536
 defined, 525
 external pass transistor, 532–534
 fixed negative, 526
 fixed positive, 525–526
 switching, 529–530
 switching regulator configuration, 537–538
 troubleshooting, 529
 variable dual-polarity power supply, 536–537
 wind turbine example, 530–531
- ICs. *See* Integrated circuits
- Ideal model, diode, 52
- IF amplifiers, 256–257
 AGC in, 605
 basic, 605–606
 basic function of, 604–605
 circuit configuration, 605
 defined, 604
 as frequency-selective circuit, 605
 front-end filters, 606
 function illustration, 604
 illustrated, 605
 superheterodyne AM receiver, 587
 superheterodyne FM receivers, 589
 as tuned amplifier, 601
- IGBT (insulated gate bipolar transistor), 204
- Impedances
 inverting amplifier, 335–336
 noninverting amplifier, 332–334
 voltage-follower, 334–335
- Index of refraction, 619
- Input bias current, 318, 751
- Input impedance
 high, 309
 infinite, 308
 inverting amplifier, 335
 noninverting amplifier, 332
 op-amp, 318
 voltage-follower, 334–335
- Input offset current, 319
- Input offset voltage
 defined, 317–318, 751
 drift, 318, 751
- Input resistance
 calculation formula, 140
 capacitively coupled amplifier, 242
- common-base (CB) amplifier, 149
 common-collector (CC) amplifier, 144
 common-drain (CD) amplifier, 209–210
 common-emitter (CE) amplifier, 139–140
 common-source (CS) amplifier, 207–208
 defined, 139
 JFET, 185–186
- Instantaneous voltage
 defined, 8
 diode data sheet, 93
- Instrument loading, 31
- Instrumentation amplifiers. *See also* Special-purpose amplifiers
 AD622, 551–552
 applications, 550
 configurations, 548–549
 defined, 548, 751
 with external gain-setting resistor, 549
 gain versus frequency, 551–552
 liquid level control system example, 553–554
 op-amps, 548
 in sensor signal amplification, 550
 shield guard driver, 550
 voltage gain, setting, 551
- Instrumentation system example, 356
- Insulated gate bipolar transistor (IGBT), 204, 751
- Integrated circuits (ICs). *See also* IC power amplifiers; IC regulators
 antilog amplifiers, 573
 defined, 293, 752
 FM transmitters, 609–610
 log amplifiers, 573
- Integrators (op-amp)
 capacitor charging, 403–404
 capacitor voltage, 404
 currents, 404
 defined, 403, 752
 example, 405–406
 illustrated, 403
 Miller, 405
 output voltage, 404
 rate of change of output, 405
- Intermediate frequency (IF), 255, 752. *See also* IF amplifiers
- Intermodulation distortion (IMD), 11
- Intrinsic (pure), 752
- Intrinsic silicon, 45
- Inverters, CMOS, 221
- Inverting amplifiers
 closed-loop gain, 329
 defined, 328, 752
 example, 329
 faults in, 341–342
 illustrated, 328
 impedances of, 335–336
 input impedance, 335
 open feedback resistor, 342
 open input resistor, 342
 output impedance, 335–336
 power supply, 341
- Inverting switching regulators. *See also* Switching regulators
 defined, 523
 inverting action, 524
 regulator action, 524
 schematic, 523
- Ions, 752

- Isolation amplifiers, 555–561. *See also* Special-purpose amplifiers
 applications, 559–560
 block diagram, 555
 capacitor-coupled, 555–557
 coupling types, 559
 defined, 555, 752
 fetal heartbeat monitors using, 559
 modulation, 556
 motor control example, 560–561
 transformer-coupled, 557–559
 wideband three-port, 560
- IV characteristic curves
 for diode, 4
 for resistors, 3
 for Thevenin circuit, 17
 zener diode, 78
- J**
- JFET stabilized oscillator, 469–471
- Junction field-effect transistors (JFETs)
 biasing, 186–193
 capacitance, 185–186
 characteristics, 179–186
 common-drain (CD) amplifier, 209
 common-gate (CG) amplifier, 213
 common-source (CS) amplifier, 206
 current sources, 192
 current-source biasing, 192–193
 cutoff voltage, 182
 data sheets, 185
 defined, 178, 752
 drain characteristic curve, 181
 drain source resistance, 470
 input resistance, 178, 185–186
 as linear amplifiers, 205–215
 n -channel, 180, 181
 operation of, 180–181
 pinch-off voltage, 182
 preamp, 214–215
 self-biasing, 186–188
 symbols, 181
 transconductance curves, 184–185
 V_{GS} , 182
 voltage-divider bias, 190–191
- K**
- Kirchhoff's current law (KCL), 114
 Kirchhoff's voltage law (KVL), 115, 261
- L**
- Large-signal type, 752
- Laterally diffused MOSFET (LDMOSFET), 223
- LC feedback oscillators
 Armstrong, 480
 Clapp, 478–479
 Colpitts, 475–478
 crystal-controlled, 480–482
 defined, 475
 Hartley, 479–480
- Leakage measurement, BJT, 166
- Leaky filter capacitors, 98–99
- Light-emitting diodes (LEDs). *See also* Diodes
 applications, 85–88
 in automotive lighting, 88
 baseball counting system example, 86
 defined, 84, 752
 displays, 88
 edge-emitting, 87
 electroluminescence, 84
 in fiber optic telecommunication systems, 87
 high-intensity, 86–88
 in home/business lighting applications, 88
 operation of, 85
 in pixel formation, 88
 semiconductive materials, 84
 7-segment display, 86
 superradiant, 87
 surface-emitting, 87
 in traffic lights, 87
- Limiters
 application, 73
 defined, 72, 752
 example, 75–76
 limiting level adjustment, 74–76
 negative, 75
 positive, 75
 superheterodyne FM receivers, 589
- Line regulation, 507–508, 752
- Linear amplifiers
 defined, 20–21
 FET, 205–215
 transfer curve, 21
- Linear components, 2–3, 752
- Linear equations, 2
- Linear multipliers
 AD532, 591
 as balanced modulators, 596–597
 defined, 590
 in demodulation, 602–603
 mixers as, 600–602
 quadrants, 591
 scale factor, 592
 transfer function, 592
- Linear power supply example
 defined, 69–70
 filter capacitor, 70–71
 fuse, 70
 rectifier bridge, 70
 regulated DC power supply, 71–72
 transformer, 70
- Linear regulators, 510, 752
- Linear variable differential transformers (LVDTs), 718
- Linearity
 DAC, 650
 defined, 752
- Line-of-sight transmission, 447
- Liquid level control system example
 block diagram, 553
 circuit, 554
 defined, 553
 level-sensing method, 553
 operation, 554
 schematic diagram, 554
- LM384. *See also* IC power amplifiers
 defined, 293
 dual-in-line packages, 293
 example, 295
 inputs, 294
 operation of, 294
 power output, 294
- LM386 audio-power amplifier
 as AM audio power amplifier, 607
 application, 607
 defined, 606
 pin configuration, 606
- LM13700, 564–565
- Load lines
 BJT, 119–120
 common-emitter (CE) amplifier, 140–142
 complementary symmetry push-pull amplifier, 276
 defined, 17, 752
 illustrated, 18
- Load regulation
 calculation of, 508
 defined, 69, 508, 752
 formula, 508
 as percentage change in output voltage, 509
- Loading effects, capacitively coupled amplifier, 241–244
- Local oscillators
 superheterodyne AM receiver, 587
 superheterodyne FM receivers, 589
- Lock range, 615
- LOG102 amplifier, 573
- Logarithmic (log) amplifiers. *See also* Special-purpose amplifiers
 with BJT, 571
 defined, 569
 with diodes, 570–571
 IC, 573
 multipliers with, 574–576
 signal compression, 573–574
- Logarithms
 bases, 24–25
 defined, 24, 569, 752
 exponential of, 572
 natural, 569, 752
- Log-ratio amplifiers, 573
- Loop gain, 366, 752
- Low-dropout (LDO) regulators, 526
- Lower trigger point (LTP), 389
- Lower-side frequency, 596
- Low-pass filters, 434–439. *See also* Active filters
 cascaded, 436–437
 class D power amplifier, 292
 critical frequency, 426–427
 defined, 426, 752
 ideal response, 426
 response, 426–427
 response curves, 426–427
 RFID system example, 437–439
 Sallen-Key, 435–436
 single-pole, 434
- LTP (lower trigger point), 389
- LVDT displacement transducers, 718
- LVDTs (linear variable differential transformers), 718
- M**
- Majority carriers, 46
- MAX2606 VCO, 609–610
- MC34119, 295–296
- Mean, 752
- Measurement
 angle, 697–703
 flow rate, 718
 motion, 718–720
 pressure, 716–718
 strain, 713–716
 temperature, 703–713
- Metal-oxide semiconductor FETs (MOSFETs).
See also MOSFET switching circuits

- biasing, 202–204
- characteristics, 194–201
- common-gate (CG) amplifier, 213
- complementary, 291–292
- data sheet, 197–198
- defined, 178, 752
- D-MOSFET, 194–196
- D-MOSFET bias, 202–203
- dual-gate, 197
- dual-gate mixer, 256
- E-MOSFET, 196–197
- E-MOSFET bias, 203–204
- IGBT, 204
- input resistance, 178–179
- LDMOSFET, 223
- as linear amplifiers, 205–215
- pH sensor circuit example, 199–201
- preamp, 215
- solar tracking system example, 224–228
- TMOSFET, 223, 224
- uses for, 178
- VMOSFET, 223, 224
- Microcontrollers, 724, 752
- Microconverters, 711
- Mid-infrared, 34
- Miller effect, 250
- Miller integrator, 405
- Minority carriers, 46
- Mixers, 607–610
 - defined, 600–602, 752
 - dual-gate MOSFET, 256
 - frequency examples, 601
 - function, 600–602
 - as linear multipliers, 600–602
 - superheterodyne AM receiver, 587
 - superheterodyne FM receivers, 589
- Modems
 - defined, 752
 - FSK, 616–618
- Modulation. *See also* Amplitude modulation (AM); Frequency modulation (FM)
 - balanced, 595–596, 749
 - defined, 556, 752
 - illustrated, 556
 - suppressed-carrier, 596
- Monostable operation, 752
- Monotonicity
 - DAC, 650
 - defined, 752
- MOSFET push-pull amplifiers, 278–281
 - class AB, 279
 - defined, 278
 - electrostatic discharge (ESD), 278
 - example, 279–280
 - power transistor data sheet, 280–281
- MOSFET switching circuits. *See also* Metal-oxide semiconductor FETs (MOSFETs)
 - advantages of, 216
 - analog multiplexer, 219
 - analog switch, 217–218
 - applications, 218–220
 - CMOS application, 220–222
 - ideal switch, 216–217
 - illustrated, 217
 - operation of, 216–217
 - power structures, 222–224
 - power switching applications, 222
 - sampling circuit, 218
 - switched-capacitor circuit, 219–220
- MOSFETs. *See* Metal-oxide semiconductor FETs
- Motion-measuring circuits. *See also* Measurement
 - acceleration transducers, 719–720
 - displacement transducers, 718–719
 - velocity transducers, 719
- Motor control system example, 560–561
- MSP430 microcontroller, 724
- Multimode graded index, 621
- Multimode step index, 620
- Multiple-channel analog switches, 634–636
- Multiple-feedback filters
 - band-pass, 443–444
 - band-stop, 448
- Multiplexers
 - analog, 634–635
 - MOSFET switching circuit, 219
- Multipliers
 - applications, 593
 - block diagram, 574
 - defined, 574
 - four-quadrant, 751
 - illustrated, 575
 - linear, 590–593
 - with log and antilog amplifiers, 574–576
 - quadrants, 591
- Multivibrators
 - astable, 488–490
 - one-shot, 493–496
- Music signals, amplitude modulation with, 599
- N**
- NAND gates, CMOS, 221
- National Semiconductor LM384, 293–295
- Natural logarithms, 569, 752
- Near-infrared, 34
- Negative feedback
 - for bias stability, 260–263
 - defined, 323, 752
 - effect on bandwidth, 363–364
 - functioning of, 323–324
 - for gain stability, 263–265
 - illustrated, 323
 - op-amp configurations with, 325–331
 - reasons for using, 324
- Negative temperature coefficient (NTC), 711
- Neutralization
 - defined, 250, 752
 - Hazeltine, 251
- Noise
 - analysis, 339
 - in circuits, 246
 - defined, 752
 - effects, reducing with hysteresis, 389–391
 - frequency, 337
 - input, 339
 - input, effect on comparator operation, 388–389
 - at low frequencies, 337
 - op-amp, 337–339
 - output, 339
 - pink, 337
 - power distribution of, 338
 - source contributors, 339
 - sources, 609
 - in VCOs, 609
 - voltage, 338, 388–389
- Noise voltages, 246
- Noninverting amplifiers
 - closed-loop gain, 326, 327
 - defined, 326, 752
 - example, 327
 - faults in, 340–341
 - feedback fraction, 326–327
 - illustrated, 326
 - impedances of, 332–334
 - input impedance, 332
 - internally open input, 341
 - open feedback resistor, 340
 - open input resistor, 341
 - output impedance, 332–334
 - voltage-follower, 327–328
- Nonlinear amplifiers, 21–22
- Nonlinearity, differential, 674–675
- Nonmonotonicity, 674, 752
- Nonzero-level detection, 387–388
- NOR gates, CMOS, 221–222
- Norton's theorem, 16, 752
- NTC (negative temperature coefficient), 711
- Nyquist rate, 653, 752
- O**
- Odd harmonics, 10–11
- Offset error, 675, 677
- Offset model, diode, 53
- Offset-resistance model, diode, 53–54
- Ohmic region, 181, 752
- One-shots
 - defined, 493, 752
 - delayed output pulse, 495
 - 555 timers as, 493–496
 - for time delay, 495–496
 - timing, 494
- One-transistor switching circuits, 154–155
- Op-amp circuits, 385–415. *See also* Operational amplifiers (op-amps)
 - comparators, 386–396
 - constant-current source, 409
 - current-to-voltage converter, 409–410
 - differentiators, 406–408
 - integrators, 403–406
 - peak detector, 410–411
 - summing amplifiers, 396–402
 - troubleshooting, 411–415
 - voltage-to-current converter, 410
- Op-amp responses. *See also* Operational amplifiers (op-amps)
 - closed-loop gain, 355
 - closed-loop response, 363–365
 - compensation and, 371–377
 - concepts, 355
 - gain as frequency dependent, 357
 - gain-versus-frequency analysis, 358–359
 - instrumentation system example, 356
 - loop gain, 366
 - open-loop bandwidth, 357
 - open-loop gain, 355
 - open-loop response, 361–362
 - oscillations, 370
 - phase margin, 366–367
 - phase shift, 359–360
 - positive feedback, 366
 - programmable gain amplifier, 359
 - stability analysis, 367–370
 - unity-gain bandwidth, 357

- Open diodes
 - effects in bridge rectifier, 97
 - symptoms in full-wave center-tapped rectifier, 97
 - troubleshooting, 96–97
 - Open-loop, 752
 - Open-loop bandwidth, 357
 - Open-loop gain, 320
 - closed-loop gain comparison, 364
 - closed-loop gain intersection, 369
 - defined, 355
 - illustrated, 355
 - Open-loop response (op-amp)
 - defined, 361
 - frequency response, 361–362
 - phase response, 362
 - Open-loop voltage gain, 752
 - Operational amplifiers (op-amps), 307–342.
 - See also* Op-amp circuits; Op-amp responses
 - bipolar, 338
 - closed-loop critical frequency, 363
 - closed-loop voltage gain, 325
 - CMRR, 320
 - common-mode input voltage range, 319
 - compensation, 371–377
 - configurations with negative feedback, 325–331
 - data sheet parameters, 317–323
 - defined, 308, 752
 - designing with, 325
 - differential, 310–316
 - faults in inverting amplifier, 341–342
 - faults in noninverting amplifier, 340–341
 - faults in voltage-follower, 341
 - frequency response, 322
 - ideal, 308–309
 - impedances for noninverting amplifier, 332–334
 - impedances of inverting amplifier, 335–336
 - input bias current, 318
 - input impedance, 318
 - input offset current, 319
 - input offset voltage, 317–318
 - input offset voltage drift with temperature, 318
 - internal block diagram, 316
 - inverting amplifier, 328–329
 - negative feedback, 323–325
 - noise, 337–339
 - noninverting amplifier, 326–328
 - as nonzero-level detector, 387
 - open-loop voltage gain, 320
 - other features, 323
 - output impedance, 319
 - packages, 308
 - parameter comparison, 322
 - phase-shift oscillators, 472
 - practical, 309
 - in RF systems, 325
 - series regulator, 512
 - signal-to-noise ratio, 339
 - slew rate, 320–321
 - spectrophotometer system example, 330–331
 - symbol, 308
 - terminals, 308
 - troubleshooting, 340–342
 - uncompensated, 361–362
 - voltage-follower, 327–328
 - voltage-follower impedances, 334–335
 - as zero-level detector, 386
 - Operational transconductance amplifiers (OTAs). *See also* Special-purpose amplifiers
 - amplitude modulator, 565–567
 - applications, 565–567
 - basic circuits, 563–564
 - defined, 561, 752
 - as inverting amplifier, 563
 - LM13700, 564–565
 - Schmitt trigger, 567
 - symbol, 561
 - synthesized sine-wave generator example, 568
 - transconductance as function of bias current, 562
 - transconductance as gain, 561–562
 - Oscillation conditions
 - Colpitts oscillator, 476
 - defined, 465
 - illustrated, 476
 - Wien-bridge oscillator, 468
 - Oscillations
 - capacitively coupled amplifier, 245–246
 - defined, 464
 - from interference, 370
 - neutralization, 250
 - RF amplifier, 250
 - start of, 465–466
 - unwanted, troubleshooting, 370
 - Oscillators, 462–493
 - Armstrong, 480
 - Clapp, 478–479
 - Colpitts, 475–478
 - concept illustration, 463
 - crystal-controlled, 480–482
 - defined, 462, 463, 752
 - feedback, 463, 464–482
 - 555 timers as, 488–493
 - Hartley, 479–480
 - LC, 475–482
 - output, 462
 - phase-shift, 472–473
 - RC, 466–474
 - relaxation, 464, 482–487
 - SAW, 487
 - square-wave, 486–487
 - start-up conditions, 465–466
 - triangular-wave, 482–484
 - twin-T, 473–474
 - types of, 463–464
 - voltage-controlled (VCO), 484–486
 - Wien-bridge, 466–472
 - Oscilloscopes
 - plotting characteristic curves on, 51–52
 - in tuning RF amplifiers, 257
 - OTAs. *See* Operational transconductance amplifiers
 - Output bounding
 - comparator, 391–393
 - defined, 391
 - example, 392–393
 - illustrated, 391
 - Output impedance
 - defined, 752
 - inverting amplifier, 335–336
 - low, 309
 - noninverting amplifier, 332–334
 - op-amp, 319
 - voltage-follower, 334–335
 - zero, 308
 - Output power
 - class A power amplifier, 268–270
 - class C power amplifier, 287
 - LM384, 294
 - Output resistance
 - capacitively coupled amplifier, 242
 - common-base (CB) amplifier, 149–151
 - common-collector (CC) amplifier, 144
 - common-emitter (CE) amplifiers, 140
 - Output voltage
 - bridge rectifiers, 62
 - differential amplifier, 317
 - integrators, 404
 - phase detectors, 611
 - step-down switching regulators, 521
 - Open-temperature sensing circuit example, 394
- ## P
- PA system power amplifier example, 281–282
 - defined, 281
 - illustrated, 282
 - power amplifier circuit, 282
 - Passband, 752
 - Peak detector, 410–411, 752
 - Peak inverse voltage (PIV)
 - bridge rectifiers, 62
 - defined, 49
 - full-wave rectifier, 60
 - Percent regulation, 68
 - Period, 7, 8, 752
 - Periodic signals, 752
 - defined, 10
 - frequency, 8
 - period, 7, 8
 - sinusoidal waves, 7, 8–9
 - PH sensor circuit example
 - defined, 199
 - handling precautions, 201
 - illustrated, 199
 - sensor circuit, 200
 - simulation, 200–201
 - waste treatment steps, 199
 - Phase angle, 753
 - Phase detectors
 - defined, 611
 - operation, 611
 - output voltage, 611
 - in PLLs, 611–612
 - Phase lag compensation, 371, 372
 - Phase margin, 366–367
 - defined, 367, 753
 - positive, 367, 368, 369
 - zero/negative, 367
 - Phase shift
 - defined, 359, 753
 - example, 359–360
 - Phase-locked loops (PLLs)
 - action when incoming frequency decreases, 614
 - action when incoming frequency increases, 615
 - block diagram, 611
 - capture range, 615
 - concept, 610–611
 - conditions for lock acquisition, 616
 - data communication with FSK modem example, 616–618

- defined, 610, 753
 - general operation, 611
 - lock range, 615
 - in lock under static conditions, 614
 - operation, 614–616
 - phase detector, 611–612
 - VCO, 612–613
 - Phase-shift oscillators, 472–473, 753
 - Photodiodes. *See also* Diodes
 - characteristics, 90
 - defined, 89, 753
 - illustrated, 89
 - operation of, 91
 - reverse current, 90
 - Photovoltaic effect, 54
 - Piezoelectric effect
 - defined, 753
 - quartz crystal, 481
 - Pinch-off voltage
 - cutoff versus, 182–183
 - defined, 182, 753
 - JFET, 182
 - PIV. *See* Peak inverse voltage (PIV)
 - Pixels, LED, 88
 - PLLs. *See* Phase-locked loops
 - P_n* junctions
 - defined, 47, 753
 - depletion region, 47
 - formation, 47
 - solar power systems example, 54–56
 - Pnp* transistors, 127
 - Pole, 753
 - Positive feedback
 - defined, 366, 753
 - occurrence, 366
 - oscillation, 464
 - Wien-bridge oscillator, 468
 - Positive temperature coefficient (PTC), 711
 - Power amplifiers, 265–293. *See also* Amplifiers
 - class A, 265–271, 750
 - class AB, 750
 - class B, 272–283, 750
 - class C, 283–289
 - class D, 289–293
 - IC, 293–296
 - PA system example, 281–282
 - superheterodyne AM receiver, 587
 - superheterodyne FM receivers, 589
 - Power control, 720–724
 - microcontrollers, 724
 - silicon-controlled rectifier, 720–722
 - thyristor, 720
 - triac, 722–723
 - zero-voltage switch, 723–724
 - Power dissipation, class C power amplifier, 284–285
 - Power gain
 - class A power amplifier, 267–268
 - computation formulas, 267
 - defined, 753
 - Power MOSFETs
 - laterally diffused MOSFET (LDMOSFET), 223
 - structures, 222–224
 - switching applications, 222
 - TMOSFET, 223, 224
 - V-groove MOSFET (VMOSFET), 223, 224
 - Power ratios, 25–28
 - Power supplies
 - DC, regulated, 71–72
 - defined, 753
 - example, 69–72
 - importance, 69
 - linear, 69–72
 - regulated, 99
 - switched-mode (SMPS), 67
 - troubleshooting, 95–99
 - with variable output voltage, 68
 - Power transistors
 - defined, 158
 - illustrated, 159
 - Preamplifiers example
 - defined, 214
 - JFET preamp, 214–215
 - MOSFET preamp, 215
 - Preemphasis, 589
 - Pressure transducers. *See also* Measurement
 - absolute, 716
 - applications, 718
 - circuit and symbols, 717
 - defined, 716
 - differential, 716–717
 - flow rate measurement, 718
 - foil strain gage, 716
 - types of, 717
 - Problem answers, odd-numbered problems, 753–761
 - Programmable gain amplifiers
 - closed-loop gain, 355
 - defined, 753
 - response, 359
 - PTC (positive temperature coefficient), 711
 - Pulse-width modulation (PWM)
 - defined, 290
 - frequency spectra, 291
 - modulator, 290
 - sine wave, 290
 - Push-pull amplifiers
 - complementary symmetry, 276
 - defined, 753
 - MOSFET, 278–281
 - single-ended, 277
 - Push-pull operation, 272–273
 - PWM. *See* Pulse-width modulation
- ## Q
- Q-point
 - BJT, 121
 - class A power amplifier, 266–267
 - closer to cutoff, 267
 - closer to saturation, 267
 - common-emitter (CE) amplifier, 140–141
 - at cutoff, 272
 - Quality factor, 753
 - Quantization, 6, 753
 - Quantization error
 - ADC, 653–654
 - avoiding with sample-and-hold amplifier, 654
 - defined, 653, 753
 - Quartz crystal, 481
 - Quiescent point, 17, 753
- ## R
- R/2R* ladder DAC. *See also* Digital-to-analog converters (DACs)
 - analysis of, 649
 - defined, 648
 - illustrated, 649
 - monolithic IC with, 650
 - Radio frequency interference (RFI), 753
 - Radiometric images, 34
 - RC coupled amplifiers. *See* Capacitively coupled amplifiers
 - RC feedback oscillators. *See also* Feedback oscillators
 - defined, 466
 - phase-shift, 472–473
 - twin-T, 473–474
 - use of, 466
 - Wien-bridge, 466–472
 - RDCs. *See* Resolver-to-digital converters
 - Recombination, 753
 - Rectification, 42
 - Rectifiers, 57–62
 - bridge, 61–62, 97, 98
 - defined, 57, 753
 - filters, 63–65
 - full-wave, 59–61
 - half-wave, 57–59
 - selection based on maximum ratings, 94
 - silicon-controlled, 721–722, 753
 - Reference thermocouples, 705
 - Regulated power supplies, 99
 - Regulation
 - defined, 754
 - line, 507–509, 752
 - load, 69, 508–509, 752
 - percent, 68
 - voltage, 507–509
 - zener diode, 80–81
 - Regulators, 506–539
 - adjustable, 68
 - current, 535–536
 - darlington feedback, 146–147
 - defined, 66, 506, 753
 - dropout voltage, 526
 - examples of, 67–68
 - IC, 66–67, 525–538
 - introduction to, 506
 - linear, 510, 752
 - low-dropout (LDO), 526
 - series, 510–515
 - shunt, 515–518
 - step-down, 519–521
 - switching, 519–525, 754
 - three-terminal, 67–68
 - Relaxation oscillators, 482–487
 - defined, 464, 753
 - square-wave, 486–487
 - triangular-wave, 482–484
 - voltage-controlled (VCO), 484–486
 - Remote sensing application, 673
 - Resistance. *See also* Input resistance; Output resistance
 - ac, 3–4
 - dc, 4
 - defined, 4
 - dynamic, 4
 - switched-capacitor circuit emulation, 220
 - Thevenin, 140
 - troubleshooting, 31
 - Resistance temperature detectors (RTDs). *See also* Temperature measurement
 - block diagram, 711
 - defined, 708, 753
 - employment methods, 708

- Resistance temperature detectors (RTDs)
(*continued*)
example, 710–711
illustrated, 710
temperature-sensing circuits, 709–710
3-wire bridge and, 708–709
uses for, 708
- Resistors
feedback, open, 340, 342
input, open, 341, 342
swamping, 148–149
- Resolution
ADC, 651–652
DAC, 650
defined, 753
- Resolvers
defined, 698, 753
voltages, 698
- Resolver-to-digital converters (RDCs)
AD2S90, 701–702
defined, 698, 753
operation, 698–700
Scott T-transformer, 699
simplified diagram, 699
specific, 701–702
wind-direction system example, 702–703
- Reverse bias
defined, 49, 753
peak inverse voltage (PIV), 49
reverse breakdown, 49–50
- Reverse breakdown, 49–50
- RF amplifiers, 247–252
defined, 247
superheterodyne AM receiver, 587
superheterodyne FM receivers, 589
terminating transmission lines, 249
transmission lines, 247–249
tuned, 250–251
tuning with oscilloscope, 257
- RF transistors
defined, 159
illustrated, 160
- RFI (radio frequency interference), 753
- RFID system example, 437–439
band-pass filters, 445
block diagram, 438
defined, 437
input block, 445
reader block diagram, 438
- Ripple voltage
comparison, 64
defined, 63, 753
- Rms voltmeters, 696
- Rms-to-DC converters, 692–696
AD637, 694–695
AGC circuits, 696
application examples, 696
averaging circuit, 692–693
complete, 693–694
conversion, 692–693
defined, 692
explicit type of, 693
implicit type of, 694
rms voltmeters, 696
square root circuit, 693
squaring circuit, 692
- Roll-off rate
active filters, 433
defined, 753
- Root mean square (RMS), 692, 753. *See also*
Rms-to-DC converters
- Rotor, 697, 753
- RTDs. *See* Resistance temperature detectors
- S**
- Sallen-Key filters
high-pass, 440–441
low-pass, 435–436
- Sample-and-hold amplifiers, 638–642
acquisition time, 640
action of, 638
AD585, 641–642
aperture jitter, 640
aperture time, 640
in avoiding quantization error, 654
basic, 638–639
defined, 638, 753
droop, 640
feedthrough, 640
illustrated, 638
performance specifications, 640–641
sample device, 641–642
specifications illustration, 641
tracking during sample time, 639–640
use of, 640
- Sampling
circuits, 218
defined, 6, 753
theory, 652
- Saturation
BJT, 118–119
common-emitter (CE) amplifier, 141
defined, 753
Q-point closer to, 267
transistor switch, 153–154
- Scale factors, 592
- Scaling adder, 399–400
- Scattering, 619
- Schmitt triggers
defined, 390, 753
OTA, 567
- Scott T-transformer, 699
- SCRs. *See* Silicon-controlled rectifiers
- SDCs. *See* Synchro-to-digital converters
- Seebeck voltage, 703
- Selectivity, 425
- Self-biasing
drain voltage determination, 187
drain-to-source voltage, 187
example, 187–188
illustrated, 187
JFETs, 186–188
negative feedback, 188
- Semiconductors
atomic structure, 43–46
conductor difference, 44–45
defined, 44, 753
- Sensor-controlled solar tracking,
226–227
- Series regulators. *See also* Regulators
connections, 511
with constant-current limiting, 514
defined, 510
with fold-back current limiting, 515
illustrated, 512
op-amp, 512
regulated output voltage, 513
regulating action, 511–513
short-circuit and overload protection, 514
voltage references, 510–511
- Settling time, 651, 753
- Shell, 753
- Shorted capacitors, 98–99
- Shorted diodes. *See also* Diodes
defined, 97
effect in bridge rectifier, 98
troubleshooting, 97–98
- Shunt regulators. *See also* Regulators
block diagram, 516
defined, 516
schematic, 516
sequence of responses, 517
short-circuit protection, 517–518
- Signal compression
concept illustration, 574
defined, 573, 753
with logarithmic amplifiers, 573–574
- Signal flow, class D power amplifier, 292
- Signal sources
independent, 14
load lines and, 17–18
Norton's theorem and, 16
Thevenin's theorem and, 14–15
- Signals. *See also* Analog signals; Digital
signals
continuous, 5
discrete, 5
frequency-domain, 10
periodic, 7–9
time-domain, 10
- Signal-to-noise ratio
defined, 338
solving for, 339
- Silicon
conductivity of, 46
defined, 44, 753
doped, 46
intrinsic, 45
- Silicon-controlled rectifiers (SCRs)
characteristic curves, 721
connections, 721
defined, 720–721, 753
illustrated, 721
turning off, 722
turning on, 722
- Single-axis solar tracking, 225
- Single-capacitor compensation. *See also*
Compensation
closed-loop configuration, 376–377
defined, 375–376
example illustration, 376
- Single-ended mode (diff-amp), 312, 753
- Single-mode step index, 620
- Single-pole filters
high-pass, 439–440
low-pass, 434
- Single-slope ADC. *See also* Analog-to-digital
converters (ADCs)
counter, 660
defined, 659
illustrated, 659
- Single-supply operation, class B power
amplifier, 276–277
- Sinusoidal waves
average value of, 8–9
defined, 7
effective value of, 9

- generation of, 7
 - instantaneous value of, 8
 - peak value of, 8
 - Skin effect, 249, 753
 - Slew rate
 - defined, 320, 753
 - example, 321
 - illustrated, 321
 - measurement, 320–321
 - SMPSs (switch-mode power supplies), 67
 - Solar panel control system example
 - block diagram, 637
 - defined, 636
 - illustrated, 636
 - timing diagram, 637
 - Solar power systems example
 - with battery backup, 56
 - solar cell panels, 55–56
 - solar cell structure, 54–55
 - Solar tracking system example
 - defined, 224
 - dual-axis solar tracking, 226–227
 - H-bridge motor control circuit, 227–228
 - MOSFETs, 224–228
 - sensor-controlled solar tracking, 226–227
 - single-axis solar tracking, 225
 - Soldering, 31
 - Source, 753
 - Source-follower, 209–210
 - Special-purpose amplifiers, 547–576
 - instrumentation, 548
 - isolation, 555–561
 - log and antilog, 569–576
 - operational transconductance, 561–568
 - types of, 547
 - Spectrophotometer system example
 - defined, 330
 - description, 330–331
 - illustrated, 330
 - photocell response curve, 331
 - photocell/amplifier PCB layout, 330
 - Spectrum
 - defined, 10, 754
 - electromagnetic, 34
 - Square root circuits, 693
 - Square-wave oscillators
 - defined, 486
 - schematic, 487
 - waveforms, 487
 - Squaring circuits, 692
 - Stability
 - analysis, 367–370
 - criteria summary, 370
 - defined, 367, 754
 - problems, 370
 - Stages, 754
 - Stairstep-ramp ADC. *See also* Analog-to-digital converters (ADCs)
 - defined, 657
 - example, 658
 - illustrated, 657
 - speed, 657–658
 - Standard amplitude modulation
 - block diagram, 598
 - defined, 597
 - example, 598–599
 - output frequency spectrum, 597
 - signal expression, 597
 - summing circuit implementation, 598
 - Standing waves, 249, 754
 - Start-up conditions
 - Colpitts oscillator, 476
 - defined, 465–466
 - Hartley oscillator, 480
 - Wien-bridge oscillator, 468–470
 - State-variable band-pass filter
 - defined, 445
 - example, 446–447
 - illustrated, 446
 - operation of, 446
 - optimization constraints, 446
 - outputs, 445
 - response curves, 446
 - State-variable band-stop filter, 448–449
 - Static errors, 695
 - Stator, 697, 754
 - Step-down switching regulators. *See also* Switching regulators
 - configuration, 538
 - defined, 519
 - output voltage, 521
 - regulating action, 521
 - schematic, 520
 - waveforms, 520
 - Step-up switching regulators. *See also* Switching regulators
 - basic action, 522
 - configuration, 538
 - defined, 521
 - schematic, 522
 - switching action, 522
 - voltage regulation, 523
 - Stimulus-response testing, 32
 - Strain
 - compressive, 713
 - defined, 713, 754
 - examples, 713
 - tensile, 713
 - Strain gages. *See also* Measurement circuits, 715–716
 - defined, 713–714, 754
 - dummy gage, 714
 - formula, 714
 - gage factor of, 714–715
 - illustrated, 714
 - Successive-approximation ADC. *See also* Analog-to-digital converters (ADCs)
 - conversion cycle steps, 662–663
 - defined, 662, 754
 - illustrated, 662
 - Summing amplifiers, 396–402
 - averaging, 398–399
 - component failure symptoms, 413–414
 - defined, 396, 754
 - digital-to-analog (D/A) conversion example, 400–401
 - four-channel mixer/amplifier example, 401–402
 - with gain greater than unity, 398
 - with n inputs, 397
 - scaling adder, 399–400
 - troubleshooting, 413–414
 - two-input, 397
 - with unity gain, 397–398
 - Superheterodyne receivers
 - AM, 586–588
 - defined, 586
 - FM, 589–590
 - Superradiant LEDs, 87
 - Suppressed-carrier modulation, 596–597
 - Surface acoustic wave (SAW) oscillators, 487
 - Surface-emitting LEDs, 87
 - Surge current, 65
 - Swamping resistors, 148–149
 - Swept frequency measurement, 450–451
 - Switched-capacitor circuit
 - defined, 219
 - illustrated, 219
 - resistance emulation, 220
 - as resistor replacement, 220
 - Switches
 - analog, 632–638
 - defined, 754
 - transistor, 152–157
 - Switching amplifiers, 21
 - Switching regulators. *See also* Regulators configurations, 537–538
 - defined, 519, 754
 - efficiency, 519
 - IC, 529–530
 - power levels range, 519
 - step-down configuration, 519–521
 - step-up configuration, 521–523
 - voltage-inverter configuration, 523–524
 - Switch-mode power supplies (SMPSs), 67
 - Synchros
 - defined, 697, 754
 - format voltages illustration, 698
 - illustrated, 697
 - voltages, 697
 - Synchro-to-digital converters (SDCs)
 - defined, 698, 754
 - operation, 698–700
 - Scott T-transformer, 699
 - Synthesized sine-wave generator example, 568
- ## T
- Temperature control system example
 - defined, 129
 - illustrated, 129
 - operation of, 130
 - temperature-to-voltage conversion circuit, 130
 - Temperature measurement, 703–713
 - resistance temperature detectors (RTDs), 708–711
 - sensor types, 703
 - thermistors, 711–712
 - thermocouple, 703–708
 - Tensile strain, 713
 - Terminals, 754
 - Testing
 - ADCs, 676
 - DACs, 674
 - dc voltages, 33
 - diodes, 52
 - equipment, 31–33
 - stimulus-response, 32
 - Thermal overload, 526, 754
 - Thermal runaway, 275
 - Thermal shunting, 708
 - Thermistors. *See also* Temperature measurement application, 712
 - in bridges, 712
 - in constant-current drive configurations, 712
 - defined, 65, 711, 754
 - negative temperature coefficient (NTC), 711
 - positive temperature coefficient (PTC), 711
 - response comparison, 712

- Thermocouples. *See also* Temperature measurement
- cold junction, 704
 - compensation, 707
 - defined, 703, 754
 - electronics interface, 704
 - electronics interface example, 705–707
 - example, 706–707
 - output, 704
 - reference, 705
 - Seebeck voltage, 703
 - signal conditioners, 707
 - thermal shunting, 708
 - unwanted, 704
- Thermography
- imager, 35
 - radiometric images, 34
 - in system fault diagnosis, 33–35
- Thevenin's theorem
- for dc circuit, 14
 - defined, 14, 754
 - use of, 15
- 3-wire bridge, 708–709
- Thyristors, 720, 754
- Time-domain signals, 10
- TMOSFET, 223, 224
- Tone generator example, 471–472
- Total internal reflection, 619
- Tracking ADC. *See also* Analog-to-digital converters (ADCs)
- defined, 658
 - illustrated, 658
 - reference voltage, 659
 - tracking action, 659
- Transconductance
- defined, 561, 754
 - of FETs, 205–206
 - as function of bias current, 562
 - as gain of OTA, 561–562
- Transconductance curves
- defined, 184
 - JFET, 184–185
- Transducers
- acceleration, 719–720
 - active, 18
 - defined, 18, 691, 754
 - displacement, 718–719
 - importance of, 691
 - passive, 18
 - pressure, 716–718
 - velocity, 719
- Transfer characteristics
- D-MOSFET, 195–196
 - E-MOSFET, 197
 - FET, 205
- Transfer curves
- defined, 20, 754
 - FET versus BJT, 205
 - linear amplifier, 21
- Transfer function, 592
- Transformer coupling, class B power amplifier, 273
- Transformer-coupled amplifiers. *See also* Amplifiers
- crossover distortion, 275
 - dc parameters, 257
 - dc signal isolation, 252
 - decoupling network, 256
 - defined, 252
 - dual-gate MOSFET mixer, 256
 - examples of, 253–254, 257–259
 - high-frequency applications, 254–259
 - illustrated, 253
 - intermediate frequency (IF), 255
 - isolation, 557–558
 - low-frequency applications, 252–254
 - oscillator frequency, 255
 - transformer coupling, 253
 - transformers at input, 252
- Transformers
- linear power supply example, 70
 - Scott-T, 699
- Transistor bias circuits
- illustrated, 160
 - troubleshooting, 160–161
- Transistor curve tracers, 164
- Transistor switches. *See also* Bipolar junction transistors (BJTs)
- action, 153
 - applications, 154
 - conditions in cutoff, 153
 - conditions in saturation, 153
 - defined, 152
 - hysteresis, 155
 - one-transistor, 154–155
 - security alarm system example, 156–157
- Transistor testers, 163–165
- Transistors. *See* Bipolar junction transistors (BJTs); Field-effect transistors (FETs)
- Transmission lines
- broken or damaged, 249
 - capacitive effects, 249–250
 - characteristic impedance, 248
 - coax, 248
 - equivalent circuit, 248
 - high-frequency considerations, 249–250
 - inductive effects, 249
 - Miller effect, 250
 - RF amplifier, 247–249
 - skin effect, 249
 - standing wave, 249
 - terminating, 249
- Triacs
- characteristic curves, 722
 - defined, 722, 754
- Triangular-wave oscillators. *See also* Relaxation oscillators
- defined, 482
 - illustrated, 482
 - practical, 483–484
 - with two op-amps, 483
 - waveforms, 483
- Trim, 754
- Troubleshooting
- analysis, 30
 - biased transistors, 160–161
 - circuit breakers, 96
 - comparators, 411–413
 - data conversion circuits, 674–678
 - defined, 29
 - half-splitting, 31
 - leaky filter capacitor, 98–99
 - materials, 33
 - measuring, 30–31
 - op-amp circuits, 411–415
 - open diodes, 96–97
 - open fuses, 96
 - operational amplifiers (op-amps), 340–342
 - plan, 30, 95–96
 - point-of-measurements in, 165
 - power supplies, 95–99
 - regulated power supply, 99
 - shorted capacitor, 98–99
 - shorted diode, 97–98
 - soldering, 31
 - summing amplifiers, 413–414
 - test equipment, 31–33
 - three-terminal regulators, 529
 - transistors with DMM, 161–163
 - unwanted oscillations, 370
- Tuned amplifiers
- automatic gain control (AGC), 251
 - defined, 250–251
 - design, 250
 - Hazeltine neutralization, 251
 - illustrated, 251
 - RF stage and mixer, 255
- Twin-T oscillators. *See also* RC feedback oscillators
- defined, 473
 - filters, 473–474
 - illustrated, 474
- Two-transistor switching circuits, 155
- ## U
- Uncompensated op-amps
- defined, 361, 754
 - example, 361–362
- Unity gain
- bandwidth, 357
 - summing amplifier with, 397–398
- Unwanted thermocouples. *See also* Thermocouples
- compensation for, 707
 - defined, 704
 - temperature-measuring circuit with, 705
- Upper trigger point (UTP), 389, 483
- Upper-side frequency, 596
- ## V
- Valence electrons, 43, 44, 754
- Varactors. *See also* Diodes
- capacitance, 82
 - defined, 82, 754
 - example, 83–84
 - in tuning circuits, 83
- Variable dual-polarity power supply example circuit, 536
- defined, 536
 - schematic, 537
 - voltage regulators, 536–537
- Variable-reactance VCOs, 608
- Vectors, 7, 754
- Velocity transducers, 719
- V-groove MOSFET (VMOSFET), 223, 224
- Voice signals, amplitude modulation with, 599
- Voltage dividers
- capacitively coupled amplifier, 243
 - illustrated, 125
 - rule, 125
- Voltage gain
- AD622, 551
 - capacitively coupled amplifier, 242
 - closed-loop, 325, 355
 - common-drain (CD) amplifier, 209
 - common-emitter (CE) amplifier, 138–139, 143–144, 148–149
 - common-source (CS) amplifier, 207

- gain of voltage divider, 243
 - infinite, 308
 - open loop, 320, 355
 - Voltage ratios, 28–29
 - Voltage regulation. *See* Regulation
 - Voltage-controlled oscillators (VCOs). *See also* Relaxation oscillators
 - capacitance, 612, 613
 - defined, 484, 754
 - example, 485–486
 - 555 timer operation as, 490–491
 - forms, 612
 - frequency determination, 485
 - as frequency modulator, 608
 - MAX2606, 609–610
 - noise in, 609
 - operation of, 484–485, 613
 - in PLLs, 612–613
 - PUT, 484–485
 - variable-reactance, 608
 - Voltage-divider bias. *See also* Bias
 - common-drain (CD) amplifier, 210
 - configurations, 126, 127
 - defined, 124, 754
 - example, 127–128
 - illustrated, 125
 - JFET, 190–191
 - parameter computation, 125
 - for *pnp* transistors, 127
 - use of, 124
 - voltage-divider rule, 125
 - Voltage-follower
 - defined, 327, 754
 - faults in, 341
 - illustrated, 328
 - input impedance, 334–335
 - op-amp, 327–328
 - output impedance, 334–335
 - Voltage(s)
 - BJT, 116–117
 - capacitor, 404
 - collector, 125
 - collector-emitter, 125
 - cutoff, 182–183
 - drain, 187
 - drain-to-source, 187
 - emitter, 125
 - feedback, 264
 - gate, 190
 - input offset, 317–318
 - instantaneous, 8
 - noise, 246, 338, 388–389
 - peak-to-peak, 8
 - pinch-off, 182–183, 753
 - resolver, 698
 - ripple, 63–64, 753
 - Seebeck, 703
 - synchro, 697–698
 - zener, 412
 - Voltage-to-current converter, 410, 754
 - Voltage-to-frequency (*V/F*) converters
 - AD650, 669–671
 - applications, 665
 - concept illustration, 666
 - defined, 665
 - illustrated, 666
 - input voltage increase, 668–669
 - operation, 666
 - operation illustration, 667
 - output, 667, 668
 - remote sensing application, 673
 - reset mode, 667
 - waveforms, 668
 - Voltmeters, 696
 - Volt-ohm-milliammeter (VOMs), 32
- W**
- Waveform generators, 32
 - Waveshaping amplifiers, 21
 - Wide-band amplifiers, 32–33
 - Wide-band three-port isolation amplifier, 560
 - Wien-bridge oscillator. *See also* RC feedback oscillators
 - basic circuit, 467–468
 - defined, 466, 754
 - JFET stabilized, 469–471
 - lead-lag network and response curve, 467
 - as noninverting amplifier, 467–468
 - positive feedback conditions, 468
 - schematics, 467
 - self-starting with zener diodes, 469
 - tone generator example, 471–472
 - Wind turbine example
 - AC-to-DC converter, 531
 - basics, 530–531
 - defined, 530
 - HAWT system operation, 531
 - Wind-direction system example, 702–703
 - Window comparator. *See also* Comparators
 - defined, 393
 - example, 394
 - illustrated, 393
- Z**
- Zener diodes. *See also* Diodes
 - application of, 78–79
 - breakdown voltages, 78
 - defined, 78, 754
 - equivalent circuit, 79–80
 - IV characteristic curve, 78
 - reverse characteristic, 79
 - voltage regulation, 80–81
 - Zero bias, 202
 - Zero-level detection, 386
 - Zero-voltage switching
 - defined, 723, 754
 - nonzero switching comparison, 723
 - use of, 723–724