
Digital Electronics

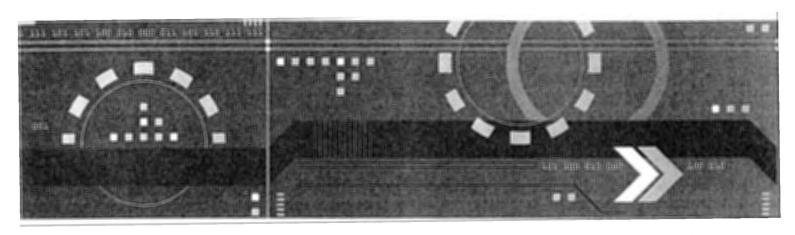




Eighth Edition

Digital Electronics

Principles and Applications

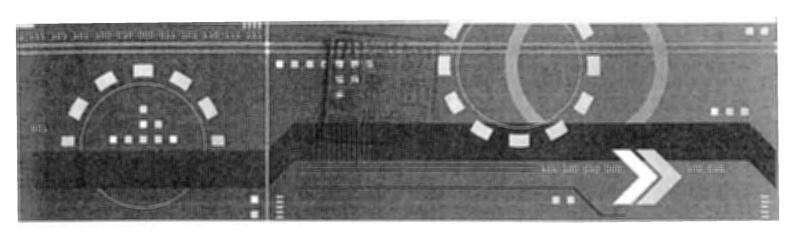

Roger Tokheim





DIGITAL ELECTRONICS: PRINCIPLES AND APPLICATIONS, EIGHTH EDITION

Published by McGraw-Hill, a business unit of The McGraw-Hill Companies, Inc., 1221 Avenue of the Americas, New York, NY, 10020. Copyright © 2014 by The McGraw-Hill Companies, Inc. All rights reserved. Printed in the United States of America. Previous editions © 2008, 2003, and 1999. No part of this publication may be reproduced or distributed in any form or by any means, or stored in a database or retrieval system, without the prior written consent of The McGraw-Hill Companies, Inc., including, but not limited to, in any network or other electronic storage or transmission, or broadcast for distance learning.

Some ancillaries, including electronic and print components, may not be available to customers outside the United States.

This book is printed on acid-free paper.

1234567890QVR/QVR109876543

ISBN 978-125-906092-2 MHID 125-906092-6

All credits appearing on page or at the end of the book are considered to be an extension of the copyright page.

The Internet addresses listed in the text were accurate at the time of publication. The inclusion of a website does not indicate an endorsement by the authors or McGraw-Hill, and McGraw-Hill does not guarantee the accuracy of the information presented at these sites.

www.mhhe.com

Contents

Preface Acknow Walkthi About t Safety . Chapter	Foreword	ix xi xii xii xiv xv xv 1	3-11 3-12 3-13 3-14 3-15 3-16	Using Inverters to Convert Gates
1-2 1-3 1-4	Why Use Digital Circuits?	. 7	Critical '	Review Questions83Thinking Questions86s to Self-Tests89
1-5 1-6	How Do You Test for a Digital Signal? Simple Instruments		Chapter	4 Combining Logic Gates 90
	ry Review Questions	23		Constructing Circuits from Boolean Expressions91
	Thinking Questionss to Self-Tests		4-2	Drawing a Circuit from a Maxterm Boolean Expression
Chapter	2 Numbers We Use in Digital Electronics 2	<i>L.</i> /	4-3	Truth Tables and Boolean Expressions 93 Sample Problem 97
2-1 2-2	Counting in Decimal and Binary	27	4-5	Simplifying Boolean Expressions
2-3	Binary to Decimal Conversion		4-7	Karnaugh Maps with Three Variables 101
2-4	Decimal to Binary Conversion	30 4	4-8	Karnaugh Maps with Four Variables 103
2-5	Electronic Translators	31	4-9	More Karnaugh Maps 104
2-6	Hexadecimal Numbers	34	4-10	A Five-Variable Karnaugh Map 105
2-7	Octal Numbers	36 4	4-11	Using NAND Logic 106
2-8	Bits, Bytes, Nibbles and Word Size	37	4-12	Computer Simulations: Logic Converter 108
Summa	ry	39	4-13	Solving Logic Problems: Data Selectors 112
Chapter	Review Questions			Programmable Logic Devices (PLDs) 116
Critical	Thinking Questions			Using De Morgan's Theorems 124
Answer	s to Self-Tests	42		Solving a Logic Problem (BASIC Stamp
Chapter	3 Logic Gates	43		Module)
3-1	The AND Gate			Review Questions
3-1	The OR Gate	75		Thinking Questions
3-3	The Inverter and Buffer.		Answers	s to Self-Tests
3-4	The NAND Gate	50	a l .	- 100 15 1 1 1 1 1
3-5	The NOR Gate	,	Chapter	
3-6	The Exclusive OR Gate			Interfacing 141
3-7	The Exclusive NOR Gate		5-1	Logic Levels and Noise Margin 141
3-8	The NAND Gate as a Universal Gate			Other Digital IC Specifications
3-9	Gates with More Than Two Inputs			MOS and CMOS ICs

5-4	Interfacing TTL and CMOS with Switches 152	Chapte	r 8 Counters	262
5-5	Interfacing TTL and CMOS with LEDs 156	0.1	D: 1 C	260
5-6	Interfacing TTL and CMOS ICs 160	8-1	Ripple Counters	
5-7	Interfacing with Buzzers, Relays,	8-2	Mod-10 Ripple Counters	
	Motors, and Solenoids	8-3	Synchronous Counters	
5-8	Optoisolators	8-4	Down Counters	
5-9	Interfacing with Servo and Stepper Motors 170	8-5	Self-Stopping Counters	
5-10	Using Hall-Effect Sensors 178	8-6	Counters as Frequency Dividers	
5-11	Troubleshooting Simple Logic Circuits 185	8-7	TTL IC Counters	
5-12	Interfacing the Servo (BASIC Stamp	8-8	CMOS IC Counters	
	Module)	8-9	A Three-Digit BCD Counter	
Summa	ary	8-10	Counting Real-World Events	284
	r Review Questions	8-11	Using a CMOS Counter in an Electronic	
_	l Thinking Questions		Game	288
	ers to Self-Tests	8-12	Using Counters—An Experimental	
			Tachometer	291
Chapte	r 6 Encoding, Decoding, and	8-13	Troubleshooting a Counter	295
	Seven-Segment Displays 196	Summa	ary	
			r Review Questions	
6-1	The 8421 BCD Code		l Thinking Questions	
6-2	The Excess-3 Code		rs to Self-Tests	
6-3	The Gray Code			
6-4	The ASCII Code	Chapte	r 9 Shift Registers	305
6-5	Encoders			
6-6	Seven-Segment LED Displays	9-1	Serial-Load Shift Registers	
6-7	Decoders	9-2	Parallel-Load Shift Registers	
6-8	BCD-to-Seven-Segment Decoder/Drivers 209	9-3	A Universal Shift Register	
6-9	Liquid-Crystal Displays 213	9-4	Using the 74194 IC Shift Register	
6-10	Using CMOS to Drive an LCD Display 218	9-5	An 8-Bit CMOS Shift Register	
6-11	Vacuum Fluorescent Displays	9-6	Using Shift Registers: Digital Roulette	318
6-12	Driving a VF Display	9-7	Troubleshooting a Simple Shift Register.	323
6-13	Troubleshooting a Decoding Circuit 227		ary	
Summ	ary	Chapte	r Review Questions	325
	er Review Questions	Critica	l Thinking Questions	327
-	1 Thinking Questions	Answe	rs to Self-Tests	328
	ers to Self-Tests			
		Chapte	r 10 Arithmetic Circuits	330
Chapte	er 7 Flip-Flops 236	10.1	D' A 11/4	220
		10-1	Binary Addition	
7-1	The R-S Flip-Flop	10-2	Half Adders	
7-2	The Clocked R-S Flip-Flop 239	10-3	Full Adders	
7-3	The D Flip-Flop	10-4	3-Bit Adders	
7-4	The J-K Flip-Flop	10-5	Binary Subtraction	
7-5	IC Latches	10-6	Parallel Subtractors	
7-6	Triggering Flip-Flops 249	10-7	IC Adders	
7-7	Schmitt Trigger	10-8	Binary Multiplication	
7-8	IEEE Logic Symbols	10-9	Binary Multipliers	345
7-9	Application: Latched Encoder-Decoder	10-10	2s Complement Notation, Addition,	
	System		and Subtraction	
Summ	ary	10-11	2s Complement Adders/Subtractors	353
Chapter Review Questions		10-12	Troubleshooting a Full Adder	355
Critical Thinking Questions			ary	357
	ers to Self-Tests		r Review Questions	

	Thinking Questions		13-4	Microcomputer Address Decoding 454		
Answers to Self-Tests		359	13-5	Data Transmission 4		
Chapter	- 11 Memories	361	13-6 13-7	Detecting Errors in Data Transmissions 46 Data Transmission in a Computer System 46		
11-1 11-2 11-3 11-4 11-5 11-6 11-7	Overview of Memory Random-Access Memory (RAM). Static RAM ICs. Using a SRAM Read-Only Memory (ROM) Using a ROM Programmable Read-Only Memory [PROM].	365 367 370 372 375	13-9 Microcontrollers 13-10 The BASIC Stamp Microcontroller Modules 13-11 Digital Signal Processing 13-12 DSP in a Digital Camera 13-13 Microcontroller: Photo Input and Ser Motor Output Summary Chapter Review Questions Critical Thinking Questions	Modules475Digital Signal Processing485DSP in a Digital Camera486Microcontroller: Photo Input and ServoMotor Output485		
11-8 11-9 11-10	Nonvolatile Read/Write Memory Memory Packaging Computer Bulk Storage Devices Digital Potentiameter Using NV Memory	384 387		TREVIEW Questions		
11-11 Summa	Digital Potentiometer: Using NV Memory					
	Review Questions		Chapte	14 Connecting with Analog Devices 499		
	Thinking Questions		14-1	D/A Conversion 500		
	rs to Self-Tests		14-2	Operational Amplifiers 50		
			14-3	A Basic D/A Converter 502		
Chapter	12 Simple Digital Systems	403	14-4	Ladder-Type D/A Converters 504		
Chapter Critical	Elements of a System A Digital System on an IC Digital Games The Digital Clock The LSI Digital Clock. The Frequency Counter. An Experimental Frequency Counter LCD Timer with Alarm. Simple Distance Sensing JTAG/Boundary Scan ry Review Questions. Thinking Questions	406 407 412 415 419 423 426 432 437 441 441	14-6 Voltage Comparators. 14-7 An Elementary Digital Voltmeter. 14-8 Other A/D Converters. 14-9 A/D Converter Specifications. 14-10 An A/D Converter IC. 14-11 Digital Light Meter. 14-12 Digitizing Temperature. Summary. Chapter Review Questions. Critical Thinking Questions. Answers to Self-Tests. Appendix A Solder and the Soldering Pro-	<u> </u>		
Chapter	13 Computer Systems	445	Glossa	ry of Terms and Symbols		
13-1 13-2 13-3	The Computer	447	Credits 549 Index 550			

)

Editor's Foreword

The McGraw-Hill Education Trade and Technology list has been designed to provide entry-level competencies in a wide range of occupations in the electrical and electronics fields. It consists of coordinated instructional materials designed especially for career-oriented students. A textbook, an experiments manual, and online resources support each major subject area covered in the series. All of these focus on theory, practice, applications, and experiences necessary for those preparing to enter technical careers.

There are two fundamental considerations in the preparation of a text like *Digital Electronics: Principles and Applications:* the needs for the learner and the needs of the employer. This text meets those needs in expert fashion. The authors and editors have drawn upon their broad teaching and technical experiences to accurately interpret and meet the needs of the student. The needs of business and industry have been identified through personal interviews, industry publications, government occupational trend reports, and reports by industry associations.

The processes used to produce and refine the series have been ongoing. Technological change is rapid, and the content has been revised to focus on current trends. Refinements in pedagogy have been defined and implemented based on classroom testing and feedback from students and instructors using the series. Every effort has

been made to offer the best possible learning materials. These include animated PowerPoint presentations, circuit files for simulation, a test generator with correlated test banks, dedicated websites for both students and instructors, and basic instrumentation labs. All of these are well coordinated and have been prepared by the author.

The widespread acceptance of *Digital Electronics: Principles and Applications* and the positive feedback from users confirm the basic soundness in content and design of all the components as well as their effectiveness as teaching and learning tools. Instructors will find the texts and manuals in each of the subject areas logically structured, well paced, and developed around a framework of modern objectives. Students will find the materials to be readable, lucidly illustrated, and interesting. They will also find a generous amount of self-study materials, review items, and examples to help them determine their own progress.

Both the initial and ongoing success of this text and others with the McGraw-Hill Trade and Technology list are due in large part to the wisdom and vision of Gordon Rockmaker, who was a magical combination of editor, writer, teacher, electrical engineer, and friend. The publisher and editor welcome comments and suggestions from instructors and students using this series.

Charles A. Schuler, Project Editor

Basic Skills in Electricity and Electronics

Charles A. Schuler, Project Editor

New Editions in This Series

Electricity: Principles and Applications, Eighth Edition, Richard J. Fowler Electronics: Principles and Applications, Eighth Edition, Charles A. Schuler

Preface

Digital Electronics: Principles and Applications, eighth edition, is an easy-to-read introductory text for students new to the field of digital electronics. Providing entry-level knowledge and skills for a wide range of occupations is the goal of this textbook and its ancillary materials. Prerequisites are general math and introductory electricity/electronics. Binary math, Boolean concepts, simple programming, and various codes are introduced and explained as needed. Concepts are connected to practical applications, and a systems approach is followed that reflects current practice in industry. Earlier editions of the text have been used successfully in a wide range of programs: electronic technology, electrical trades and apprenticeship training, computer repair, communications electronics, and computer science, to name a few. This concise and practical text can be used in any program needing a quick and readable overview of digital principles.

New to this Edition

Chapter 1

- Digital applications, including automotive fuel indicators, vehicle speed sensors, and engine control module.
- A new section on where digital circuit applications are used.
- · Information on logic probe use in troubleshooting.
- · A revised instruments section.

Chapter 2

Subsection on applications of encoders and decoders.

Chapter 3

- Updated information on practical chips including lower voltage ICs.
- · Expanded most self-test sections.

Chapter 4

- Expanded several self-test sections.
- · Revised material on data selectors.

Chapter 5

- Information on low-voltage ICs.
- · Added many application assignments on interfacing.

Chapter 6

- Updated applications of the Gray code, including the shaft encoder, and new information on the quadrature encoder.
- Updated information on display technologies.

Chapter 7

- Application of an R-S latch.
- A new detailed application of a latched encoderdecoder system.

Chapter 8

· Expanded self-test questions.

Chapter 10

- Expanded several self-tests.
- · Updated binary subtraction section.

Chapter 11

- · Updated overview of memory section.
- · Updated nonvolatile read/write memory section
- Updated memory packaging section.
- Expanded bulk storage section, including more information on USB flash drives.
- · Internet research topics.

Chapter 12

- Expanded self-test and critical thinking questions.
- Information on distance sensing with coverage of several sensor technologies.
- A DIY application demonstrating a distance sensor triggering the timed operation of a stepper motor.

Chapter 13

- Updated microcomputer section.
- · Updated data transmission section.

- · A revised microcontrollers section.
- Application of a microcontroller with photo input and servo motor output.

Chapter 14

· Expanded self-test questions.

Additional Resources

An *Experiments Manual* for *Digital Electronics* contains a comprehensive test, a variety of hands-on lab exercises and experiments, and additional problems for each chapter in the textbook.

The Online Learning Center (OLC) at www.mhhe. com/tokheim8e includes comprehensive Multisim files, keyed to circuits found in the eighth edition, and a Multisim primer (written by Patrick Hoppe of Gateway Technical College), which provides a tutorial on the software for new users. The Multisim program itself is not included on the

website, but the latest version, version 12, can be purchased through McGraw-Hill at a discount when you adopt this textbook. Visit **www.mhhe.com/tokheim8e** or contact your McGraw-Hill sales representative for more information.

The OLC also features chapter study resources, links to industry and association sites, and assignments and tests for students. Instructors can access the instructor side of the OLC to find a wide selection of information including:

- An Instructor's Manual that includes a list of the parts and equipment needed to perform lab experiments, learning outcomes for each chapter, answers to chapter review questions and problems, and more.
- PowerPoint presentations that correlate to all chapters and special PowerPoint presentations on breadboarding, soldering, circuit interrupters (GFCI and AFCI), and instrumentation.
- A test generator, EZ Test, which includes a test bank with questions for each chapter.

Acknowledgments

Thanks to family members Marshall, Rachael, Dan, Jack, Ben and Carrie for their help on this project. I would also like to thank the reviewers who helped evaluate the textbook; I am grateful for their time and expertise.

Mike Carter

Mercedes-Benz Institute

Richard Fornes

Apollo Career Center Adult Education

J. C. Morrow

Hopkinsville Community College

Tom Neal

Southern Crescent Technical College

Randy Owens

State Fair Community College

Chrys Panayiotou

Indian River State College

G. Albert Popson

West Virginia Wesleyan College

Joseph Tront

Virginia Tech

Mark Winans

Central Texas College


Jillian Wooldridge

Erie Institute of Technology

Walkthrough

Digital Electronics: Principles and Applications, eighth edition, is designed for a first course in digital electronics. It provides a concise, modern, and practical approach that's suitable for a range of electricity and electronics

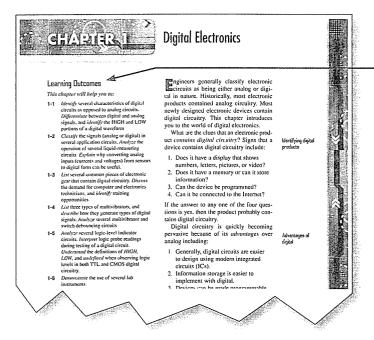programs. With its easy-to-read style, numerous full-color illustrations, and accessible math level, the text is ideal for readers who need to learn the essentials of digital electronics and apply them to on-the-job situations.



Each chapter begins with a list of *learning* outcomes that tell the reader what he or she should expect to accomplish by the end of the chapter. The outcomes are tied to the chapter subsections.

Key terms are carefully defined and explained in the text and listed in the margins so students can easily identify them.

Supply the missing want in each statement.

1. Refer to Fig. 1-2. The +5-V level of the (analog, digital) signal could also be called a logical to a (HIGH, LOW).

2. A(n) (analog, digital) signal which varies continuously in step with the input.

(INPUT Electronic Block is classified as a (n) (analog, digital) device is one that has a signal which varies continuously in step with the input.

(INPUT Electronic Block is classified as a (n) (analog, digital) signal.

5. An analog circuit some that processes analog signals while a digital circuit processes — signals

OUTPUT Electronic Block days and a descriptic cross drapping a size were into a spare were

The *self-tests* can either help students identify areas that need further study or serve as positive reinforcement for material that students already know. After completing a self-test, students may check their answers in the *Answers to Self-Tests* sections at the end of each chapter.

Microprocessorbased systems


. .

2-6 Hexadecimal Numbers

The hesadecimal number system uses the 16 symbols 0, 1, 2, 3, 4, 5, 6, 7, 8, 0, 8, E. D. E. and F and is referred to as the house 16 system. Figure 2-9 shows the equivalent hinary and hexadecimal representations for the decimal numbers 0 through 17. The letter "A" stands for decimal 10, "B" for decimal 11, and so on. The advantage of the hexadecimal system is its usefulness in converting directly from a 4-bit binary number. For instance, bexadecimal F stands for the 4-bit binary number 1111 Hexadecimal number in the stands of the 4-bit binary number. For instance, the hexadecimal number A6 would represent the 8-bit binary number.

number 10100110. Hexadecimal notation is widely used in niteraprocessor-based systems to represent 4, 8-, 16-, 32-, or 64-bit binary numbers.

The number 10 represents how many objects? It can be observed from the table shown in Fig. 2-9 that the number 10 could mean ten objects, or sixteen objects of special objects, or sixteen objects of special objects of special objects of special objects objects objects of the number. Subscripts are sometimes added to a number to indicate the base of the number (II), represents ien objects. The subscript (II) in this example) indicates it is a haze 10, or decimal, number, Using subscripts, the number (II), represents two objects since this is in binary (Inter 2). A configuration is not subscribed in the single subscripts, the number (II), represents two objects since this is in binary (Inter 2). A configuration is not subscribed in the single subscripts, the number is the single subscript.

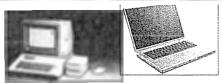

A photographic history of the computer One of the first computers was the Enlac (upper left), developed in the 1940s. The 1970s marked the espacied use of the computer by businesses. The maintaine computer legy possible proper right) was the load of the time. In the 1980s personal computers such as the Apple lie (lower left) brought computers into our homes and schools. Today, personal computers can go anywhere, as abopto computers lower applit increase in popularity.

--@ A Changing Field. Electronics is among the most exciling areas of technical study. New developments are reported weekly, laterestingly, most developments are based on the fundamentals termed in the first classes in electricity, analo and digital circuits, computer technology and robotics, and communications.

1-2 Why Use Digital Circuits?

Electronics designers and technicians must have a working knowledge of both analog and digital systems. The designer must decide if the system will use analog or digital techniques or

a combination of both. The technicians must build a prototype or troubleshoot and repair digital, analog, and combined systems. Analog electronic systems have been popular in the past, Older TVs, telephones, and automo-

ides featured analyse circuits. Before modern

nies festurett ansisse cerentis. Before medern digital computers, variago computers were used in some military applications such as fire control on ships.

Most teal-world information is analog in nature. Natural phenomena, such as time, temperature, humidifiy, wind speed, radiation, and sound intensity, are analog in nature You probably have already measured voltage.

 $(\hat{A} + \hat{B} + \hat{C}) = K$. The resulting minterm expression can be written in conventional form as $A \cdot B \cdot C + \hat{A} \cdot \hat{B} \cdot C = Y$ using overbars or in the shortened keyboard version ABC + A'B'C = Y using apostruphes. It must be understood that the logic diagrams that would be wired using the maxtern



George Boole was born in Lincoln, England, on November 2, 1815. He was a self-laught mathe-matician who invented modern symbolic logic and pioneered the calculus of operators. Around 1850, George Boole created



The features History of Electronics and About Electronics add depth to the topics and highlight new and interesting technologies or facts.

Digital Circuitry: Advantages and Limitations

Some of the advantages for using digital cir-cuitry instead of analog are as follows:

- ceuty instead of analog are as follows:

 I hat,pensive ICs can be used with few external components.

 Information can be stored for short periods or indefinitely.

 Data can be used for precise calculation.

 Systems can be designed more easily using compatible digital logic familities.

 Systems can be programmed and show some manner of "incluffigence".

 Alchanumeric inclure, and video

- 6. Alphanumeric, picture, and video
- 7. Digital circuits are less affected by unwanted
- Such circuits are compatible with the Internet and computers.

The limitations of digital circuitry are as

Most real-world events are analog in nature.
 Analog processing is usually simpler and faster.


Digital circuits are appearing in more and more products primarily because of low-cost, reliable digital ICs. Other reasons for their growing popularity are accuracy, added sta-bility, computer compatibility, memory, ease



Internet connections encourage students to do online research on certain topics.

Critical facts and principles are reviewed in the Summary and Review section at the end of each chapter.

Chapter 1 Summary and Review

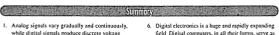

<

- Analog signals vary gradually and continuously, white digital signals produce discrete voltage levels commanly referred to ax HIGH and LOW.
 Most modern electronic equipment contains both analog and digital circuitry
 Logic levels are different for various digital logic families, such as TTL and CMOS. These logic levels are commonly referred to as HIGH, LOW, and undefined Figure 1-20 details these TTL and
- Digital electronics is a huge and rapidly expanding field Digital computers, in all their forms, serve as the backbone of the Internet.
 Bistable, monostable, and stable multivibrators are used to generate digital signals. These are sometimes called latches, one-shet, and freerunning multivibrators, respectively.
 Logic level indicators may take the town of simple LED and resistor circuits, voltmeters, or logic probes.


Chapter Review Questions...continued Critical Thinking Questions 2-4. At the option of your instructor, use circuit simulation software to (a) draw the logic dis-agram of the binary-to-decimal decoder circuit shown in Fig. 2-18. (b) operate the circuit, and (c) demonstrate the binary-to-decimal decoder simulation to your instructor. 2-1. If the digital circuits in a computer only respond to binary numbers, why are octal and hexadecimal numbers used extensively by computer specialists?

2-2. In a digital system such as a microcomputer, it is common to consider an 8-bit group (called

Chapter review questions are found at the end of each chapter, as are critical thinking questions.

About the Author

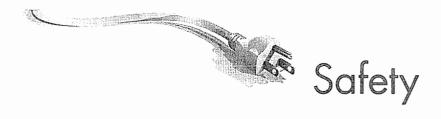Over several decades, Roger L. Tokheim has published many textbooks and lab manuals in the areas of digital electronics and microprocessors. His books have been translated into nine languages. He taught technical subjects including electronics for more than 35 years in public schools.



Electric and electronic circuits can be dangerous. Safe practices are necessary to prevent electrical shock, fires, explosions, mechanical damage, and injuries resulting from the improper use of tools.

Perhaps the greatest hazard is electrical shock. A current through the human body in excess of 10 milliamperes can paralyze the victim and make it impossible to let go of a "live" conductor or component. Ten milliamperes is a rather small amount of current flow: It is only *ten one-thousandths* of an ampere. An ordinary flashlight can provide more than 100 times that amount of current!

Flashlight cells and batteries are safe to handle because the resistance of human skin is normally high enough to keep the current flow very small. For example, touching an ordinary 1.5-V cell produces a current flow in the microampere range (a microampere is one-millionth of an ampere). The amount of current is too small to be noticed.

High voltage, one the other hand, can force enough current through the skin to produce a shock. If the current approaches 100 milliamperes or more, the shock can be fatal. Thus, the danger of shock increases with voltage. Those who work with high voltage must be properly trained and equipped.

When human skin is moist or cut, its resistance to the flow of electricity can drop drastically. When this happens, even moderate voltages may cause a serious shock. Experienced technicians know this, and they also know that so-called low-voltage equipment may have a high-voltage section or two. In other words, they do not practice two methods of working with circuits: one for high voltage and one for low voltage. They follow safe procedures at all times. They do not assume protective devices are working. They do not assume a circuit is off even though the switch is in the OFF position. They know the switch could be defective.

Even a low-voltage, high-current-capacity system like an automotive electrical system can be quite dangerous. Short-circuiting such a system with a ring or metal watchband can cause very severe burns—especially when the ring or band welds to the points being shorted.

As your knowledge and experience grow, you will learn many specific safe procedures for dealing with electricity and electronics. In the meantime:

- 1. Always follow procedures.
- 2. Use service manuals as often as possible. They often contain specific safety information. Read, and comply with, all appropriate material safety data sheets.
- 3. Investigate before you act.
- 4. When in doubt, *do not act*. Ask your instructor or supervisor.

General Safety Rules for Electricity and Electronics

Safe practices will protect you and your fellow workers. Study the following rules. Discuss them with others, and ask your instructor about any you do not understand.


- 1. Do not work when you are tired or taking medicine that makes you drowsy.
- 2. Do not work in poor light.
- 3. Do not work in damp areas or with wet shoes or clothing.
- 4. Use approved tools, equipment, and protective devices.
- Avoid wearing rings, bracelets, and similar metal items when working around exposed electric circuits.
- 6. Never assume that a circuit is off. Double-check it with an instrument that you are sure is operational.
- Some situations require a "buddy system" to guarantee that power will not be turned on while a technician is still working on a circuit.
- Never tamper with or try to override safety devices such as an interlock (a type of switch that automatically removes power when a door is opened or a panel removed).
- 9. Keep tools and test equipment clean and in good working condition. Replace insulated probes and leads at the first sign of deterioration.
- Some devices, such as capacitors, can store a *lethal* charge. They may store this charge for long periods

- of time. You must be certain these devices are discharged before working around them.
- 11. Do not remove grounds and do note use adaptors that defeat the equipment ground.

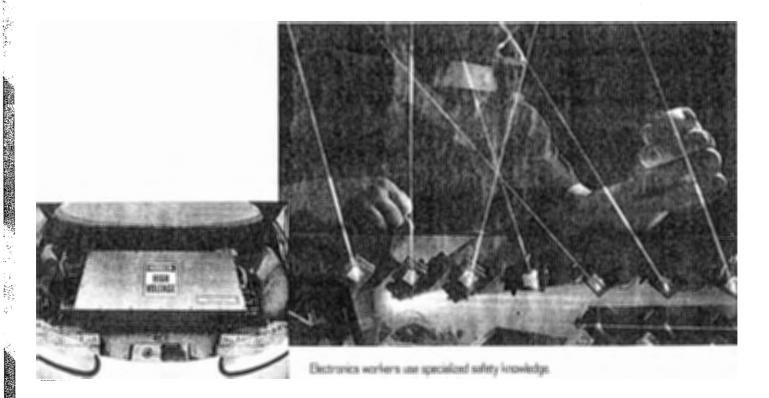- 12. Use only an approved fire extinguisher for electrical and electronic equipment. Water can conduct electricity and may severely damage equipment. Carbon dioxide (CO₂) or halogenated-type extinguishers are usually preferred. Form-type extinguishers may also be desired in *some* cases. Commercial fire extinguishers are rated for the type of fires for which they are effective. Use only those rated for the proper working conditions.
- 13. Follow directions when using solvents and other chemicals. They may be toxic, flammable, or may damage certain materials such as plastics. Always read and follow the appropriate material safety data sheets.
- 14. A few materials used in electronic equipment are toxic. Examples include tantalum capacitors and beryllium oxide transistor cases. These devices should not be crushed or abraded, and you should wash your hands thoroughly after handling them. Other materials (such as heat shrink tubing) may produce

- irritating fumes if overheated. Always read and follow the appropriate material safety data sheets.
- 15. Certain circuit components affect the safe performance of equipment and systems. Use only exact or approved replacement parts.
- 16. Use protective clothing and safety glasses when handling high-vacuum devices such as picture tubes and cathode-ray tubes.
- 17. Don't work on equipment before your know proper procedures and area aware of any potential safety hazards.
- 18. Many accidents have been caused by people rushing and cutting corners. Take the time required to protect yourself and others. Running, horseplay, and practical jokes are strictly forbidden in shops and laboratories.
- 19. Never look directly into light-emitting diodes or fiber-optic cables; some light sources, although invisible, can cause serious eye damage.

Circuits and equipment must be treated with respect. Learn how they work and the proper way of working on them. Always practice safety: your health and life depend on it.





Digital Electronics

Learning Outcomes

This chapter will help you to:

- 1-1 Identify several characteristics of digital circuits as opposed to analog circuits.

 Differentiate between digital and analog signals, and identify the HIGH and LOW portions of a digital waveform.
- 1-2 Classify the signals (analog or digital) in several application circuits. Analyze the operation of several liquid-measuring circuits. Explain why converting analog inputs (currents and voltages) from sensors to digital form can be useful.
- 1-3 List several common pieces of electronic gear that contain digital circuitry. Discuss the demand for computer and electronics technicians, and identify training opportunities.
- **1-4** List three types of multivibrators, and describe how they generate types of digital signals. Analyze several multivibrator and switch debouncing circuits.
- 1-5 Analyze several logic-level indicator circuits. Interpret logic probe readings during testing of a digital circuit. Understand the definitions of HIGH, LOW, and undefined when observing logic levels in both TTL and CMOS digital circuitry.
- **1-6** Demonstrate the use of several lab instruments.

ngineers generally classify electronic circuits as being either analog or digital in nature. Historically, most electronic products contained analog circuitry. Most newly designed electronic devices contain digital circuitry. This chapter introduces you to the world of digital electronics.

What are the clues that an electronic product *contains digital circuitry*? Signs that a device contains digital circuitry include:

- 1. Does it have a display that shows numbers, letters, pictures, or video?
- 2. Does it have a memory or can it store information?
- 3. Can the device be programmed?
- 4. Can it be connected to the Internet?

If the answer to any one of the four questions is yes, then the product probably contains digital circuitry.

Digital circuitry is quickly becoming pervasive because of its *advantages* over analog including:

- 1. Generally, digital circuits are easier to design using modern integrated circuits (ICs).
- 2. Information storage is easier to implement with digital.
- 3. Devices can be made programmable with digital.
- 4. More accuracy and precision are possible.
- 5. Digital circuitry is less affected by unwanted electrical interference called noise.

All persons working in electronics must have knowledge of digital electronic circuits. You will use simple integrated circuits and displays to demonstrate the principles of digital electronics. Identifying digital products

Advantages of digital

1-1 What Is a Digital Signal?

Analog signal

In your experience with electricity and electronics you have probably used analog circuits. The circuit in Fig. 1-1(a) puts out an analog signal or voltage. As the wiper on the potentiometer is moved upward, the voltage from points A to B gradually increases. When the wiper is moved downward, the voltage gradually decreases from 5 to 0 volts (V). The waveform diagram in Fig. 1-1(b) is a graph of the analog output. On the left side the voltage from A to B is gradually increasing to 5 V; on the right side the voltage is gradually decreasing to 0 V. By stopping the potentiometer wiper at any midpoint, we can get an output voltage anywhere between 0 and 5 V. An analog device, then, is one that has a signal which varies continuously in step with the input.

A digital device operates with a digital signal. Figure 1-2(a) pictures a square-wave generator. The generator produces a square waveform that is displayed on the oscilloscope. The digital signal is only at +5 V or at 0 V, as diagrammed in Fig. 1-2(b). The voltage at point A moves from 0 to 5 V. The voltage then stays at +5 V for a time. At point B the voltage drops immediately from +5 to 0 V. The voltage then stays at 0 V for a time. Only two voltages are present in a digital electronic circuit. In the waveform diagram in Fig. 1-2(b) these voltages are labeled HIGH and LOW. The HIGH voltage is +5 V; the LOW voltage is 0 V. Later we shall call the HIGH voltage (+5 V) a logical 1 and the LOW voltage (0 V) a logical 0. Circuits that handle only HIGH and LOW signals are called digital circuits.

The digital signal in Fig. 1-2(b) could also be generated by a simple on-off switch. A digital signal could also be generated by a transistor turning on and off. Digital electronic signals are usually generated and processed by integrated circuits (ICs).

Both analog and digital signals are represented in graph form in Figs. 1-1 and 1-2. A signal can be defined as useful information transmitted within, to, or from electronic circuits. Signals are commonly represented as a voltage varying with time, as they are in Figs. 1-1 and 1-2. However, a signal could be an electric current that either varies continuously (analog) or has an on-off (HIGH-LOW)

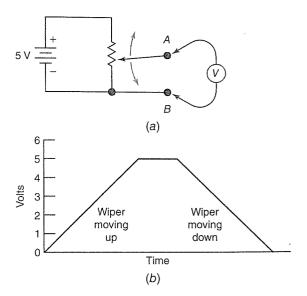


Fig. 7-1 (a) Analog output from a potentiometer. (b) Analog signal waveform.

characteristic (digital). Within most digital circuits, it is customary to represent signals in the voltage versus time format. When digital circuits are interfaced with nondigital devices such as lamps and motors, then the signal can be thought of as current versus time.

The standard *volt-ohm-millimeter* (VOM) shown in Fig. 1-3(a) is an example of an *analog* measuring device. As the voltage, resistance, or current being measured by the VOM increases, the needle *gradually and continuously moves* up the scale. A *digital multimeter* (DMM) is shown in Fig. 1-3(b). This is an example of a *digital* measuring device. As the

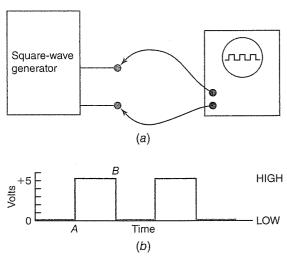


Fig. 3-2 (a) Digital signal displayed on scope. (b) Digital signal waveform.

Volt-ohm-millimeter

HIGH and LOW signals Digital multimeter

Digital circuits

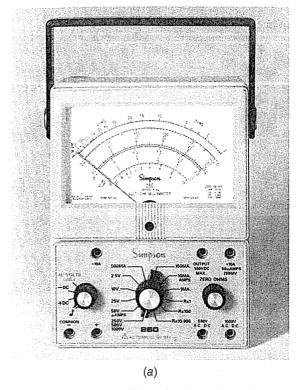




Fig. 1-3 (a) Analog meter. (b) Digital multimeter (DMM). Courtesy Fluke Corporation. Reproduced with permission

current, resistance, or voltage being measured by the DMM increases, the display *jumps upward in small steps*. The DMM is an example of digital circuitry taking over tasks previously performed only by analog devices. This *trend toward digital circuitry* is growing. Currently, the modern technician's bench probably has both a VOM and a DMM.

Trend toward digital circuitry

-√W- Self-Test

Supply the missing word in each statement.

- 1. Refer to Fig. 1-2. The +5-V level of the _____ (analog, digital) signal could also be called a logical 1 or a _____ (HIGH, LOW).
- 2. A(n) _____ (analog, digital) device is one that has a signal which varies continuously in step with the input.
- 3. Refer to Fig. 1-4. The input to the electronic block is classified as a(n) _____ (analog, digital) signal.
- 4. Refer to Fig. 1-4. The *output* from the electronic block is classified as a(n) _____ (analog, digital) signal.
- An analog circuit is one that processes analog signals while a digital circuit processes ______ signals.



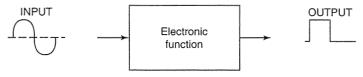


Fig. 1-4 Block diagram of electronic circuit shaping a sine wave into a source wave.

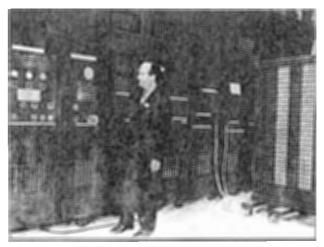


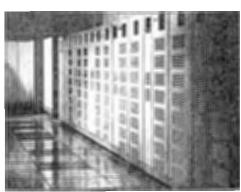








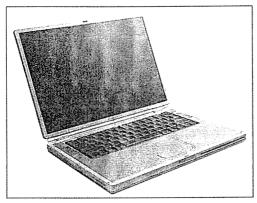

A photographic history of the computer. One of the first computers was the Eniac (*upper left*), developed in the 1940s. The 1970s marked the expanded use of the computer by businesses. The mainframe computer (*upper right*) was the tool of the time. In the 1980s personal computers such as the Apple IIe (*lower left*) brought computers into our homes and schools. Today, personal computers can go anywhere, as laptop computers (*lower right*) increase in popularity.

ABOUT ELECTRONICS

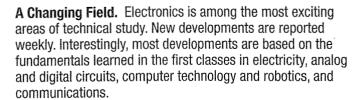

1-2 Why Use Digital Circuits?

Electronics designers and technicians must have a working knowledge of both analog and digital systems. The designer must decide if the system will use analog or digital techniques or a combination of both. The technicians must build a prototype or troubleshoot and repair digital, analog, and combined systems.

Analog electronic systems have been popular in the past. Older TVs, telephones, and automobiles featured analog circuits. Before modern digital computers, analog computers were used in some military applications such as fire control on ships.

Most real-world information is analog in nature. Natural phenomena, such as time, temperature, humidity, wind speed, radiation, and sound intensity, are analog in nature. You probably have already measured voltage, current, resistance, power, capacitance, inductance, and frequency in other electricity and electronics courses. Other things to be measured include pressure, weight, oxygen (and other gases), ultrasonic sound, acceleration and tilt, vibration, direction (compass), global positioning, proximity, magnetic fields, linear distance, and angle of rotation (angular speed). They are all analog in nature. Engineers and technicians commonly use *sensors* to measure these things. Many sensors emit an analog signal.

A simple analog electronic system for measuring the amount of liquid in a tank is illustrated in Fig. 1-5. The input to the system is a varying resistance. The processing proceeds according to the Ohm's law formula, I = V/R. The output indicator is an ammeter which is calibrated as a water tank gauge. In the analog system in Fig. 1-5 as the water rises, the input resistance drops. Decreasing the resistance R causes an increase in current (I). Increased current causes the ammeter (water tank gauge) to read higher.

The analog system in Fig. 1-5 is simple and efficient. The gauge in Fig. 1-5 gives an indication of the water level in the tank. If more information is required about the water level, then a digital system such as the one shown in Fig. 1-6 might be used.

Digital systems are required when data must be stored, used for calculations, or displayed as numbers and/or letters. A somewhat more complex arrangement for measuring the amount of liquid in a water tank is the digital system shown in Fig. 1-6. The input is still a variable resistance as it was in the analog system. The resistance is converted into numbers by the analog-to-digital (A/D) converter. The central processing unit (CPU) of a computer can manipulate the input data, output the information, store the information, calculate things such as flow rates in and out, calculate the time until the tank is full (or empty) based on flow rates, and so forth. Digital systems are valuable when calculations, data manipulations, data storage, and alphanumeric or video outputs are required. Data transfers via the Internet are common.

Analog-to-digital (A/D) converter Central processing unit (CPU)

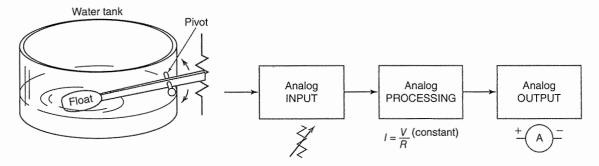


Fig. 1-5 Analog system used to interpret float level in water tank.

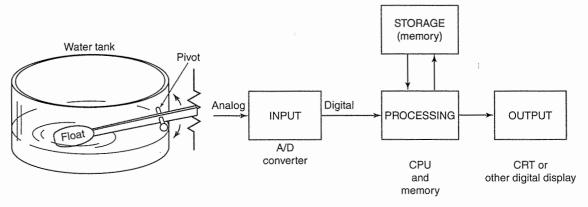


Fig. 1-5 Digital system used to interpret float level in water tank.

Application: Automobile Fuel Indicators

Older automobile circuitry was analog in nature. Consider the traditional fuel gauge system sketched in Fig. 1-7(a). The fuel tank sending unit has a float that moves a wiper on a resistive material. Increasing the fuel level in the tank raises the float, causing the wiper to move left on the resistor. The resistor's value decreases. Decreased circuit resistance causes an increase in current in the series circuit (via Ohm's law, I = V/R). The increased current causes the needle on the fuel gauge (an ammeter) to move clockwise toward F on the meter face. The older-style fuel gauge diagram in Fig. 1-7(a) is an example of an analog circuit.


Newer automobiles may use the information from the fuel tank sending unit for several purposes. Figure 1-7(b) shows the analog voltage from the fuel tank sending unit entering the instrument panel module. The computer module converts the analog input to digital information (A/D converter). The computer module also receives signals from the *vehicle speed sensor*, *engine control module* (ECM). The input information is processed by the computer module. The instrument control module will drive a traditional-looking fuel gauge located on the instrument panel. A tachometer is probably also located on the instrument panel. With the inputs

shown in Fig. 1-7(b), the instrumentation computer module calculates the average-fuel-consumption and miles-to-empty data. The driver sees this information displayed on an LCD screen.

It will be noted that information from the sensors in Fig. 1-7(b) comes in various forms. The fuel tank sending unit delivers a *variable-voltage signal* to the computer module. With higher levels of fuel in the tank the sending unit generates a higher positive voltage.

The vehicle speed sensor sends a variable-frequency signal. At lower vehicle speeds the sensor emits a low-frequency signal. At higher speeds a high-frequency signal is sent to the computer module.

The engine control module sends several *digital signals* to the instrument control module. The engine control module determines how much fuel is injected into the cylinders of the engine and the timing.

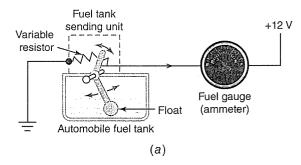

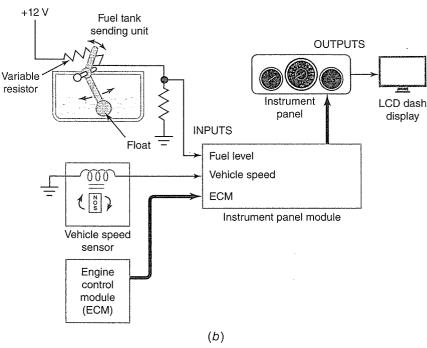


Fig. 1-7 (a) Automobile fuel tank sending unit and fuel gauge. (b) Modern automobile fuel indicator system with computer module.

Digital Circuitry: Advantages and Limitations

Some of the advantages for using digital circuitry instead of analog are as follows:

- 1. Inexpensive ICs can be used with few external components.
- 2. Information can be stored for short periods or indefinitely.
- 3. Data can be used for precise calculations.
- 4. Systems can be designed more easily using compatible digital logic families.
- 5. Systems can be programmed and show some manner of "intelligence."
- 6. Alphanumeric, picture, and video information can be viewed using a variety of electronic displays.

- 7. Digital circuits are less affected by unwanted electrical interference called *noise*.
- 8. Such circuits are compatible with the Internet and computers.

The *limitations of digital circuitry* are as follows:

- 1. Most real-world events are analog in nature.
- 2. Analog processing is usually simpler and faster.

Digital circuits are appearing in more and more products primarily because of low-cost, reliable digital ICs. Other reasons for their growing popularity are accuracy, added stability, computer compatibility, memory, ease of use, simplicity of design, and compatibility with a variety of displays.

Internet Connection

Search the web for the following terms: fuel tank sending unit, vehicle speed sensor, and engine control module.

-√/-


SelfTes

Answer the following questions.

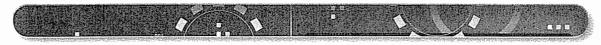- 6. Generally, electronic circuits are classified as either analog or ______.
- 7. Measurements of time, speed, weight, pressure, light intensity, and position are _____ (analog, digital) in nature.
- 8. Refer to Fig. 1-5. As the water level drops, the input resistance increases.

 This causes the current *I* to _______ (decrease, increase) and the water level gauge (ammeter) will read _____ (higher, lower).
- 9. Refer to Figs. 1-5 and 1-6. If this water tank were part of the city water system, where rates of water use are important, the system in Fig. _____ (1-5, 1-6) would be most appropriate.

- True or false. The most important reason why digital circuitry is becoming more popular is that digital circuits are usually simpler and faster than analog circuits.
- 11. Refer to Fig. 1-7(a). This traditional auto fuel tank gauge assembly that senses and indicates the fuel level is an example of a(n) _____ (analog, digital) circuit.
- 12. Refer to Fig. 1-7(*b*). The input voltage from the fuel tank sending unit is a digital signal before it enters the instrument panel module. (T or F)
- 13. Refer to Fig. 1-7(*b*). The input from the engine control module (ECM) having to do with fuel flow and time is _____ (analog, digital) in nature.



1-3 Where Are Digital Circuits Used?

Digital electronics is a huge and rapidly expanding field. The global system of interconnected computer networks called the *Internet* serves billions of users. Digital computers, in

all their forms, serve as the backbone of the Internet. The Internet consists of academic, business, private, and government networks. The Internet allows users to access huge amounts of information using the World Wide Web (WWW). The Internet also supports two-way communications with e-mail and social

networking sites including Facebook. Huge amounts of data are transferred via the Internet by banks, manufacturers, the military, medical professions, security companies, governments, and businesses. The global economy could hardly survive without the capabilities of digital computers, huge memory banks, and the Internet.

Millions of individual electronic devices must be designed, manufactured, tested, and repaired by technicians. Electronics technicians and engineers are in great demand. A few applications of digital electronics are suggested by the images on the tablet sketched in Fig. 1-8.



Fig. 1-B Applications of digital electronics.

Jobs for technicians are available with most high-technology businesses. Many government jobs call for some skills in computer technology including electronics. Highly skilled technicians work on extremely sophisticated military electronics. It is reported that the half the cost of some military aircraft is electronics in nature. The military has many outstanding advanced electronics training programs. Ask about these when you visit a military recruiter.

The driving experience of a modern automobile has been greatly enhanced by electronics. Automobile engines have more power, run smoother, and use less fuel due to precise electronic engine control. More automobiles contain entertainment systems that are outstanding. Bluetooth for cell phones, GPS, and touch screen displays are common. Assisted parking and blind spot detection are standard on many autos. Safety features like antiskid and traction and stability control systems depend digital electronics. Ask your school counselor about opportunities in your area.

To cut down on thefts, the key to your automobile may contain a transmitter whose signal is picked up by a transponder ECM. The transponder reads the wireless signal from the key, allowing the engine to start. Some modern automobiles have more than 50 electronic control modules (computers). Auto mechanics must be trained in modern electricity and electronics. Check with your area technical college to survey training openings. Automanufacturers also run outstanding training classes.

Most measuring instruments you may use at work in the lab will contain digital circuitry. These might include a logic probe, digital multimeter (DMM), capacitance meter, frequency counter, function generator (signal generator), and programmable power supply. Modern oscilloscopes may also feature some digital circuitry.

Many hands-on lab activities will be provided. A updated *Experiments Manual for Digital Electronics* is available that presents many hands-on lab activities chapter by chapter.



Self-Test

Answer the following questions.

- 14. List at least four devices that use digital circuitry.
- 15. Computer and electronics technicians are in great demand. (T or F)
- 16. The military has excellent electronics training schools. (T or F)
- 17. All auto mechanics that are specialists in electronics are self-taught. (T or F)
- 18. List at least two measuring instruments you will use as a technician and that contain digital circuitry.



1-4 How Do You Generate a Digital Signal?

Digital signals are composed of two well-defined voltage levels. Most of the voltage levels used in this class will be about +3 V to +5 V for HIGH and near 0 V (GND) for LOW. These are commonly called *TTL voltage levels* because they are used with the *transistor-transistor logic* family of ICs.

Generating a Digital Signal

A TTL digital signal could be made manually by using a mechanical switch. Consider the simple circuit shown in Fig. 1-9(a). As the blade of the single-pole, double-throw (SPDT) switch is moved up and down, it produces the *digital waveform* shown at the right. At time period t_1 , the voltage is 0 V, or LOW. At t_2 the voltage is +5 V, or HIGH. At t_3 , the voltage is again 0 V, or LOW, and at t_4 , it is again +5 V, or HIGH.

The action of the switch causing the LOW, HIGH, LOW, HIGH waveform in Fig. 1-9(a) is called *toggling*. By definition, to *toggle* (the verb) means to switch over to an opposite state. As an example in Fig. 1-9(a), if the switch moves from LOW to HIGH we say the output has toggled. Again if the switch moves from HIGH to LOW we say the output has again toggled.

One problem with a mechanical switch is *contact bounce*. If we could look very carefully at a switch toggling from LOW to HIGH, it might look like the waveform in Fig. 1-9(b). The waveform first goes directly from LOW to

HIGH (see point A) but then, because of contact bounce, drops to LOW (see point B) and then back to HIGH again. Although this happens in a very short time, digital circuits are fast enough to see this as a LOW, HIGH, LOW, HIGH waveform. Note that Fig. 1-9(b) shows that there is actually a range of voltages that are defined HIGH and LOW. The *undefined region* between HIGH and LOW may cause trouble in digital circuits and should be avoided.

To cure the problem illustrated in Fig. 1-9(b), mechanical switches are sometimes debounced. A block diagram of a debounced logic switch is shown in Fig. 1-9(c). Note the use of the debouncing circuit, or latch. Some of the mechanical logic switches you will use on laboratory equipment will have been debounced with latch circuits. Latches are sometimes called *flip-flops*. Notice in Fig. 1-9(c) that the output of the latch during time period t_1 is LOW but not quite 0 V. During t_2 the output of the latch is HIGH even though it is something less than a full +5 V. Likewise t_3 is LOW and t_4 is HIGH in Fig. 1-9(c).

It might be suggested that a push-button switch be used to make a digital signal. If the button is pressed, a HIGH should be generated. If the push button is released, a LOW should be generated. Consider the simple circuit in Fig. 1-10(a). When the push button is pressed, a HIGH of about +5 V is generated at the output. When the push button is released, however, the voltage at the output is *undefined*. There is an open circuit between the power supply and the output. This would not work properly as a logic switch.

TTL voltage levels Transistortransistor logic

Debounced logic switch

Digital waveform Latch (flip-flop)

Contact bounce

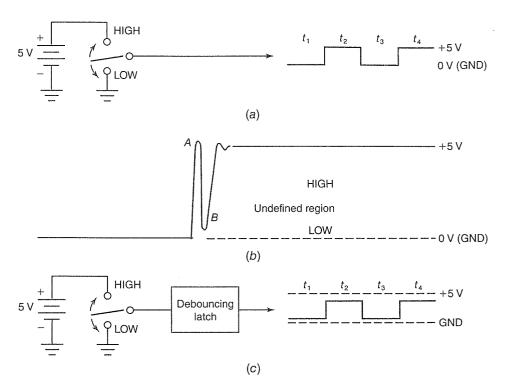


Fig. 1-9 (a) Generating a digital signal with a switch. (b) Waveform of contact bounce caused by a mechanical switch. (c) Adding a debouncing latch to a simple switch to condition the digital signal.

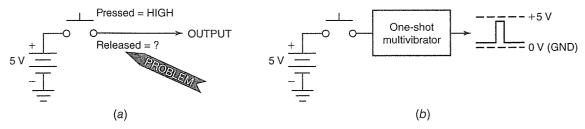


Fig. 1-10 (a) Push button will not generate a digital signal. (b) Push button used to trigger a one-shot multivibrator for a single-pulse digital signal.

A normally open push-button switch can be used with a special circuit to generate a digital pulse. Figure 1-10(b) shows the push button connected to a *one-shot multivibrator* circuit. Now for each press of the push button, a *single short, positive pulse* is output from the one-shot circuit. The pulse width of the output is determined by the design of the multivibrator and *not* by how long you hold down the push button.

Multivibrator Circuits

Multivibrator types: astable, bistable, and monostable

One-shot

multivibrator

Free-running IVIV (clock)

Both the latch circuit and the one-shot circuit were used earlier. Both are classified as *multivibrator* (MV) circuits. The latch is also called a flip-flop or a *bistable multivibrator*. The one-shot is also called the *monostable multivibrator*. A third type of MV circuit is the *astable multivibrator*. This is also called a *free-running*

multivibrator. In many digital circuits it may be referred to simply as the *clock*.

The free-running MV oscillates by itself without the need for external switching or an external signal. A block diagram of a free-running MV is shown in Fig. 1-11. The free-running MV generates a continuous series of TTL level pulses. The output in Fig. 1-11 alternately toggles from LOW to HIGH, HIGH to LOW, etc.

In the laboratory, you will need to generate digital signals. The equipment you will use will have slide switches, push buttons, and freerunning clocks that will generate TTL level signals similar to those shown in Figs. 1-9, 1-10, and 1-11. In the laboratory, you will use *logic switches* which will have been debounced using a latch circuit as in Fig. 1-9(c). You will also use a *single-pulse clock* triggered by a push-button switch.

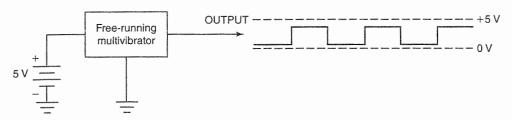


Fig. 1-11 Free-running multivibrator generates a string of digital pulses.

The single-pulse clock push button will be connected to a one-shot multivibrator as shown in Fig. 1-10(b). Finally, your equipment will have a free-running clock. It will generate a continuous series of pulses, as shown in Fig. 1-11.

Wiring a Multivibrator

Astable, monostable, and bistable MVs can all be wired using discrete components (individual resistors, capacitors, and transistors) or purchased in IC form. Because of their superior performance, ease of use, and low cost, the IC forms of these circuits will be used in this course. A schematic diagram for a practical free-running clock circuit is shown in Fig. 1-12(a). This clock circuit produces a low-frequency (1- to 2-Hz) TTL level output. The heart of the free-running clock circuit is a common 555 timer IC. Note that several resistors, a capacitor, and a power supply must also be used in the circuit.

A typical breadboard wiring of this freerunning clock is sketched in Fig. 1-12(b). Notice the use of a solderless breadboard. Also note that pin 1 on the IC is immediately counterclockwise from the notch or dot near the end of the eightpin IC. The wiring diagram in Fig. 1-12(b) is shown for your convenience. You will normally have to wire circuits on solderless breadboards directly from the schematic diagram.

Wiring a Debounced Switch

Simple mechanical switches introduce problems when used as input devices to digital circuits. The push-button switch (SW₁) shown in Fig. 1-13(a) is being pressed or closed at point A (see output waveform). Because of switch bounce the output signal goes HIGH, LOW, and then HIGH again. Likewise when the push-button switch is released (opened) at point B, more bouncing occurs. Switch bounce from input switches must be eliminated.

To solve the problem of switch bounce, a *debouncing circuit* has been added in Fig. 1-13(b). Now when the push-button switch is closed at point C (see output waveform), no bouncing occurs and the output toggles from LOW to HIGH. Likewise when SW_1 is opened at point D, no bouncing is observed on the waveform and the output toggles from HIGH to LOW.

An input switch with a debouncing circuit attached is drawn in Fig. 1-14. Observe that the 555 timer IC is at the heart of the debouncing circuit. When push-button switch SW_1 is closed (see point E on waveform), the output toggles from LOW to HIGH. Later when SW_1 is opened

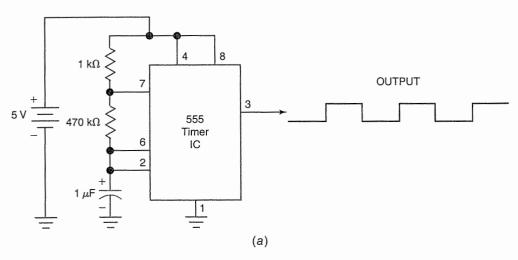


Fig. 1-12(a) Schematic diagram of a free-running clock using a 555 timer IC.


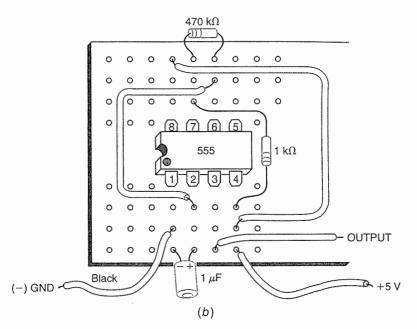


Fig. 1-12(b) Wiring the free-running clock circuit on a solderless breadboard.

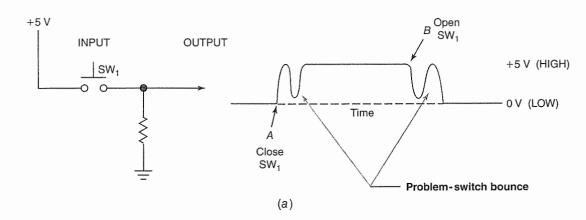

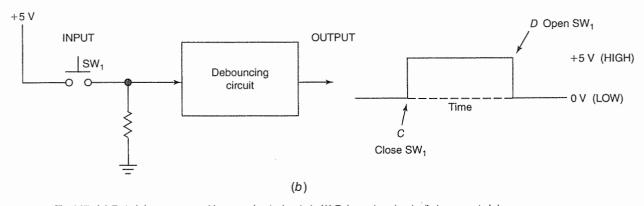


Fig. 1-13 (a) Switch bounce caused by a mechanical switch. (b) Debouncing circuit eliminates switch bounce.

(see point F on wave-form), the output of the 555 timer IC remains HIGH for a delay period. After the delay period (about 1 second for this circuit) the output toggles from HIGH to LOW. The delay period can be adjusted by changing the capacitance value of capacitor C_2 . Decreasing the capacitance

value of C_2 will decrease the delay time at the output, while increasing C_2 will increase the delay.

Wiring a One-Shot Multivibrator

A one-shot multivibrator (MV) is also called a monostable multivibrator. The one-shot circuit

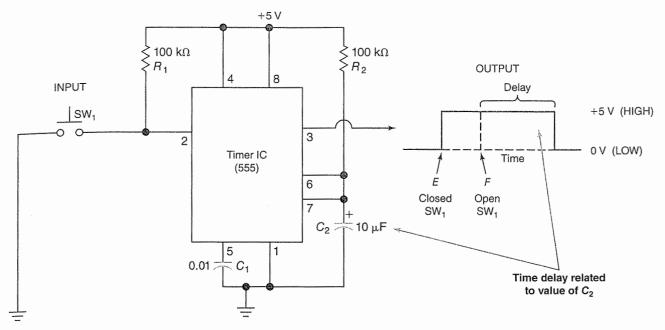


Fig. 1-14 Switch debouncing circuit.

responds to an input trigger pulse with an output pulse of a given width or time duration.

A one-shot MV circuit that can be wired in the lab is drawn in Fig. 1-15. The 74121 one-shot multivibrator IC uses a simple push-button switch to raise the voltage at input B from GND to about +3 V. This is the trigger voltage. When triggered, the one-shot MV outputs a short pulse at the two outputs. The *normal output Q* (pin 6) emits a short positive pulse about 2 to 3 ms

in duration. The complementary output \overline{Q} emits the opposite output, or a short negative pulse. On digital devices called flip-flops the outputs are commonly labeled Q and \overline{Q} (say not Q), and their outputs are always opposite or complementary. On complementary outputs, if Q is HIGH then \overline{Q} is LOW but if Q is LOW then \overline{Q} is HIGH. The outputs of the 74121 one-shot multivibrator IC come directly from an internal flip-flop and are therefore labeled Q and \overline{Q} .

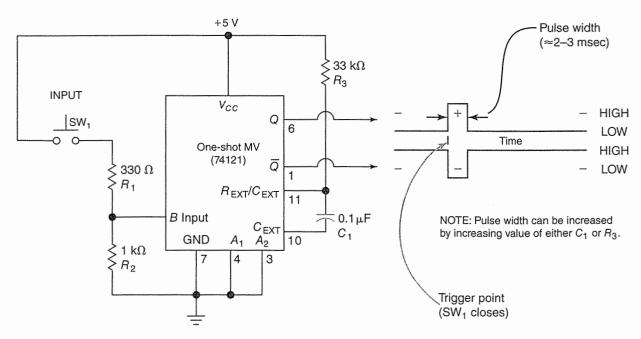


Fig. 1-15 One-shot multivibrator circuit using the 74121 TTL IC.

The *pulse width* generated by a one-shot multivibrator is dependent on the design of the MV and not how long the input switch is pressed. The pulse width of the one-shot MV sketched in Fig. 1-15 can be increased by increasing the value of capacitor C_1 and/or resistor R_3 . Decreasing the values of capacitor C_1 and resistor R_3 will decrease the pulse width.

As a practical matter, the input switch in Fig. 1-15 may have to be debounced, or the multivibrator IC could emit more than a single pulse. Using a good-quality "snap-action" pushbutton switch may also help avoid the problem of false triggering by the one-shot MV circuit.

Digital Trainer

A typical digital trainer used during lab sessions is featured in Fig. 1-16. The photograph actually shows a pair of PC boards specifically designed to be used with this textbook's

companion experiments manual. Dynalogic's DT-1000 digital trainer board on the left includes a solderless breadboard for hooking up circuits. It also includes input devices such as 12 logic switches (two are debounced), a keypad, a one-shot MV, and a variable frequency clock (astable MV). Output devices mounted on the DT-1000 trainer board include 16 LED output indicators, a piezo buzzer, a relay, and a small dc motor. Power connections are available on the upper left of the DT-1000 digital trainer board. On the right in Fig. 1-16 is a second PC board which contains sophisticated LED, LCD, and VFD displays. Dynalogic's DB-1000 display board is very useful when seven-segment displays are used as outputs. These boards along with individual ICs and other components could be used during your lab sessions to enable you to gain practical experience in digital electronics.



Internet Connection

Search the web for LED, LCD, and VFD seven-segment displays.

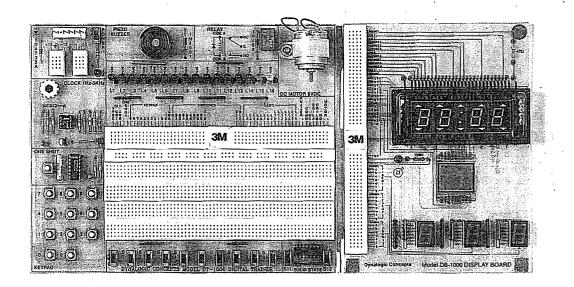


Fig. 1-16 Digital trainer and display boards used to set up lab experiments.


Self-Test

Supply the missing word in each statement.

- 19. Refer to Fig. 1-9(c). The digital signal at t_2 is _____ (HIGH, LOW), while it is _____ (HIGH, LOW) at t_3 .
- 20. Refer to Fig. 1-10(*a*). When the push button is released (open), the output is
- 21. Refer to Fig. 1-9(c). The debouncing latch is also called a flip-flop or _____ multivibrator.

- 22. Refer to Fig. 1-10(b). The one-shot multivibrator used for generating the digital signal is also called a(n) ___ multivibrator.
- 23. Refer to Fig. 1-12. A 555 _____ IC and several discrete components are being used to generate a continuous series of TTL level pulses. This free-running clock is also called a free-running multivibrator or _____ multivibrator.
- 24. Refer to Fig. 1-14. The 555 timer IC is being used along with several discrete components to ___ ____ (debounce, increase the voltage of) push-button switch SW₁.
- 25. Refer to Fig. 1-15. The 74121 IC is being used as a ___ _____ (free-running, oneshot) multivibrator.
- 26. Refer to Fig. 1-15. The 74121 IC has two outputs (labeled Q and \overline{Q}) generating ____ (complementary, in-phase) output pulses.

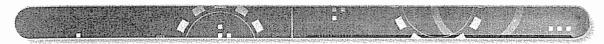- 27. Refer to Fig. 1-15. The time duration or pulse width of the output of the one-shot MV is determined by the __
 - a. Amount of time switch SW, is closed.
 - b. Values of components C_1 and R_3 .
- 28. Refer to Fig. 1-16. The one shot at the left on the DT-1000 board emits a single pulse each time the push-button switch is pressed. The one shot is also called a(n). (astable, monostable) multivibrator.
- 29. Refer to Fig. 1-16. The clock at the left on the DT-1000 board generates a string of digital pulses. The clock is also called a(n) ___ _____ (astable, bistable) multivibrator.
- 30. Refer to Fig. 1-16. The DT-1000 digital trainer board on the left features several output devices. List at least three of these output devices.
- 31. Refer to Fig. 1-16. The DB-1000 display board on the right features what three types of seven-segment displays?



How Do You Test for a 1-5 Digital Signal?

In the last section you generated digital signals using various MV circuits. These are the methods you will use in the laboratory to generate input signals for the digital circuits constructed. In this section, several simple methods of testing the *outputs* of digital circuits will be discussed.

Consider the circuit in Fig. 1-17(a). The input is provided by a simple SPDT switch and power supply. The output indicator is an LED (lightemitting diode). The 150- Ω resistor limits the current through the LED to a safe level. When the switch in Fig. 1-17(a) is in the HIGH (up) position, +5 V is applied to the anode end of the LED. The LED is forward-biased, current flows upward, and the LED lights. With the switch in the LOW (down) position, both the anode and cathode ends of the LED are grounded, and it does not light. Using this indicator, a light means HIGH and no light generally means LOW.

Output indicators

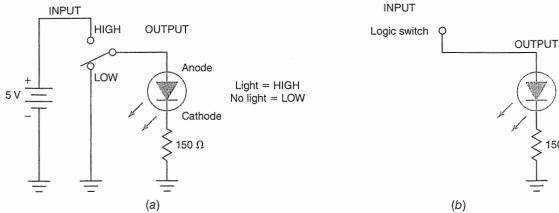


Fig. 1-17 (a) Simple LED output indicator. (b) Logic switch connected to simple LED output indicator.

The simple LED output indicator is shown again in Fig. 1-17(*b*). This time a simplified diagram of a logic switch forms the input. The logic switch acts like the switch in Fig. 1-17(*a*) except it may be debounced. The output indicator is again the LED with a series-limiting resistor. When the input logic switch in Fig. 1-17(*b*) generates a LOW, the LED will not light. However, when the logic switch produces a HIGH, the LED will light.

Another LED output indicator is illustrated in Fig. 1-18. The LED acts exactly the same as the one shown previously. It lights to indicate a logical HIGH and does not light to indicate a LOW. The LED in Fig. 1-18 is driven by an NPN transistor instead of directly by the input.

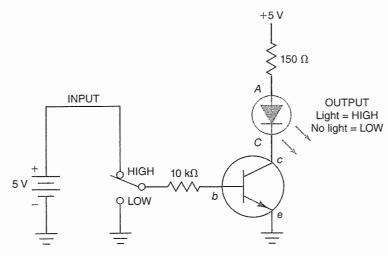


Fig. 1-18 Transistor-driven LED output indicator.

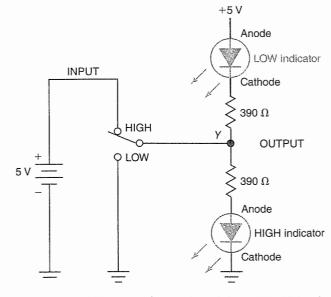


Fig. 3-19 LED output indicators that will show LOW, HIGH, and undefined logic levels.

The transistorized circuit in Fig. 1-18 holds an advantage over the direct-drive circuit in that it draws less current from the switch or an output of the digital circuit under test. Light-emitting diode output indicators wired like the one shown in Fig. 1-18 may be found in your laboratory equipment.

Consider the output indicator circuit using two LEDs shown in Fig. 1-19. When the input is HIGH (+5 V), the bottom LED lights while the top LED does not light. When the input is LOW (GND), only the top LED lights. If point *Y* in the circuit in Fig. 1-19 enters the undefined region between HIGH and LOW or is not connected to a point in the circuit, both LEDs light.

Output voltages from a digital circuit can be measured with a standard voltmeter. With the TTL family of ICs, a voltage from 0 to 0.8 V is considered a LOW. A voltage from 2 to 5 V is considered a HIGH. Voltages between about 0.8 and 2 V are in the undefined region and signal trouble in TTL circuits.

Logic levels are shown in graphic form in Fig. 1-20. It should be noted that a typical operating voltage for transistor-transistor logic (TTL) circuits is +5 V. Depending on the subfamily of complementary metal-oxide semiconductor (CMOS) digital circuits, they may operate on a wide range of operating voltages including +12 V, +9 V, +5 V, or even less. The definition of what TTL and CMOS circuits consider HIGH and LOW is different. Notice that the range of voltages between HIGH and LOW in both TTL and CMOS is called the *undefined region*. Voltages in the undefined region cause trouble in digital circuits.

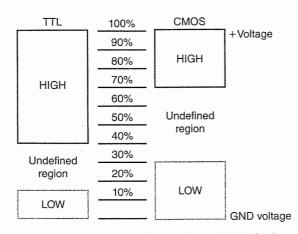


Fig. 1-20 Defining logic levels for the TTL and CMOS families of digital ICs.

A handy portable measuring instrument used to determine logic level is the *logic probe*. A simple version of the logic probe is sketched in Fig. 1-21(a). Before testing a circuit, this logic probe requires the operator to select the type of digital circuitry being tested. Move the selector switch to either TTL or CMOS. TTL and CMOS are two different families of digital circuits. The graph in Fig. 1-20 suggested the definitions of HIGH, LOW, and undefined are different.

Power to operate the logic probe is provided by the digital circuit you are testing. The two leads coming out the end of the logic probe are connected to the +V (red lead) and negative GND (black lead). The pointed metal tip of the logic probe is touched to the point in the circuit you are testing. The appropriate output LED on the logic probe will light (HIGH or LOW), depending on the logic level at the input metal tip.

A TTL digital circuit is being tested with a simple logic probe in Fig. 1-21(b). Switch logic

Logic probe

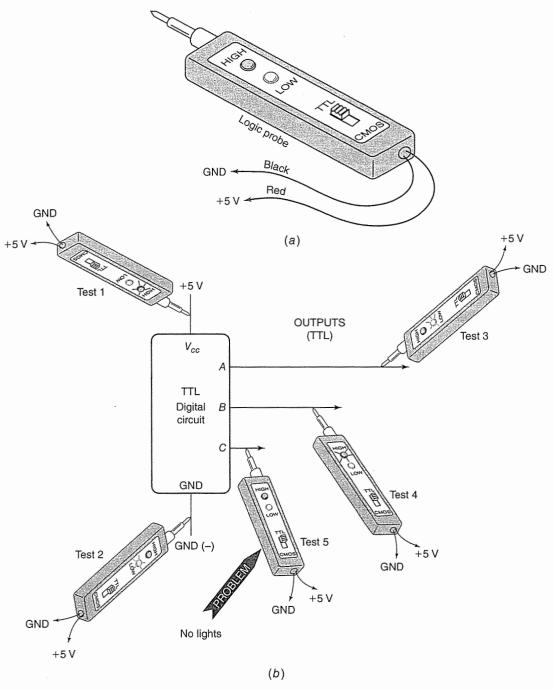


Fig. 1-21 (a) Simple logic probe. (b) Testing a TTL digital circuit with a logic probe.

probe to TTL (not CMOS). The red and black leads are connected to the voltages that operate the circuit. Next turn the power on. Five logic probe tests are performed as follows:

Test #1: Touch tip to +5-V input. Result: Reads HIGH logic level. This is correct.

Test #2: Touch tip to GND input. Result: Reads LOW logic level. This is correct.

Test #3: Touch tip to output *A*. Result: Reads LOW logic level. This is correct.

Test #4: Touch tip to output *B*. Result: Reads HIGH logic level. This is correct.

Test #5: Touch tip to output *C*. Result: *No reading* on HIGH or LOW indicators. This means that the output is neither HIGH nor LOW but floating in the undefined region or is open. This is a problem that must be repaired!

A floating output from a digital circuit was detected in test #5 in Fig. 1-21(b). Floating inputs or outputs commonly mean a fault in the circuit and must be repaired.

Testing with a logic probe as in Fig. 1-21(b) can be one of the steps in troubleshooting. Knowledge of circuit operation is the *key to effective troubleshooting*.

You will notice that we are testing a TTL digital circuit that has static outputs. Logic probes are good for this type of testing but *not suited* for circuits that have constantly changing outputs.

In the laboratory, you will use a logic probe to test and troubleshoot your breadboarded digital circuits. The operating instructions are different for each model of logic probe. Read the instruction manual on the unit you will be using.

-\\- Self-Test

Supply the missing word or words in each statement.

- 32. Refer to Fig. 1-17. If the input is HIGH, the LED will _____ (light, not light) because the diode is _____ (forward-, reverse-) biased.
- 33. Refer to Fig. 1-18. If the input is LOW, the transistor is turned ______ (off, on) and the LED _____ (does, does not) light.
- 34. Refer to Fig. 1-19. If the input is HIGH, the ______ (bottom, top) LED lights because its _____ (cathode, anode) has +5 V applied, forward-biasing the diode.
- 35. Refer to Fig. 1-20 and assume a 5-V power supply. In a TTL circuit, a voltage of 2.5 V would be considered a(n) _____ (HIGH, LOW, undefined) logic level.

- 36. Refer to Fig. 1-20 and assume a +12-V power supply. In a CMOS circuit, a voltage of 2 V would be considered a(n)

 (HIGH, LOW, undefined) logic level.
- 37. Refer to Fig. 1-21(*a*). This logic probe is powered by _____.
 - a. A solar cell.
 - b. A 9-V battery.
 - c. Power from the circuit being tested.
- 38. Refer to Fig. 1-21(*b*). Test #5 indicates an open or output *C* of the digital circuit is floating in the undefined region for TTL circuits. (T or F)
- 39. Refer to Fig. 1-21(*b*). The finding detected in test #5 will not cause problems because the unit is a TTL digital circuit. (T or F)



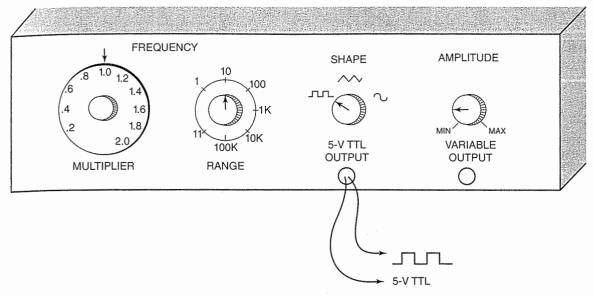


Fig. 1-22 Function generator.

1-6 Simple Instruments

Several basic commercial instruments used with digital circuits are introduced in this section. Simplified generic instruments are featured. Real commercial function generators, logic probes, and oscilloscopes have more advanced features.

Function Generator

One useful *output device* available in most school and industrial labs is the *function generator*. A simple function generator is sketched in Fig. 1-22. If you work with a digital trainer (DT-1000 trainer in Fig. 1-16) in your school lab, it may contain outputs like those of a function generator.

To use the function generator, you first select the *shape* of the waveform. A square wave would be selected when working with most digital circuits. Second, the *frequency* (in hertz, or Hz) may be selected using the range switch along with the variable multiplier dial. Third, the output voltage is selected. This function generator features two separate voltage outputs (5-V TTL and variable). The 5-V TTL output is handy for driving many TTL logic circuits. If you use the variable output on the function generator, the amplitude knob will adjust the output voltage.

What is the *shape* and *frequency* of the waveform being generated by the function generator pictured in Fig. 1-22? The shape knob is in the square-wave position. The range

frequency selector knob points at 10 Hz. The multiplier frequency dial points at 1. The output frequency is 10 Hz (range \times multiplier = frequency or $10 \times 1 = 10$ Hz). In Fig. 1-22, the output is taken from the 5-V TTL output of the instrument. This output will directly drive a TTL logic circuit.

Logic Probe

The most basic instrument for testing the digital logic levels is the *logic probe*. A simple logic probe is sketched in Fig. 1-23. The slide switch is used to select the type of logic family under test, either TTL or CMOS. The logic probe pictured in Fig. 1-23 is set to test a TTL-type digital circuit. Typically, two leads provide power to the logic probe. The red lead is connected to the positive (+) of the

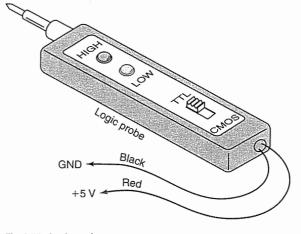


Fig. 1-23 Logic probe.

power supply and the black lead is connected to negative (–) or GND of the power supply. After powering the logic probe, the needlelike probe is touched to the test point in the circuit. Either the HIGH (red LED) or LOW (green LED) indicator will light. If neither or both indicators light, it usually means the voltage is somewhere between HIGH and LOW (undefined region). As a reminder, definitions for *HIGH*, *LOW*, and *undefined* logic levels are detailed in Fig. 1-20.

The logic probe will be a useful tool when you wire and test digital circuits in the school lab. Read the operating instructions for your specific logic probe.

Oscilloscope

The oscilloscope is a very versatile piece of test equipment. A simplified generic oscilloscope, or "scope," is sketched in Fig. 1-24. The basic function of the oscilloscope is to *graph time* versus input voltage. Time is the horizontal

distance on the screen and voltage is the vertical deflection. Oscilloscopes work best on signals that repeat over and over.

Consider the digital signal of 4 V p-p, 100 Hz shown entering the scope's input in Fig. 1-24. The *horizontal sweep time* knob on the scope has been set to 2 ms (2 milliseconds = 0.002 second). This will cause a dot of light to move across the screen from left to right at 2 ms per division (20 ms to cross the entire screen). The dot of light will then jump back to the left end of the screen to start the process again. The *vertical deflection* knob on the scope is set at 1 V per division.

In this example, a signal voltage of 0 V, to +4 V is entering the input. Starting at the left edge of the scope face, first, the dot is deflected four divisions (1 V per division) upward for the first 5 ms. Second, the input voltage drops to 0 V, and the lighted dot traces the bottom line for 5 ms. Third, the input voltage jumps to +4 V with the second upper trace. Fourth, the voltage

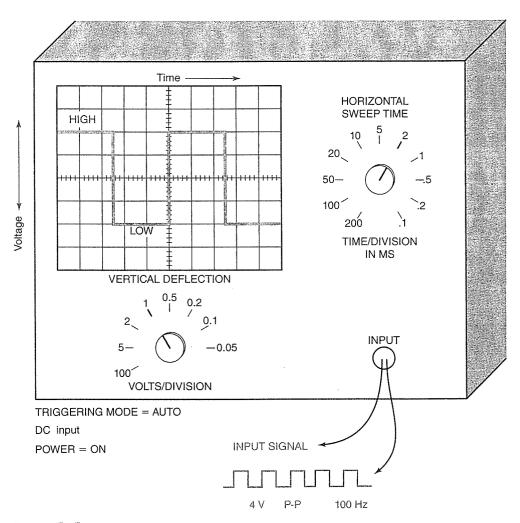


Fig. 1-24 Oscilloscope.

drops to 0 V with the second lower trace. Finally, the lighted dot jumps back to the left of the screen and then repeats. TTL logic levels are labeled on Fig. 1-24 as HIGH (+4 V) and LOW (0 V).

Consider the wave traced on the oscilloscope's screen in Fig. 1-24. The shape of the signal is a square wave. Square waves are useful in digital electronics. A careful look will show that *two* waveforms are displayed on the screen. We say that two *cycles* are displayed.

Look at the waveform on the scope in Fig. 1-24. What is the *time duration* for one cycle? You will count five divisions. This means that the time duration of the first cycle is 10 ms (5 divisions \times

2 ms/division = 10 ms). From the time duration of 10 ms (0.010 second), you can *calculate the frequency* of the input voltage using the formula f=1/t, where f is the frequency in Hz (cycles per second) and t is the time in seconds. Calculating the frequency of the input signal in Fig. 1-24 yields a frequency of 100 Hz (f=1/0.01 s). Notice that the oscilloscope has aided us in determining the *shape* and *frequency* of the input waveform.

Oscilloscopes you will use in the lab will be more complicated than the simplified version shown in Fig. 1-24. However, the basic function of the scope has been illustrated.

Calculate frequency

W.

SaliTes

Supply the answers for each question.

- 40. List two instruments used to detect and measure digital signals.
- 41. A ______ (function generator, logic analyzer) is a laboratory instrument that can generate electronic signals. This
- instrument has controls available for varying the voltage, shape, and frequency of the output signal.
- 42. Refer to Fig. 1-25. How many cycles are displayed on the screen of the oscilloscope?


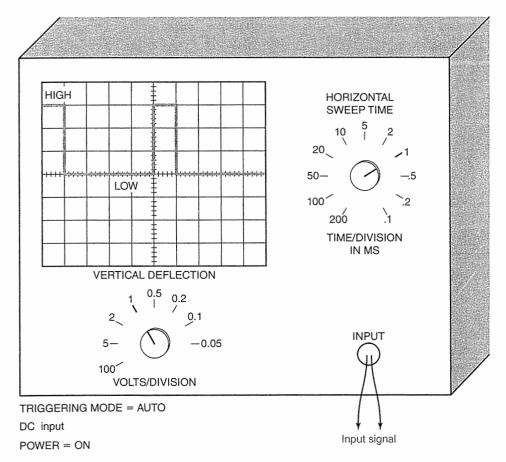


Fig. 1-25 Oscilloscope problem.

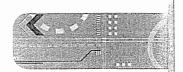- 43. Refer to Fig. 1-25. What is the time duration for one cycle?
- 44. Refer to Fig. 1-25. What is the frequency of the input signal?
- 45. Refer to Fig. 1-25. What is the peak-to-peak (p-p) voltage of the input signal?
- 46. Refer to Fig. 1-25. The digital input signal stays HIGH for ______ (1 ms, 10 ms) and goes LOW for _____ (4 ms, 8 ms).



Chapter 1 Summary and Review



Summary

- Analog signals vary gradually and continuously, while digital signals produce discrete voltage levels commonly referred to as HIGH and LOW.
- 2. Most modern electronic equipment contains both analog and digital circuitry.
- 3. Logic levels are different for various digital logic families, such as TTL and CMOS. These logic levels are commonly referred to as HIGH, LOW, and undefined. Figure 1-20 details these TTL and CMOS logic levels.
- 4. Digital circuits have become very popular because of the availability of low-cost digital ICs. Other advantages of digital circuitry are computer compatibility, memory, ease of use, simplicity of design, accuracy, and stability.
- 5. Modern automobiles are examples of the extensive use of both analog sensors interfaced with dozens of digital engine control modules (ECMs). These ECMs make thousands of decisions a second, controlling the overall driving quality and safety of the modern automobile.

- 6. Digital electronics is a huge and rapidly expanding field. Digital computers, in all their forms, serve as the backbone of the Internet.
- 7. Bistable, monostable, and astable multivibrators are used to generate digital signals. These are sometimes called latches, one-shot, and free-running multivibrators, respectively.
- 8. Logic level indicators may take the form of simple LED and resistor circuits, voltmeters, or logic probes. Light-emitting diode logic level indicators will probably be found on your laboratory equipment.
- 9. A function generator is a lab instrument used to generate electronic signals. The operator can vary an output signal's voltage, frequency, and shape.
- 10. An oscilloscope is a widely used test and troubleshooting instrument used to graph signals. Oscilloscopes are useful in showing waveform shape, time duration, and frequency of repetitive signals.

Chapter Review Questions

Answer	the	foll	lowing	questions.

- 1-1. Define the following:
 - a Analog signal.
 - b. Digital signal.
- 1-2. Draw a square-wave digital signal. Label the bottom "0 V" and the top "+5 V." Label the HIGH and LOW on the waveform. Label the logical 1 and logical 0 on the waveform.
- 1-3. List two devices that contain digital circuits which do mathematical calculations.
- 1-4. Refer to Fig. 1-6. The processing, storage of data, and output in this system consist mostly of ______ (analog, digital) circuits.
- 1-5. Refer to Fig. 1-7(*a*). The gradually varying current sent from the fuel tank sending unit to the fuel

- gauge on this older auto instrument panel is classified as a(n) _____ (analog, digital) signal.
- 1-6. Refer to Fig. 1-7(b). The modern automobile instrument panel module is a digital computerlike unit that can drive the fuel gauge and calculate and display fuel consumption as average miles per gallon and miles till empty. List the sensors and modules that must input data into the instrument panel module.
- 1-7. Traditionally, most consumer electronic devices (TVs, radios, and phones) have used _____ (analog, digital) circuitry.
- 1-8. Unwanted electrical interference in electronic circuitry is commonly called ______ (gobo, noise).

Chapter Review Questions...continued

1-9.	An electronic product that has an alphanumeric		would be considered a(n)(HIGH,
	display, is programmable, and can store infor-		LOW, undefined) logic level.
	mation for sure contains (analog,	1-25.	Refer to Fig. 1-20 and assume a 10-V power
	digital) circuitry.		supply. In a CMOS circuit, a voltage of 9 V
1-10.	Digital circuitry is becoming more pervasive		would be considered a(n) (HIGH,
	because information storage is easy, the device		LOW, undefined) logic level.
	can be programmed, and(greater,	1-26.	Refer to Fig. 1-20 and assume a 10-V power
	less) accuracy and precision are possible.		supply. In a CMOS circuit, a voltage of 0.5 V
1-11.	List two electronic devices you personally use		would be considered a(n) (HIGH,
	that contain digital circuitry.		LOW, undefined) logic level.
1-12.	The military has excellent electronics training	1-27.	When referring to digital ICs, TTL stands for
	schools. (T or F)		•
1-13.	List two pieces of lab equipment you will use	1-28.	When referring to digital ICs, CMOS stands for
	that contains digital circuitry.		
1-14.	Refer to Fig. 1-9. When using a SPDT switch to	1-29.	Refer to Fig. 1-14. The 555 timer IC is wired to
	produce a digital signal, a(n) latch is		function as a(n) (astable MV, switch
	used to condition the output.		debouncing) circuit.
1-15.	Refer to Fig. 1-10. A(n),	1-30.	Refer to Fig. 1-14. Increasing the capacitance
	multivibrator is commonly used to condition the		value of C_2 will (decrease, increase)
	output of a push-button switch when generating		the time delay of the output waveform.
	a single digital pulse.	1-31.	Refer to Fig. 1-15. The 74121 IC can be de-
1-16.	An astable, or, multi-		scribed as a(n) (astable, bistable,
	vibrator produces a string of digital pulses.		monostable) multivibrator.
1-17.	The circuit in Fig. 1-12 is classed as a(n)	1-32.	Refer to Fig. 1-15. Activating input switch
	(astable, bistable) multivibrator.		SW ₁ causes a short (negative pulse,
1-18.	Refer to Fig. 1-16. The one-shot MV on the		positive pulse) to be emitted from the normal
	DT-1000 trainer produces a (series		Q output of the 74121 one-shot multivibrator
	of pulses, single pulse) when the push button is		IC.
	pressed once.	1-33.	A flip-flop is the name for a device classified
1-19.	Refer to Fig. 1-16. The clock on the DT-1000		as a(n) (astable, bistable, monos-
	trainer produces a (continuous series		table) multivibrator.
	of pulses, single pulse) and the circuit can be	1-34.	The repeated action of a switch or other device
	referred to as a(n) (astable, mono-		causing a LOW, HIGH, LOW, HIGH output is
	stable) multivibrator.		called (complementing, toggling).
1-20.	Refer to Fig. 1-16. The two solid-state logic	1-35.	Refer to Fig. 1-22. The output from the function
	switches on the DT-1000 trainer are		generator is a 5-V TTL square-wave signal that
	(analog, debounced).		has a frequency of Hz.
1-21.	Refer to Fig. 1-16. The DB-1000 board	1-36.	Refer to Fig. 1-23. This logic probe can test
	features what three types of seven-segment		either TTL or (CMOS, PPC) logic
	displays?		circuits.
1-22.	The LED in Fig. 1-17(b) lights when the input	1-37.	The advantage of the oscilloscope in testing
	logic switch is (HIGH, LOW).		and troubleshooting is that voltage, time dura-
1-23.	Refer to Fig. 1-19. The(bottom, top)		tion, frequency, and the (quantum
	LED lights when the input switch is LOW.		level, shape) of a waveform can be easily
1-24.	Refer to Fig. 1-20 and assume a 5-V power		determined.
	supply. In a TTL circuit, a voltage of 1.2 V		

Critical Thinking Questions

- 1-1. List several advantages of digital over analog circuits.
- 1-2. When you are looking at electronic equipment, what are some clues that might indicate it contains at least some digital circuitry?
- 1-3. Refer to Fig. 1-9(*a*). What is the main drawback of this circuit for generating a digital signal?
- 1-4. Refer to Fig. 1-10(a). What is the difficulty with this circuit for generating a digital signal?
- 1-5. Refer to Fig. 1-26. From the oscilloscope settings and display, determine the following signal characteristics:
 - a. Voltage (peak-to-peak).
 - b. Waveform shape.
 - c. Time duration (one cycle).
 - d. Frequency (f = 1/t).

- 1-6. At the option of your instructor, use circuit simulation software to (1) draw a free-running clock circuit using a 555 timer IC such as that pictured in Fig. 1-27, (2) test the operation of the clock circuit, and (3) determine the approximate frequency of the clock using the time period measurements from the scope and the formula f = 1/t.
- 1-7. At the option of your instructor, use circuit simulation software to (1) draw the clock circuit in Fig. 1-27 as in question 1-6, (2) change the resistance of R_2 to $100 \text{ k}\Omega$, (3) test the operation of the clock circuit, and (4) determine the approximate frequency of the clock using the time period measurements from the scope and the formula f = 1/t.

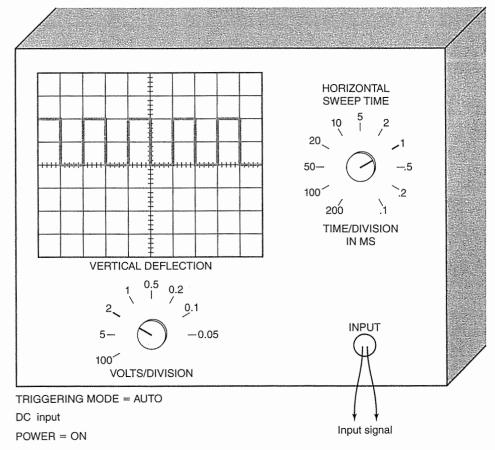


Fig. 1-26 Oscilloscope problem.

Critical Thinking Questions...continued

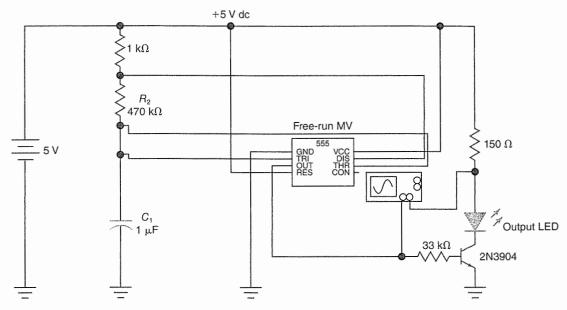


Fig. 1-27 Circuit simulation problem—clock circuit.



Answers to Self-Tests

- 1. digital, HIGH
- 2. analog
- 3. analog
- 4. digital
- 5. digital
- 6. digital
- 7. analog
- 8. decrease, lower
- 9. 1–6
- 10. F
- 11. analog
- 12. F
- 13. digital
- 14. many possible:
 - computers memory
 - digital clock
 - digital cameras
 - many phones
 - auto ECMs

- 15. T
- 16. T
- 17. F
- 18. DMM
 - logic probe
 - logic analyzer
 - oscilloscope
- 19. HIGH, LOW
- 20. undefined
- 21. bistable
- ZI. DISTABLE
- 22. monostable
- 23. timer, astable
- 24. debounce
- 25. one-shot
- 26. complementary
- 27. b
- 28. monostable
- 29. astable
- 30. LED (logic indicators), piezo buzzer, dc motor, relay

- 31. LED, LCD, VF
- 32. light, forward-
- 33. off, does not
- 34. bottom, anode
- 35. HIGH
- 36. LOW
- 37. C
- 38. T
- 39. F
- 40. logic probe, oscilloscope
- 41. function generator
- 42. 2
- 43. 5 ms or 0.005 s
- 44. 200 Hz
- 45. 3 V
- 46. 1 ms, 4 ms





Numbers We Use in Digital Electronics

Learning Outcomes

This chapter will help you to:

- **2-1** Demonstrate understanding of the idea of place value in the decimal, binary, octal, and hexadecimal number systems.
- **2-2** Convert binary numbers to decimal and decimal numbers to binary.
- 2-3 Analyze several block diagrams that electronically translate from decimal to binary and binary to decimal. Understand the use of terms encode, encoder, decode, and decoder in digital electronics.
- 2-4 Convert hexadecimal numbers to binary, binary to hexadecimal, hexadecimal to decimal, and decimal numbers to hexadecimal.
- **2-5** Convert octal numbers to binary, binary to octal, octal to decimal, and decimal numbers to octal.
- **2-6** *Use* terms such as *bit*, *nibble*, *byte*, and *word* when describing data groupings.

ost people understand us when we say we have nine pennies. The number 9 is part of the *decimal* number system we use every day. But digital electronic devices use a number system called *binary*. Digital computers and many other digital systems use other number systems, including *hexadecimal* and *octal*. Men and women who work in electronics must know how to convert numbers from the everyday decimal system to the binary, hexadecimal, and octal systems.

Besides decimal, binary, hexadecimal, and octal, many other codes are used in digital electronics. Some of these codes include binary coded decimal (BCD), the Gray code, and the ASCII code. Arithmetic circuits represent positive and negative binary numbers using 2s complement numbers. Many of these specialized codes will be studied in later chapters.

2-1 Counting in Decimal and Binary

A number system is a code that uses symbols to refer to a number of items. The *decimal number system* uses the symbols 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9. The decimal number system contains 10 symbols and is sometimes called the *base 10 system*. The *binary number system* uses only the two symbols 0 and 1 and is sometimes called the *base 2 system*.

Figure 2-1 compares a number of coins with the symbols we use for counting. The decimal symbols that we commonly use for counting from 0 to 9 are shown in the left column; the right column has the symbols we use to count nine coins in the binary system. Notice that the 0 and 1 count in binary is the same as in decimal counting. To represent two coins, the binary

Decimal number system

Base 10 system

Binary number system

Base 2 system

number 10 (say "one zero") is used. To represent three coins, the binary number 11 (say "one one") is used. To represent nine coins, the binary number 1001 (say "one zero zero one") is used.

For your work in digital electronics you should memorize the binary symbols used to count to at least 15.

Self-Test

Supply the missing word or number in each statement.

- 1. The binary number system is sometimes called the _____ system.
- 2. Decimal 8 equals ______ in binary.

- 3. The binary number 0110 equals _ in decimal.
- 4. The binary number 1001 equals _ in decimal.



COI	NS						DECIMAL SYMBOL	
No	coins	3					0	0
							1	1
0							2	10
	0	(9)					3	11
		(1)					4	100
							5	101
							6	110
(1)				(3)			7	111
	9	0	9	0	(6)	()	8	1000
	(1)		(1)	(7)			() 9	1001

Fig. 2-1 Symbols for counting.

2-2 Place Value

The clerk at the local store totals your bill and asks you for \$2.43. We all know that this amount equals 243 cents. Instead of paying

with 243 pennies, however, you could probably give the clerk the money shown in Fig. 2-2: two \$1 dollar bills, four dimes, and three pennies. This money example illustrates the very important idea of place value.

Consider the decimal number 648 in Fig. 2-3. The digit 6 represents 600 because of its placement three positions left of the decimal point. The digit 4 represents 40 because of its placement two positions left of the decimal point. The digit 8 represents eight units because of its placement one position left of the decimal point. The total number 648, then, represents six hundred and forty-eight units. This is an example of place value in the decimal number system.

The binary number system also uses the idea of place value. What does the binary number 1101 (say "one one zero one") mean? Figure 2-4 shows that the digit 1 nearest the binary point is the units, or 1s, position, and so we add one item. The digit 0 in the 2s position tells us we

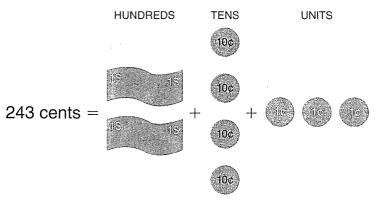


Fig. 2-2 An example of place value.

28



Fig. 2-3 Place value in the decimal system.

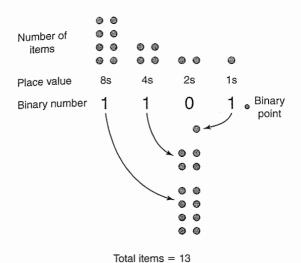


Fig. 2-4 Place value in the binary number system.

have no 2s. The digit 1 in the 4s position tells us to add four items. The digit 1 in the 8s position tells us to add eight more items. When we count all the items, we find that the binary number 1101 represents 13 items.

How about the binary number 1100 (say "one one zero zero")? Using the system from Fig. 2-4, we find that we have the following:

8s	4s	2s	1s	place value
yes	yes	no	no	binary
(1)	(1)	(0)	(0)	number
••	••			number of items
••	••			
••				
••				

The binary number 1100, then, represents 12 items.

Figure 2-5 shows each place in the value of the binary system. Notice that each place value is determined by multiplying the value to the right by 2. The term "base 2" for binary comes from this idea.

Many times the weight or value of each place in the binary number system is referred to as a *power of 2*. In Fig. 2-5, place values for a binary number are shown in decimal and also in powers of 2. For instance, the 8s place is the same as the 2³ position, the 32s place the same as the 2⁵ position and so on.

Recall that 2^4 means $2 \times 2 \times 2 \times 2$ which equals 16. From Fig. 2-5 it is noted that the fifth place left of the binary point is 2^4 or the 16s place.

Powers of 2

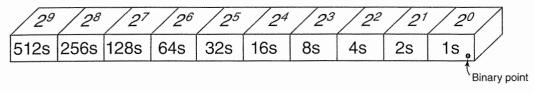


Fig. 2-5 Value of the places left of the binary point.

-№ Self-Test

Supply the missing number in each statement.

- 5. The 1 in the binary number 1000 has a place value of ______ in decimal.
- 6. The binary number 1010 equals _____ in decimal.
- 7. The binary number 100000 equals _____ in decimal.
- 8. The number 2⁷ equals ______ in decimal.

- 9. The binary number 11111111 equals _____ in decimal.
- 10. The first place left of the binary point has a value of 1 or ______(2⁰, 2¹).



2-3 Binary to Decimal Conversion

Binary to decimal conversion

While working with digital equipment you will have to convert from the binary code to decimal numbers. If you are given the binary number 110011, what would you say it equals in decimal? First write down the binary number as:

Binary
$$\begin{bmatrix} 1 & 1 & 0 & 0 & 1 & 1 \\ \hline \downarrow & \downarrow & & \downarrow & \downarrow & \\ Decimal & 32+16 & + & 2+1 & = 51 \end{bmatrix}$$
 binary


Binary point

Start at the *binary point* and work to the left. For each binary 1, place the decimal value of that position (see Fig. 2-5) below the binary digit. Add the four decimal numbers to find the decimal equivalent. You will find that binary 110011 equals the decimal number 51.

Another practical problem is to convert the binary number 101010 to a decimal number. Again write down the binary number as:

Starting at the binary point, write the place value (see Fig. 2-5) for each binary 1 below the square in decimals. Add the three decimal numbers to get the decimal total. You will find that the binary number 101010 equals the decimal number 42.

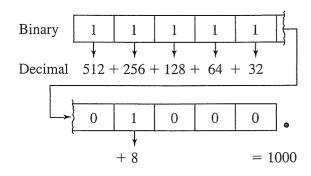Now try a long and difficult binary number: convert the binary number 1111101000 to a decimal number. Write down the binary number as:



From Fig. 2-5, convert each binary 1 to its correct decimal value. Add the decimal values to get the decimal total. The binary number 1111101000 equals the decimal number 1000.



Connection

Search the web for code conversion programs.



Supply the missing number in each statement.


- 12. The binary number 1111 equals _ in decimal.
- 13. The binary number 100010 equals _ in decimal.
- 14. The binary number 1000001010 equals ____ in decimal.



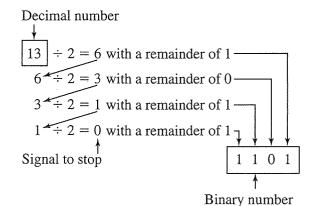2-4 Decimal to Binary Conversion

Many times while working with digital electronic equipment you must be able to convert a decimal number to a binary number. We shall teach you a method that will help you to make this conversion.

Suppose you want to convert the decimal number 13 to a binary number. One procedure you can use is the repeated divide-by-2 process shown next:




Decimal to binary conversion


Repeated divide-by-2 process

Notice that 13 is first divided by 2, giving a quotient of 6 with a remainder of 1. This remainder becomes the 1s place in the binary number. The 6 is then divided by 2, giving a quotient of 3 with a remainder of 0. This remainder becomes the 2s place in the binary number. The 3 is then divided by 2, giving a quotient of 1 with a remainder of 1. This remainder becomes the 4s place in the binary number. The 1 is then divided by 2, giving a quotient of 0 with a remainder of 1. This remainder becomes the 8s place in the binary number. When the quotient becomes 0, you stop the divide-by-2 process. The decimal number 13 has been converted to the binary number 1101.

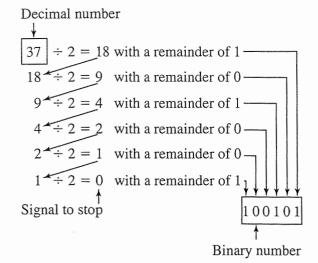Practice this procedure by converting the decimal number 37 to a binary number. Follow the procedure used before:



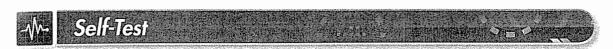Notice that you stop dividing by 2 when the quotient becomes 0. According to this procedure, the decimal number 37 is equal to the binary number 100101.



Supply the missing number in each statement.

- 15. The decimal number 39 equals _____ in binary.
- 16. The decimal number 100 equals _____ in binary.
- 17. The decimal number 133 equals _____ in binary.



2-5 Electronic Translators

If you were to try to communicate with a French-speaking person who did not know the English language, you would need someone to translate the English into French and then the French into English. A similar problem exists in digital electronics. Almost all digital circuits (calculators, computers) understand only binary numbers. But most people understand only decimal numbers. Thus we must have electronic devices that can translate from decimal to binary numbers and from binary to decimal numbers.

Figure 2-6 diagrams a typical system that might be used to translate from decimal to binary numbers and back to decimals. The device that translates from the keyboard decimal numbers to binary is called an *encoder*; the device

labeled *decoder* translates from binary to decimal numbers.

The bottom of Fig. 2-6 shows a typical conversion. If you press the decimal number 9 on the keyboard, the encoder will convert the 9 into the binary number 1001. The decoder will convert the binary 1001 into the decimal number 9 on the output display.

Encoders and decoders are very common electronic circuits in all digital devices. A pocket calculator, for instance, must have encoders and decoders to translate electronically from decimal to binary numbers and back to decimal. When you press the number 9 on the keyboard, the number appears on the output display.

In modern electronic systems, the encoding and decoding may be performed by *hardware* as suggested in Fig. 2-6, or by computer programs

Electronic translators

Decoders

Hardware

Encoders

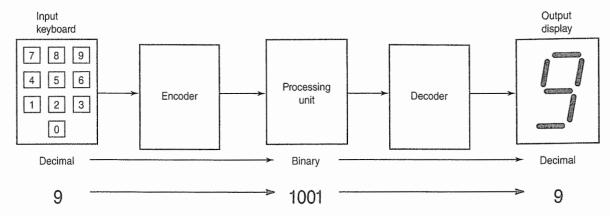


Fig. 2-6 A system using encoders and decoders.

Software

or *software*. In computer jargon to *encrypt* means to encode. Likewise, in computer software to decode means to convert unreadable or encrypted codes into readable numbers or text. In electronics hardware, to decode means to translate from one code to another. Usually an electronic decoder converts encrypted codes into a more readable form.

You can buy encoders and decoders that translate from any of the commonly used codes in digital electronics. Most of the encoders and decoders you will use will be packaged as single ICs.

General Definitions

Here are some general definitions:

Decode (verb). To translate from an encrypted code into a more readable form; for example, converting binary code to decimal.

Decoder (noun). A logic device that translates from binary code to decimal. Generally, it makes the conversion from processed data in a digital system to a more readable form such as alphanumeric.

Encode (verb). To translate or encrypt; for example, converting a decimal input into a binary code.

Encoder (noun). A logic device that translates from decimal to another code such as binary. Generally, it converts input information to a code useful to digital circuits.

Application: Encoders and Decoders

Manufacturers of integrated circuits (ICs) produce various encoders and decoders. These ICs make the job of translation from decimal to binary or binary to decimal easy.

The block diagram in Fig. 2-7(a) is an overview of an encoder-decoder system you may construct in the lab in later chapters. The encoder section features a 74147 decimal-to-binary encoder IC. The center block in Fig. 2-7(a) is the processing section. The simple processing in this example is to invert or complement the 4-bit binary number using a 7404 inverter IC. The final block in Fig. 2-7(a) shows a decoder that would translate binary to decimal. The decimal is displayed on a seven-segment LED. The 7447 binary-to-seven-segment LED decoder/driver IC performs this task. Various manufacturers produce these ICs.

The action of the encoder-decoder system when the decimal 7 is pressed on the keypad is detailed in Fig. 2-7(b).

Step 1. Press 7. Input 7 of the 74147 IC is activated by a LOW.

Step 2. Encoder (74147 IC) outputs *inverted binary* of 1000.

Step 3. Inverter (7404 IC) changes inverted binary 1000 to real binary of 0111. To invert or complement a binary number, change each bit to its opposite.

Step 4. Decoder (7447 IC) converts from binary 0111 to seven-segment LED code by driving lines to segments *a*, *b*, and *c* LOW. This lights only segments *a*, *b*, and *c* on the LED display, forming the decimal number 7.

The action of the encoder-decoder system when the decimal 2 is pressed on the keypad is detailed in Fig. 2-7(c).

Step 1. Press 2. Input 2 of the 74147 IC is activated by a LOW.

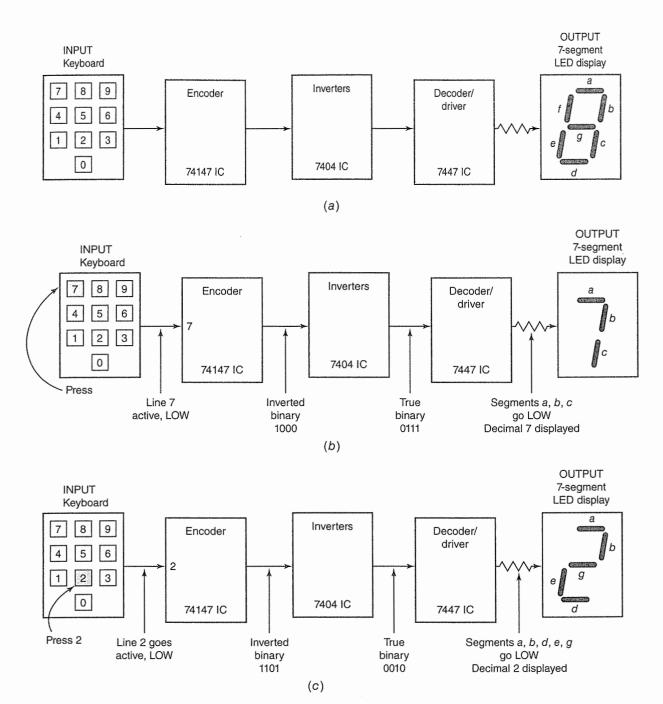


Fig. 2-7 (a) Encoder-decoder system (block diagram form). (b) Press 7 on keypad; result is 7 on the LED display. (c) Press 2 on keypad; result is 2 on the LED display.

Step 2. Encoder (74147 IC) outputs *inverted binary* of 1101.

Step 3. Inverter (7404 IC) changes inverted binary 1101 to real binary of 0010.

Step 4. Decoder (7447 IC) converts from binary 0010 to seven-segment LED code by driving lines to segments *a*, *b*, *d*, *e*, and *g* LOW. This lights only segments *a*, *b*, *d*, *e*, and *g* on the LED display, forming the decimal number 2.

A search of the Internet will reveal many other codes that are related to binary. Some of these codes will be covered later in this textbook.

You used hardware (integrated circuits) to make code conversions in this section. Most code conversions are done with software (programming of a microprocessor or microcontroller).

Self-Test

Supply the missing word in each statement.

- 18. A(n) ______ is an electronic device that translates a decimal input number to binary.
- 19. The processing unit of a calculator outputs binary. This binary is converted to a decimal output display by an electronic device called a(n) ______.
- 20. To translate or encrypt from a readable form of data to a binary-coded form is called _____ (decoding, encoding).
- 21. To translate from an encrypted code (such as binary) to a more readable form (such

- as decimal) is called _____ (decoding, encoding).
- 22. Refer to Fig. 2-8. With input line 3 to the 74147 encoder IC activated with a LOW, the 4-bit output at point *A* would be _____ (4 bits).
- 23. Refer to Fig. 2-8. The output from the 7404 inverter IC at point *B* would be ______ (4 bits).
- 24. Refer to Fig. 2-8. The output of the 7447 decoder IC would drive which segment lines LOW?

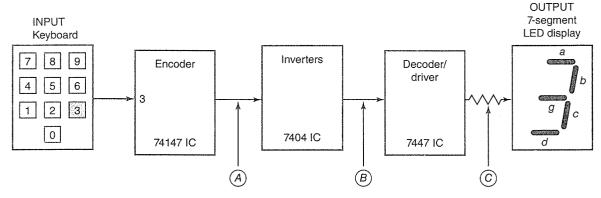


Fig. 2-8 Encoder-decoder system.



2-6 Hexadecimal Numbers

Hexadecimal number system Base 16 system Hexadecimal notation

Microprocessorbased systems Subscripts Base 10

Base 2

The hexadecimal number system uses the 16 symbols 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, and F and is referred to as the base 16 system. Figure 2-9 shows the equivalent binary and hexadecimal representations for the decimal numbers 0 through 17. The letter "A" stands for decimal 10, "B" for decimal 11, and so on. The advantage of the hexadecimal system is its usefulness in converting directly from a 4-bit binary number. For instance, hexadecimal F stands for the 4-bit binary number 1111. Hexadecimal notation is typically used to represent a binary number. For instance, the hexadecimal number A6 would represent the 8-bit binary

number 10100110. Hexadecimal notation is widely used in *microprocessor-based systems* to represent 4, 8-, 16-, 32-, or 64-bit binary numbers.

The number 10 represents how many objects? It can be observed from the table shown in Fig. 2-9 that the number 10 could mean ten objects, two objects, or sixteen objects depending on the base of the number. Subscripts are sometimes added to a number to indicate the base of the number. Using subscripts, the number 10_{10} represents ten objects. The subscript (10 in this example) indicates it is a base 10, or decimal, number. Using subscripts, the number 10_{2} represents two objects since this is in binary (base 2). Again using subscripts, the number

Decimal	Binary	Hexadecimal
0	0000	0
1	0001	1
2	0010	2
3	0011	3
4	0100	4
5	0101	5
6	0110	6
7	0111	7
8	1000	8
9	1001	9
10	1010	Ά
11	1011	В
12	1100	С
13	1101	D
14	1110	E
15	1111	F
16	10000	10
17	10001	11

Fig. 2-9 Binary and hexadecimal equivalents to decimal

10₁₆ represents sixteen objects since this is in hexadecimal (base 16).

Converting hexadecimal numbers to binary and binary numbers to hexadecimal is a common task when working with microprocessors and microcontrollers. Consider converting $C3_{16}$ to its binary equivalent. In Fig. 2-10(a), each hexadecimal digit is converted to its 4-bit binary equivalent (see Fig. 2-9). Hexadecimal C equals the 4-bit binary number 1100, while 3_{16} equals 0011. Combining the binary groups yields $C3_{16} = 11000011_2$.

Now reverse the process and convert the binary number 11101010 to its hexadecimal equivalent. The simple process is detailed in Fig. 2-10(b). The binary number is divided into 4-bit groups starting at the binary point. Next, each 4-bit group is translated into its equivalent hexadecimal number with the help of the table shown in Fig. 2-9. The example in Fig. 2-10(b) shows $11101010_2 = EA_{16}$.

Consider converting hexadecimal $2DB_{16}$ to its decimal equivalent. The place values for the first three places in the hexadecimal number are shown across the top in Fig. 2-11 as 256s, 16s, and 1s. In Fig. 2-11 there are eleven 1s. There are thirteen 16s, which equals 208. There are two 256s, which equals 512. Adding 11 + 208 + 512 will equal 731_{10} . The example given in Fig. 2-11 shows that $2DB_{16} = 731_{10}$.

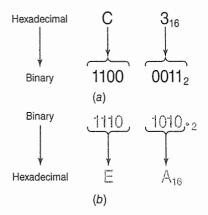


Fig. 2-10 (a) Converting a hexadecimal number to binary. (b) Converting a binary number to hexadecimal.

Place value	256s	16s	1s	_
Hexadecimal	2	D	B ₁₆	
	\downarrow	1	↓`°	
	256	16	1	
	× 2 512	× 13 208	× 11	
¥	312	200	11	
Decimal	512 +	208	$+ 11 = 731_{10}$	

Fig. 2-11 Converting a hexadecimal number to decimal.

Now reverse the process and convert the decimal number 47 to its hexadecimal equivalent. Figure 2-12 details the repeated divideby-16 process. The decimal number 47 is first divided by 16, resulting in a quotient of 2 with a remainder of 15. The remainder of 15 (F in hexadecimal) becomes the least significant digit (LSD) of the hexadecimal number. The quotient (2 in this example) is transferred to the dividend position and divided by 16. This results in a quotient of 0 with a remainder of 2. The 2 becomes the next digit in the hexadecimal number. The process is complete because the integer part of the quotient is 0. The divideby-16 process shown in Fig. 2-12 converts 47₁₀ to its hexadecimal equivalent of 2F₁₆.

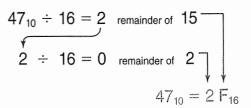


Fig. 2-12 Converting a decimal number to hexadecimal using the repeated divide-by-16 process.

Base 16

Hex-to-binary conversion

Binary-to-hex conversion

Decimal-to-hex conversion

Repeated divide-by-16 process




Connection
Search the web

for number system conversion tools.



Supply the missing number in each statement.

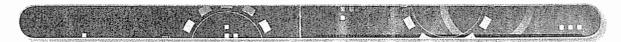- 25. Decimal 15 equals _____ in hexadecimal.
- 26. Hexadecimal A6 equals ______ in binary.
- 27. Binary 11110 equals ______ in hexadecimal.
- 28. Hexadecimal 1F6 equals _____ in decimal.
- 29. Decimal 63 equals ______ in hexadecimal.



2-7 Octal Numbers

Some older computer systems use octal numbers to represent binary information. The *octal number system* uses the eight symbols 0, 1, 2, 3, 4, 5, 6, and 7. Octal numbers are also referred to as *base* 8 numbers. The table shown in Fig. 2-13 gives the equivalent binary and octal representations for decimal numbers 0 through 17. The advantage of the octal system is its usefulness in converting directly from a 3-bit binary number. Octal notation is used to represent binary numbers.

Octal-to-binary conversion

Octal number system

Converting octal numbers to binary is a common operation when using some computer systems. Consider converting the octal number 67₈ (say "six seven base eight") to its binary

Decimal	Binary	Octal
0	000	0
1	001	1
2	010	2
3	011	3
4	100	4
5	101	5
6	110	6
7	111	7
8	001 000	10
9	001 001	11
10	001 010	12
11	001 011	13
12	001 100	14
13	001 101	15
14	001 110	16
15	001 111	17
16	010 000	20
17	010 001	21

Fig. 2-13 Binary and octal equivalents to decimal numbers.

Octal 	6	7 ₈	
Binary V Octal	100	001 1 (b)	101°2 5 ₈

Fig. 2-14 (a) Converting an octal number to binary. (b) Converting a binary number to octal.

equivalent. In Fig. 2-14(a), each octal digit is converted to its 3-bit binary equivalent. Octal 6 equals 110, while 7 equals 111. Combining the binary groups yields $67_8 = 110111_2$.

Now reverse the process and convert binary 100001101 to its octal equivalent. The simple process is detailed in Fig. 2-14(b). The binary number is divided into 3-bit groups (100 001 101) starting at the binary point. Next, each 3-bit group is translated into its equivalent octal number. The example in Fig. 2-14(b) shows 100 001 101₂ = 415_e.

Consider *converting octal* 415 (say "four one five base eight") to its decimal equivalent. The place values for the first three places in the octal number are shown across the top in Fig. 2-15 as 64s, 8s, and 1s. There are five 1s and one 8. There are four 64s, which equals 256. Adding $5 + 8 + 256 = 269_{10}$. The example in Fig. 2-15 shows that $415_8 = 269_{10}$.

Now reverse the process and convert the decimal number 498 to its octal equivalent. Figure 2-16 details the repeated divide-by-8

Octal-to-decimal conversion

Decimal-to-octal conversion

Repeated divide-by-8 process

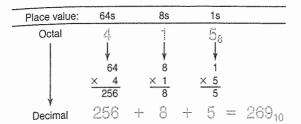


Fig. 2-15 Converting an octal number to decimal.

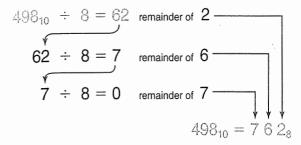


Fig. 2-16 Converting a decimal number to octal using the repeated divide-by-8 process.

process. The decimal number 498 is first divided by 8, resulting in a quotient of 62 with a remainder of 2. The remainder (2) becomes the LSD of the octal number. The quotient (62 in this example) is transferred to the dividend position and divided by 8. This results in a quotient of 7 with a remainder of 6. The 6 becomes the next digit in the octal number. The last quotient (7 in this example) is transferred to the dividend position and divided by 8. The

ABOUT ELECTRONICS



Microprocessors Then and Now. The Intel 4004 4-bit microprocessor was unveiled in 1971. The 4004 processor contained about 2300 transistors. Using a web search, determine current microprocessor complexity.

quotient is 0 with a remainder of 7. The 7 is the most significant digit (MSD) in the octal number. The divide-by-8 process shown in Fig. 2-16 converts 498_{10} to its octal equivalent of 762_8 . Note that the signal to end the repeated divide-by-8 process is when the quotient becomes 0.

Technicians, engineers, and programmers must be able to convert between number systems. Many commercial calculators can aid in making binary, octal, hexadecimal, and decimal conversions. These calculators also perform arithmetic operations on binary, octal, and hexadecimal as well as decimal numbers.

Most home and school computers feature various calculators. When working with varied number systems, select the *scientific calculator*. This will allow you to make number system conversions (between binary, octal, hex, and decimal). The scientific calculator will also allow arithmetic calculations (add, subtract, etc.) in various number systems.

-∕M- Self-Test

Supply the missing number in each statement.

- 30. Octal 73 equals _____ in binary.
- 31. Binary 100000 equals _____ in octal.
- 32. Octal 753 equals ______ in decimal.
- 33. Decimal 63 equals ______ in octal.

2-8 Bits, Bytes, Nibbles and Word Size

A single binary number (either a 0 or a 1) is called a *bit*. Bit is an abbreviation for a *b*inary digit. The bit is the smallest unit of data in a digital system. Physically in a digital circuit a single bit is commonly represented by a HIGH or LOW voltage. On a magnetic storage medium

(such as a hard disk) a bit is a small section that can be either a 1 or 0. On an optical disk (such as a CD-ROM) a bit is a small area that either is a pit or no pit for a 1 or 0.

All but the simplest digital devices handle larger data groups which in computer jargon may be called *words*. For most computer systems, the width of the main data bus is the same as the *word size*. For instance, a microprocessor

Bit

Word size

Nibble

Byte

or microcontroller might operate on and store 8-bit groups as a single unit of data. Many common microprocessors have word lengths of 8, 16, 32, or 64 bits. A 16-bit piece of data is commonly referred to as a word. A double-word contains 32 bits. A quad-word features 64 bits.

An 8-bit group of data that represents a number, letter, punctuation mark, control character, or some operation code (op code) in a digital device is called a byte. For instance, the hexadecimal number 4F is shorthand for the byte 0100 1111. A byte is an abbreviation for binary term. A byte represents a small amount of information, and in memory devices we talk of kilobytes (210 or 1024 bytes), megabytes (220 or 1,048,576 bytes), or gigabytes (230 or 1,073, 741,824 bytes) of storage.

A simple digital device might be designed to handle a 4-bit group of data. A half-byte or a 4-bit group of data is called a nibble. For instance, the hexadecimal number C is shorthand for the nibble 1100.

In summary, the common names for binary digit groupings are

Bit	1 bit (such as 0 or 1)
Nibble	4 bits (such as 1010)
Byte	8 bits (such as 1110 1111)
Word	16 bits (such as 1100 0011

1111 1010)

Double-word 32 bits (such as 1001 1100

1111 0001 0000 1111 1010

0001)

64 bits (such as 1110 1100 Quad-word


1000 0000 0111 0011 1001 1000 0011 0000 1111 1110

1001 0111 0101 0001)




Supply the missing word in each statement.

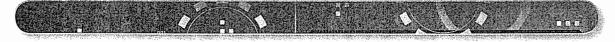- 34. A single binary digit (such as a 0 or 1) is commonly called a _____ (bit, word).
- 35. An 8-bit data group that represents a number, letter, punctuation mark, or control character is commonly referred to as a _____ (byte, nibble).
- 36. A 4-bit data group that represents some number or code is called a _ (nibble, octet).
- 37. The length of data groups in a computer system is commonly referred to as its _ (memory, word) size.
- 38. A 32-bit data group in a computer system is commonly referred to as a _____ (double-word, nibble).
- 39. A word in a computer system most often suggests a _____ (16-bit, 256-bit) data group.



Chapter 2 Summary and Review

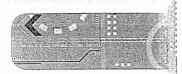

Summary

- 1. The decimal number system contains 10 symbols: 0, 1, 2, 3, 4, 5, 6, 7, 8, and 9.
- 2. The binary number system contains two symbols: 0 and 1.
- 3. The place values left on the binary point in binary are 128, 64, 32, 16, 8, 4, 2, and 1.
- All men and women in the field of digital electronics must be able to convert binary to decimal numbers and decimal to binary numbers.
- 5. Encoders are electronic circuits that convert decimal numbers to binary numbers.
- 6. Decoders are electronic circuits that convert binary numbers to decimal numbers.
- 7. By general definition, to encode means to convert a readable code (such as decimal) to an encrypted code (such as binary).

- 8. By general definition, to decode means to convert a machine code (such as binary) to a more readable form (such as alphanumeric).
- 9. The hexadecimal number system contains 16 symbols: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, and F.
- 10. Hexadecimal digits are widely used to represent binary numbers in the computer field.
- 11. The octal number system uses eight symbols: 0, 1, 2, 3, 4, 5, 6, and 7. Octal numbers are used to represent binary numbers in a few computer systems.
- 12. Data groupings have common names including bit, nibble (4 bits), byte (8 bits), word (16 bits), doubleword (32 bits), and quad-word (64 bits).

Chapter Review Questions

Answer the following questions.

- 2-1. How would you say the decimal number 1001?
- 2-2. How would you say the binary number 1001?
- 2-3. Convert the binary numbers in **a** to **j** to decimal numbers:
 - a. 1
- f. 10000
- b. 100
- g. 10101
- c. 101
- h. 11111
- d. 1011
- i. 11001100
- e. 1000
- j. 11111111
- 2-4. Convert the decimal numbers in **a** to **j** to binary numbers:
 - a. 0
- f. 64
- b. 1
- g. 69
- c. 18
- g. 09
- d. 25
- h. 128i. 145
- e. 32
- j. 1001

- 2-5. Encode the decimal numbers in **a** to **f** to binary numbers:
 - a. 9
- d. 13
- b. 3
- e. 10
- c. 15
- f. 2
- 2-6. Decode the binary numbers in **a** to **f** to decimal numbers:
 - a. 0010
- d. 0111
- b. 1011
- e. 0110
- c. 1110
- f. 0000
- 2-7. What is the job (function) of an encoder?
- 2-8. What is the job (function) of a decoder?
- 2-9. Write the decimal numbers from 0 to 15 in binary.
- 2-10. Convert the hexadecimal numbers in **a** to **d** to binary numbers:
 - a. 8A
- c. 6C
- b. B7
- d. FF

Chapter Review Questions...continued

- 2-11. Convert the binary numbers in a to d to hexadecimal numbers: a. 01011110 c. 11011011 b. 00011111 d. 00110000
- 2-13. Decimal $4095 = _{16}$.

- 2-16. A single 0 or 1 is commonly called a ___ (bit, word).
- 2-17. An 8-bit group of 1s and 0s, which represents a number, letter, or op code, is commonly called a ____ (byte, nibble).

2-18.	A nibble is	a term	that describes a
		(4-bit,	12-bit) data group.

- 2-19. Microprocessor-based systems (such as a computer) commonly identify the size of a data group as _____ (file, word) length.
- 2-20. To encrypt data from a readable form (such as alphanumeric) to machine code usable by digital circuits is called _____ (encoding, interfacing).

Critical Thinking Questions

- 2-1. If the digital circuits in a computer only respond to binary numbers, why are octal and hexadecimal numbers used extensively by computer specialists?
- 2-2. In a digital system such as a microcomputer, it is common to consider an 8-bit group (called a byte) as having a meaning. Predict some of the possible meanings of a byte (such as 11011011₂) in a microcomputer.
- 2-3. At the option of your instructor, use circuit simulation software to (a) draw the logic diagram of the decimal-to-binary encoder circuit sketched in Fig. 2-17, (b) operate the circuit, and (c) demonstrate the decimal-to-binary encoder simulation to your instructor.
- 2-4. At the option of your instructor, use circuit simulation software to (a) draw the logic diagram of the binary-to-decimal decoder circuit shown in Fig. 2-18, (b) operate the circuit, and (c) demonstrate the binary-to-decimal decoder simulation to your instructor.
- 2-5. At the direction of your instructor, use a scientific calculator to convert from one number system to another. Show the instructor your procedure and results.
- 2-6. At the direction of your instructor, use a website to convert from one number system to another. Show the instructor your results.

Critical Thinking Questions...continued

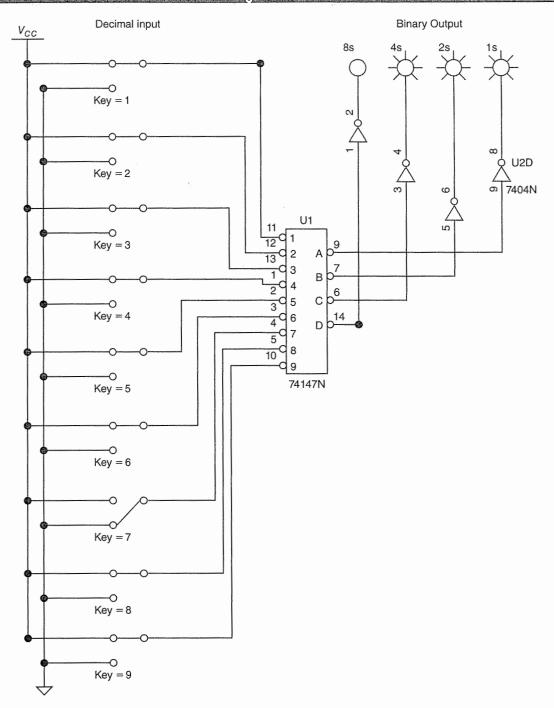


Fig. 2-17 Decimal-to-binary encoder circuit.

Critical Thinking Questions...continued


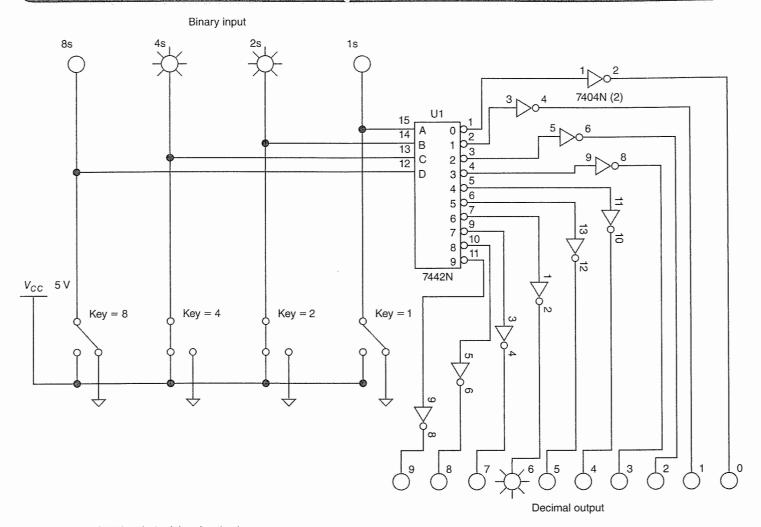


Fig. 2-18 Binary (BCD)-to-decimal decoder circuit.

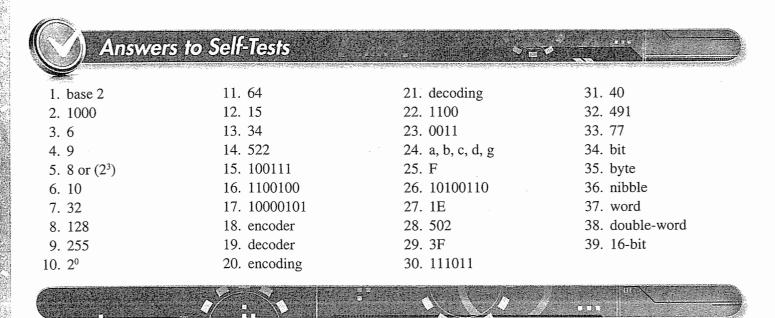



Logic Gates

Learning Outcomes

This chapter will help you to:

- 3-1 Memorize the name, symbol, truth table, function, and Boolean expression for the seven basic logic gates (AND, OR, NOT, NAND, NOR, XOR, XNOR).
- 3-2 Draw a logic diagram of any of the seven basic logic functions using only NAND gates.
- **3-3** Sketch logic diagrams illustrating how two-input gates could be used to create gates with more inputs.
- **3-4** *Convert* one type of basic gate to any other logic function by using inverters.
- **3-5** *Identify* pin numbers and manufacturer's markings on both TTL and CMOS DIP package ICs.
- **3-6** *Troubleshoot* simple logic gate circuits.
- 3-7 Recognize new logic gate symbols used in dependency notation (IEEE standard 91-1984).
- **3-8** Analyze the operation of several simple logic gate applications.

omputers, calculators, and other digital devices are sometimes looked upon by the general public as being magical. Actually, digital electronic devices are extremely logical in their operation. The basic building block of any digital circuit is a *logic gate*. Persons working in digital electronics understand and use logic gates every day. Remember that logic gates are the building blocks for even the most complex computers. Logic gates can be constructed by using simple switches, relays, vacuum tubes, transistors and diodes, or ICs. Because of their availability, wide use, and low cost, ICs will be used to construct digital circuits. A variety of logic gates are available in all logic families including TTL and CMOS.

The task performed by a logic gate is called its *logic function*. Logic functions can be implemented by hardware (logic gates) or by programming devices such as microcontrollers or computers.

Logic gates

Logic function

3-1 The AND Gate

The AND gate is sometimes called the "all or nothing gate." Fig. 3-1 shows the basic idea of the AND gate using simple switches.

What must be done in Fig. 3-1 to get the output lamp (L_1) to light? You must close both switches A and B to get the lamp to light. You could say that switch A and switch B must be closed to get the output to light. The AND gates you will operate most often are constructed of diodes and transistors and packaged inside an IC. To show the AND gate, we use the logic symbol in Fig. 3-2. This is the symbol you will memorize and use from now on for AND gates.

"All or nothing" gate

AND gate logic symbol



as an AND gate.

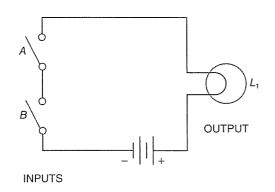


Fig. 3-1 AND circuit using switches.



Fig. 3-2 AND gate logic symbol.

The term "logic" is usually used to refer to a decision-making process. A logic gate, then, is a circuit that can decide to say yes or no at the output based upon the inputs. We already determined that the AND gate circuit in Fig. 3-1 says yes (light on) at the output only when we have a yes (switches closed) at *both* inputs.

Now let us consider an actual circuit similar to one you will set up in the laboratory. The AND gate in Fig. 3-3 is connected to input switches A and B. The output indicator is an LED. If a LOW voltage (GND) appears at both inputs A and B, then the output LED is not lit. This situation is illustrated in line 1 of the truth table in Fig. 3-4. Notice also in line 1 that the inputs and outputs are given as binary digits. Line 1 indicates that if the inputs are binary 0 and 0, then the output will be a binary 0. Carefully look over the four combinations of switches A and B in Fig. 3-4. Notice that

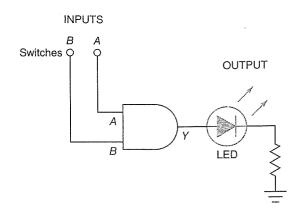


Fig. 3-3 Practical AND gate circuit.

only binary 1s at both A and B will produce a binary 1 at the output (see the last line of the table).

It is a +5 V compared to GND appearing at A, B, or Y that is called a binary 1 or a HIGH voltage. A binary 0, or LOW voltage, is defined as a GND voltage (near 0 V compared to GND) appearing at A, B, or Y. We are using positive logic because it takes a positive 5 V to produce what we call a binary 1. You will use positive logic in most of your work in digital electronics.

The table in Fig. 3-4 is called a *truth table*. The truth table for the AND gate gives all the possible input combinations of *A* and *B* and the resulting outputs. Thus the truth table defines the exact operation of the AND gate. The truth table in Fig. 3-4 is said to describe the AND *function*. You should memorize the truth table for the AND function. The unique output from the AND gate is a HIGH only when all inputs are HIGH. The output column in Fig. 3-4 shows that *only* the last line in the AND truth table generates a 1 while the rest of the outputs are 0.

So far you have memorized the logic symbol and the truth table for the AND gate. Now you

	INP	ОUТ	PUT		
В		Α		Y	
Switch voltage	Binary	Switch voltage	Binary	Light	Binary
LOW	0	LOW	0	No	0
LOW	0	HIGH	1	No	0
HIGH	1	LOW	0	No	0
HIGH	1	HIGH	1	Yes	1

Fig. 3-4 AND truth table.

Positive logic

Truth table

AND function

will learn a shorthand method of writing the statement "input A is ANDed with input B to get output Y." The short method used to represent this statement is called its Boolean expression ("Boolean" from Boolean algebra-the algebra of logic). The Boolean expression is a universal language used by engineers and technicians in digital electronics. Figure 3-5 shows the ways to express that input A is ANDed with input B to produce output Y. The top expression in Fig. 3-5 is how you would tell someone in the English language that you are logically ANDing inputs A and B to get output Y. Next in Fig. 3-5 you see the Boolean expression for ANDing inputs A and B. Note that a multiplication dot (·) is used to symbolize the AND function in Boolean expressions. In common practice the Boolean expression $A \cdot B = Y$ can be simplified to AB = Y. Both $A \cdot B = Y$ or AB = Y describe the two-input AND function.

Examine the output column of the AND truth table in Fig. 3-5. You will notice that the *unique output* is the last line in the truth table when output Y is HIGH. The AND function's unique output is a HIGH output *only* when all inputs are HIGH.

Summary

The four commonly used methods of expressing the ANDing of inputs A and B are detailed

In the English language	Input A is ANDed with input B to get output Y.
As a Boolean expression	$A \cdot B = Y$ AND symbol
As a logic symbol	A
	A B Y
	0 0 0
As a truth table	0 1 0
	1 0 0
	1 1 1

Fig. 3-5 Four ways to express the logical ANDing of A and B.

Boolean expression

Boolean algebra

in Fig. 3-5. All these methods are widely used and must be learned by persons working in the electronics industry.

The term *logic function* implies the logical relationship between inputs and output while *logic gate* suggests the physical implementation. We might say that an AND logic gate (IC) performs the AND function.

The unique output of the AND function is a HIGH output only when all inputs are HIGH.

-√/>-

Self-Test

Answer the following questions.

- 1. Write the Boolean expression for a twoinput AND gate.
- 2. Refer to Fig. 3-3. When both inputs are HIGH, output *Y* will be ______ (HIGH, LOW) and the LED will _____ (light, not light).
- 3. Refer to Fig. 3-6. The output of the AND gate at time period t_1 is a logical _____(0, 1).
- 4. Refer to Fig. 3-6. The output of the AND gate at time period t_2 is a logical ______(0, 1).
- 5. Refer to Fig. 3-6. The output of the AND gate at time period t_3 is a logical _____(0, 1).

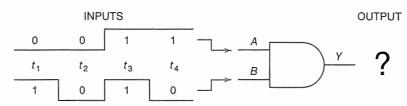


Fig. 3-6 Pulse train problem.

- 6. Refer to Fig. 3-6. The output of the AND gate at time period t_{4} is a logical (0, 1).
- 7. The unique output of an AND gate is a _ (HIGH, LOW) output only when all inputs are HIGH.
- 8. Refer to Fig. 3-7. If all three inputs (A, B, and C) to the AND gate are HIGH, then output Y will be _____ (HIGH, LOW).

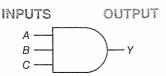


Fig. 3-7 Logic symbol for a threeinput AND gate.



The OR Gate 3-2

OR gate "Any or all" gate

Inclusive OR

function

The OR gate is sometimes called the "any or all gate." Figure 3-8 illustrates the basic idea of the OR gate using simple switches. Looking at the circuit in Fig. 3-8, you can see that the output lamp will light when either or both of the input switches are closed but not when both are open. A truth table for the OR circuit is shown in Fig. 3-9. The truth table lists the switch and light conditions for the OR gate circuit in Fig. 3-8. The truth table in Fig. 3-8 is said to describe the inclusive OR function. The unique output from the OR gate is a LOW only when all inputs are LOW. The output column in Fig. 3-9 shows that

INPUTS OUTPUT

OR gate truth table

Fig. 3-8 OR circuit using switches.

only the first line in the OR truth table generates a 0 while all others are 1.

The logic symbol for the OR gate is diagrammed in Fig. 3-10. Notice in the logic diagram that inputs A and B are being ORed to produce an output Y. The engineer's Boolean expression for the OR function is also illustrated in Fig. 3-10. Note that the plus (+) sign is the Boolean symbol for OR.

You should memorize the logic symbol, Boolean expression, and truth table for the OR gate.

A brief summary of the OR function is shown in Fig. 3-11. It lists four methods of describing the logical ORing of two variables (A and B).

The unique output of the OR function is a LOW output only when all inputs are LOW. Examining the Y output column of the OR truth table in Fig. 3-11 shows that the first line describes the unique output condition for this logic gate.

	INP	OUT	PUT		
А	A B		1	1	
Switch	Binary	Switch	Binary	Light	Binary
Open	0	Open	0	No	0
Open	0	Closed	1	Yes	1
Closed	1	Open	0	Yes	1
Closed	1	Closed	1	Yes	1

Fig. 3-9 OR gate truth table.

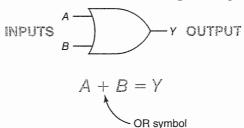


Fig. 3-10 OR logic gate symbol and Boolean expression.

Describing the OR Function

Input A is ORed with input B to yield output Y.
A + B = Y
A
A B Y
0 0 0
0 1 1
1 0 1
1 1 1

Fig. 3-11 Four ways to express the logical ORing of inputs A and B.

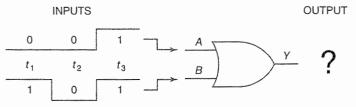


Fig. 3-12 Pulse train problem.

NA Self-Test

Answer the following questions.

- 9. Write the Boolean expression for a twoinput OR gate.
- 10. Refer to Fig. 3-12. The output of the OR gate at time period t_1 is a logical ______(0, 1).
- 11. Refer to Fig. 3-12. The output of the OR gate at time period t_2 is a logical ______(0, 1).
- 12. Refer to Fig. 3-12. The output of the OR gate at time period t_3 is a logical ______(0, 1).
- 13. The unique output of an OR gate is a _____ (HIGH, LOW) output only when all inputs are LOW.

- 14. Technically the truth table in Fig. 3-11 describes the _____ (exclusive, inclusive) OR logic function.
- 15. Refer to Fig. 3-13. If all three inputs (*A*, *B*, and *C*) to the OR gate are LOW, then output *Y* will be _____ (HIGH, LOW).

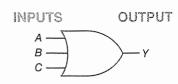


Fig. 3-13 Logic symbol for a three-input OR gate.



3-3 The Inverter and Buffer

NOT circuit

Inverter

Complements Inverts INVERT function Negated

Invert bubble


Noninverting buffer/driver


All the gates so far have had at least two inputs and one output. The *NOT circuit*, however, has only one input and one output. The NOT circuit is often called an *inverter*. The job of the NOT circuit (inverter) is to give an output that is not the same as the input. The logic symbol for the inverter (NOT circuit) is shown in Fig. 3-14.

If we were to put in a logic 1 at input A in Fig. 3-14, we would get out the opposite, or a logical 0, at output Y. We say that the inverter complements or inverts the input. Figure 3-14 also shows how we would write a Boolean expression for the NOT, or INVERT function. Notice the use of the overbar (–) symbol above the output to show that A has been inverted or complemented. We say that the Boolean term \overline{A} would be "not A."

An alternative NOT symbol used in Boolean expressions is also shown in Fig. 3-14. Notice the use of the apostrophe symbol to show that *A* has been inverted or complemented. We would say that the Boolean term *A'* would be "not A" or "A not." The use of the overbar is the preferred NOT symbol, but the apostrophe is common when Boolean expressions are shown on a computer screen as in circuit simulation programs.

The truth table for the inverter is shown in Fig. 3-15. If the voltage at the input of the inverter is LOW, then the output voltage is HIGH. However, if the input voltage is HIGH, then the

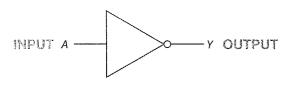

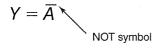

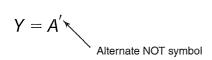


Fig. 3-14 A logic symbol and Boolean expression for an inverter.

INPUT		OUTPUT	
A	1	Υ	
Voltages	Binary	Voltages	Binary
LOW	0	HIGH	1
HIGH	1	LOW	0

Fig. 3-15 Truth table for an inverter.

output is LOW. As you learned, the output is always opposite the input. The truth table also gives the characteristics of the inverter in terms of binary 0s and 1s.

You learned that when a signal passes through an inverter, it can be said that the input is inverted or complemented. We can also say it is *negated*. The terms "negated," "complemented," and "inverted," then, mean the same thing.

The logic diagram in Fig. 3-16 shows an arrangement where input A is passed through two inverters. Input A is first inverted to produce a "not A" (\overline{A}) and then inverted a second time for a "double not A" (\overline{A}) . In terms of binary digits, we find that when the input 1 is inverted twice, we end up with the original digit. Therefore we find that \overline{A} equals A. Thus, a Boolean term with two bars over it is equal to the term under the two bars, as shown at the bottom of Fig. 3-16.

Two symbols found in logic diagrams that look something like an inverter symbol are pictured in Fig. 3-17. The logic symbol in Fig. 3-17(a) is an alternative symbol for an inverter and performs the NOT function. The placement of the *invert bubble* on the left side of the inverter symbol in Fig. 3-17(a) might suggest that this is an active LOW input.

The symbol in Fig. 3-17(b) is that of a non-inverting buffer/driver. The noninverting buffer serves no logical purpose (it does not invert), but is used to supply greater drive current at its output than is normal for a regular gate. Since

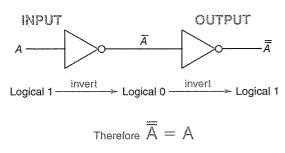


Fig. 3-16 Effect of double inverting.


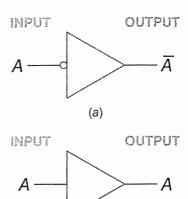


Fig. 3-17 (a) Alternative inverter logic symbol (note bubble at input). (b) Noninverting buffer/driver logic symbol.

(b)

regular digital ICs have limited drive current capabilities, the noninverting buffer/driver is important when interfacing ICs with other devices such as LEDs or lamps. Buffer/drivers are available in both noninverting and inverting form.

Another device that you will encounter in your work in digital electronics is the symbol in Fig. 3-18(a). It represents a common type of buffer/driver used with bus systems (buses are used in computers). The unit detailed in Fig. 3-18 is a three-state buffer. It looks like a regular buffer/driver device except that it has an extra control input. According to the truth table for the three-state buffer in Fig. 3-18(b), when the control (C) input goes HIGH, its output goes to a high-impedance state (high-Z state). In the high-impedance state, the output will act like an open switch between the output of the buffer and the bus. In its high-impedance state, the output of the buffer has no effect on the logic level on the bus to which it is connected. This allows several logic devices with three-state

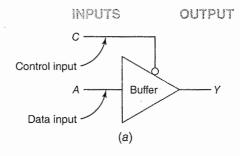

INPL	JTS	ОИТРИТ
С	Α	Υ
L	L	L
L .	Н	Н
Н	X	(Z)
Control input	Data input	-

L = Low voltage level

H = High voltage level

X = Don't care (Does not affect output)

(Z) = High impedance

(b)

Fig. 3-18 Noninverting buffer/driver (three-state output).

(a) Logic symbol for three-state buffer; (b) truth table for three-state buffer.

outputs to be connected to a bus at the same time, however, only one three-state device can be active at a time.

When the control input to the three-state buffer goes LOW (see Fig. 3-18), the buffer will transfer true (noninverted) data from input to output.

In summary, you now know the logic symbols, Boolean expression, and truth table for the inverter or NOT gate. Second, you can recognize the symbol for a noninverting buffer/driver and know its purpose is to drive LEDs, lamps, and so forth. Third, you can recognize a three-state buffer/driver and know it is used when connecting to bus systems.

three-state buffer

-/N- Self-Te

Answer the following questions.

- 16. Refer to Fig. 3-14. If input *A* is HIGH, output *Y* from the inverter will be
- 17. Refer to Fig. 3-16. If input *A* to the left inverter is LOW, the output from the right inverter will be _____.
- 18. Write the Boolean expression used to describe the action of an inverter.

- List two words that are used to mean "inverted."
- 20. Refer to Fig. 3-17(*b*). If input *A* is LOW, the output from this buffer will be
- 21. Refer to Fig. 3-19. The output of the three-state buffer during time period t_1 is ______ (HIGH, LOW, high impedance).

- 22. Refer to Fig. 3-19. The output of the three-state buffer during time period t_2 is _____ (HIGH, LOW, high impedance).
- 23. Refer to Fig. 3-19. The output of the three-state buffer during time period t_3 is ______ (HIGH, LOW, high impedance).

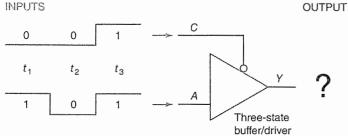


Fig. 3-19 Pulse train problem.



3-4 The NAND Gate

The AND, OR, and NOT gates are the three basic circuits that make up all digital circuits. The *NAND gate* is a NOT AND, or an inverted AND function. The standard logic symbol for the NAND gate is diagrammed in Fig. 3-20(a). The little *invert bubble* (small circle) on the right end of the symbol means to invert the output of AND.

Figure 3-20(b) shows a separate AND gate and inverter being used to produce the *NAND* logic function. Also notice that the Boolean expressions for the AND gate $(A \cdot B)$ and the NAND $(\overline{A} \cdot \overline{B})$ are shown on the logic diagram in Fig. 3-20(b).

The truth table for the NAND gate is shown at the right in Fig. 3-21. Notice that the truth table for the NAND gate is developed by *inverting the outputs* of the AND gate. The AND gate outputs are also given in the table for reference.

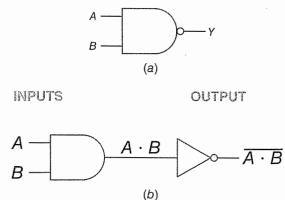


Fig. 3-20 (a) NAND gate logic symbol. (b) A Boolean expression for the output of a NAND gate.

INPUTS		OUT	PUT
В	А	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Fig. 3-21 Truth tables for AND and NAND gates.

Describing the NAND Function

In the English language			: NANDed ielding ou		
As a Boolean expression		* B =	OT symbol Y or ID symbol Or (A		Y
As a logic symbol		А В)o- y	
		Α	В	Υ	
		0	0	1	
As a truth table		0	1	1	
		1	0	1	
		1	1	0	
	<u> </u>				

Fig. 3-22 Four ways to express the logical NANDing of inputs A and B.

NAND gate

Invert bubble

NAND logic

NAND Boolean

NAND truth table

expression

function

symbol

NAND gate logic

Do you know the logic symbol, Boolean expression, and truth table for the NAND gate? You must commit these to memory. The unique output from the NAND gate is a LOW only when all inputs are HIGH. The NAND output column in Fig. 3-21 shows that *only* the last line in the truth table generates a 0 while all other outputs are 1.

A brief summary of the NAND function is shown in Fig. 3-22. It lists four methods of describing the logical NANDing of two variables (A and B). Several alternative methods

of writing the *NAND Boolean expression* are given in Fig. 3-22. The first two are traditional Boolean expressions using long overbars while the last [(AB)' = Y] is a computer version used to represent the NAND function.

The unique output of the NAND function is a LOW output only when all inputs are HIGH. Examining the *Y* output column of the NAND truth table in Fig. 3-22 shows that the last line describes the unique output condition for this logic gate.

3/2

Self-Test

Answer the following questions.

- 24. Write a Boolean expression for a twoinput NAND gate.
- 25. Refer to Fig. 3-23. The output of the NAND gate at time period t_1 is a logical ______ (0, 1).
- 26. Refer to Fig. 3-23. The output of the NAND gate at time period t_2 is a logical ______(0, 1).
- 27. Refer to Fig. 3-23. The output of the NAND gate at time period t_3 is a logical ______(0, 1).

- 28. The unique output of an NAND gate is a _____ (HIGH, LOW) output only when all inputs are HIGH.
- 29. Refer to Fig. 3-24. Write a Boolean expression that would represent the three-input NAND gate.
- 30. Refer to Fig. 3-24. If all three inputs (*A*, *B*, and *C*) to the NAND gate are HIGH, then output *Y* will be _____ (HIGH, LOW).

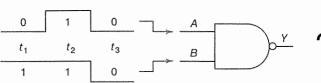


Fig. 3-23 Pulse train problem.

INPUTS

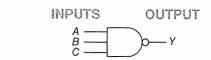


Fig. 3-24 Logic symbol for a three-input NAND gate.



OUTPUT

3-5 The NOR Gate

The *NOR gate* is actually a NOT OR gate. In other words, the output of an OR gate is inverted to form a NOR gate. The *logic symbol* for the NOR gate is diagrammed in Fig. 3-25(a). Note that the NOR symbol is an OR symbol with a small *invert bubble* (small circle) on the right side. The NOR function is being performed by an OR gate and an inverter in Fig. 3-25(b). The Boolean expression for the OR function (A + B)


is shown, The Boolean expression for the final NOR function is $\overline{A+B}$.

The truth table for the NOR gate is shown in Fig. 3-26. Notice that the NOR gate truth table is just the complement of the output of the OR gate. The output of the OR gate is also included in the truth table in Fig. 3-26 for reference.

You now should memorize the symbol, Boolean expression, and truth table for the NOR gate. You will encounter these items often in your work in digital electronics. The unique NOR gate

NOR gate logic symbol

Invert bubble

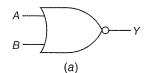

INPUTS

OUTPUT

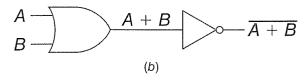


Fig. 3-25 (a) NOR gate logic symbol. (b) Boolean expression for the output of a NOR gate.

INPUTS		ОИТРИТ	
В	А	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Fig. 3-26 Truth table for OR and NOR gates.

NOR Boolean expression

NOR truth table

output from the NOR gate is a HIGH only when all inputs are LOW. The output column in Fig. 3-26 shows that *only* the first line in the NOR *truth table* generates a 1 while all other outputs are 0.

A brief summary of the NOR function is shown in Fig. 3-27. It lists four methods of describing the logical NORing of two variables

Describing the NOR Function

In the English language	Input A is input B yie	NORed velding out	vith tput Y.
As a Boolean expression	 A + (A	$\overline{B} = 0$ $\overline{B} = 0$ $\overline{B} = 0$ $\overline{B} = 0$	Y or
As a logic symbol	А\(\)) о—
	А	В	Y
	0	0	1
As a truth table	0	1	0
	1	0	0
	1	. 1	0

Fig. 3-27 Four ways to express the logical NORing of inputs A and B.

(A and B). Several alternative methods of writing the NOR Boolean expression are given in Fig. 3-27. The first is the traditional Boolean expression using a long overbar, while the last (A + B)' = Y is a computer version representing the NOR function.

The unique output of the NOR function is a HIGH output only when all inputs are LOW.

-W-

Self-Test

Answer the following questions.

- 31. Write a Boolean expression for a two-input NOR gate.
- 32. Refer to Fig. 3-28. The output of the NOR gate at time period t_1 is a logical ______ (0, 1).
- 33. Refer to Fig. 3-28. The output of the NOR gate at time period t_2 , is a logical ______ (0, 1).
- 34. Refer to Fig. 3-28. The output of the NOR gate at time period t_3 is a logical ______ (0, 1).
- 35. The unique output of an NOR gate is a _____ (HIGH, LOW) output only when all inputs are LOW.
- 36. Refer to Fig. 3-29. Write a Boolean expression that would represent the three-input NOR gate.


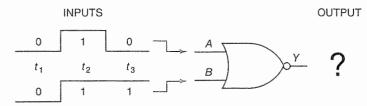


Fig. 3-28 Pulse train problem.

37. Refer to Fig. 3-29. If all three inputs (*A*, *B*, and *C*) to the NOR gate are LOW, then output *Y* will be _____ (HIGH, LOW).

Fig. 3-29 Logic symbol for a three-input NOR gate.

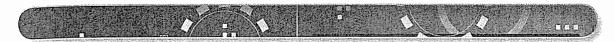

3-6 The Exclusive OR Gate

The exclusive OR gate is sometimes referred to as the "odd but not even gate." The term "exclusive OR gate" is often shortened to "XOR gate." The logic symbol for the XOR gate is diagrammed in Fig. 3-30(a); the Boolean expression for the XOR function is illustrated in Fig. 3-30(b). The symbol \oplus means the terms are XORed together.

The output for the XOR gate is shown at the right in Fig. 3-31. Notice that if any but not all of

the inputs are 1, then the output will be a binary, or logical, 1. The OR gate truth table is also given in Fig. 3-31, so that you may compare the OR gate truth table with the XOR gate *truth table*.

The unique characteristic of the XOR gate is that it produces a HIGH output only when an *odd* number of HIGH inputs are present. To demonstrate this idea, Fig. 3-32 depicts a three-input XOR gate logic symbol, a Boolean expression, and a truth table. In Fig. 3-32(b) the three-input XOR function is described in the output column (Y). The HIGH outputs are generated only when

Exclusive OR gate

XOR truth table

XOR gate

XOR function


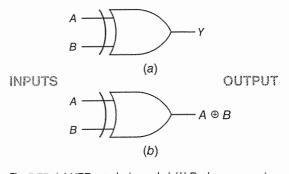


Fig. 3-30 (a) XOR gate logic symbol. (b) Boolean expression for the output of an XOR gate.

INPUTS		ОИТ	PUT
В	Α	OR	XOR
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

Fig. 3-31 Truth table for OR and XOR gates.

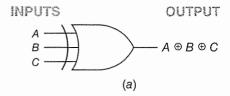

3-input XOR

INPUTS			OUTPUT
С	В	Α	Υ
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1
(b)			

Fig. 3-32 (a) Three-input XOR gate symbol and Boolean expression. (b) Truth table for three-input XOR gate.

XDR gate logic symbol

XOR Boolean expression

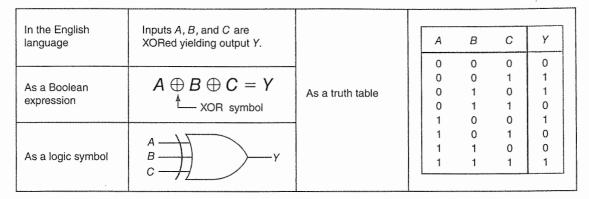


Fig. 3-33 Four ways to express the XDRing of inputs A, B, and \mathcal{L} .

an odd number of HIGH inputs are present (lines 2, 3, 5, and 8 in the truth table). If an even number of HIGH inputs to the XOR gate are present, the output will be LOW (lines 1, 4, 6, and 7 in the truth table). The XOR gates are used in a variety of arithmetic circuits.


A brief summary of the XOR (exclusive OR) function is shown in Fig. 3-33. It lists four methods of describing the logical XORing of three variables (A, B and C). The unique output of the XOR gate is a HIGH only when an *odd number* of inputs are HIGH.



Answer the following questions.

- 38. Write a Boolean expression for a three-input XOR gate.
- 39. Refer to Fig. 3-34. The output of the XOR gate at time period t_1 is a logical ______(0, 1).
- 40. Refer to Fig. 3-34. The output of the XOR gate at time period t_2 is a logical ______ (0, 1).
- 41. Refer to Fig. 3-34. The output of the XOR gate at time period t_3 is a logical ______ (0, 1).
- 42. Refer to Fig. 3-34. The output of the XOR gate at time period t_4 is a logical ______ (0, 1).

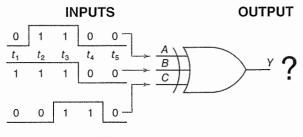- 43. Refer to Fig. 3-34. The output of the XOR gate at time period t_5 is a logical ______ (0, 1).
- 44. The unique output of an XOR gate is a HIGH when an _____ (even, odd) number of inputs are HIGH.



3-34 Pulse train problem.




Exclusive NOR gate XNOR function XNOR gate logic symbol

XNOR truth table

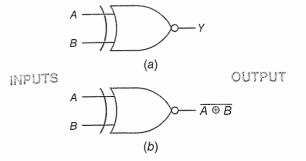3-7 The Exclusive NOR Gate

The term "exclusive NOR gate" is often shortened to "XNOR gate." The *logic symbol* for the XNOR gate is shown in Fig. 3-35(a). Notice that it is the XOR symbol with the added invert bubble on the output side. Figure 3-35(b) illustrates one of the Boolean expressions used for

the XNOR function. Observe that the Boolean expression for the XNOR gate is $\overline{A \oplus B}$. The bar over the $A \oplus B$ expression tells us we have inverted the output of the XOR gate. Examine the truth table in Fig. 3-35(c). Notice that the output of the XNOR gate is the complement of the XOR truth table. The XOR gate output is also shown in the table in Fig. 3-35(c).



INPUTS		OUTPUT	
А	В	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1
(c)			

Fig. 3-35 (a) XNOR gate logic symbol. (b) Boolean expression for the output of an XNOR gate. (c) Truth table for XOR and XNOR gates.

You now will have mastered the logic symbol, truth table, and *Boolean expression* for the XNOR gate.

A brief summary of the XNOR (exclusive NOR) function is shown in Fig. 3-36. It lists four methods of describing the logical XNORing of three variables (A, B and C). The unique

Describing the XNOR Function

In the English language	Inputs A, B, and C are XNORed yielding output Y.
As a Boolean expression	$ \begin{array}{c} $
As a logic symbol	A B C
As a truth table	A B C Y 0 0 0 1 0 0 1 0 0 1 0 0 0 1 1 1 1 0 0 0 1 0 1 1 1 1 0 1 1 1 1 0

Fig. 3-36 Four ways to express the logical XNDRing of inputs $A,\,B,\,\mathrm{and}\,\,C.$

XNOR Boolean expression

output of the XNOR gate is a LOW only when an *odd number* of inputs are HIGH which is the opposite from the XOR gate.

-/v- Self-Test

Answer the following questions.

- 45. Write a Boolean expression for a three-input XNOR gate.
- 46. Refer to Fig. 3-37. The output of the XNOR gate at time period t_1 is a logical ______ (0, 1).
- 47. Refer to Fig. 3-37. The output of the XNOR gate at time period t_2 is a logical ______ (0, 1).
- 48. Refer to Fig. 3-37. The output of the XNOR gate at time period t_3 is a logical _______(0, 1).
- 49. Refer to Fig. 3-37. The output of the XNOR gate at time period t_4 is a logical ______ (0, 1).

- 50. Refer to Fig. 3-37. The output of the XNOR gate at time period t_5 is a logical ______(0, 1).
- 51. The unique output of an XNOR gate is a _____ (HIGH, LOW) when an odd number of inputs are HIGH.


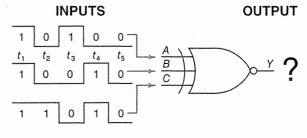


Fig. 3-37 Pulse train problem.

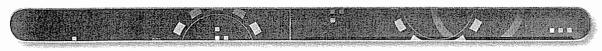

NANO gate as a universal gate

3-8 The NAND Gate as a Universal Gate

XNOR gate

So far in this chapter you have learned the basic building blocks used in all digital circuits. You also have learned about the seven types of gating circuits and now know the characteristics of the AND, OR, NAND, NOR, XOR, and XNOR gates and the inverter. You can buy ICs that perform any of these seven basic functions.

In looking through manufacturers' literature you will find that NAND gates seem to be more widely available than many other types of gates. Because of the NAND gate's wide use,

we shall show how it can be used to make other types of gates. We shall be using the NAND gate as a "universal gate."

The chart in Fig. 3-38 shows how you would wire NAND gates to create any of the other basic logic functions. The logic function to be performed is listed in the left column of the table; the customary symbol for that function is listed in the center column. In the right column of Fig. 3-38 is a symbol diagram of how NAND gates would be wired to perform the logic function. The chart in Fig. 3-38 need *not* be memorized, but it may be referred to as needed in your future work in digital electronics.

LOGIC FUNCTION	SYMBOL	CIRCUIT USING NAND GATES ONLY
Inverter	$A \longrightarrow \overline{A}$	$A \longrightarrow \overline{A}$
AND	A — A · B	A
OR	$A \longrightarrow A + B$	A — — — — — — — — — — — — — — — — — — —
NOR	$A \longrightarrow A + B$	$A \longrightarrow A + B$
XOR	$A \oplus B$	$A \oplus B$
XNOR	$ \begin{array}{c} A \\ B \end{array} $	$A \longrightarrow A \oplus B$

Fig. 3-38 Substituting NAND gates.



Self-Test

Answer the following questions.

- 52. The NAND gate can perform the invert function if the inputs are _____ (connected together, left open).
- 53. Refer to Fig. 3-39. Write a simple Boolean expression that would describe this two-input logic circuit (use *A* and *B* for inputs, *Y* as output).
- 54. Refer to Fig. 3-39. The output at Y from this logic diagram at time period t_1 is a logical ______(0, 1).
- 55. Refer to Fig. 3-39. The output at Y from this logic diagram at time period t_2 is a logical ______(0, 1).

- 56. Refer to Fig. 3-39. The output at Y from this logic diagram at time period t_3 is a logical ______ (0, 1).
- 57. Refer to Fig. 3-40. The output at Y from this logic diagram at time period t_1 is a logical _______(0, 1).
- 58. Refer to Fig. 3-40. The output at Y from this logic diagram at time period t_2 is a logical ______(0,1).
- 59. Refer to Fig. 3-40. The output at Y from this logic diagram at time period t_3 is a logical ______ (0,1).

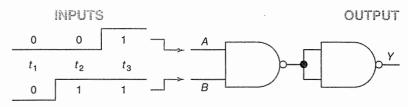


Fig. 3-39 Pulse train problem.

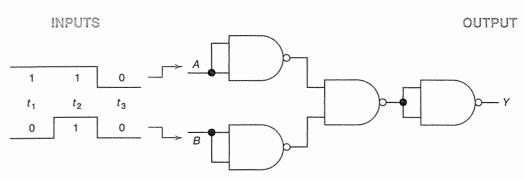


Fig. 3-40 Pulse train problem.



3-9 Gates with More Than Two Inputs


Figure 3-41(a) shows a three-input AND gate. The Boolean expression for the three-input AND gate is $A \cdot B \cdot C = Y$, as illustrated in Fig. 3-41(b). All the possible combinations of inputs A, B, and C are given in the truth table in Fig. 3-41(c); the outputs for the three-input

AND gate are tabulated in the right column of the truth table. Notice that with three inputs the possible combinations in the truth table have increased to eight (2³).

How could you produce a three-input AND gate as illustrated in Fig. 3-41 if you have only two-input AND gates available? The solution is given in Fig. 3-42(a). Note the wiring of the two-input AND gates on the right side of the

Gates with more than two inputs

Three-input AND gate

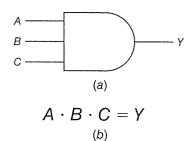

INPUTS			OUTPUT
A	В	С	Υ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
(c)			

Fig. 3-41 Three-input AND gate. (a) Logic symbol. (b) Boolean expression. (c) Truth table.

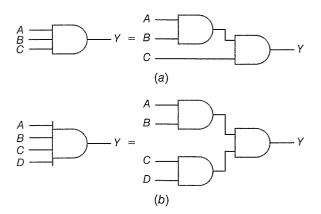



Fig. 3-42 Expanding the number of inputs. (a) Using two AND gates to wire three-input AND. (b) Using three AND gates to wire four-input AND.

Four-input AND qate

Four-input OR gate

diagram to form a three-input AND gate. Figure 3-42(b) illustrates how a *four-input* AND *gate* could be wired by using available two-input AND gates.

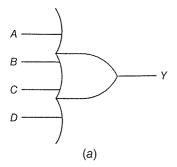The logic symbol for a four-input OR gate is illustrated in Fig. 3-43(a). The Boolean expression for the *four-input* OR *gate* is A + B + C + D = Y. This Boolean expression is written in Fig. 3-43(b). Read the Boolean expression A + B + C + D = Y as "input A or input B or input C or input D will equal output Y."



$$A + B + C + D = Y$$

INPUTS				OUTPUT
A	В	С	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1
		(c)		

Fig. 3-43 Four-input OR gate. (a) Lagic symbol illustrating the method used to show extra inputs beyond the width of the symbol. (b) Boolean expression. (c) Truth table.

Remember that the + symbol means the logic function OR in Boolean expressions. The truth table for the four-input OR gate is shown in Fig. 3-43(c). Notice that because of the four inputs there are 16 possible combinations (2⁴) of A, B, C, and D. To wire the four-input OR gate, you could buy the correct gate from a manufacturer of digital logic circuits or you could use two-input OR gates to wire the four-input OR gate. Figure 3-44(a) diagrams how you could wire a four-input OR gate using two-input OR gates. Figure 3-44(b) shows how to convert two-input OR gates into a three-input OR gate. Notice that the pattern of connecting both OR and

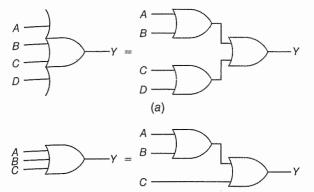


Fig. 3-44 Expanding the number of inputs to an OR gate.

AND gates to expand the number of inputs is the same (compare Figs. 3-42 and 3-44).

(b)

Expanding the number of inputs of a NAND gate is somewhat more difficult than expanding

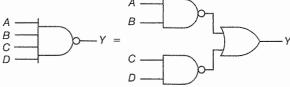


Fig. 3-45 Expanding the number of inputs to a NAND gate.


AND and OR gates. Figure 3-45 shows how a *four-input NAND gate* can be wired using 2 two-input NAND gates and 1 two-input OR gate.

You frequently will run into gates that have from two to as many as eight and more inputs. The basics covered in this section are a handy reference when you need to expand the number of inputs to a gate. Four-input NAND gate

-√v- Self-Test

Answer the following questions.

- 60. Write the Boolean expression for a three-input NAND gate.
- 61. The truth table for a three-input NAND gate would have _____ lines to include all the possible input combinations.
- 62. Write the Boolean expression for a four-input OR gate.
- 63. The truth table for a five-input NOR gate would contain _____ lines to include all the possible input combinations.
- 64. Refer to Fig. 3-46. This circuit generates the six-input _____ (AND, NAND, OR) logic function at output *Y*.

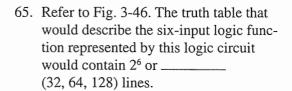

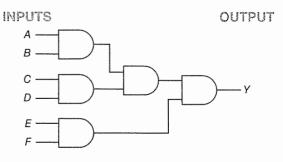


Fig. 3-46 Six-input logic circuit.



3-10 Using Inverters to Convert Gates

Frequently it is convenient to convert a basic gate such as an AND, OR, NAND, or NOR to another logic function. This can be done easily with the use of inverters. The chart in Fig. 3-47 is a handy

guide for converting any given gate to any other logic function. Look over the chart: Notice that in the top section only the outputs are inverted. Inverting the outputs leads to rather predictable results, shown on the right side of the chart.

The center section of the chart shows only the gate inputs being inverted. For instance, if Using inverters to convert gates

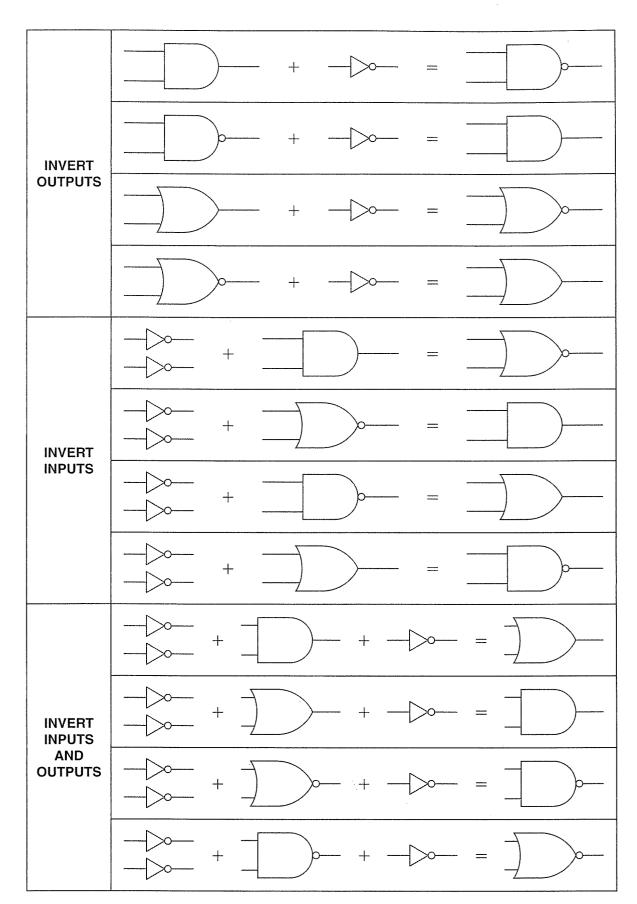


Fig. 3-47 Gate conversions using inverters. The \pm symbol here indicates combining the functions.

you invert both inputs of an OR gate, the gate generates the NAND function. This fact is emphasized in Fig. 3-48(a). Notice that the *invert bubbles* have been added to the inputs of the OR gate in Fig. 3-48(a), which converts the OR gate to a NAND function. Also, in the center section of the chart the inputs of the AND gate are being inverted. This is redrawn in Fig. 3-48(b). Notice that the invert bubbles at the input of the AND gate convert it into a NOR function. The new symbols at the left (with the input invert bubbles) in Fig. 3-48 are used in some logic diagrams in place of the more standard NAND and NOR logic symbols at the right. Be aware of these new symbols

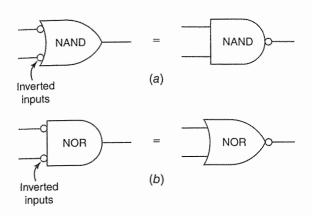


Fig. 3-48 Common alternative logic symbols. (a) NAND symbols. (b) NOR symbols. Nate: Invert bubbles at inputs commonly mean an active-LOW input.

because you will run into them in your future work in digital electronics.

Figure 3-49 illustrates how adding inverters (invert bubbles) to a logic symbol is described in Boolean expression form. Consider the NAND symbol at the left in Fig. 3-49(a) as an AND with an inverter attached to the output. The Boolean expression for the AND gate alone is $A \cdot B = Y$. Adding the inverter to the *output* of the AND gate in Fig. 3-49(a) is symbolized in the Boolean expression as a *long overbar* as $\overline{A \cdot B} = Y$. At the right in Fig. 3-49(a) is a simple truth table describing the NAND logic function.

Next consider the *alternative NAND symbol* in Fig. 3-49(b). Notice that the inverters (invert bubbles) are attached to the *inputs* of the OR symbol. Inverters at an input are symbolized with a short overbar as shown in Fig. 3-49(b). The $\overline{A} + \overline{B} = Y$ expression describes the alternative NAND logic symbol with its logic function shown in the NAND truth table at the right. The two Boolean expressions $\overline{A \cdot B} = Y$ and $\overline{A} + \overline{B} = Y$ both describe the NAND logic function. The two logic symbols at the left in Fig. 3-49 both produce the NAND truth table.

Applying *DeMorgan's theorem* (part of Boolean algebra) is a systematic way of converting simple logic functions to fundamental AND or OR circuits. DeMorgan's theorem will be covered in some detail in Chapter 4.


Invert bubbles

Alternative NDR symbol

Alternative NAND symbol

NAND truth table

Α	В	Y
0	0	1
0	1	1
1	0	1
1	1	0

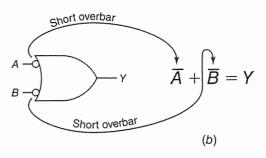

ong overbar

 AND truth table

 A
 B
 Y

 0
 0
 1

 0
 1
 1

 1
 0
 1

 1
 1
 0

Fig. 3-49 (a) NAND logic symbols. (b) Boolean expressions, and truth tables.

 $\overline{\cdot B} = Y$

(a)

The bottom section of the chart in Fig. 3-47 shows both the inputs and the outputs being inverted. Notice that by using inverters at the inputs and outputs, you can convert back and forth from AND to OR and from NAND to NOR.

With the 12 conversions shown in the chart in Fig. 3-47, you can convert any basic gate (AND, OR, NAND, and NOR) to any other gate with just the use of inverters. You will *not* need to memorize the chart in Fig. 3-47, but remember it for reference.


W:

Selfles

Supply the missing word in each sentence.

- 66. The OR gate can be converted to the NAND function by adding ______ to the inputs of the OR gate.
- 67. Adding inverters to the inputs of the AND gate produces the ______logic function.
- 68. Adding an inverter to the output of an AND gate produces the ______logic function.
- 69. Adding inverters to all inputs and outputs of an AND gate produces the ______logic function.
- 70. Write the Boolean expression for the standard NOR logic symbol shown in Fig. 3-50(*a*) (use long overbar).

71. Write the Boolean expression that best describes the alternative NOR logic symbol shown in Fig. 3-50(*b*) (use two short overbars).

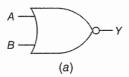

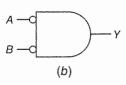


Fig. 3-50 NOR logic symbols.



3-11 Practical TTL Logic Gates

The popularity of digital circuits is due partly to the availability of inexpensive ICs. Manufacturers have developed many *families of digital ICs*. These families are groups of devices that can be used together. The ICs in a family are said to be compatible and can be easily connected to one another.

One group of families is manufactured using bipolar technology. These ICs contain parts comparable to discrete bipolar transistors. Transistor-transistor logic (TTL) digital ICs are constructed using bipolar-junction transistors (BJTs), diodes, and resistors.

A second group of digital IC families uses metal-oxide semiconductor (MOS) technology. CMOS Complementary metal-oxide semiconductor, (COMOS) ICs contain parts comparable to insulated-gate field-effect transistors (IGFETs). The CMOS family is a very low

power and widely used family using MOS technology. In the laboratory, you will have an opportunity to use both TTL and CMOS ICs.

IC Packaging

A traditional type of IC is illustrated in Fig. 3-51(a). This case style is referred to as a dual in-line package (DIP) by IC manufacturers. This particular IC is called a 14-pin DIP IC.

Just *counterclockwise* from the notch on the IC in Fig. 3-51(a) is pin 1. The pins are numbered counterclockwise from 1 to 14 when viewed from the top of the IC. A dot on the top of the DIP IC as in Fig. 3-51(b) is another method used to locate pin 1.

The ICs in Fig. 3-51(a) and (b) have longer pins that are commonly inserted through holes drilled in a printed circuit board and soldered to copper traces on the *bottom*. The two ICs in Fig. 3-51(c) and (d) are much smaller and have shorter pins bent to be soldered to the traces on

Families of digital ICs

Dual in-line package (DIP)

Bipalar technology

Metal-oxide semiconductor (MOS) technology

CMOS family

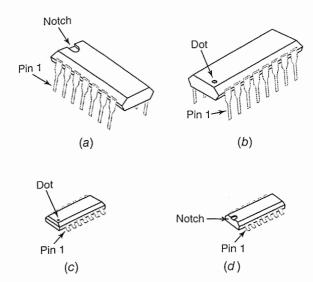


Fig. 3-51 Dual in-line package (DIP) ICs. Regular and micro size. (a) Regular-size DIP- locating pin 1 using a notch. (b) Regular-size DIP-locating pin 1 using a dot. (c) Micro-size DIP surface mount IC locating pin 1 using a dot. (d) Microsize DIP surface-mount IC locating pin 1 using a notch.

the *top* of the PC board. The smaller micropackages in Fig. 3-51(c) and (d) are commonly called *SMT* (*surface-mount technology*) packages. The SMT packages are typically much smaller in order to save PC board space and are easier to align when being positioned and soldered using automated manufacturing equipment. Two methods of locating pin 1 on the small SMT packages are illustrated in Fig. 3-51(c) and (d). In your school lab you will probably use the larger DIP IC, which is shown in Fig. 3-51(a) with long pins because they can be inserted into a solderless breadboard.

Manufacturers of ICs provide pin diagrams similar to the one shown in Fig. 3-52. This IC contains 4 two-input AND gates. Thus, it is called a quadruple two-input AND gate. This 7408 unit is one of many of the 7400 series of TTL ICs available. The power connections to the IC are the GND (pin 7) and V_{CC} (pin 14) pins. All other pins are the inputs and outputs to the four TTL AND gates.

IC Wiring

Given the logic diagram in Fig. 3-53(a), wire this circuit using the 7408 TTL IC. A wiring diagram for the circuit is shown in Fig. 3-53(b). A 5-V dc regulated power supply is typically used with TTL devices. The positive (V_{cc}) and negative (GND) power connections are made to pins 14 and 7 of the IC. Input switches (A and B) are wired to pins

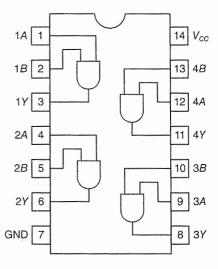


Fig. 3-52 Pin diagram for the 7408 digital IC.

1 and 2 of the 7408 IC. Notice that if a switch is in the *up position*, a logical 1 (+5 V) is applied to the input of the AND gate. If a switch is in the down position, however, a logical 0 is applied to the input. At the right in Fig. 3-53(b), an LED and 150- Ω limiting resistor are connected to GND. If the output at pin 3 is HIGH (near +5 V), current will flow through the LED. When the LED is lit, it indicates a HIGH output from the AND gate.

IC Part Numbers

The top of a typical *TTL digital IC* is shown in Fig. 3-54(a). The block form of the letters "NS" on the top of the IC shows the manufacturer as National Semiconductor. The DM7408N part number can be divided into sections as shown in Fig. 3-54(b). The prefix "DM" is the manufacturer's code (National Semiconductor uses the letters "DM" as a prefix). The core part number is 7408, which is a quadruple two-input AND gate TTL IC. This core part number is the same from manufacturer to manufacturer. The trailing letter "N" (the suffix) is a code used by several manufacturers to designate the DIP.

The top of another digital IC is shown in Fig. 3-55(a). The letters "SN" on this IC stand for the manufacturer, Texas Instruments. On this unit, the suffix "J" stands for a ceramic DIP packaging. This is typically referred to as the *commercial grade*. The core part number of the IC in Fig. 3-55 is 74LS08. This is similar to the 7408 quadruple two-input AND gate IC discussed earlier. The letters "LS" in the center of the core number designate the type of TTL circuitry used in the IC. In this case "LS" stands for *low-power Schottky*.



For related information, visit the website for Fairchild Semiconductor. www.fairchildsemi .com

SMT

TTL digital IC

pin diagrams


7400 series of TTL ICs

Commercial grade

Low-power Schottky



For data sheets see, www.jameco.com or other supplier.

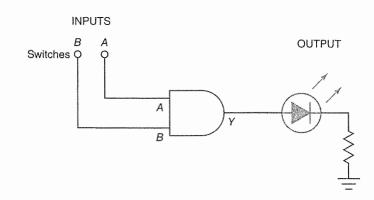

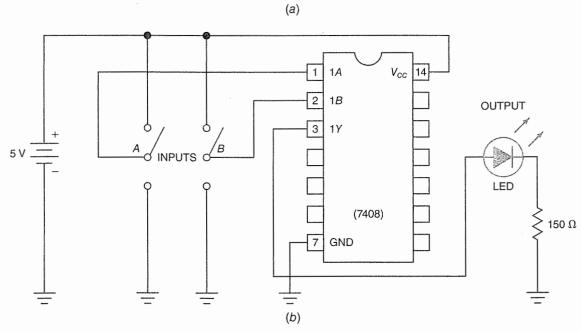


Fig. 3-53 (a) Logic diagram for a two-input AND gate circuit. (b) Wiring diagram to implement the two-input AND function.

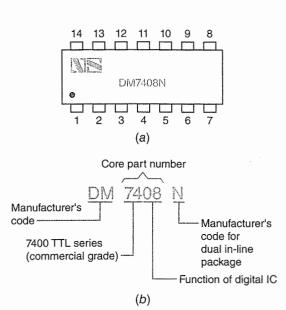


Fig. 3-54 (a) Marking on a typical digital IC. (b) Decoding the part number on a typical IC.

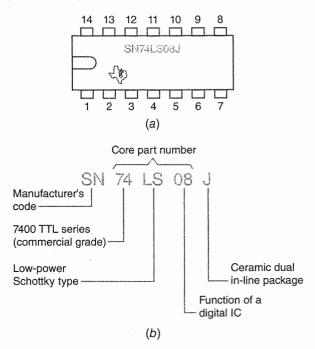


Fig. 3-55 (a) Markings on a Texas Instruments digital IC.
(b) Decoding the part number of a typical low-power Schottky IC.

Marking on a typical digital IC

Decoding the part number on a typical IC

The internal letter(s) in a *core part number* of a 7400 series IC tell something about the *logic family* or *subfamily*. Typical internal letters used are:

AC = FACT Fairchild Advanced CMOS Technology logic (a newer advanced family of CMOS)

ACT = FACT Fairchild Advanced CMOS
Technology logic (a newer family
of CMOS with TTL logic levels)

ALS = advanced low-power Schottky TTL logic (a subfamily of TTL)

AS = advanced Schottky TTL logic (a subfamily of TTL)

C = CMOS logic (an early family of CMOS)

F = FAST Fairchild Advanced Schottky TTL logic (a new subfamily of TTL)

FCT = FACT Fairchild Advanced CMOS
Technology logic (a family of
CMOS with TTL logic levels)

H = high-speed TTL logic (a subfamily of TTL)

HC = high-speed CMOS logic (a family of CMOS)

HCT = high-speed CMOS logic (a family of CMOS with TTL inputs)

L = low-power TTL logic (a subfamily of TTL)

LS = low-power Schottky TTL logic (a subfamily of TTL)

S = Schottky TTL logic (a subfamily of TTL)

The internal letters give information about the speed, power consumption, and process technology of digital ICs. Because of these speed and power consumption differences, manufacturers usually recommend that exact part numbers be used when replacing digital ICs. When the letter "C" is used inside a 7400 series part number, it designates a CMOS and not a TTL digital IC. The internal letters "HC," "HCT," "AC," "ACT," and "FCT" also designate *CMOS ICs*.

Data manuals from manufacturers contain much valuable information on digital ICs. They contain pin diagrams and packaging information. Data manuals also contain details on part numbering and other valuable data for the technician, student, or engineer. Manufacturer's websites usually have data sheets available for download at no cost. Core part number

Logic families or subfamilies

CMOS ICs



www.ti.com

-M- Self-Test

Answer the following questions.

- 72. List two popular digital IC families.
- 73. Refer to Fig. 3-51(*a*). This IC uses the case style called the _____ package.
- 74. A _______ -V dc power supply is used with TTL ICs. The V_{cc} pin is connected to the ______ (-, +) of the supply.
- 75. Refer to Fig. 3-53(*b*). How is the 7408 IC described by the manufacturer?
- 76. What can you tell about a digital IC that has the marking "74LS08N" printed on the top?
- 77. A digital IC with markings of 74F08 on top would be a quad two-input AND gate from what TTL subfamily?
- 78. A digital IC with markings of 74ACT08 on top would be a quad two-input AND gate using ______ (CMOS, TTL) technology and supporting TTL logic levels.



3-12 Practical CMOS Logic Gates

The older 7400 series of TTL logic devices has been extremely popular for many decades. One of its disadvantages is its higher-power

consumption. In the late 1960s, manufacturers developed CMOS digital ICs which consume little power and were perfect for battery-operated electronic devices. CMOS stands for complementary metal-oxide semiconductor.

Complementary metal-oxide semiconductor Unused inputs
4000 series
74C00 series
74HC00 series
FACT series

Several families of compatible CMOS ICs have been developed. The first was the 4000 series. Next came the 74C00 series and more recently the 74HC00 series of CMOS digital ICs. In 1985, the FACT (Fairchild Advanced CMOS Technology) 74AC00 series, 74ACT00 series, and 74FCT00 series of extremely fast, low-power CMOS digital ICs were introduced by Fairchild. Many large-scale integrated (LSI) circuits such as digital wristwatch and calculator chips are also manufactured using the CMOS technology.

IC Packaging

A typical 4000 series CMOS IC is pictured in Fig. 3-56(a). Note that pin 1 is marked as such on the top of the IC immediately counterclockwise from the notch. The CD4081BE part number can be divided into sections as shown in Fig. 3-56(b). The prefix CD is the manufacturer's code for CMOS digital ICs. The core part number is 4081B, which stands for a CMOS quadruple two-input AND gate IC. This core part number is almost always the same from manufacturer to manufacturer. The trailing letter "E" is the manufacturer's packaging code for a plastic DIP IC. The letter "B" is a "buffered version" of the original 4000A series. The buffering provides the 4000B series devices with greater output drive and some protection from static electricity.

Figure 3-56(c) is a pin diagram for the CD4081BE CMOS quad two-input AND gate IC. The power connections are V_{DD} (positive voltage) and V_{SS} (GND or negative voltage). The labeling of the power connections on TTL and 4000 series CMOS ICs is different. This difference can be observed by comparing Figs. 3-52 and 3-56(c).

IC Wiring

Given the schematic diagram in Fig. 3-57(a), wire this circuit using the 4081B CMOS IC. A wiring diagram for the circuit is shown in Fig. 3-57(b). A 5-V dc power supply is shown but the 4000 series CMOS ICs can use voltages from 3 to 18 V dc. Care is taken in removing the 4081 from its conductive foam storage because CMOS ICs can be damaged by static charges. Do not touch the pins when inserting the 4081 CMOS IC in a socket or mounting board. V_{DD} and V_{SS} power connections are made with the

power off. When using CMOS, all unused inputs are tied to GND or $V_{\rm DD}$. In this example, unused inputs (C, D, E, F, H, G) are grounded. The output of the AND gate (pin 3) is connected to the driver transistor. The transistor turns the LED on when pin 3 is HIGH or off when the output is LOW. Finally, inputs A and B are connected to input switches.

When the input switches in Fig. 3-57(b) are in the up position, they generate a HIGH input. A LOW input is generated when the switches are in the down position. Two LOW inputs to

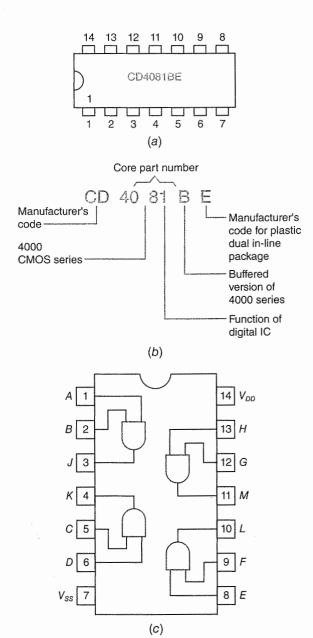


Fig. 3-56 (a) Markings on CMOS digital IC. (b) Decoding the part number on a typical 4000B series CMOS IC. (c) Pin diagram for the 4081B CMOS IC.

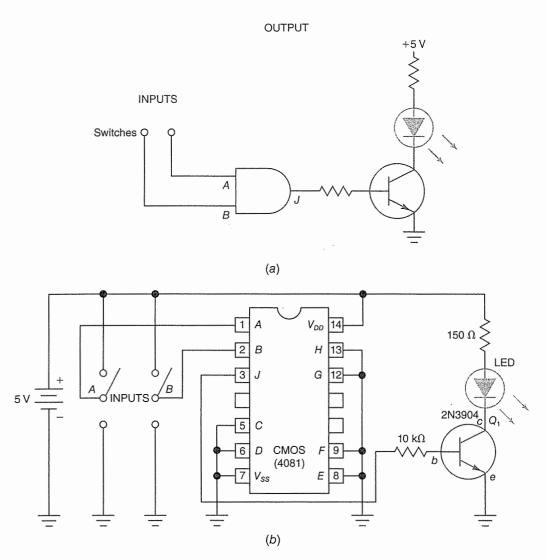


Fig. 3-57 (a) Logic diagram for a two-input AND gate circuit. (b) Wiring diagram using the 4081 CMOS IC to implement the two-input AND function.

the AND gate produce a LOW output at pin 3 of the IC. The LOW output turns off the transistor, and the LED does not light. Two HIGH inputs to the AND gate produce a HIGH output at pin 3. The HIGH (about +5 V) output at the base of Q_1 turns on the transistor and the LED lights. The 4081 CMOS IC will generate a two-input AND truth table.

CMOS Subfamilies

Several families of CMOS digital ICs are available. A 4000 series IC was used as an example in this section. The newer 74HC00 series CMOS digital ICs have gained favor because they are somewhat more compatible with the popular TTL logic. The 74HC00 series of CMOS ICs also has more drive capabilities than the older

4000 and 74C00 series units and operates at high frequencies. The "HC" in the 74HC00 series part number stands for high-speed CMOS.

The FACT Fairchild Advanced CMOS Technology logic series is a later CMOS family of ICs. It includes the 74AC00-, 74ACT00-, 74ACTQ00-, 74FCT00-, and 74FCTA00-series subfamilies of CMOS digital ICs. The FACT logic family has good operating characteristics exceeding many CMOS and TTL subfamilies. For direct replacement of 74LS00 and 74ALS00 TTL series ICs, the 74ACT00-, 74ACTQ00-, 74FCT00-, and 74FCTA00-series circuits with TTL-type input voltage characteristics are included in the FACT CMOS family. FACT logic devices are ideal for portable systems because of their extremely

Cautions when using CMOS ICs low power consumption and excellent highspeed characteristics.

Caution must be used so that static charges do not damage CMOS ICs. All unused inputs to CMOS gates must be grounded or connected to V_{DD} . Most important, input voltages must not exceed the GND (V_{SS}) to V_{DD} voltage.

Lower-Voltage ICs

Manufacturers continue to crowd more and more semiconductor elements (transistors, diodes, and resistors) on a single chip. The chips are then packaged in smaller IC packages. The higher density means the components are extremely close together. This is good for speed of operation. The higher densities are bad because of heating and the problem of not enough insulating materials between components. To solve the drawbacks caused by high-density

integrated circuits, manufacturers have lowered the power supply voltage from the traditional 5 V to 3 V and lower. The lower-voltage 3-V chips (ICs) can operate on power sources ranging from about 2.7 to 3.6 V. Some ultra-low-voltage ICs operate on 1.8-V power supplies. The compact low-voltage ICs are used in most applications today including handheld consumer electronics.

An example of a low-voltage CMOS IC is pictured in Fig. 3-58(a). The part number is SN74LVC08. The tiny 14-pin package is for surface mounting on a printed circuit board. The package is referred to as a *small-outline IC* (SOIC) package. Note the beveled corner of the IC. This aids us in identifying pin 1 of this IC.

The decoding of the SN74LVC08 part number from the IC is detailed in Fig. 3-58(b). The SN is the manufacturer's code (Texas

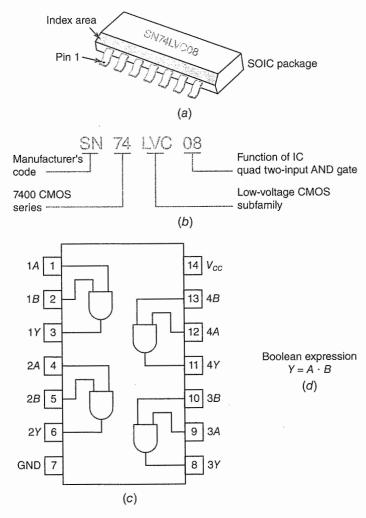


Fig. 3-58 (a) Markings on low-voltage CMOS digital IC. (b) Decoding the part number on 74LVCOB IC. (c) Pin diagram for the 74LVCOB IC. (d) Boolean expression for the two-input AND gate.

Instruments uses SN). The 74 identifies this as part of the popular 7400 series of digital ICs. The LVC section of the part number is short for "low-voltage CMOS" which is a subfamily of digital CMOS ICs.

The pin diagram in Fig. 3-58(c) shows the power pins ($V_{CC} = +3 \text{ V}$ and GND = - of power supply). The other 12 pins are either inputs to or outputs from the 4 two-input AND gates in the 74LVC08 IC. Finally, the Boolean expression for a single two-input AND gate is given as $Y = A \cdot B$.

Many low-voltage subfamilies of digital ICs have been developed. They are considered low voltage digital ICs if they operate on power supplies of less than 5 V. Some operate on about 3 V. Others operate on voltages as low as 1.8 V. A few subfamilies of low-voltage digital IC are listed below:

74LVC (low-voltage CMOS). Operates on 3 V. Can tolerate 5-V inputs. This series contains a wide variety of logic gates and many other logic devices.

74ALVC (advanced low-voltage CMOS). Operates on 3 V only. High-performance subfamily.

74AVC (advanced very low voltage CMOS). Operates on power supplies as low as 1.2 V to a high of 3.3 V. Very high performance.

Sall-Test

Answer the following questions.

- 79. The primary advantage of CMOS digital ICs is their _ ____ (high, low) power consumption.
- 80. While TTL must use a 5-V power supply, 4000 series CMOS ICs can operate on dc voltages from _____ to ____V.
- 81. Refer to Fig. 3-56. How is this 4081B IC described by the manufacturer?
- 82. What rule (dealing with unused inputs) must be followed when wiring CMOS ICs?
- 83. Refer to Fig. 3-57. With both inputs A and B at +5 V, output J goes.

- (HIGH, LOW) turning ____ off) transistor Q_1 causing the LED to
- 84. New designs of compact electronics equipment would consider low-voltage CMOS chips over older 4000 series ICs. (T or F)
- 85. Refer to Fig. 3-58(*a*). This 74LVC08 IC is housed in a 14-pin small outline package (SOIC) designed for surface mounting. (T or F)
- 86. Refer to Fig. 3-58. The 74LVC08 IC is an example of a low-voltage CMOS IC that operates on 3 V. (T or F)



Traubleshooting Simple 3-13 **Gate Circuits**

The most basic piece of test equipment used in digital troubleshooting is the logic probe. A simple logic probe is pictured in Fig. 3-59. The slide switch on the unit is used to select the type of logic family under test, either TTL or CMOS. The logic probe in Fig. 3-59 is set to test a TTL type of digital circuit in this example. Typically, two leads provide power to the logic probe. The red lead is connected to the positive (+) of the power supply while the black lead of the logic probe is connected to the

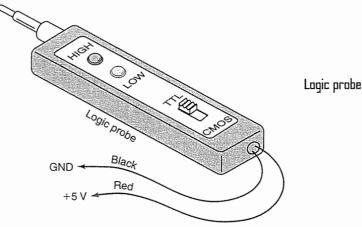


Fig. 3-59 Logic probe.

ABOUT ELECTRONICS

Communications in Orbit. Satellites in geostationary earth orbit (GEO) enable fax, videoconferencing, Internet, long-distance fixed phone service, television, and broadband multimedia to be provided in developing areas of the world. Satellites in medium-earth orbit (MEO) are used for mobile cell phones, fixed phones, and other personal communications. Satellites in low-earth orbit (LEO) are used for handheld mobile phones, paging, fax, ship or truck tracking, fixed ordinary phones, broadband multimedia, and monitoring of remote industrial spots. In the aftermath of the earthquake pictured, search and rescue teams kept in touch with one another using satellite technology and were also able to maintain international communications.



Printed circuit (PC) board

negative (—) or GND of the power supply. After powering the logic probe, the needlelike probe is touched to a test point or node in the circuit. The logic probe will light either the HIGH or the LOW indicator. If neither indicator lights,

it usually means that the voltage is somewhere between the HIGH and LOW.

In practical electronic equipment most digital ICs are mounted on a *printed circuit (PC)* board. An example is shown in Fig. 3-60(a).

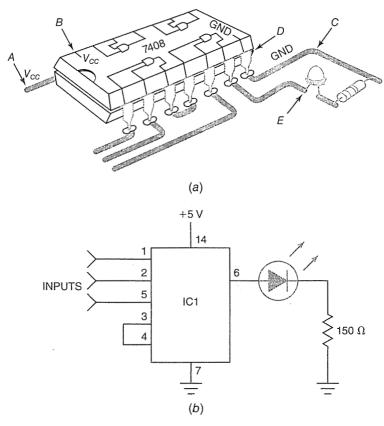


Fig. 3-60 (a) Digital IC mounted on a printed circuit (PC) board. (b) Wiring or schematic diagram of a digital gating circuit.

Also available to the student or technician is a circuit wiring diagram or schematic similar to that in Fig. 3-60(b). Many times the +5-V (V_{cc}) and GND connections to the ICs are not shown on the wiring diagram. However, they are always understood to be present. Pin numbers are usually given in a wiring diagram. The IC type may not be given on the schematic but is usually listed on a parts list in the equipment manual.

The first step in troubleshooting is to use your senses. *Feel* the flat top of the ICs to determine if they are hot. Some ICs operate cool; others run slightly warm. CMOS ICs should always be cool. *Look* for broken connections, solder bridges, broken PC board traces, and bent IC pins. *Smell* for possible overheating. *Look* for signs of excessive heat, such as discoloration or charring.

The next step in troubleshooting might involve checking whether each IC has power. With the logic probe connected to power, check at the points labeled A, B (the V_{CC} pin), C, and D in Fig. 3-60(a). Nodes A and B should give a bright HIGH light on the logic probe. Nodes C and D (GND) should give a bright LOW light on the logic probe.

The next step might be to trace the path of logic through the circuit. The circuit is equal to a three-input AND gate in this example (Fig. 3-60). Its unique state is a HIGH when all inputs are HIGH. Check pins 1, 2, and 5 of the IC in Fig. 3-60(a) with the logic probe. Manipulate the equipment to get all inputs HIGH. When all inputs are HIGH, the output (pin 6 of the IC) should be HIGH and the circuit LED should light. If the unique state works, try several other input combinations and verify their proper operation.

Refer to Fig. 3-60(*a*). Assume a HIGH reading at node *A* and a LOW reading on the logic

probe at node *B* (pin 14 of the IC). This probably means an open circuit in the PC board trace or a faulty solder joint between points *A* and *B*. If DIP IC sockets are used, the thin part of the IC pin can be bent. This common difficulty causes an open between the IC pin and the socket and PC board trace.

Refer to Fig. 3-60(a). Assume LOW readings at pins 1, 2, and 3 with no reading (neither LED on the logic probe lit) at pin 4. No reading on most logic probes means a voltage between LOW and HIGH (perhaps 1 to 2 V in TTL). This input (pin 4) is floating (not connected) and is considered to be a HIGH by the TTL circuitry inside the 7408 IC. The output of the first AND gate (pin 3) is supposed to pull the input to the second AND gate (pin 4) LOW. If it does not, the fault could be in the PC board trace, solder connections, or a bent IC pin. Internal opens and shorts also occur in digital ICs.

Troubleshooting a comparable CMOS circuit proceeds in the same way with a few exceptions. The logic probe must be set to CMOS instead of TTL. *Floating inputs* on CMOS ICs can harm the IC. A LOW in CMOS is defined as approximately 0 to 20 percent of the power supply voltage. A HIGH in CMOS is defined as approximately 80 to 100 percent of supply voltage.

Summary

Troubleshooting *first* involves using your senses. *Second*, check with a logic probe to see if each IC has power. *Third*, determine the exact job of the gating circuit, and test for the unique output conditions. *Finally*, check other input and output conditions. Short-circuit conditions can occur inside ICs as well as in the wiring. Digital ICs should be replaced with exact subfamily replacements when possible.

Steps in troubleshooting

Floating inputs

-\\\- Self-Test

Answer the following questions.

- 87. Refer to Fig. 3-59. With what two logic families can this logic probe be used?
- 88. What is the first step in troubleshooting gating circuits using TTL ICs?
- 89. What is the second step in troubleshooting?
- 90. Floating inputs to CMOS ICs are _____ (allowed, not allowed).



Dependency notation

IEEE standard symbols

IEEE logic gate symbols

3-14 IEEE Logic Symbols

The logic gate symbols you have memorized are the traditional ones recognized by all workers in the electronics industry. These symbols are very useful in that they have distinctive shapes. Manufacturers' data manuals include traditional logic symbols and are recently including the newer *IEEE functional logic symbols*. These newer symbols are in accordance with ANSI/IEEE Standard 91-1984 and IEC

Publication 617-12. These newer IEEE symbols are commonly referred to as *dependency notation*. For simple gating circuits, the traditional logic symbols are probably preferred, but the IEEE standard symbols have advantages as ICs become more complicated.

Figure 3-61 shows the traditional logic symbols and their IEEE counterparts. All IEEE logic symbols are rectangular. There is an identifying character or symbol inside the rectangle. For instance, notice in Fig. 3-61 that


LOGIC FUNCTION	TRADITIONAL LOGIC SYMBOL	IEEE LOGIC SYMBOL*
AND	A	А —Y В —Y
OR	A	A — ≥ 1 Y
NOT	A	A1Y
NAND	В	A & Y B & Y
NOR	A	A — ≥ 1 Y
XOR	A	A — = Y
XNOR	A	A


^{*}ANSI/IEEE Standard 91-1984 and IEC Publication 617-12.

Fig. 3-61 Comparing traditional and IEEE logic gate symbols.

the ampersand (&) character is printed inside the IEEE standard AND gate symbol. Characters outside the rectangle are not part of the standard symbol and may vary from manufacturer to manufacturer. The invert bubble on traditional logic symbols (NOT, NAND, NOR, and XOR) is replaced with a right triangle on corresponding IEEE standard symbols. The IEEE right triangle can also be used on inputs to signify an active LOW input. You have memorized the traditional logic gate symbols. You will not have to memorize the IEEE logic gate symbols but should be aware they exist.

Recent manufacturers' data manuals may give both the traditional and IEEE functional logic symbols for a particular IC. For instance, logic symbols for the 7408 quadruple two-input AND gate are illustrated in Fig. 3-62. The traditional logic diagram for the 7408 IC is shown in Fig. 3-62(a). The IEEE logic diagram for the 7408 IC is reproduced in Fig. 3-62(b). Note in the IEEE symbol for the 7408 IC that only the top AND gate contains the & symbol, but it is understood that the lower three rectangles also represent two-input AND gates.

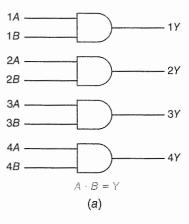

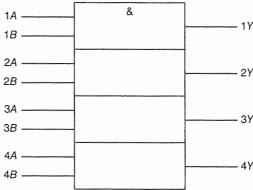

This symbol is in accordance with ANSI/IEEE Standard 91-1984 and IEC Publication 617-12.

Fig. 3-62 Logic symbol for 7408 quadruple two-input AND gate. (a) Traditional symbol (most common).

(b) IEEE functional logic symbol (newer method).

₩-

Self-Test

Answer the following questions.

- 91. Draw the IEEE standard logic symbol for a three-input AND gate.
- 92. Draw the IEEE standard logic symbol for a three-input OR gate.
- 93. Draw the IEEE standard logic symbol for a three-input NAND gate.
- 94. The right triangle on IEEE symbols replaces the invert _____ on traditional logic symbols.



3-15 Simple Logic Gate Applications

Consider the use of the AND gate in Fig. 3-63(a). Input A is the input which *controls* whether the clock signal is blocked or passed through the AND gate to output Y. The clock

waveform is considered to be continuous. If the control input to the AND gate goes HIGH, the gate is said to be *enabled*. This means that the clock signal passes through the gate to the output with no change. The AND gate is shown in its enabled mode in Fig. 3-63(b). If the control input to the AND gate goes LOW, the gate is

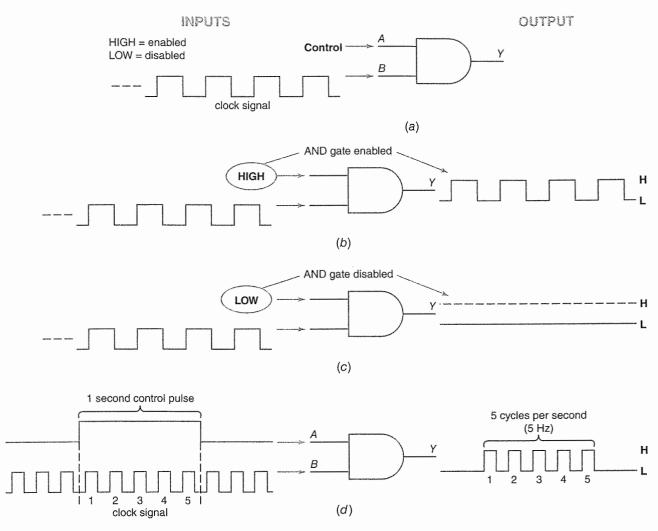


Fig. 3-63 The AND gate used as a control gate.

said to be *disabled*. Being disabled means the output of the AND gates stays LOW and the clock signal is blocked from passing through to the output. The AND gate is shown in its disabled mode in Fig. 3-63(c).

The control input to the AND gate in Fig. 3-63 is said to an *active HIGH* input. By definition, an active HIGH input is a digital input which executes its function when a HIGH is present. The job or function of the gate in Fig. 3-63 was to pass (not block) the clock signal.

The AND gate in Fig. 3-63(d) serves as a special control gate. This circuit is a very fundamental *frequency counter* circuit. The control pulse at input A to the AND is exactly 1 second allowing the clock signal to pass through the gate for only 1s. In this example 5 pulses pass through the AND gate from input B to output Y during

the one second. Counting the pulses at the output of the gate in Fig. 3-63(d) means that the clock signal must be 5 cycles per second (5 Hz).

Consider the use of a push-button switch to activate the clear (CLR) input of an 8-bit binary counter IC in Fig. 3-64. With SW₁ open, the *pull-up resistor* R_1 pulls the input of the inverter HIGH. The output of the inverter is LOW at this time, and the *CLR* input to the counter IC is not active (disabled). Pressing input switch SW₁ applies a LOW to the input of the inverter whose output goes HIGH enabling the *CLR* input of the counter. This clears the counters output to 00000000. The bubble at the input of the inverter in Fig. 3-64 (IC_1) indicates that the active state is a LOW while the lack of a bubble on the CLR input to the binary counter IC_2 symbol indicates an active HIGH input.

Active HIGH input Pull-up resistor

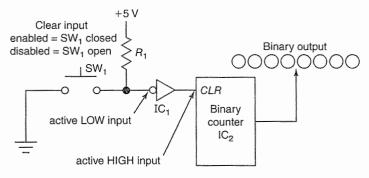


Fig. 3-64 Active LOW and active HIGH inputs.

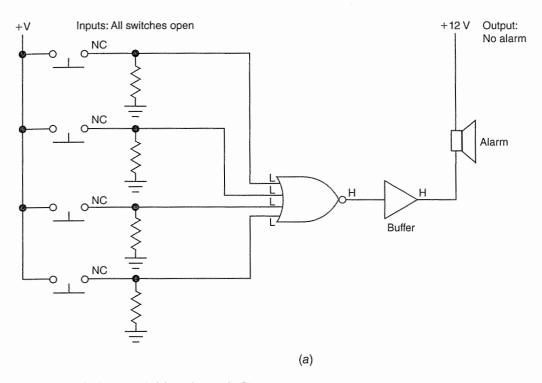



Fig. 3-65 Simple alarm circuit. (a) No alarm with all inputs open.

Consider the simplified automobile alarm system shown in Fig. 3-65(a). The alarm will sound when any one or all of the door-mounted normally closed (NC) push-button switches are released (closed) by a door opening. Each input to the NOR gate has a *pull-down resistor* attached to pull the inputs to the gate LOW when the switches are open. The bubble at the output of the NOR gate suggests that it has an *active LOW* output. The NOR gate in Fig. 3-65(a) has active HIGH inputs. With all the auto doors closed and all input switches open as shown in Fig. 3-65(a), the inputs to the NOR gate are LLLL causing a HIGH output. The alarm is disabled.

If any car door opens, the door mounted switch springs closed as shown in Fig. 3-65(*b*). The inputs to the NOR gate are HLLL causing a LOW output. The noninverting buffer also outputs a LOW which turns on the alarm. The alarm sounds. The buffer provides extra current to drive the alarm device.

To disable the alarm system a switch SW_1 has been added along with an OR gate in Fig. 3-65(c). The OR gate is redrawn to look like a AND symbol with inverted inputs and output. This arrangement produces the OR function (see the conversion chart in Fig. 3-47). The reason the alternative symbol was used is

Pull-down resistor

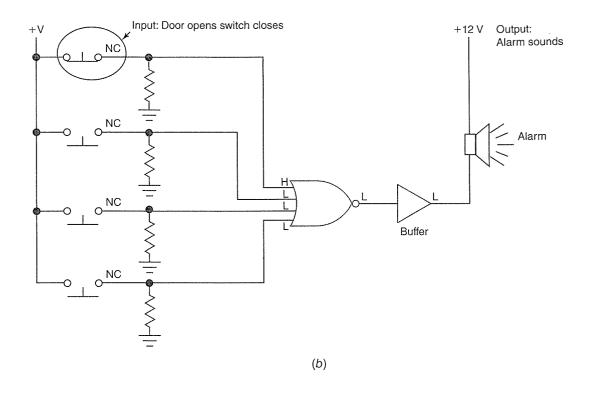

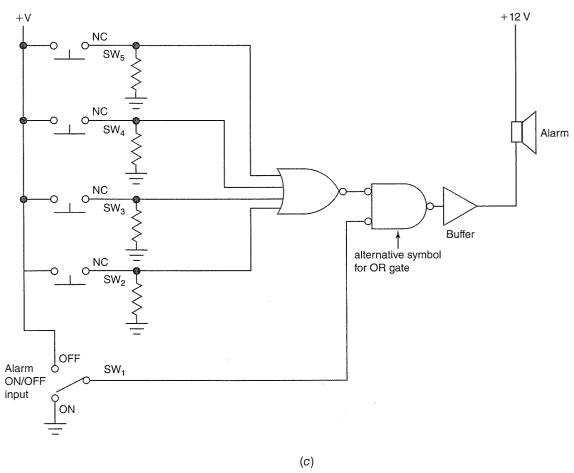


Fig. 3-65 (continued) (b) Alarm sound with top input switch closed. (c) Adding ON/OFF switch to alarm.

to suggest that it takes two LOW inputs to generate a LOW output and sound the alarm. The two bubbles at the inputs to the alternative OR symbol means it takes a LOW from the ON/OFF switch as well as a LOW from the NOR gate to produce an active LOW output turning on the alarm. The alarm is turned off or

disabled by placing SW₁ in the OFF position which passes a HIGH to the OR gate. A HIGH at any input to an OR gate will always generate a HIGH output and disable the alarm.

This example was given to alert students that traditional logic symbols as well as their alternative symbols appear in manufacturer's literature.

-V/\-

Sell-Test

Answer the following questions.

- 96. Refer to Fig. 3-63(c). When the control input to the AND is LOW, the gate is _____ (disabled, enabled) and the clock signal is blocked from passing through to the output.
- 97. Refer to Fig. 3-63(b). When the control input to the AND is HIGH, the gate is enabled and the clock signal is _____ (blocked from passing through, passed through) to the output.
- 98. Refer to Fig. 3-63(*d*). The AND gate along with a 1-second positive control pulse demonstrates the concept used in an electronic lab instrument called a _____ (digital multimeter, frequency counter).
- 99. Refer to Fig. 3-64. To clear the binary counter to binary 0000000, the push button is _____ (pressed, released)

- causing the input to the inverter IC to go $_$ (HIGH, LOW) driving the CLR input to IC₂ $_$ (HIGH, LOW).
- 100. Refer to Fig. 3-64. The clear or CLR pin to the binary counter IC is an _____ (active HIGH, active LOW) input.
- 101. Many times logic symbols attach a small _____ to show either an active LOW input or an active LOW output.
- 102. Refer to Fig. 3-65(c). If switch SW₁ is LOW and switch SW₂ is closed by the opening of a car door, the alarm _____ (does not sound, sounds).
- 103. Refer to Fig. 3-65(c). If switch SW₁ is HIGH and both SW₁ and SW₂ are closed by the opening of car doors, the alarm _____ (does not sound, sounds).



3-16 Logic Functions Using Software (BASIC Stamp Module)

It is common for logic functions (AND, OR, XOR, etc.) to be programmed using software. In this section, we will program logic functions using a high-level language called PBASIC (a version of BASIC used by Parallax, Inc.). The programmable hardware device used in these examples will be the BASIC Stamp 2 (BS2) Microcontroller Module by Parallax, Inc. The hardware needed to program the BASIC Stamp Microcontroller Module is sketched in Fig. 3-66(a). The hardware includes the BASIC Stamp 2 module, a PC system, a serial cable for downloading (or USB cable on certain models),

and assorted electronic components (switches, resistors, and an LED). The actual BS2 IC is sketched in Fig. 3-66(b). Notice that the BS2 module takes the form of a 24-pin DIP IC. The BS2 module is manufactured using several components including a PIC16C57 microcontroller with PBASIC interpreter in firmware, EEPROM program memory, and other parts.

The procedure for programming the BASIC Stamp Module to operate as a two-input AND gate is represented in Fig. 3-66. The steps in wiring and programming the BASIC Stamp 2 module are:

1. Refer to Fig. 3-66. Wire the two active HIGH push-button switches and connect them to ports P11 and P12. Wire the

PBASIC

EEPROM

BASIC Stamp 2 module

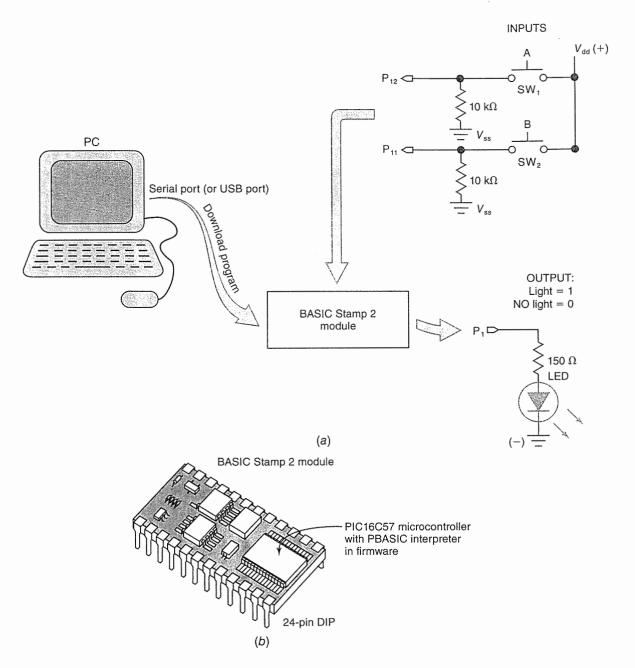


Fig. 3-66 (a) BASIC Stamp 2 module wired as a two-input AND gate. (b) Physical appearance of the BS2 by Parallax, Inc.

- red LED output indicator and connect it to port P1. The ports will be defined as either an output or inputs in the PBASIC program.
- Load the PBASIC text editor program (version for the BS2 IC) into the PC.
 Type your PBASIC program describing the two-input AND logic function. A PBASIC program titled 'Two-input AND function is listed in Fig. 3-67.
- 3. Attach a serial cable (or USB cable on certain models) between the PC and the BASIC Stamp 2 development board (such as the Board of Education by Parallax, Inc.).

- 4. With the BASIC Stamp 2 module turned on, download your PBASIC program from the PC to BS2 module using the RUN command.
- 5. Disconnect the serial or USB cable from the BS2 module.
- 6. Test the two-input AND program by pressing the input switches. The output indicator (red LED) will light only when both input switches are activated (pressed). The PBASIC program stored in EEPROM program memory in the BASIC Stamp 2 Module will start each time the BS2 IC is turned on.

PBASIC Program: 2-input AND Function

Consider the PBASIC program titled 'Two-input AND function in Fig. 3-67. Line 1 starts with an apostrophe ('), which means this is a remark statement. Remark statements are used to clarify the program and are not executed by the microcontroller. Lines 2-4 are lines of code to declare variables that will be used later in the program. As an example, line 2 reads-A VAR Bit. This tells the microcontroller that A is a variable name that will hold only 1 bit (a 0 or 1). Lines 5-7 are lines of code that declare which ports are used as inputs and which port is an output. As an example, line 5 reads—INPUT 11. This informs the microcontroller that port 11 (P11) will be used as an input in this program. Another example in line 7 reads OUTPUT 1, which declares that port 1 will be used as an output. Notice that line 7 code is followed by a remark statement—'Declare port 1 as an output. The remark statements at the right in this PBASIC program are not required, but they aid in understanding the purpose for lines of code.

Next consider the main routine with the starts with the **Ckswitch:** line of code. In

PBASIC, any word followed by a colon (:) is called a *label*. A label is a reference point in the program that usually locates the beginning of a main or subroutine.

In the 'two-input AND function sample program, the label Ckswitch: is the starting point in the main routine used to check the condition of input switches A and B and logically AND the inputs. The Ckswitch: routine repeats continuously because either lines 14 (GOTO Ckswitch) or 18 (GOTO Ckswitch) will always return the program to the beginning of the Ckswitch: main routine.

Line 9 of the PBASIC program initializes or turns off the output LED. The OUT1 = 0 statement causes port 1 (P1) of the BS2 IC to go LOW. Lines 10 and 11 assign the current binary value at input ports 11 (P11) and 12 (P12) to variables **B** and **A**. For instance, if both input switches are pressed, then both variable **B** and **A** would hold logical 1.

Line 12 of the PBASIC program is code that logically ANDs the values in variables A and B. As an example, if both inputs are HIGH, then variable Y = 1. Line 13 is an IF-THEN statement used for making decisions. If Y = 1, then the PBASIC statement IF Y = 1 THEN

Label

PBASIC program

Remark statement

Declare variables



Downloads from Parallax site www.parallax.com.

'Two-input AND function	'Title of program (Fig. 3-67)	L1
A VAR Bit	'Declare A as variable, 1 bit	L2
B VAR Bit	'Declare B as variable, 1 bit	L3
Y VAR Bit	'Declare Y as variable, 1 bit	L4
INPUT 11	'Declare port 11 as an input	L5
INPUT 12	'Declare port 12 as an input	L6
OUTPUT 1	'Declare port 1 as an output	L7
Ckswitch:	'Label for check switch routine	L8
OUT1 = 0	'Initialize: port 1 at 0, red LED off	L9
A = IN12	'Assign value: port 12 input to variable A	L10
B = IN11	'Assign value: port 11 input to variable B	L11
Y = A & B	'Assign value: ANDed with B to variable Y	L12
If $Y = 1$ THEN Red	'If $Y = 1$ then go to red subroutine, otherwise next line	L13
GOTO Ckswitch	'Go to Ckswitch—begin check switch routine again	L14
Red:	'Label for lighting red LED, means HIGH output	L15
OUT1 = 1	'Output P1 goes HIGH, lights red LED	L16
PAUSE 100	'Pause for 100 ms (milliseconds)	L17
GOTO Ckswitch	'Go to Ckswitch: begin check switch routine again	L18

Fig. 3-67 Program for two-input AND function.

Red will cause the program to jump to the **Red**: label or the subroutine that lights the red LED. If Y = 0, then the first section of PBA-SIC statement **IF** Y = 1 **THEN Red** is false. This will cause the program to proceed to the next line of code (line 14—GOTO Ckswitch). Line 14 (GOTO Ckswitch) sends the program back to the beginning of the main routine with the label of Ckswitch:

The **Red:** subroutine in the PBASIC program 'two-input AND function causes the port 1 (pin P1) of the BS2 IC to go HIGH using the **OUT1** = 1 statement. This turns on and lights the red LED. Line 17 (**PAUSE 100**) causes the LED to stay on for an extra 100 ms (milliseconds). Line 18 (**GOTO Ckswitch**) sends the program back to the main routine labeled **Ckswitch:**

The PBASIC program 'two-input AND function runs continuously while the BASIC Stamp 2 module is powered. The PBASIC program is held in EEPROM program memory for future use. Turning the BS2 off and then on again will restart the program. The current

PBASIC listing can be changed by downloading a different program.

Programming Other Logic Functions

Other logic functions can also be programmed using PBASIC and the BASIC Stamp module. These include OR, NOT, NAND, NOR, XOR, and XNOR. The next PBASIC program titled 'two-input OR function, in Fig. 3-68, is used with the hardware from Fig. 3-66 and operates like a two-input OR gate. This program listing looks almost the same as the earlier PBASIC program except for the title line ('Two-input OR function) and line $12 (Y = A \mid B)$.

Line 12 of the 'Two-input OR function program shows inputs A and B being ORed with the resulting output being assigned to variable Y. The symbol for the OR function in PBASIC is the vertical line (I) and not the plus sign (+) that is used in traditional Boolean expressions.

The chart in Fig. 3-69 details the PBASIC code used to generate logic functions using

'Two-input OR function	'Title of program (Fig. 3-68)	L1
A VAR Bit	'Declare A as variable, 1 bit	L2
B VAR Bit	'Declare B as variable, 1 bit	L3
Y VAR Bit	'Declare Y as variable, 1 bit	L4
INPUT 11	'Declare port 11 as an input	L5
INPUT 12	'Declare port 12 as an input	L6
OUTPUT 1	'Declare port 1 as an output	L7
Ckswitch:	'Label for check switch routine	L8
OUT1 = 0	'Initialize: port 1 at 0, red LED off	L9
A = IN12	'Assign value: port 12 input to variable A	L10
B = IN11	'Assign value: port 11 input to variable B	L11
$Y = A \mid B$	'Assign value: A ORed with B to variable Y	L12
If $Y = 1$ THEN Red	'If $Y = 1$ then go to red subroutine, otherwise next line	L13
GOTO Ckswitch	'Go to Ckswitch—begin check switch routine again	L14
Red:	'Label for lighting red LED, means HIGH output	L15
OUT1 = 1	'Output P1 goes HIGH, lights red LED	L16
PAUSE 100	'Pause for 100 ms (milliseconds)	L17
GOTO Ckswitch	'Go to Ckswitch: begin check switch routine again	L18

Fig. 3-68 Program for two-input OR function.

LOGIC FUNCTION	BOOLEAN EXPRESSION	PBASIC CODE (BS2 IC)
AND	$A \cdot B = Y$	Y = A & B
OR	A + B = Y	Y = A B
NOT	$A = \overline{A}$	Y = ~ (A)
NAND	$\overline{A \cdot B} = Y$	Y = ~ (A & B)
NOR	$\overline{A+B}=Y$	Y = ~ (A B)
XOR	$A \oplus B = Y$	Y = A ^ B
XNOR	$\overline{A \oplus B} = Y$	$Y = \sim (A^B)$

Fig. 3-69 Logic functions implemented using PBASIC code with the BASIC Stamp 2 module by Parallax, Inc.

the BASIC Stamp 2 module. Notice the use of unique symbols in PBASIC to define AND, OR, NOT, and XOR logic functions. The ampersand (&) symbol is used for AND, and the vertical line (|) denotes the OR logic function. The tilde (~) is used for NOT. The circumflex accent (^) symbol is used to show the XOR logic function.

From Fig. 3-69, notice the use of both the tilde (\sim) and ampersand (&) symbols in the NAND function. An example of the two-input NAND function would be $Y = \sim (A \& B)$. Likewise in PBASIC code, both the tilde (\sim) and

vertical line (I) symbols are used in the NOR function. An example of the 2-input NOR function would be $Y = \sim (A \mid B)$.

From Fig. 3-69, notice the use of the circumflex accent (^) symbol to define the exclusive OR (XOR) logic function. The PBASIC code for the two-input XOR logic function would be $Y = A \land B$. In PBASIC, both the tilde (~) and circumflex accent (^) symbols are used to describe the XNOR logic function. An example would be $Y = \sim (A \land B)$, which describes A XNORed with B and the output being assigned to Y.

₩

Self-Test

Answer the following questions.

- 104. The BS2 IC by Parallax is described as a BASIC Stamp _____ (microcontroller, multiplexer) module.
- 105. The BASIC Stamp 2 module can be programmed in a high-level language called FORTRAN by its manufacturer (T or F).
- 106. The PBASIC assignment statment $\mathbf{Y} = \mathbf{A} \mid \mathbf{B} \mid \mathbf{C}$ is for the three-input _______(OR, XOR) logic function.
- 107. Write the PBASIC assignment statement that would describe the two-input NAND logic function.
- 108. Write the PBASIC assignment statement that would describe the Boolean expression $A \cdot B = Y$.

- 109. Write the PBASIC assignment statement that would describe the Boolean expression $\overline{A \oplus B} = Y$.
- 110. Write the PBASIC assignment statement that would describe the Boolean expression $\overline{A+B}=Y$.
- 111. In Fig. 3-66(a), if input P12 is HIGH and P11 is LOW and the PBASIC program titled **'Two-input OR function** is loaded into the BS2 IC, then output P1 will be _____ (HIGH, LOW), and the LED will _____ (light, not light).
- 112. In Fig. 3-66(a), if input P12 is HIGH and P11 is LOW and the PBASIC program titled 'Two-input AND function is loaded into the BS2 IC, then output P1 will be _____ (HIGH, LOW), and the red LED will _____ (light, not light).





Chapter 3 Summary and Review

Summary

- 1. Binary logic gates are the basic building blocks for all digital circuits.
- 2. Figure 3-70 shows a summary of the seven basic logic gates. This information should be memorized.
- 3. NAND gates are widely employed and can be used to make other logic gates.
- 4. Logic gates are often needed with 2 to 10 inputs. Several gates may be connected in the proper manner to get more inputs.
- 5. AND, OR, NAND, and NOR gates can be converted back and forth by using inverters. Refer to Fig. 3-47.

LOGIC FUNCTION	LOGIC SYMBOL	BOOLEAN EXPRESSION	TRUTH TABLE		
			INPUTS		OUTPUT
			В	Α	Υ
AND	A	$A \cdot B = Y$	0	0	0
AND		$A \cdot B = I$	0	1	0
			1	0	0
			1	1	1
			0	0	0
OR	$A \longrightarrow Y$	A + B = Y	0	1	1
) On	В	A + B - 1	1	0	1
			1	1	1
Inverter	A	$A = \overline{A}$		0	1
mverter		A - A		1	0
	A	$\overline{A \cdot B} = Y$	0	0	1
NAND			0	1	1
10.010			1	0	1
			1	1	0
	A	$\overline{A+B}=Y$	0	0	1
NOR			0	1	0
""			11	0	0
			1	1	0
	<i>A B Y</i>	A ⊕ B = Y	0	0	0
XOR			0.	1	1
,,,,,,,			1	0	+ 1
			1	1	0
	A	Ā ⊕ B = Y	0	0	1
XNOR			0	1	0
ANOIT			1	0	0
			1	1	1

Fig. 3-70 Summary of basic logic gates.

Summary...confinued

- 6. Logic gates are sometimes packaged in DIP ICs.
 The larger traditional DIP ICs are used on throughthe-hole printed circuit boards. Modern small-size DIP ICs are used for surface mounting.
- Both TTL and CMOS digital ICs are used in very small systems. Modern high-speed low-power CMOS ICs are used in many new designs. Low-voltage (such as 74LVC) ICs are popular.
- 8. Very low power consumption is an advantage of CMOS digital ICs.
- 9. A technical person's knowledge of the normal operation of a circuit, powers of observation, and skill in the use and interpretation of test data are all important in troubleshooting.
- 10. Logic symbols sometimes have small bubbles attached. These bubbles usually indicate that these pins are active LOW inputs or outputs.
- 11. When using CMOS ICs, all unused inputs must go to V_{DD} or GND. Care must be exercised in storing

- and handling CMOS ICs to avoid static electricity. Input voltages to a CMOS IC must never exceed the power supply voltages.
- 12. The logic probe, knowledge of the circuit, and your senses of sight, smell, and touch are basic tools used in troubleshooting gating circuits.
- 13. Figure 3-61 compares the traditional logic gate symbols with the newer IEEE standard logic symbols.
- Logic functions can be implemented by hard-wiring logic gates or by programming various programmable devices.
- 15. The chart in Fig. 3-69 shows the PBASIC (Parallax, Inc.'s version of BASIC for the BS2 IC) code used in programming the logic functions AND, OR, NOT, NAND, NOR, XOR, and XNOR. This code is executed using a device called a microcontroller (BASIC Stamp 2 module).

Chapter Review Questions

Answer the following questions.

- 3-1. Draw the traditional logic symbols for \mathbf{a} to \mathbf{j} (label inputs A, B, C, D and outputs Y):
 - a. Two-input AND gate
 - b. Three-input OR gate
 - c. Inverter (two symbols)
 - d. Two-input XOR gate
 - e. Four-input NAND gate
 - f. Two-input NOR gate
 - g. Two-input XNOR gate
 - h. Two-input NAND gate (special symbol)
 - i. Two-input NOR gate (special symbol)
 - i. Buffer (noninverting)
 - k. Three-state buffer (noninverting)
- 3-2. Write the Boolean expression for the following (label inputs *A*, *B*, *C*, *D*, and outputs *Y*):
 - a. Three-input AND function
 - b. Two-input NOR function
 - c. Three-input XOR function
 - d. Four-input XNOR function
 - e. Two-input NAND function

- 3-3. Draw the truth table for the following (label inputs *A*, *B*, *C*, and outputs *Y*):
 - a. Three-input OR
 - b. Three-input NAND
 - c. Three-input XOR
 - d. Two-input NOR
 - e. Two-input XNOR
- 3-4. Look at the chart in Fig. 3-70. Which logic gate always responds with an output of logical 0 only when all inputs are HIGH?
- 3-5. Which logic gate might be called the "all or nothing gate"?
- 3-6. Which logic gate might be called the "any or all gate"?
- 3-7. Which logic circuit complements the input?
- 3-8. Which logic gate might be called the "any but not all gate"?
- 3-9. The unique output of a(n) _____ (AND, NAND) gate is a HIGH only when all inputs are HIGH.
- 3-10. The unique output of a(n) _____ (NAND, OR) gate is a LOW only when all inputs are LOW.

Chapter Review Questions...continued

- 3-11. The unique output of a ______(NOR, XOR) gate is a HIGH only when an odd number of inputs are HIGH.3-12. The unique output of a(n) ______(NA)
- 3-12. The unique output of a(n) _____ (NAND, OR) gate is a LOW only when all inputs are HIGH.
- 3-13. The unique output of a ______ (NAND, NOR) gate is a HIGH only when all inputs are LOW.
- 3-14. Given an AND gate and inverters, draw how you would produce a NOR function.
- 3-15. Given a NAND gate and inverters, draw how you would produce an OR function.
- 3-16. Given a NAND gate and inverters, draw how you would produce an AND function.
- 3-17. Given 4 two-input AND gates, draw how you would produce a five-input AND gate.
- 3-18. Given several two-input NAND and OR gates, draw how you would produce a four-input NAND gate.
- 3-19. Switches arranged in series (see Fig. 3-1) act like what type of logic gate?
- 3-20. Switches arranged in parallel (see Fig. 3-8) act like what type of logic gate?
- 3-21. Figure 3-51(*b*) illustrates a(n) _____ (8, 16)-pin _____ (three letters) IC.
- 3-22. Draw a wiring diagram similar to Fig. 3-53(*b*) for a circuit that will perform the three-input AND function. Use a 7408 IC, a 5-V dc power supply, three input switches, and an output indicator.
- 3-23. The PC board pad labeled ______ (A, C) is pin 1 of the IC in Fig. 3-71.
- 3-24. The PC board pad labeled _____ (letter) is the GND pin on the 7408 IC in Fig. 3-71.
- 3-25. The PC board pad labeled _____ (letter) is the V_{CC} pin on the 7408 IC in Fig. 3-71.
- 3-26. The unit shown in Fig. 3-72 is a ______ (low-power, standard) TTL 14-pin DIP IC.
- 3-27. Pin 1 of the IC shown in Fig. 3-72 is labeled with the letter ______.
- 3-28. The pin labeled with a "C" on the IC in Fig. 3-72 is pin number _____.
- 3-29. Figure 3-60(*b*) is an example of a _____ (logic, wiring) diagram that might be used by service personnel.

- 3-30. Refer to Fig. 3-60(*a*). If all input pins (1, 2, and 5) are HIGH and output pin 6 is HIGH but point *E* is LOW, the LED ______ (will, will not) light and the circuit _____ (is, is not) working properly.
- 3-31. Refer to Fig. 3-60(a). List several possible problems if pin 6 is HIGH but point E is LOW.
- 3-32. Refer to Fig. 3-60(a). An *internal open* between the output of the first AND gate and pin 3 might give neither a HIGH nor LOW indication on the logic probe. This means that both pins 3 and 4 are floating ______ (HIGH, LOW).
- 3-33. Refer to Fig. 3-73. The core number of this IC is ______, which means it is a ______ (CMOS, TTL) logic device.
- 3-34. Pin 1 of the IC shown in Fig. 3-73 is labeled with the letter _____.

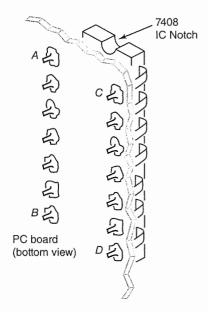


Fig. 3-71 An IC soldered to a PC board.

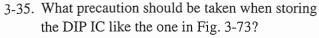


Fig. 3-72 Top view of a digital IC.


Chapter Review Questions...continued



Fig. 3-73 Top view of a digital IC.



- 3-36. Refer to Fig. 3-74(*a*). These CMOS digital devices are enclosed in a tiny SOIC package which is fastened to a PC board using ______ (point-to-point wiring, surface mounting).
- 3-37. Refer to Fig. 3-74(*a*). Pin 1 on the 74LVC00 IC is located at the pin labeled ______(*A*, *B*, *C*, or *D*).
- 3-38. Refer to Fig. 3-74(*b*). The 74LVC00 IC contains four separate two-input _____ (AND, NAND) logic gates.
- 3-39. Refer to Fig. 3-74. The 74LVC00 is a low-voltage CMOS IC operating on a ______ (3, 12)-volt power source.
- 3-40. Refer to Fig. 3-74. Write a Boolean expression that would describe the logic of a single gate in the 74LVC00 IC.
- 3-41. Draw the IEEE standard logic symbol for a three-input NOR gate.
- 3-42. Draw the IEEE standard logic symbol for a three-input XNOR gate.
- 3-43. The right ______ (circle, triangle) at the output of an IEEE standard NAND logic symbol signifies to invert the output of the AND function.
- 3-44. The IEEE standard AND logic symbol uses the _____ sign to signify the AND function.
- 3-45. A microcontroller (such as the BASIC Stamp 2 module) can be programmed to perform logic functions (AND, OR, etc.). (T or F)
- 3-46. The ______ (BS2, BX10) module by Parallax is programmed in a high-level

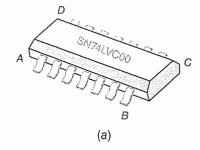

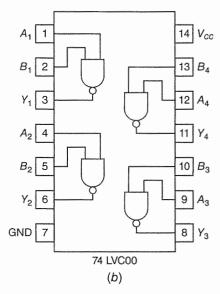


Fig. 3-74 74LVC00 IC. (a) SOIC package. (b) Pin diagram.

- computer language called PBASIC (a version of BASIC).
- 3-47. When programming the BASIC Stamp 2 module, the PBASIC code used to represent the Boolean expression A + B = Y (two-input OR) is ______ ($\mathbf{Y} = \mathbf{A} \ \mathbf{OR} \ \mathbf{B}, \ \mathbf{Y} = \mathbf{A} | \mathbf{B}$).
- 3-48. When programming the BS2 microcontroller module, the PBASIC code used to represent the two-input NAND function would be $[Y = A + B, Y = \sim (A \& B)].$
- 3-49. The PBASIC code **Y** = **A** ^ **B** ^ **C** represents the assignment statement for the three-input ______(AND, XOR) logic function.

Critical Thinking Questions

- 3-1. What three-input logic gate would you use in your design if you require a HIGH output *only* when all three input switches go HIGH?
- 3-2. What four-input logic gate would you use in your design if you require a HIGH output only when an *odd* number of input switches are HIGH?
- 3-3. Refer to Fig. 3-48(*a*). Explain why the OR gate with inverted inputs produces the NAND function.
- 3-4. Inverting both inputs of a two-input NAND gate produces a circuit that generates the _____ logic function.
- 3-5. Inverting both inputs and the output of a two-input OR gate produces a circuit that generates the ______ logic function.
- 3-6. Refer to Fig. 3-57. If input *A* is HIGH and input *B* is LOW, output *J* (pin 3) will be

- 3-7. Refer to Fig. 3-57. Why are pins 5, 6, 8, 9, 12, and 13 grounded in this circuit?
- 3-8. Refer to Fig. 3-60. If the 7408 TTL IC developed an internal "short circuit," the top of the IC would probably feel _____ (hot, cool) to the touch.
- 3-9. Draw a logic diagram (use AND and inverter symbols) for the Boolean expression $\overline{A} \cdot \overline{B} = Y$.
- 3-10. The Boolean expression $\overline{A} \cdot \overline{B} = Y$ is one representation of the ______ (NAND, NOR) logic function.
- 3-11. Draw a waveform to represent the logic levels (*H* and *L*) at output *Y* of the AND gate in Fig. 3-75.

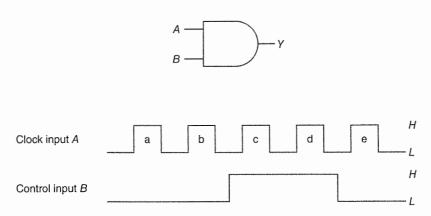


Fig. 3-75 Pulse train problem.

Critical Thinking Questions...continued




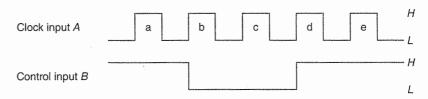


Fig. 3-76 Pulse train problem.

- 3-12. Draw a waveform to represent the logic levels (*H* and *L*) at output *Y* of the NOR gating circuit in Fig. 3-76.
- 3-13. Prove to your instructor that both logic diagrams drawn in Fig. 3-48(a) will generate a two-input NAND truth table. (*Hint*: Think of the bubbles as inverters.) You may use one of the following methods (ask instructor):
 - a. Wire and test logic circuits in hardware.
 - b. Wire and test logic circuits using a computer circuit simulation software.
 - c. Use a series of truth tables to make your proof.
- 3-14. Prove to your instructor that both logic diagrams drawn in Fig. 3-48(*b*) will generate a two-input NOR truth table. (*Hint:* Think of the bubbles as inverters.) You may use one of the following methods (ask instructor):
 - a. Wire and test logic circuits in hardware.
 - b. Wire and test logic circuits using a computer circuit simulation software.
 - c. Use a series of truth tables to make your proof.

- 3-15. Refer to Fig. 3-77(a). The normally open switches are wired _____ (active HIGH, active LOW) inputs.
- 3-16. Refer to Fig. 3-77(a). The LED at P1 will light when port 1 becomes _____ (HIGH, LOW).
- 3-17. Refer to Fig. 3-77. What three lines of PBASIC computer code declare which BS2 IC ports are inputs?
- 3-18. Refer to Fig. 3-77. What is the purpose of line 11 of the PBASIC code?
- 3-19. Refer to Fig. 3-77. If all inputs to the BASIC Stamp 2 module are HIGH, the output will be _____ (HIGH, LOW), and the red LED will _____ (light, not light).
- 3-20. Answer selected questions asked by your instructor about the PBASIC program and the programming and operation of the BASIC Stamp 2 module detailed in Fig. 3-77.

Critical Thinking Questions...continued

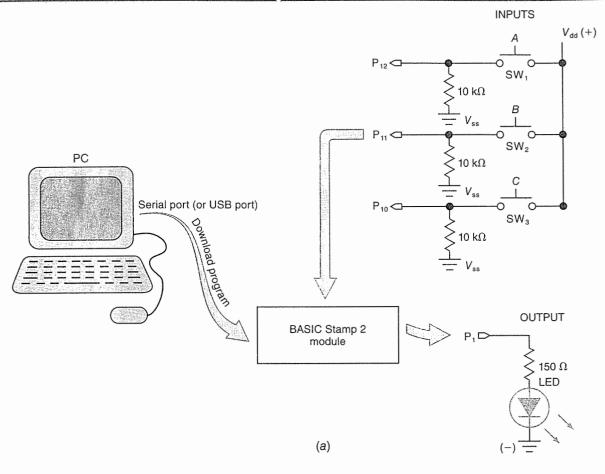

```
'Three-input XOR function
                                        '<---Line 1
                                        '<---Line 2
         VAR Bit
Α
                                        '<---Line 3
         VAR
                Bit
В
C
         VAR
                Bit
                                        '<---Line 4
                                        'Declare Y a variable, 1 bit
Y
         VAR Bit
                                        '<---Line 6
INPUT 10
                                        '<---Line 7
INPUT 11
                                        '<---Line 8
INPUT 12
OUTPUT 1
                                        'Declare port 1 as output (red LED)
                                        'Label for check switch routine
Ckswitch:
         OUT1 = 0
                                        '<---Line 11
                                        '<---Line 12
         A = IN12
                                        '<---Line 13
         B = IN11
                                        '<---Line 14
         C = IN10
         Y = A \wedge B \wedge C
                                        '<---Line 15
         If Y = 1 THEN Red
                                        'If Y = 1 then go to red subroutine, otherwise next line
GOTO Ckswitch
                                        'Go to Ckswitch—begin check switch routine again
                                        'Label for lighting red LED, means HIGH
Red:
         OUT1 = 1
                                        '<---Line 19
         PAUSE 100
                                        '<---Line 20
GOTO Ckswitch
                                        'Go to Ckswitch: begin check switch routine again
```

Fig. 3-77 (a) Wiring of BASIC Stamp 2 module used with the three-input XOR function program. (b) PBASIC program loaded into BS2 module.



Answers to Self-Tests

- 1. $A \cdot B = Y \text{ or } AB = Y$
- 2. HIGH, light
- 3. 0
- 4. 0
- 5. 1
- 6. 0
- 7. HIGH
- 8. HIGH
- 9. A + B = Y
- 10. 1
- 11.0 12. 1
- 13. LOW
- 14. inclusive
- 15. LOW
- 16. LOW 17. LOW
- 18. $Y = \overline{A}$ or Y = A'
- 19. negated,
- complemented
- 20. LOW
- 21. HIGH
- 22. LOW
- 23. high-impedance
- 24. $\overline{A \cdot B} = Y \text{ or } \overline{AB} = Y$ or (AB)' = Y
- 25. 1
- 26. 0
- 27. 1
- 28. LOW
- 29. $\overline{A \cdot B \cdot C} = Y$ or $\overline{ABC} = Y$ or
- (ABC)' = Y
- 30. LOW 31. $\overline{A+B} = Y$ or

(A+B)'=Y


32. 1

- 33. 0
- 34. 0
- 35. HIGH
- 36. $\overline{A + B + C} = Y$ or (A + B + C)' = Y
- 37. HIGH
- 38. $A \oplus B \oplus C = Y$
- 39. 1
- 40.0
- 41. 1
- 42. 1
- 43. 0
- 44. odd
- 45. $\overline{A \oplus B \oplus C} = Y$
- 46. 0
- 47. 0
- 48. 0
- 49. 1
- 50. 1
- 51. LOW
- 52. connected together
- 53. $A \cdot B = Y \text{ or } AB = Y$
- 54. 0
- 55. 0
- 56. 1
- 57. 0
- 58. 0
- 59. 1
- 60. $\overline{A \cdot B \cdot C} = Y \text{ or } \overline{ABC}$
- = Y or (ABC)' = Y
- 61. eight
- 62. $\overline{A+B+C+D} = Y$ or (A + B + C + D)'
 - = Y
- 63. $32(2^5)$
- 64. AND
- 65. 128

- 66. inverters
- 67. NOR
- 68. NAND
- 69. OR
- 70. $\overline{A + B} = Y$
- 71. $\overline{A} \cdot \overline{B} = Y$
- 72. TTL, CMOS
- 73. dual in-line package (DIP)
- 74.5, +
- 75. TTL quad two-input AND gate
- 76. package = DIP
 - family = low-power
 - Schottky
 - function = quad
 - two-input AND
- 77. FAST (Fairchild Advanced Schottky
 - TTL)
- 78. CMOS
- 79. low
- 80. 3, 18
- 81. CMOS quad two-input AND gate
- 82. All unused CMOS inputs must be con-
- nected (not floating) 83. HIGH
- 84. T
- 85. T
- 86. T
- 87. TTL and CMOS
- 88. Use your senses to locate possible open circuits, short circuits,
 - or overloading

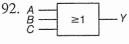- 89. Check that each IC has power
- 90. not allowed







- 94. bubble
- 95. traditional
- 96. disabled
- 97. passed through
- 98. frequency counter
- 99. pressed, LOW, HIGH
- 100. active HIGH
- 101. bubble
- 102. sounds
- 103. does not sound
- 104. microcontroller
- 105. false
- 106. OR
- 107. $Y = {\sim}(A \& B)$
- 108. Y = A & B
- 109. $Y = {(A \hat{B})}$
- 110. $Y = {\sim}(A \mid B)$
- 111. HIGH, light 112. LOW, not light



Combining Logic Gates

Learning Outcomes

This chapter will help you to:

- **4-1** *Draw* logic diagrams from minterm and maxterm Boolean expressions.
- **4-2** Design a logic diagram from a truth table by first developing a minterm Boolean expression and then drawing the AND-OR logic diagram.
- **4-3** Reduce a minterm Boolean expression to its simplest form using two-, three-, four-, and five-variable Karnaugh maps.
- **4-4** Simplify AND-OR logic circuits using NAND gates.
- 4-5 Convert back and forth from Boolean expression to truth table to logic symbol diagram using computer simulation software (such as the Logic Converter instrument from Multisim or Electronic Workbench).
- **4-6** Solve logic problems using data selectors.
- **4-7** *Understand* the fundamentals of selected programmable logic devices (PLDs).
- **4-8** Convert minterm-to-maxterm and maxterm-to-minterm Boolean expressions using De Morgan's theorems.
- **4-9** *Use* a "keyboard version" of Boolean expressions.
- **4-10** *Program* several logic functions using a BASIC Stamp 2 Microcontroller Module.

arlier you memorized the symbol, truth table, and Boolean expression for each logic gate. These gates are the building blocks for more complicated digital devices. In this chapter you will use your knowledge of gate symbols, truth tables, and Boolean expressions to solve real-world problems in electronics.

You will be connecting gates to form what engineers refer to as *combinational logic circuits*. By definition, combinational logic is an interconnection of logic gates to generate a specified logic function where the inputs result in an immediate output, having no memory or storage capabilities. Digital circuits that have a memory or storage capability are called *sequential logic circuits* and will be studied later.

You will be combining gates (ANDs, ORs) and inverters to solve logic problems that do not require memory. The "tools of the trade" for solving combinational logic problems are truth tables, Boolean expressions, and logic symbols. Do you know your truth tables, Boolean expressions, and logic symbols? An understanding of combination a logic is knowledge required of all who work as a technician, troubleshooter, designer, or engineer in electronics.

To gain maximum experience you should try to implement your combinational logic circuits in hardware in the laboratory. Logic gates are packaged in inexpensive, easyto-use integrated circuits (ICs). Also, your combinational logic circuits can be tested using circuit simulation software on your computer.

Combinational logic problems can be solved with "hard logic" using traditional

Combinational logic circuits

Sequential logic circuits

ICs. More complicated combinational logic problems are solved with *programmable logic devices (PLDs)*. You can also program a microcontroller using a PC and the BASIC Stamp 2 module to solve combinational logic problems.

4-1 Constructing Circuits from Boolean Expressions

We use Boolean expressions to guide us in building logic circuits. Suppose you are given the Boolean expression A + B + C = Y (read as "A or B or C equals output Y") and told to build a circuit that will perform this logic function. Looking at the expression, notice that each input must be ORed to get output Y. Figure 4-1 illustrates the *gate* needed to do the job.

Now suppose you are given the Boolean expression $\overline{A} \cdot B + A \cdot \overline{B} + \overline{B} \cdot C = Y$ (read as "not A and B, or A and not B, or not B and C equals output Y"). How would you construct a circuit that will do the job of this expression?


The first step is to look at the Boolean expression and note that you must $OR \ \overline{A} \cdot B$ with $A \cdot \overline{B}$ with $\overline{B} \cdot C$. Figure 4-2(a) shows that a three-input OR gate will form the output Y. This may be redrawn as in Fig. 4-2(b).


The second step used in constructing a logic circuit from the given Boolean expression $\overline{A} \cdot B + A \cdot \overline{B} + \overline{B} \cdot C = Y$ is shown in Fig. 4-3. Notice in Fig. 4-3(a) that an AND gate has been added to feed the $\overline{B} \cdot C$ to the OR gate and an inverter has been added to form the \overline{B} for the input to AND gate 2. Figure 4-3(b) adds AND gate 3 to form the $A \cdot \overline{B}$ input to the OR gate. Finally, Fig. 4-3(c) adds AND gate 4 and inverter 6 to form the $\overline{A} \cdot B$ input to the OR gate. Figure 4-3(c) is the circuit that would be constructed to perform the required logic given in the Boolean expression $\overline{A} \cdot B + A \cdot \overline{B} + \overline{B} \cdot C = Y$.

Notice that we started at the output of the logic circuit and worked toward the inputs. You have now experienced how combinational logic circuits are constructed from Boolean expressions.



Fig. 4-1 Logic diagram for Boolean expression A + B + C = Y.

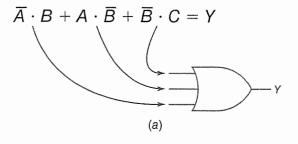

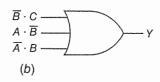

Constructing logic circuit from a Boolean expression


Fig. 4-2 Step 1 in constructing a logic circuit.


Boolean expressions come in two forms. The *sum-of-products (SOP) form* is the type we saw in Fig. 4-2. Another example of this form is $A \cdot B + B \cdot C = Y$. The other Boolean expression form is the *product of sums (POS)*; an example is $(D + E) \cdot (E + F) = Y$. The sum-of-products form is called the *minterm form* in

Sum-of-products (SOP) form

Product-of-sums (POS) form

Minterm form

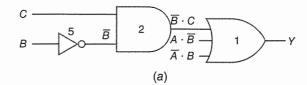

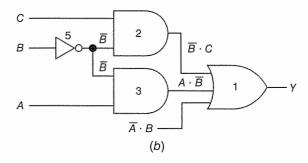

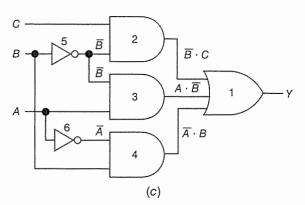


Fig. 4-3 Step 2 in constructing a logic circuit.

Maxterm form

Circuit simulation software

engineering texts. The product-of-sums form is called the *maxterm form* by engineers, technicians, and scientists.

Computer *circuit simulation software*, such as Electronics Workbench or Multisim, will draw a logic diagram from a Boolean expression.

This software can draw logic diagrams from either minterm or maxterm Boolean expressions. Professionals in digital design will commonly use computer circuit simulations. Your instructor may have you use circuit simulation software in the lab.

--{}}- | Self-Te

Answer the following questions.


1. Construct logic circuits using AND, OR, and NOT gates for the following minterm Boolean expressions:

a.
$$\overline{A} \cdot \overline{B} + A \cdot B = Y$$

b.
$$\overline{A} \cdot \overline{C} + A \cdot B \cdot C = Y$$

c.
$$A \cdot D + \overline{B} \cdot \overline{D} + C \cdot \overline{D} = Y$$

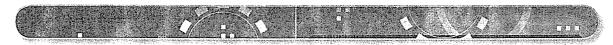- 2. A minterm Boolean expression is also called the ______ form.
- 3. A maxterm Boolean expression is also called the ______ form.
- 4. The minterm Boolean expression $A \cdot D + \overline{B} \cdot \overline{D} + C \cdot \overline{D} = Y$ has a pattern that is called the _____ (product-of-sums, sum-of-products) form.
- 5. The maxterm Boolean expression $(A + D) \cdot (B + \overline{C}) \cdot (A + C) = Y$ has a pattern that is called the ______ (product-of-sums, sum-of-products) form.



4-2 Drawing a Circuit from a Maxterm Boolean Expression

Suppose you are given the maxterm Boolean expression $(A + B + C) \cdot (\overline{A} + \overline{B}) = Y$. The first step in constructing a logic circuit for this Boolean expression is shown in Fig. 4-4(a). Notice that the terms (A + B + C) and $(\overline{A} + \overline{B})$ are ANDed together to form output Y. Figure 4-4(b) shows the logic circuit redrawn.

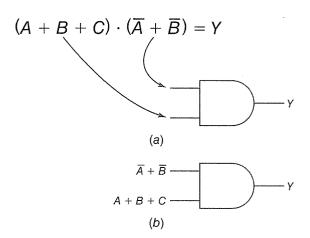


Fig. 4-4 Step 1 in constructing a product-of-sums logic circuit.

The second step in drawing the logic circuit is shown in Fig. 4-5. The $(\overline{A} + \overline{B})$ part of the expression is produced by adding OR gate 2 and inverters 3 and 4, as illustrated in Fig. 4-5(a). Then, the expression (A + B + C) is delivered to the AND gate by OR gate 5 in Fig. 4-5(b). The logic circuit shown in Fig. 4-5(b) is the

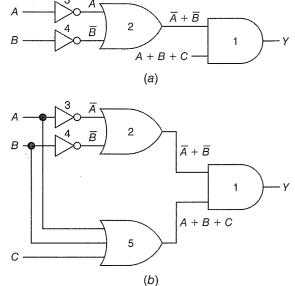


Fig. 4-5 Step 2 in constructing a product-of-sums logic circuit.

complete logic circuit for the maxterm Boolean expression $(A + B + C) \cdot (\overline{A} + \overline{B}) = Y$.

In summary, we work from right to left (from output to input) when converting a Boolean expression to a logic circuit. Notice that we use only AND, OR, and NOT gates when constructing combinational logic circuits. Maxterm and minterm Boolean expressions both can be converted to logic circuits. Minterm expressions

create AND-OR logic circuits similar to that in Fig. 4-3(c), whereas maxterm expressions create OR-AND logic circuits similar to that in Fig. 4-5(b).

You now should be able to identify minterm and maxterm Boolean expressions, and you should be able to convert Boolean expressions to combinational logic circuits by using AND, OR, and NOT gates.



Self-Test

Answer the following questions.

6. Construct a logic circuit using AND, OR, and NOT gates from the following Boolean expressions:

a.
$$(A + B) \cdot (\overline{A} + \overline{B}) = Y$$

b.
$$(\overline{A} + B) \cdot \overline{C} = Y$$
.

c.
$$(A + B) \cdot (\overline{C} + \overline{D}) \cdot (\overline{A} + C) = Y$$

- 7. Refer to question 6. These Boolean expressions are in _____ (maxterm, minterm) form.
- 8. Refer to question 6. These Boolean expressions are in _____ (product-of-sums, sum-of-products) form.
- Maxterm Boolean expressions are used to create _____ (AND-OR, OR-AND) logic circuits.



4-3 Truth Tables and Boolean Expressions

Boolean expressions are a convenient method of describing how a logic circuit operates. The *truth table* is another precise method of describing how a logic circuit works. As you work in digital electronics, you may have to convert information from truth-table form to a Boolean expression.

Truth Table to Boolean Expression

Look at the truth table in Fig. 4-6(a). Notice that only two of the eight possible combinations of inputs A, B, and C generate a logical 1 at the output. The two combinations that generate a 1 output are shown as $\overline{C} \cdot B \cdot A$ (read as "not C and B and A") and $C \cdot \overline{B} \cdot \overline{A}$ (read as "C and not B and not A"). Figure 4-6(B) shows how the combinations are ORed together to form the Boolean expression for the truth table. Both the truth table in Fig. 4-6(B) and the Boolean expression in Fig. 4-6(B) describe how the logic circuit should work.

Truth table

11	IPUT	S	OUTPUT	
С	В	Α	Y	
0	0	0	0	
0	0	1	0	
0	1	0	0	$\overline{C} \cdot B \cdot A = 1$
0	1	1	1	$U \cdot B \cdot A = 1$
1	0	0	1	$C \cdot \overline{B} \cdot \overline{A} = 1$
1	0	1	0	O B A I
1	1	0	. 0	
1	1	1	0	
			(a)

(b) Boolean expression


$$\overline{C} \cdot B \cdot A + C \cdot \overline{B} \cdot \overline{A} = Y$$

Fig. 4-6 Forming a minterm Boolean expression from a truth table.

The truth table is the origin of most logic circuits. You must be able to convert the truth-table information into a Boolean expression as in this section. Remember to look for combinations of variables that generate a logical 1 output in the truth table.

Forming a Boolean expression from a truth table

(a) Boolean expression

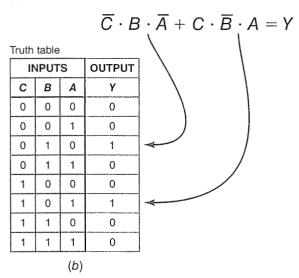


Constructing a truth table from a Boolean expression

Fig. 4-7 Constructing a truth table from a minterm Boolean expression.

Boolean Expression to Truth Table

Occasionally you must reverse the procedure you have just learned. That is, you must take a Boolean expression and from it construct a truth table. Consider the Boolean expression in Fig. 4-7(a). It appears that two combinations of inputs A, B, and C generate a logical 1 at the output. In Fig. 4-7(b) we find the correct combinations of A, B, and C that are given in the

arouge electronics.

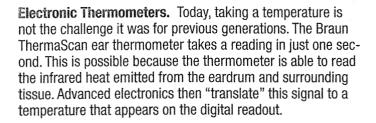



(a) Boolean expression

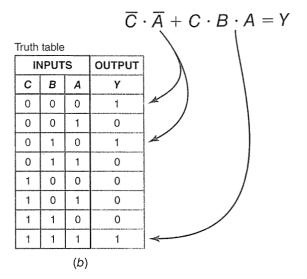


Fig. 4-8 Constructing a truth table from a minterm Boolean expression.

Boolean expression and mark a 1 in the output column. All other outputs in the truth table are 0. The Boolean expression in Fig. 4-7(a) and the truth table in Fig. 4-7(b) both accurately describe the operation of the same logic circuit.

Suppose you are given the Boolean expression in Fig. 4-8(a). At first glance it seems that this would produce two outputs with a logical 1. However, if you look closely at Fig. 4-8(b) you will see that the Boolean expression $\overline{C} \cdot \overline{A} + C \cdot B \cdot A = Y$ actually generates three logical 1s in the output column. The "trick" illustrated in Fig. 4-8 should make you very cautious. Make sure you have all the combinations that generate a logical 1 in the truth table. The Boolean expression in Fig. 4-8(a) and the truth table in Fig. 4-8(b) both describe the same logic circuit or logic function.

You have now converted truth tables to Boolean expressions and Boolean expressions to truth tables. You were reminded that the Boolean expressions you worked with were minterm Boolean expressions. The procedure for producing maxterm Boolean expressions from a truth table is quite different.

Circuit Simulation Conversions

Circuit simulation software running on modern computers can accurately convert Boolean expressions to truth tables or truth tables to Boolean expressions. We will demonstrate the use of one popular electronic circuit simulator.

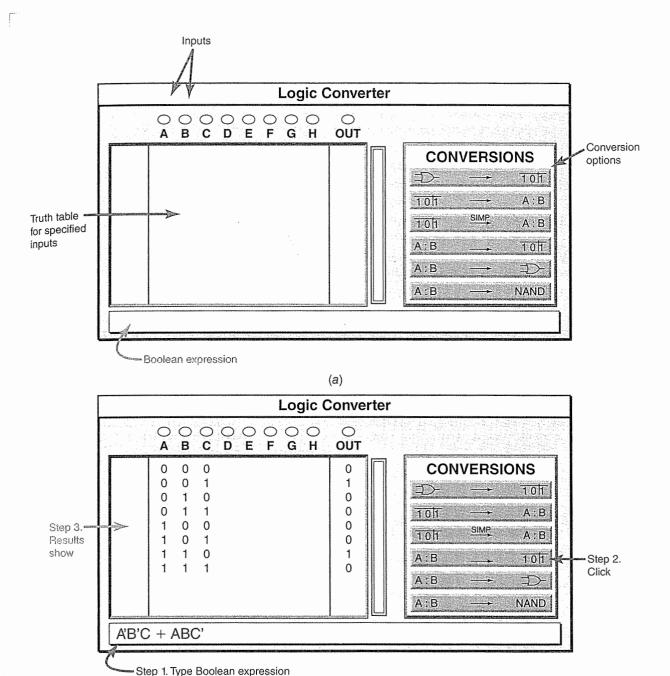


Fig. 4-9 Lagic converter instrument from an electronic circuit simulator. (a) Lagic converter instrument layout. (b) The three steps in converting a Boolean expression to a truth table.

(b)

Multisim logic converter

One easy-to-use circuit simulator is Electronics Workbench (EWB) or Multisim. The EWB software contains an instrument called a *logic converter*, shown in Fig. 4-9(a). To use this EWB instrument to convert a Boolean expression to a truth table, you would take the following steps:

Step 1. Type the expression in the bottom section (see Fig. 4-9(b)).

Step 2. Activate the Boolean expression to a truth-table option (see Fig. 4-9(b)).

Step 3. View the resulting truth table on the computer monitor (see Fig. 4-9(b)).

The Boolean expression A'B'C + ABC' entered in step 1, Fig. 4-9(b), is a shortened *keyboard version* of the $C \cdot \overline{B} \cdot \overline{A} + \overline{C} \cdot B \cdot A = Y$ in Fig. 4-6(b). It is important to recognize that A'B'C + ABC' equals $C \cdot \overline{B} \cdot \overline{A} + \overline{C} \cdot B \cdot A = Y$. The apostrophe in the keyboard version of a Boolean expression means the same as an overbar over that letter. Therefore A' (say "A not") means the same as

Boolean expression keyboard version \overline{A} (say "A not"). Notice that the *order* that the variables appear in the Boolean expression are reversed. This difference in order has no effect on the logic function. Therefore, ABC means the same as CBA. Also notice that the AND dot between variables has been eliminated so that $A \cdot B \cdot C$ can be shortened to ABC.

Compare the output columns in Figs. 4-6(a) and 4-9(b). Both these truth tables describe the same logic function although the output columns seem different. This is because the order of the input variables are listed as CBA in Fig. 4-6(a) whereas they appear as ABC in Fig. 4-9(b). Truth table line 5 (100)

in Fig. 4-6(a) is the same as line 2 (001) in Fig. 4-9(b). This demonstrates that the headings on truth tables and Boolean expression representations vary. Workers in electronics will become familiar with several methods of labeling truth tables and variations in Boolean expressions.

Electronic circuit simulators such as EWB can commonly handle either minterm or maxterm Boolean expressions. Observe from Fig. 4-9(a) that five other logic conversions are available using this version of EWB. Your instructor may have you use the many features available on your electronic circuit simulation software.

W- Self-Test

Answer the following questions.

10. Refer to Fig. 4-10. Write the sum-of-products Boolean expression that describes of the logic function of this truth table.

Truth table

11	IPUT	OUTPUT	
С	В	Α	Υ
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Fig. 4-10 Three-variable truth table.


- 11. Refer to Fig. 4-11. The Boolean expression $\overline{C} \cdot \overline{B} \cdot \overline{A} + \overline{C} \cdot \overline{B} \cdot A = Y$ produces a truth table that has HIGH (1) outputs in which two lines?
- 12. Construct a truth table for the Boolean expression $C \cdot B \cdot \overline{A} + C \cdot \overline{B} \cdot A = Y$.
- 13. The procedure illustrated in Fig. 4-6 converts a truth table to a _____ (maxterm, minterm) Boolean expression.

Truth table

	II.	IPUT	OUTPUT	
	С	В	Y	
line 0	0	0	0	
line 1	0	0	1	
line 2	0	1	0	
line 3	0	1	1	
line 4	1	0	0	
line 5	1	0	1	
line 6	1	1	0	
line 7	1	1	1	

Fig. 4-11 Three-variable truth table.

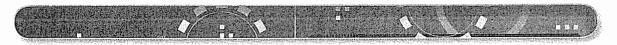- 14. The procedure illustrated in Figs. 4-7 and 4-8 converts a ______ (maxterm, minterm) Boolean expression to a truth
- 15. Write the keyboard version of the Boolean expression $\overline{C} \cdot \overline{B} \cdot A + B \cdot \overline{A} = Y$.
- 16. The Boolean expression $A \cdot B \cdot C = Y$ means the same as ABC = Y. (*T* or *F*)
- 17. The Boolean expression $A \cdot B \cdot C = Y$ will generate the same truth table as $C \cdot B \cdot A = Y$. (*T* or *F*)
- 18. A'C' + AB = Y is the keyboard version of the traditional Boolean expression $(\overline{A} + \overline{C}) \cdot (A + B) = Y \cdot (T \text{ or } F)$



4-4 Sample Problem

The procedures in Secs. 4-1 to 4-3 are useful skills as you work in digital electronics. To assist you in developing your skills, we shall take an everyday logic problem and work from truth table to Boolean expression to logic circuit as shown in Fig. 4-12.


Let us assume that we are designing a simple electronic lock. The lock will open only when certain switches are activated. Figure 4-12(a) is the truth table for the electronic lock. Notice that the two combinations of input switches, A, B, and C generate a 1 at the output. A HIGH (or 1) output will open the lock. Figure 4-12(b) shows how we form the minterm Boolean expression for the electronic lock circuit. The logic circuit in Fig. 4-12(c) is then drawn from the Boolean expression. Look over the sample problem in Fig. 4-12, and be sure you can follow how we converted from the truth table to the Boolean expression and then to the logic circuit.

Many electronic circuit simulation programs can handle these conversions. For instance, the logic converter instrument in Electronics Workbench or Multisim could make these conversions. The logic converter instrument from Electronics Workbench or Multisim will be used to solve the lock problem presented earlier. The steps in solving this lock problem using this software are represented in Fig. 4-13. These steps are:

Step 1: Fill out the lock problem truth table [see Fig. 4-13(*a*)].

Step 2: Activate the truth table to Boolean expression [see Fig. 4-13(a)]. The resulting Boolean expression will be A'B'C + ABC.

Step 3: Activate the Boolean expression to logic circuit button [see Fig. 4-13(*b*)]. The resulting AND-OR logic will be displayed on the EWB screen.

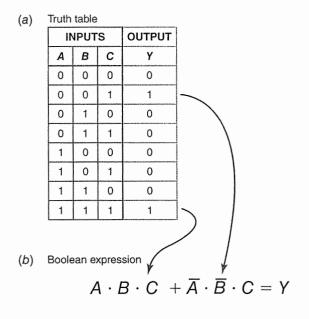


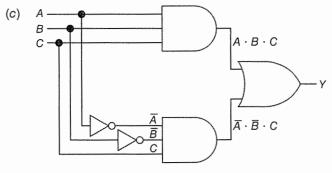


Fig. 4-12 Electronic lock problem. (a) Truth table. (b) Boolean expression. (c) Logic circuit.

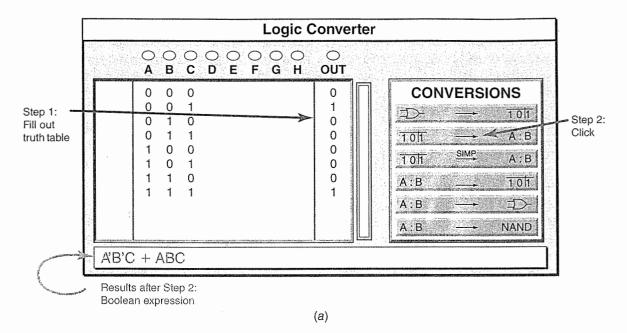

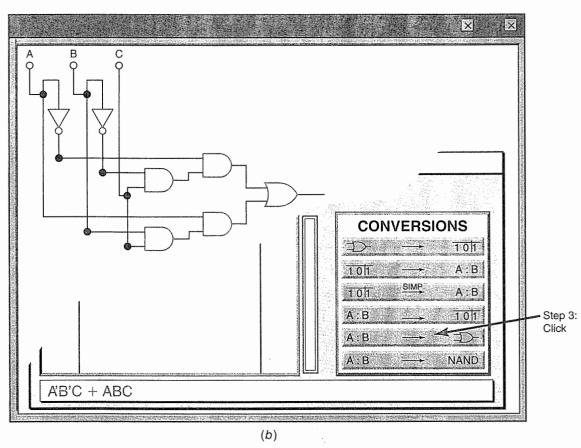


Fig. 4-13 EWB logic converter software used to solve logic problem. (a) Truth table to Boolean expression. (b) Boolean expression to logic circuit conversion.

You should now be able to solve a logic problem like the one described in this section. You can solve these problems either by hand (Fig. 4-12) or by using simulation software

(Fig. 4-13). The following test will give you some practice in solving problems dealing with truth tables, Boolean expressions, and combinational logic circuits.

Answer the following questions.

- 19. Using the truth table in Fig. 4-14, for an electronic lock, write the minterm Boolean expression for this truth table.
- 20. From the Boolean expression developed in question 19, draw a logic symbol diagram for the electronic lock problem.

Truth table

	NPUT TTCH		OUTPUT
С	C B		Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1 1		1	0

Fig. 4-14 Truth table for lock problem.



4-5 Simplifying Boolean Expressions


Consider the Boolean expression $\overline{A} \cdot B + A$. $\overline{B} + A \cdot B = Y$ in Fig. 4-15(a). In constructing a logic circuit for this Boolean expression, we find that we need three AND gates, two inverters, and one 3-input OR gate. Figure 4-15(b) is a logic circuit that would perform the logic of the Boolean expression $\overline{A} \cdot B + A \cdot \overline{B} + A \cdot B = Y$. Figure 4-15(c) details the truth table for the Boolean expression and logic circuit in Fig. 4-15(a) and (b). Immediately you recognize the truth table in Fig. 4-15(c) as the truth table for a two-input OR gate. The simple Boolean expression for a two-input OR gate is A + B =Y, as shown in Fig. 4-15(d). The logic circuit for a two-input OR gate in its simplest form is diagrammed in Fig. 4-15(e).

The example summarized in Fig. 4-15 shows how we must try to simplify our original Boolean expression to get a simple, inexpensive logic circuit. In this case we were lucky enough to notice that the truth table belonged to an OR gate. However, usually we must use more systematic methods of simplifying our Boolean expression. Such methods include applying Boolean algebra, *Karnaugh mapping*, and computer simulations.

Boolean algebra was originated by George Boole (1815–1864). Boole's algebra was adapted in the 1930s for use in digital logic circuits; it is

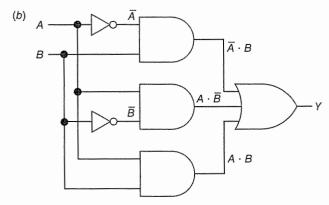(a) Original Boolean expression

$$\overline{A} \cdot B + A \cdot \overline{B} + A \cdot B = Y$$



(c)

Truth table						
INP	UTS	OUTPUT				
Α	В	Y				
0 0		0				
0 1		1				
1	0	1				
1	1	1				

(d) Simplified Boolean expression

$$A + B = Y$$

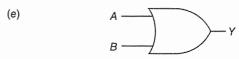


Fig. 4-15 Simplifying Boolean expressions. (a) Unsimplified Boolean expression. (b) Complex logic diagram. (c) Truth table. (d) Simplified Boolean expression: two-input OR by inspection. (e) Simple logic diagram.

Boolean algebra

Karnaugh mapping

Tabular method of simplification

Quine-McCluskey method the basis for the tricks we shall use to simplify Boolean expressions. Only selected topics in Boolean algebra are covered in this text. Many of you who continue on in digital electronics and engineering will study Boolean algebra in detail.

Karnaugh mapping, an easy-to-use graphic method of simplifying Boolean expressions, is

covered in detail in Secs. 4-6 to 4-10. Several other simplification methods are available, including Veitch diagrams, Venn diagrams, and the *tabular method of simplification*. The tabular method used by computer software such as Multisim is called the *Quine-McCluskey method*.

-√V- Self-Test

Supply the missing word or words in each statement.

- 21. The logic circuits in Fig. 4-15(*b*) and (*e*) produce _____ (different, identical) truth tables.
- 22. Boolean expressions can many times be simplified by inspection or by using
- methods that include _____ algebra or ____ mapping.
- 23. Karnaugh mapping is a systematic graphic method of logic circuit simplification, but the _____ method is better suited for computer simplification.



4-6 Karnaugh Maps

Maurice Karnaugh

Karnaugh map

Looping

In 1953 Maurice Karnaugh published an article about his system of mapping and thus simplifying Boolean expressions. Figure 4-16 illustrates a Karnaugh map. The four squares (1, 2, 3, 4) represent the four possible combinations of A and B in a two-variable truth table. Square 1 in the Karnaugh map, then, stands for $\overline{A} \cdot \overline{B}$, square 2 for $\overline{A} \cdot B$, and so forth.

Let us map the familiar problem from Fig. 4-15. The original Boolean expression $\overline{A} \cdot B + A \cdot \overline{B} + A \cdot B = Y$ is rewritten in Fig. 4-17(a) for your convenience. Next, 1s are placed in each square of the Karnaugh map, as shown in Fig. 4-17(b). The filled-in *Karnaugh map* (*K map*) is now ready for *looping*. The looping technique

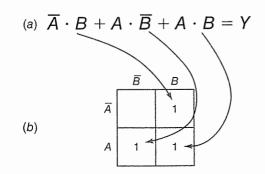


Fig. 4-17 Marking 1s on a Karnaugh map.

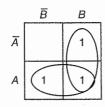


Fig. 4-18 Looping 1s together on a Karnaugh map.

Truth table **INPUTS OUTPUT** Α В 2 0 $\overline{A}\overline{B}$ 0 ĀΒ 0 1 $A \overline{B}$ 1 0 ABKarnaugh map

Fig. 4-16 The meaning of the squares in a Karnaugh map.

is shown in Fig. 4-18. Adjacent 1s are looped together in groups of two, four, or eight. Looping continues until all 1s are included inside a loop. Each loop represents a new term in the simplified Boolean expression. Notice that we have two loops in Fig. 4-18. These two loops mean that we shall have two terms ORed together in our new simplified Boolean expression.

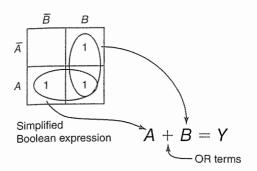


Fig. 4-19 Simplifying a Boolean expression from a Karnaugh map.

Now let us simplify the Boolean expression based upon the two loops that are redrawn in Fig. 4-19. First the bottom loop: Notice that an A is included along with a B and a \overline{B} . The B and \overline{B} terms can be *eliminated* according to the rules of Boolean algebra. This leaves the A term in the bottom loop. Likewise, the vertical loop

contains an A and a \overline{A} , which are eliminated, leaving only a B term. The leftover A and B terms are then ORed together, giving the simplified Boolean expression A + B = Y.

The procedure for simplifying a Boolean expression sounds complicated. Actually, this procedure is quite easy after some practice. Here is a summary of the six steps:

- 1. Start with a minterm Boolean expression.
- 2. Record 1s on a Karnaugh map.
- 3. Loop adjacent 1s (loops of two, four, or eight squares).
- 4. Simplify by dropping terms that contain a term and its complement within a loop.
- 5. OR the remaining terms (one term per loop).
- 6. Write the simplified minterm Boolean expression.

Simplifying Boolean expressions




Self-Test

Answer the following questions.

24. The map shown in Fig. 4-17 was developed by _____.

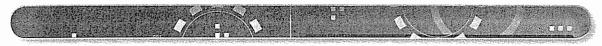25. List the six steps used in simplifying a Boolean expression using a Karnaugh map.




4-7 Karnaugh Maps with Three Variables

Consider the unsimplified Boolean expression $A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C} = Y$ as given in Fig. 4-20(a). A three-variable Karnaugh map is illustrated in Fig. 4-20(b). Notice the eight possible combinations of A, B, and C, which are represented by the eight squares in the map. Tabulated on the map are four 1s, which represent each of the four terms in the original Boolean expression. The Karnaugh map with loops is redrawn in Fig. 4-20(c). Adjacent groups of two 1s are looped. The bottom loop contains both a B and a \overline{B} . The B and \overline{B} terms are eliminated. The bottom loop still contains the A and \overline{C} , giving the $A \cdot \overline{C}$ term. The upper loop contains both a C and a \overline{C} . The C and \overline{C} terms are eliminated, leaving the $\overline{A} \cdot \overline{B}$ term. A minterm Boolean expression is formed by adding the OR symbol. The simplified Boolean expression is written in Fig. 4-20(*d*) as $A \cdot \overline{C} + \overline{A} \cdot \overline{B} = Y$.

You can see that the simplified Boolean expression in Fig. 4-20 would take fewer electronic parts than the original expression. Remember that the much different looking simplified Boolean expression produces the same truth table as the original Boolean expression.

It is critical that the Karnaugh map be prepared just as the one shown in Fig. 4-20. Note that as you progress downward on the left side of the map, only one variable changes for each step. At the top left \overline{A} \overline{B} is listed, while directly below is \overline{A} B (\overline{B} changed to B). Then, progressing downward from \overline{A} B to AB, the \overline{A} term is changed to A. Finally, moving downward from AB to A \overline{B} , the B term is changed to \overline{B} . The Karnaugh map will not work properly if it is not laid out correctly.

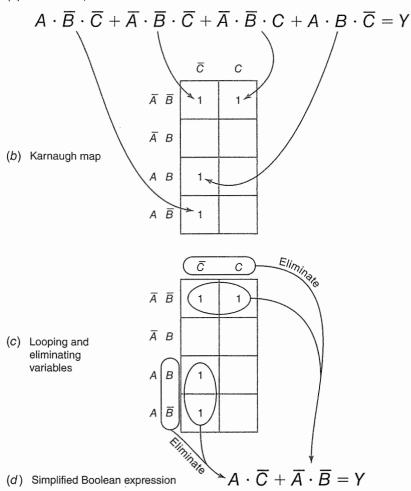Three-variable Karnaugh map (a) Boolean expression



Simplifying a Boolean expression

Fig. 4-20 Simplifying a Boolean expression using a Karnaugh map. (a) Unsimplified expression. (b) Mapping 1s. (c) Looping 1s and eliminating variables. (d) Forming simplified minterm expression.



Answer the following questions.

- 26. Simplify the Boolean expression $\overline{A} \cdot \overline{B} \cdot C + \overline{A} \cdot B \cdot C + A \cdot \overline{B} \cdot \overline{C} + A \cdot \overline{B} \cdot C = Y$ by:
 - a. Plotting 1s on a three-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complement appears within the loop(s)
 - d. Writing the simplified minterm Boolean expression

- 27. Simplify the Boolean expression $\overline{A} \cdot B \cdot \overline{C} + \overline{A} \cdot B \cdot C + A \cdot B \cdot \overline{C} + A \cdot B \cdot C$ = Y by:
 - a. Plotting 1s on a three-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complement appears within the loop(s)
 - d. Writing the simplified minterm Boolean expression



4-8 Karnaugh Maps with Four Variables

The truth table for four variables has 16 (24) possible combinations. Simplifying a Boolean expression that has four variables sounds complicated, but a Karnaugh map makes the job of simplifying easy.

Consider the Boolean expression $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D + \overline{A} \cdot \overline{B} \cdot C \cdot D = Y$, as in Fig. 4-21(a). The four-variable Karnaugh map in Fig. 4-21(b) gives the 16 possible combinations of A, B, C, and D. These are represented in the 16 squares of the map. Tabulated on the map are six 1s, which represent the six terms in the original Boolean expression. The Karnaugh

map is redrawn in Fig. 4-21(c). Adjacent groups of two 1s and four 1s are looped. The bottom loop of two 1s eliminates the D and \overline{D} terms. The bottom loop then produces the $A \cdot \overline{B} \cdot \overline{C}$ term. The upper loop of four 1s eliminates the C and \overline{C} and B and \overline{B} terms. The upper loop then produces the $\overline{A} \cdot D$ term. The $A \cdot \overline{B} \cdot \overline{C}$ and $\overline{A} \cdot D$ terms are then ORed together. The simplified minterm Boolean expression is written in Fig. 4-21(d) as $A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot D = Y$.

Observe that the same procedure and rules are used for simplifying Boolean expressions with two, three, or four variables and that larger loops in a Karnaugh map eliminate more variables. You must take care to make sure that the maps look just like the ones in Figs. 4-20 and 4-21.

Karnaugh maps with four variables

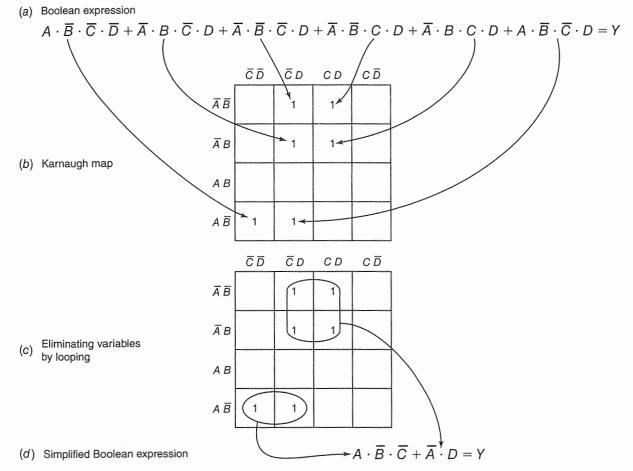



Fig. 4-21 Simplifying a four-variable Boolean expression using a Karnaugh map.

-√N- Self-Test

Answer the following questions.

- 28. Simplify the Boolean expression $\overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} + A \cdot B \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot C \cdot \overline{D} = Y$ by:
 - a. Plotting 1s on a four-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complements appear within loops
 - d. Writing the simplified minterm Boolean expression

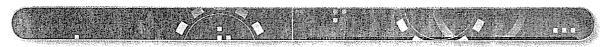- 29. Simplify the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D + \overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot \overline{D} + A \cdot B \cdot C \cdot \overline{D} = Y$ by:
 - a. Plotting 1s on a four-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complement appears within the loop(s)
 - d. Writing the simplified minterm Boolean expression



4-9 More Karnaugh Maps

This section presents some sample Karnaugh maps. Notice the unusual looping procedures used on most maps in this section.

Consider the Boolean expression in Fig. 4-22(a). The four terms are shown as four 1s on the Karnaugh map in Fig. 4-22(b).

adjacent to the right side. Also notice the elimination of the A and \overline{A} and C and \overline{C} terms. The simplified Boolean expression of $B \cdot \overline{D} = Y$ is shown in Fig. 4-22(c).

Another unusual looping variation is illustrated by the side of the side o

The correct looping procedure is shown. No-

tice that the Karnaugh map is considered to

be wrapped in a cylinder, with the left side

Another unusual looping variation is illustrated in Fig. 4-23(a). Notice that, while looping, the top and bottom of the map are adjacent to one another, as if rolled into a cylinder. The

(a) Boolean expression

$$A \cdot B \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} +
\overline{A} \cdot B \cdot C \cdot \overline{D} + A \cdot B \cdot C \cdot \overline{D} = Y$$


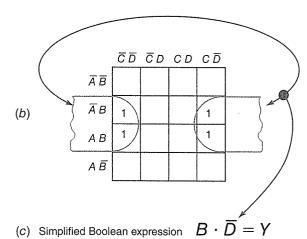


Fig. 4-22 Simplifying a Boolean expression by considering th

Fig. 4-22 Simplifying a Boolean expression by considering the map as a vertical cylinder. In this way, the four 1s can be looped.

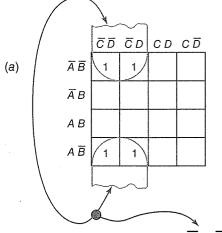

(b) Simplified Boolean expression $\overline{B}\cdot\overline{C}=Y$


Fig. 4-23 Simplifying a Boolean expression by considering the map as a horizontal cylinder. In this way, the four 1s can be looped.

K map looping

variations

simplified Boolean expression for this map is given as $\overline{B} \cdot \overline{C} = Y$ in Fig. 4-23(b). The A and \overline{A} as well as the D and \overline{D} terms have been eliminated in Fig. 4-23.

Figure 4-24(a) shows still another unusual looping pattern. The four corners of the Karnaugh map are considered connected, as if the map were formed into a ball. The four corners are then adjacent and may be formed into one loop as shown. The simplified Boolean expression is $\overline{B} \cdot \overline{D} = Y$, given in Fig. 4-24(b). In this example, the A and \overline{A} as well as the C and \overline{C} terms have been eliminated.

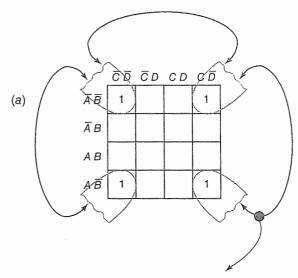

(b) Simplified Boolean expression $\,\,\overline{B}\cdot\overline{D}={\mathsf Y}\,\,$

Fig. 4-24 Simplifying a Boolean expression by thinking of the Karnaugh map as a ball. In this way, the 1s at the four corners can be enclosed in a single loop.

-V\^-

Self-Test

Answer the following questions.

- 30. Simplify the following Boolean expression $\overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D + \overline{A} \cdot \overline{B} \cdot C \cdot D = Y$ by:
 - a. Plotting 1s on a four-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complements appear within loops
 - d. Writing the simplified minterm Boolean expression

- 31. Simplify the following Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + A \cdot \overline{B} \cdot \overline{C} +$
 - $A \cdot \overline{B} \cdot C + A \cdot B \cdot C = Y$ by:
 - a. Plotting 1s on a three-variable Karnaugh map
 - b. Looping groups of two or four 1s
 - c. Eliminating variables whose complements appear within loops
 - d. Writing the simplified minterm Boolean expression



4-10 A Five-Variable Karnaugh Map

The Karnaugh map becomes three-dimensional when solving logic problems with more than four variables. A *three-dimensional Karnaugh* map will be used in this section.

A five-variable unsimplified Boolean expression is given in Fig. 4-25(a). A five-variable Karnaugh map is drawn in Fig. 4-25(b). Notice that it has 2 four-variable Karnaugh

maps stacked to make it three-dimensional. The top map is the E plane while the bottom is the \overline{E} (E not) plane.


Each of the nine terms in the unsimplified Boolean expression is plotted as a 1 on the Karnaugh map in Fig. 4-25(b). Adjacent groups of two, four, and eight are looped. The four 1s on the E and \overline{E} planes are also adjacent so that the entire group is enclosed in a cylinder and is considered a single group of eight 1s.

Five-variable Karnaugh map

Three-dimensional Karnaugh map

$$\begin{array}{l} A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E} + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D \cdot \overline{E} + \overline{A} \cdot B \cdot \overline{C} \cdot D \cdot \overline{E} + \\ \overline{A} \cdot \overline{B} \cdot C \cdot D \cdot \overline{E} + \overline{A} \cdot B \cdot C \cdot D \cdot \overline{E} + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D \cdot E + \\ \overline{A} \cdot B \cdot \overline{C} \cdot D \cdot E + \overline{A} \cdot \overline{B} \cdot C \cdot D \cdot E + \overline{A} \cdot B \cdot C \cdot D \cdot E = Y \end{array}$$

(a) Unsimplified Boolean expression

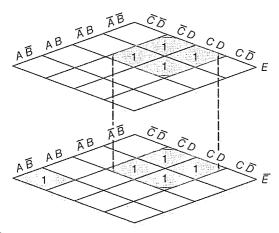

(b) Karnaugh map. Plotting 1s and looping

$$A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E} + \overline{A} \cdot D = Y$$

(c) Simplified Boolean expression

Fig. 4-25 Using a five-variable Karnaugh map to simplify a Boolean expression.

Looping cylinder

The next step is the conversion of the looped 1s on the Karnaugh map to a simplified minterm Boolean expression. The lone 1 on the \overline{E} plane of the map in Fig. 4-25(b) cannot be simplified and is written as $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E}$ in Fig. 4-25(c). The eight 1s enclosed in the

looping cylinder can be simplified. The E and \overline{E} , the C and \overline{C} , and the B and \overline{B} variables are eliminated leaving the term $\overline{A} \cdot D$. The terms $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E}$ and $\overline{A} \cdot D$ are ORed yielding the simplified minterm Boolean expression shown in Fig. 4-25(c) as $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E} + \overline{A} \cdot D = Y$.



Answer the following questions.

- 32. Simplify the Boolean expression $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot \overline{E} + A \cdot \overline{B} \cdot \overline{C} \cdot D \cdot \overline{E} + A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} \cdot E + A \cdot \overline{B} \cdot \overline{C} \cdot D \cdot E + \overline{A} \cdot B \cdot C \cdot D \cdot E + \overline{A} \cdot \overline{B} \cdot C \cdot D \cdot E = Y \text{ by:}$
 - a. Plotting 1s on a five-variable Karnaugh map

- b. Looping groups of two, four, or eight adjacent 1s
- c. Eliminating variables whose complements appear within loops or cylinders
- d. Writing the simplified minterm Boolean expression



4-11 Using NAND Logic

Earlier you learned that the NAND gate can be used as a universal gate. In this section, you will see how NAND gates are used in wiring combinational logic circuits. NAND gates might be used because they are easy to use and readily available.

Suppose your supervisor gives you the Boolean expression $A \cdot B + A \cdot \overline{C} = Y$, as shown in Fig. 4-26(a). You are told to solve this logic problem at the least cost. You first draw the

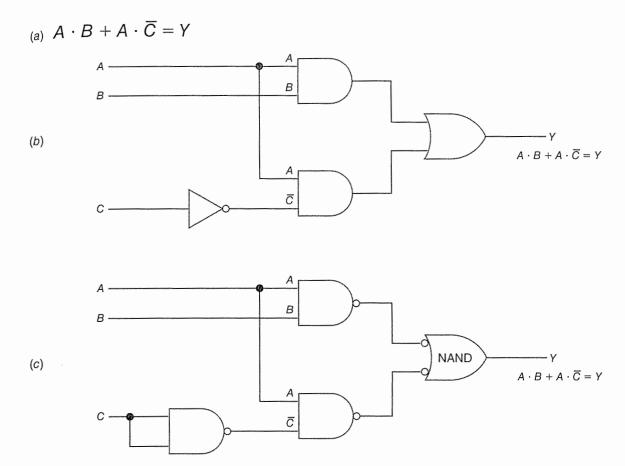


Fig. 426 Using NAND gates in logic circuits. (a) Boolean expression. (b) AND-OR logic circuit. (c) Equivalent NAND-NAND logic circuit.

logic circuit for the Boolean expression shown in Fig. 4-26(b), using AND gates, an OR gate, and an inverter. Checking manufacturer's data manuals, you determine that you must use three different ICs to do the job.

Your supervisor suggests that you try *using NAND logic*. You redraw your logic circuit to look like the NAND-NAND logic circuit in Fig. 4-26(c). Upon checking a catalog, you find you need only one IC that contains the four NAND gates to do the job. Recall that the OR symbol with invert bubbles at the inputs is another symbol for a NAND gate. You finally test the circuit in Fig. 4-26(c) and find that it performs the logic $A \cdot B + A \cdot \overline{C} = Y$. Your supervisor is pleased you have found a circuit that requires only one IC, as compared to the circuit in Fig. 4-26(b), which uses three ICs.

Remembering this trick will help you appreciate why NAND gates are used in many logic circuits. If your future job is in digital circuit design, this can be a useful tool for making your final circuit the best for the least cost.

You may have questioned why the NAND gates in Fig. 4-26(c) could be substituted for the

AND and OR gates in Fig. 4-26(*b*). If you look carefully at 4-26(*c*), you will see two AND symbols feeding into an OR symbol. From previous experience we know that if we invert twice, we have the original logic state. Hence the two invert bubbles in Fig. 4-26(*c*) between the AND and OR symbols cancel one another. Because the two invert bubbles cancel one another, we end up with two AND gates feeding an OR gate.

In summary, using NAND gates involves these steps:

- 1. Start with a minterm (sum-of-products) Boolean expression.
- 2. Draw the AND-OR logic diagram using AND, OR, and NOT symbols.
- 3. Substitute NAND symbols for each AND and OR symbol, keeping all connections the same.
- 4. Substitute NAND symbols with all inputs tied together for each inverter.
- Test the logic circuit containing all NAND gates to determine if it generates the proper truth table.

AND-OR logic circuit

NAND-NAND logic circuit

Using NAND logic



Answer the following questions.

- 33. The logic circuit in Fig. 4-26(b) is called _(AND-OR, NAND-NAND) circuit.
- 34. The logic circuits in Fig. 4-26(b) and (c) generate _____ (different, identical) truth tables.
- 35. List five steps in converting a sum-ofproducts Boolean expression to a NAND-NAND logic circuit.
- 36. Convert the minterm Boolean expression $\overline{A} \cdot \overline{B} + A \cdot B = Y$ to NAND logic by:
 - a. Drawing an AND-OR logic diagram of this expression
 - b. Redrawing the AND-OR diagram as a NAND-NAND logic diagram
- 37. Convert the minterm Boolean expression A'B' + ABC = Y to NAND logic by:
 - a. Drawing an AND-OR logic diagram of this expression
 - b. Redrawing the AND-OR diagram as a NAND-NAND logic diagram



4-12 Computer Simulations: Logic Converter

Designers and engineers have used professional Logic converter by computer simulation software running on power-Multisim ful workstations for decades. More recently easyto-use electronic circuit simulators that will run on a PC (personal computer) have become avail-

able. Inexpensive educational versions of circuit simulation software are very user-friendly.

Recall that three methods used to describe a combinational logic circuit is by its truth table, Boolean expression, or logic symbol diagram. A useful computer simulation instrument called a logic converter will convert back and forth between truth table, Boolean expressions, and combinational logic diagrams. The logic converter makes many of the tasks performed earlier in this chapter fast, easy, and accurate. The logic converter instrument, which is part of circuit simulation software by Electronics Workbench and Multisim, is sketched in Fig. 4-27. The tasks that this instrument can perform are listed as buttons on the right side under the title Conversions. The conversion options are (from top to bottom):

- 1. Logic diagram to truth table.
- 2. Truth table to unsimplified Boolean expression.
- 3. Truth table to simplified Boolean expression.
- 4. Boolean expression to truth table.

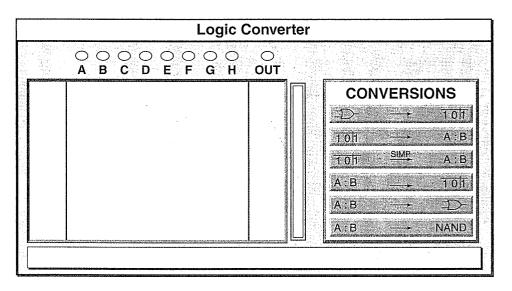


Fig. 4-27 Lagic Converter screen (from Electronics Workbench or Multisim).

- 5. Boolean expression to logic diagram using AND, OR, and NOT gates.
- 6. Boolean expression to logic diagram using NAND gates only.

You will notice that these are the same subjects covered earlier in the chapter.

An experiment using most of the conversion functions of the logic converter is illustrated in Fig. 4-28.

Step 1. in the experiment is to draw the logic symbol diagram and connect it to the logic converter as shown in Fig. 4-28(a). You will notice that this is an AND-OR pattern of logic gates that is equivalent to a minterm or sum-of-products Boolean expression.


Step 2. shows the logic converter enlarged on the screen and the top button (logic diagram to truth table) being activated. The results of this conversion are shown in Fig. 4-28(*b*) as an equivalent four-input truth table.

Step 3. illustrates the second button from the top (truth table to unsimplified Boolean expression) on the logic converter being activated. The result of this conversion is shown near the bottom of the screen in Fig. 4-28(b). The unsimplified Boolean expression is shown in its keyboard version as A'B'C'D' + A'B'CD' + A'BCD + ABCD.

Step 4. illustrates the third button from the top (truth table to simplified Boolean expression) on the logic converter being activated. The result of this conversion is shown near the bottom of the screen in Fig. 4-28(c). The simplified Boolean expression is shown in its keyboard version as A'B'D' + BCD.

Step 5. illustrates the bottom button (Boolean expression to NAND logic gate diagram) on the logic converter being activated. The result of this conversion is shown as a NAND-NAND logic circuit near the upper left of the screen in Fig. 4-28(d).

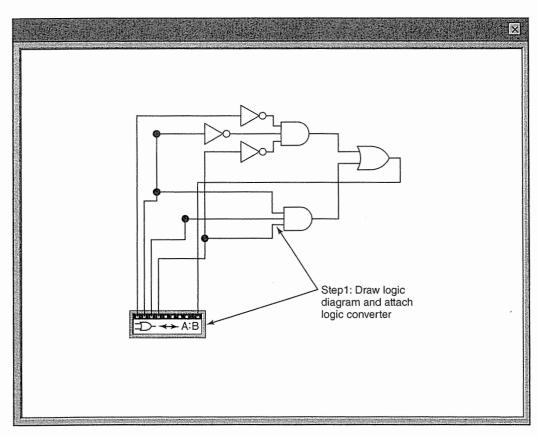In summary, modern computer simulations, such as the logic converter instrument we observed, make the task of converting back and forth between representations of logic functions easier, more accurate, and less time-consuming. Computer software and simulations are commonly used in the development stage of digital circuitry.



(a)

Fig. 4-28 (a) Step 1. Draw logic diagram.

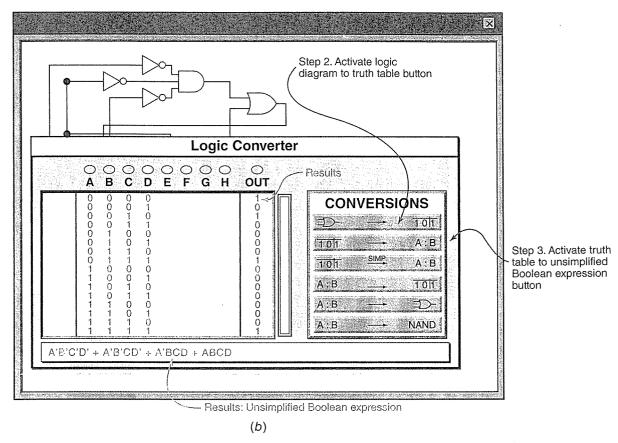


Fig. 4-28 (b) Steps 2 and 3. Generate truth table and unsimplified Boolean expression.

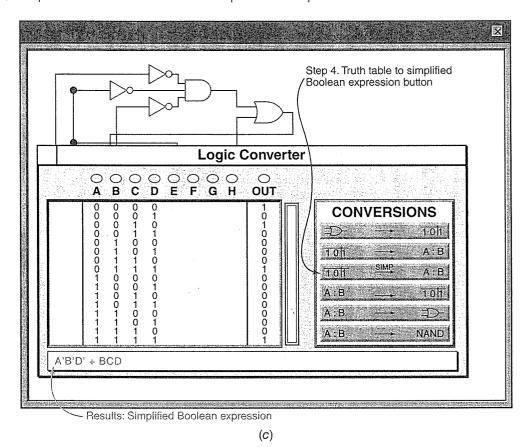


Fig. 4-28 (c) Step 4. Generate simplified Boolean expression.

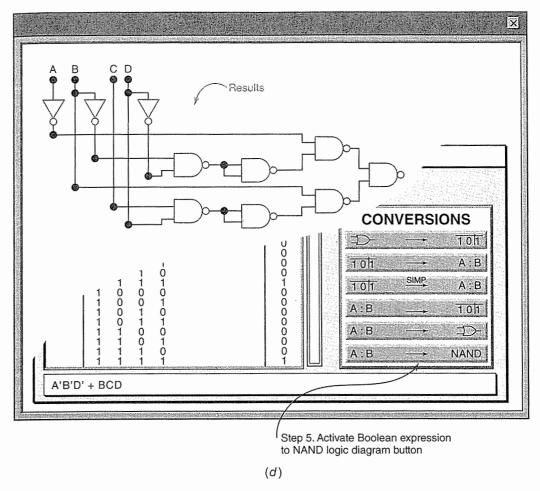



Fig. 4-28 (d) Step S. Generate the NAND logic diagram.



Answer the following questions with the aid of the logic converter from Electronics Workbench or Multisim.

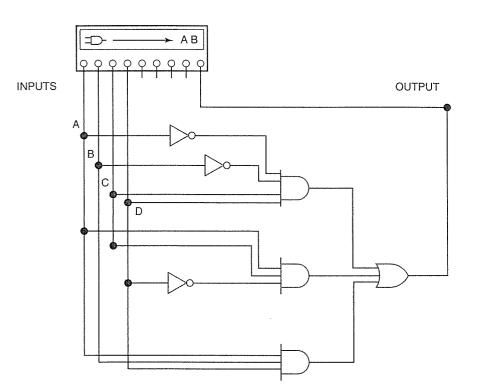- 38. Using the logic converter, (a) draw the AND-OR logic diagram in Fig. 4-29, (b) generate and copy its four-variable truth table, and (c) generate its simplified minterm Boolean expression.
- 39. Using the logic converter, (a) enter the minterm Boolean expression AC'D + BD', (b) generate and redraw the four-variable truth table for this expression,

- and (c) generate and copy the AND-OR logic diagram that represents this logic function.
- 40. Using the logic converter, (a) copy the truth table in Fig. 4-30 into the logic converter, (b) generate and write the unsimplified Boolean expression for this truth table, (c) generate and write the simplified Boolean expression, and (d) generate and sketch the AND-OR logic diagram for the simplified expression.



INPUTS OUTPUT D Α В С O O

Fig. 4-29 Logic converter problem.

Fig. 4-30 Truth table.



4-13 Solving Logic Problems: Data Selectors

Manufacturers of ICs have simplified the job of solving simple combinational logic problems by producing *data selectors*. A data selector is often a *one-package solution* to a complicated logic problem. The data selector actually contains a rather large number of gates packaged inside a single IC.

1-of-8 data selector A 1-of-Fig. 4-31. bered from

A 1-of-8 data selector is illustrated in Fig. 4-31. Notice the eight data inputs numbered from 0 to 7 on the left. Also notice the three data selector inputs labeled A, B, and C at the bottom of the data selector. The output of the data selector is labeled W.

The basic job the data selector performs is transferring data from a *given* data input (0 to 7) to the output (W). Which data input is selected is determined by which binary number you place on the data selector inputs at the bottom (see Fig. 4-31).

The data selector in Fig. 4-31 functions in the same manner as a rotary switch. Figure 4-32 shows the data at input 3 being transferred to the output by the *rotary switch* contacts.

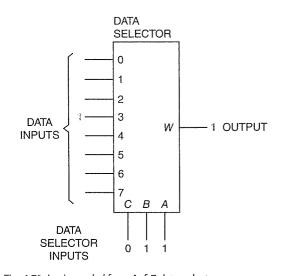


Fig. 4-31 Logic symbol for a 1-of-8 data selector.

In like manner the data from data input 3 in Fig. 4-31 are being transferred to output W of the data selector. In the rotary switch you must mechanically change the switch position to transfer data from another input. In the 1-of-8 data selector in Fig. 4-31, you need only change the binary input at the data selector inputs to transfer data from another data input

Rotary switch

Data Selector

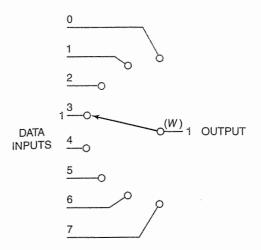


Fig. 4-32 Single-pole, eight-position rotery switch works as a data selector.

to the output. Remember that the data selector operates somewhat as a rotary switch in transferring logical 0s or 1s from a given input to the single output.

Solving Logic Problems

Now you will learn how data selectors can be used to solve logic problems. Consider the *simplified* Boolean expression shown in Fig. 4-33(a). For your convenience a logic circuit for this complicated Boolean expression is drawn in Fig. 4-33(b). Using standard ICs, we probably would have to use from six to nine IC packages to solve this problem. This would be quite expensive because of the cost of the ICs and printed circuit board space.

(a) Simplified Boolean expression

$$A \cdot B \cdot C \cdot D + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + A \cdot \overline{B} \cdot \overline{C} \cdot D + A \cdot B \cdot \overline{C} \cdot \overline{D} + \\ \overline{A} \cdot B \cdot C \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + \overline{A} \cdot \overline{B} \cdot C \cdot D = Y$$


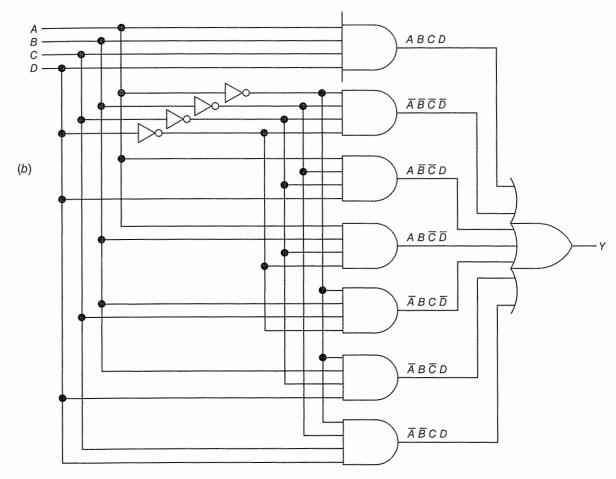


Fig. 4-33 (a) Simplified Boolean expression. (b) Logic circuit for Boolean expression.

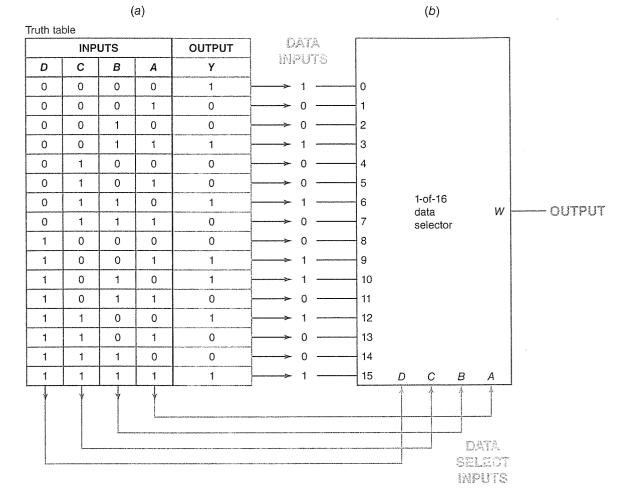

Solving logic problem with a data selector

Fig. 4-34 Solving logic problem with a data selector IC.

1-of-16 data selector

A less costly solution to the logic problem is to use a data selector. The Boolean expression from Fig. 4-33(a) is repeated in truthtable form in Fig. 4-34(a). A 1-of-16 data selector is added in Fig. 4-34(b). Notice that logical 0s and 1s are placed at the 16 data inputs of the data selector corresponding to the truth-table output column Y. These are permanently connected for this truth table. Data selector inputs (D, C, B, and A) are switched to the binary numbers on the input side of the truth table. If the data selector inputs D, C, B, and A are at binary 0000, then a logical 1 is transferred to output W of the data selector. The first line of the truth table requires that a logical 1 appear at output W when D, C, B, and A are all 0s. If data selector inputs D, C, B, and A are at binary 0001, a logical 0 appears at output W, as required by the truth table. Any combination of D, C, B, and A generates the proper output according to the truth table.

Summary

We used the data selector to solve a complicated logic problem. In Fig. 4-33 we found we needed at least six ICs to solve this logic problem. Using the data selector in Fig. 4-34, we solved this problem by using only one IC.

The data selector seems to be an easy-to-use and efficient way to solve combinational logic problems. Commonly available data selectors can solve logic problems with three, four, or five variables. When using manufacturers' data manuals, you will notice that data selectors are also called *multiplexers*.

Multiplexers



Self-Test

Supply the missing word, letter, or number in each statement.

- 41. Figure 4-31 illustrates the logic symbol for a 1-of-8 _____.
- 42. Refer to Fig. 4-31. If all data select inputs are HIGH, data at input _____ (number) are selected and transferred to output _____ (letter) of the data selector.
- 43. The action of a data selector is often compared to that of a mechanical _____switch.
- 44. Refer to Fig. 4-34. If all data select inputs are HIGH, data from input _____ (number) will be transferred to output *W*.

- Under these conditions, output *W* will be _____(HIGH, LOW).
- 45. Data selector ICs might also be listed in catalogs as _____(counters, multiplexers) suggesting another use of these devices.
- 46. Refer to Fig. 4-35(a). Write the minterm Boolean expression that describes this truth table. *Note:* This Boolean expression cannot be simplified.
- 47. Refer to Fig.4-35(*b*). Redraw the 1-of-16 data selector with the proper data inputs that solve the logic problem described in the truth table.

(a)

Truth table

	INP	OUTPUT		
Α	A B		D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1 1 0		1	0
1	1 1 1		0	0
1 1		1	1	1

(b)

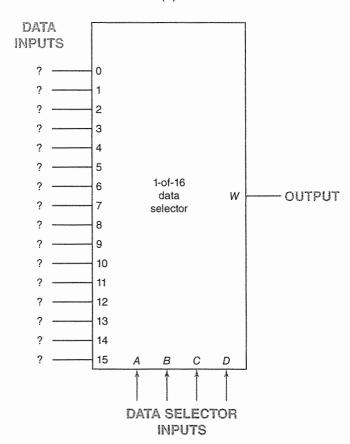


Fig. 4-35 Logic problem with a data selector IC.



4-14 Programmable Logic Devices (PLDs)

Programmable logic device (PLD)

A programmable logic device (PLD) is an IC that can be programmed by the user to execute a complex logic function. Simple PLDs are used to implement combinational logic. Other more complex PLDs have memory characteristics (registers) and can be used in the design of sequential logic circuits (such as counters). The PLD is a one-package solution to many logic problems. The PLD has many inputs and multiple outputs. The PLD can implement minterm (sum-of-products) Boolean expressions using AND-OR logic.

The term *PLD* is the common name for devices that may have proprietary names and acronyms. For instance, PLD might refer to specific devices such as:

PAL for programmable array logic
GAL for generic array logic
ELPD for electrically programmable devices
IFL for integrated fuse logic
FPL for fuse-programmable logic
PLA for programmable logic arrays
PEEL for programmable electrically
erasable logic
FPGA for field-programmable gate arrays
CPLD for complex programmable logic
device
SRAM FPGA or static RAM fieldprogrammable gate array

PLD is the most generic term for a group of programmable logic devices used to implement digital logic. However, PLD is commonly associated with simpler devices such as PALs and GALs. More complex designs can be implemented using *field-programmable logic arrays* (FPLAs). Three major catagories of FPLAs are complex programmable logic devices (CPLDs), static RAM field-programmable gate arrays (SRAM FPGAs), and antifuse FPGAs. PLDs are limited to hundreds of gates while FPGAs contain thousands of logic gates. If your instructor has you program PLDs in class, the PLDs will probably be either PALs or GALs.

Advantages of PLDs

Using PLDs cuts costs because fewer ICs are used to implement a logic circuit. Software

development tools are available from the manufacturers of the ICs for programming your design in the PLD. Development software makes it easy to make changes in the logic design. Other advantages of PLDs are the lower cost of inventory because they are somewhat generic logic devices. Upgrades and modifications are more easily made in prototypes and products using programmable logic devices. The PLD is a very reliable component. Proprietary logic designs can be more easily hidden from competitors. PLDs are inexpensive because they are available from many sources and are manufactured in large quantities. For instance, a recent catalog lists the cost of a simple PAL at less than one dollar even when ordered in small quantities.

Programming PLDs

The PLD is commonly programmed in the local development lab, school lab, or shop and not at the manufacturer. Development software is available from several manufacturers for PLDs. Some common development software used by schools might include:

- ABEL software from Lattice Semiconductor Corp.
- CUPL software from Logical Devices, Inc.

Many manufacturers allow downloading a version of their development software for temporary use by students, engineers, and designers.

A common system used in schools and small labs for programming PLDs is sketched in Fig. 4-36. The system includes a PC (personal computer), development software, an IC programmer (IC burner), and a cable to connect the IC programmer to the PC (serial cable shown).

The general steps in programming are shown in Fig. 4-36. Step 1 includes loading the development software. Step 2 would include entering the logic design as required by the development software and informing the software which device (for instance a PAL10H8 IC) you will use to implement the design. Development software will allow you to describe your logic circuit in at least three ways. They are by (1) Boolean expression (sum-of-products form), (2) truth table, or (3) logic diagram. Describing your logic circuit can also take other forms. Step 3 would have you compiling and simulating your design to check for proper operation. Step 4

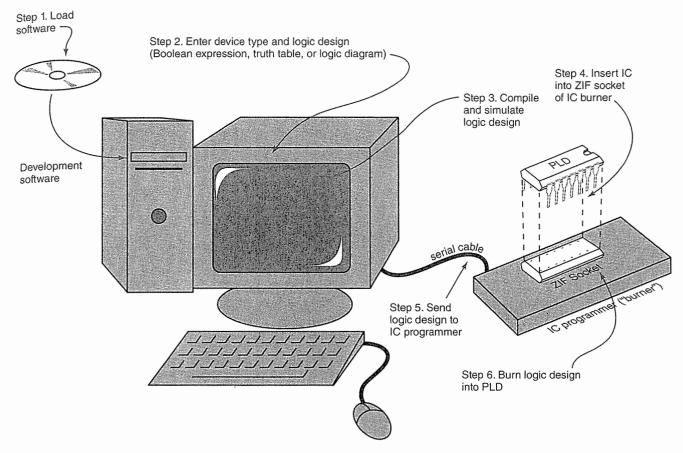


Fig. 436 Typical equipment for programming a PLD.


includes placing your PLD integrated circuit in the ZIF (zero insertion force) IC socket. Step 5 shows sending your design via the serial output cable to the IC programmer. Step 6 would be to "burn" or program the PLD IC. In summary, Fig. 4-36 shows both the hardware and the general procedure for programming a PLD.

What's Inside the PLD


A simplified version of a programmable logic device is detailed in Fig. 4-37(a). Notice that it has the look of the AND-OR circuits you worked with earlier to implement a sum-ofproduct (minterm) Boolean expression. This simple logic circuit has two inputs and one output while a typical commercial PLD may have 12 inputs and 10 outputs, as is the case for the PAL12H10 IC. The simplified PLD sketched in Fig. 4-37(a) has intact (not blown) fuses used for programming the AND gates. The OR gate is not programmable in the device. The PLD in Fig. 4-37(a) is shown as it comes from the manufacturer-with all fuses intact (not blown). The PLD in Fig. 4-37(a) needs to be programmed by burning open selected fuses.

The PLD in Fig. 4-37(b) has been programmed to implement the sum-of-products (minterm) Boolean expression $A \cdot \overline{B} + \overline{A} \cdot B =$ Y. Notice that the top four-input AND gate (gate 1) has two fusible links burned open, leaving the A and \overline{B} terms connected. Gate 1 ANDs the A and \overline{B} terms. AND gate 2 has two burnedopen fuses, leaving the \overline{A} and B inputs connected. Gate 2 ANDs the \overline{A} and B terms. AND gate 3 is not needed to implement this Boolean expression. All fuses are left intact as shown in Fig. 4-37(b), which means the output of AND gate 3 will always be a logical 0. This logical 0 will have no effect on the operation of the final OR gate. The OR gate in Fig. 4-37(b) logically ORs the $A \cdot \overline{B}$ and $\overline{A} \cdot B$ terms implementing the Boolean expression.

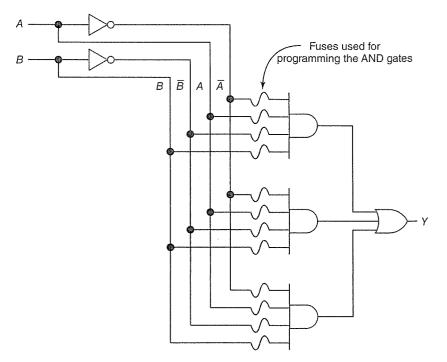In the simple example detailed in Fig. 4-37(b), the $A \cdot \overline{B} + \overline{A} \cdot B = Y$ minterm Boolean expression was implemented using a PLD. You can see from Fig. 4-37(b) that AND gate 3 was not used in this circuit and this seems wasteful. Remember that the PLD is a generic logic device that can be used to solve many problems. Sometimes parts of the



Fuses intact (as from manufacturer)

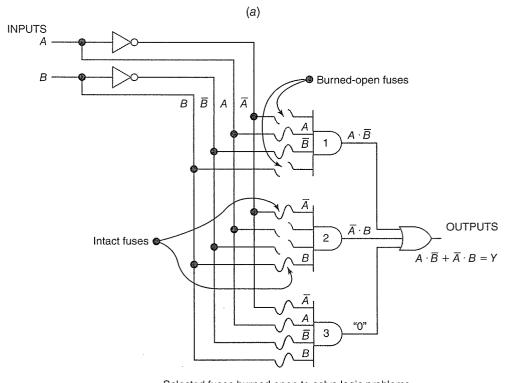

Selected fuses burned open to solve logic problems

(b)

Fig. 4-37 Simplified PLO.

logic will not be used. Recall that the IC programmer depicted in Fig. 4-36 "burns open" selected fuses. The IC programmer instrument is therefore commonly called the *PLD burner*.

The sample problem in Fig. 4-37(b) would not be solved using a PLD. Designers and engineers look to the most cost-effective method to implement electronic designs. The Boolean expression $A \cdot \overline{B} + \overline{A} \cdot B = Y$ describes the

PLD burner

two-input XOR function which might be implemented cheaper using a dedicated two-input XOR gate IC.

An abbreviated notation system used with PLDs is illustrated in Fig. 4-38. Note that all

AND and OR gates appear to have only one input, while in reality each AND gate has four inputs, and the OR gate has three inputs. The PLD represented in Fig. 4-38(a) has all fuses intact before programming. The X mark at an

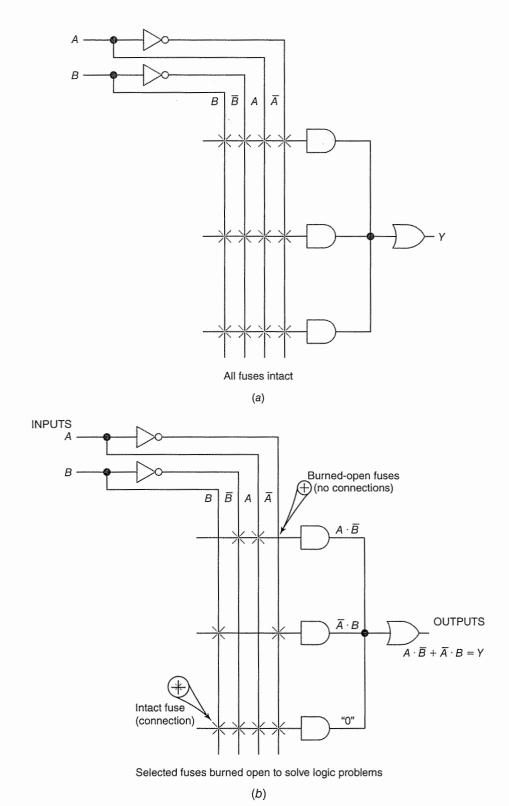


Fig. 4-38 Notation system used with PLDs.

intersection of lines represents an intact fuse when using the abbreviated notation system.

The Boolean expression $A \cdot \overline{B} + \overline{A} \cdot B = Y$ was implemented earlier in Fig. 4-37(b). The same Boolean expression is implemented in Fig. 4-38(b) but using the abbreviated notation system to describe the programming of the PLD. Notice that an X at an intersection of lines means an intact (not blown) fuse, while no X means a burned-open fuse (no connection).

The abbreviated notation system used in Fig. 4-38 is sometimes called a *fuse map*. The fuse map is a graphic or "paper-and-pencil" method of describing the programming of a PLD. In practice you would use a computer system like that in Fig. 4-36 to perform PLD programming, but the fuse maps are useful for visualizing the inside organization or architecture of the PLD. The fuse map also assists in understanding what is happening inside a PLD when it is programmed.

A more complex PLD is illustrated in Fig. 4-39. This PLD features four inputs and three outputs.

It is common for decoders to have many inputs and outputs as they translate from code to code. The PLD sketched in Fig. 4-39 is not a commercial product because it is much too simple.

Three combinational logic problems have been solved using the PLD in Fig. 4-39. First the Boolean expression $\overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot D$ $+ \overline{A} \cdot B \cdot C \cdot D = Y_1$ is implemented using the upper group of AND-OR gates. Recall that the X on the fuse map means an intact fuse while no X means a burned-open fuse. The second Boolean expression $A \cdot B \cdot C \cdot D + \overline{A} \cdot B \cdot C \cdot \overline{D} = Y_2$ is implemented using the middle group of AND-OR gates. Note that the bottom AND gate in the middle group is not needed. Therefore it has all eight fuses intact, which means it generates a logical 0 having no effect on the output of the OR gate. The third Boolean expression $\overline{A} \cdot \overline{B} \cdot C \cdot D$ + $A \cdot B \cdot C \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} = Y_3$ is implemented using the bottom group of AND-OR gates.

A more complicated PLD architecture is suggested in Fig. 4-40. This PLD provides both

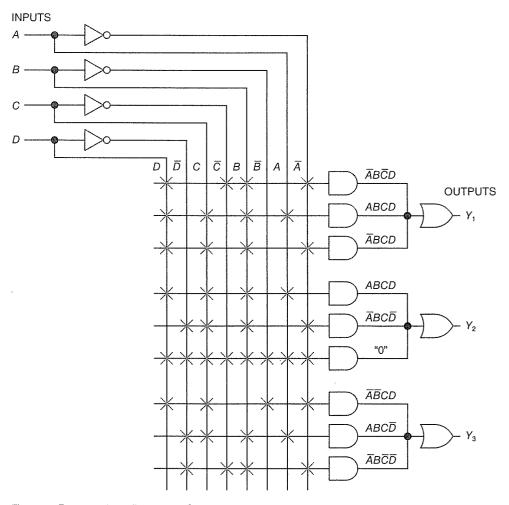


Fig. 4-39 Programming a PLD using a fuse map.

Fuse map

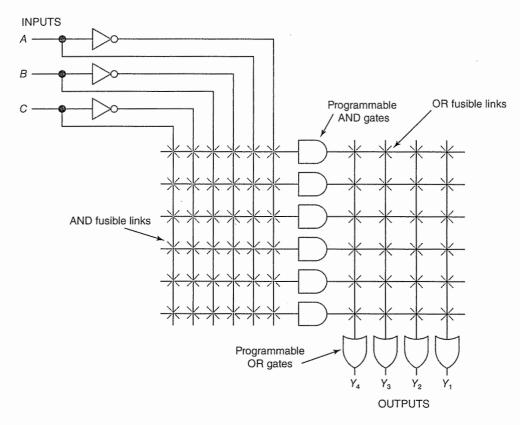


Fig. 4-40 PLD with programmable AND and OR arrays. Like an FPLA (field-programmable logic array).

programmable AND and OR arrays. The programmable logic devices studied earlier contained only programmable AND gates. This type of device is sometimes called a *field-programmable logic array (FPLA)*. Notice that all the links are intact (not burned) in this simplified example.

Practical PLDs

One catalog of ICs groups programmable logic devices first by the process technology used to manufacturer the device (such as CMOS or TTL). Second, they may be grouped as either one-time programmable or erasable. The erasable units can be either the UV (ultraviolet) light type or electrically erasable. Third, they may be grouped by whether the PLD has combinational logic or registered/latched outputs. Traditionally PLDs have been used to implement complex combinational logic designs (such as decoders). The registered PLDs contain both gates and a means of latching output data or of designing sequential logic circuits (such as counters).

The PAL10H8 is an example of a small commercial PLD (a PAL in this case). The

pin diagram in Fig. 4-41 shows a simple view of the PAL10H8 programmable logic device housed in a 20-pin DIP IC. The PAL10H8 has

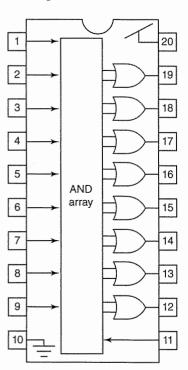


Fig. 4-41 PAL10H8 programmable logic IC with a programmable AND array.

Field-programmable logic array (FPLA)

10 inputs and 8 outputs with a programmable AND array. The OR array is not programmable in this unit and has active HIGH outputs. The PAL10H8 is also available in other IC packages.

If your school has programming equipment, you will probably use low-cost PALs with fusible links. PALs can be programmed only once. Your instructor may have you use slightly more expensive GALs which look like a PAL on the inside except the "fuses" are electronic cells (using E²CMOS technology) which can be turned on or off during programming. The GAL is useful because it can be erased and reprogrammed.

PAL/GAL IC part identification guidelines are illustrated in Fig. 4-42. The first letters on the left identify the technology family used to manufacture the PLD. The older PAL uses the TTL technology. The newer GAL uses CMOS technology. Moving right, the next number (10 in this example) is the number of inputs to the AND array. Moving right, the next letter (L in this example) identifies the type of

output (in this example the output is an active LOW). Moving right, the next number (8 in this example) is the number of outputs. Any trailing letters deal with speed/power, packaging, and the temperature range of the PLD. Some manufacturers may add to this list. Many PLDs allow output pins on the IC to be configured as either an input or output.

As an example, suppose a 20-pin DIP IC had PAL14H4 printed on its top. According to the guidelines from Fig. 4-42, this would be a PAL using TTL technology with 14 inputs and 4 outputs. It would have active HIGH outputs. Recall that a PAL can be programmed only once. Data sheets must be examined to find out more information on the IC.

A second example, suppose a 20-pin DIP IC has GAL16V8 printed on its top. According to the guidelines from Fig. 4-42, this would be a GAL using E²CMOS technology with up to 16 inputs and 8 outputs. The outputs can be configured as either inputs or outputs, and recall that GAL technology allows the E²CMOS cells to be reprogrammed.

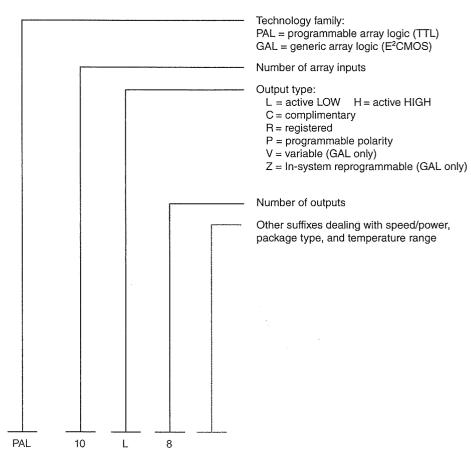


Fig. 4-42 Decoding a PAL part number.

-\\\- Self-Test

Answer the following questions.

- 48. In electronics technology, the acronym PLD stands for _____
- 49. In electronics technology, the acronym PAL stands for ______
- 50. In electronics technology, the acronym GAL stands for _____
- 51. In electronics technology, the acronym FPLA stands for _____
- 52. Programmable logic devices from the PAL family are commonly used for implementing _____ (combinational, fuzzy) logic.
- 53. FPLAs, PALs, and GALs are commonly programmed ______ (by the manufacturer, by the local user).
- 54. Programming simple PALs consists of _____(burning open selected fusible links, turning E²CMOS in the array either on or off).
- 55. The equipment needed to program PLDs includes a PC, development software, the correct PLD IC, a serial cable, and an instrument called a ______(PLD burner or programmer, logic analyzer).
- 56. The development software used for programming a PLD allows your logic design to be entered in at least three

- forms. These include a truth table, a logic symbol diagram, or a _____ (Boolean expression, Winchester table).
- 57. PLDs such as the PAL you studied are organized to implement _____ (maxterm, sum-of-products) Boolean expressions using and AND-OR pattern of logic gates.
- 58. A programmable logic device IC with a number printed on top of PAL12H6 would be based on TTL technology, have _____(6, 12) inputs, have _____(6, 12) outputs with the outputs being _____(active HIGH, active LOW).
- A programmable logic device IC with a number printed on the top of GAL16V8 would be based on ______(CMOS, TTL) technology.
- 61. Refer to Fig. 4-41. The PAL10H8 IC has a programmable _____(AND, OR) gate array and can implement sum-of-products Boolean expressions.
- 62. The PLD shown in fuse map form in Fig. 4-43 would implement what Boolean expression?

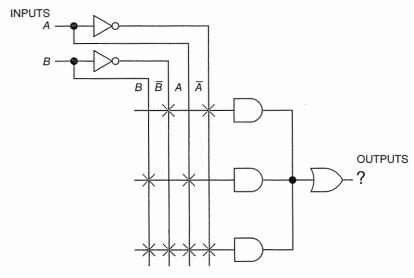


Fig. 4-43 PLD fuse map.



4-15 Using De Morgan's Theorems

Boolean algebra, the algebra of logic circuits, has many laws or theorems. *De Morgan's theorems* are very useful. They allow us to convert back and forth from minterm to maxterm forms of Boolean expressions. They also allow us to eliminate long overbars that cover several variables.

De Morgan's theorems can be stated in the form shown in Fig. 4-44. The first theorem $(\overline{A} + \overline{B} = \overline{A} \cdot \overline{B})$ shows that the long overbar covering the $\overline{A} + \overline{B}$ term can be eliminated. A simple example of the first theorem is shown in the example section [Fig. 4-44(b)] when the customary NOR logic symbol $(\overline{A} + \overline{B} = Y)$ is shown as equivalent to the alternative NOR symbol $(\overline{A} \cdot \overline{B} = Y)$.

De Morgan's second theorem is stated in Fig. 4-44(c) as $\overline{A \cdot B} = \overline{A} + \overline{B}$. A simple example of the second theorem is shown in the example section where the customary NAND logic symbol $\overline{A \cdot B}$ is shown as equivalent to the alternative NAND symbol $(\overline{A} + \overline{B} = Y)$.

Boolean Expressions: Keyboard Version

The long overbars in Boolean expressions (for example, $\overline{A \cdot B}$) are somewhat more difficult to show in the keyboard versions of an expression. For instance, the keyboard version of $\overline{A \cdot B}$ would be (AB)'. The apostrophe *outside* the parenthesis means a long overbar. Next consider the Boolean expression $\overline{A \cdot B \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{C}} = \overline{Y}$. The keyboard version of this expression would be

(a) First theorem

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

(c) Second theorem

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Fig. 4-44 De Morgan's theorems and practical examples.

((ABC') + (A'B'C'))'. The customary Boolean expression for the NOR function is $\overline{A+B}$ while the keyboard version could be typed as (A+B)'. Do not be surprised when working with some circuit simulation programs if the software converts a minterm to a maxterm or maxterm to a minterm type expression. For instance, it might convert the conventional NAND notation $(\overline{A} \cdot \overline{B})$ to alternative NAND notation (A'+B'). Computer circuit simulation programs use De Morgan's theorems to make these conversions.

Minterm to Maxterms or Maxterm to Minterms

Four steps are needed to convert a maxterm-to-minterm Boolean expression or from minterm-to-maxterm form. The four steps, which are based on De Morgan's theorems, are as follows:

Step 1. Change all ORs to ANDs and all ANDs to ORs.

Step 2. Complement each individual variable (add short overbars to each).

Step 3. Complement the entire function (add long overbar to entire function).

Step 4. Eliminate all groups of double overbars.

As an example, consider converting the customary NAND expression $(\overline{A \cdot B} = Y)$ to its alternative NAND form $(\overline{A} + \overline{B} = Y)$. Follow the four-step process in Fig. 4-45 to get familiar with the procedure. At the end of the procedure, the alternative NAND expression is shown as $\overline{A} + \overline{B} = Y$, but on the computer it would be represented as A' + B' = Y.

(b) Example—first theorem

$$A \longrightarrow A \longrightarrow Y$$

$$B \longrightarrow \overline{A + B} = Y$$

$$\overline{A \cdot B} = Y$$

$$\overline{A \cdot B} = Y$$

(d) Example—second theorem

$$A \longrightarrow A \longrightarrow A \longrightarrow Y$$

$$B \longrightarrow \overline{A \cdot B} = Y$$

$$\overline{A} + \overline{B} = Y$$

Begin. Customary NAND expression.

$$\overline{A \cdot B} = Y$$

Step 1. Change all ORs to ANDs and all ANDs to ORs.

$$\overline{A + B} = Y$$

Step 2. Complement each individual variable (short overbar).

$$\overline{\overline{A} + \overline{B}} = Y$$

Step 3. Complement the entire function (long overbar).

$$\overline{\overline{A} + B} = Y$$

Step 4. Eliminate all groups of double overbars.

$$\overline{A} + B = Y$$

End. Alternative NAND expression.

$$\overline{A} + \overline{B} = Y$$

Fig. 4-45 Four-step process using De Morgan's second theorem to convert conventional NAND to alternative NAND. Note that the long overbar is eliminated.

Now we will use the four-step procedure in converting a more complicated maxterm expression to its minterm form. Conversions from maxterm-to-minterm or minterm-to-maxterm form are commonly undertaken to get rid of long overbars in the Boolean expression. The new example illustrated in Fig. 4-46 will change the maxterm expression $(\overline{A} + \overline{B} + \overline{C})$. $(A + B + \overline{C}) = Y$ to its minterm equivalent and eliminate the long overbar. Carefully follow the conversion process in Fig. 4-46. The result of this conversion yields the minterm form $A \cdot B$. $C + \overline{A} \cdot \overline{B} \cdot C = Y$, which performs exactly the same logic function as the maxterm expression $(\overline{A} + \overline{B} + \overline{C}) \cdot (A + B + \overline{C}) = Y$. The resulting minterm expression can be written in conventional form as $A \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot C = Y$ using overbars or in the shortened keyboard version ABC + A'B'C = Y using apostrophes.

It must be understood that the logic diagrams that would be wired using the maxterm

Begin. Maxterm expression.

$$(\overline{\overline{A} + \overline{B} + \overline{C}}) \cdot (A + B + \overline{\overline{C}}) = Y$$

Step 1. Change all ORs to ANDs and all ANDs to ORs.

$$\overline{A \cdot B \cdot C} + A \cdot B \cdot \overline{C} = Y$$

Step 2. Complement each individual variable (short overbars).

$$\overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} + \overline{A} \cdot \overline{B} \cdot \overline{\overline{C}} = Y$$

Step 3. Complement the entire function (long overbar).

$$\overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} + \overline{A} \cdot \overline{B} \cdot \overline{\overline{C}} = Y$$

Step 4. Eliminate all groups of double overbars.

$$(\underbrace{\blacksquare} \underbrace{\blacksquare} \underbrace{\neg \blacksquare} \underbrace{\neg \blacksquare} \underbrace{)^{\#}}$$

$$A \cdot B \cdot C + A \cdot B \cdot C = Y$$

End. Minterm expression.

$$A \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot C = Y$$

Fig. 4-46 Four-step process using De Morgan's theorems to convert from maxterm-to-minterm form.

Note that the long overbar is eliminated.



George Boole was born in Lincoln, England, on November 2, 1815. He was a self-taught mathematician who invented modern symbolic logic and pioneered the calculus of operators. Around 1850, George Boole created Boolean algebra, which underlies the theory of logic.



History of Electronics

Augustus De Morgan (1806–1871) was born in Madras Province, India. He taught mathematics at the University of London for 30 years, and published many texts on arithmetic, algebra, trigonometry, and calculus, and important treatises on the theory of probability and formal logic. De Morgan contributed the method of changing from sum-of-products to product-of-sums.

energenaugliche



expression $(\overline{A} + \overline{B} + \overline{C}) \cdot (A + B + \overline{C}) = Y$ or its equivalent minterm form $A \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot C = Y$ from Fig. 4-46 would *look different*, but they would generate the same truth table. It is said that they generate the same logic function.

Summary

In summary, De Morgan's theorems are useful for converting from maxterm-to-minterm or minterm-to-maxterm form of Boolean expressions. We commonly make this conversion to eliminate long overbars in a Boolean expression. A second reason to use De Morgan's theorems might be to examine two different logic diagrams that perform the same logic function. One logic diagram might be simpler than the other.

-₩- Self-Test

Answer the following questions.

- 63. State two of De Morgan's theorems.
- 64. Convert the maxterm Boolean expression $(A + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C}) = Y$ to its minterm form. Show each step as is done in Fig. 4-46.
- 65. Convert the minterm Boolean expression $\overline{A} \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot \overline{C} = Y$ to its maxterm form. Show each step as is done in Fig. 4-46.
- 66. Write the Boolean expression $\overline{A \cdot B \cdot C} + \overline{A \cdot B \cdot C} = Y$ in the keyboard

- version using apostrophes instead of overbars.
- 67. Draw a logic symbol diagram for the Boolean expression (A'BC + A'B'C')' = Y. Hint: Use a two-input NOR gate nearest the output.
- 68. Draw a logic symbol diagram for the Boolean expression ((A + B + C + D)(A' + D)(A' + B' + C'))' = Y. Hint: Use three-input NAND gate nearest the output.



4-16 Solving a Logic Problem (BASIC Stamp Module)

It is common for logic functions to be programmed using software. In this section we will solve combinational logic problems using a high-level language called PBASIC (a version of BASIC used by Parallax, Inc.). The programmable hardware device used in these examples will be the BASIC Stamp 2 (BS2) Microcontroller Module by Parallax, Inc. The hardware includes the BASIC Stamp 2

module, a PC system, a serial cable (or USB cable) for downloading, and assorted electronic components (switches, resistors, and LEDs).

The truth table in Fig. 4-47(a) details the logic problem to be solved. From the truth table it appears that there are three separate combinational logic problems with outputs labeled Y1, Y2, and Y3. The schematic diagram in Fig. 4-47(b) shows three active HIGH input switches (A, B, and C) and three colored output indicators (LEDs). The programmable device

Truth table

	INPUTS		OUTPUTS				
А	В	С	Red V i	Green Y2	Yellow Y3		
0	0	0	1	1	1		
0	0	1	0	1	1		
0	1	0	0	0	1		
0	1	1	0	0	1		
1	0	0	0	0	0		
1	0	1	0	1	1		
1	1	0	0	0	0		
1	1	1	1	1	0		
(a)							

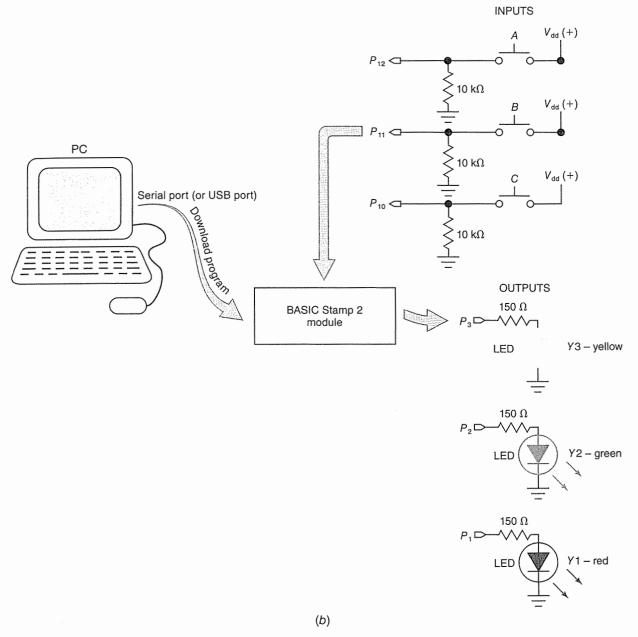


Fig. 4-47 Three-input three-output logic problem. (a) Truth table. (b) BASIC Stamp 2 module wiring diagram.

used to solve this logic problem is the BASIC Stamp 2 Microcontroller Module.

The procedure for solving the logic problem with the use of the BASIC Stamp 2 module is detailed below. The steps in wiring and programming the BASIC Stamp 2 module are:

- 1. Refer to Fig. 4-47(b). Wire the three active HIGH push-button switches and connect them to ports P10, P11, and P12. Wire the red, green, and yellow LED output indicators with limiting resistors and connect them to ports P1, P2, and P3 of the BASIC Stamp 2 module. The ports will be defined as either outputs or inputs in the PBASIC program.
- Load the PBASIC text editor program (version for the BS2 IC) into the PC. Type your PBASIC program describing the three-input, three-output logic problem. A PBASIC program titled '3in-3out logic problem is listed in Fig. 4-48.
- 3. Attach a serial cable (or USB cable) between the PC and the BASIC Stamp 2 development board (such as the Board of Education by Parallax, Inc.).
- 4. With the BASIC Stamp 2 module turned on, download your PBASIC program from the PC to BS2 module using the RUN command.
- 5. Disconnect the serial cable (or USB cable) from the BS2 module.
- 6. Test the program by pressing the input switches (*A*, *B*, and *C*) while observing the outputs (red, green, and yellow LEDs). The PBASIC program stored in EEPROM program memory in the BASIC Stamp 2 module will start each time the BS2 IC is turned on.

PBASIC Program: 3in-3out Logic Problem

Consider the PBASIC program titled '3in-3out logic problem in Fig. 4-48. Line 1 starts with an apostrophe ('), which means this is a *remark statement*. Remark statements are used to clarify the program and are not executed by the microcontroller. Lines 2–7 are lines of code to *declare variables* that will be used later in the program. As an example, line 2 reads A VAR Bit. This tells the microcontroller that A is a variable name that will hold only 1 bit (a 0 or 1).

Lines 8–13 are lines of code that *declare* which ports are used as inputs or outputs. As an example, line 9 reads **INPUT 11**. This informs the microcontroller that port 11 (*P*11) will be used as an input in this program. Another example in line 11 reads **OUTPUT 1**, which declares that port 1 will be used as an output. Notice that line 11 code is followed by a *remark statement* **'Declare port 1 as output Y1 (red LED)**. The remark statements at the right in this PBASIC program are not required, but they aid in understanding the purpose for lines of code.

Next consider the main routine with the starts with the **CkAllSwit:** line of code (line 14). In PBASIC, any word with a colon (:) after it is called a *label*. A label is a reference point in the program that usually locates the starting point of a routine.

In the '3in-3out logic problem sample program, the label CkAllSwit: is the starting point in the main routine used to check the condition of input switches A, B, and C. The Boolean expression using variables A, B, and C is then evaluated. The CkAllSwit: routine repeats continuously because either lines 29 or 38 (GOTO CkAllSwit) will always return the program to the beginning of the CkAllSwit: routine.

Lines 15–17 of the PBASIC program initializes or turns off all three output LEDs. As an example, the OUT1 = 0 statement causes port 1 (P1) of the BS2 IC to go LOW. Lines 18–20 assign the current binary value at input ports 10 (P10), 11 (P11), and 12 (P12) to variables C, B, and A. For instance, if all input switches were pressed, then all variables A, B, and C would all equal to logical 1.

Line 21 of the PBASIC program evaluates the Boolean expression $Y1 = (A\&B\&C) \mid (\sim A\&\sim B\&C)$. As an example, if all inputs are HIGH, then variable Y1 = 1 (see last line in truth table—Fig. 4-47). Line 22 is an IF-THEN statement used for making decisions. If Y1 = 1, then the PBASIC statement IF Y1 = 1 THEN Red will cause the program to jump to the Red: label or the subroutine that lights the red LED. If Y1 = 0, then the first section of PBASIC statement IF Y1 = 1 THEN Red is false. The false will cause the program to proceed to the next line of code (line 23).

The **Red:** subroutine (lines 30–32) in the PBASIC program **'3-in-3out logic problem** causes the port 1 (pin P1) of the BS2 IC to

'3in-3out logic problem	'Title of program	L1
A VAR Bit B VAR Bit C VAR Bit	'Declare A as variable, 1 bit 'Declare B as variable, 1 bit 'Declare C as variable, 1 bit	L2 L3 L4
Y1 VAR Bit	'Declare Y1 as variable, 1 bit	L4 L5
Y2 VAR Bit	'Declare Y2 as variable, 1 bit	L6
Y3 VAR Bit		L7
INPUT 10	'Declare port 10 as an input	L8
INPUT 11	'Declare port 11 as an input	L9
INPUT 12	'Declare port 12 as an input	L10
OUTPUT 1	'Declare port 1 as an output Y1 (red LED)	L11
OUTPUT 2	'Declare port 2 as output Y2 (green LED)	L12
OUTPUT 3		L13
CkAllSwit:	'Label for main routine	L14
OUT1 = 0	'Initialize port 1 at 0, red LED off	L15
OUT2 = 0	'Initialize port 2 at 0, green LED off	L16
OUT3 = 0	'Initialize port 3 at 0, yellow LED off	L17
A = IN12	'Assign value: port 12 input to variable A	L18
B = IN11	'Assign value: port 11 input to variable B	L19
C = IN10	'Assign value: port 10 input to variable C	L20
Y1 = (A&B&C) (A&B&C)	'Assign value of expression to variable Y1	L21
If $Y1 = 1$ THEN Red	'If $Y = 1$ then go to Red:, otherwise next line	L22
CkGreen:	Maria 1 - Company 1 - 4 - 111 X/O	L23
$Y2 = (-A\&-B) \mid (A\&C)$	'Assign value of expression to variable Y2	L24
If $Y2 = 1$ THEN Green	'If $Y2 = 1$ then go to Green:, or next line	L25
CkYellow:	'A seign value of augustion to reviel 1- 3/2	L26
$Y3 = (\text{-A}) \mid (\text{-B&C})$ If $Y2 = 1$ THEN Yellow	'Assign value of expression to variable Y3	L27
If Y3 = 1 THEN Yellow	'If Y3 = 1 then go to Yellow:, or next line 'Go to CkAllSwit- start main routine	L28
GOTO CkAllSwit	Go to CKAnswit- start main routine	L29
Red:	'Label for light red LED subroutine	L30
OUT1 = 1	'Output P1 goes HIGH, red LED lights	L31
GOTO CkGreen	'Go to CkGreen:	L32
Green:	'Label for light green LED subroutine	L33
OUT2 = 1	'Output P2 goes HIGH, green LED lights	L34
GOTO CkYellow	'Go to CkYellow:	L35
Yellow:	'Label for light yellow LED subroutine	L36
OUT3 = 1		L37
GOTO CkAllSwit	'Start main routine again at CkAllSwit:	L38

Fig. 4-48 Program for the 3in-3out logic problem.

go HIGH using the **OUT1** = **1** statement. This turns on and lights the red LED. Line 32 (**GOTO CkGreen**) sends the program back to the routine labeled **CkGreen**: (Lines 23–25).

After the PBASIC program is downloaded to the BASIC Stamp 2 unit, the module wired as in Fig. 4-47(*b*) will perform the logic functions detailed in the truth table [Fig. 4-47(*a*)]. You have programmed the logic functions called for in the truth table into the microcontroller module.

The PBASIC program '3-in-3out logic problem will run continuously while the BASIC Stamp 2 module is powered. The PBASIC program is held in EEPROM program memory for future use. Turning the BS2 off and then on again will restart the program. Downloading a different PBASIC program to the BASIC Stamp module will erase the old program and start execution of the new listing.

-M- Self-Test


Answer the following questions.

- 69. Refer to Fig. 4-47(b). Inputs A, B, and C are wired as ______(active HIGH, active LOW) switches, which generate a HIGH when the pushbuttons are depressed.
- 70. Refer to Fig. 4-47(*b*). If the outputs from the BASIC Stamp 2 module are P3 = HIGH, P2 = LOW, and P1 = HIGH, which LED(s) will light?
- 71. Refer to Fig. 4-47(a). The logic function in output column Y1 can be described by the Boolean expression ______
- 72. When using the BASIC Stamp 2 module, the program is typed on a PC using the PBASIC text editor and then ______ (downloaded, poured) through a serial cable to the microcontroller unit.
- 73. Refer to Figs. 4-47 and 4-48. If only pushbuttons A and C are depressed, which LEDs will light?

- 74. The program line $Y2 = (\sim A \& \sim B) \mid (A \& C)$ is the PBASIC version of what Boolean expression?
- 75. Refer to line 25 of Fig. 4-48. If variable Y2 = 0, then the next PBASIC program code executed would be _____ (line 26, line 33).
- 76. Refer to line 22 of Fig. 4-48. If variable *Y*1 = 1, then the next PBASIC program code executed would be _____ (line 23, line 30).
- 77. Refer to Figs. 4-47 and 4-48. The BASIC Stamp 2 module knows that ports *P*10, *P*11, and *P*12 are _____ (inputs, outputs) because they are declared as such in the PBASIC program listing.
- 78. Refer to the Fig. 4-48 listing. The main routine labeled **CkAllSwit:** in the PBASIC program begins with line 14 and ends with ______ (line 29, line 38) repeating over and over until power to the BASIC Stamp 2 module is turned off.




Chapter 4 Summary and Review

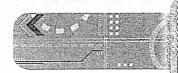

Summary

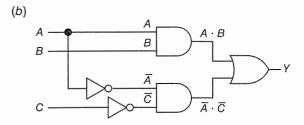- 1. Combining gates in combinational logic circuits from Boolean expressions is a necessary skill for most competent technicians and engineers.
- 2. Workers in digital electronics must have an excellent knowledge of gate symbols, truth tables, and Boolean expressions and know how to convert from one form to another.
- 3. The minterm Boolean expression (sum-of-products form) might look like the expression in Fig. 4-49(a). The Boolean expression $A \cdot B + \overline{A} \cdot \overline{C} = Y$ would be wired as shown in Fig. 4-49(b).
- 4. The pattern of gates shown in Fig. 4-49(*b*) is called an AND-OR logic circuit.
- 5. The maxterm Boolean expression (product-of-sums form) might look like the expression in Fig. 4-49(c). The Boolean expression $(A + \overline{C}) \cdot (\overline{A} + B) = Y$ would be wired as shown in Fig. 4-49(d). This is an OR-AND logic circuit.
 - (a) Minterm Boolean expression

$$A \cdot B + \overline{A} \cdot \overline{C} = Y$$



(c) Maxterm Boolean expression

$$(A + \overline{C}) \cdot (\overline{A} + B) = Y$$


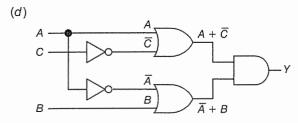


Fig. 4-49 (a) Minterm expression. (b) AND-DR logic circuit. (c) Maxterm expression. (d) DR-AND logic circuit.

- 6. A Karnaugh map is a convenient method of simplifying Boolean expressions.
- 7. AND-OR logic circuits can be wired easily by using only NAND gates, as shown in Fig. 4-50.
- 8. Data selectors are a simple, one-package method of solving many gating problems.
- 9. Computer simulations can easily and accurately convert back and forth between Boolean expressions, truth tables, and logic diagrams. The simulations can also simplify Boolean expressions.
- 10. Programmable logic devices (PLDs) are inexpensive one-package solutions to many complex logic problems. In this chapter, simple PLDs are used to solve combinational logic problems but may also be applied to sequential logic designs.
- 11. De Morgan's theorems are useful in converting maxterm-to-minterm and minterm-to-maxterm Boolean expressions.
- 12. A keyboard version of a Boolean expression is used with computer systems. An example would be $\overline{A} \cdot B = Y$ is equivalent to (A'B)' = Y.

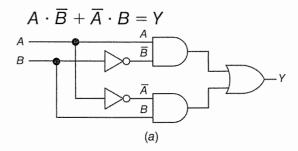

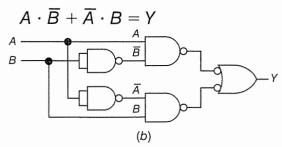


Fig. 4-50 (a) AND-OR logic circuit. (b) Equivalent NAND-NAND logic circuit.

Summary...continued

- 13. BASIC Stamp modules are microcontroller-based devices that can generate logic functions. They are programmed using Boolean expressions.

 The programs are downloaded from the PC to the BASIC Stamp module. The PC is then
- disconnected, and the BASIC Stamp module will execute the correct logic.
- 14. The traditional Boolean expression $\overline{A} \cdot \overline{B} + B \cdot C = Y$ would be coded in PBASIC as $Y = (\sim A \& \sim B) \mid (B \& C)$, and its logic function implemented by a BASIC Stamp module.

Chapter Review Questions

Answer the following questions.

- 4-1. Logic gate circuits whose outputs respond immediately (no memory characteristic) to a change at the inputs are called _____ (combinational, sequential) logic circuits.
- 4-2. Draw a logic diagram for the Boolean expression $\overline{A} \cdot \overline{B} + B \cdot C = Y$. Use one OR gate, two AND gates, and two inverters.
- 4-3. The Boolean expression $\overline{A} \cdot \overline{B} + B \cdot C = Y$ is in _____ (product-of-sums, sum-of-products) form.
- 4-4. The Boolean expression $(A + B) \cdot (C + D) = Y$ is in _____ (product-of-sums, sum-of-products) form.
- 4-5. A Boolean expression in product-of-sums form is also called a ______ expression.
- 4-6. A Boolean expression in sum-of-products form is also called a ______ expression.
- 4-7. Write the minterm Boolean expression that would describe the truth table in Fig. 4-51. Do not simplify the Boolean expression.
- 4-8. Draw a truth table (three variables) that represents the Boolean expression $\overline{C} \cdot \overline{B} + C \cdot \overline{B} \cdot A = Y$.

	OUTPUT		
С	В	A	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Fig. 4-51 Truth table.

- 4-9. The truth table in Fig. 4-52 is for an electronic lock. The lock will open only when a logical 1 appears at the output. First, write the minterm Boolean expression for the lock. Second, draw the logic circuit for the lock (use AND, OR, and NOT gates).
- 4-10. List the six steps for simplifying a Boolean expression using a Karnaugh map as discussed in Sec. 4-6.
- 4-11. Use a Karnaugh map to simplify the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C} + A \cdot \overline{B} \cdot \overline{C} = Y$. Write the simplified Boolean expression in minterm form.
- 4-12. Use a Karnaugh map to simplify the Boolean expression $A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + A \cdot \overline{B} \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot C \cdot D + A \cdot \overline{B} \cdot C \cdot D = Y$.
- 4-13. From the truth table in Fig. 4-51, do the following:
 - a. Write the unsimplified Boolean expression.
 - b. Use a Karnaugh map to simplify the Boolean expression from a.
 - c. Write the simplified minterm Boolean expression for the truth table.

	OUTPUT		
С	В	A	Υ
0	0	0	0
0	0	1	0
0	.1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Fig. 4-52 Truth table.

Chapter Review Questions...continued

- d. Draw a logic circuit from the simplified Boolean expression (use AND, OR, and NOT gates).
- e. Redraw the logic circuit from d using only NAND gates.
- 4-14. Use a Karnaugh map to simplify the Boolean expression $\overline{A} \cdot \overline{B} \cdot C \cdot D + A \cdot B \cdot \overline{C} \cdot \overline{D} + A \cdot B \cdot C \cdot \overline{D} + A \cdot \overline{B} \cdot C \cdot D = Y$. Write the answer as a minterm Boolean expression.
- 4-15. From the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot \overline{B} \cdot C \cdot D + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot \overline{D} + A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} = Y \text{ do the following:}$
 - a. Draw a truth table for the expression.
 - b. Use a Karnaugh map to simplify.
 - c. Draw a logic circuit of the simplified Boolean expression (use AND, OR, and NOT gates).
 - d. Draw a circuit to solve this problem using a 1-of-16 data selector.
- 4-16. From the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D \cdot E + \overline{A} \cdot B \cdot \overline{C} \cdot D \cdot E + A \cdot B \cdot \overline{C} \cdot D \cdot E + A \cdot \overline{B} \cdot \overline{C} \cdot D \cdot E + A \cdot B \cdot \overline{C} \cdot D \cdot \overline{E} + \overline{A} \cdot \overline{B} \cdot C \cdot D \cdot \overline{E} + \overline{A} \cdot \overline{B} \cdot C \cdot D \cdot \overline{E} + \overline{A} \cdot \overline{B} \cdot C \cdot \overline{D} \cdot \overline{E} = Y \text{ do the following:}$
 - a. Use a Karnaugh map to simplify.
 - b. Write the simplified minterm Boolean expression.
 - c. Draw a logic circuit from the simplified Boolean expression (use AND, OR, and NOT gates).
- 4-17. The Boolean algebra laws that allow us to convert from minterm-to-maxterm or maxterm-to-minterm forms of expressions are called
- 4-18. Based on De Morgan's first theorem, $\overline{A+B} =$
- 4-19. Based on De Morgan's second theorem, $\overline{\overline{A} \cdot \overline{B}} =$
- 4-20. Using De Morgan's theorems, convert the maxterm Boolean expression $(\overline{A} + \overline{B} + \overline{C})$. $(\overline{A} + \overline{B} + \overline{C}) = Y$ to its minterm form. This will remove the long overbar.
- 4-21. Using De Morgan's theorems, convert the minterm Boolean expression $\overline{A} \cdot \overline{B} \cdot C + A \cdot B \cdot C = Y$ to its maxterm form. This will remove the long overbar.
- 4-22. Write the keyboard version of the Boolean expression $A \cdot \overline{B} + \overline{A} \cdot B = Y$.

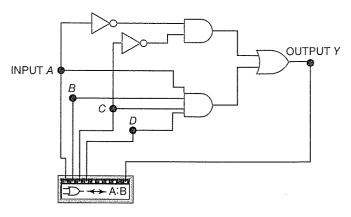


Fig. 4-53 Logic converter problem.

- 4-23. Write the keyboard version of the Boolean expression $\overline{A} \cdot \overline{B} \cdot C = Y$.
- 4-24. Write the keyboard version of the Boolean expression $(\overline{A+B})$ $(\overline{C}+D)=Y$.
- 4-25. Using the logic converter from Electronics
 Workbench or Multisim, (a) draw the logic diagram shown in Fig. 4-53 on the logic converter screen, (b) generate and write its truth table, (c) generate and write it unsimplified Boolean expression, and (d) generate and copy down its simplified Boolean expression.
- 4-26. Using the logic converter from Electronics
 Workbench or Multisim, (a) enter the truth
 table shown in Fig. 4-54 on the logic converter
 screen, (b) generate and write the simplified
 Boolean expression, and (c) generate and draw
 the AND-OR logic symbol diagram for the truth
 table.
- 4-27. Using the logic converter from Electronics Workbench or Multisim, (a) enter the Boolean expression A'C' + BC + ACD' on the logic converter screen, (b) generate and draw the four-variable truth table, and (c) generate and draw the AND-OR logic symbol diagram that is equivalent to the Boolean expression.
- 4-28. Using the logic converter from Electronics Workbench or Multisim, (a) enter the five-variable truth table shown in Fig. 4-55 on the logic converter screen, (b) generate and copy the simplified Boolean expression, and (c) generate and draw the AND-OR logic symbol diagram that is equivalent to the truth table and simplified Boolean expression.

Chapter Review Questions...continued

	INP	UTS	OUTPUT	
Α	В	С	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Fig. 4-54 Truth table.

- 4-29. In electronic technology, PAL is a common acronym for ______.
- 4-30. In electronic technology, PLD is a common acronym for ______.
- 4-31. In electronic technology, GAL is a common acronym for ______.
- 4-32. In electronic technology, FPGA is a common acronym for ______.
- 4-33. In electronic technology, CPLD is a common acronym for ______.
- 4-34. The _____ (PAL, CPLD) is the simpler programmable logic device and is usually used to implement combinational logic designs.
- 4-35. List several advantages of using PLDs to implement a logic design.
- 4-36. In the case of a PAL, to "burn" the IC means to _____ (close, open) selected fusible links in the programmable device.
- 4-37. To solve the logic problem described in the truth table in Fig. 4-56, draw a PLD fuse map like the one pictured in Fig. 4-57. An *X* at an intersection on the fuse map means an intact fusible link.

INPUTS			OUTPUT		
Α	В	С	D	Ε	Υ
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	0	1	0
1	0	1	1	0	0
1	1	1	1	1	0
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

Fig. 4-55 Truth table.

4-38. Draw a PLD fuse map like the one pictured in Fig. 4-57 that will solve the logic problem described by the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot D + A \cdot \overline{B} \cdot C \cdot \overline{D} = Y$. An X at an intersection on the fuse map means an intact fusible link.

Chapter Review Questions...continued

	INP	UTS	OUTPUT	
A	В	С	D	Υ
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Fig. 4-56 Truth table.

- 4-39. BASIC Stamp modules are _____ (microcontroller-based, vacuum tube-based) devices that can be programmed to generate logic functions.
- 4-40. Refer to Fig. 4-47(*a*). The PBASIC code (~A&~B) | (A&C) when used in an assignment statement would generate the logic for truth table output column ______ (Y1, Y2, Y3).
- 4-41. Refer to Fig. 4-47(*b*). What three BASIC Stamp 2 module ports are used as inputs in this circuit?
- 4-42. Refer to Fig. 4-47(*b*) and the PBASIC program listed in Fig. 4-48. Which lines of code define which ports are inputs and which are outputs?
- 4-43. Refer to Fig. 4-47 and the Fig. 4-48 listing. If only push-buttons *B* and *C* are activated (depressed), which LED(s) will light?

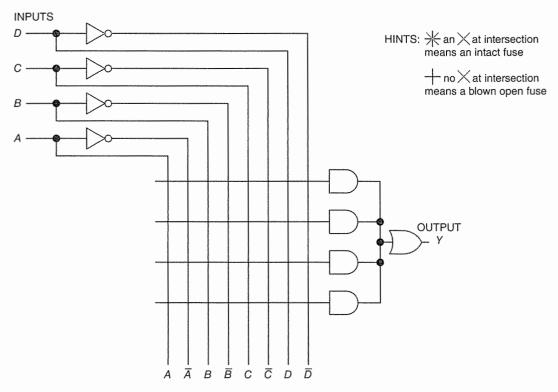


Fig. 4-57 Fuse map problem.

Critical Thinking Questions

- 4-1. When implemented, a minterm Boolean expression produces what pattern of logic gates?
- 4-2. When implemented, a maxterm Boolean expression produces what pattern of logic gates?
- 4-3. Simplify the Boolean expression $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D + \overline{A} \cdot B \cdot \overline{C} \cdot D + \overline{A} \cdot B \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + A \cdot \overline{B} \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot C \cdot D = Y.$
- 4-4. Do you think it is possible to develop a maxterm (product-of-sums) Boolean expression from a truth table?
- 4-5. Do you think the Karnaugh map shown in Fig. 4-21(*b*) can be used to simplify either minterm or maxterm Boolean expressions?
- 4-6. A six-variable truth table would have how many combinations?

- 4-7. Write the keyboard version of the Boolean expression $\overline{A} \cdot \overline{B} \cdot C + A \cdot B \cdot \overline{C} + A \cdot \overline{B} \cdot C = Y$ as you may have to do when entering information into a computer circuit simulator.
- 4-8. Write a *maxterm* Boolean expression for the logic diagram shown in Fig. 4-58.
- 4-9. Using De Morgan's theorems (or circuit simulator software if available) write the *minterm* Boolean expression that would describe the logic function of the circuit in Fig. 4-58. *Hint:* Use the maxterm expression developed in question 4-8.
- 4-10. Draw a three-variable truth table that would describe the logic function of the circuit in Fig. 4-58. *Hint:* Work from the minterm expression developed in question 4-9.


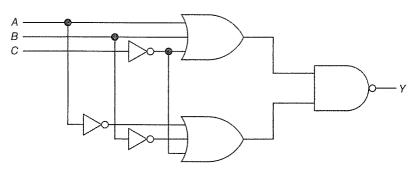



Fig. 4-58 Logic circuit

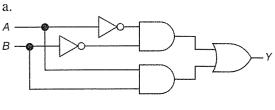


Answers to Self-Tests


1. See logic circuits a, b, and c below.




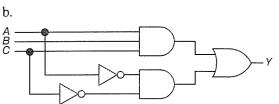


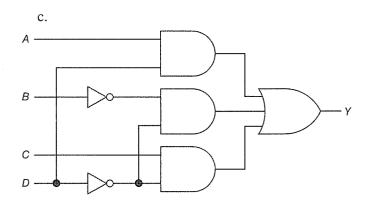

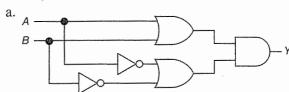- 2. sum-of-products
- 3. product-of-sums
- 4. sum-of-products
- 5. product-of-sums
- 6. See logic circuits a, b, and c below.



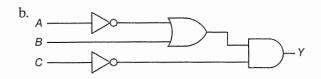

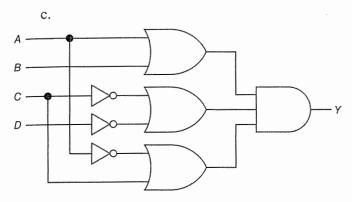


- 7. maxterm
- 8. product-of-sums
- 9. OR-AND
- 10. $C \cdot B \cdot \overline{A} + C \cdot B \cdot A = Y$
- 11. lines 0 and 1
- 12. See table below.


	OUTPUT		
С	В	A	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- 13. minterm
- 14. minterm
- 15. C'B'A + BA' = Y

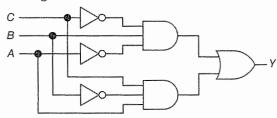- 16. T
- 17. T
- 18. F
- 19. $\overline{C} \cdot B \cdot \overline{A} + C \cdot \overline{B} \cdot A = Y$
- 20. See figure below.




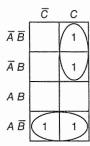- 21. identical
- 22. Boolean, Karnaugh
- 23. Quine-McCluskey or tabular method
- 24. Maurice Karnaugh
- 25. 1. Start with a minterm Boolean expression.
 - 2. Record 1s on a Karnaugh map.
 - 3. Loop adjacent 1s (loops of two, four, or eight squares).
 - 4. Simplify by dropping terms that contain a term and its complement within a loop.
 - 5. OR the remaining terms (one term per loop).
 - 6. Write the simplified minterm Boolean expression.
- 26. See a-c below.




 $d. \overline{A} \cdot C + A \cdot \overline{B} = Y$

27. See a-c below.

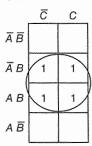


d. B = Y

28. See a-c below.

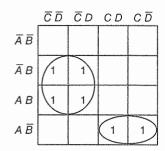


$$d. B \cdot \overline{C} + A \cdot \overline{B} \cdot C = Y$$

29. See a-c below.

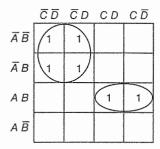


$$d. \overline{A} \cdot \overline{C} + A \cdot B \cdot C = Y$$

30. See a-c below.

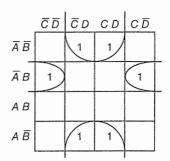


$$d. \overline{A} \cdot B \cdot \overline{D} + \overline{B} \cdot D = Y$$

31. See a-c below.

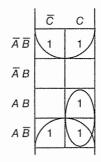

d.
$$\overline{B} + A \cdot C = Y$$

32. See a-c below.

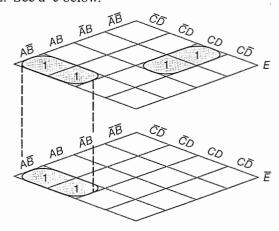


$$d. A \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot C \cdot D \cdot E = Y$$


33. AND-OR


34. identical

- 35. 1. Start with a minterm Boolean expression.
 - 2. Draw the AND-OR logic diagram using AND, OR, and NOT symbols.
 - 3. Substitute NAND symbols for each AND and OR symbol, keeping all connections the same.
 - 4. Substitute NAND symbols with all inputs tied together for each inverter.
 - 5. Test the logic circuit containing all NAND gates to determine that it generates the proper truth table.

36. a.

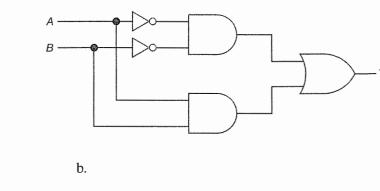

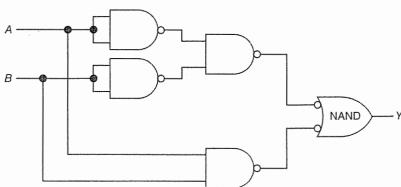

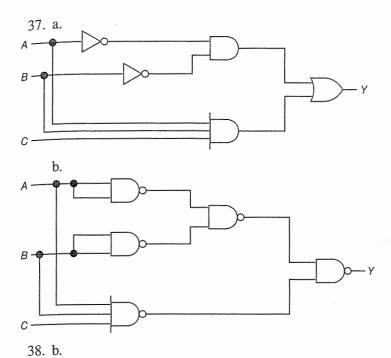

	INP	OUTPUT		
Α	В	С	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0

c. A'B'CD + ACD' + ABD

0

1

1

0

1

1

1

1


1

1


_	_		
2	n	1	L
7	7	-	1

	INP	OUTPUT		
Α	В	С	D	Υ
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

c.

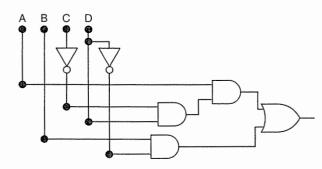

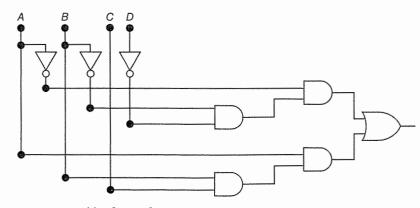
40. b. *A'B'C'D'* + *A'B'CD'* + *ABCD'* + *ABCD* c. *A'B'D'* + *ABC* d.



- 41. data selector
- 42. 7, W.
- 43. rotary
- 44. 15, HIGH

45. multiplexers

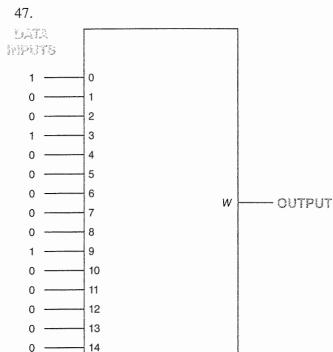46.
$$\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D} + \overline{A} \cdot \overline{B} \cdot C \cdot D + A \cdot \overline{B} \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot D = Y$$



DATA SELECT INPUTS Step 4. Eliminate double overbars.

End.
$$\overline{A} \cdot B \cdot C + A \cdot \overline{B} \cdot C = Y$$

65. Begin.
$$\overline{\overline{A} \cdot B \cdot C + \overline{A} \cdot \overline{B} \cdot \overline{C}} = Y$$

Step 1.
$$(\overline{\overline{A} + B + C}) \cdot (\overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}}) = Y$$

Step 2.
$$(\overline{\overline{A}} + \overline{B} + \overline{C}) \cdot (\overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}}) = Y$$


Step 3.
$$(\overline{\overline{A}} + \overline{B} + \overline{C}) \cdot (\overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}}) = Y$$

Step 4. Eliminate double overbars.

End.
$$(A + \overline{B} + \overline{C}) \cdot (A + B + C) = Y$$

66.
$$(A'BC + A'B'C')'$$

67.

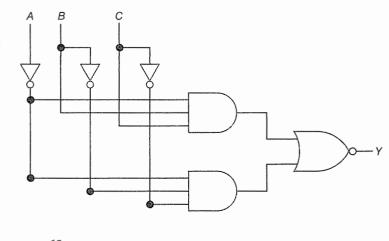

68.

- 48. programmable logic device
- 49. programmable array logic

15

- 50. generic array logic
- 51. field-programmable logic array
- 52. combinational
- 53. by the local user
- 54. burning open selected fusible links
- 55. PLD burner or programmer
- 56. Boolean expression
- 57. sum-of-products
- 58. 12, 6, active HIGH
- 59. CMOS
- 60.8
- 61. AND
- 62. $\overline{A} \cdot \overline{B} + A \cdot B = Y$
- 63. $\overline{A+B} = \overline{A} \cdot \overline{B}$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

64. Begin.
$$(\overline{A + \overline{B} + \overline{C}}) \cdot (\overline{A} + B + \overline{C}) = Y$$

Step 1.
$$(\overline{A \cdot \overline{B} \cdot \overline{C}}) + (\overline{A} \cdot B \cdot \overline{\overline{C}}) = Y$$

Step 2.
$$(\overline{A} \cdot \overline{B} \cdot \overline{C}) + (\overline{A} \cdot \overline{B} \cdot \overline{C}) = Y$$

Step 3.
$$(\overline{\overline{A}} \cdot \overline{\overline{B}} \cdot \overline{C}) + (\overline{\overline{A}} \cdot \overline{B} \cdot \overline{\overline{C}}) = Y$$

- 69. active HIGH
- 70. yellow (*Y*3), red (*Y*1)
- 71. $\overline{A} \cdot \overline{B} \cdot \overline{C} + A \cdot B \cdot C = Y$
- 72. downloaded
- 73. green (Y2) and yellow (Y3)
- 74. $\overline{A} \cdot \overline{B} + A \cdot C = Y$
- 75. line 26
- 76. line 30
- 77. inputs
- 78. line 29



IC Specifications and Simple Interfacing

Learning Outcomes

This chapter will help you to:

- **5-1** Determine logic levels using TTL and CMOS voltage profile diagrams.
- **5-2** Use selected TTL and CMOS IC specifications such as input and output voltages and noise margin.
- 5-3 Understand other IC specifications including drive capability, fan-in, fan-out, propagation delay, and power consumption.
- **5-4** List several safety precautions for handling and designing with CMOS ICs.
- **5-5** Recognize several simple switch interface and debouncing circuits using both TTL and CMOS ICs.
- 5-6 Analyze interfacing circuits for LEDs and incandescent lamps using both TTL and CMOS ICs.
- **5-7** Explain the basics of current sourcing and current sinking when using TTL ICs.
- **5-8** *Draw* TTL-to-CMOS and CMOS-to-TTL interface circuits.
- **5-9** Describe the operation of interface circuits for buzzers, relays, motors, and solenoids using both TTL and CMOS ICs.
- **5-10** *Analyze* interfacing circuits featuring an optoisolator.
- **5-11** Describe a servo motor, and summarize how it is controlled using pulse-width modulation (PWM).
- **5-12** List the primary characteristics and features of a stepper motor. Describe the operation of stepper motor drive circuits.
- **5-13** Characterize the operation of a Hall-effect sensor and its application in a device such as a Hall-effect switch.
- **5-14** Demonstrate the interfacing of an opencollector Hall-effect switch with TTL and CMOS ICs as well as LEDs.
- **5-15** *Troubleshoot* a simple logic circuit.
- **5-16** Demonstrate interfacing a servo motor to a BASIC Stamp 2 Microcontroller Module. Explain the actions of the servo motor when controlled by the microcontroller module.

The driving force behind the increased use of digital circuits has been the availability of a variety of logic families. Integrated circuits within a logic family are designed to interface easily with one another. For instance, in the TTL logic family you may connect an output directly into the input of several other TTL inputs with no extra parts. The designer can have confidence that ICs from the same logic family will interface properly. Interfacing between logic families and between digital ICs and the outside world is a bit more complicated. Interfacing can be defined as the design of the interconnections between circuits that shift the levels of voltage and current to make them compatible. A fundamental knowledge of simple interfacing techniques is required of technicians and engineers who work with digital circuits. Most logic circuits are of no value if they are not interfaced with "real-world" devices.

5-1 Logic Levels and Noise Margin


In any field of electronics most technicians and engineers start investigating a new device in terms of voltage, current, and resistance or impedance. In this section just the *voltage characteristics* of both TTL and CMOS ICs will be studied.

Logic Levels: TTL

How is a logical 0 (LOW) or logical 1 (HIGH) defined? Figure 5-1 shows an inverter (such as the 7404 IC) from the bipolar TTL logic family. Manufacturers specify that for correct operation, a LOW *input* must range from GND to 0.8 V. Also, a HIGH *input* must be in the range from 2.0 to 5.5 V. The unshaded section from

Logic families: TTL and CMOS

Interfacing

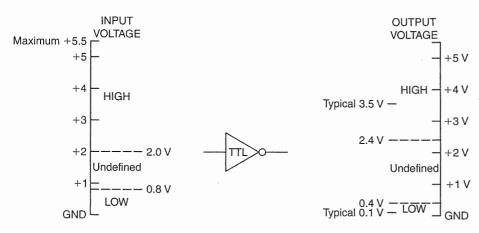

TTL valtage profile

Fig. 5-1 Defining TTL input and output voltage levels.

0.8 to 2.0 V on the input side is the undefined area, or indeterminate region. Therefore, an input of 3.2 is a HIGH input. An input of 0.5 V is considered a LOW input. An input of 1.6 V is in the undefined region and should be avoided. Inputs in the undefined region yield unpredictable results at the output.

Expected outputs from the TTL inverter are shown on the right in Fig. 5-1. A typical LOW output is about 0.1 V. A typical HIGH output might be about 3.5 V. However, a HIGH output could be as low as 2.4 V according to the voltage profile diagram in Fig. 5-1. The HIGH output depends on the resistance value of the load placed at the output. The greater the load current, the lower the HIGH output voltage. The unshaded section on the output voltage side in Fig. 5-1 is the undefined region. Suspect trouble if the output voltage is in the undefined region (0.4 to 2.4 V).

The voltages given for LOW and HIGH logic levels in Fig. 5-1 are for a TTL device. These voltages are different for other logic families.

Internet Connection

Find data sheets for ICs at www.onsemi.com or www.ti.com.

Logic Levels: CMOS

The 4000 and 74C00 series CMOS logic families of ICs operate on a wide range of power supply voltages (from +3 to +15 V). The definition of a HIGH and LOW logic level for a typical CMOS inverter is illustrated in Fig. 5-2(a). A 10-V power supply is being used in this voltage profile diagram.

The CMOS inverter shown in Fig. 5-2(a) will respond to any input voltage within 70–100 percent of V_{DD} (+10 V in this example) as a HIGH. Likewise, any voltage within 0 to 30 percent of V_{DD} is regarded as a LOW input to ICs in the 4000 and 74C00 series.

Typical output voltages for CMOS ICs are shown in Fig. 5-2(a). Output voltages are normally almost at the *voltage rails* of the power supply. In this example, a HIGH output would be about +10 V, while a LOW output would be about 0 V or GND.

The 74HC00 series and the newer 74AC00 and 74ACQ00 series operate on a lower voltage power supply (from +2 to +6 V) than the older 4000 and 74C00 series CMOS ICs. The input and output voltage characteristics are summarized in the voltage profile diagram in Fig. 5-2(b). The definition of HIGH and LOW for both input and output on the 74HC00, 74AC00, and 74ACQ00 series is approximately the same as for the 4000 and 74C00 series CMOS ICs. This can be seen in a comparison of the two voltage profiles in Fig. 5-2(a) and (b).

The 74HCT00 series and newer 74ACT00, 74ACTQ00, 74FCT00, and 74FCTA00 series of CMOS ICs are designed to operate on a 5-V power supply like TTL ICs. The function of the 74HCT00, 74ACT00, 74ACTQ00, 74FCT00, and 74FCTA00 series of ICs is to interface between TTL and CMOS devices. These CMOS ICs with a "T" designator can serve as direct replacements for many TTL ICs.

A voltage profile diagram for the 74HCT00, 74ACT00, 74ACTQ00, 74FCT00, and 74FCTA00 series CMOS ICs is drawn in Fig. 5-2(c). Notice that the definition of LOW and HIGH at the *input* is the same for these "T" CMOS ICs as it is for regular bipolar TTL ICs. This can be seen in a comparison of the input side of the voltage profiles of TTL and the "T" CMOS ICs [see Figs. 5-1 and 5-2(c)]. The output voltage profiles for all the CMOS ICs are

142

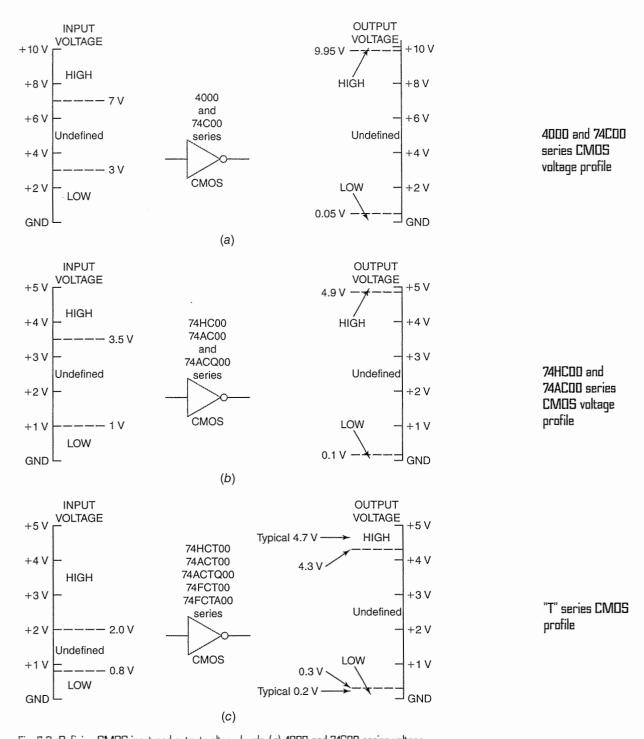


Fig. 5-2 Defining CMOS input and output voltage levels. (a) 4000 and 74000 series voltage profile. (b) 74HC00, 74AC00, and 74ACQ00 series voltage profile. (c) 74HCT00, 74ACT00, 74FCT00, 74FCTA00 series voltage profile.

similar. In summary, the "T" series CMOS ICs have typical TTL input voltage characteristics with CMOS outputs.

Logic Levels: Low-Voltage CMOS

As digital circuits become smaller it is useful to use power supply voltages that are lower than the common +5 V. The definition of HIGH and LOW logic levels for a typical *low-voltage CMOS* IC is detailed in Fig. 5-3.

Two modern low-voltage CMOS families are the 74ALVC00 series (advanced low-voltage CMOS) and the 74LVX00 series (low-voltage CMOS with 5-V tolerant inputs). The 74LVX00

Low-Voltage CMOS


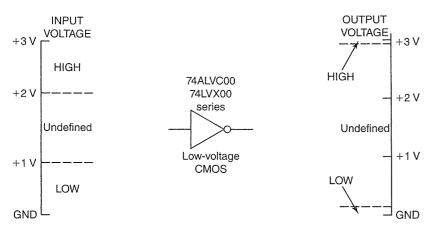


Fig. 5-3 Defining low-voltage CMOS input and output voltage levels.

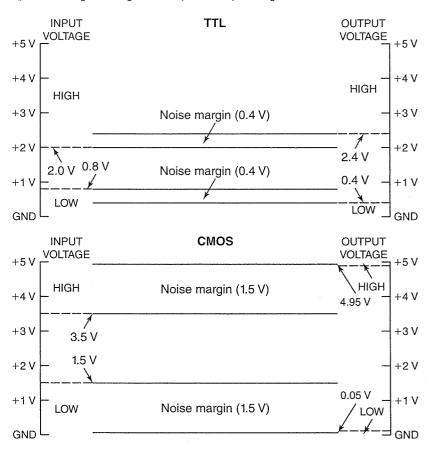

Comparing TTL and CMOS noise margins

Fig. 5-4 Defining and comparing TTL and CMOS noise margins.

Noise immunity

Advantages of

CMOS

Noise margin

gested in Fig. 5-3 without harm.

As detailed in the voltage profile diagram in Fig. 5-3, input voltages above +2 V are considered HIGH, while input voltages below +0.8 V are in the LOW range. The output voltages from

ICs can tolerate higher input voltage than sug-

these low-voltage CMOS ICs would be near the voltage rails of +3 V and GND.

Many low-voltage CMOS ICs can operate on supply voltages as low as about +1.7 V. The voltage profile would look about like that in

Fig. 5-3, but the scaling on the left edge of the profile would be different.

Noise Margin

The most often cited *advantages of CMOS* are its low power requirements and good noise immunity. *Noise immunity* is a circuit's insensitivity or resistance to undesired voltages or noise. It is also called *noise margin* in digital circuits.

The noise margins for typical TTL and CMOS families are compared in Fig. 5-4. The

noise margin is much better for the CMOS than for the TTL family. You may introduce almost 1.5 V of unwanted noise into the CMOS input before getting unpredictable results.

Noise in a digital system is *unwanted voltages* induced in the connecting wires and printed circuit board traces that might affect the input logic levels, thereby causing faulty output indications.

Consider the diagram in Fig. 5-5. The LOW, HIGH, and undefined regions are defined for TTL inputs. If the actual input voltage is 0.2 V, then the margin of safety between it and the undefined region is 0.6 V (0.8 - 0.2 = 0.6 V). This is the *noise margin*. In other words, it would take more than +0.6 V added to the LOW voltage (0.2 V in this example) to move the input into the undefined region.

In actual practice, the noise margin is even greater because the voltage must increase to the *switching threshold*, which is shown as 1.2 V in Fig. 5-5. With the actual LOW input at +0.2 V and the switching threshold at about +1.2 V, the actual noise margin is 1 V (1.2 - 0.2 = 1 V).

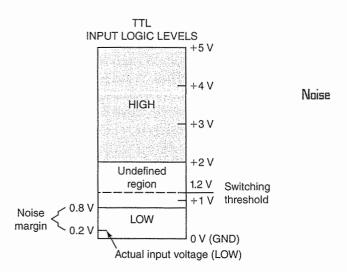


Fig. 5-5 TTL input logic levels showing noise margin.

The switching threshold is *not* an absolute voltage. It does occur within the undefined region but varies widely because of manufacturer, temperature, and the quality of the components. However, the logic levels are guaranteed by the manufacturer.

Switching threshold



Self-Test

Supply the missing word in each statement.

- 1. The design of interconnections between two circuits to make them compatible is called ______.
- 2. An input of +3.1 V to a TTL IC would be considered _____ (HIGH, LOW, undefined).
- 3. An input of +0.5 V to a TTL IC would be considered _____ (HIGH, LOW, undefined).
- 4. An output of +2.0 V from a TTL IC would be considered _____ (HIGH, LOW, undefined).
- 5. An input of +6 V (10-V power supply) to a 4000 series CMOS IC would be considered ______ (HIGH, LOW, undefined).
- 6. A typical HIGH output (10-V power supply) from a CMOS IC would be about ______ V.
- 7. An input of +4 V (5-V power supply) to a 74HCT00 series CMOS IC would

- be considered _____ (HIGH, LOW, undefined).
- 8. The _____ (CMOS, TTL) family of ICs has better noise immunity.
- The switching threshold of a digital IC is the *input* voltage at which the output logic level switches from HIGH to LOW or LOW to HIGH. (T or F)
- 10. The 74FCT00 series of ______ (CMOS, TTL) ICs has an input voltage profile that looks like that of a TTL IC.
- 11. Refer to Fig. 5-3. The 74ALVC00 series ICs would be referred to as _____ (high-impedance, low-voltage) CMOS chips because it can operate on a +3-V power source.
- Refer to Fig. 5-3. An input of +2.5 V to a 74ALVC00 series IC would be considered a(n) ______ (HIGH, LOW, undefined) logic level.



Fan-out

5-2 Other Digital IC Specifications

Digital logic voltage levels and noise margins were studied in the last section. In this section, other important specifications of digital ICs will be introduced. These include drive capabilities, fan-out and fan-in, propagation delay, and power dissipation.


Drive Capabilities

Drive capabilities

A bipolar transistor has its maximum wattage and collector current ratings. These ratings determine its *drive capabilities*. One indication of output drive capability of a digital IC is called its

fan-out. The *fan-out* of a digital IC is the number of "standard" inputs that can be driven by the gate's output. If the fan-out for standard TTL gates is 10, this means that the output of a single gate can drive up to 10 inputs of the gates *in the same subfamily*. A typical fan-out value for standard TTL ICs is 10. The fan-out for low-power Schottky TTL (LS-TTL) is 20 and for the 4000 series CMOS it is considered to be about 50.

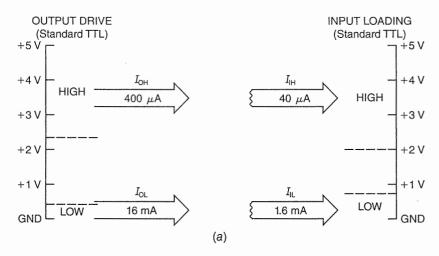Another way to look at the current characteristics of gates is to examine their output drive and input loading parameters. The diagram in Fig. 5-6(a) is a simplified view of the output



	Device Family	Output Drive*	Input Loading
	Standard TTL	$I_{\rm OH} = 400 \ \mu {\rm A}$ $I_{\rm OL} = 16 \ {\rm mA}$	$I_{ m IH}=40~\mu{ m A}$ $I_{ m IL}=1.6~{ m mA}$
Ę	Low-Power Schottky	$I_{\rm OH} = 400 \; \mu {\rm A}$ $I_{\rm OL} = 8 \; {\rm mA}$	$I_{IH} = 20 \mu A$ $I_{IL} = 400 \mu A$
F	Advanced Low-Power Schottky	$I_{\mathrm{OH}} = 400 \ \mu \mathrm{A}$ $I_{\mathrm{OL}} = 8 \ \mathrm{mA}$	$I_{\text{IH}} = 20 \mu\text{A}$ $I_{\text{IL}} = 100 \mu\text{A}$
	FAST Fairchild Advanced Schottky TTL	$I_{OH} = 1 \text{ mA}$ $I_{OL} = 20 \text{ mA}$	$I_{ m lH} = 20 \ \mu { m A}$ $I_{ m lL} = 0.6 \ { m mA}$
	4000 Series	I _{OH} = 400 μA I _{OL} = 400 μA	I _{in} = 1 μA
	74HC00 Series	$I_{OH} = 4 \text{ mA}$ $I_{OL} = 4 \text{ mA}$	$I_{in} = 1 \mu A$
CMOS	FACT Fairchild Advanced CMOS Technology Series (AC/ACT/ACQ/ACTQ)	$I_{OH} = 24 \text{ mA}$ $I_{OL} = 24 \text{ mA}$	$I_{in} = 1 \mu A$
	FACT Fairchild Advanced CMOS Technology Series (FCT/FCTA)	$I_{ m OH}=$ 15 mA $I_{ m OL}=$ 64 mA	$I_{in} = 1 \mu A$

^{*}Buffers and drivers may have more output drive.

(b)

Fig. 3-6 (a) Standard TTL voltage and current profiles. (b) Output drive and input loading characteristics for selected TTL and CMOS logic families.

drive capabilities and input load characteristics of a standard TTL gate. A standard TTL gate is capable of handling 16 mA when the output is LOW $(I_{\rm OL})$ and 400 μ A when the output is HIGH $(I_{\rm OH})$. This seems like a mismatch until you examine the input loading profile for a standard TTL gate. The input loading (worst-case conditions) is only 40 μ A with the input HIGH $(I_{\rm IH})$ and 1.6 mA when the input is LOW $(I_{\rm IL})$. This means that the output of a standard TTL gate can drive 10 inputs (16 mA/1.6 mA = 10). Remember, these are worst-case conditions, and in actual bench tests under static conditions these input load currents are much less than specified.


A summary of the *output drive* and *input loading* characteristics of several families of digital ICs is detailed in Fig. 5-6(b). Look over this chart of very useful information. You will

need these data later when interfacing TTL and CMOS ICs.

Notice the outstanding output drive capabilities of the FACT series of CMOS ICs [see Fig. 5-6(b)]. The superior drive capabilities, low power consumption, excellent speed, and great noise immunity make the FACT series of CMOS ICs one of the preferred logic families for new designs. The newer FAST TTL logic series also has many desirable characteristics that make it suitable for new designs.

The load represented by a single gate is called the *fan-in* of that family of ICs. The input loading column in Fig. 5-6(b) can be thought of as the fan-in of these IC families. Notice that the fan-in or input loading characteristics are different for each family of ICs.

Suppose you are given the interfacing problem in Fig. 5-7(a). You are asked if the 74LS04 Fan-in

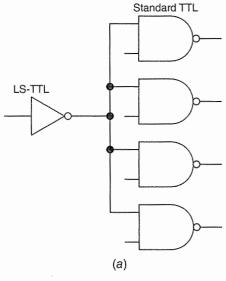

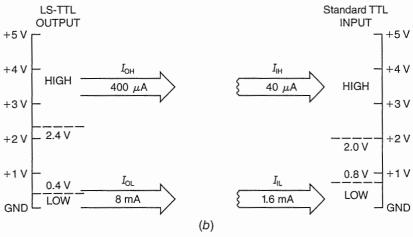


Fig. S-7 Interfacing LS-TTL to standard TTL problem. (a) Logic diagram of interfacing problem.
(b) Voltage and current profiles for visualizing the solution to the problem.



Propagation delay

inverter has enough fan-out to drive the four standard TTL NAND gates on the right.

The voltage and current profiles for LS-TTL and standard TTL gates are sketched in Fig. 5-7(b). The voltage characteristics of all TTL families are compatible. The LS-TTL gate can drive 10 standard TTL gates when its output is HIGH (400 μ A/40 μ A = 10). However, the LS-TTL gate can drive only five standard TTL gates when it is LOW (8 mA/1.6 mA = 5). We could say that the fan-out of LS-TTL gates is only 5 when driving standard TTL gates. It is true that the LS-TTL inverter can drive four standard TTL inputs in Fig. 5-7(a).

Propagation Delay

Speed, or quickness of response to a change at the inputs, is an important consideration in high-speed applications of digital ICs. Consider the waveforms in Fig. 5-8(a). The top waveform shows the input to an inverter going from LOW to HIGH and then from HIGH to

LOW. The bottom waveform shows the output response to the changes at the input. The slight delay between the time the input changes and the time the output changes is called the *propagation delay* of the inverter. Propagation delay is measured in seconds. The propagation delay for the LOW-to-HIGH transition of the input to the inverter is different from the HIGH-to-LOW delay. Propagation delays are shown in Fig. 5-8(a) for a standard TTL 7404 inverter IC.


The typical propagation delay for a standard TTL inverter (such as the 7404 IC) is about 12 ns for the LOW-to-HIGH change while only 7 ns for the HIGH-to-LOW transition of the input.


Representative minimum propagation delays are summarized on the graph in Fig. 5-8(b). The lower the propagation delay specification for an IC, the higher the speed. Notice that the AS-TTL (advanced Schottky TTL) and AC-CMOS are the fastest with minimum propagation delays of about 1 ns for a simple inverter. The



Internet Connection

Visit www.fairchildse miconductor.com.

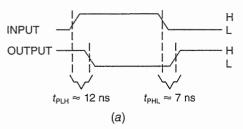

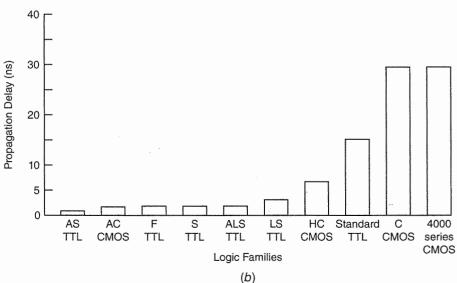

Propagation delays

Fig. 5-B (a) Waveforms showing propagation delays for a standard TTL inverter.
(b) Graph of propagation delays for selected TTL and CMOS families.

older 4000 and 74C00 series CMOS families are the slowest families (highest propagation delays). Some 4000 series ICs have propagation delays of over 100 ns. In the past, TTL ICs were considered faster than those manufactured using the CMOS technology. Currently, however, the FACT CMOS series rival the best TTL ICs in low propagation delays (high speed). For extremely high-speed operation, the ECL (emitter-coupled logic) and the developing gallium arsenide families are required.

Power Dissipation

Generally, as propagation delays decrease (increased speed), the power consumption and related heat generation increase. Historically, a standard TTL IC might have a propagation delay of about 10 ns compared with a propagation delay of about 30 to 50 ns for a 4000 series CMOS IC. The 4000 CMOS IC, however, would consume only 0.001 mW, while the standard TTL gate might consume 10 mW of power. The power dissipation of CMOS increases with frequency. So at 100 kHz, the 4000 series gate may consume 0.1 mW of power.

The speed versus power graph in Fig. 5-9 compares several of the TTL and CMOS families. The vertical axis on the graph represents the propagation delay (speed) in nanoseconds, while the horizontal axis depicts the power consumption (in milliwatts) of each

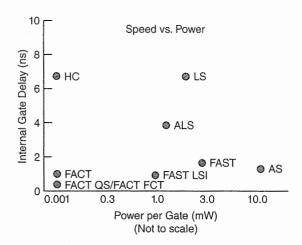


Fig. 5-9 Speed versus power for selected TTL and CMOS families. (Courtesy of National Semiconductor Corporation.)

FACT series CMOS ICs Emitter-coupled logic (ECL)

Power dissipation

Speed versus power chart

gate. Families with the most desirable combination of both speed and power are those near the lower left corner of the graph. A few years ago many designers suggested that the ALS (advanced low-power Schottky TTL) family was the best compromise between speed and power dissipation. With the introduction of new families, it appears that the FACT (Fairchild advanced CMOS technology) series is now one of the best compromise logic families. Both the ALS and the FAST (Fairchild advanced Schottky TTL) families are also excellent choices.

-M- Self-Test

Supply the missing word in each statement.

- 13. The number of "standard" input loads that can be driven by an IC is called its _____ (fan-in, fan-out).
- 14. The _____ (4000 series CMOS, FAST TTL series) gates have more output drive capabilities.
- 15. Refer to Fig. 5-6(b). The calculated fanout when interfacing LS-TTL to LS-TTL
- 16. The 4000 series CMOS gates have very low power dissipation, good noise immunity, and ______ (long, short) propagation delays.
- 17. Refer to Fig. 5-8(*b*). The fastest CMOS subfamily is _____.



IC manufacturers
refer to RoHS. RoHS
stands for what?



Cautions when using CMOS

Conductive foam

PMOS NMOS

Complementary symmetry metal-oxide semiconductor ICs

5-3 MOS and CMOS ICs

MOS ICs

The enhancement type of metal-oxide semiconductor field-effect transistor (MOSFET) forms the primary component in MOS ICs. Because of their simplicity, MOS devices use less space on a silicon chip. Therefore, more functions per chip are typical in MOS devices than in bipolar ICs (such as TTL). Metal-oxide semiconductor technology is widely used in large-scale integration (LSI) and very large-scale integration (VLSI) devices because of this packing density on the chip. Microprocessors, memory, and clock chips are typically fabricated using MOS technology. Metal-oxide semiconductor circuits are typically of either the PMOS (P-channel MOS) or the newer, faster NMOS (N-channel MOS) type. Metal-oxide semiconductor chips are smaller, consume less power, and have a better noise margin and higher fan-out than bipolar ICs. The main disadvantage of MOS devices is their relative lack of speed.

CMOS ICs

Complementary symmetry metal-oxide semi-conductor (CMOS) devices use both P-channel and N-channel MOS devices connected end to end. Complementary symmetry metal-oxide semiconductor ICs are noted for their exceptionally low power consumption. The CMOS family of ICs also has the advantages of low cost, simplicity of design, low heat dissipation, good fan-out, wide logic swings, and good noise-margin performance. Most CMOS families of digital ICs operate on a wide range of voltages. Some low-voltage CMOS ICs operate on power supplies as low as +1.7 V.

Historically, the main disadvantage of many CMOS ICs was that they were slower than bipolar digital ICs such as TTL devices. In more recent times, CMOS families such as 74AC00 and 74ALVC00 series feature very low propagation delays (perhaps 2 to 5 ns) for use in high-speed digital circuits. For comparison, older 7400 series logic circuits may have propagation delays of about 6 ns. Extra care must be taken when handling CMOS ICs because they must be protected from static discharges. A static charge or transient voltage in a circuit can damage the very thin silicon dioxide layers inside the CMOS chip. The silicon dioxide layer acts like the dielectric in a capacitor and can be punctured by static discharge and transient voltages.

If you do work with CMOS ICs, manufacturers suggest preventing damage from static discharge and transient voltages by:

- 1. Storing CMOS ICs in special *conductive* foam or static shielding bags or containers
- 2. Using battery-powered soldering irons when working on CMOS chips or grounding the tips of ac-operated units
- 3. Changing connections or removing CMOS ICs only when the power is enturned off
- 4. Ensuring that input signals do not exceed power supply voltages
- 5. Always turning off input signals before circuit power is turned off
- 6. Connecting all unused input leads to either the positive supply voltage or GND, whichever is appropriate (only unused CMOS outputs may be left unconnected)

FACT CMOS ICs are much more tolerant of static discharge.

The extremely low power consumption of CMOS ICs makes them ideal for battery-operated portable devices. Complementary symmetry metal-oxide semiconductor ICs are widely used in a variety of portable devices.

A typical CMOS device is shown in Fig. 5-10. The top half is a P-channel MOSFET, while the bottom half is an N-channel MOSFET. Both are enhancement-mode MOSFETs. When the input voltage (V_{in}) is LOW, the top MOSFET is on and the bottom unit is off. The output voltage (V_{out}) is then HIGH. However, if V_{in} is HIGH, the bottom device is on and the top MOSFET is off. Therefore, V_{out} is LOW. The device in Fig. 5-10 acts as an inverter.

Notice in Fig. 5-10 that the V_{DD} of the CMOS unit goes to the positive supply voltage. The V_{DD} lead is labeled V_{CG} (as in TTL) by many manufacturers.

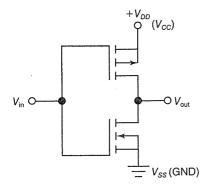


Fig. **5-10** CMOS structure using P-channel and N-channel MOSFETs in series.

CMOS structure

The "D" in V_{DD} stands for the *drain* supply in MOSFET. The V_{SS} lead of the CMOS unit is connected to the negative of the power supply. This connection is called GND (as in TTL) by some manufacturers. The "S" in V_{SS} stands for *source* supply in a MOSFET. CMOS ICs typically operate on 3-, 5-, 6-, 9-, or 12-V power supplies.

The CMOS technology is used in making several families of digital ICs. The most popular are the 4000, 74C00, 74HC00, 74ALVC00, and FACT series ICs. The 4000 series is the oldest. This family has all the customary logic functions plus a few devices that have no equivalent in TTL families. For instance, in CMOS it is possible to produce transmission gates or bilateral switches. These gates can conduct or allow a signal to pass in either direction like relay contacts.

The 74C00 series is an older CMOS logic family that is the pin-for-pin, function-for-function equivalent of the 7400 series of TTL ICs. As an example, a 7400 TTL IC is designated as a quadruple ("quad") two-input NAND gate as is the 74C00 CMOS ICs.

The 74HC00 series CMOS logic family is designed to replace the 74C00 series and many 4000 series ICs. It has pin-for-pin, function-for-function equivalents for both 7400 and 4000 series ICs. It is a high-speed CMOS family with good drive capabilities. It operates on a 2- to 6-V power supply.

The FACT (Fairchild advanced CMOS technology) logic IC series includes the 74AC00, 74ACQ00, 74ACT00, 74ACTQ00, 74FCT00, and 74FCTA00 subfamilies. The FACT family provides pin-for-pin, function-for-function equivalents for 7400 TTL ICs. The FACT series was designed to outperform existing CMOS and most bipolar logic families. It features low power consumption even at modest frequencies (0.1 mW/gate at 1 MHz). Power consumption does however increase at higher frequencies (>50 mW at 40 MHz). It has outstanding noise immunity, with the "Q" devices having patented noise-suppression circuitry. The "T" devices have TTL voltage level inputs. The propagation delays for the FACT series are outstanding [see Fig. 5-8(b)]. FACT ICs show excellent resistance to static electricity. The series is also radiation-tolerant making it good in space, medical, and military applications. The output drive capabilities of the FACT family are outstanding [see Fig. 5-6(b)].

Extremely compact digital devices may use lower-voltage power sources where $V_{CC}=3.3~{\rm V},$ $V_{CC}=2.5~{\rm V},$ or $V_{CC}=1.8~{\rm V}.$ The 74ALVC00 series of CMOS ICs may be used because of its low power consumption, 3.6-V tolerant inputs/outputs, TTL direct interface, static protection, and very high speeds (low propagation delays, about 2 to 3 ns).

FACT series CMOS ICs

4000 series

Transmission gates Bilateral switches 74C00 series

74HCOO series

-√- Self-Test

Supply the missing word in each statement.

- 19. Large-scale integration (LSI) and very large-scale integration (VLSI) devices make extensive use of ______ (bipolar, MOS) technology.
- 20. The letters CMOS stand for _____
- 21. The most important advantage of using CMOS is its _____.
- 22. The V_{ss} pin on a CMOS IC is connected to _____ (positive, GND) of the power supply.
- 23. The V_{DD} pin on a CMOS IC is connected to _____ (positive, GND) of the power supply.
- 24. The _____ (FACT, 4000) series of CMOS ICs are a good choice for new

- designs because of their low power consumption, good noise immunity, excellent drive capabilities, and outstanding speed.
- 25. The 74FCT00 would have the same logic function and pinout as the 7400 quad two-input NAND gate IC. (T or F)
- The 74ALVC00 series of ICs use
 _____ (CMOS, TTL) technology in their manufacture.
- 27. Older series of CMOS ICs (such as the 4000 series) were _____ (not, very) sensitive to static electricity.
- 28. Older series of CMOS ICs (such as the 4000 series) featured low power consumption but were lacking because of high propagation delays. (T or F)



Explore BiCMOS or BiMOS technology at en.wikipedia.org.





Interfacing TTL and 5-4 CMOS with Switches


One of the most common means of entering information into a digital system is the use of switches or a keyboard. Examples might be the switches on a digital clock, the keys on a calculator, or the keyboard on a microcomputer. This

+5 V **INPUT OUTPUT** TTL (a)

Pull-up resistor

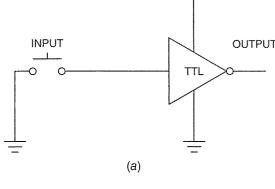

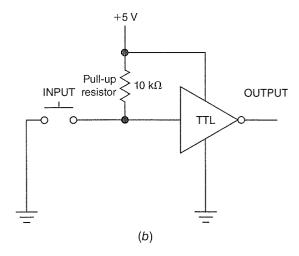

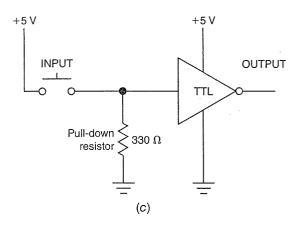


Switch-to-TTL interfaces Switch-to-CMOS interfaces

Fig. 5-11 Switch-to-TTL interfaces. (a) Simple active LOW switch interface. (b) Active LOW switch interface using pull-up resistor. (c) Active HIGH switch interface using pull-down resistor.

section will detail several methods of using a switch to enter data into either TTL or CMOS digital circuits.

Three simple switch interface circuits are depicted in Fig. 5-11. Pressing the push-button switch in Fig. 5-11(a) will drop the input of the TTL inverter to ground level or LOW. Releasing the push-button switch in Fig. 5-11(a) opens the switch. The input to the TTL inverter now is allowed to "float." In TTL, inputs usually float at a HIGH logic level.

Floating inputs on TTL are not dependable. Figure 5-11(b) is a slight refinement of the switch input circuit in Fig. 5-11(a). The $10-k\Omega$ resistor has been added to make sure the input to the TTL inverter goes HIGH when the switch is open. The $10-k\Omega$ resistor is called a *pull-up* resistor. Its purpose is to pull the input voltage up to +5 V when the input switch is open. Both circuits in Fig. 5-11(a) and (b) illustrate active

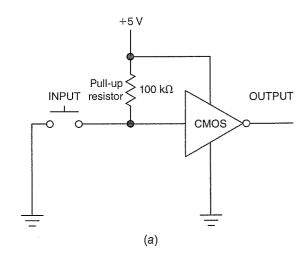

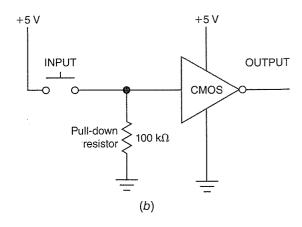


Fig. 5-12 Switch-to-CMOS interfaces. (a) Active LOW switch interface with pull-up resistor. (b) Active HIGH switch interface with pull-down resistor.

LOW switches. They are called active LOW switches because the inputs go LOW only when the switch is activated.

An active HIGH input switch is sketched in Fig. 5-11(c). When the input switch is activated, the +5 V is connected directly to the input of the TTL inverter. When the switch is released (opened), the input is pulled LOW by the *pull-down resistor*. The value of the pull-down resistor is relatively low because the input current required by a standard TTL gate may be as high as 1.6 mA [see Fig. 5-6(b)].

Two switch-to-CMOS interface circuits are drawn in Fig. 5-12. An active LOW input switch is drawn in Fig. 5-12(a). The $100\text{-k}\Omega$ pull-up resistor pulls the voltage to +5 V when the input switch is open. Figure 5-12(b) illustrates an active HIGH switch feeding a CMOS inverter. The $100\text{-k}\Omega$ pull-down resistor makes sure the input to the CMOS inverter is near ground when the input

switch is open. The resistance value of the pullup and pull-down resistors is much greater than those in TTL interface circuits. This is because the input loading currents are much greater in TTL than in CMOS. The CMOS inverter illustrated in Fig. 5-12 could be from the 4000, 74C00, 74HC00, or the FACT series of CMOS ICs.

Switch Debouncing

The switch interface circuits in Figs. 5-11 and 5-12 work well for some applications. However, none of the switches in Figs. 5-11 and 5-12 were *debounced*. The lack of a debouncing circuit can be demonstrated by operating the counter shown in Fig. 5-13(a). Each press of the input switch should cause the decade (0-9) counter to increase by 1. However, in practice each press of the switch increases the count by 1, 2, 3, or sometimes more. This means that several pulses are being fed into the clock (CLK) input

Pull-down resistor

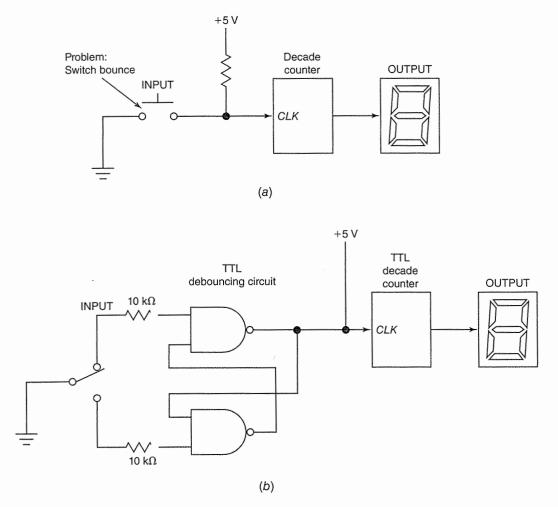


Fig. 5-13 (a) Black diagram of switch interfaced to a decimal counter system. (b) Adding a debouncing circuit to make the decimal counter work properly.

RS flip-flop or latch Switch debouncing circuit of the counter each time the switch is pressed. This is caused by switch bounce.

A switch debouncing circuit has been added to the counting circuit in Fig. 5-13(b). The decade counter will now count each HIGH-LOW cycle of the input switch. The cross-coupled

NAND gates in the debouncing circuit are sometimes called an RS *flip-flop or latch*. Flip-flops will be studied later in greater detail.

Several other switch debouncing circuits are illustrated in Fig. 5-14. The simple debouncing circuit drawn in Fig. 5-14(a) will work only on


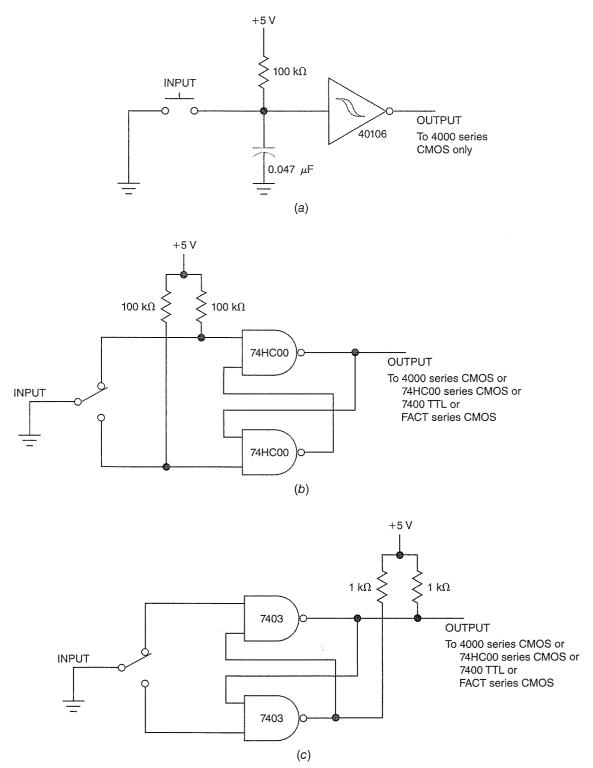


Fig. 5-14 Switch debouncing circuits. (a) A 4000 series switch debouncing circuit. (b) General-purpose switch debouncing circuit that will drive CMOS or TTL inputs. (c) Another general-purpose switch debouncing circuit that will drive CMOS or TTL inputs.

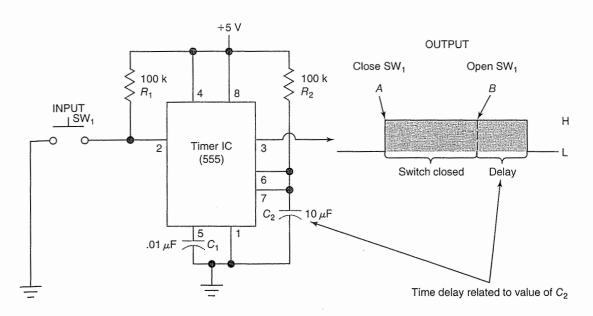

Internet Connection Go to www

Go to www .elmelectronics.com for custom debouncing ICs.

Fig. 5-15 Switch debouncing circuit using the SSS timer IC.

the slower 4000 series CMOS IC. The 40106 CMOS IC is a special inverter. The 40106 is a *Schmitt trigger inverter*, which means it has a "snap action" when changing to either HIGH or LOW. A Schmitt trigger can also change a slow-rising signal (such as a sine wave) into a square wave.

The switch debouncing circuit in Fig. 5-14(b) will drive 4000, 74HC00, or FACT series CMOS or TTL ICs. Another general-purpose switch debouncing circuit is illustrated in Fig. 5-14(c). This debouncing circuit can drive either CMOS or TTL inputs. The 7403 is an *open-collector* NAND TTL IC and needs pull-up resistors as shown in Fig. 5-14(c). The external pull-up resistors make it possible to have an output voltage of just about +5 V for a HIGH. Open-collector

TTL gates with external pull-up resistors are useful when driving CMOS with TTL.

Another switch debouncing circuit using the versatile 555 timer IC is sketched in Fig. 5-15. When push-button switch SW_1 is closed (see point A on output waveform), the output toggles from LOW to HIGH. Later when input switch SW_1 is opened (see point B on waveform), the output of the 555 IC remains HIGH for a delay period. After the delay period (about 1 second for this circuit) the output toggles from HIGH to LOW.

The delay period can be adjusted for the switch debouncing circuit shown in Fig. 5-15. One method of adjusting the time delay is to change the capacitance value of C_2 . Decreasing the value of C_2 will decrease the delay time at the output of the 555 IC. Increasing the capacitance value of C_2 will increase the delay time.

Schmitt trigger inverter

Open-collector TTL output

-√∿- Self-Test


Answer the following questions.

- 29. Refer to Fig. 5-11(a). The input to the TTL inverter goes ______ (HIGH, LOW) when the switch is pressed (closed) but _____ (floats HIGH, goes LOW) when the input push button is open.
- 30. Refer to Fig. 5-11(*b*). The 10- $k\Omega$ resistor, which ensures the input of the TTL inverter, will go HIGH when the switch

- that is open is called a _____ (filter, pull-up) resistor.
- 31. Refer to Fig. 5-13(b). The cross-coupled NAND gates that function as a debouncing circuit are sometimes called a(n) ______ or latch.
- 32. Refer to Fig. 5-11(c). Pressing the switch causes the input of the inverter to go _____(HIGH, LOW) while the output goes _____(HIGH, LOW).

- 33. Refer to Fig. 5-12. The inverters and associated resistors form switch debouncing circuits. (T or F)
- 34. Refer to Fig. 5-13(*a*). This decade counter circuit lacks what circuit?
- 35. Refer to Fig. 5-14(c). The 7403 is a TTL inverter with a(n) _____ output.
 - a. Open collector
 - b. Totem pole
 - c. Tri state
- 36. Refer to Fig. 5-15. Pressing (closing) input switch SW₁ caused the output of the 555 IC to toggle from _____ (HIGH to LOW, LOW to HIGH).

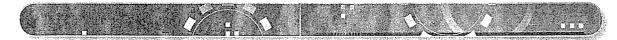- 37. Refer to Fig. 5-15. Releasing (opening) input switch SW₁ (see point *B* on output waveform) causes the output of the 555 IC to
 - a. Immediately toggle from HIGH to LOW
 - b. Toggle from LOW to HIGH after a delay time of about 1 millisecond
 - c. Toggle from HIGH to LOW after a delay time of about 1 second
- 38. Refer to Fig. 5-15. The time delay at the output of the 555 IC can be decreased by _____ (decreasing, increasing) the capacitance value of C_2 .



5-5 Interfacing TTL and CMOS with LEDs

Many of the lab experiments you will perform using digital ICs require an output indicator. The *LED* (*light-emitting diode*) is perfect for this job because it operates at low currents and voltages. The maximum current required by many LEDs is about 20 to 30 mA with about 2 V applied. An LED will light dimly on only 1.7 to 1.8 V and 2 mA.

CMOS-To-LED Interfacing

Interfacing 4000 series CMOS devices with simple LED indicator lamps is easy. Figure 5-16(*a*–*f*) shows six examples of CMOS ICs driving LED indicators. Figure 5-16(*a*) and (*b*) show the CMOS supply voltage at +5 V. At this low voltage, no limiting resistors are needed in series with the LEDs. In Fig. 5-16(*a*), when the output of the CMOS inverter goes HIGH, the LED output indicator lights. The opposite is true in Fig. 5-16(*b*): when the CMOS output goes LOW, the LED indicator lights.

Figure 5-16(c) and (d) show the 4000 series CMOS ICs being operated on a higher supply voltage (\pm 10 to \pm 15 V). Because of the higher voltage, a 1-k Ω limiting resistor is placed in series with the LED output indicator lights. When the output of the CMOS inverter in Fig. 5-16(c) goes HIGH, the LED output indicator lights. In Fig. 5-16(d), however, the LED indicator is activated by a LOW at the CMOS output.

Figure 5-16(*e*) and (*f*) show CMOS buffers being used to drive LED indicators. The circuits may operate on voltages from +5 to +15 V. Figure 5-16(*e*) shows the use of an inverting CMOS buffer (like the 4049 IC), while Fig. 5-16(*f*) uses the noninverting buffer (like the 4050 IC). In both cases, a 1-k Ω limiting resistor must be used in series with the LED output indicator.

TTL-To-LED Interfacing

Standard TTL gates are sometimes used to drive LEDs directly. Two examples are illustrated in Fig. 5-16(g) and (h). When the output of the inverter in Fig. 5-16(g) goes HIGH, current will flow through the LED causing it to light. The indicator light in Fig. 5-16(h) only lights when the output of the 7404 inverter goes LOW. The circuits in Fig. 5-16 are not recommended for critical uses because they can exceed the output current ratings of the ICs. However, the circuits in Fig. 5-16 have been tested and work properly as simple output indicators.

Current Sourcing and Current Sinking

When reading technical literature or listening to technical discussions, you may encounter terms such as *current sourcing* and *current sinking*. The idea behind these terms is illustrated in Fig. 5-17 using TTL ICs to drive LEDs.

In Fig. 5-17(a) the output of the TTL AND gate is HIGH. This HIGH at the output of the AND gate lights the LED. In this example, we

Current sourcing

Light-emitting diode

(LED)

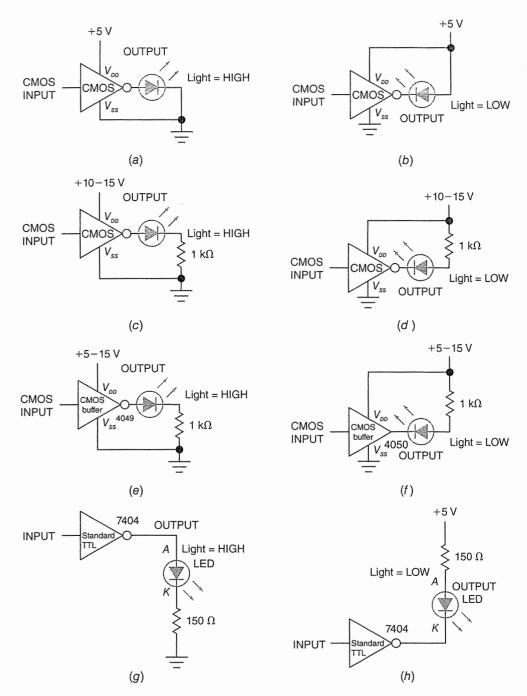


Fig. S-16 Simple CMOS- and TTL-to-LED interfacing. (a) CMOS active HIGH. (b) CMOS active LOW. (c) CMOS active HIGH, supply voltage = 10 to 15 V. (d) CMOS active LOW, supply voltage = 10 to 15 V. (e) CMOS inverting buffer to LED interfacing. (f) CMOS noninverting buffer to LED interfacing. (g) TTL active HIGH. (h) TTL active LOW.

Simple CMOS-to-LED interfacing Simple TTL-to-LED interfacing

talk of the IC as being the source of current (conventional current flow from + to -). The sourcing current is sketched on the schematic diagram in Fig. 5-17(a). The source current appears to "flow from the IC" through the external circuit (LED and limiting resistor) to ground.

In Fig. 5-17(b) the output of the TTL NAND gate is LOW. This LOW at the output of the

NAND gate lights the LED. In this example, we refer to the IC as sinking the current. The *sinking current* is sketched on the schematic diagram in Fig. 5-17(*b*). The sinking current appears to start with +5 V above the external circuit (limiting resistor and LED) and "sink to ground" through the external circuit (limiting resistor and LED) and the output pin of the NAND IC.

Conventional current flow Current sinking


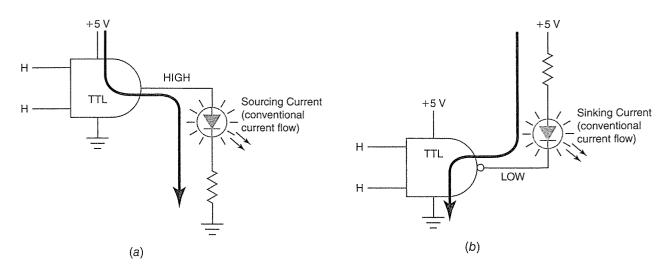


Fig. S-17 (a) Current sourcing. (b) Current sinking.

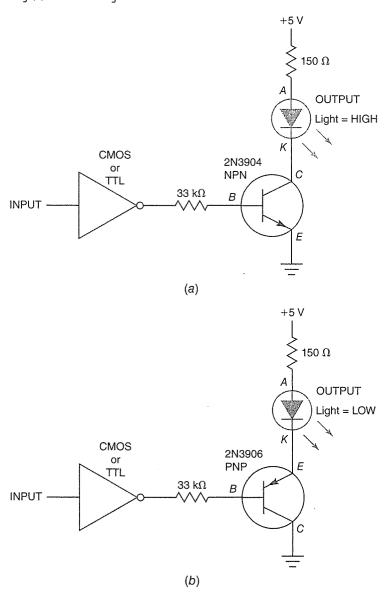

Interfacing to LEDs using a transistor drive circuit

Fig. 5-18 Interfacing to LEDs using a transistor driver circuit. (a) Active-HIGH output using a NPN transistor driver. (b) Active-LOW output using a PNP transistor driver (simplified logic probe).

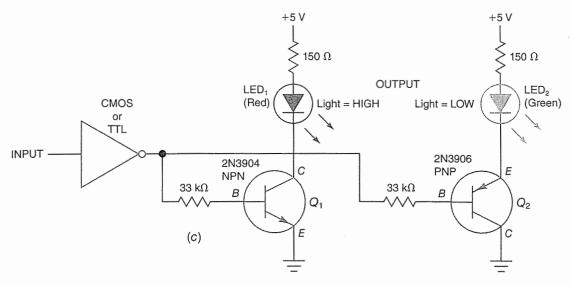


Fig. S-18 (cont.) Interfacing to LEDs using a transistor driver circuit. (c) HIGH-LOW indicator circuit (simplified logic probe).

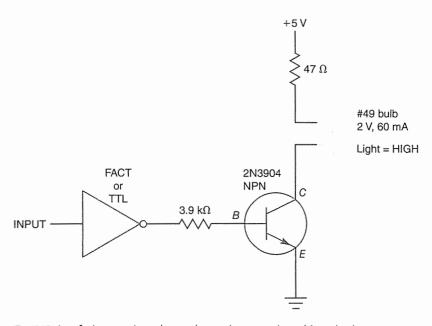


Fig. 5-19 Interfacing to an incandescent lamp using a transistor driver circuit.

Interfacing to an incandescent lamp

Improved LED Output Indicators

Three improved LED output indicator designs are diagrammed in Fig. 5-18. Each of the circuits uses transistor drivers and can be used with either CMOS or TTL. The LED in Fig. 5-18(a) lights when the output of the inverter goes HIGH. The LED in Fig. 5-18(b) lights when the output of the inverter goes LOW. Notice that the indicator in Fig. 5-18(b) uses a PNP instead of an NPN transistor.

The LED indicator circuits in Fig. 5-18(a) and (b) are combined in Fig. 5-18(c). The red light (LED,) will light when the inverter's

output is HIGH. During this time LED_2 will be off. When the output of the inverter goes LOW, transistor Q_1 turns off while Q_2 turns on. The green light (LED_2) lights when the output of the inverter is LOW.

The circuit in Fig. 5-18(c) is a very basic logic probe. However, its accuracy is less than most logic probes.

The indicator light shown in Fig. 5-19, uses an incandescent lamp. When the output of the inverter goes HIGH, the transistor is turned on and the lamp lights. When the inverter's output is LOW, the lamp does not light.

Transistor driver circuit

-√V- Self-Test

Supply the missing word(s) in each statment.

- 39. Refer to Fig. 5-16(*a*–*f*). The _____ (4000, FAST) series CMOS ICs are being used to drive the LEDs in these circuits.
- 40. Refer to Fig. 5-16(h). When the output of the inverter goes HIGH, the LED _____ (goes out, lights).
- 41. Refer to Fig. 5-18(*a*). When the output of the inverter goes LOW, the transistor is turned ______ (off, on) and the LED _____ (does not light, lights).
- 42. Refer to Fig. 5-18(c). When the output of the inverter goes HIGH, transistor ______(Q_1 , Q_2) is turned on and the ______(green, red) LED lights.
- 43. Refer to Fig. 5-20. The TTL decoder IC has _____ (active HIGH, active LOW) outputs.
- 44. Refer to Fig. 5-20. The TTL decoder IC is said to be _____ (sinking current,

- sourcing current) as it lights segment a of the LED display.
- 45. Refer to Fig. 5-20. Segment *d* on the display is not glowing because it takes a _____ (HIGH, LOW) logic level at output *d* of the IC to light the LED.

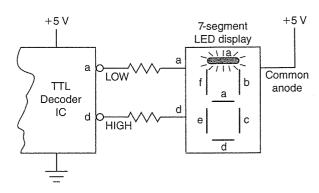


Fig. S-20 TTL decoder IC driving common-anode seven-segment LED display.



Interfacing TTL and CMOS ICs

5-6 Interfacing TTL and CIMOS ICs

CMOS and TTL logic levels (voltages) are defined differently. These differences are illustrated in the voltage profiles for TTL and CMOS shown in Fig. 5-21(a). Because of the differences in voltage levels, CMOS and TTL ICs usually cannot simply be connected together. Just as important, current requirements for CMOS and TTL ICs are different.

Look at the voltage and current profile in Fig. 5-21(a). Note that the output drive currents for the standard TTL are more than adequate to drive CMOS inputs. However, the voltage profiles do not match. The LOW outputs from the TTL are compatible because they fit within the wider LOW input band on the CMOS IC. There is a range of possible HIGH outputs from the TTL IC (2.4 to 3.5 V) that do not fit within the HIGH range of the CMOS IC. This incompatibility could cause problems. These problems can be solved by using a *pull-up resistor*

between gates to pull the HIGH output of the standard TTL up closer to +5 V. A completed circuit for interfacing standard TTL to CMOS is shown in Fig. 5-21(b). Note the use of the 1-k Ω pull-up resistor. This circuit works for driving either 4000 series, 74HC00, or FACT series CMOS ICs.

Several other examples of TTL-to-CMOS and CMOS-to-TTL interfacing using a common 5-V power supply are detailed in Fig. 5-22. Figure 5-22(a) shows the popular LS-TTL driving any CMOS gate. Notice the use of a 2.2-k Ω pull-up resistor. The pull-up resistor is being used to pull the TTL HIGH up near +5 V so that it will be compatible with the input voltage characteristics of CMOS ICs.

In Fig. 5-22(b), a CMOS inverter (any series) is driving an LS-TTL inverter *directly*. Complementary symmetry metal-oxide semiconductor ICs can drive LS-TTL and ALS-TTL (advanced low-power Schottky) inputs: most CMOS ICs cannot drive standard TTL inputs without special interfacing.

CMOS-to-TTL interfacing

TTL-CMOS

interfacing

Pull-up resistor

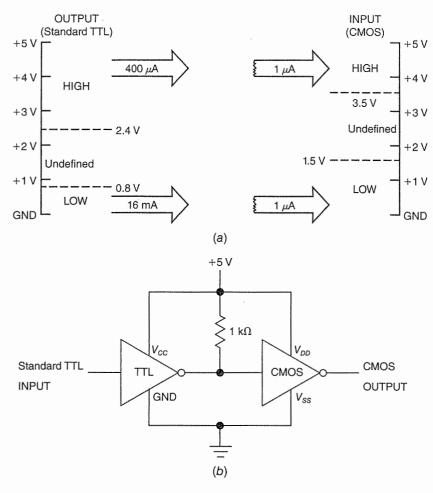


Fig. S-21 TTL-to-CMOS interfacing. (a) TTL output and CMOS input profiles for visualizing compatibility. (b) TTL-to-CMOS interfacing using a pull-up resistor.

TTL-to-CMOS interfacing

Manufacturers have made interfacing easier by designing special buffers and other interface chips for designers. One example is the use of the 4050 noninverting buffer in Fig. 5-22(c). The 4050 buffer allows the CMOS inverter to have enough drive current to operate up to two standard TTL inputs.

The problem of voltage incompatibility from TTL (or NMOS) to CMOS was solved in Fig. 5-21 using a pull-up resistor. Another method of solving this problem is illustrated in Fig. 5-22(*d*). The 74HCT00 series of CMOS ICs is specifically designed as a convenient interface between TTL (or NMOS) and CMOS. Such an interface is implemented in Fig. 5-22(*d*) using the 74HCT34 noninverting IC.

The 74HCT00 series of CMOS ICs is widely used when interfacing between NMOS devices

and CMOS. The NMOS output characteristics are almost the same as for LS-TTL.

The modern FACT series of CMOS ICs has excellent output drive capabilities. For this reason FACT series chips can drive TTL, CMOS, NMOS, or PMOS ICs directly as illustrated in Fig. 5-23(a). The output voltage characteristics of TTL do not match the input voltage profile of 74HC00, 74AC00, and 74ACQ00 series CMOS ICs. For this reason, a pull-up resistor is used in Fig. 5-23(b) to make sure the HIGH output voltage of the TTL gate is pulled up near the +5-V rail of the power supply. Manufacturers produce "T"-type CMOS gates that have the input voltage profile of a TTL IC. TTL gates can directly drive any 74HCT00, 74ACT00, 74FCT00, 74FCTA00, or 74ACTQ00 series CMOS IC, as summarized in Fig. 5-23(c).

FACT series of CMOS ICs

74HCTOO series of CMOS ICs

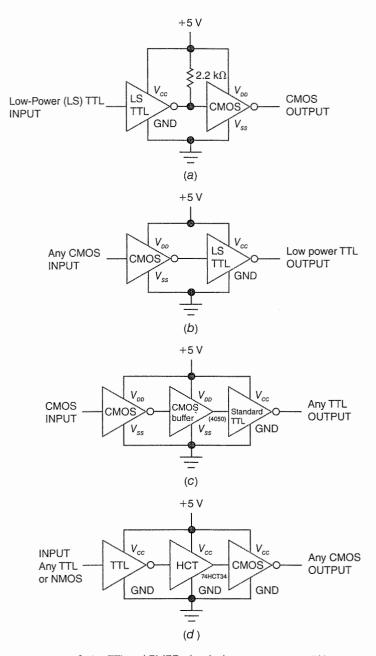


Fig. 5-22 Interfacing TTL and CMOS when both use a common +5-V power supply. (a) Low-power Schottky TTL to CMOS interfacing using a pull-up resistor. (b) CMOS to low-power Schottky TTL interfacing. (c) CMOS to standard TTL interfacing using a CMOS buffer IC. (d) TTL to CMOS interfacing using a 74HCTOO series IC.

Interfacing CMOS devices with TTL devices takes some added components when each operates on a different voltage power supply. Figure 5-24 shows three examples of TTL-to-CMOS and CMOS-to-TTL interfacing. Figure 5-24(a) shows the TTL inverter driving a general-purpose NPN transistor. The transistor and associated resistors translate the lower-voltage TTL outputs to the higher-voltage inputs needed to operate the CMOS inverter.

+5 V TTL AC **FACT** Bipolar TTL HC & HCT **NMOS** (a) **PMOS FACT** +5 V $4.7 \text{ k}\Omega$ AC TTL FAST HC AS/ALS AC ACQ (b) +5 V TTL CMOS **FAST** HCT AS/ALS ACT FCT **FCTA** (c) **ACTQ**

Fig. S-23 Interfacing FACT with other families. (a) FACT driving most other TTL and CMOS families.
(b) TTL-to-FACT interfacing using a pull-up resistor.
(c) TTL-to-"T" CMOS ICs.

The CMOS output has a voltage swing from about 0 to almost +10 V. Figure 5-24(b) shows an open-collector TTL buffer and a 10- $k\Omega$ pullup resistor being used to translate the lower TTL to the higher CMOS voltages. The 7406 and 7416 TTL ICs are two inverting, open-collector (OC) buffers.

Interfacing between a higher-voltage CMOS inverter and a lower-voltage TTL inverter is shown in Fig. 5-24(c). The 4049 CMOS buffer is used between the higher-voltage CMOS inverter and the lower-voltage TTL IC. Note that the CMOS buffer is powered by the lower-voltage (+5 V) power supply in Fig. 5-24(c).

CMOS buffer

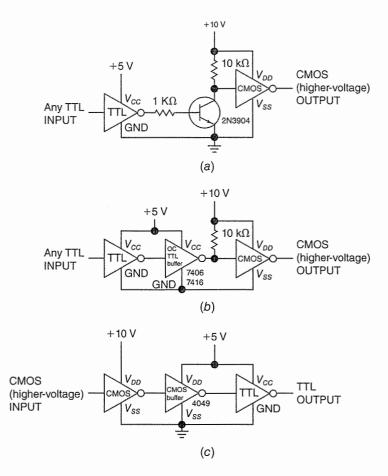


Fig. 5-24 Interfacing TTL and CMOS when each use a different power supply voltage. (a) TTL-to-CMOS interfacing using a driver transistor. (b) TTL-to-CMOS interfacing using an open collector TTL buffer IC. (c) CMOS-to-TTL interfacing using a CMOS buffer IC.

Looking at the voltage and current profiles [such as in Fig. 5-21(a)] is a good starting point when learning about or designing an interface. Manufacturers' manuals are also very helpful.

Several techniques are used to interface between different logic families. These include the use of pull-up resistors and special interface ICs. Sometimes no extra parts are needed.

Supply the missing word in each statement.

- 46. Refer to Fig. 5-21(a). According to this profile of TTL output and CMOS input characteristics, the logic devices _____ (are, are not) voltage compatible.
- 47. Refer to Fig. 5-22(a). The 2.2-k Ω resistor in this circuit is called a _____ resistor.
- 48. Refer to Fig. 5-22(c). The 4050 buffer is a special interface IC that solves the _____ (current drive, voltage) incompatibility between the logic families.
- 49. Refer to Fig. 5-24(a). The ______ (NMOS IC, transistor) translates the TTL logic levels to the higher-voltage CMOS logic levels.



5-7 Interfacing with Buzzers, Relays, Motors, and Solenoids

The objective of many electromechanical systems is to control a simple output device. This device might be as simple as a light, buzzer, relay, electric motor, stepper motor, or solenoid. Interfacing to LEDs and lamps has been explored. Simple interfacing between logic elements and buzzers, relays, motors, and solenoids will be investigated in this section.

Interfacing with Buzzers

Piezo buzzer

The *piezo buzzer* is a modern signaling device drawing much less current than older buzzers and bells. The circuit in Fig. 5-25 shows the interfacing necessary to drive a piezo buzzer with digital logic elements. A standard TTL or FACT CMOS inverter is shown driving a piezo buzzer

directly. The standard TTL output can sink up to 16 mA while a FACT output has 24 mA of drive current. The piezo buzzer draws about 3 to 5 mA when sounding. Notice that the piezo buzzer has polarity markings. The diode across the buzzer is to suppress any transient voltages that might be induced in the system by the buzzer.

Many logic families do not have the current capacity to drive a buzzer directly. A transistor has been added to the output of the inverter in Fig. 5-25(b) to drive the piezo buzzer. When the output of the inverter goes HIGH, the NPN transistor is turned on and the buzzer sounds. A LOW at the output of the inverter turns the transistor off, switching the buzzer off. The diode protects against transient voltages. The interface circuit sketched in Fig. 5-25(b) will work for both TTL and CMOS.

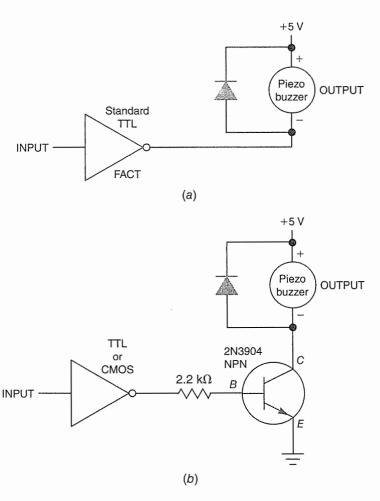


Fig. 5-25 Logic device to buzzer interfacing. (a) Standard TTL or FACT CMOS inverter driving a piezo buzzer directly. (b) TTL or CMOS interfaced with buzzer using a transistor driver.

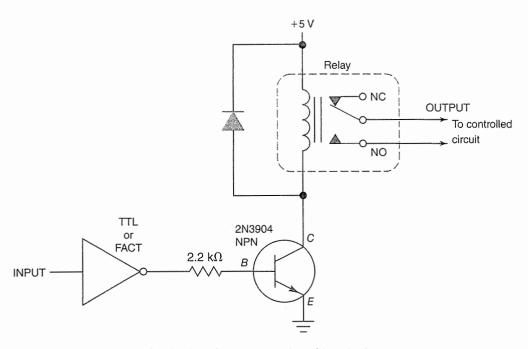


Fig. 5-26 TTL or CMOS interfaced with a relay using a transistor driver circuit.

Interfacing Using Relays

A relay is an excellent method of isolating a logic device from a high-voltage circuit. Figure 5-26 shows how a TTL or CMOS inverter could be interfaced with a relay. When the output of the inverter goes HIGH, the transistor is turned on and the relay is activated. When activated, the normally open (NO) contacts of the relay close as the armature clicks downward. When the output of the inverter in Fig. 5-26 goes LOW, the transistor stops conducting and the relay is deactivated. The armature springs upward to its normally closed (NC) position. The clamp diode across the relay coil prevents voltage spikes which might be induced in the system.

The circuit in Fig. 5-27(a) uses a relay to isolate an electric motor from the logic devices. Notice that the logic circuit and dc motor have separate power supplies. When the output

of the inverter goes HIGH, the transistor is turned on and the NO contacts of the relay snap closed. The dc motor operates. When the output of the inverter goes LOW, the transistor stops conducting and the relay contacts spring back to their NC position. This turns off the motor.

The electric motor in Fig. 5-27(a) produces rotary motion. A solenoid is an electric device that can produce linear motion. A solenoid is being driven by a logic gate in Fig. 5-27(b). Note the separate power supplies. This circuit works the same as the motor interface circuit in Fig. 5-27(a).

In summary, voltage and current characteristics of most buzzers, relays, electric motors, and solenoids are radically different from those of logic circuits. Most of these electric devices need special interfacing circuits to drive and isolate the devices from the logic circuits.

Relay

Clamp diode

Logic device to relay interface


-W- Self-Test

Supply the missing word(s) in each statement.

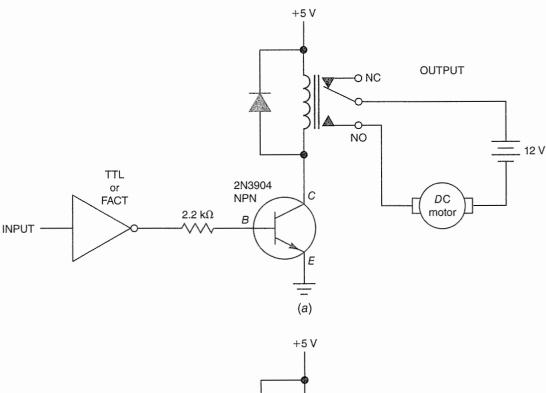- 50. Refer to Fig. 5-25(a). If the piezo buzzer draws only 6 mA, it ______ (is, is not) possible for a 4000 series CMOS IC to drive the buzzer directly [see Fig. 5-6(b) for 4000 series data].
- 51. Refer to Fig. 5-25(*b*). When the input to the inverter goes LOW, the transistor turns ______ (off, on) and the buzzer _____ (does not sound, sounds).
- 52. Refer to Fig. 5-26. The purpose of the diode across the coil of the relay is to

- suppress _____ (sound, transient voltages) induced in the circuit.
- 53. Refer to Fig. 5-27(a). The dc motor will run only when a _____ (HIGH, LOW) appears at the output of the inverter.
- 54. If an electric motor produces rotary motion then a solenoid produces _____ (linear, circular) motion.
- 55. The main purpose of the relay in Fig. 5-27 is to _____ (combine, isolate) the

- logic circuitry from the higher-voltage/current motor or solenoid.
- 56. Refer to Fig. 5-27(*a*). If the input to the inverter is LOW, its output goes HIGH which _____ (turns on, turns off) the NPN transistor.
- 57. Refer to Fig. 5-27(a). When the transistor is turned on, current flows through the coil of the relay and the armature snaps from the ______ (NC to the NO, NO to the NC) position which activates the motor circuit.



Logic device to solenoid interfacing

Logic device to

motor interfacing

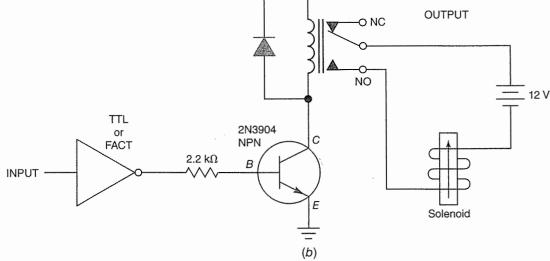


Fig. 5-27 Using a relay to isolate higher voltage/current circuits from digital circuits. (a) Interfacing TTL or CMOS with an electric motor. (b) Interfacing TTL or CMOS with a solenoid.



5-8 Optoisolators

The relay featured in Fig. 5-27 isolated the lower-voltage digital circuitry from the high-voltage/current devices such as a solenoid and electric motor. *Electromechanical relays* are relatively large and expensive but are a widely used method of control and isolation. Electromechanical relays can cause unwanted voltage spikes and noise due to the coil windings and opening and closing of contact points. A useful alternative to an electromagnetic relay when interfacing with digital circuits is the *optoisolator* or *optocoupler*. One close relative of the optoisolator is the *solid-state relay*.

One economical optoisolator is featured in Fig. 5-28. The 4N25 optoisolator consists of a gallium arsenide infrared-emitting diode optically coupled to a silicon phototransistor detector enclosed in a six-pin dual in-line package (DIP). Figure 5-28(a) details the pin diagram for the 4N25 optoisolator with the names of the pins. On the input side, the LED is typically activated with a current of about 10 to 30 mA. When the input LED is activated, the light activates (turns on) the phototransistor. With no current through the LED the output phototransistor of the optoisolator is turned off (high resistance from emitter to collector).

A simple test circuit using the 4N25 optoisolator is shown in Fig. 5-28(b). The digital signal from the output of a TTL or FACT inverter directly drives the infrared-emitting diode. The circuit is designed so the LED is activated when the output of the inverter goes LOW, which allows the inverter to sink the 10 to 20 mA LED current to ground. When the LED is activated, infrared light shines (inside the package) activating the phototransistor. The transistor is turned on (low resistance from emitter to collector) dropping the voltage at the collector (OUTPUT) to near 0 V. If the output of the inverter goes HIGH, the LED does not light and the NPN phototransistor turns off (high resistance from emitter to collector). The output (at the collector) is pulled to about +12 V (HIGH) by the 10-k Ω pull-up resistor. In this example, notice that the input side of the circuit operates on +5 V while the output side in this example uses a separate +12-V power supply. In summary, the input and output sides of the circuit are isolated from one another.

In Fig. 5-28(b), when pin 2 of the optoisolator goes LOW, the output at the collector of the transistor goes LOW. The grounds of the separate power supplies should not be connected to complete the isolation between the low- and high-voltage sides of the optoisolator.

A simple application of the optoisolator being used to interface between TTL circuitry and a piezo buzzer is diagrammed in Fig. 5-28(c). In this example the pull-up resistor is removed because we are using the NPN phototransistor in the optoisolator to sink the 2 to 4 mA of current when the transistor is activated. A LOW at the output of the inverter (pin 2 of optoisolator) activates the LED, which in turn activates the phototransistor.

To control heavier loads using the optoisolator, we could attach a power transistor to the output as is done in Fig. 5-28(d). In this example, if the LED is activated, it activates the phototransistor. The output of the optoisolator (pin 5) drops LOW, which turns off the power transistor. The emitter-to-collector resistance of the power transistor is high, turning off the dc motor. When the output of the TTL inverter goes HIGH, it turns off the LED and the phototransistor in the optoisolator. The voltage at output pin 5 goes positive, which turns on the power transistor and operates the dc motor. Optoisolator



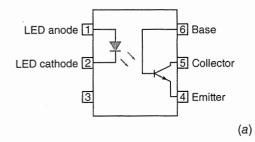


Fig. 5-28 (a) The 4N25 optoisolator pin out and six-pin DIP.

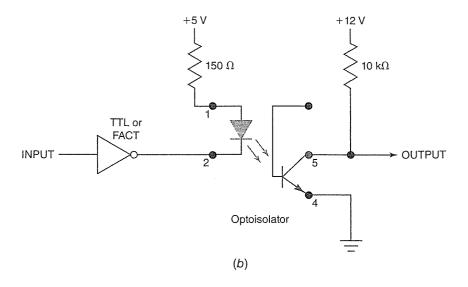

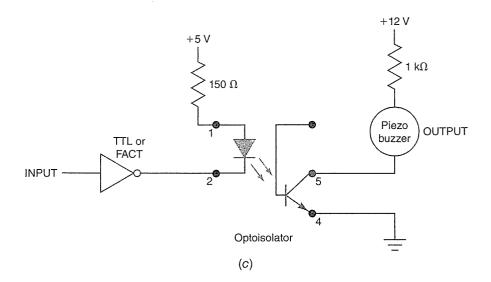



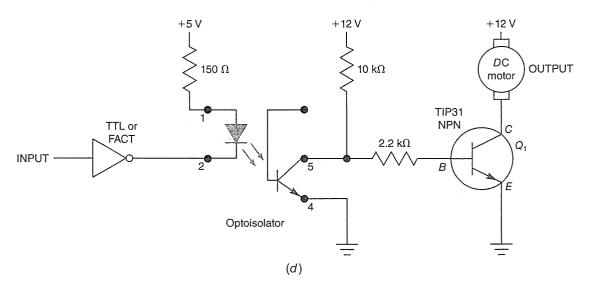



Fig. 5-28 (cont.) (b) Basic optoisolator circuit separates 5-V and 12-V circuits. (c) Optoisolator driving pieza buzzer. (d) Optoisolator isolating low-voltage digital circuit from high-voltage/current motor circuit.

If the power transistor (or other power-handling device such as a triac) in Fig. 5-28(d) were housed in the isolation unit, the entire device is sometimes a *solid-state relay*. Solid-state relays can be purchased to handle a variety of outputs included in either ac or dc loads. The output circuitry in a solid-state relay may be more complicated than that shown in Fig. 5-28(d).

Several examples of solid-state relay packages are shown in Fig. 5-29. The unit in Fig. 5-29(a) is a smaller PC-mounted unit. The larger bolted-on solid-state relay has screw terminals and can handle greater ac currents and voltages.

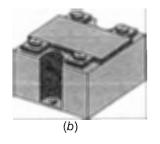In summary, it is common to isolate digital circuitry from some devices because of high operating voltages and currents or because of dangerous feedback in the form of voltage spikes and noise. Traditionally, electromagnetic relays have been used for isolation, but optoisolators and solid-state relays are an inexpensive and effective alternative when interfacing with





Solid-state relay

Fig. 5-29 (a) Solid-state relay—small PC-mounted package.
(b) Solid-state relay—heavy-duty package.

digital circuits. A typical optoisolator, shown in Fig. 5-28(a), contains an infrared-emitting diode that activates a phototransistor. If you are building an interface project using the parallel port from an IBM-compatible PC, you will want to use optoisolators between your circuits and the computer. The PC parallel-port outputs and inputs operate with TTL level signals. Good isolation protects your computer from voltage spikes and noise.


1 7173 412	100000000000000000000000000000000000000
2071 PER	
PERSONAL REPORTED	\$5000000000000000000000000000000000000

Self-Test

Supply the missing word(s) in each statement.

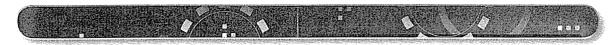- 58. Refer to Fig. 5-27(*a*). The ______ (relay, transistor) isolates the digital circuitry from the higher-voltage and noisy dc motor circuit.
- 59. The 4N25 optoisolator device contains an infrared-emitting diode optically coupled to a ______ (phototransistor, triac) detector enclosed in a six-pin DIP.
- 60. Refer to Fig. 5-28(b). If the output of the TTL inverter goes LOW, the infrared LED ______ (does not light, lights), which _____ (activates, deactivates) the phototransistor and the voltage at pin 5 (output) goes _____ (HIGH, LOW).
- 61. Refer to Fig. 5-28(*b*). The 10-kΩ resistor connecting the collector of the phototransistor to +12 V is called a(n) _____ resistor.
- 62. Refer to Fig. 5-28(*c*). If the output of the TTL inverter goes HIGH, the LED

- _____ (does not light, lights), which _____ (activates, deactivates) the phototransistor and the voltage at pin 5 (output) goes (HIGH, LOW) and the buzzer _____ (does not sound, sounds).
- 63. Refer to Fig. 5-28(d). If the output of the TTL inverter goes HIGH, the LED does not light, which deactivates (turns off) the phototransistor and the voltage at pin 5 (output) goes more positive. This positive-going voltage at the base of the power transistor ______ (turns on, turns off) Q_1 and the dc motor _____ (does not run, runs).
- 64. The ______ (electromagnetic, solid-state) relay is a close relative of an optoisolator.
- 65. Refer to Fig. 5-28(c). If the *input* to the inverter is HIGH then the piezo buzzer _____ (will not sound, will sound).



5-9 Interfacing with Servo and Stepper Motors

The dc motor mentioned previously in this chapter is a device that rotates continuously when power is applied. The control over the dc motor is limited to ON-OFF, or if you reverse the direction of current flow through the motor the direction of rotation reverses. A simple dc motor does not facilitate good speed control, and it will not rotate a given number of degrees to stop for angular positioning. Where precision positioning or exacting speed are required, a regular dc motor does not do the job.

Servo Motor

Both the servo and the stepper motor can rotate to a given position and stop and also reverse direction. The word "servo" is short for servo motor. "Servo" is a general term for a motor in which either the angular position or speed can be controlled precisely by a servo loop which uses feedback from the output back to input for control. The most common servos are the inexpensive units used in model aircraft, model cars, and some educational robot kits. These servos are geared-down dc motors with builtin electronics that respond to different pulse widths. These servos use feedback to ensure the device rotates to and stays at the current angular position. These servos are popular in remote-control models and toys. They commonly have three wires (one wire for input and two wires for power) and are not commonly used for continuous rotation.

The position of a hobby servo's output shaft is determined by the width or duration of the control pulse. The width of the control pulse commonly varies from about 1 to 2 ms. The concept of controlling the hobby servo motor using a control pulse is sketched in Fig. 5-30. The *pulse generator* emits a constant frequency of about 50 Hz. The pulse width (or pulse duration) can be changed by the operator using an input device such as a potentiometer or joystick. The internally geared motor and feedbackand-control circuitry inside the servo motor responds to the continuous stream of pulses by rotating to a new angular position. As an example, if the pulse width is 1.5 ms, the shaft moves to the middle of its range as illustrated in Fig. 5-30(a). If the pulse width decreases to 1 ms, the output shaft takes a new position rotating about 90° clockwise as shown in Fig. 5-30(b). Finally if the pulse width increases to 2 ms as in Fig. 5-30(c), the output shaft moves counterclockwise to its new position.

The changing of the pulse duration is called *pulse-width modulation* (PWM). In the example shown in Fig. 5-30, the pulse generator outputs a constant frequency of 50 Hz but the pulse width can be adjusted.

A sketch of the internal functions of a servo motor is shown in Fig. 5-30(d). The servo contains a dc motor and speed-reducing gear. The last gear drives the output shaft and is also connected to a potentiometer. The potentiometer senses the angular position of the output. The varying resistance of the potentiometer is fed back to the control circuitry and repeatedly compares the pulse width of the external (input) pulse with an internally generated pulse from a one-shot inside the control circuit. The internal pulse width is varied based on the feedback from the potentiometer.

For the servo motor in Fig. 5-30 suppose the *external pulse width is 1.5-ms* and the internal pulse width is 1.0-ms. After comparing the pulses, the control circuitry would start to rotate the output shaft in a CCW direction. After each external pulse (50 times per second) the control circuitry would make a small CCW shaft adjustment until the external and internal pulse widths are both 1.5-ms. At this point the shaft would stop in the position shown in Fig. 5-30(*a*).

Next for the servo motor in Fig. 5-30 suppose the *external pulse width changes to 1 ms* and the internal pulse width, based on the feedback from the potentiometer, is at 1.5 ms. After comparing the pulses, the control circuitry would start to rotate the output shaft in a CW direction. After each external pulse (50 times per second) the control circuitry would make a small CW shaft adjustment until the external and internal pulse width are both 1.0 ms. At this point the shaft would stop in the position shown in Fig. 5-30(*b*).

When both external and internal pulse widths are equal for the servo motor in Fig. 5-30, the control circuitry stops the dc motor. For instance, if both the external and internal pulse widths are 2.0 ms, then the output shaft would freeze in the position shown in Fig. 5-30(c).



Find more information on how servo motors work.

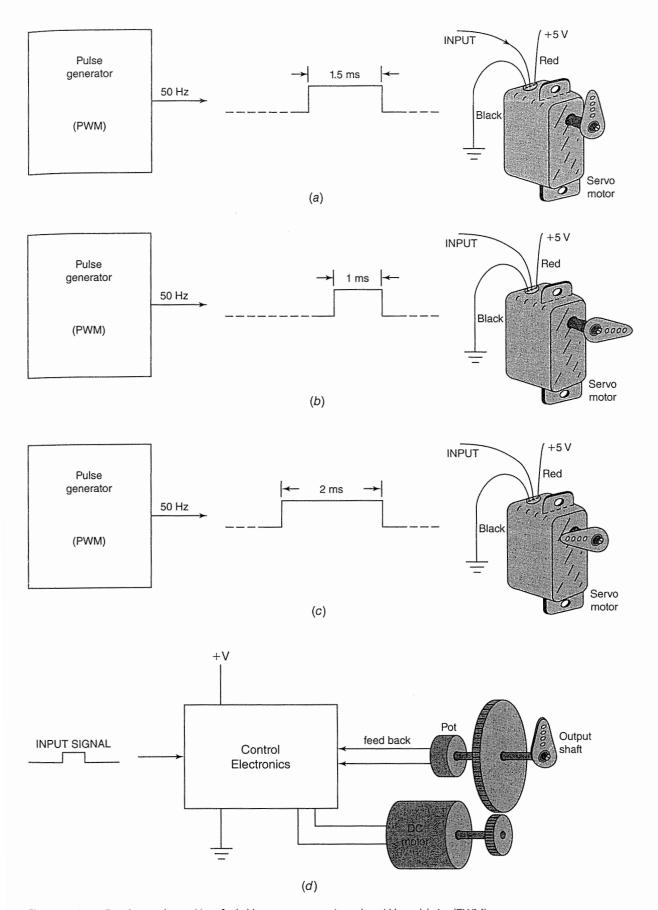


Fig. 5-30 Controlling the angular position of a hobby servo motor using pulse-width modulation (PWM). (Note: Some hobby servos rotate in the opposite direction as the pulse width increases.)

Some hobby servo motors may have opposite rotational characteristics from the unit featured in Fig. 5-30. Some servos are internally wired so that a narrow pulse (1 ms) would cause full CCW rotation instead of CW rotation shown in Fig. 5-30(b). Likewise, a wide pulse (2 ms) would cause full CW rotation. This is opposite that pictured in Fig. 5-30(c).

Stepper Motor

The stepper motor can rotate a fixed angle with each input pulse. A common four-wire stepper motor is sketched in Fig. 5-31(a). From the label you can see some of the important characteristics of the stepper motor. This stepper motor is designed to operate on 5-V dc. Each of the two coils $(L_1 \text{ and } L_2)$ has a resistance of 20 Ω . Using Ohm's law we calculate that the dc current through each coil is 0.25 A or 250 mA (I = V/R, substituting I = 5/20, then I =0.25 A). The 2 ph means this is a two-phase or bipolar (as opposed to unipolar) stepper motor. Bipolar stepper motors typically have four wires coming from the case as is shown in Fig. 5-31(a). Unipolar stepper motors can have five to eight wires coming from the unit. The label on the stepper motor in Fig. 5-31(a) indicates that each step of the motor is 18° (meaning each input pulse rotates the shaft of the stepper motor an angle of 18°).

Other important characteristics that might be given in a catalog or manufacturer's data sheet are physical size, inductance of coils, holding torque, and detent torque of motor. A schematic of the stepper motor's coils would probably be included. Notice that there are two coils in the schematic diagram of this stepper motor. A control sequence is also usually given for a stepper motor.

A simplified exploded view of a stepper motor is drawn in Fig. 5-31(c). Of interest is the permanent magnet rotor attached to the output shaft. Some stepper motors have a gearlike softiron rotor with the number of poles unequal to the number of poles in the stator. These are referred to as variable reluctance stepper motors. There are two stators as shown in Fig. 5-31(c). A series of poles are visible on both stator 1 and 2. The number of poles on a single stator are the number of steps required to complete one revolution of the stepper motor. For instance, if

Degs. in circle/single-step angle = steps per revolution 360°/18° = 20 steps per revolution

a stepper motor has a single step angle of 18°,

you can calculate the number of steps in a revo-

In this example, each stator has 20 visible poles. Notice that the poles of stator 1 and 2 are not aligned but are one-half the single-step angle, or 9° different. Common stepper motors are

available in step angles of 0.9°, 1.8°, 3.6°, 7.5°, 15°, and 18°.

lution as

Stepper Motor Control Sequence

The stepper motor responds to a standard control sequence. That control sequence for a sample bipolar stepper motor is charted in Fig. 5-32(a). Step 1 on the chart shows coil lead L_1 at about +5 V, while the other end of the coil (\overline{L}_1) is grounded. Likewise, step 1 also shows coil lead L, at about +5 V while the other end of the coil $(\overline{L_2})$ is grounded. In step 2, note that the polarity of coil L_1/\overline{L}_1 is reversed while L_2/\overline{L}_2 stays the same, causing a clockwise (CW) rotation of one step (18° for the sample stepper motor). In step 3, only the polarity of coil L_2/\overline{L}_2 is reversed, causing a second CW rotation of one step. In step 4, only the polarity of coil L_1/L_1 is reversed, which causes a third CW rotation of a single step. In step 1, only the polarity of L_2/L_2 has been reversed, causing a fourth CW rotation of a single step. Continuing the sequence of steps 2, 3, 4, 1, 2, 3, and so on would cause the stepper motor to continue rotating in a CW direction 18° at each step.

To reverse the stepper motor's direction of rotation, move upward on the control sequence chart in Fig. 5-32(a). Suppose we are at step 2 at the bottom of the chart. Moving upward to step 1, the polarity of only coil L_1/\overline{L}_1 changes and the motor rotates one step counterclockwise (CCW). Moving upward again to step 4, the polarity of only coil L_2/\overline{L}_2 changes and the motor rotates a second step CCW. In step 3, the polarity of only coil L_1/\overline{L}_1 changes as the motor rotates a third step CCW. CCW rotation continues as long as the sequence 2, 1, 4, 3, 2, 1, 4, 3, and so forth from the control sequence is followed.

In summary, CW rotation occurs when you progress downward on the control sequence

Control sequence for stepper motor

Bipolar stepper motor

Variable reluctance stepper motor

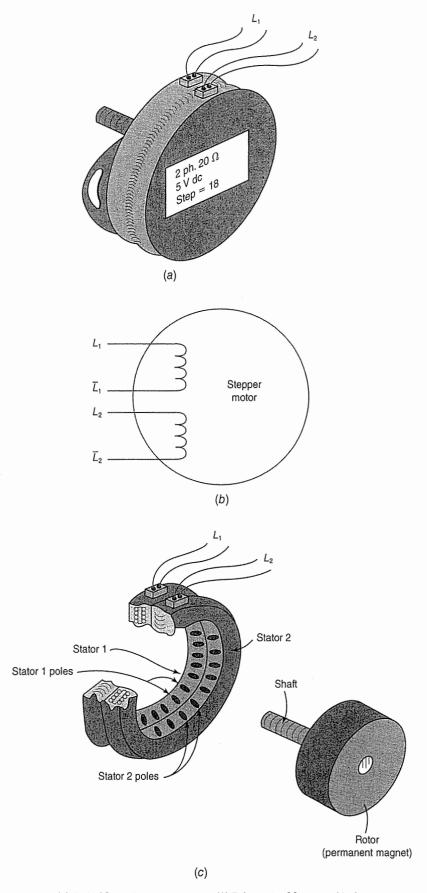


Fig. 5-31 (a) Typical four-wire stepper motor. (b) Schematic of four-wire bipolar stepper motor. (c) Simple exploded view of typical permanent magnet type stepper motor.

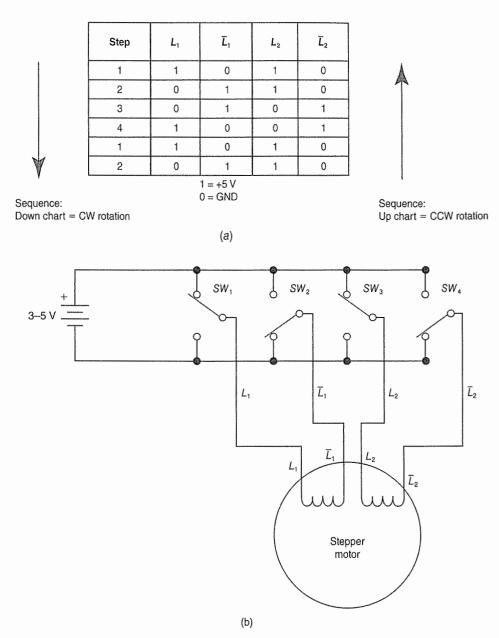


Fig. 5-32 (a) Bipolar control sequence chart. (b) Test circuit for hand checking a four-wire bipolar stepper motor.

chart in Fig. 5-32(a). Counterclockwise rotation occurs when you stop at any step on the chart in Fig. 5-32(a) and then progress upward. The stepper motor is excellent at exact angular positioning, which is important in computer disk drives and printers, robotics and all types of automated machinery, and NC machine tools. The stepper motor can also be used for continuous rotation applications where the exact speed of rotation is important. Continuous rotation of a stepper motor can be accomplished by sequencing through the control sequence quickly. For instance, suppose you want the motor from Fig. 5-31(a) to rotate

at 600 rpm. This means that the motor rotates 10 revolutions per second (600 rpm/60 s = 10 rev/s). You would have to send the code from the control sequence in Fig. 5-32(a) to the stepper motor at a frequency of 200 Hz ($10 \text{ rev/s} \times 20 \text{ steps per rev} = 200 \text{ Hz}$).

Stepper Motor Interfacing

Consider the simple test circuit in Fig. 5-32(b) which could be used to check a bipolar stepper motor. The single-pole, double-throw (SPDT) switches are currently set to deliver the voltages defined by step 1 on the control sequence


chart in Fig. 5-32(a). As you change the voltage inputs to the coils as specified by step 2, then step 3, and then step 4, and so on, the motor rotates by stepping in a CW direction. If you reverse the order and sequence upward on the control sequence chart in Fig. 5-32(a), the motor reverses and rotates by stepping in a CCW direction. The circuit in Fig. 5-32(b) is an impractical interface circuit but can be used for hand testing a stepper motor.

A practical bipolar stepper motor interface is based on the MC3479 stepper motor driver IC from Motorola. The schematic diagram in Fig. 5-33(a) details how you might wire the

MC3479 driver IC to a bipolar stepper motor. The MC3479 IC has a logic section that generates the proper control sequence to drive a bipolar stepper motor. The motor driver section has a drive capability of 350 mA per coil. Each step of the motor is triggered by a single positive-going clock pulse entering the CLK input (pin 7) of the IC. One input control sets the direction of rotation of the stepper motor. A logic 0 at the CW/CCW input to the MC3479 allows CW rotation, while a logic 1 input at pin 10 changes to CCW rotation of the stepper motor.

The MC3479 IC also has a full/half input (pin 9) which can change the operation of the

Bipolar stepper motor

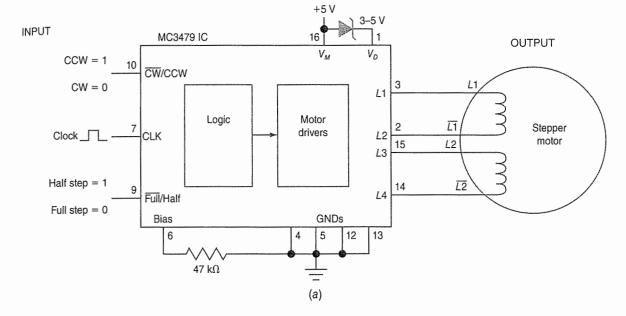

Step	L ₁	L ₂	L ₃	L ₄			
1	1	0	1	0			
2	0	1	1	0			
3	0	1	0	1			
4	1	0	0	1			
1	1	0	1	0			
2	0	1	1	0			
(b)							

Step	L ₁	L ₂	L ₃	L ₄			
1	1	0	1	0			
2	1	1	1	0			
3	0	1	1	0			
4	0	1	1	1			
5	0	1	0	1			
6	1	1	0	1			
7	1	0	0	1			
8	1	0	1	1			
1	1	0	1	0			
2	1	1	1	0			
3	0	1	1	0			
4	0	1	1	1			
(c)							

Fig. 5-33 (a) Using the MC3479 stepper motor driver IC to interface with a bipolar stepper motor. (b) Control sequence of the MC3479 IC in the full-step mode. (c) Control sequence for the MC3479 IC in the half-step mode.



Find the data sheet for the MC3479 IC at onsemi.com. Unipolar stepper motor

MC 3479 stepper motor driver IC

5804 stepper motor driver IC IC from stepping by full steps or half steps. In the full-step mode, the stepper motor featured in Fig. 5-31 rotates 18° for each clock pulse (each single step). In the half-step mode, the stepper motor rotates half of a regular step or only 9° per clock pulse. The control sequence used by the MC3479 IC in the full-step mode is shown in chart form in Fig. 5-33(b). Note that this is the same control sequence used in Fig. 5-32(a). The control sequence used by the MC3479 IC in the half-step mode is detailed in chart form in Fig. 5-33(c). These control sequences are standard for bipolar or two-phase stepper motors and are built into the logic block of the MC3479 stepper motor driver IC. Specialized ICs such as the MC3479 stepper motor driver are usually the simplest and least expensive method of solving the problem of generating the correct control sequences, allowing for either CW or CCW rotation, and allowing the stepper motor to operate in either the full-step or half-step mode. The motor driver circuitry of the MC3479 is included inside the IC so lowerpower stepper motors can be driven directly by the IC as illustrated in Fig. 5-33(a).

Unipolar or four-phase stepper motors have five or more leads exiting the motor. Specialized ICs are also available for generating the correct control sequence for these four-phase motors. One such product is the *EDE1200 unipolar stepper motor IC* by E-LAB Engineering. The EDE1200 has many of the same features of the Motorola MC3479 except it does not have the motor drivers inside the IC. External driver transistors or a driver IC must be used in conjunction with the EDE1200 unipolar stepper motor IC. The control sequence for four-phase (unipolar) and two-phase (bipolar) stepper motors is different.

Note the use in Fig. 5-34 of two power supplies (+5 V and +12 V), both connected to the same 5804 IC. The +5-V supply powers the

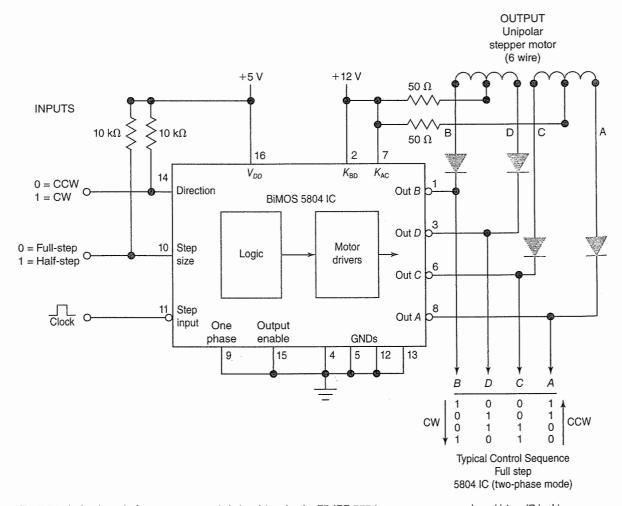


Fig. 5-34 A six-wire unipolar stepper motor is being driven by the BiMOS 5804 stepper motor translator/driver IC in this schematic diagram.

input and logic sections of the 5804 IC. The +12-V supply powers the high current, high-voltage active LOW outputs.

A typical full-step control sequence generated by the 5804 IC's logic section is shown at the lower right in Fig. 5-34. When a 5804 output goes LOW, it sinks the high current from the coils of the stepper motor.

The four Schottky diodes allow normal currents to flow through while protecting the 5804 IC from damaging voltage spikes. Pull-up resistors (two 10 k Ω) are shown at the upper left of Fig. 5-34.

This is a circuit you could construct in the lab.

Summary

In summary, a simple permanent magnet dc motor is good for continuous rotation applications. Servo motors (such as the hobby servo motor) are good for angular positioning of a shaft. Pulse-width modulation (PWM) is a technique used to rotate the servo to an exact angular position. Stepper motors can be used for angular positioning of a shaft or for controlled continuous rotation.

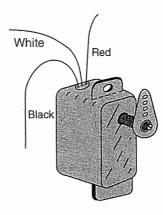


Fig. 5-35 Art for self-test questions 69, 70 and 71.

-/k- Self-Test

Answer the following questions.

- 66. The _____ (dc motor, servo motor) is a good choice for continuous rotation applications not requiring speed control.
- 67. The ______ (dc motor, stepper motor) is a good choice for applications that require exact angular positioning of a shaft.
- 68. Both the servo and stepper motors can be used in applications that require exact angular positioning. (T or F)
- 69. Refer to Fig. 5-35. This device, which might be found in a radio-controlled airplane or car, is called a ______ (servo motor, stepper motor).
- 70. Refer to Fig. 5-35. The red lead is connected to + of the power supply, the black lead to ground, and the white lead to the servo is the _____ (input, output) lead.
- 71. Refer to Fig. 5-35. This hobby servo motor is controlled by inputs from a pulse generator using ______ (pulse-amplitude, pulse-width) modulation.

- 72. The device featured in Fig. 5-31 is a _____ (bipolar, unipolar) stepper motor.
- 73. The chart in Fig. 5-32(a) shows the _____ sequence for a _____ (bipolar, unipolar) stepper motor.
- 74. Refer to Fig. 5-32(a). If we are at step 4 and progress upward on the control sequence chart to step 3, the stepper motor rotates in a ______ (CCW, CW) direction.
- 75. Refer to Fig. 5-33(a). The _____ (logic, motor drive) block inside the MC3479 IC assures that the control sequence for driving a bipolar stepper motor is followed.
- 76. Refer to Fig. 5-33(a). The maximum drive current for each coil available using the MC3479 is ______ (10, 350) mA, which allows it to drive many smaller stepper motors directly.
- 77. Refer to Fig. 5-33(a) and assume input pins 9 and 10 are HIGH. When a clock pulse enters pin 7, the attached stepper motor rotates ______ (CCW, CW) a _____ (full step, half step).



For information on servo mechanisms and stepper motors see en.wikipedia.org



5-10 Using Hall-Effect Sensors

The Hall-effect sensor is often used to solve difficult switching applications. Hall-effect sensors are magnetically activated sensors or switches. Hall-effect sensors are immune to environmental contaminants and are suitable for use under severe conditions. Hall-effect sensors operate reliably under oily and dirty, hot or cold, bright or dark, and wet or dry conditions.

Several examples of where Hall-effect sensors and switches might be used in a modern automobile are graphically summarized in Fig. 5-36. Hall-effect sensors and switches are also used in other applications such as ignition systems, security systems, mechanical limit switches, computers, printers, disk drives, keyboards, machine tools, position detectors, and brushless dc motor commutators.

Many of the advances in automotive technology revolve around accurate reliable sensors sending data to the central computer. The central computer gathers the sensor data and controls many functions of the engine and other systems of the automobile. The computer also gathers and stores data from the sensors to be used by the *on-board diagnostics* system (OBD I or the newer OBD II). Only some of the many sensors in an automobile are Hall-effect devices.

Basic Hall-Effect Sensor

The basic Hall-effect sensor is a semiconductor material represented in Fig. 5-37(a). A source voltage (bias voltage) will cause a constant bias current to flow through the Hall-effect sensor. As demonstrated in Fig. 5-37(a), when a magnetic field is present, a voltage is generated by the Hall-effect sensor. The Hall voltage is proportional to the strength of the magnetic field. As an example, if no magnetic field is present, then the sensor will produce no Hall-effect voltage at the output. As the magnetic field increases, the Hall voltage increases proportionally. In summary, if a biased Hall sensor is placed in a magnetic field, the voltage output

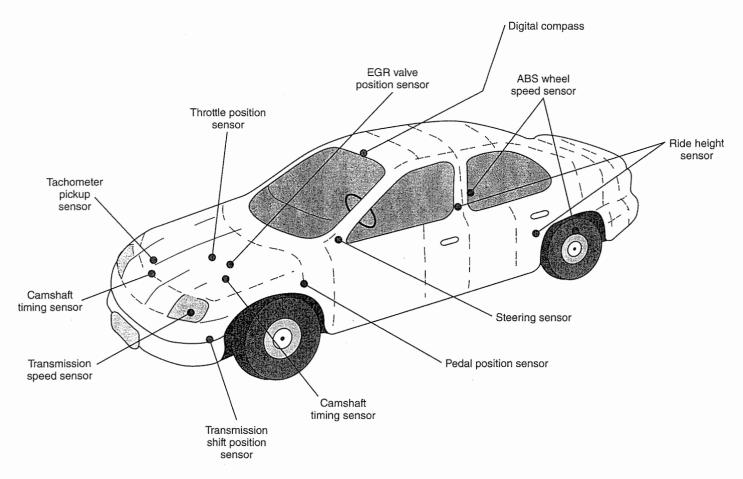


Fig. 5-36 Hall-effect sensors used in a modern automobile.

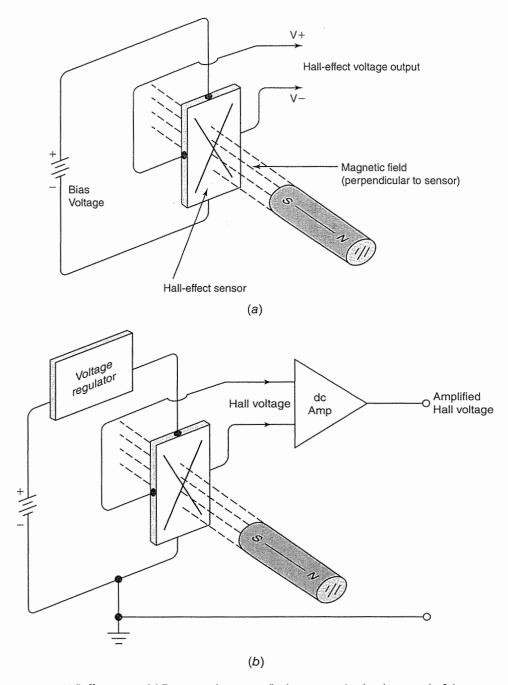


Fig. S-37 Hall-effect sensor. (a) Sensor produces a small voltage proportional to the strength of the magnetic field. (b) Adding a voltage regulator and dc amplifier to produce a more usable Hall-effect sensor.

will be directly proportional to the strength of the magnetic field. The Hall effect was discovered by E. F. Hall in 1879.


The output voltage of the Hall-effect sensor is small and is commonly amplified to be more useful. A Hall-effect sensor with a dc amplifier and voltage regulator is sketched in Fig. 5-37(b). The output voltage is linear and proportional to the strength of the magnetic field.

Hall-Effect Switch

Hall-effect devices are produced in rugged IC packages. Some are designed to generate a linear output voltage such as the sensor sketched in Fig. 5-37(b). Others are designed to operate as switches. A commercial Hall-effect switch is featured in Fig. 5-38. The Hall-effect switch detailed in Fig. 5-38 is the 3132 bipolar Hall-effect switch produced by Allegro Microsystems, Inc.



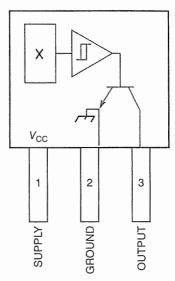For more information on Hall-effect sensors and switches, visit www .allegromicro.com.



Pinning is shown viewed from branded side.

(a)


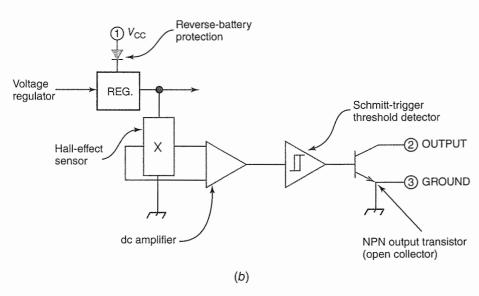


Fig. S-38 Allegro Microsystem's 3132 bipolar Hall-effect switch. (a) Pin diagram. (b) Functional block diagram.

The three-lead package in Fig. 5-38(a) shows that pins 1 and 2 are for connecting the external power supply (+ to V_{cc} and — to ground). Pin 3 is the output of this bounce-free switch. The pinout in Fig. 5-38(a) is correct when viewing the 3132 Hall-effect switch from the printed side (branded side) of the IC package. A functional block diagram of Allegro Microsystem's 3132 Hall-effect switch is drawn in Fig. 5-38(b). Notice that the symbol for the Hall-effect sensor is a rectangle with an X inside. Added to the sensor are several sections that convert the analog Hall-effect device into a digital switch. The *Schmitttrigger threshold detector* produces a snap-action

bounce-free output needed for digital switching. Its output is either HIGH or LOW. The open-collector output transistor is included so the IC can drive a load up to 25 mA continuously.

The two most important characteristics of a magnetic field are its *strength* and its *polarity* (south or north poles of the magnet). Both of these characteristics are used in the operation of the bipolar 3132 Hall-effect switch. To demonstrate the operation of the bipolar Hall-effect switch, study the circuit in Fig. 5-39(a) including the 3132 IC. An output indicator LED with 150- Ω limiting resistor has been added at the output of the IC.

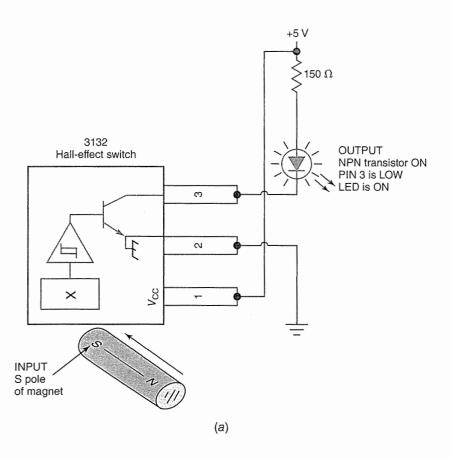

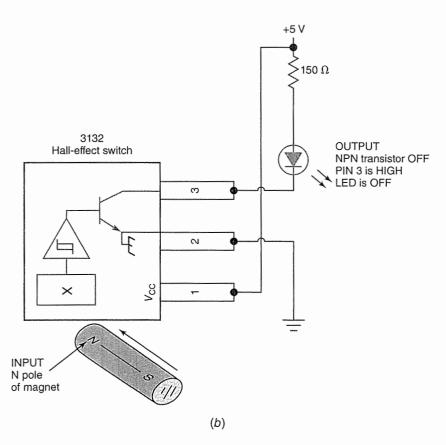


Fig. S-39 Controlling 3132 Hall-effect switch with opposite poles of a magnet. (a) Turning on switch with S pole. (b) Turning off switch with N pole.

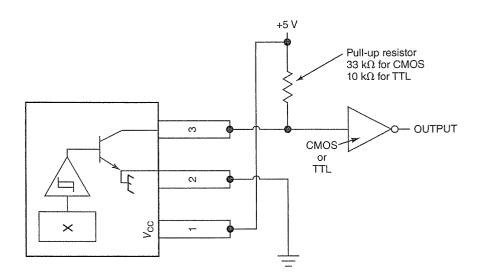


Fig. 5-40 Interfacing Hall-effect switch IC with either TTL or CMOS.

In Fig. 5-39(a), the south pole of the magnet approaches the branded side (side with printing) of the IC causing the internal NPN transistor to turn on. This causes pin 3 of the IC to drop LOW causing the LED to light.


In Fig. 5-39(b), the north pole of the magnet approaches the branded side (side with printing) of the IC causing the internal NPN transistor to turn off. This causes pin 3 of the IC to go HIGH, and the LED does not light.

The 3132 Hall-effect switch was bipolar because it required a S pole and then a N pole to make it toggle between ON and OFF. Unipolar Halleffect switches are also available which turn on and off by just increasing (switch on) and decreasing (switch off) the magnetic field strength and not changing polarity. One such unipolar Halleffect switch is the 3144 by Allegro Microsystems, Inc. The 3144 unipolar Hall-effect switch is Air gap a close relative the 3132 bipolar Hall-effect switch you have already studied. The unipolar 3144 IC shares the same pin-out diagram [Fig. 5-38(a)] and functional block diagram [Fig. 5-38(b)] as the bipolar 3132 Hall-effect switch. The 3144 Halleffect switch features a snap-action digital output. The 3144 IC also features an NPN output transistor that will sink 25 mA.

The Hall-effect switch IC drawn in Fig. 5-40 has an NPN driver transistor with an open collector. Interfacing a Hall-effect switch IC with digital ICs (TTL or CMOS) requires the use of a pull-up resistor as shown in Fig. 5-40. Typical values for the pull-up are shown as 33 k Ω for CMOS and $10~k\Omega$ for TTL. The Hall-effect switch shown in Fig. 5-41 Hall-effect gear-tooth sensor with rotating gear for Fig. 5-40 could be either the 3132 or 3144 ICs.

Gear-Tooth Sensing

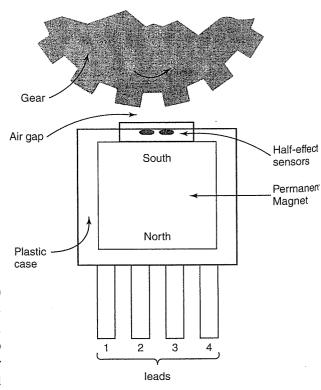Other common Hall-effect switching devices include gear-tooth sensing ICs. Gear-tooth sensing ICs contain one or more Hall-effect sensors and a built-in permanent magnet. A sketch of typical gear-tooth sensing IC and gear is shown in Fig. 5-41. The south pole of the permanent magnet produces a magnetic field that varies with the position of the gear. When a gear tooth moves



triggering.

into position to shorten the air gap, the field gets stronger and the Hall-effect sensor switches. Gear-tooth sensors are commonly used in mechanical systems including automobiles to count the position, rotation, and speed of gears.

It is a characteristic of Hall-effect switch ICs to function as a bounce-free switch. This is

sometimes difficult with mechanical switches. You will observe that the magnet does not have to touch the surface of the Hall-effect switch to turn it on and off. These are touch-free switches that can operate under severe environmental conditions. Simple Hall-effect switch ICs are small, rugged, and very inexpensive.

-₩-

Self-Test

Answer the following questions.

- 78. A Hall-effect sensor is a(n) _____ (magnetically, optically) activated device.
- 79. Hall-effect devices such a _____ (gear-tooth sensors, thermocouples) and switches are commonly used in automobiles because they are reliable, inexpensive, and can operate under severe conditions.
- 80. Refer to Fig. 5-42. The semiconductor material shown with the *X* on it is called the _____ (electromagnet, Hall-effect sensor).
- 81. Refer to Fig. 5-42. Moving the permanent magnet closer to the Hall-effect sensor increases the magnetic field causing the output voltage to ______ (decrease, increase).
- 82. Refer to Fig. 5-43. The 3132 Hall-effect IC is a _____ (bipolar, unipolar) switch.
- 83. Refer to Fig. 5-43(*a*). Output transistor of the IC is turned on and the output at pin 3 goes ______(HIGH, LOW)

- when the south pole of a magnet approaches the Hall-effect sensor in the 3132 causing the LED to ______ (light, not light).
- 84. Refer to Fig. 5-43(b). Output transistor of the IC is turned ______ (on, off) and the output at pin 3 goes _____ (HIGH, LOW) when the north pole of a magnet approaches the Hall-effect sensor in the 3132 causing the LED to not light.
- 85. Refer to Fig. 5-38. The snap action causing a digital output (either HIGH or LOW) from the IC is caused by the _____ (dc amplifier, Schmitt-trigger) section of the IC.
- 86. Hall-effect switches are small, bouncefree, rugged, and _____ (inexpensive, very expensive).
- 87. The open-collector of the NPN driver transistor used in both the 3132 and 3144 Hall-effect switches requires the use a _____ (pull-up, transition) resistor when sending digital signals to either CMOS or TTL logic devices.


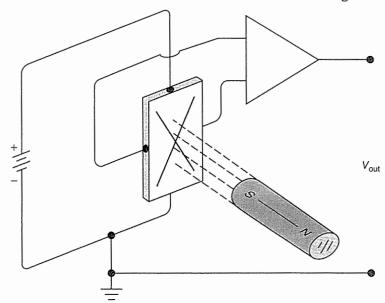


Fig. 5-42 Hall-effect sensor.

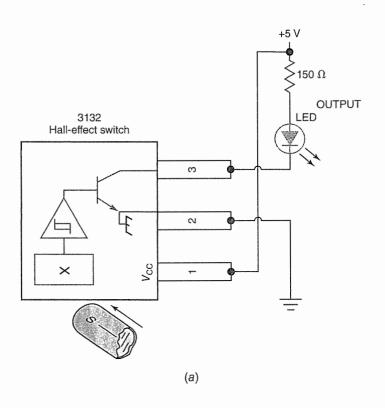

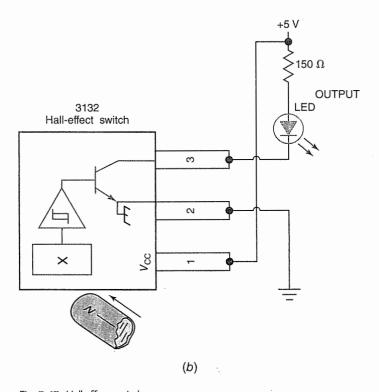


Fig. 5-43 Hall-effect switch.



5-11 Troubleshooting Simple Logic Circuits

One test equipment manufacturer suggests that about three-quarters of all faults in digital circuits occur because of open input or output circuits. Many of these faults can be isolated in a logic circuit using a logic probe.

Consider the combinational logic circuit mounted on a printed circuit board in Fig. 5-44(a). The equipment manual might include a schematic similar to the one shown in Fig. 5-44(b). Look at the circuit and schematic,

and determine the logic diagram. From that you can determine the Boolean expression and truth table. You will find that in this example, two NAND gates are feeding an OR gate. This is equivalent to the four-input NAND function.

The fault in the circuit in Fig. 5-44(a) is shown as an open circuit in the input to the OR gate. Now let's troubleshoot the circuit to see how we find this fault.

1. Set the logic probe to TTL, and connect the power.

Troubleshooting using a logic probe

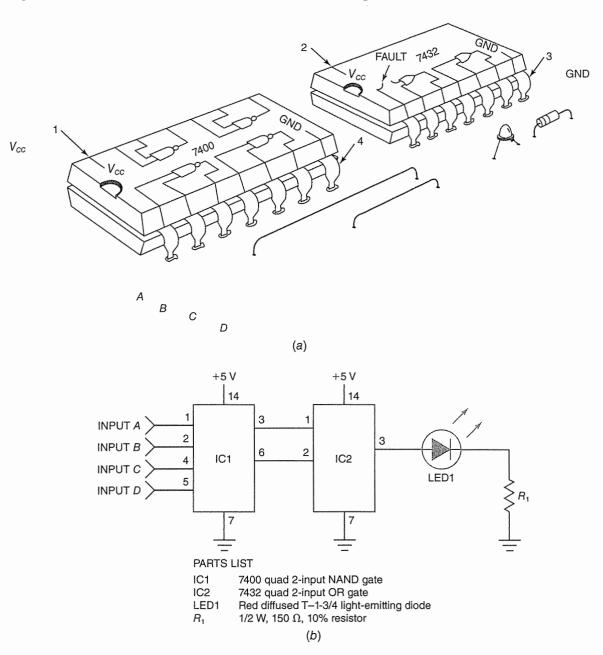


Fig. 5-44 Troubleshooting problem. (a) Testing a faulty circuit mounted on a PC board. (b) Schematic diagram of four-input NAND circuit.


- 2. Test nodes 1 and 2 [see Fig. 5-44(*a*)]. *Result*: Both are HIGH.
- 3. Test nodes 3 and 4. *Result:* Both are LOW. *Conclusion:* Both ICs have power.
- 4. Test the four-input NAND circuit's unique state (inputs *A*, *B*, *C*, and *D* are all HIGH). Test at pins 1, 2, 4, and 5 of the 7400 IC. *Results:* All inputs are HIGH, but the LED still glows and indicates a HIGH output. *Conclusion:* The unique state of the four-input NAND circuit is faulty.
- 5. Test the outputs of the NAND gates at pins 3 and 6 of the 7400 IC. *Results:* Both outputs are LOW. *Conclusion:* The NAND gates are working.
- 6. Test the inputs to the OR gate at pins 1 and 2 of the 7432 IC. *Results:* Both inputs are LOW. *Conclusion:* The OR gate inputs at pins 1 and 2 are correct, but the output is still incorrect. Therefore, the OR gate is faulty, and the 7432 IC needs to be replaced.

-W-

Self-Test

Supply the missing word in each statement.

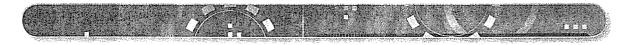- 88. Most faults in digital circuits occur because of ______ (open, short) circuits in the inputs and outputs.
- 89. A simple piece of test equipment, such as a(n) ______, can be used for checking
- a digital logic circuit for open circuits in the inputs and outputs.
- 90. Refer to Fig. 5-44. With inputs *A*, *B*, *C*, and *D* all HIGH, the output (pin 3 of IC2) should be _____ (HIGH, LOW).



5-12 Interfacing the Servo (BASIC Stamp Module)

Programmable devices are very common in modern digital electronics. This section will explore interfacing of the BASIC Stamp 2 Microcontroller Module with a simple servo.

Review Sec. 5-9 on servo motors. Hobby servo motor operation is summarized in Fig. 5-30. Notice the use of pulse-width modulation (PWM) to control the angular position of the servo motor. In this section, you will program a BASIC Stamp 2 (BS2) Microcontroller Module to act as the *PWM pulse generator* sketched in Fig. 5-30(*a*), (*b*), and (*c*). Notice in Fig. 5-30 that the positive pulse widths are 2 ms for fully CCW rotation, 1 ms for fully CW rotation, or 1.5 ms for centering of the servo's output shaft.

Consider the hobby servo motor connected to the BASIC Stamp 2 module in Fig. 5-45. This is a test circuit to rotate the servo (1) fully CCW, (2) fully CW, and (3) to finally center the output shaft.

The procedure for solving the logic problem with the use of the BASIC Stamp 2 module is

detailed below. The steps in wiring and programming the BASIC Stamp 2 module are:

- 1. Refer to Fig. 5-45. Wire the hobby servo motor to port P14 of the BASIC Stamp 2 module. Note the color coding (red = V_{dd} and black = V_{ss} or GND) of the power wires.
- 2. Load the PBASIC text editor program (version for the BS2 IC) into the PC. Type your PBASIC program describing the 'Servo Test 1. A PBASIC program titled 'Servo Test 1 is listed in Fig. 5-46.
- 3. Attach a serial cable (or USB cable) between the PC and the BASIC Stamp 2 development board (such as the Board of Education by Parallax, Inc.).
- 4. With the BASIC Stamp 2 module turned on, download your PBASIC program from the PC to BS2 module using the RUN command.
- 5. Disconnect the serial cable (or USB cable) from the BS2 module.
- 6. Observe the rotation of the servo output shaft. The PBASIC program stored in EEPROM program memory in the BASIC Stamp 2 module will restart each time the BS2 IC is turned on.

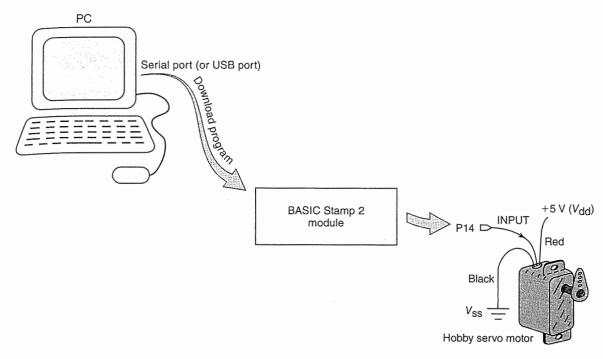


Fig. 5-45 Hobby servo motor connected to a BASIC Stamp 2 module for testing.

PBASIC Program — ServoTest 1

Consider in Fig. 5-46 the PBASIC program titled 'ServoTest 1. Lines 1 and 2 both begin with an apostrophe (') meaning these are *remark statements*. Remark statements are used

to clarify the program and are not executed by the microcontroller. Line 3 is a line of code to declare a variable that will be used later in the program As an example, line 3 reads C VAR Word. This tells the microcontroller that C is

'ServoTest 1 'Test servo in 3 different positi	'Title of program (See Fig. 5-45.) ons, CCW, CW and centered	L1 L2
C VAR Word	'Declare C as variable, 16-bit length	L3
FOR C = 1 TO 75 PULSOUT 14, 1000 PAUSE 20 NEXT	'Begin counting loop, C = 1 thru 75 'Pulse output (HIGH) at pin 14 for 2 ms 'Pause for 20 ms, output LOW 'Back to FOR if C < 75	L4 L5 L6 L7
FOR C = 1 TO 75 PULSOUT 14, 500 PAUSE 20 NEXT	'Begin counting loop, C = 1 thru 75 'Pulse output (HIGH) at pin 14 for 1 ms 'Pause for 20 ms, output LOW 'Back to FOR if C < 75	L8 L9 L10 L11
FOR C = 1 TO 75 PULSOUT 14, 750 PAUSE 20 NEXT	'Begin counting loop, C = 1 thru 75 'Pulse output (HIGH) at pin 14 for 1.5 ms 'Pause for 20 ms, output LOW 'Back to FOR if C < 75	L12 L13 L14 L15
END	보고 하는데 아이들의 전 사람들도 되는데 하는데 함께 살았다. 하다. 그리고 있다 그 보고 보고 있는데 얼마 하는데 보고 보고 보고 있다.	L16

Fig. 5-46 PBASIC program listing for ServoTest 1.

a variable name that will hold a word length value (16 bits). The 16-bit variable C can hold a range of values from 0 to 65535 in decimal.

Lines 4–7 produce the full CCW rotation of the servo motor shaft. The FOR-NEXT loop will be executed 75 times (C = 1 to 75). The PULSOUT 14, 1000 code (L5) generates a HIGH pulse at pin 14 for 2 milliseconds (2 $\mu seconds \times 1000 = 2000~\mu s = 2~ms$). Pin 14 then drops LOW after the 2-ms positive pulse. The PAUSE 20 code (L6) allows pin 14 to remain LOW for 20 ms. This first FOR-NEXT loop (L4–7) will cause the hobby servo motor to turn fully CCW.

Lines 8–11 produce the full CW rotation of the servo motor shaft. The FOR-NEXT loop will be executed 75 times (C=1 to 75). The PULSOUT 14, 500 code (L9) generates a HIGH pulse at pin 14 for 1 millisecond (2 μ seconds \times 500 = 1000 μ s = 1 ms). Pin 14 then drops LOW after the 1-ms positive pulse. The PAUSE 20 code (L10) allows pin 14 to remain LOW for 20 ms. This second FOR-NEXT

loop (L8–11) will cause the hobby servo motor to turn fully CW.

Lines 12–15 cause the servo motor shaft to center itself. The FOR-NEXT loop will be executed 75 times (C = 1 to 75). The PULSOUT 14, 750 code (L13) generates a HIGH pulse at pin 14 for 1.5 milliseconds (2 µseconds \times 750 = 1500 µs = 1.5 ms). Pin 14 then drops LOW after the 1.5-ms positive pulse. The PAUSE 20 code (L14) allows pin 14 to remain LOW for 20 ms. This last FOR-NEXT loop (L12–15) will cause the hobby servo motor shaft to move to the center of its range. The END statement (L16) causes the program to stop executing.

The PBASIC program 'ServoTest 1 will run once while the BS2 module is powered. The PBASIC program is held in EEPROM program memory for future use. Turning the BS2 off and then on again will restart the program. Downloading a different PBASIC program to the BASIC Stamp module will erase the old program and start execution of the new listing.

Salf-Test

Answer the following questions.

- 91. The angular position of a hobby servo motor is controlled by a technique called _____ (amplitude, pulse-width) modulation.
- 92. Refer to Fig. 5-46. Variable *C* may hold only a single bit of data. (T or F)
- 93. Refer to Fig. 5-46. Each of the three FOR-NEXT loops will be repeated _____ (20, 75) times.
- 94. Refer to Fig. 5-46. The purpose of the **PAUSE 20** statement is to permit the

- microcontroller to cool off for 20 minutes. (T or F)
- 95. Refer to Fig. 5-46. The **PULSOUT 14**, **750** output a positive pulse to pin 14 with a time duration of _____ millisecond(s).
- 96. Refer to Figs. 5-45 and 5-46. What is the effect on the servo's output shaft when the FOR-NEXT loop in lines 12–15 is totally executed (75 times through the loop)?



Chapter 5 Summary and Review



Summary

- 1. Interfacing is the design of circuitry between devices that shifts voltage and current levels to make them compatible.
- 2. Interfacing between members of the same logic family is usually as simple as connecting one gate's output to the next logic gate's input, etc.
- 3. In interfacing between logic families or between logic devices and the "outside world," the voltage and current characteristics are very important factors.
- 4. Noise margin is the amount of unwanted induced voltage that can be tolerated by a logic family. Complementary symmetry metal-oxide semiconductor ICs have better noise margins than TTL families.
- The fan-out and fan-in characteristics of a digital IC are determined by its output drive and input loading specifications.
- 6. Propagation delay (or speed) and power dissipation are important IC family characteristics.
- 7. The ALS-TTL, FAST (Fairchild advanced Schottky TTL), and FACT (Fairchild advanced CMOS technology) logic families are very popular owing to a combination of low power consumption, high speed, and good drive capabilities. Earlier TTL and CMOS families are still in use.
- 8. Advanced low-voltage CMOS ICs (such as the 74ALVC00 series) are used in many modern designs. These low-voltage CMOS ICs feature low power consumption, TTL direct interface, static protection, and very high speeds.
- Many CMOS ICs are sensitive to static electricity and must be stored and handled properly. Other precautions to be observed include turning off an input signal before circuit power and connecting all unused inputs.
- 10. Simple switches can drive logic circuits using pull-up and pull-down resistors. Switch debouncing is usually accomplished using latch circuits.

- 11. Driving LEDs and incandescent lamps with logic devices usually requires a driver transistor.
- 12. Most TTL-to-CMOS and CMOS-to-TTL interfacing requires some additional circuitry. This can take the form of a simple pull-up resistor, special interface IC, or transistor driver.
- 13. Interfacing digital logic devices with buzzers and relays usually requires a transistor driver circuit. Electric motors and solenoids can be controlled by logic elements using a relay to isolate them from the logic circuit.
- 14. Optoisolators are also called optocouplers. Solidstate relays are a variation of the optoisolator. Optoisolators are used to electrically isolate digital circuitry from circuits that contain motors or other high-voltage/current devices that might cause voltage spikes and noise.
- 15. Hobby servo motors are used for angular positioning of an output shaft. A pulse generator employing pulse-width modulation (PWM) is used to drive a these inexpensive servo motors.
- Hobby servo motors can be driven by programmable devices such as the BASIC Stamp 2 Microcontroller Module.
- 17. Stepper motors operate on dc and are useful in applications where precise angular positioning or speed of an output shaft is important.
- 18. Stepper motors are classified as either bipolar (two phase) or unipolar (four phase). Other important characteristics are step angle, voltage, current, coil resistance, and torque.
- 19. Specialized ICs are useful for interfacing and driving stepper motors. The logic section of the IC generates the correct control sequence to step the motor.
- 20. A Hall-effect sensor is a magnetically activated device used in Hall-effect switches. Hall-effect switches are classified as either bipolar (need S and N poles of magnet to activate) or unipolar (need S pole or no magnetic field to activate).

Summary...continued

- 21. External magnetic fields are commonly used to activate a Hall-effect sensor or switch. Gear-tooth sensors have Hall-effect sensors and a permanent magnet encapsulated in the IC. Hall-effect gear-
- tooth sensors are triggered by ferrous metals (such as steel gear teeth) passing near the IC.
- 22. Each logic family has its own definition of logical HIGH and LOW. Logic probes test for these levels.

		രണ്ടാ	IMIE
Answer	the following questions.	5-13.	Modern logic families such as the 74ALVC00 series feature (high-, low-)
5-1.	Applying 3.1 V to a TTL input is interpreted by the IC as a(n) (HIGH, LOW, undefined) logic level (5-V power source).		voltage operation, low power consumption, good static protection, and very
5-2.	A TTL output of 2.0 V is considered a(n) (HIGH, LOW, undefined) output	514	(high, low) propagation delays (for high-speed operation). The (CMOS, TTL) logic family has
<i>5</i> 2	(5-V power source).	J 1-1.	better noise immunity.
5-3.	Applying 2.4 V to a CMOS input (10-V power supply) is interpreted by the IC as a(n) (HIGH, LOW, undefined) logic level.	5-15.	Refer to Fig. 5-4. The noise margin for the TTL family is about V.
5-4.	Applying 3.0 V to a 74HC00 series CMOS	5-16.	Refer to Fig. 5-4. The noise margin for the CMOS family is about V.
	input (5-V power supply) is interpreted by the IC as a(n) (HIGH, LOW, undefined)	5-17.	Refer to Fig. 5-5. The switching threshold for
	logic level.	5 10	TTL is always exactly 1.4 V (T or F). The fan-out for standard TTL is said to be
5-5.	A "typical" HIGH output voltage for a TTL gate would be about (0.1, 0.8, 3.5) V.	J-10.	(10, 100) when driving other stan-
5-6.	A "typical" LOW output voltage for a TTL gate	£ 10	dard TTL gates.
	would be about (0.1, 0.8, 3.5) V.	5-19.	Refer to Fig. 5-6(<i>b</i>). A single ALS-TTL output will drive (5, 50) standard TTL
5-7.	A "typical" HIGH output voltage for a CMOS gate (10-V power supply) would be about		inputs.
	V.	5-20.	Refer to Fig. 5-6(b). A single 74HC00 series CMOS output has the capacity to drive at least
5-8.	A "typical" LOW output voltage for a CMOS gate (10-V power supply) would be about		(10, 50) LS-TTL inputs.
	V.	5-21.	Refer to Fig. 5-47. If both family <i>A</i> and <i>B</i> are TTL, the inverter (can, may not be
5-9.	Applying 3.0 V to a 74HCT00 series CMOS input (5-V power supply) is interpreted by the		able to) drive the AND gates.
	IC as a(n) (HIGH, LOW, undefined)	5-22.	Refer to Fig. 5-47. If family A is ALS-TTL
5 10	logic level.		and family <i>B</i> is standard TTL, the inverter (can, may not be able to) drive the
5-10.	Applying 1.0 V to a 74HCT00 series CMOS input (5-V power supply) is interpreted by the	5.0 0	AND gates.
	IC as a(n) (HIGH, LOW, undefined)	5-23.	Refer to Fig. 5-47. If both families <i>A</i> and <i>B</i> are ALS-TTL, the inverter (can, may
5-11	logic level. The 74ALVC series of logic ICs are modern		not be able to) drive the AND gates.
	(CMOS, TTL) chips.	5-24.	The (4000, 74AC00) series CMOS ICs have greater output drive capabilities.
5-12.	Applying 2.4 V to a 74ALVC00 series (3-V power supply) input would be interpreted by the	5-25.	Refer to Fig. 5-8(b). The logic
	IC as a(n) (HIGH, LOW, undefined)		family has the lowest propagation delays and is
	logic level.		considered the (fastest, slowest).

Chapter Review Questions...continued

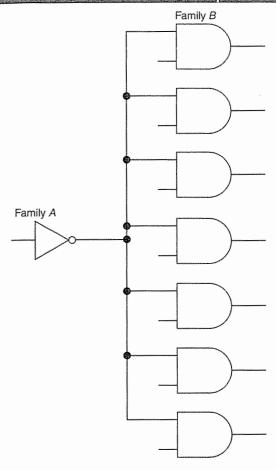


Fig. 5-47 Interfacing problem.

- 5-26. The 74FCT08 IC would have the same logic function and pin-out as the standard TTL IC with part number ______.
- 5-27. Generally, _____ (CMOS, TTL) ICs consume the least power.

- 5-28. List several precautions that should be observed when working with CMOS ICs.
- 5-29. The V_{DD} pin on a 4000 series CMOS IC is connected to _____ (ground, positive) of the dc power supply.
- 5-30. Refer to Fig. 5-11(*b*). With the switch open, the inverter's input is ______ (HIGH, LOW) while the output is _____ (HIGH, LOW).
- 5-31. Refer to Fig. 5-12(*a*). When the switch is open, the _____ resistor causes the input of the CMOS inverter to be pulled HIGH.
- 5-32. Refer to Fig. 5-48. Component R_1 is called a _____ resistor.
- 5-33. Refer to Fig. 5-48. Closing *SW*₁ causes the input to the inverter to go ______ (HIGH, LOW) and the LED ______ (goes out, lights).
- 5-34. Refer to Fig. 5-48. With SW_1 open, a ______ (HIGH, LOW) appears at the input of the inverter causing the output LED to _____ (go out, light).
- 5-35. The common switch debouncing circuits in Fig. 5-14(b) and (c) are called RS flip-flops or
- 5-36. Refer to Fig. 5-15. Closing input switch SW_1 causes the output of the 555 IC to toggle from _____ (HIGH to LOW, LOW to HIGH).
- 5-37. Refer to Fig. 5-15. Opening input switch SW_1 causes the output of the 555 IC to toggle from HIGH to LOW ______.
 - a. immediately
 - b. after a delay of about 1 second
 - c. after a delay of about 1 microsecond

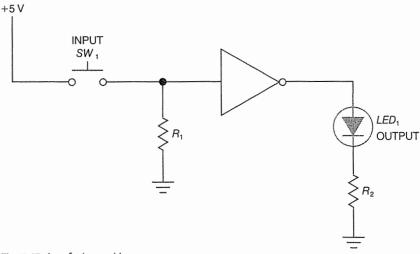


Fig. 5-48 Interfacing problem.

Chapter Review Questions...continued

- 5-38. A TTL output can drive a regular CMOS input with the addition of a(n) ______ resistor.
- 5-39. Any CMOS gate can drive at least one LS-TTL input. (T or F)
- 5-40. A 4000 series CMOS output can drive a standard TTL input with the addition of a(n)
- 5-41. Open-collector TTL gates require the use of _____ resistors at the outputs.
- 5-42. Refer to Fig. 5-25(b). The transistor functions as a(n) _____ (AND gate, driver) in this circuit.
- 5-43. Refer to Fig. 5-25(*b*). When the input to the inverter goes LOW, its output goes _____ (HIGH, LOW) which _____ (turns off, turns on) the transistor allowing current to flow through the transistor and piezo buzzer to sound the buzzer.
- 5-44. Refer to Fig. 5-27(a). When the input to the inverter goes LOW, its output goes HIGH which ______ (turns off, turns on) the NPN transistor; the coil of the relay is ______ (activated, deactivated), the relay armature clicks downward, and the dc motor ______ (rotates, will not rotate).
- 5-45. Refer to Fig. 5-27(b). When the input to the inverter goes HIGH, its output goes LOW which ______ (turns off, turns on) the NPN transistor; the coil of the relay is _____ (activated, deactivated), the armature of the relay _____ (clicks, will not click) downward, and the solenoid _____ (is, will not be) activated.
- 5-46. Refer to Fig. 5-28. The 4N25 optoisolator contains a gallium arsenide _____ (infrared-emitting diode, incandescent lamp) optically coupled to a phototransistor output.
- 5-47. Refer to Fig. 5-28(*b*). If the input to the inverter goes HIGH, its output goes LOW which ______ (activates, deactivates) the LED, the phototransistor is ______ (turned off, turned on), and the output voltage goes ______ (HIGH, LOW).
- 5-48. Refer to Fig. 5-28(*c*). The piezo buzzer sounds when the input to the inverter goes _____ (HIGH, LOW).
- 5-49. Refer to Fig. 5-28(d). This is an example of good design practice by using an optoisolator to

- isolate the low-voltage digital circuit from the higher-voltage noisy motor circuit. (T or F)
- 5-50. Refer to Fig. 5-28(*d*). The dc motor turns on when a _____ (HIGH, LOW) logic level appears at the input of the inverter.
- 5-51. A solid-state relay is a close relative of the optoisolator. (T or F)
- 5-52. The electromagnetic device well suited to continuous rotation in either direction is the _____ (dc motor, hobby servo motor).
- 5-53. Refer to Fig. 5-49. The pulse generator will vary the _____ causing the servo motor to adjust the angular position of the output shaft.
 - a. Frequency from about 30 to 100 Hz
 - b. Pulse width from about 1 to 2 ms
 - c. Pulse amplitude from about 1 to 5 V
- 5-54. A ______ (dc motor, stepper motor) should be used when the application calls for exact angular positioning of a shaft (as in a robot wrist).
- 5-55. The stepper motor sketched in Fig. 5-31(*a*) is classified as a unipolar or four-phase unit. (T or F)
- 5-56. The device featured in Fig. 5-31 is a ______ (permanent magnet, variable reluctance) type stepper motor.
- 5-57. The step angle for the stepper motor in Fig. 5-31(a) is ______ degrees.
- 5-58. The control sequence shown in Fig. 5-32(*a*) is for a _____ (bipolar, unipolar) stepper motor.
- 5-59. Refer to Fig. 5-33(*a*). How is the MC3479 IC described by its manufacturer?
- 5-60. Refer to Fig. 5-33(*a*) and assume pins 9 and 10 of the MC3479 IC are LOW. When a single

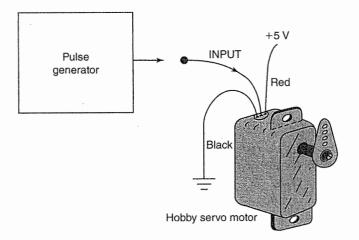


Fig. 5-49 Driving a servo motor.

Chapter Review Questions...continued

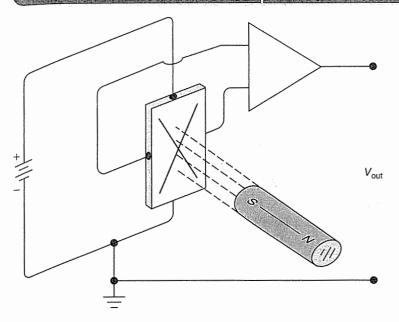


Fig. 5-50 Art for chapter review questions 5-64, 5-65, and 5-69.

- clock pulse enters the CLK input (pin 7), the stepper motor rotates a ______ (full step, half step) in the _____ (CCW, CW) direction.
- 5-61. Refer to Fig. 5-33(a) and assume pins 9 and 10 of the MC3479 IC are HIGH and the stepper motor has a step angle of 18°. Under these conditions, how many clock pulses must enter the CLK input to cause the stepper motor to rotate one revolution?
- 5-62. The Hall-effect sensor is a _____ (magnetically, pressure-) activated device.
- 5-63. Hall-effect devices such as gear-tooth sensors and switches are commonly used in automobiles because they are rugged, reliable, operate under severe conditions, and are inexpensive. (T or F)
- 5-64. Refer to Fig. 5-50. The sections of this Hall-effect device are the Hall-effect sensor, the bias battery, and a ______ (dc amplifier, multiplexer).
- 5-65. Refer to Fig. 5-50. Moving the magnet closer to the Hall-effect sensor increases the strength of the magnetic field which causes the output voltage to ______ (decrease, increase).
- 5-66. Refer to Fig. 5-51. If the Hall-effect IC uses unipolar switching, then increasing the magnetic field by moving the south pole of the magnet toward the sensor will turn the switch _____ (off, on), while removing the permanent magnet

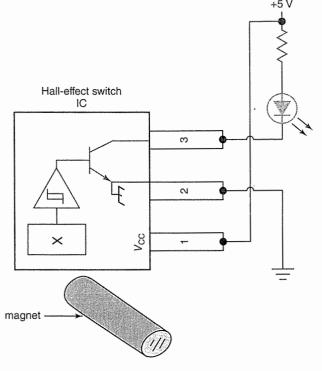


Fig. 5-51 Art for chapter review questions 5-66, 5-67, 5-68, and 5-70.

- completely will turn the switch _____ (off, on).
- 5-67. Refer to Fig. 5-51. If the IC is the bipolar 3132 Hall-effect switch, then the ______ (N, S) pole of the magnet will turn the device on while the ______ (N, S) pole will turn the output transistor off.
- 5-68. Refer to Fig. 5-51. If the IC is the bipolar 3132 Hall-effect switch, then moving the north pole of the magnet near the sensor will turn _____ (off, on) the switch, the voltage at pin 3 will _____ (drop LOW, raise HIGH), and the LED will _____ (light, not light).
- 5-69. Refer to Fig. 5-50. The output of this device is _____ (analog, digital) in nature.
- 5-70. Refer to Fig. 5-51. The output of this IC is _____ (analog, digital) in nature.
- 5-71. Refer to Fig. 5-45. The BASIC Stamp 2
 ______ (Audio-amplifier, Microcontroller)
 Module substitutes as a PWM generator to rotate the servo motor.
- 5-72. In Parallax's PBASIC language, the statement **PULSOUT 14, 750** generates 14 negative pulses each 750 µs. (T or F)

Critical Thinking Questions

- 5-1. How would you define interfacing?
- 5-2. How do you define *noise* in a digital system?
- 5-3. What is the propagation delay of a logic gate?
- 5-4. List several advantages of CMOS logic elements.
- 5-5. Why might a design engineer use the 74ALVC00 series of logic ICs for a new tiny handheld device?
- 5-6. Refer to Fig. 5-45. If family *A* is standard TTL and family *B* is ACT-CMOS, the inverter _____ (can, may not be able to) drive the AND gates.
- 5-7. Refer to Fig. 5-18(*c*). Explain the operation of this HIGH-LOW indicator circuit.
- 5-8. What is the purpose of "T"-type CMOS ICs (HCT, ACT, etc.)?
- 5-9. What electromechanical device could be used to isolate higher-voltage equipment (such as motors or solenoids) from a logic circuit?
- 5-10. An electric motor converts electric energy into motion.
- 5-11. A(n) ______ is an electromechanical device that converts electric energy into linear motion.
- 5-12. Why is the FACT-CMOS series considered by many engineers to be one of the best logic families for new designs?
- 5-13. Refer to Fig. 5-26. Explain the circuit action when the inverter input is LOW.
- 5-14. Refer to Fig. 5-27(*a*). Explain the circuit action when the inverter input is HIGH.
- 5-15. An optoisolator prevents the transmission of _____ (the signal, unwanted noise) from one electronic system to another that operates on a different voltage.
- 5-16. Refer to Fig. 5-28(*d*). Explain the circuit action when the inverter input is LOW.
- 5-17. If the coil resistance of a 12-V stepper motor is 40 Ω , what is the current draw for the coil?

- 5-18. If a stepper motor is designed with a step angle of 3.6°, how many steps are required for one revolution of the motor?
- 5-19. Why are Hall-effect devices such as switches and gear-tooth sensors so widely used in modern automobiles?
- 5-20. Explain what we mean by current sinking.
- 5-21. What is PWM, and how is it used to drive a hobby servo motor?
- 5-22. Refer to Fig. 5-33(*c*). What do you notice as you progress down the control sequence for a stepper motor (*Hint*: Direction of current flow through windings)?
- 5-23. Refer to Fig. 5-38(*b*). What is the purpose of the Schmitt trigger in the Hall-effect switch?
- 5-24. Refer to Fig. 5-38(*b*). The output of the driver transistor in this IC is the _____ (open-collector, totem-pole) type.
- 5-25. Describe the difference between the operation of a bipolar and a unipolar Hall-effect switch.
- 5-26. Design circuits including the following interfaces: switches with TTL ICs; LEDs with TTL and CMOS ICs; TTL and CMOS ICs; and CMOS ICs with buzzers, relays, and motors.
- 5-27. How would you use an optoisolator to interface between TTL ICs and higher-voltage devices (buzzer and motor)?
- 5-28. Describe interfacing with a stepper motor.
- 5-29. How would you apply Hall-effect switches (both bipolar and unipolar) to drive a CMOS counter IC?
- 5-30. Describe using a pulse-width modulator (PWM) to control a servo motor.
- 5-31. Design and demonstrate a TTL logic block that controls a stepper motor driver IC and stepper motor.
- 5-32. Describe driving a servo motor using a microcontroller (BASIC Stamp 2 system).



Answers to Self-Tests

- 1. interfacing
- 2. HIGH
- 3. LOW

- 4. undefined
- 5. undefined
- 6. +10

- 7. HIGH
- 8. CMOS
- 9. T
- 10. CMOS
- 11. low-voltage
- 12. HIGH
- 13. fan-out
- 14. FAST TLL series
- 15. 20 (8 mA/400
 - $\mu A = 20$)
- 16. long
- 17. FACT series CMOS
- 18. the same
- 19. MOS
- 20. complementary symmetry metal-oxide semiconductor
- 21. low power consumption
- 22. GND
- 23. positive
- 24. FACT
- 25. T
- 26. CMOS
- 27. very
- 28. T
- 29. LOW, floats HIGH
- 30. pull-up
- 31. RS flip-flop
- 32. HIGH, LOW
- 33. F
- 34. switch debouncing circuit
- 35. open collector
- 36. LOW to HIGH
- 37. C
- 38. decreasing
- 39. 4000
- 40. goes out
- 41. off, does not light
- 42. Q_1 , red
- 43. active LOW
- 44. sinking current
- 45. LOW
- 46. are not
- 47. pull-up
- 48. current drive
- 49. transistor
- 50. is not

- 51. on, sounds
- 52. transient voltages
- 53. HIGH
- 54. linear
- 55. isolate
- 56. turns on
- 57. NC to the NO
- 58. relay
- 59. phototransistor
- 60. lights, activates, LOW
- 61. pull-up
- 62. does not light, deactivates, HIGH, does not sound
- 63. turns on, runs
- 64. solid-state
- 65. will sound
- 66. dc motor
- 67. stepper motor
- 68. T
- 69. servo motor
- 70. input
- 71. pulse-width
- 72. bipolar
- 73. control, bipolar
- 74. CCW
- 75. logic
- 76. 350
- 77. CCW, half step
- 78. magnetically
- 79. gear-tooth sensors
- 80. Hall-effect sensor
- 81. increase
- 82. bipolar
- 83. LOW, light
- 84. OFF, HIGH
- 85. Schmitt-trigger
- 86. inexpensive
- 87. pull-up
- 88. open
- 89. logic probe or voltmeter
- 90. LOW
- 91. pulse-width
- 92. F
- 93. 75
- 94. F
- 95. 1.5
- 96. rotates to the center of its range





Encoding, Decoding, and Seven-Segment Displays

Learning Outcomes

This chapter will help you to:

- **6-1** *Convert* decimal numbers to BCD code and BCD to decimal.
- **6-2** *Identify* the characteristics and applications of several commonly used codes.
- **6-3** Compare decimal numbers with excess-3 code, Gray code, and 8421 BCD code.
- **6-4** Interpret the operation of a 4-bit Gray code shaft encoder using optical encoding. Understand the use of a 2-bit quadrature encoder in determining direction of shaft rotation.
- **6-5** Convert ASCII code to letters and numbers, and convert characters to ASCII code.
- 6-6 Demonstrate detailed understanding of an encoder (74147 decimal-to-BCD encoder IC).

 Interpret operational details from truth tables, pin-outs, and logic diagrams (74147 encoder IC).
- **6-7** Describe the construction of several lightemitting diode (LED) displays. Test the operation of a seven-segment LED.
- **6-8** Demonstrate understanding of typical decoders including a BCD-to-seven-segment decoder/ driver.
- 6-9 Interpret operational details from truth tables, pin-outs, and logic diagrams (7447 BCD-to-seven-segment decoder/driver IC). Wire a 7447 decoder/driver to a common-anode seven-segment LED display.
- 6-10 Describe the construction and operation of a liquid-crystal display (LCD). Identify operational details of a CMOS decoder/driver system used to drive an LCD. Demonstrate understanding of color LCDs by answering selected questions.
- 6-11 Interpret operational details from truth table, pinouts, and logic diagrams (74HC4543 BCD-to-seven-segment latch/decoder/driver IC for driving an LCD). Explain the functioning of the CMOS decoder/latch/driver IC interfaced with a LCD.
- **6-12** *Describe* the construction and operation of a vacuum fluorescent (VF) display.
- 6-13 Interpret operational details from truth table, pin outs, and logic diagrams (CMOS 4511 BCD-to-seven-segment latch/decoder/driver IC). Explain the functioning of the CMOS latch/decoder/driver IC interfaced with a VF display.
- **6-14** Troubleshoot two faulty decoder/driver seven-segment display circuits.

sent numbers. Digital electronic circuits use various forms of binary. Many special codes are used in digital electronics to represent numbers, letters, punctuation marks, and control characters. This chapter covers several common codes used in digital electronic equipment. Electronic translators, which convert from one code to another, are widely used in digital electronics. This chapter introduces you to several common encoders and decoders used for translating from code to code.

In modern electronic systems, the encoding and decoding may be performed by hardware or by computer programs or software. In computer jargon, to encrypt means to encode. So an encoder is an electronic device that translates from decimal to an encrypted code (such as binary) which is not as easy to interpret. In general, to encode means to convert input information to a code useful to digital circuitry.

In general, to *decode* means to translate from one code to another. In common use, a *decoder* would be a logic device that translates from an encrypted code into a code that is more understandable. An example of decoding would be to translate from binary to decimal.

6-1 The 8421 BCD Code

How would you represent the decimal number 926 in binary form? In other words, how would you convert 926 to the binary number 1110011110? The decimal-to-binary conversion

would be done using the repeated divide- by-2 method illustrated in Fig. 6-1.

Following the repeated divide-by-2 process shown in Fig. 6-1, recall that the decimal number 926 is first divided by 2 yielding a quotient of 463 with a remainder of 0. The remainder of 0 becomes the least significant bit (LSB is the 1s place) in the binary number. Next the first quotient is divided-by-2 yielding 231 (463/2 = 231) with a remainder of 1. This remainder of 1 holds the 2s place in the binary number. This process is continuous until the quotient becomes 1. When the quotient becomes 0 the process is complete. Studying Fig. 6-1 will help refresh your memory about the repeated divide-by-2 process used to convert a decimal number to its binary equivalent.

The binary number 1110011110 does not make much sense to most of us. A code that uses binary in a different way from the preceding example is called the 8421 binary-coded decimal code. This code is frequently referred to as just the BCD code.

The decimal number 926 is converted to the BCD (8421) code in Fig. 6-2(a). The result is that the decimal number 926 equals 1001 0010 0110 in the 8421 BCD code.



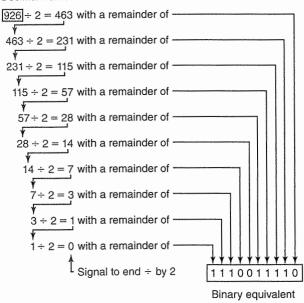


Fig. 6-1 Converting decimal to binary numbers using the repeated divide-by-2 method.

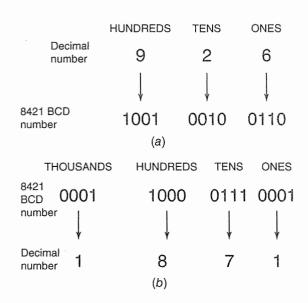


Fig. 5-2 (a) Converting from decimal to 8421 BCD code. (b) Converting from BCD to decimal.

Converting from decimal to 8421 BCD code

Converting from BCD to decimal

Notice from Fig. 6-2(a) that each group of four binary digits represents a decimal digit. The right group (0110) represents the 1s place value in the decimal number. The middle group (0010) represents the 10s place value in the decimal number. The left group (1001) represents the 10os place value in the decimal number.

Suppose you are given the 8421 BCD number 0001 1000 0111 0001. What decimal number does this represent? Figure 6-2(b) shows how you translate from the BCD code to a decimal number. We find that the BCD number 0001 1000 0111 0001 is equal to the decimal number 1871. The 8421 BCD code does not use the numbers 1010 1011 1100 1101 1110 1111. These are considered invalid numbers.

The 8421 BCD code is very widely used in digital systems. As pointed out, it is common practice to substitute the term "BCD code" to mean the 8421 BCD code. A word of caution, however: Some BCD codes do have different weightings of the place values, such as the 4221 code and the excess-3 code. If seven-segment displays need to show decimal digits 0 through 9, the BCD code is a good choice.

BCD code

Converting decimal to binary numbers

Supply the missing number in each statement.

- 1. The decimal number 29 is the same as _____ in binary.
- 2. The decimal number 29 is the same as _____ in the 8421 BCD code.
- 3. The 8421 BCD number 1000 0111 0110 0101 equals ______ in decimal.
- 4. The ______ (ASCII, 8421 BCD) code would be the preferred output from the counter shown in Fig. 6-3.
- 5. Refer to Fig. 6-3. If the output from the counter is 0111 1001_{BCD} entering the decoders, what will the seven-segment displays read?
- 6. Refer to Fig. 6-3. If the seven-segment displays read decimal 85, then the BCD code between the counter and decoders is
- 7. Refer to Fig. 6-3. If the seven-segment displays read decimal 81, then the BCD code between the counter and decoders will be 0101 0001. (T or F)

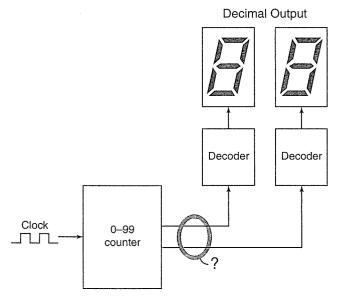


Fig. 6-3 Two-digit counter with decimal output.



6-2 The Excess-3 Code

The term "BCD" is a general term, usually referring to an 8421 code. Another code that is really a BCD code is the *excess-3 code*. To convert a decimal number to the excess-3 form, we *add 3 to each digit of the decimal number* and convert to binary form. Figure 6-4 shows how the decimal number 4 is converted to the excess-3 code number 0111. Some decimal numbers are converted to excess-3 code in Table 6-1. You probably have noticed that the excess-3 code for decimal numbers is rather difficult to figure out. This is because the binary digits are not weighted as they are in

regular binary numbers and in the 8421 BCD code. The excess-3 code is used in some arithmetic circuits because it is self-complementing.

The 8421 and excess-3 codes are but two of many BCD codes used in digital electronics. The 8421 code is by far the most widely used BCD code.

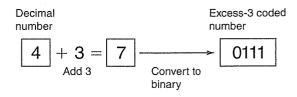


Fig. 6-4 Converting a decimal number to the excess-3 code.

Excess-3 code

Converting a decimal number to the excess-3 code



Self-Test

Supply the missing number in each statement.

- 8. The decimal number 18 equals ______in excess-3 code.
- 9. The excess-3 code number 1001 0011 equals ______ in decimal.



Table 64	The Excess 8	Code		Table 6-2	The Gray	Bule :		
Decimal Number		Excess-3 Number		Decimal Number	Binary Number		8421 BCD Number	Gray Code Number
0			0011	0	0000		0000	0000
1			0100	1	0001		0001	0001
2			0101	2	0010		0010	0011
3			0110	3	0011		0011	0010
4			0111	4	0100		0100	0110
5			1000	5	0101		0101	0111
6			1001	6	0110		0110	0101
7			1010	7	0111		0111	0100
8			1011	8	1000		1000	1100
9			1100	9	1001		1001	1101
14		0100	0111	10	1010	0001	0000	1111
27		0101	1010	11	1011	0001	0001	1110
38		0110	1011	12	1100	0001	0010	1010
459	0111	1000	1100	13	1101	0001	0011	1011
606	1001	0011	1001	14	1110	0001	0100	1001
	Hundreds	Tens	Ones	15	1111	0001	0101	1000
ACASCANICAL ACCIONA				16	10000	0001	0110	11000
				17	10001	0001	0111	11001

6-3 The Gray Code

Table 6-2 compares the *Gray code* with some codes you already know. The important characteristic of the Gray code is that only *one bit changes* as you *count* from top to bottom, as shown in Table 6-2. The Gray code cannot be used in arithmetic circuits. The Gray code is used for input and output devices in digital systems. You can see from Table 6-2 that the Gray code is not classed as one of the many BCD codes. Also notice that it is quite difficult to translate from decimal numbers to the Gray code and back to decimals again. There is a method for making this conversion, but we usually use electronic decoders to do the job for us.

Shaft Encoder

The Gray code, which was invented by Frank Gray of Bell Labs, is commonly associated with the *optical encoding* of a shaft's angular position. A simple example of this idea is sketched in Fig. 6-5. The encoder disk is attached to a shaft. The lighter areas of the disk represent transparent areas; the darker areas are opaque. A light source (usually infrared) shines from above the disk, and light detectors are positioned below. The disk is free to rotate while the light sources and detectors stay in their position.

Gray code

Optical encoding

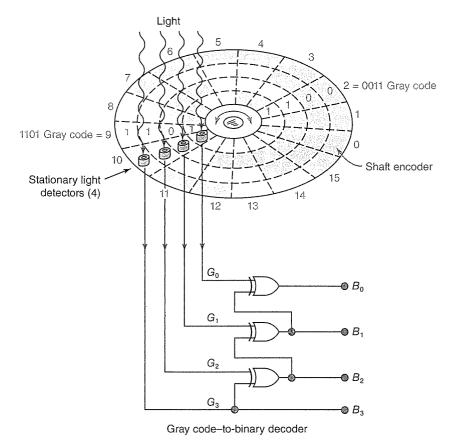


Fig. 6-5 Gray code used on shaft encoder to determine angular position of shaft.

In the example shown in Fig. 6-5, light passes through all four transparent areas activating all four light detectors. In this example the detectors send the Gray code 1111 to the Gray code—to-binary decoder. The decoder translates Gray code to binary. As this is only a 4-bit shaft position encoder disk, the resolution is only 1 of 16. It can only detect a change in angular shaft position each 22.5° ($360^{\circ}/16 = 22.5^{\circ}$). The encoder disk in Fig. 6-5 serves to show how shaft positioning might be accomplished using the Gray code.

In Fig. 6-5, each of the four stationary light detectors located below the *shaft encoder* generates a HIGH (logical 1) when light strikes the photosensitive detector. In this example, the shaft encoder disk is rotated so all detectors receive light and are activated (emit a logical 1). Gray code 1111 equals segment 10₁₀. The Gray code—to-binary decoder in Fig. 6-5 would convert the Gray code 1111 to binary 1010.

The purpose of the shaft encoder is to locate the angular position of a shaft or wheel as might be required in a robot, machine tool, or servomechanism. In Fig. 6-5, imagine if the shaft encoder rotated 90 degrees counterclockwise

so segment 6 was over the light detectors. The four segment 6 windows (opaque, transparent, opaque, and transparent) would cause the light detectors to generate the Gray code 0101. The Gray code—to-binary decoder would translate Gray code 0101 to binary 0110. The angular position would be used in a processing unit (such as a microcontroller) to aid the operation of a robot or machine tool.

The shaft encoder may be built into a motor, gear, or wheel. The shaft encoder will probably be divided into many more segments. More segments mean that the Gray code number will consist of many more digits. Devices called *absolute encoders* use Gray code to determine angular position.

Quadrature Encoder

The shaft encoder demonstrated in Fig. 6-5 employed the Gray code to determine angular position of a shaft. In robotics and other electromechanical devices the direction of rotation of a shaft must be signaled to the processing unit (such as a microcontroller). A simple 16-position rotary encoder is sketched in Fig. 6-6. Its output is a form of Gray code called 2-bit quadrature.

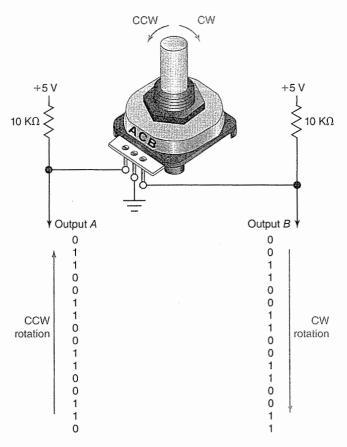


Fig. 6-6 Rotary encoder generating a 2-bit quadrature code. Code in chart is for one rotation of the encoder.

A diagram of how the encoder might be connected to generate the 2-bit quadrature code is shown in the lower section of Fig. 6-6. Notice that the output exhibits the Gray code characteristic that only one bit changes as we step down (or up) the chart.

The rotary encoder's direction of rotation can be determined from the 2-bit code that is generated. In Fig. 6-6, first imagine that you are nine lines down on the chart (00) and the output goes to $10 \ (A = 1 \ \text{and} \ B = 0)$. From the chart you would know that the shaft was rotated one position clockwise (CW). Second, imagine

that you are five lines down on the chart (00) and the output goes to 01 (A = 0 and B = 1). From the chart you would know that the shaft was rotated one position counterclockwise (CCW). A processor such as a microcontroller would be programmed to decide the direction of rotation of the shaft of the encoder.

In summary, you have observed a 4-bit Gray code being used with a shaft encoder to determine the angular position of a shaft. Second, you analyzed the 2-bit quadrature code output from a rotary encoder to determine the direction of rotation of rotary encoder.

-\r-\ Self-Tesi

- 10. The Gray code _____ (is, is not) a BCD-type code.
- 11. What characteristic is most important about the Gray code?
- 12. The inventor of the Gray code was _____ of Bell Labs.
- 13. The Gray code is most commonly associated with ______ of a shaft's angular position using a shaft encoder.

- 14. Refer to Fig. 6-5. The transparent areas of the encoder disk permit light to activate the light detectors generating a _____ (HIGH, LOW) logic level.
- 15. Refer to Fig. 6-5. If segment 7 were rotated under the light detectors, the shaft encoder would generate a Gray code of _______ [4 bits] which is decoded to binary 0111.
- 16. Refer to Fig. 6-6. The 16-position rotary encoder generates a ______ (4-bit Gray code, 2-bit quadrature code).
- 17. Refer to Fig. 6-6. Imagine that you are three lines down on the chart (11) and the output goes to A = 0 and B = 1. From the chart you find that the shaft rotated in a _____ (CCW, CW) direction.



6-4 The ASCII Code

The ASCII code is widely used to send information to and from microcomputers. The standard ASCII code is a 7-bit code used in transferring coded information from keyboards and to computer displays and printers. The abbreviation ASCII (pronounced "ask-ee") stands for the *American Standard Code for Information Interchange*.

Table 6-3 is a summary of the ASCII code. The ASCII code is used to represent numbers, letters, punctuation marks, as well as control characters. For instance, the 7-bit ASCII code 111 1111 stands for DEL from the top chart. From the bottom chart we see that DEL means delete.

What is the coding for "A" in ASCII? Locate A on the top chart in Table 6-3. Assembling the

7-bit code gives 100 0001 = A. This is the code you would expect to be sent to a micro-computer's CPU if you pressed the A key on the keyboard.

Some care must be used in applying Table 6-3 to specific equipment. Be aware that the shaded control characters may have other meanings on specific computers or other equipment. However, common control characters such as BEL (bell), BS (backspace), LF (line feed), CR (carriage return), DEL (delete), and SP (space) are used on most computers. The exact meaning of the ASCII control codes should be looked up in your equipment manual.

The ASCII code is an *alphanumeric code*. It can represent both letters and numbers. Several other alphanumeric codes are *EBCDIC* (extended binary-coded decimal interchange code), *Baudot*, and *Hollerith*.

American Standard Code for Information Interchange


Alphanumeric code EBCDIC

Baudot

Hollerith



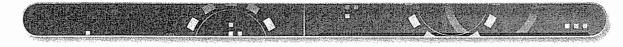- 18. ASCII is classified as a(n) _____ code because it can represent both numbers and letters.
- 19. The letters ASCII stand for _____
- 20. The letter R is represented by the 7-bit ASCII code _____.
- 21. The ASCII code 010 0100 represents what character?



ASCII code

Tabl	e 6 G	The AS		je										
						→	0	0	0	0	1	1	1	1
						>	0	0	1	1	0	0	1	1
V	\downarrow	√				→	0	1	0	1	0	1	0	1
Bit	Bit	Bit	Bit	Bit	Bit	Bit								
7	6	5	4	3	2	1								
			0	0	0	0	NUL	DLE	SP	0	@	Р	\	Р
			0	0	0	1	SOH	DC1	!	1	Α	Q	а	q
			0	0	1	0	STX	DC2	rt	2	В	R	b	r
			0	0	1	1	ETX	DC3	#	3	С	S	С	S
			0	1	0	0	EOT	DC4	\$	4	D	Т	d	t
			0	1	0	1	ENQ	NAK	%	5	Е	U	е	u
			0	1	1	0	ACK	SYN	&	6	F	٧	f	٧
			0	1	1	1	BEL	ETB	,	7	G	W	g	w
			1	0	0	0	BS	CAN	(8	Н	Х	h	х
			1	0	0	1	HT	EM)	9		Υ	i	У
			1	0	1	0	LF	SUB	*	:	J	Z	j	z
			1	0	1	1	VT	ESC	+	;	К	[k	1
			1	1	0	0	FF	FS	,	<	L	١	ı	ı
			1	1	0	1	CR	GS	_	=	М]	m	}
			1	1	1	0	so	RS	•	>	N	۸	n	~
		***	1	1	1	1	S1	US	1	?	0		0	DEL

- 35	361	149	SE.	m		œ	35	150	т	8	54,	œ
4				12	3	Ħ	•		П	п		
-		- 8	ш		-		25	•	ы	ы	ш	~

NUL	Null	DLE	Data link escape
SOH	Start of heading	DC1	Device control 1
STX	Start of text	DC2	Device control 2
ETX	End of text	DC3	Device control 3
EOT	End of transmission	DC4	Device control 4
ENQ	Enquiry	NAK	Negative acknowledge
ACK	Acknowledge	SYN	Synchronous idle
BEL	Bell	ЕТВ	End of transmission block
BS	Backspace	CAN	Cancel
HT	Horizontal tabulation (skip)	EM	End of medium
LF	Line feed	SUB	Substitute
VT	Vertical tabulation (skip)	ESC	Escape
FF	Form feed	FS	File separator
CR	Carriage return	GS	Group separator
SO	Shift out	RS	Record separator
SI	Shift in	US	Unit separator
DEL	Delete	SP	Space

6-5 Encoders

A digital system using an *encoder* is shown in Fig. 6-7. The encoder in this system must translate the decimal input from the keyboard to an 8421 BCD code. This encoder is called a *10-line-to-4-line priority encoder* by the manufacturer. Figure 6-8(a) is a block diagram of this encoder. If the decimal input 3 on the encoder is activated, then the logic circuit inside the unit outputs the BCD number 0011 as shown.

A more accurate description of a 10-line-to-4-line priority encoder is shown in Fig. 6-8(*b*). This is a connection diagram for the 74147 10-line-to-4-line priority encoder. Note the bubbles at both the inputs (1 to 9) and the outputs (*A* to *D*). The bubbles mean that the 74147 priority encoder has both *active LOW inputs* and *active LOW outputs*. A truth table is given for the 74147 priority

encoder in Fig. 6-8(c). Note that only LOW logic levels (L on the truth table) activate the appropriate input. The active state for the outputs on this IC are also LOW. Notice that in the last line of the truth table in Fig. 6-8(c), the L (logical 0) at input 1 activates only the A output (the least significant bit of the 4-bit group).

The 74147 TTL IC in Fig. 6-8(c) is packaged in a 16-pin DIP. Internally, the IC consists of circuitry equivalent to about 30 logic gates.

The 74147 encoder in Fig. 6-8 has a *priority* feature. This means that if two inputs are activated at the same time, only the larger number will be encoded. For instance, if both the 9 and the 4 inputs were activated (LOW), then the output would be LHHL, representing decimal 9. Note that the outputs need to be complemented (inverted) to form the true binary number of 1001.

Active LOW inputs
Active LOW
outputs

10-line-to-4-line

priority encoder


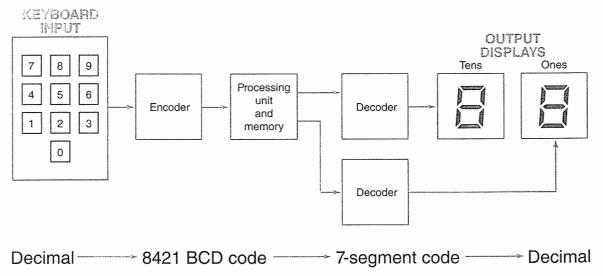


Fig. 5-7 A digital system.

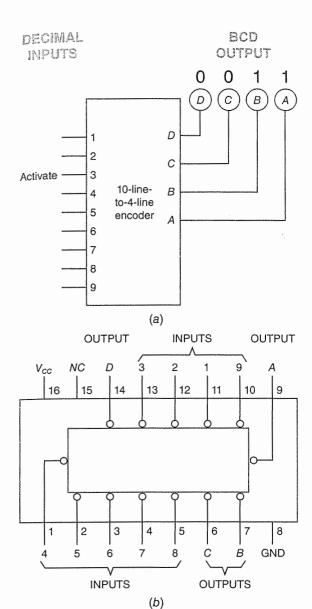

- 22. Refer to Fig. 6-8. The 74147 encoder IC has active ______ (HIGH, LOW) inputs and active _____ (HIGH, LOW)
- 23. Refer to Fig. 6-8. If only input 7 of the 74147 encoder is LOW, what is the logic state at each of the four outputs?
- 24. Refer to Fig. 6-8(*b*). What is the meaning of a bubble on the logic symbol at input 4 (pin 1 on the 74147 IC)?
- 25. Refer to Fig. 6-8. If both inputs 2 and 8 go LOW on the 74147 encoder, what is the logic state at each of the four outputs?





				OUTPUTS								
1	2	3	4	5	6	7	8	9	D	С	В	Α
Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
X	X	X	Χ	X	X	X	Χ	L	L	Н	Η	L
X	X	X	Χ	X	X	Χ	L	Н	L	Н	Η	Н
X	X	X	Χ	Χ	X	L	Н	Н	Н	L	L	L
X	X	X	Χ	X	L	Н	Н	Н	Н	L	L	Н
X	X	X	Χ	L	Н	Н	Н	Н	Н	L	Н	L
X	X	X	L	Η	Н	Н	Н	Н	Н	L	Н	Н
X	Χ	L	Η	Н	Н	Η	Н	Н	Н	Η	L	L
Х	L	Н	Н	Н	Н	Н	Н	Н	Н	Н	L	Н
L	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н	L

H = HIGH logic level, L = LOW logic level, X = Don't care
(c)


Fig. 6-8 (a) 10-line-to-4-line encoder.

- (b) Pin diagram for 74147 encoder IC.
- (c) Truth table for 74147 encoder.

6-6 Seven-Segment LED Displays

The common task of decoding from machine language to decimal numbers is suggested in the system in Fig. 6-7. A very common output device used to display decimal numbers is the seven-segment display. The seven segments of the display are labeled a through g in Fig. 6-9(a). The displays representing decimal digits 0 through 9 are shown in Fig. 6-9(b). For instance, if segments a, b, and c are lit, the decimal 7 is displayed. If, however, all segments a through g are lit, the decimal 8 is displayed.

Seven-segment display

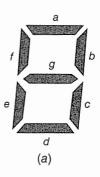



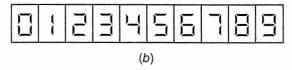


Fig. 6-9 (a) Segment identification. (b) Decimal numbers on typical seven-segment display.

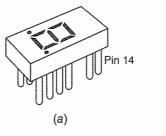

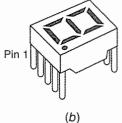

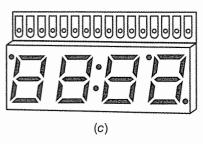


Fig. 6-10 (a) DIP seven-segment LED display. (b) A common 10-pin single-digit package. Note the location of pin 1. Pins are numbered counterclockwise from pin 1 when viewed from the top of the display. (c) Multidigit package.

74147 encoder IC

Several common seven-segment display packages are shown in Fig. 6-10. The seven-segment LED display in Fig. 6-10(a) fits a regular 14-pin DIP IC socket. Another single-digit seven-segment LED display is shown in Fig. 6-10(b). This display fits crosswise into a wider DIP IC socket. Finally, the unit in Fig. 6-10(c) is a multidigit LED display widely used in digital clocks.

Display Technologies


The seven-segment display may be constructed with each of the segments being a thin filament that glows. This type of unit is called an *incandescent display* and is similar to a regular lamp. Another type of display is the *gas-discharge tube*, which operates at high voltages. It gives off an orange glow. The modern *vacuum fluorescent (VF) display* gives off a blue-green glow when lit and operates at low voltages. The *liquid-crystal display (LCD)* creates numbers in a black or silvery color. The common LED display gives off a characteristic reddish glow when lit.


Anode wire Diode chip Reflector Cathode Anode lead index flat Cathode lead Shorter lead (cathode) (a) Flat area Anode Shorter lead (cathode) Cathode (b)

Fig. 6-11 (a) Cutaway view of standard lightemitting diode. (b) Identifying the cathode lead of the LED.

Light-Emitting Diode

A basic single *LED* (*light-emitting diode*) is illustrated in Fig. 6-11. The cutaway view of the LED in Fig. 6-11(*a*) shows the small exposed diode chip with a reflector to project the light upward toward the plastic lens.

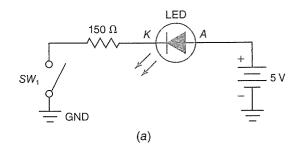

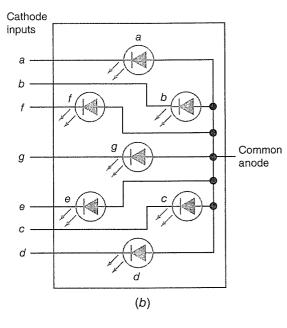

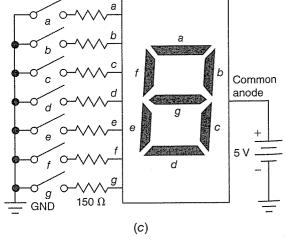


Fig. 6-12 (a) Operation of a simple LED. (b) Wiring a commonanode seven-segment LED display. (c) Driving a seven-segment LED display with switches.

Incandescent

Gas-discharge tube

fluorescent (VF)

Liquid-crystal display (LCD)

display

Vacuum

display

Of importance during use is determining the cathode lead of an LED. The index area (flat area) on the rim of a round LED is the cathode side. In Fig. 6-11 both the *flat area on the rim* and the *shorter of two leads* identifies the *cathode* of an LED.

The LED is basically a *PN-junction diode*. When the diode is forward-biased, current flows through the PN junction and the LED lights and is focused by the plastic lens. Many LEDs are fabricated from *gallium arsenide* (GaAs) and several related materials. LEDs come in several colors including red, green, orange, blue, amber, yellow, infrared, and multicolor.

A single LED is being tested in Fig. 6-12(a). When the switch (SW_1) is closed, current flows from the 5-V power supply through the LED, causing it to light. The series resistor limits current to about 20 mA. Without the limiting resistor, the LED would burn out. Typically, LEDs can accept only about 1.7 to 2.1 V across their terminals when lit. Being a diode, the LED is sensitive to polarity. Hence, the *cathode* (K) must be toward the negative (GND) terminal, while the *anode* (A) must be toward the positive terminal of the power supply.

Seven-Segment LED Display

A seven-segment LED display is shown in Fig. 6-12(b). Each segment (a through g) contains an LED, as shown by the seven symbols.

The display shown has all the anodes tied together and coming out the right side as a single connection (common anode). The inputs on the left go to the various segments of the display. The device in Fig. 6-12(b) is referred to as a common-anode seven-segment LED display. These units can also be purchased in common-cathode form.

To understand how segments on the display are activated and lit, consider the circuit in Fig. 6-12(c). If switch b is closed, current flows from GND through the limiting resistor to the b-segment LED and out the common-anode connection to the power supply. Only segment b will light.

Suppose you wanted the decimal 7 to light on the display in Fig. 6-12(c). Switches a, b, and c would be closed, lighting the LED segments a, b, and c. The decimal 7 would light on the display. Likewise, if the decimal 5 were to be lit, switches a, c, d, f, and g would be closed. These five switches would ground the correct segments, and a decimal 5 would appear on the display. Note that it takes a GND voltage (LOW logic level) to activate the LED segments on this display.

Mechanical switches are used in Fig. 6-12(c) to drive the seven-segment display. Usually power for the LED segments is provided by an IC. The IC is called a *display driver*. In practice, the display driver is usually packaged in the same IC as the decoder. Therefore, it is common to speak of *seven-segment decoder/drivers*.

Common anode PN-junction diode Common cathode

Gallium arsenide (GaAs)

Display driver
Seven-segment
LED display
Seven-segment
decoder/drivers

-∕M- Self-Test

Supply the missing word or words in each statement.

- 26. Refer to Fig. 6-9(a). If segments a, c, d, f, and g are lit, the decimal number will appear on the seven-segment display.
- 27. The seven-segment unit that gives off a bluegreen glow is a(n) _____ (vacuum fluorescent, incandescent, LCD) display.
- 28. The letters "LED" stand for ___
- 29. Refer to Fig. 6-12(c). If switches b and c are closed, segments _____ and ____ will light. This _____

- (LCD, LED) seven-segment unit will display the decimal number _____.
- On a single LED, as in Fig. 6-11, the flat area on the rim of the plastic identifies the _____lead.
- 31. Refer to Fig. 6-12(c). The seven resistors at the cathode inputs to the LED display are for ______ (current limiting, voltage multiplying).
- 32. Refer to Fig. 6-12(*b*). This seven-segment LED display has ______ (active HIGH, active LOW) inputs.
- 33. Refer to Fig. 6-12(c). Closing input switches b, c, f, and g causes the decimal number ______ to be displayed.



6-7 Decoders


Decoder

A decoder, like an encoder, is a code translator. Figure 6-7 shows two decoders being used in the system. The decoders are translating the 8421 BCD code to a seven-segment display code that lights the proper segments on the display. The display will be a decimal number. Figure 6-13 shows the BCD number 0101 at the input of the BCD-to-seven-segment decoder/driver. The decoder activates outputs

Combinational logic circuits

uits

ABOUT BLECTRONICS

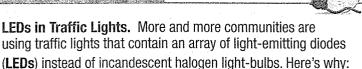

- LEDs are brighter and cover the entire surface.
- LEDs last longer and save replacement costs.
- **LEDs** save energy costs and in some areas may even be powered by solar panels.

a, c, d, f, and g to light the segments shown in Fig. 6-13. The decimal number 5 lights up on the display.

Decoders come in several varieties, such as the ones illustrated in Fig. 6-14. Notice in Fig. 6-14 that the same block diagram is used for the 8421 BCD, the excess-3, and the Gray decoder.

Other decoders are available such as BCD converters, BCD-to-binary converters, 4-to-16-line decoders, and 2-to-4-line decoders. Other encoders available are a decimal-to-octal and 8-to-3-line priority encoder.

Decoders, like encoders, are *combinational logic circuits* with several inputs and outputs. Most decoders contain from 20 to 50 gates. Most decoders and encoders are packaged in single IC packages. Specialized encoders and decoders can be fabricated using programmable logic devices (PLDs).

Decoding can also be achieved using flexible programmable devices such as BASIC Stamp modules. These modules by Parallax contain a microcontroller and associated EEPROM memory.

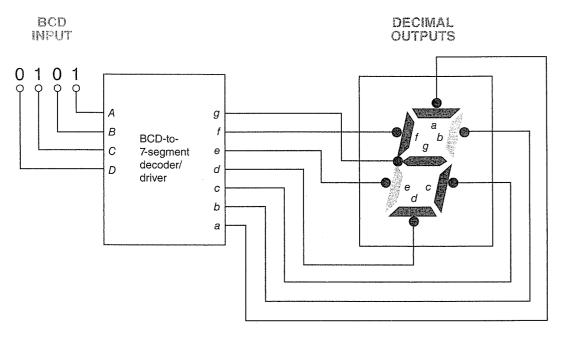


Fig. 8-13 A decoder driving a seven-segment display.


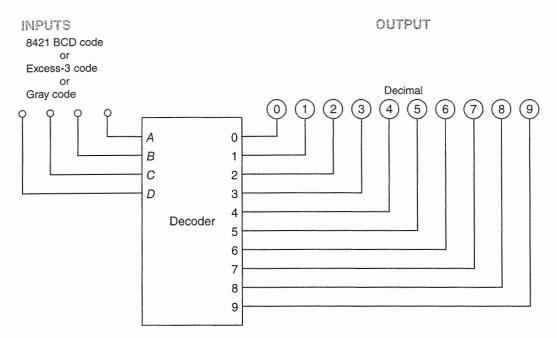


Fig. 5-14 A typical decoder block diagram. Note that inputs may be 8421 BCD, excess-3, or Gray code.

-W- Self-Test

Answer the following questions.

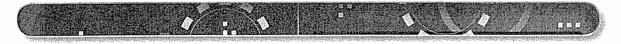- 34. Refer to Fig. 6-13. If the BCD input to the decoder/driver is 1000, which segments on the display will light? The seven-segment LED display will read what decimal number?
- 35. List at least three types of decoders.
- 36. Refer to Fig. 6-13. If the seven-segment
- display were an LED type, seven _____ (limiting resistors, switches) would need to be added between the decoder and the display.
- 37. Refer to Fig. 6-13. If the display reads decimal 3, the BCD input is ______
- 38. Refer to Fig. 6-13. If the BCD input is 0111, what segments are illuminated? What decimal number is displayed?



6-8 BCD-to-Seven-Segment Decoder/Drivers

A logic symbol for a commercial TTL 7447A BCD-to-seven-segment decoder/driver is shown in Fig. 6-15(a). The BCD number to be decoded is applied to the inputs labeled D, C, B, and A. When activated with a LOW, the lamp-test (LT) input activates all outputs (a to g). When activated with a LOW, the blanking input (BI) makes all outputs HIGH, turning all attached displays off. When activated with a LOW, the ripple-blanking input (RBI) blanks the display only if it contains a 0. When the


RBI becomes active, the BI/RBO pin temporarily becomes the *ripple-blanking output* (RBO) and drops to a LOW. Remember that "blanking" means to cause no LEDs on the display to light.

The seven outputs on the 7447A IC are all active LOW outputs. In other words, the outputs are normally HIGH and drop to a LOW when activated.

The exact operation of the 7447A decoder/driver IC is detailed in the truth table furnished by Texas Instruments and reproduced in Fig. 6-15(b). The decimal displays generated by the 7447A decoder are shown in Fig. 6-15(c).

7447A BCD-toseven-segment decoder/driver

Blanking input (BI)

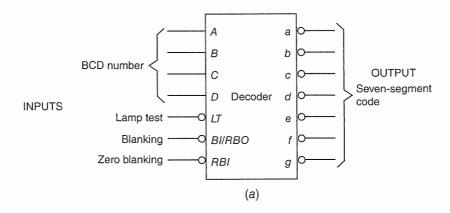


Decimal		١	INPUTS OUTPUTS								Note				
function	LT	RBI	D	С	В	Α	BIIBNO	а	b	С	d	е	f	g	11010
0	Н	Н	L	L	L	L	Н	ON	ON	ON	ON	ON	ON	OFF	
1	Н	Х	L	L	L	Н	Н	OFF	ON	ON	OFF	OFF	OFF	OFF	
2	Н	X	L	L	Н	ĻL	Н	ON	ON	OFF	ON	ON	OFF	ON	
3	Н	Х	L	L	Н	Н	Н	ON	ON	ON	ON	OFF	OFF	ON	
4	Н	Х	L	Н	L	L	Н	OFF	ON	ON	OFF	OFF	ON	ON	
5	Н	X	L	Н	L	Н	Н	ON	OFF	ON	ON	OFF	ON	ON	
6	Н	X	L	Н	Н	L	Н	OFF	OFF	ON	ON	ON	ON	ON	
7	Н	X	L	Н	Н	Н	Н	ON	ON	ON	OFF	OFF	OFF	OFF	
8	Н	Х	Н	L	L	L	Н	ON	ON	ON	ON	ON	ON	ON	1
9	Н	Х	Н	L	L	Н	Н	ON	ON	ON	OFF	OFF	ON	ON	
10	Н	X	Н	L	Н	L	Н	OFF	OFF	OFF	ON	ON	OFF	ON	
11	Н	Х	Н	L	Н	Н	Н	OFF	OFF	ON	ON	OFF	OFF	ON	
12	Н	Х	Н	Н	L	L	Н	OFF	ON	OFF	OFF	OFF	ON	ON	
13	Н	Х	Н	Н	L	Н	Н	ON	OFF	OFF	ON	OFF	ON	ON	
14	Н	X	Н	Н	Н	L	н	OFF	OFF	OFF	ON	ON	ON	ON	
15	Н	Х	Н	Н	Н	Н	Н	OFF	OFF	OFF	OFF	OFF	OFF	OFF	
BI	Х	Х	Х	Χ	Χ	Χ	L	OFF	OFF	OFF	OFF	OFF	OFF	OFF	2
RBI	Н	L	L	L	L	L	, L	OFF	OFF	OFF	OFF	OFF	OFF	OFF	3
LT	L	X	X	X	X	Χ	Н	ON	ON	ON	ON	ON	ON	ON	4

H = HIGH level, L = LOW level, X = Irrelevant

Notes:

- The blanking input (BI) must be open or held at a HIGH logic level when output functions 0 through 15 are desired. The ripple-blanking input (RBI) must be open or HIGH if blanking of a decimal zero is not desired.
- 2. When a LOW logic level is applied directly to the blanking input (BI), all segment outputs are OFF regardless of the level of any other input.
- 3. When ripple-blanking input (RBI) and inputs A, B, C, and D are at a LOW level with the lamp test (LT) input HIGH, all segment outputs go OFF and the ripple-blanking output (RBO) goes to a LOW level (response condition).
- 4. When the blanking input/ripple-blanking output (*Bl/RBO*) is open or held HIGH and a LOW is applied to the lamp test (*LT*) input, all segment outputs are ON.

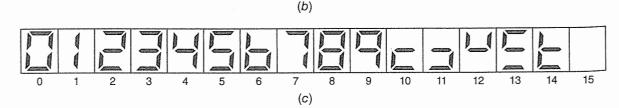

7447A TTL decoder IC

Fig. 6-15 (a) Logic symbol for 7447A TTL decoder IC. (b) Truth table for 7447A decoder. (Courtesy of Texas Instruments, Inc.)
(c) Format of readouts on seven-segment display using the 7447A decoder IC.



History of Electronics

Douglas Engelbart

What is commonly known today as the computer mouse was engineered in 1963 by Douglas Engelbart and was originally called an X-Y position indicator for a display system. Engelbart's early mouse was an electronic marble that was housed in a wooden box that had a red button and a copper wire tail. After retiring from Stanford Research Institute, Englebart developed a keyboard that had only five buttons.



Note that *invalid BCD inputs* (decimals 10, 11, 12, 13, 14, and 15) do generate unique outputs on the 7447A decoder.

The 7447A decoder/driver IC is typically connected to a common-anode seven-segment LED display. Such a circuit is shown in Fig. 6-16. It is especially important that the seven $150-\Omega$ limiting resistors be wired between the 7447A IC and the seven-segment display.

Assume that the BCD input to the 7447A decoder/driver in Fig. 6-16 is 0001 (LLLH). This is equal to line 2 of the truth table in Fig. 6-15(b). This input combination causes segments b and

c on the seven-segment display to light (outputs b and c drop to LOW). Decimal 1 is displayed. The LT and two BIs are not shown in Fig. 6-16. When not connected, they are assumed to be "floating" HIGH and therefore disabled in this circuit. Good design practice suggests that these "floating" inputs should be connected to +5 V to make sure they stay HIGH.

Many applications, such as a calculator or cash register, require that the *leading zeros be blanked*. The illustration in Fig. 6-17 shows the use of the 7447A decoder/drivers operating a group of displays as in a cash register. The

Invalid BCD inputs

Good design practice

"Floating" inputs

Blanking leading zeros

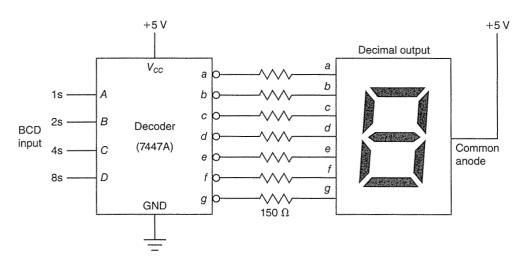


Fig. 6-16 Wiring a 7447A decoder and seven-segment LEO display.

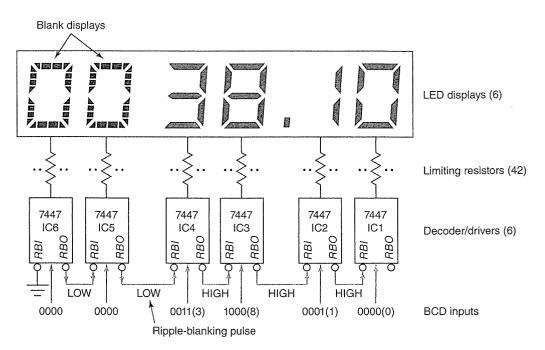


Fig. 6-17 Using the ripple-blanking input (RBI) of the 7447A decoder/driver to blank leading zeros in a multidigit display.

six-digit display example details how the blanking of leading 0s would be accomplished using the 7447A IC driving LED displays.

The current inputs to the six decoders are shown across the bottom of the drawing in Fig. 6-17. The current BCD input is 0000 0000 0011 1000 0001 0000 (003810 in decimal). The two left 0s should be blanked, so the display reads 38.10. The blanking of the leading 0s is handled by wiring the RBI and RBO pins to each 7447A decoder IC together as shown in Fig. 6-17.

Working from left to right in Fig. 6-17, notice that the RBI input of IC6 is grounded. From the 7447A decoder's truth table in Fig. 6-15(b) it can be determined that when RBI is LOW and when all BCD inputs are LOW, then all segments of the display are blanked or off. Also

the RBO is forced LOW. This LOW is passed to the RBI of IC5.

Continuing in Fig. 6-17 with the BCD input to IC5 as 0000 and the RBI at LOW, the display is also blanked. The RBO of IC5 is forced LOW and is passed to the RBI input of IC4. Even with the RBI LOW, IC4 *does not* blank the display because the BCD input is 0011. The RBO of IC4 remains HIGH, which is sent to IC3.

A question arises about the right LED display in Fig. 6-17. The BCD input to IC1 is 0000_{BCD} and a zero (0) appears on the display. The zero on the IC1 display is not blanked because the RBI input is not activated (RBI = HIGH). The first row of the truth table in Fig. 6-15(*b*) shows that the 7447A decoder/driver will display the zero when the RBI is HIGH.

NE Self-Test

Check your understanding by answering the following questions.

- 39. Refer to Fig. 6-15. The 7447A decoder/driver IC has active ______ (HIGH, LOW) BCD inputs and active _____ (HIGH, LOW) outputs.
- 40. Refer to Fig. 6-15. The lamp-test, blanking, and zero-blanking inputs of the
- 7447A are active _____ (HIGH, LOW) inputs.
- 41. The RBI and RBO inputs of the 7447A are commonly used for blanking ______ on calculator and cash register multidigit displays.
- 42. What will the seven-segment display read during each time period $(t_1 \text{ to } t_7)$ for the circuit shown in Fig. 6-18?

- 43. List the segments on the seven-segment display that will light during each time period $(t_1 \text{ to } t_2)$ for the circuit in Fig. 6-18.
- 44. The Bİ, RBI, and LT inputs are not shown on the 7447A's logic symbol in Fig. 6-18. They have all been left disconnected, meaning they will "float HIGH" and be disabled. (T or F)
- 45. Refer to Fig 6-16. The 7447A decoder/driver IC is said to be ______ (sinking, sourcing) current when segments on the LED display are lit.
- 46. Refer to Fig. 6-16. The 7447A decoder/driver IC is designed to operate a _____ (common-anode, common-cathode) seven-segment LED display.
- 47. Refer to Fig. 6-15(*b*). The lamp-test (LT) pin on the 7447A IC is an _____ (active HIGH, active LOW) input.
- 48. Refer to Fig. 6-15(*b*). If both the BI and LT inputs to the 7447A IC are activated by a LOW, all segments of an attached LED display are ______ (OFF, ON).

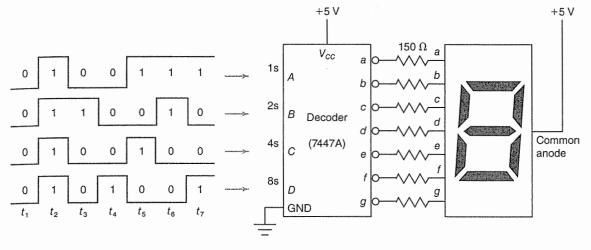


Fig. 6-18 Decoder-LED display circuit.



6-9 Liquid-Crystal Displays

The LED actually *generates* light, where the LCD simply *controls* available light. The LCD has gained wide acceptance because of its very low power consumption. The LCD is also well suited for use in sunlight or in other brightly lit areas. The DMM (digital multimeter) in Fig. 6-19 uses a modern LCD.

The LCD is also suited for more complex displays than just seven-segment decimal. The LCD display in Fig. 6-19 contains an analog scale across the bottom as well as the larger digital readout. In practice you will find that the DMM LCD has several other symbols, which you can also observe on the DMM in Fig. 6-19.

Monochrome LCD

The construction of a common LCD unit is shown in Fig. 6-20. This unit is called the

field-effect LCD. When a segment is energized by a low-frequency, square-wave signal, the LCD segment appears black, while the rest of the surface remains shiny. Segment e is energized in Fig. 6-20. The nonenergized segments are nearly invisible.

The key to LCD operation is the liquid crystal, or *nematic fluid*. This nematic fluid is sandwiched between two glass plates. An ac voltage is applied across the nematic fluid, from the top metalized segments to the metalized backplane. When affected by the field of the ac voltage, the nematic fluid transmits light differently and the energized segment appears as black on a silvery background.

The twisted-nematic field-effect LCD uses a polarizing filter on the top and bottom of the display as shown in Fig. 6-20. The backplane and segments are internally wired to contacts

Liquid-crystal displays Field-effect LCD

Nematic fluid



Digital multimeter

Fig. 6-19 Digital multimeter (DMM) using a liquid-crystal display.

on the edge of the LCD. Only two of the many contacts are shown in Fig. 6-20.

Driving the LCD

Decimal 7 is displayed on the LCD shown in Fig. 6-21. The BCD-to-seven-segment decoder on the left is receiving a BCD input of 0111. This input activates the a, b, and c outputs of the


decoder (a, b, and c) are HIGH in this example). The remaining outputs of the decoder are LOW (d, e, f, and g) = LOW. The 100-Hz square-wave input is always applied to the backplane of the display. This signal is also applied to each of the CMOS XOR gates used to drive the LCD. Note that the XOR gates produce an inverted waveform when activated (a, b, and c) XOR gates are activated). The 180° out-of-phase signals to the backplane and segments a, b, and c cause these areas of the LCD to turn black. The inphase signals from XOR gates d, e, f, and g do not cause these segments to be activated. Therefore, these segments remain nearly invisible.

The XOR gates used as LCD drivers in Fig. 6-21 are CMOS units. TTL XOR gates are not used because they cause a small dc offset voltage to be developed across the LCD's nematic fluid. The *dc voltage* across the nematic fluid *will destroy the LCD* in a short time.

In actual practice, the decoder and XOR LCD display drivers pictured in Fig. 6-21 are usually packaged in a single CMOS IC. The 100-Hz square-wave signal frequency is not critical and may range from 30 to 200 Hz. Liquid-crystal displays are sensitive to low temperatures. At below-zero temperatures the LCD display's turn-on and turn-off times become slow. However, the long lifetime and extremely low power consumption make them ideal for battery or solar cell operation.

Commercial LCDs

Figure 6-22 illustrates two examples of typical commercial monochrome LCD devices. Note that both have pins which can be soldered into a

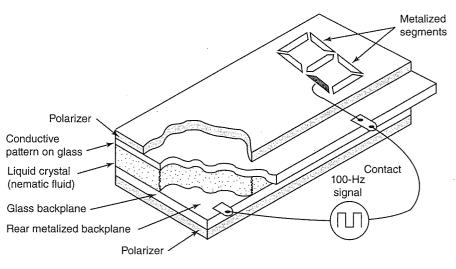

Construction of a field-effect LCD

Fig. 6-20 Construction of a field-effect LCD.

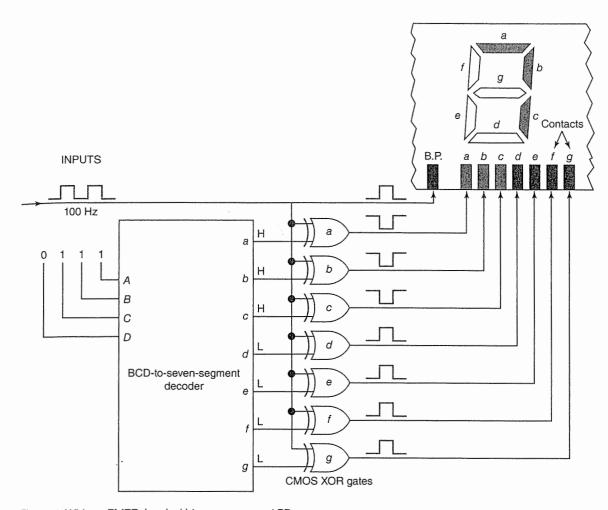


Fig. 6-21 Wiring a CMOS decoder/driver system to an LCO.

printed circuit board. In the lab, these LCD displays may be plugged into solderless mounting boards. However, this must be done with great care because there are many fragile pins. Most labs will have the LCDs mounted on a printed circuit board with the appropriate connectors.

A simple two-digit seven-segment LCD is sketched in Fig. 6-22(a). Notice the use of two glass plates. Because of the thin glass used in LCDs, care must be taken not to drop or bend the display. Notice in Fig. 6-22(a) that two plastic headers with pins are fastened on each side of the glass backplane. Only the common or backplane pin is labeled. Each segment and decimal point has a pin connection on this LCD package.

Another commercial monochrome LCD is illustrated in Fig. 6-22(b). This LCD has a more complex display, including symbols. This unit comes in a 40-pin package. All segments, decimal points, and symbols are assigned a pin number. Only the backplane or common pin is noted

on the drawing. Manufacturers' data sheets must be consulted for actual pin numbers.

Inexpensive monochrome LCDs use the twisted-nematic field-effect technology. These are constructed and operate like the one sketched in Fig. 6-20. Simple monochrome LCDs are used in phones, calculators, watches, and clocks. More complex monochrome LCDs might be used for bar graphs (such as on the DMM in Fig. 6-19), maps, diagram waveforms; charting the bottom of lakes and showing fish in depth finders; and in radio and GPS receivers. A host of lower-cost products from alarm clocks to ebook readers may use monochrome LCDs.

Color LCDs

Older color TVs and computer monitors used cathode-ray tube (CRT) technology. The CRTs displayed bright colors in high resolutions. CRTs lost favor because they were large and heavy and used a lot of power.

Twisted-nematic field-effect technology

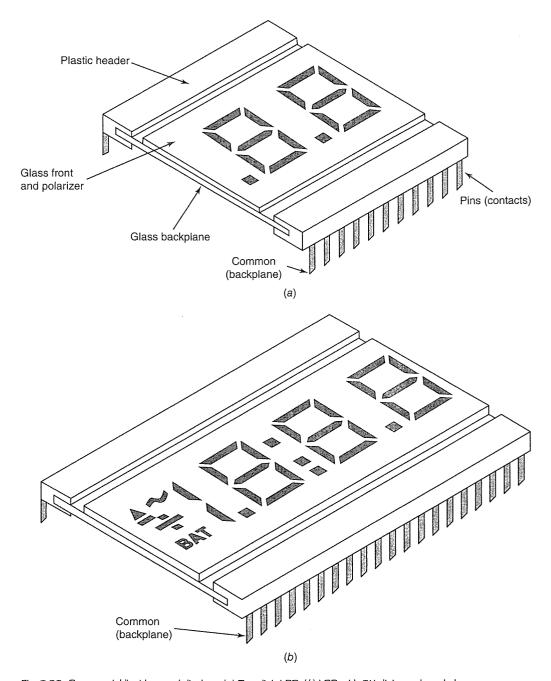



Fig. 6-22 Commercial liquid-crystal displays. (a) Two-digit LCD. (b) LCD with 3½ digits and symbols.

Color LCDs are commonly used in light-weight battery-power laptop and tablet computers. Color LCDs are appearing on computer desktops in place of the bulky CRT monitors. Color LCDs are generally classified as either passive-matrix LCDs or the newer more expensive active-matrix LCDs (AMLCDs). The future favors the active-matrix LCD because it is faster, brighter, and has a wider viewing angle than the passive-matrix types. However, active-matrix LCDs are more expensive than the passive-matrix type.

A simplified sketch of the construction of an active-matrix LCD is shown in Fig. 6-23. Like the monochrome LCD it has polarizers top and bottom. The active-matrix LCD also contains nematic fluid (liquid crystal) sandwiched in the sealed display much like the monochrome type display. Below the nematic fluid are *thin-film transistors* that can be turned on or off individually. The thin-film transistors are something like window blinds that can be opened or closed when turned on or off. For simplicity, think of each thin-film transistor as a pixel in

Passive-matrix LCDs

Active-matrix LCDs (AMLCDs)

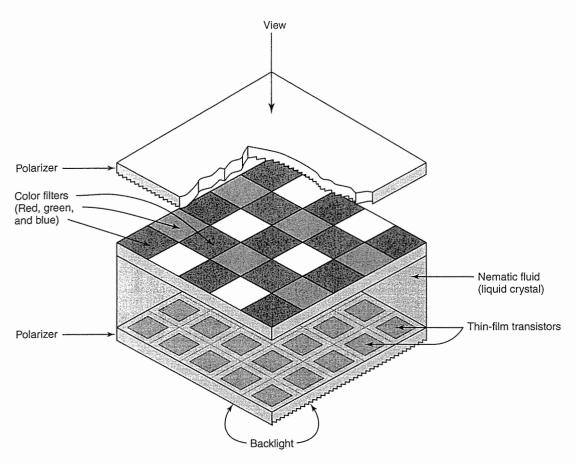

Internet Connection

Learn more about LCOs at www .howstuffworks.com

Fig. 6-23 Construction of an active-matrix LCD using thin-film transistor (TFT) technology.

the computer display. Recall that a *pixel* is the smallest element that can light or not light on an LCD monitor. A monitor may have several million pixels on the screen. You can see that the cutaway diagram of the active-matrix LCD shown in Fig. 6-23 is only a tiny section of an entire monitor screen. To add color to the tiny points of light, colored filters are added to the display in Fig. 6-23. Red, green, and blue filters

are used to produce all colors when mixed properly. Computer monitors must be fairly bright so backlighting is added to the activematrix LCD screen.

It must be understood that Fig. 6-23 presents only the concept of the active-matrix LCD using thin-film transistor (TFT) technology. The exact geometry and parts may vary in real devices.

Pixel

-\\-\- Self-Test

Supply the missing word or words in each statement.

- 49. Digits appear ______ (black, silver) on a _____ (black, silver) background on the field-effect LCD.
- 50. The LCD uses a liquid crystal, or _____ fluid, which transmits light differently when affected by a magnetic field from an ac voltage.
- 51. A(n) _____ (ac, dc) voltage applied to an LCD will damage the unit.

- 52. The LCD unit consumes a ______ (large amount, moderate amount, very small amount) of power.
- 53. Refer to Fig. 6-24. The XOR gates used to drive the LCD display are ______ (CMOS, TTL) devices.
- 54. Refer to Fig. 6-24. With an input of 0101_{BCD} to the decoder, the output display with form the decimal _____ on the monochrome LCD.
- 55. Refer to Fig. 6-24. With the BCD input to the decoder of 0101, what segments of

the monochrome LCD are activated and show up as dark on a lighter background?

66. Refer to Fig. 6-24. With the BCD input to

56. Refer to Fig. 6-24. With the BCD input to the decoder of 0101, the outputs of XOR

gates *a*, *c*, *d*, *f*, and *g* are ______ (in phase, 180° out of phase) with the BP (backplane) signal.

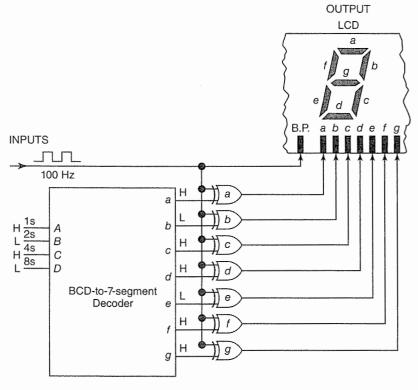


Fig. 6-24 Driving a liquid-crystal display.



6-10 Using CMOS to Drive an LCD Display

A block diagram of an LCD decoder/driver system is sketched in Fig. 6-25(a). The input is 8421 BCD. The latch is a temporary memory to hold the BCD data. The BCD-to-seven-segment decoder operates somewhat like the 7447A decoder that was studied earlier. Note that the output from the decoder in Fig. 6-25(a) is in seven-segment code. The last block before the display is the LCD driver. This consists of XOR gates as in Fig. 6-21. The drivers and backplane (common) of the display must be driven with a 100-Hz square-wave signal. In actual practice the latch, decoder, and LCD driver are all available in a single CMOS package. The 74HC4543 and 4543 ICs described by the manufacturer as a BCD-to-seven-segment latch/decoder/driver for LCDs are such packages.

A wiring diagram for a single LCD driver circuit is shown in Fig. 6-25(b). The 74HC4543 decoder/driver CMOS IC is being employed. The 8421 BCD input is 0011 (decimal 3). The 0011_{BCD} is decoded into seven-segment code. A separate 100-Hz clock feeds the signal to both the LCD backplane (common) and the Ph (phase) input of the 74HC4543 IC. The driving signals in this example are sketched for each segment of the LCD. Note that only out-of-phase signals will activate a segment. In-phase signals (such as segments e and f in this example) do not activate LCD segments.

A pin diagram for the 74HC4543 BCD-toseven-segment latch/decoder/driver CMOS IC is reproduced in Fig. 6-26(a), page 220. Detailed information on the operation of the 74HC4543 IC is contained in the truth table in Fig. 6-26(b). On the output side of the truth table, an "H" means the segment is ON while an "L" means

74HC4543 BCDto-seven-segment latch/decoder/ driver CMOS IC

BCD-to-sevensegment latch/ decoder/driver for LCD

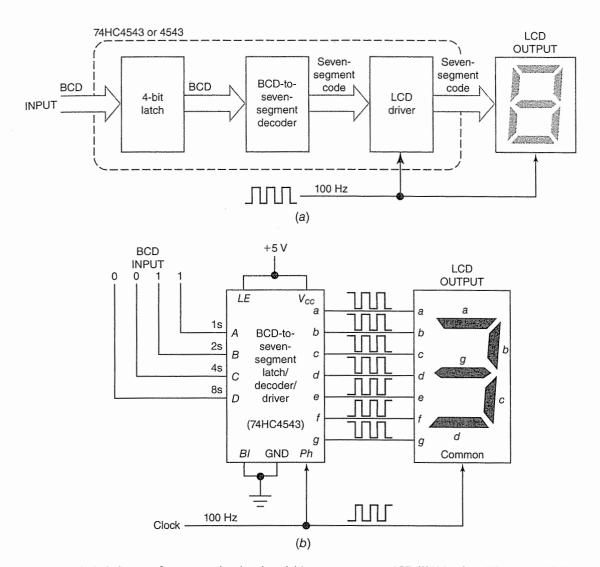


Fig. 6-25 (a) Block diagram of system used to decode and drive a seven-segment LCD. (b) Using the 74HC4S43 CMOS IC to decode and drive the LCD.


the segment is OFF. The format of the decimal numbers generated by the decoder is shown in Fig. 6-26(c). Note especially the numbers 6 and 9. The 74HC4543 decoder forms the

6 and 9 differently from the 7447A TTL decoder studied earlier. Compare Fig. 6-26(c) with Fig. 6-15(c) to see the differences.

-₩-

Self-Test

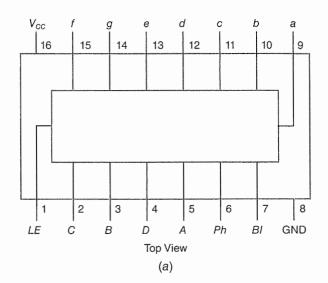- 57. Refer to Fig. 6-25(a). The job of the decoder block is to translate from _____ code to _____ code.
- 58. Refer to Fig. 6-25. All of the drive lines going from the driver to the LCD carry a square-wave signal. (T or F)
- 59. Refer to Fig. 6-27. What is the decimal reading on the LCD for each input pulse $(t_1 \text{ to } t_2)$?
- 60. Refer to Fig. 6-27. For input pulse t_5 only, which drive lines have an *out-of-phase* signal appearing on them?
- 61. Refer to Fig. 6-25. The LCD driver block inside the 4543 IC will probably contain a group of _____ (AND, XOR) gates.
- 62. Refer to Fig. 6-25. What block in the 74HC4543 IC is a type of memory device?
- 63. Refer to Fig. 6-25(*b*). What activates segments *a*, *b*, *c*, *d*, and *g* on the LCD?




Truth Table

77 017	Tull lable													
		IN	PUT	S	-					OU	TPU	S		
LE	BI	Ph*	D	С	В	Α	а	ь	С	d	е	f	g	Display
Х	Н	L	Х	X	Χ	Х	L	L	L	L	L	L	L	Blank
Н	L	L	L	L	L	L	Ι	Н	Н	Н	Н	Н	L	0
Н	L	L	L	L	L	Н	L	Н	Н	L	L	L	L	1
Н	L	L	L	L	Н	L	Н	Н	L	Н	Н	L	Н	2
Н	L	L	L	L	Н	Н	Н	Н	Н	Н	L	L	Н	3
Н	L	L	L	Н	L	L	L	Н	Η	L	L	Н	Н	4
Н	L	L	L	Н	L	Н	Н	L	Н	Н	L	Η	Н	5
Н	L	L	L	Н	Н	L	Н	L	Н	Н	Η	Н	Н	6
Н	L.	L	L	Н	Н	Н	Н	Н	Н	L	L	L	L	7
Н	L	L	Н	L	L	L	Н	Н	Н	Н	Н	Н	Н	8
Н	L	L	Н	L	L	Н	Н	Н	Н	Н	L	Н	Н	9
Н	L	L	Н	L	Η	L	L	L	L	L	L	L	L	Blank
H	L	L	Н	L	Η	Н	L	L	L	L	L	L	L	Blank
Н	L	L	Н	Н	L	L	L	L	L	L	L	L	L	Blank
Н	L	L	Н	Н	L	Н	L	L	L	L	L	L	L	Blank
Н	L	L	Н	Н	Н	L	L	L	L	L	L	L	L	Blank
Н	L	L	Н	Н	Н	Н	L	L	L	L	L	L	L	Blank
L	L	L	Х	Х	Х	X				†				†
‡	‡	Н		:	‡		Inverse of output combinations above						Display as above	


- X = don't care
- = for liquid crystal readouts, apply a square wave to Ph
- \dagger = depends upon the BCD code previously applied when LE = H \ddagger = same as above combinations

(b)

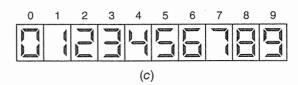

74HC4543 BCDto-seven-segment latch/decoder/ driver CMOS IC

Fig. 6-26 The 74HC4S43 BCD-to-seven-segment latch/decoder/driver CMOS IC. (a) Pin diagram. (b) Truth table. (\bar{c}) Format of digits formed by the 74HC4543 decoder IC.

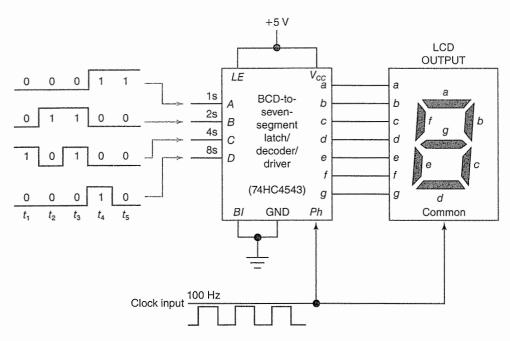

Internet Connection

Read about the history of display technology at en.wikipedia.org.

Fig. 6-27 Decoder/LCD circuit for problems S9 and 60.



6-11 Vacuum Fluorescent Displays

The vacuum fluorescent (VF) display is a modern relative of the triode vacuum tube. A schematic symbol for a triode vacuum tube is sketched in Fig. 6-28(a). The three parts of the triode tube are called the plate (P), grid (G), and cathode (K). The cathode is also called the filament or the heater. The plate is also called the anode.

The cathode/heater is a fine tungsten wire coated with a material such as barium oxide. The cathode gives off electrons when heated. The grid is a stainless steel screen. The plate can be thought of as the "collector of electrons" in the triode tube.

Assume that the cathode (K) of the triode tube in Fig. 6-28(a) is heated and has "boiled off" some electrons into the vacuum surrounding the cathode. Next, assume that the grid (G) becomes positive. The electrons are attracted to the grid. Next, assume that the plate (P) becomes positive. When the plate becomes positive, electrons will be attracted through the screenlike grid to the plate. Finally, the triode is conducting electricity from cathode to anode.

You can stop the triode tube from conducting in one of two ways. First, make the grid slightly negative (leave the plate positive). This

will repel the electrons, and they will not pass through the grid to the plate. Second, leave the grid positive, and drop the plate voltage to 0. The plate will not attract electrons, and the triode tube does not conduct electricity from cathode to anode.

The schematic symbol in Fig. 6-28(b) represents a single digit of a VF display. Notice the single cathode (K), single grid (G), and seven plates (P_a to P_g). Each of the seven plates has been coated with a zinc-oxide fluorescent material. Electrons striking the fluorescent material on the plate will cause it to glow a blue-green color. The seven plates in the schematic in Fig. 6-28(b) represent the seven segments of a normal numeric display. Note that the entire unit is held in a glass enclosure containing a vacuum.

A single-digit seven-segment display is being operated in Fig. 6-28(c). The cathode (heater) is being powered by direct current in this example, with +12 V applied to the grid (G). Two plates (P_c and P_f) are grounded. Each of the remaining five plates has +12 V applied. The high positive voltage on the five plates (P_a , P_b , P_a , P_e , and P_g) causes these plates to attract electrons. These five plates glow a blue-green color as electrons strike their surface.

Vacuum fluorescent (VF) display

Plate (P)


Grid (G)

Cathode (K)

Filament

Heater

Zinc-oxide fluorescent material

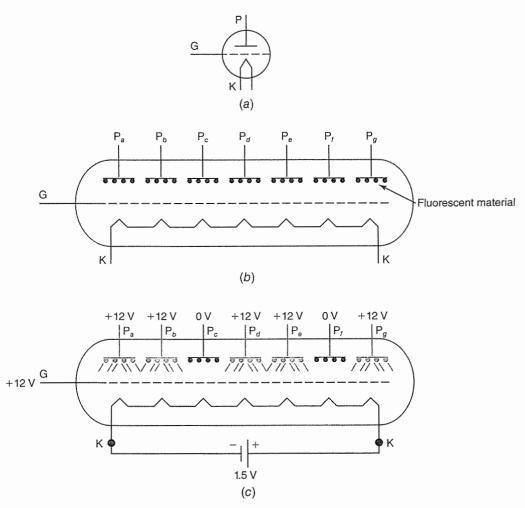

Triode vacuum tube VF display

Fig. 6-28 (a) Schematic symbol for a triode vacuum tube. (b) Schematic symbol for a single digit of a VF display. (c) Lighting plates on the VF display.

In actual practice, the plates of the VF display tube are shaped like segments of a number or other shapes. Figure 6-29(a) is a view of the physical arrangement of cathode, grid, and plates. Notice that the plates are arranged in seven-segment format in this display unit. The screen above the segments is the grid. Above the grid are the cathodes (filaments or heaters). Each segment, grid, or cathode lead comes out the side of the sealed glass vacuum tube. The VF display shown in Fig. 6-29(a) would be viewed from above the unit looking downward. The fine wire cathodes and grid would be almost invisible. Lighted segments (plates) show through the mesh (grid).


A commercial vacuum fluorescent display is sketched in Fig. 6-29(b). This VF display contains 4 seven-segment numeric displays, a colon, and 10 triangle-shaped symbols. The internal parts of most VF displays are visible

through the sealed glass package. Visible in the display are the cathodes (filaments or heaters) stretched horizontally across the display. These are very fine wires and are barely visible on a commercial display. Next, the grids are shown in five sections. Each of the five grids can be activated individually. Finally, the fluorescent-coated plates form the numeric segments, colons, and other symbols.

Vacuum fluorescent displays are based on an older technology, but they have gained some favor in recent years. This is because they can operate at relatively low voltages and power and have an extremely long life and fast response. They can display in various colors (with filters), have good reliability, and low cost. Vacuum fluorescent displays are compatible with the popular 4000 series CMOS family of ICs. They are widely used in readouts found in automobiles, VCRs, TVs, household appliances, and digital clocks.

Internet Connection

For information on solid-state display, visit the website for Lumex, Inc.

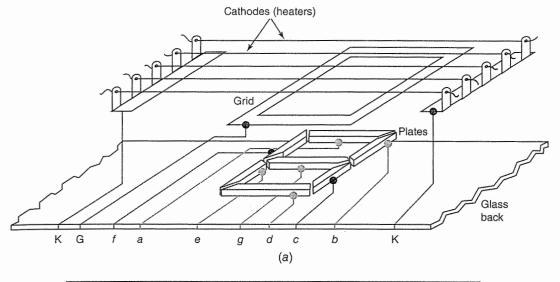

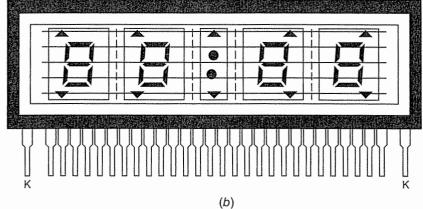


Fig. 6-29 (a) Typical construction of VF display. (b) Commercial four-digit VF display.

Construction of vacuum fluorescent display

-/w- Self-Test

- 64. A VF display glows with a(n) ______ color when activated.
- 65. Refer to Fig. 6-30. Which plates of this VF display will glow?
- 66. Name the parts of the vacuum fluorescent display labeled *A*, *B*, and *C* in Fig. 6-31.
- 67. Refer to Fig. 6-31. What segments of the VF display glow, and what decimal number is lit?

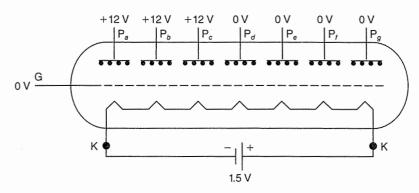


Fig. 6-30 VF display with no positive grid voltage.

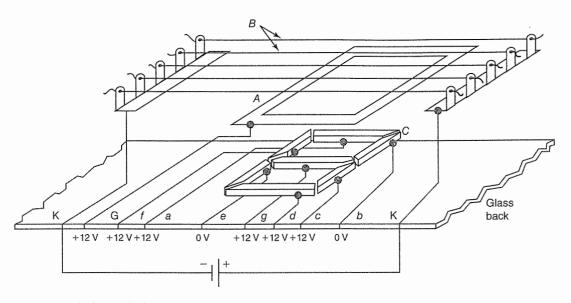


Fig. 5-31 Single-digit VF display problem.



Driving a VF display

4511 BCD-to-sevensegment latch/ decoder/driver CIMOS IC

6-12 Driving a VF Display

The voltage requirements for operating VF displays are somewhat higher than for LED or LCD units. This requirement makes them compatible with 4000 series CMOS ICs. Recall that 4000 series CMOS ICs can operate on voltages up to 18 V.

A wiring diagram of a simple BCD decoder/driver circuit is detailed in Fig. 6-32. In this example, 1001_{BCD} is translated into the decimal 9 on the VF display. The circuit uses the 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC. In this example, the a, b, c, f, and g output lines are HIGH (+12 V) with only the d and e lines LOW.

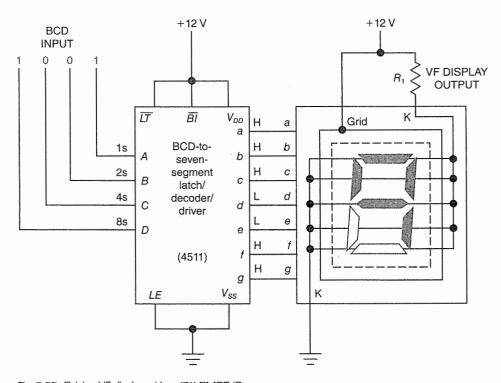



Fig. 6-32 Driving VF display with a 4511 CMOS IC.

The +12-V supply is connected directly to the grid in Fig. 6-32. The cathode (filament or heater) circuit contains a resistor (R_1) to limit the current through the heaters to a safe level. The +12 V is also used to supply power for the 4511 decoder/driver CMOS IC. Note the labels on the power connections to the 4511 IC. The V_{DD} pin connects to +12 V while V_{SS} goes to ground (GND).

The pin diagram, truth table, and number formats for the 4511 CMOS IC are shown in Fig. 6-33. The 4511 BCD-to-seven-segment latch/decoder/driver IC's pin diagram is shown in Fig. 6-33(a). This is the top view of this 16-pin DIP CMOS IC. Internally, the 4511 IC is organized like the 74HC4543 unit. The latch, decoder, and driver sections are illustrated

in the shaded section of the block diagram in Fig. 6-25(a).

The truth table in Fig. 6-33(b) shows seven inputs to the 4511 decoder/driver IC. The BCD data inputs are labeled D, C, B, and A. The \overline{LT} input stands for lamp test. When activated by a LOW (row 1 on the truth table), all outputs go HIGH and light all segments of an attached display. The \overline{BI} input stands for blanking input. When \overline{BI} is activated with a LOW, all outputs go LOW and all segments of an attached display are blanked. The LE (latch enable) input can be used like a memory to hold data on display while the BCD input data changes. If LE=0, then data passes through the 4511 IC. However, if LE=1, then the last data present at the data inputs (D, C, B, A) is

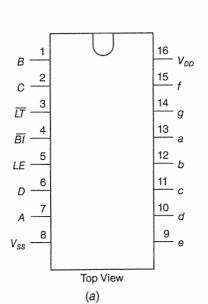

Truth Table **INPUTS OUTPUTS** ĹΤ LE ΒĪ D C В Α b d Display а С f g e Х Χ Χ Χ Χ Χ Χ Χ Χ Χ Χ O O n Χ Χ Χ X = Don't care

* Depends upon the BCD code appiled during the 0 to 1 transition of *LE*.

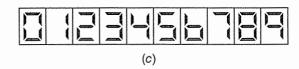


Fig. 6-33 The 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC. (a) Pin diagram. (b) Truth table. (c) Format of digits using the 4511 decoder IC.

4511 BCD-to-sevensegment latch/ decoder/driver CMOS IC latched and held on the display. The LE, \overline{BI} , and \overline{LT} inputs are all disabled in the circuit in Fig. 6-32.

Next, refer to the output side of the truth table in Fig. 6-33. On the 4511 IC, a HIGH or 1 is an active output. In other words, an output of 1 turns on a segment on the attached display.

Therefore, a 0 output means the display's segment is turned off.

The format of the digits generated by the 4511 BCD-to-seven-segment decoder IC are illustrated in Fig. 6-33(c). Especially note the formation of the decimal numbers 6 and 9.

-Vr Self-Test

- 68. Refer to Fig. 6-32. The +12-V power supply is being used because the _____ (CMOS, TTL) 4511 decoder/driver IC and the ____ (LCD, VF) display operate properly at this voltage.
- 69. Refer to Fig. 6-32. What is the purpose of resistor R_1 in this circuit?
- 70. Refer to Fig. 6-34. What is the decimal reading on the vacuum fluorescent display for each input pulse $(t_1 \text{ to } t_4)$?
- 71. Refer to Fig. 6-34. During pulse (t_4) what voltages are applied to the seven plates (segments) of the VF display?


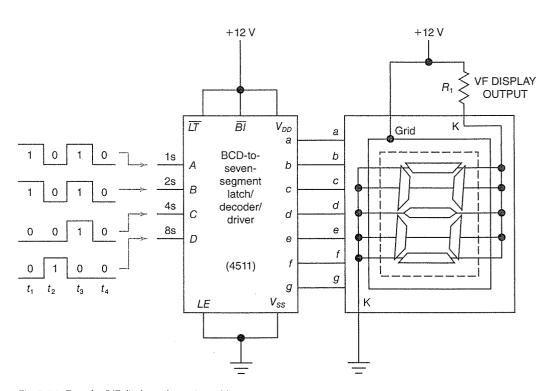


Fig. 6-34 Decoder/VF display pulse-train problem.

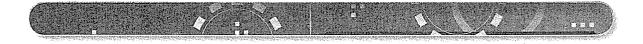

6-13 Troubleshooting a Decoding Circuit

Circuit 1

Consider the BCD-to-seven-segment decoder circuit in Fig. 6-35. The problem is that segment a of the display does not light. The technician first checks the circuit visually. Then the IC is checked for signs of excessive heat. The V_{CC} and GND voltages are checked with a voltmeter or logic probe. In this example, the results of these tests did not locate the problem.

Next, the temporary jumper wire from GND to the LT input of the 7447A IC should cause all segments on the display to light, giving a decimal 8 indication. Segment a on the display still does not light. The logic probe is used to check the logic levels at the outputs (a to g) of

the 7447A decoder. They are all L (LOW) in Fig. 6-35, as required. Next, the logic levels are checked on the display side of the resistors. They are all H (HIGH) except the faulty line, which is LOW. The LOW and HIGH pattern in Fig. 6-35 indicates a voltage drop across each of the bottom six resistors. The LOW indications on both ends of the top resistor in Fig. 6-35 indicate an open circuit in the segment *a* section of the seven-segment display. Segment *a* of the display must be faulty. The entire seven-segment LED display is replaced. The replacement must have the same pin diagram and be a common-anode LED display. After replacement, the circuit is checked for proper operation.

Circuit 2

The circuit shown in Fig. 6-36 produces no display. The hurried technician checks the $V_{\rm CC}$

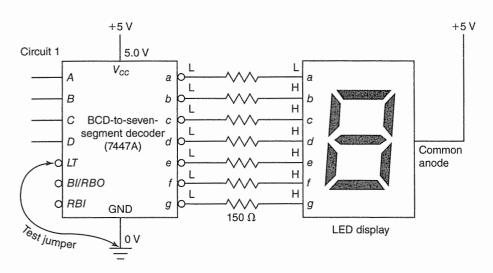


Fig. 6-35 Troubleshooting a faulty decoder/LEO display circuit.

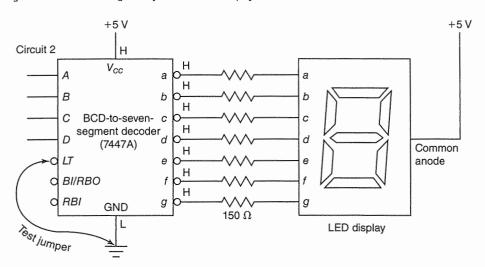


Fig. 6-36 Troubleshooting a faulty decoder circuit with blank LEO display.



Look up digital light processing (DLP) at en.wikipedia.org or www.dlp.com.

Troubleshooting faulty decoder/LED display circuit and GND pins with a logic probe. The readings as shown in Fig. 6-36 seem all right. The test jumper wire from the LT to the GND should light all segments of the LED display. No segments on the display light. The logic probe shows faulty HIGH readings at all the outputs (a to g) of the 7447A IC. The technician checks the voltage at V_{cc} with a DMM. The reading is 4.65 V. This is quite low. The technician now touches the top of the 7447A IC. It is very hot. The chip (7447A) has an *internal short circuit* and must be replaced. The 7447A IC is

replaced, and the circuit is checked for proper operation.

In this example, the technician forgot to use his or her own senses first. A simple touch of the top of the DIP IC circuit would have suggested a bad 7447A chip. Note that the HIGH reading on the $V_{\rm CC}$ pin did not give the technician an accurate picture. The voltage was actually 4.65 V instead of the normal 5.0 V. In this case the voltmeter reading gave the technician a clue as to the difficulty in the circuit. The short circuit was dropping the power supply voltage to 4.65 V.

Internal short circuit



- 72. What is the first step in troubleshooting a digital logic circuit?
- 73. An internal ______ (open, short) circuit in a TTL IC will many times cause the IC to become excessively hot.



Chapter 6 Summary and Review



Summary

- Many codes are used in digital equipment. You should be familiar with decimal, binary, octal, hexadecimal, 8421 BCD, excess-3, Gray, and ASCII codes.
- 2. Converting from code to code is essential for your work in digital electronics. Table 6-4 will aid you in converting from several of the codes.
- The most popular alphanumeric code is the 7-bit ASCII code. The ASCII code is widely used in microcomputer keyboard and display interfacing. Extended ASCII uses 8 bits.
- 4. Electronic translators are called encoders and decoders. The complicated logic circuits are

- manufactured in single IC packages. Decoding can also be implemented using programmable devices such as PLDs or microcontroller modules.
- Seven-segment displays are very popular devices for reading out numbers. Light-emitting diode (LED), liquid-crystal display (LCD), and vacuum fluorescent (VF) types are popular displays.
- The BCD-to-seven-segment decoder/driver is a common decoding device. It translates from BCD machine language to decimal numbers. The decimal numbers appear on seven-segment LED, LCD, or VF displays.

Table 6-4			1900			
				BCD Codes		Gray
Decimal Number	Binary Number	842	1		Excess-3	code
0	0000		0000		0011	0000
1	0001		0001		0100	0001
2	0010		0010		0101	0011
3	0011		0011		0110	0010
4	0100		0100		0111	0110
5	0101		0101		1000	0111
6 }	0110		0110		1001	0101
7	0111		0111		1010	0100
8	1000		1000		1011	1100
9	1001		1001		1100	1101
10	1010	0001	0000	0100	0011	1111
11	1011	0001	0001	0100	0100	1110
12	1100	0001	0010	0100	0101	1010
13	1101	0001	0011	0100	0110	1011
14	1110	0001	0100	0100	0111	1001
15	1111	0001	0101	0100	1000	1000
16	10000	0001	0110	0100	1001	11000
17	10001	0001	0111	0100	1010	11010
18	10010	0001	1000	0100	1011	11011
19	10011	0001	1001	0100	1100	11010
20	10100	0010	0000	0101	0011	11110

Chapter Review Questions

Answer	the following question	S.	6-13.	List two general names for code translators, or
6-1	Write the binary num	bers for the decimal num-		electronic code converters.
0 1.	bers in a to f :	oolo loi tuo deelintai nain	6-14.	A(n) (decoder, encoder) is the
	a. 17	d. 75		electronic device used to convert the decimal
				input of a calculator keypad to the BCD code
	b. 31	e. 150		used by the central processing unit.
	c. 42	2. 000	6-15.	A(n) (decoder, encoder) is the
6-2.		numbers for the decimal	0 10.	electronic device used to convert the BCD of
	numbers in <i>a</i> to <i>f</i> :			the central processing unit of a calculator to the
	a. 17	d. 1632		
	b. 31	e. 47,899	(1(decimal display output.
	c. 150	f. 103,926	0-10.	Which segments of the seven-segment display
6-3.	Write the decimal nu	mbers for the 8421 BCD		will light when the following decimal numbers
	numbers in <i>a</i> to <i>f</i> :			appear? Use the letters a, b, c, d, e, f , and g as
	a. 0010			answers.
	b. 1111			a. 0 f. 5
	c. 0011 0000			b. 1 g. 6
	d. 0111 0001 0110 0	000		c. 2 h. 7
				d. 3 i. 8
	e. 0001 0001 0000 0			e. 4 j. 9
	f. 0101 1001 1000 1		6-17.	The seven-segment displays that you will
6-4.		de numbers for the deci-		use emit light (usually red) and are of the
	mal numbers in a to a			(LCD, LED) type.
	a. 7	c. 59	6-18	The(LCD, LED) seven-
	b. 27		0-10.	segment display is used where battery operation
6-5.	Why is the excess-3 of	code used in some arithme-		demands low power consumption.
	tic circuits?		<i>c</i> 10	
6-6.	List two codes you le	arned about that are classi-	0-19.	The (LCD, LED) display is
	fied as BCD codes.		 .	used where the unit must be read in bright light
6-7.	Write the Gray code	numbers for the decimal	6-20.	Refer to Fig. 6-37. All the outputs from the
	numbers in a to f .			7447A decoder are(HIGH,
	a. 1	d. 4		LOW). This is (correct, not
		e. 5		correct) for this circuit.
	c. 3	f. 6	6-21.	Both a voltmeter and a(n) are
<i>6</i> 0		(Gray, XS3) code is com-		used to troubleshoot the circuit in Fig. 6-37.
0-6.			6-22.	Refer to Fig. 6-37. Segment <i>b</i> of the LED
	•	h optical encoding of a		display appears to be (open,
	shaft's angular position			partially short-circuited). The display should be
6-9.		teristic of the Gray code is		replaced with a commonLEI
	•	anges as you decrement or		display having the same pin diagram as the one
	increment the count.			in the circuit.
6-10.		he 7-bit ASCII code for the	6.23	Refer to Fig. 6-38. With the BCD input shown,
	capital letter S is	•	0-25.	_
6-11.	The letters "ASCII" s	tand for	6.04	the six-digit display reads
6-12.	Standard ASCII is a(1	n)bit	0-24.	The front and back panels of an
	(alpl	nanumeric, BCD) code that		(LCD, LED) seven-segment display are
	is used to represent n	umber, letters, punctuation		made of glass and can be broken by rough
	marks, and control ch	-		handling.
	•			

Chapter Review Questions...continued

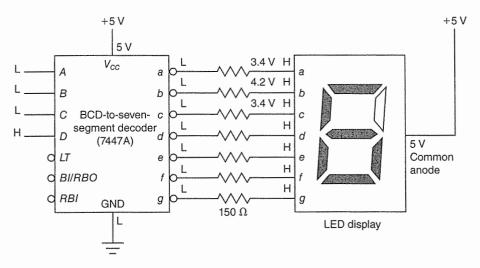


Fig. 6-37 Troubleshooting problems. Logic levels and voltages given on faulty decoder/LED display circuit.

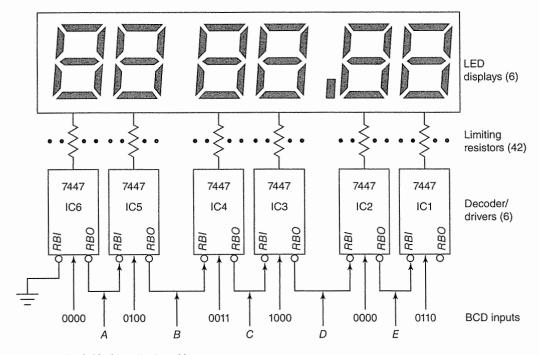


Fig. 6-38 Ripple-blanking circuit problem.

- 6-25. Refer to Fig. 6-39. With the driving signals shown, the LCD will display the decimal number ______. The input must be the BCD number _____.
- 6-26. Vacuum fluorescent displays can operate on 12 V, which makes them very compatible with _____ (CMOS, TTL) ICs and automotive applications.
- 6-27. Refer to Fig. 6-40. What will the VF seven-segment display read for each input pulse?
- 6-28. Refer to Fig. 6-40. List the approximate voltages at each of the seven plates and the grid of the VF display during pulse t_4 .

Chapter Review Questions...continued

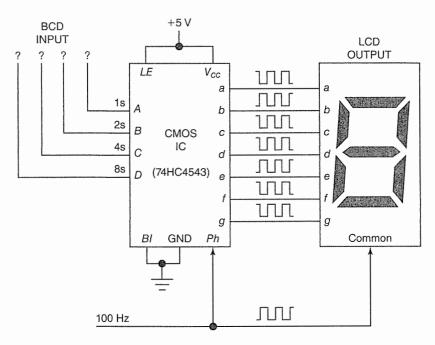


Fig. 6-39 Decoder/LCD circuit problem.

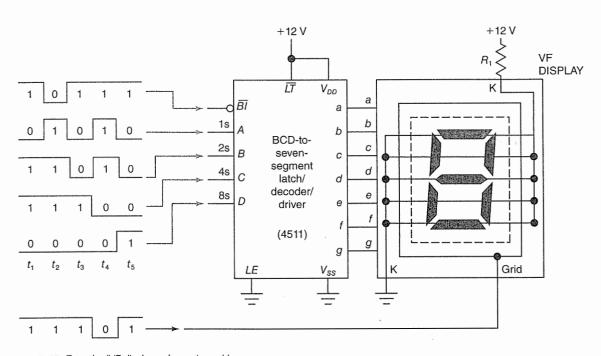


Fig. 6-40 Decoder/VF display pulse-train problem.

Critical Thinking Questions

- 6-1. Convert the following 8421 BCD numbers to binary.
 - a. 0011 0101
 - b. 1001 0110
 - c. 0111 0100
- 6-2. As you count in the Gray code, what is the most important characteristic?
- 6-3. Refer to Fig. 6-7. If the decoder chip is a 4511 and the circuit operates on a 12-V power supply, then the output displays are probably _____ (LED, VF) units.
- 6-4. Refer to Fig. 6-8. Why would the output of the 74147 10-line-to-4-line encoder read 0111 when *both* inputs 2 and 7 are activated at the same time?
- 6-5. What is the purpose of the 7447A TTL IC, and with which type of seven-segment display is it compatible?
- 6-6. The 7447A decoder TTL IC contains 44 gates and is considered a ______ (combinational, sequential) logic circuit. The 7447A decoder has _____ [number] active LOW inputs, _____ [number] active HIGH inputs, and _____ [number] active LOW outputs.
- 6-7. List the condition (HIGH or LOW) of each of the ripple-blanking lines *A* to *E* in Fig. 6-38.
- 6-8. Refer to Fig. 6-39. List the three functions of the 74HC4543 CMOS IC.

- 6-9. At the option of your instructor, use circuit simulation software to (1) draw the logic circuit sketched in Fig. 6-41, (2) generate a truth table for the logic circuit, and (3) determine if it is a Gray code—to-binary decoder or a binary-to—Gray code decoder.
- 6-10. At the option of your instructor, use circuit simulation software (such as Electronics Workbench or Multisim) to (a) draw the binary-to-decimal decoder circuit sketched in Fig. 6-42, (b) test the operation of the decoder circuit, and (c) demonstrate the operation of the binary-to-decimal decoder circuit simulation to your instructor.

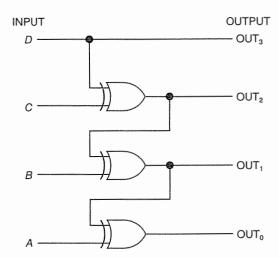


Fig. 6-41 Logic circuit.

Critical Thinking Questions...continued

Decimal Output

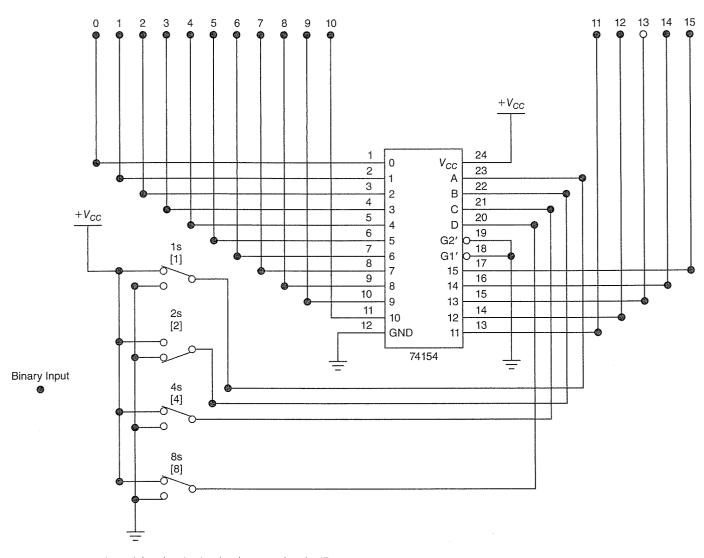


Fig. 6-42 Binary-to-decimal decoder circuit using the 74154 decoder IC.



Answers to Self-Tests

- 1. 11101
- 2. 0010 1001
- 3. 8765
- 4. 8421 BCD
- 5. 79
- 6. 1000 0101_{BCD}
- 7. F
- 8. 0100 1011
- 9.60

- 10. is not
- 11. Only one digit changes as you count in the Gray code.
- 12. Frank Gray
- 13. optical encoding
- 14. HIGH
- 15. 0111
- 16. 2-bit quadrature code
- 17. CW

- 18. alphanumeric
- 19. American Standard Code for Information Interchange
- 20. 101 0010
- 21. \$
- 22. LOW, LOW
- 23. output D = HIGH
 - output C = LOW
 - output B = LOW
 - output A = LOW
- 24. The invert bubble means that input 4 is an active LOW input; it is activated by a logical 0.
- 25. output D = LOW
 - output C = HIGH
 - output B = HIGH
 - output A = HIGH
- 26. 5
- 27. vacuum fluorescent
- 28. light-emitting diode
- 29. b, c, LED, 1
- 30. cathode
- 31. current limiting
- 32. active LOW
- 33. 4
- 34. all segments, 8
- 35. 1. BCD to seven segment
 - 2. 8421 BCD to decimal
 - 3. Excess 3 to decimal
 - 4. Gray code to decimal
 - 5. BCD to binary
 - 6. Binary to BCD
- 36. limiting resistors
- 37. 0011
- 38. a, b, c; 7
- 39. HIGH, LOW
- 40. LOW
- 41. leading zeros
- 42. pulse $t_1 = 0$
 - pulse t_2 = blank display (not a BCD number)
 - pulse $t_3 = 2$
 - pulse $t_A = 8$
 - pulse $t_5 = 5$
 - pulse $t_6 = 3$
 - pulse $t_7 = 9$
- 43. pulse $t_1 = a, b, c, d, e, f$
 - pulse t_2 = blank display
 - pulse $t_3 = a, b, d, e, g$

- pulse $t_4 = a, b, c, d, e, f, g$
- pulse $t_5 = a, c, d, f, g$
- pulse $t_6 = a, b, c, d, g$
- pulse $t_{\gamma} = a, b, c, f, g$
- 44. T
- 45. sinking
- 46. common-anode
- 47. active LOW
- 48. OFF
- 49. black, silver
- 50. nematic
- 51. dc
- 52. very small amount
- 53. CMOS
- 54. 5
- 55. a, c, d, f, g
- 56. 180° out of phase
- 57. BCD, seven-segment
- 58. T
- 59. pulse $t_1 = 4$
 - pulse $t_2 = 2$
 - pulse $t_3 = 6$
 - pulse $t_{A} = 9$
 - pulse $t_5 = 1$
- 60. *b* and *c*
- 61. XOR
- 62. 4-bit latch
- 63. out-of-phase signals between inputs and common (backplane)
- 64. blue-green (also blue or green)
- 65. none
- 66. part A = grid
 - part B = cathode (heaters)
 - part C =plates
- 67. a, c, d, f, g; 5
- 68. CMOS, VF
- 69. limit current through cathodes to a safe level
- 70. pulse $t_1 = 3$
 - pulse $t_2 = 8$
 - pulse $t_3 = 7$
 - pulse $t_A = 0$
- 71. segment a-f = +12 V, segment g = GND
- 72. Use your senses to locate open or short circuits or ICs that are too hot.
- 73. short



Flip-Flops

Learning Dutcomes

This chapter will help you to:

- **7-1** Explain the function of each input and output on the R-S flip-flop. Use key words dealing with flip-flops, including set, reset, hold, active LOW, and active HIGH. Describe some uses of latches and their operation.
- **7-2** *Interpret* clocked R-S flip-flop waveforms and truth tables. *Explain* the modes of operation.
- **7-3** *Analyze* the truth table with modes of operation for the 7474 D flip-flop.
- **7-4** *Predict* the operation of several J-K flipflop ICs, including the toggle mode.
- **7-5** Describe the use and operation of the 7475 4-bit latch in a simple system.
- **7-6** *Classify* flip-flops as synchronous or asynchronous and *compare* triggering.
- **7-7** *Describe* the operation of Schmitt-triggered devices and *cite* some applications.
- **7-8** *Compare* traditional with IEEE/ANSI flipflop symbols.
- **7-9** Analyze and explain the operation of a latched encoder-decoder system.

ngineers classify logic circuits into two groups. We have already worked with combination logic circuits using AND, OR, and NOT gates. The other group of circuits is classified as sequential logic circuits. Sequential circuits involve timing and memory devices. The basic building block for combinational logic circuits is the logic gate. The basic building block for sequential logic circuits is the flip-flop (FF). This chapter covers several types of flip-flop circuits. In later chapters you will wire flip-flops together. Flip-flops are wired to form counters, shift registers, and various memory devices.

Combination logic circuits

Sequential logic circuits

Counters

Shift registers

Memory devices

7-1 The R-S Flip-Flop

The logic symbol for the R-S flip-flop is drawn in Fig. 7-1. Notice that the R-S flip-flop has two inputs, labeled S and R. The two outputs are labeled Q and \overline{Q} (say "not Q" or "Q not"). In flip-flops the outputs are always opposite, or complementary. In other words, if output Q=1, then output $\overline{Q}=0$, and so on. The R-S flip-flop symbol from Fig. 7-1 labels the outputs as normal and complementary. The letters S and R at the left of the R-S flip-flop symbol are often referred to as the set and reset inputs. The inputs are active LOW (see bubble).

The R-S flip-flop may also be referred to as an *R-S latch*. The term "latch" refers to its use as a temporary memory device. A latch such as the R-S flip-flop in Fig. 7-1 can hold one bit of information.

R-S flip-flop

Complementary

Set and reset

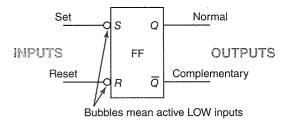


Fig. 7-1 Logic symbol for an R-S flip-flop.

Table 7-1	Truth	Table f	ir RS F	lip-Flap	
Mode of operation	Inpi S	uts R	Outp Q	uts	Effect on output Q
Prohibited	0	0	.1	1	Prohibited: Do not use
Set	0	1	1	0	For setting Q to 1
Reset	1	0	0	1	For resetting Q to 0
Hold	1	1	Q	\overline{Q}	Depends on previous state

The truth table in Table 7-1 details the operation of the R-S flip-flop. When the S and R inputs are both 0, both outputs go to a logical 1. This is called a *prohibited state* for the flip-flop and is not used. The second line of the truth table shows that when input S is 0 and R is 1, the Q output is set to logical 1. This is called the *set condition*. The third line shows that when input R is 0 and S is 1, output Q is reset (cleared) to 0. This is called the *reset condition*. Line 4 in the truth table shows both inputs (R and R) at 1. This is the idle or at rest condition and leaves R0 and R1 in their previous complementary states. This is called the *hold condition*.

From Table 7-1, it may be observed that it takes a logical 0 to activate the set (set Q to 1). It also takes a logical 0 to activate the reset, or clear (clear Q to 0). Because it takes a logical 0 to enable, or activate, the flip-flop, the logic symbol in Fig. 7-1 has invert bubbles at the R and S inputs. These invert bubbles indicate that the set and reset inputs are activated by a logical 0.

R-S flip-flops can be purchased in an IC package, or they can be wired from logic gates, as shown in Fig. 7-2. The NAND gates in Fig. 7-2 form an R-S flip-flop. This NAND-gate R-S flip-flop operates according to the truth table in Table 7-1. Technically, the R-S flip-flop in Fig. 7-2 might be referred to as an \overline{R} - \overline{S} flip-flop or \overline{R} - \overline{S} latch. The overbars above the R and S mean these are active LOW inputs. These overbars are used by some industry sources.

Many times *timing diagrams*, or *waveforms*, are given for sequential logic circuits. These diagrams show the voltage level and timing between inputs and outputs and are similar to what you would observe on an oscilloscope. The horizontal distance is *time*, and the vertical distance is *voltage*. Figure 7-3 shows the input waveforms (*R*, *S*)

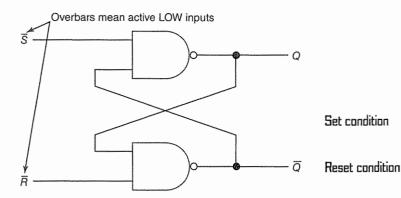



Fig. 7-2 Wiring an R-S flip-flop using NAND gates.

and the output waveforms (Q, \overline{Q}) for the R-S flip-flop. The bottom of the diagram lists the lines of the truth table from Table 7-1. The Q waveform shows the set and reset conditions of the output; the logic levels (0, 1) are on the right side of the waveforms. Waveform diagrams of the type shown in Fig. 7-3 are very common when dealing with sequential logic circuits. Study this diagram to see what it tells you. The waveform diagram is really a type of truth table.

Recall that there are three types of multivibrators (MVs). They are the monostable MV, the astable MV, and the bistable multivibrator. The R-S flip-flop is one of several bistable MVs. The R-S flip-flop is most commonly known as a latch and is listed under this heading in IC catalogs. A latch is a fundamental binary memory device for holding data. Latches are commonly used at the output of a digital device to hold the data until the next device is ready to receive the input. Latches are commonly organized into groups of 4-bits, 8-bits, or more into registers. An 8-bit register would be a group of eight latches holding a byte of information. You may recall that R-S flip-flops were also used for switch debouncing.

Hold condition

R-S latch

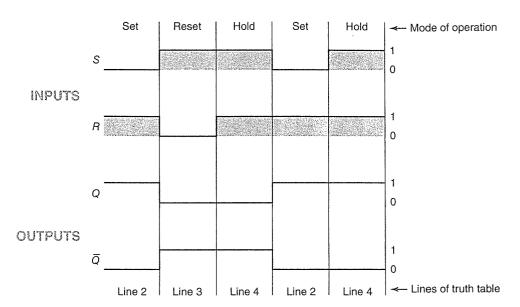

Waveform diagram

Fig. 7-3 Waveform diagram for an R-S flip-flop.

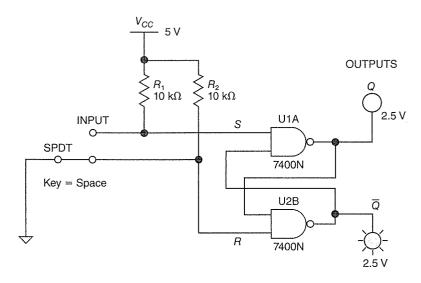


Fig. 7-4 SPDT switch debouncing circuit.

Internet Connection

Figure 7-4 shows the application of an R-S flip-flop in an SPDT switch debouncing circuit.

Commercial versions of the R-S flip-flop are available. One example is the 74LS279 Quad S-R Latch IC. It contains four latches like the one you studied from Fig. 7-2. Later in this chapter you will study the 7475/74LS75/74HC75 4-bit latch in detail.

Do you know the logic symbol and truth table for the R-S flip-flop? Do you know the four modes of operation for the R-S flip-flop?

Answer the following questions.

- 1. The R-S flip-flop in Fig. 7-1 has active __ (HIGH, LOW) inputs.
- 2. List the mode of operation of the R-S flip-flop for each input pulse shown in
- Fig. 7-5. Answer with the terms "set," "reset," "hold," and "prohibited."
- 3. List the binary output at the normal output (Q) of the R-S flip-flop for each of the pulses shown in Fig. 7-5.

Look up latch or SR latch at en.wikipedia .orq.

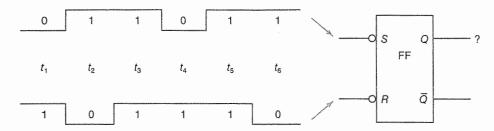


Fig. 7-5 R-S flip-flop pulse-train problem.



7-2 The Clocked R-S Flip-Flop

The logic symbol for a *clocked R-S flip-flop* is shown in Fig. 7-6. Observe that it looks almost like an R-S flip-flop except that it has one extra input labeled *CLK* (for clock).

The operation of the clocked R-S flip-flop is detailed in Fig. 7-7. The *CLK input* is at the top of the diagram. Notice that the clock pulse (1) has no effect on output Q with inputs S and R in the 0 position. The flip-flop is in the *idle*, or *hold*, mode during clock pulse 1. At the preset S position, the S (set) input is moved to 1, but output Q is not yet set to 1. The rising edge of clock pulse 2 permits Q to go to 1. Pulses 3 and 4 have no effect on output Q. During pulse 3, the flip-flop is in its set mode, and during pulse 4, it is in its hold mode. Next, input R is preset

to 1. On the rising edge of clock pulse 5, the Q output is reset (or cleared) to 0. The flip-flop is in the reset mode during both clock pulses 5 and 6. The flip-flop is in its hold mode during clock pulse 7; therefore, the normal output (Q) remains at 0.

Notice that the outputs of the clocked R-S flip-flop *change only on a clock pulse*. We say that this flip-flop operates *synchronously*;

Clocked R-S flip-flop

CLK input


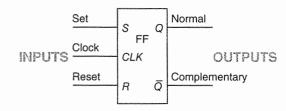


Fig. 7-8 Logic symbol for a clocked R-S flip-flop.

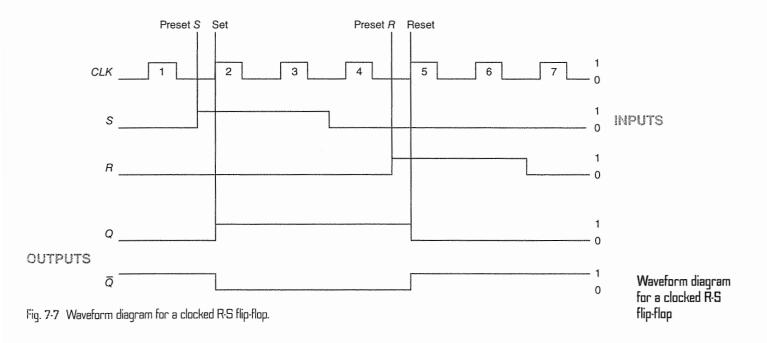

Flip-Flops Chapter 7

INPUTS OUTPUTS Mode of operation Effect on CLK S O R output Q No change Hold 0 No change Reset or 0 Reset O 1 1 cleared to 0 0 0 Set to 1 Set 1 Prohibited Prohibited do not use

(a)

Truth table for a clocked R-5 flip-flop

Wiring a clocked R-S flip-flop using CLK or enable $\bar{\alpha}$ (b)

Fig. 7-8 (a) Truth table for a clocked R-S flip-flop (b) Wiring a clocked R-S flip-flop using NAND gates.

Synchronous operation

NAND gates

Memory characteristic it operates in step with the clock. Synchronous operation is very important in most digital circuits, where each step must happen in an exact order.

Another characteristic of the clocked R-S flip-flop is that once it is set or reset, it stays that way even if you change some inputs. This is a memory characteristic, which is extremely valuable in many digital circuits. This characteristic is evident during the hold mode of operation. In the waveform diagram in Fig. 7-7, this flip-flop is in the hold mode during clock pulses 1, 4, and 7.

Figure 7-8(a) shows a truth table for the clocked R-S flip-flop. Notice that only the top three lines of the truth table are usable; the bottom line is prohibited and not used. Observe that the R and S inputs to the clocked R-S flipflop are active HIGH inputs. That is, it takes a HIGH on input S while R = 0 to cause output O to be set to 1.

Figure 7-8(b) shows a wiring diagram of a clocked R-S flip-flop. Notice that two NAND gates have been added to the inputs of the R-S flip-flop to add the clocked feature. The CLK input may be labeled with a C or E for enable by various manufacturers.

It is important to remember that the memory characteristics exhibited by flip-flops are among the fundamental reasons why digital technology has become so widely used in modern electronic products. It is strongly suggested that you actually experiment with R-S and clocked R-S flip-flops either on a circuit simulator or with actual ICs on a solderless breadboard. Operating flip-flops in the lab will help you better understand their operation.



Self-Test

Answer the following questions.

- 4. The set and reset inputs (S, R) of the clocked R-S flip-flop in Fig. 7-6 are active _____ (HIGH, LOW) inputs.
- 5. List the mode of operation of the clocked R-S flip-flop for each input pulse shown in Fig. 7-9. Answer with the terms "set," "reset," "hold," and "prohibited."
- 6. List the binary output at the normal output (Q) of the clocked R-S flip-

- flop for each of the pulses shown in Fig. 7-9.
- 7. To *set* a flip-flop means to cause the normal output (*Q*) to go _____ (HIGH, LOW).
- 8. Refer to Fig. 7-9. The *CLK* on this clocked R-S flip-flop might be labeled *EN* for ______ (encoder, enable) by some manufacturers.

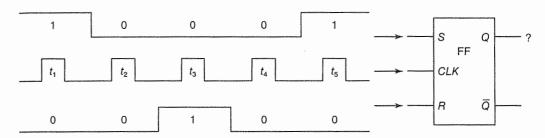


Fig. 7-9 Clocked R-S flip-flop pulse-train problem.



7-3 The D Flip-Flop

The logic symbol for the D flip-flop is shown in Fig. 7-10(a). It has only one data input (D) and a clock input (CLK). The outputs are labeled Q and \overline{Q} . The D flip-flop is often called a delay flip-flop. The word "delay" describes what happens to the data, or information, at input D. The data (a 0 or 1) at input D is delayed one clock pulse from getting to output Q. A simplified truth table for the D flip-flop is shown in Fig. 7-10(b). Notice that output Q follows input D after one clock pulse (see Q^{n+1} column).


A D flip-flop may be formed from a clocked R-S flip-flop by adding an inverter, as shown in Fig. 7-11. More commonly you will use a D flip-flop contained in an IC. Figure 7-12(a) shows a typical commercial D flip-flop. Two extra inputs [PS (preset) and CLR (clear)] have been added to the D flip-flop in Fig. 7-12(a). The PS input sets output Q to 1 when enabled by a logical 0. The CLR input clears output Q to 0 when enabled by a logical 0. The PS and CLR inputs will override the D and CLK inputs. The

D and CLK inputs operate as they did in the D flip-flops in Fig. 7-10.

Note the addition of a small triangle on the *CLK* input of the IC symbol in Fig. 7-12(a). This small triangle inside the 7474 IC symbol in Fig. 7-12(a) means the flip-flop is *edge-triggered*.

O flip-flop

Delay flip-flop Edge triggering

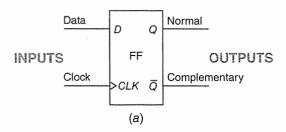

Input	Output			
D	Q ⁿ⁺¹			
0	0			
1	1			
(b)				

Fig. 7-10 D flip-flop. (a) Logic symbol (b) Simplified truth table.

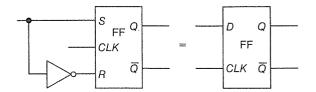


Fig. 7-11 Wiring a D flip-flop.

Synchronous operation


7474 TTL D flip-flop Shift registers Storage registers During synchronous operation, edge triggering means the bit of data present at input D is transferred to output Q on the positive edge (LOW-to-HIGH transition) of the clock pulse. The 7474 D flip-flop IC is said to be *positive-edge-triggered*.

A more detailed truth table for the commercial 7474 TTL D flip-flop is shown in Fig. 7-12(b). Remember that the asynchronous (not synchronous) inputs (PS and CLR) override the synchronous inputs. The asynchronous inputs are in control of the D flip-flop in the first three lines of the truth table in Fig. 7-12(b). The synchronous inputs (D and CLK) are irrelevant

as shown by the "X"s on the truth table. The prohibited condition, line 3 on the truth table, should be avoided.

With both asynchronous inputs disabled (PS = 1 and CLR = 1), the D flip-flop can be set and reset using the D and CLK inputs. The last two lines of truth table use a clock pulse to transfer data from input D to output Q of the flip-flop. Being in step with the clock, this is called *synchronous operation*. Note that this flip-flop uses the LOW-to-HIGH transition of the clock pulse to transfer data from input D to output Q.

D flip-flops are sequential logic devices which are widely used temporary memory devices. D flip-flops are wired together to form *shift registers* and *storage registers*. These registers are commonly used in digital systems. Remember that the D flip-flop *delays* data from reaching output *Q* one clock pulse and is called a *delay flip-flop*. D flip-flops are sometimes also called *data flip-flops*

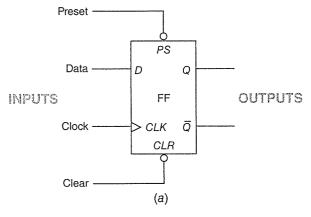

		INP	OUTPUTS			
Mode of operation	Asynchronous				Synchronous	
	PS	CLR	CLK	D	Q	Q
Asynchronous set	0	1	Х	Х	1	0
Asynchronous reset	1	0	Х	Х	0	1
Prohibited	0	0.11	Χ	Χ	1	- 1
Set	1	1	*	1	1	0
Reset	1	1	†	0	0	1

0 = LOW

1 = HIGH

X = Irrelevant

 \uparrow = LOW-to-HIGH transition of clock pulse

(b)

Fig. 7-12 (a) Logic symbol for commercial D flip-flop. (b) Truth table for 7474 D flip-flop.

or *D-type latches*. D flip-flops are available in both TTL and CMOS IC form. A few typical CMOS D flip-flops might be the 74HC74, 74AC74, 74FCT374, 74HC273, 74AC273,

4013, and 40174. D flip-flops are so popular with designers that more than 50 different ICs are available in just the FACT CMOS logic series.



Self-Test

Answer the following questions.

- 9. List the mode of operation of the 7474 D flip-flop for each input pulse shown in Fig. 7-13. Answer with the terms "asynchronous set," "asynchronous reset," "prohibited," "set," and "reset."
- 10. List the binary output at the normal output (Q) of the D flip-flop for each of the pulses shown in Fig. 7-13.
- 11. Refer to Fig. 7-12(a). The ">" at the *CLK* input means that this D flip-flop uses *edge triggering* (data transfers from *D* to *Q* on the LOW-to-HIGH transition of the clock pulse). (T or F)
- 12. Refer to Fig. 7-12. Both *PS* and *CLR* are _____ (active HIGH, active LOW) inputs to the 7474 D flip-flop.

7474 D flip-flop

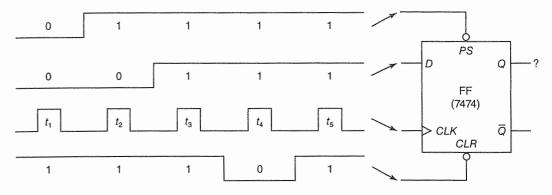


Fig. 7-13 D flip-flop problem for test items 9 and 10.



7-4 The J-K Flip-Flop

The J-K flip-flop has the features of all the other types of flip-flops. The logic symbol for the J-K flip-flop is illustrated in Fig. 7-14(a). The inputs labeled J and K are the data inputs. The input labeled CLK is the clock input. Outputs Q and \overline{Q} are the usual normal and complementary outputs on a flip-flop. A truth table for the J-K flip-flop is shown in Fig. 7-14(b). When the J and K inputs are both 0, the flip-flop is in the hold mode. In the hold mode, the data inputs have no effect on the outputs. The outputs "hold" the last data present.


Lines 2 and 3 of the truth table show the reset and set conditions for the *Q* output. Line 4

illustrates the useful *toggle* position of the J-K flip-flop. When both data inputs J and K are at 1, repeated clock pulses cause the output to turn off-on-off-on-off-on, and so on. This off-on action is like a toggle switch and is called *toggling*.

The logic symbol for the commercial 7476 $TTL\ J-K\ flip-flop$ is shown in Fig. 7-15(a). Added to the symbol are two asynchronous inputs (preset and clear). The synchronous inputs are the J and K data and clock inputs. The customary normal (Q) and complementary \overline{Q} outputs are also shown. A detailed truth table for the commercial 7476 $J-K\ flip-flop$ is drawn in Fig. 7-15(b). Recall that asynchronous inputs (such as PS and CLR) override synchronous inputs. The asynchronous inputs are activated

J-K flip-flop

Toggling

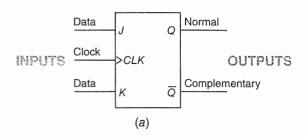

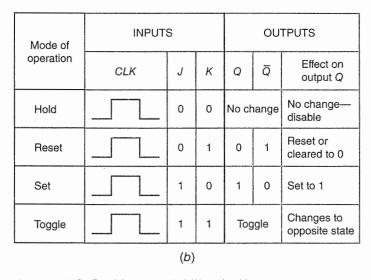


Fig. 7-14 J-K flip-flop. (a) Logic symbol. (b) Truth table.

in the first three lines of the truth table. The synchronous inputs are irrelevant (overridden) in the first three lines in Fig. 7-15(b); therefore, an "X" is placed under the *J*, *K*, and *CLK* inputs for these rows. The prohibited state occurs when both asynchronous inputs are activated at the same time. The prohibited state is not useful and should be avoided.

When both asynchronous inputs (PS and CLR) are disabled with a 1, the synchronous inputs can be activated. The bottom four lines of the truth table in Fig. 7-15(b) detail the hold, reset, set, and toggle modes of operation for the 7476 J-K flip-flop uses the entire pulse to transfer data from the J and K data inputs to the Q and \overline{Q} outputs.


A second commercial J-K flip-flop is the 74LS112 TTL-LS J-K flip-flop. The logic symbol for the 74LS112 J-K flip-flop is drawn in Fig. 7-16(a). The 74LS112 flip-flop features two active LOW asynchronous inputs (preset and clear). The two data inputs are labeled J and K. The clock (CLK) input has a bubble with the > symbol inside the block. This means that the 74LS112 flip-flop uses negative-edge triggering. In other words the flip-flop is activated on

the HIGH-to-LOW transition of the input clock pulse. The 74LS112 J-K flip-flop has the customary normal (Q) and complementary (\overline{Q}) outputs.

The pin diagram for a 16-pin DIP 74LS112 IC is sketched in Fig. 7-16(*b*). Notice that the 74LS112 IC contains two J-K flip-flops, both with asynchronous inputs (*PS* and *CLR*) and complementary outputs (Q and \overline{Q}). The 74LS112 IC is also available in other IC packages.

The truth table for the 74LS112 J-K flipflop is drawn in Fig. 7-16(c). The 74LS112 flip-flop has the same modes of operation as the 7476. The first three lines of the truth table show the asynchronous inputs (PS and CLR) overriding the synchronous inputs (J, K, and CLK). Notice that the asynchronous pins are active LOW inputs. The last four lines of the truth table detail the hold, reset, set, and toggle modes of operation. The *CLK* inputs triggers the flip-flop on the HIGH-to-LOW transition of the clock pulse. This is called negative-edge triggering. The last line of the truth table in Fig. 7-16(c) is the useful toggle mode. With the asynchronous inputs disabled (PS = 1, CLR = 1) and the data inputs both HIGH (J = 1, K = 1), each clock pulse will cause the

negative-edge triggering

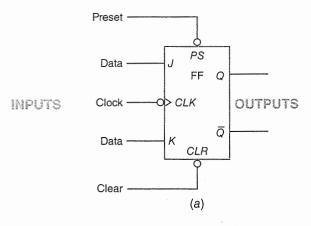

		-		OUTPUTS			
Mode of operation	Asynchronous		Synchronous			0017013	
	PS	CLR	CLK	J	К	Q	Q
Asynchronous set	0	1	X	X	Х	1	0
Asynchronous reset	1	0	Х	Х	X	0	1
Prohibited	0	Ò	×	X	Χ	1	1
Hold	1	1	5	0	0	No ch	nange
Reset	1	1		0	1	0	1
Set	1	1	ЛL	1	0	1	0
Toggle	1	1		1	1	Opposi	te state

7476 J-K flip-flop

0 = LOW

1 = HIGH

X = Irrelevant

r = Positive clock pulse

(b)

Fig. 7-15 $\,$ (a) Logic symbol for commercial J-K flip-flop. (b) Truth table for 7476 J-K flip-flop.

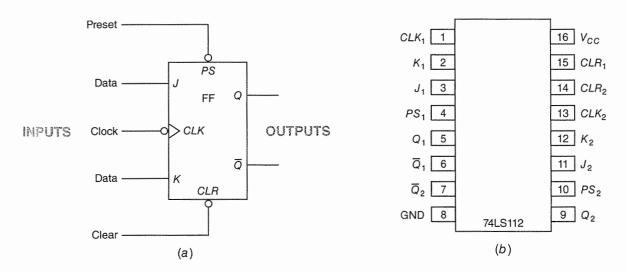


Fig. 7-16 74LS112 J-K flip-flop IC. (a) Logic symbol, (b) pin diagram.

1			OUTPUTS				
Mode of operation	Asynchronous				Synchronous		
	PS	CLR	CLK	J	К	Q	Q
Asynchronous set	0	1	×	×	×	1	0
Asynchronous reset	1	0	Х	Х	Х	0	1
Prohibited	0	0	X	X	X	1	1
Hold	1	1	\	0	0	No ch	ange
Reset	1	1	\	0	1	0	1
Set	1	1	\	1	0	1	0
Toggle	1	1	1	1	1	Opposi	te state

^{0 =} LOW

(c)

Fig. 7-16 (cont.) (c) truth table.

outputs to toggle to their opposite state. For instance, output Q might go from HIGH, LOW, HIGH, LOW, on repeated clock pulses. This is a useful feature when building circuits such as counters.

J-K flip-flops are used in many digital circuits. You will use the J-K flip-flop especially in *counters*. Counters are found in almost every digital system.

In summary, the J-K flip-flop is considered the "universal" flip-flop. Its unique feature is the toggle mode of operation so useful in designing counters. When the J-K flip-flop is wired for use only in the toggle mode, it is commonly called a *T flip-flop*. J-K flip-flops are available in both TTL and CMOS IC form. Typical CMOS J-K flip-flops are the 74HC76, 74AC109, and 4027 ICs.

T flip-flap

Counters

-√\- Self-Test

Answer the following questions.

- 13. List the mode of operation of the 7476

 J-K flip-flop after each input pulse shown in Fig. 7-17. Answer with the terms "asynchronous set," "asynchronous reset," "prohibited," "hold," "reset," "set," and "toggle."
- 14. List the binary output at the normal output (*Q*) of the J-K flip-flop after each of the pulses shown in Fig. 7-17.
- 15. Refer to Fig. 7-18. Both J-K flip-flops are in the _____ (reset, set, toggle) mode of operation in this circuit.
- 16. Refer to Fig. 7-18. The 74LS112 flip-flops used in this circuit are triggered on the ______ (HIGH-to-LOW, LOW-to-HIGH) transition of a clock pulse.
- 17. List the 2-bit binary output of the J-K flip-flops after each of the pulses shown in Fig. 7-18.
- 18. Refer to Fig. 7-18. The circuit using J-K flip-flops seems to operate as a 2-bit _____ (adder, counter).

^{1 =} HIGH

X = Irrelevant

^{↓ =} HIGH-to-LOW clock transition

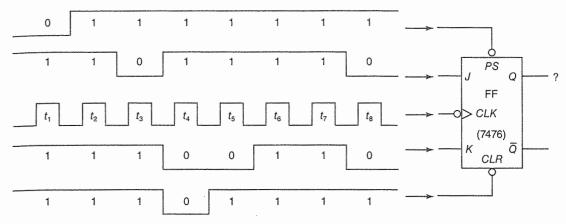


Fig. 7-17 J-K flip-flop problem for test items 13 and 14.

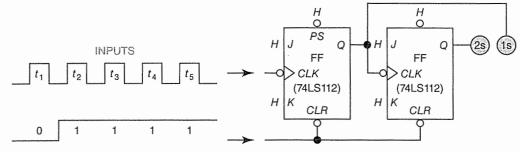


Fig. 7-18 J-K flip-flop problem for test items 15-18.



7-5 IC Latches

Consider the block diagram of the digital system in Fig. 7-19(a). Press and hold the decimal number 7 on the keyboard. A 7 will be observed on the seven-segment display. Release the 7 on the keyboard, and the 7 disappears from the display. It is

obvious that a *memory device* is needed to hold the BCD code for 7 at the inputs to the decoder. A device that serves as a temporary buffer memory is called a *latch*. A 4-bit latch has been added to the system in Fig. 7-19(b). Now when the decimal number 7 on the keyboard is *pressed and released*, the seven-segment display continues to show a 7.

Memory device

Latch


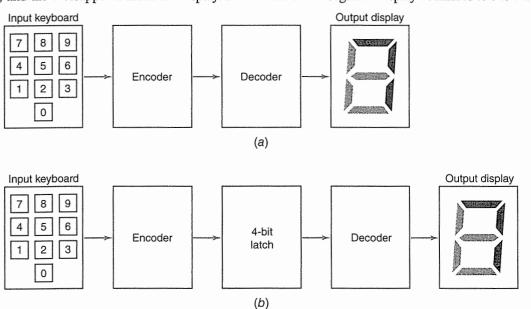


Fig. 7-19 Electronic encoder-decoder system. (a) Without buffer memory. (b) With buffer memory (latch) added.

Electronic encoderdecoder system

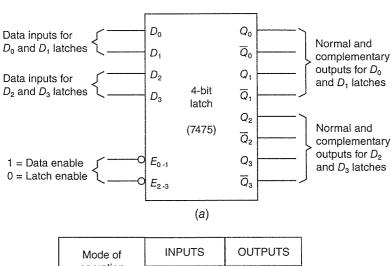

Mode of	INP	UTS	OUTPUTS		
operation	Ε	D	Q	Q	
	1	0	0	1	
Data enabled	1	1	1	0	
Data latched	0	Х	No ch	ange	

0 = LOW

1 = HIGH

X = Irrelevant

(b)

Fig. 7-20 (a) Logic symbol for commercial 7475 4-bit transparent latch. (b) Truth table for 7475 D latch.

Data-latched mode

D flip-flop

7475 TTL 4-bit transparent latch

Data latched

counters
shift registers
delay unit
frequency dividers

Data-enabled mode

The term "latch" refers to a digital storage device. The *D flip-flop* is a good example of a device used to latch data. However, other types of flip-flops are also used for the latching function.

Manufacturers have developed many latches in IC form. The logic diagram for the 7475 TTL 4-bit transparent latch is shown in Fig. 7-20(a). This unit has four D flip-flops enclosed in a single IC package. The D_0 data input and the normal Q_0 and complementary \overline{Q}_0 outputs form the first D flip-flop. The enable input (E_{0-1}) is similar to the clock input on the D flip-flop. When E_{0-1} is enabled, data at both D_0 and D_1 are transferred to their outputs.

A simplified truth table for the 7475 latch IC is shown in Fig. 7-20(b). If the enable input is at a logical 1, data is transferred, without a separate clock pulse, from the D input to the Q and \overline{Q} outputs. As an example, if $E_{0-1}=1$ and $D_1=1$, then without a clock pulse output Q_1 would be set to 1 while \overline{Q}_1 would be reset to 0. In the data-enabled mode of operation, the Q outputs follow their respective D inputs on the 7475 latch.

Consider the last line of the truth table in Fig. 7-20(*b*). When the enable input drops to 0, the

7475 IC enters the data-latched mode. The data that was at Q remains the same even if the D inputs change. The data is said to be latched. The 7475 IC is called a transparent latch because when the enable input is HIGH, the normal outputs follow the data at the D inputs. Note that the D_0 and D_1 flip-flops in the 7475 IC are controlled by the E_{0-1} enable input, whereas the E_{2-3} input controls the D_2 and D_3 pair of flip-flops.

One use of a flip-flop is to hold, or latch, data. When used for this purpose, the flip-flop is called a latch. Flip-flops have many other uses, including *counters*, *shift registers*, *delay units*, and *frequency dividers*.

Latches are available in all logic families. Several typical CMOS latches are the 4042, 4099, 74HC75, and 74HC373 ICs. Latches are sometimes built into other ICs such as the 4511 and 4543 BCD-to-seven segment latch/decoder/driver chips you may have already studied.

One of the primary advantages of digital over analog circuitry is the availability of easy-to-use memory devices. The latch is the most fundamental memory device used in digital electronics. Almost all digital equipment contains simple memory devices called latches.

Self-Test

Supply the missing word in each statement.

- 19. When the 7475 latch IC is in its dataenabled mode of operation, the ______ outputs follow their respective *D* inputs.
- 20. A _____ (HIGH, LOW) at the enable inputs places the 7475 latch IC in the data-latched mode of operation.
- 21. In the data-latched mode, a change at any of the *D* inputs to the 7475 latch IC has ______ (an immediate effect on their respective outputs; no effect on the outputs).
- 22. When a flip-flop is used to temporarily hold data, it is sometimes called



7-6 Triggering Flip-Flops

We have classified flip-flops as synchronous or asynchronous in their operation. *Synchronous flip-flops* are all those that have a clock input. We found that the clocked R-S, the D, and the J-K flip-flops operate in step with the clock.

When using manufacturers' data manuals, you will notice that many synchronous flip-flops are also classified as either edge-triggered or master/slave. Figure 7-21 shows two edge-triggered flip-flops in the toggle position. On clock pulse 1, the positive edge (positive-going edge) of the pulse is identified. The second waveform shows how the positive-edge-triggered flipflop toggles each time a positive-going pulse occurs (see pulses 1 to 4). On pulse 1 in Fig. 7-21, the negative edge (negative-going edge) of the pulse is also labeled. The bottom waveform shows how the negative-edge-triggered flipflop toggles. Notice that it changes state, or toggles, each time a negative-going pulse comes along (see pulses 1 to 4). Especially notice the difference in timing between the positive- and negative-edge-triggered flip-flops. This triggering time difference is quite important for some applications.

It is common to show the type of triggering on the flip-flop. The logic symbol for a D flip-flop with positive-edge triggering is shown in Fig. 7-22(a). Note the use of the small > inside the flip-flop logic symbol near the clock input. This > symbol says data are transferred to the output on the edge of the pulse. A logic symbol for a D flip-flop using negative-edge triggering is shown in Fig. 7-22(b). The added invert bubble at the clock input shows that triggering occurs on the negative-going edge of the clock pulse. Finally, a typical D latch symbol is shown in Fig. 7-22(c). Note the lack of a > symbol next to the enable (similar to a clock) input. This means that this unit is not considered an edge-triggered unit. Like the R-S flip-flop, the D latch is considered asynchronous. Recall that the D latch normal output (Q) follows its input Triggering flip-flops

Synchronous flip-flops

Positive-edgetriggered flip-flop

Negative-edgetriggered flip-flop

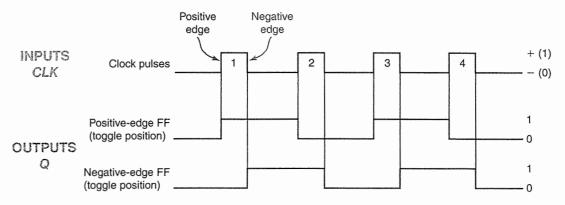


Fig. 7-21 Waveforms for positive- and negative-edge-triggered flip-flops.

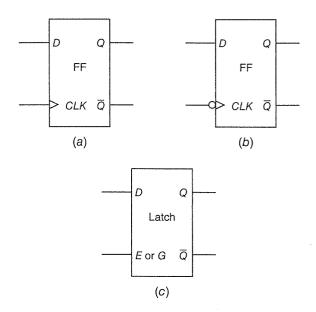


Fig. 7-22 (a) Logic symbol for positive-edge-triggered D flipflop. (b) Logic symbol for negative-edge-triggered D flip-flop. (c) Logic symbol for D latch.

(D) when the enable (E) input is HIGH. The data are latched when the enable input drops to LOW. Several manufacturers label the enable input with a "G" on the D latch.

Another class of flip-flop triggering is the master/slave type. The *J-K master/slave flip-flop* uses the entire pulse (positive edge and negative edge) to trigger the flip-flop. Figure 7-23 shows the triggering of a master/slave flip-flop.

Pulse 1 shows four positions (a to d) on the waveform. The following sequences of operation takes place in the master/slave flip-flop at each point on the clock pulse:

- Point *a*: Leading edge—isolate input from output.
- Point *b*: Leading edge—enter information from *J* and *K* inputs.
- Point c: Trailing edge—disable J and K inputs.
- Point *d*: Trailing edge—transfer information from input to output.

A very interesting characteristic of the master/slave flip-flop is shown during pulse 2, Fig. 7-23. Notice that at the beginning of pulse 2, the outputs are disabled. For a very brief moment, the J and K inputs are moved to the toggle positions (see point e) and then disabled. The J-K master/slave flip-flop "remembers" that the J and K inputs were in toggle positions, and it toggles at point f on the waveform diagram. This memory characteristic happens only while the clock pulse is HIGH (at logical 1).

Master/slave triggering has become obsolete with the newer edge-triggered flip-flops. For instance, the master/slave 7476 flip-flop is replaced by the 74LS76 device. It has the same pin diagrams and functions, but the newer 74LS76 IC uses negative-edge triggering.

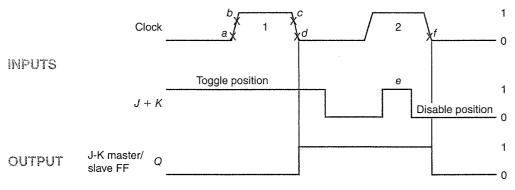


Fig. 7-23 Triggering the J-K master/slave flip-flop.

J-K master/ slave flip-flop

Triggering the J-K master/slave flip-flop.

-⁄∿- Self-Tesi

Supply the missing word in each statement.

- 23. A positive-edge-triggered flip-flop changes state on the _____ (HIGH-to-LOW, LOW-to-HIGH) transition of the clock pulse.
- 24. A negative-edge-triggered flip-flop changes state on the _____ (HIGH-to-LOW, LOW-to-HIGH) transition of the clock pulse.

- 25. The ">" near the clock input inside a flip-flop logic symbol means _____
- 26. The 74LS112 J-K flip-flop detailed in Fig. 7-16 uses ______ (positive-edge triggering, negative-edge triggering).
- 27. The 7474 D flip-flop detailed in Fig. 7-12 uses _____ (positive-edge triggering, negative-edge triggering).
- 28. J-K master/slave flip-flops (such as the 7476 IC) using the entire pulse to trigger the unit have become obsolete, replaced by the newer edge-triggered flip-flops. (T or F)



7-7 Schmitt Trigger

Digital circuits prefer waveforms with fast *rise* and fall times. The waveform on the right side of the inverter symbol in Fig. 7-24 is an example of a good digital signal. The square wave's L-to-H and H-to-L edges are vertical. This means that the rise and fall times are very fast (almost instantaneous).

The waveform to the left of the inverter symbol in Fig. 7-24 has very slow rise and fall times. The poor waveform on the left in Fig. 7-24 might lead to unreliable operation if fed directly into counters, gates, or other digital circuitry. In this example, a *Schmitt-trigger inverter* is being used to "square up" the input signal and make it more useful. The Schmitt trigger in Fig. 7-24 is reshaping the waveform. This is called *signal conditioning*. Schmitt triggers are widely used in *signal conditioning*.

A voltage profile of a typical TTL inverter (7404 IC) is reproduced in Fig. 7-25(a). Of special interest is the *switching threshold* of the 7404 IC. The switching threshold may vary from chip to chip, but it is always in the undefined region. Figure 7-25(a) shows that a typical 7404 IC has a switching threshold of +1.2 V. In other words, when the voltage rises to +1.2 V, the output changes from HIGH to LOW. However, if the

voltage drops below +1.2 V, the output switches from LOW to HIGH. Most regular gates have a single switching threshold voltage whether the input voltage is rising (L to H) or falling (H to L).

A voltage profile for a 7414 Schmitt-trigger inverter TTL IC is sketched in Fig. 7-25(b). Note that the switching threshold is different for positive-going (V +) and negative-going (V -) voltages. The voltage profile for the 7414 IC shows that the switching threshold is 1.7 V for a positive-going (V+) input voltage. However, the switching threshold is 0.9 V for a negative-going (V-) input voltage. The difference between these switching thresholds (1.7 V and 0.9 V) is called hysteresis. Hysteresis provides for excellent noise immunity and helps the Schmitt trigger square up waveforms with slow rise and fall times.

Schmitt triggers are also available in CMOS. These include the 40106, 4093, 74HC14, and 74AC14 ICs.

One of the characteristics of a bistable multivibrator (or flip-flop) is that its outputs are either HIGH or LOW. When changing states (H to L or L to H), they do so rapidly without the outputs being in the undefined region. This "snap action" of the output is also characteristic of Schmitt triggers.

Rise and fall times

7414 Schmitttrigger inverter TTL IC

Schmitt-trigger inverter Hysteresis

Signal conditioning

Switching threshold

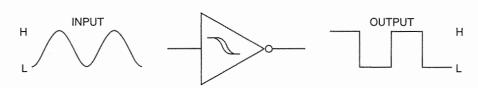


Fig. 7-24 Schmitt trigger used for wave shaping.

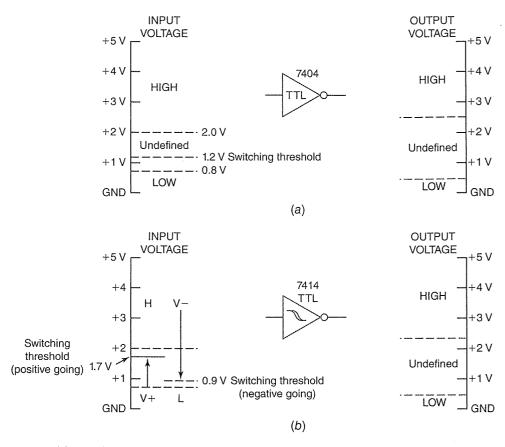


Fig. 7-25 (a) TTL voltage profiles with switching threshold. (b) Voltage profiles for 7414 TTL Schmitt-trigger IC showing switching thresholds.



Answer the following questions.

- 29. The ______ is a good device for squaring up a waveform with slow rise and fall times.
- 30. Draw the schematic symbol for a Schmitt-trigger inverter.
- 31. A Schmitt trigger is said to have _____ because its switching thresholds are different for positive-going and negative-going inputs.
- 32. Schmitt triggers are commonly used for _____ (memory, signal conditioning).



IEEE logic symbols

7-8 IEEE Logic Symbols

The flip-flop logic symbols you have learned are the traditional ones recognized by most workers in the electronics industry. Manufacturers' data manuals usually include traditional symbols and are including new IEEE standard logic symbols.

The table in Fig. 7-26 shows the traditional flip-flop and latch logic symbols learned in this

chapter along with their IEEE counterparts. All IEEE logic symbols are rectangular and include the number of the IC directly above the symbol. Smaller rectangles show the number of duplicate devices in the package. Notice that all inputs are on the left of the IEEE symbol and outputs are on the right.

The IEEE 7474 D flip-flop symbol shows four inputs labeled "S" (for "set"), ">C1" (for "positive-edge-triggered clock"), "1D"

Flip-Flop/ Latch IC	Traditional Logic Symbol	IEEE Logic Symbol*
7474 TTL Dual D Flip-flop	Preset ———————————————————————————————————	7474 1 Preset
7476 TTL Dual Master/ Slave J-K Flip-flop	Preset — PS Q FF Clock — CLK (7476) K Q CLR	7476 1 Preset
7475 TTL 4-bit Transparent Latch	$\begin{array}{c} \text{Data} & \left\{ \begin{array}{c} - & D_0 & Q_0 \\ - & D_1 & \bar{Q}_0 \\ - & D_2 & Q_1 \\ - & D_3 & Q_2 \\ - & D_3 & Q_2 \\ - & D_3 & Q_3 \\ - & D_3 & D_3 \\ - $	7475 1 Data — 1D — 1Q Enable — C1 — 1Q 2 Data — 2D — 2Q 2 Data — 3D — 3Q Enable — C3 — 3Q Enable — C4 — 4Q 4 Data — 4D — 4Q

*IEEE Standard 91-1984

Fig. 7-26 Comparing traditional and IEEE symbols for several flip-flops.

(for "data"), and "R" (for "reset"). The triangles at the S and R inputs on the IEEE 7474 symbol identify them as active LOW inputs. The 7474 outputs are on the right of the IEEE symbol with no internal identifying markings. The \overline{Q} outputs have triangles suggesting active LOW outputs. The markings inside the IEEE logic symbols are standard while the outside markings vary from manufacturer to manufacturer.

Consider the IEEE logic symbol for the 7476 dual master/slave J-K flip-flop in Fig. 7-26. The internal inputs are marked "S" ("set"), "1J" ("J data"), "C1" ("Clock"), "1K" ("K data"), and "R" ("reset"). The "7476" above the symbol identifies the specific TTL

IC. The markings near the Q and \overline{Q} outputs are the unique IEEE symbols for pulse triggering. The IEEE logic symbol for the 7476 IC shows that there are two active LOW inputs (S and R) and a single active LOW output (\overline{Q}) on each J-K flip-flop. The active LOW inputs and outputs are marked with a small right triangle. The symbol is repeated below to indicate that the 7476 IC package contains two identical J-K flip-flops.

The IEEE standard logic symbol for the 7475 4-bit transparent latch is reproduced in Fig. 7-26. Note the four rectangles to represent the four D-type latches in the 7475 IC package. The four \overline{Q} output leads are marked with small triangles.

Answer the following questions.

- 33. The "C" marking inside the IEEE symbol stands for the control input or the _____ inputs on the flip-flops.
- 34. The complementary (\overline{Q}) outputs of the flip-flops and latches on an IEEE symbol
- are designated with the _____symbol.
- 35. The asynchronous clear on the 7474 and 7476 flip-flop are active ______ inputs and are marked with the letter "R," which stands for _____.



7-9 Application: Latched Encoder-Decoder System

You have worked hard learning the detailed operation of various logic gates, encoders, decoders, flip-flops, and input/output devices. Now you apply your knowledge of digital devices as these components are connected together to form a simple digital system.

A simplified block diagram of the latched encoder-decoder system is reproduced in Fig. 7-27. The encoder translates one of eight inputs from the keypad to inverted binary form. The latch-enable circuitry generates a positive pulse for each keystroke. This positive pulse (latch-enable pulse) causes the transfer of the encoder output to the complementary \overline{Q} outputs of the 3-bit latch. This latches normal binary that can be observed on the three LEDs at the top center. The 3-bit latch holds binary data at the decoder inputs. The decoder translates from

binary-to-seven-segment code, lighting the proper segments of the LED display.

The task of entering a single decimal number and having it appear on a seven-segment displays seems simple. The electronics to make this happen is fairly complex and well suited to using ICs that contain many gates. It has been calculated that for using the ICs called for in Fig. 7-28, the gate count would total from 60 to 90.

A wiring diagram will be developed from the block diagram sketched in Fig. 7-27. Components that you have studied will be used to implement a working version of the latched encoder-decoder system.

A detailed wiring diagram of the latched encoder-decoder circuit is reproduced in Fig. 7-28. The circuit was constructed using Multisim.

A summary of the features are:

 Input: Keypad with eight active LOW normally open switches.


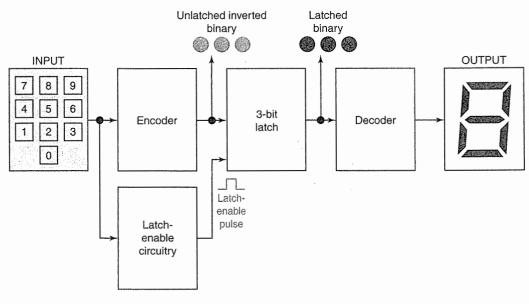


Fig. 7-27 Block diagram of a latched encoder-decoder system.

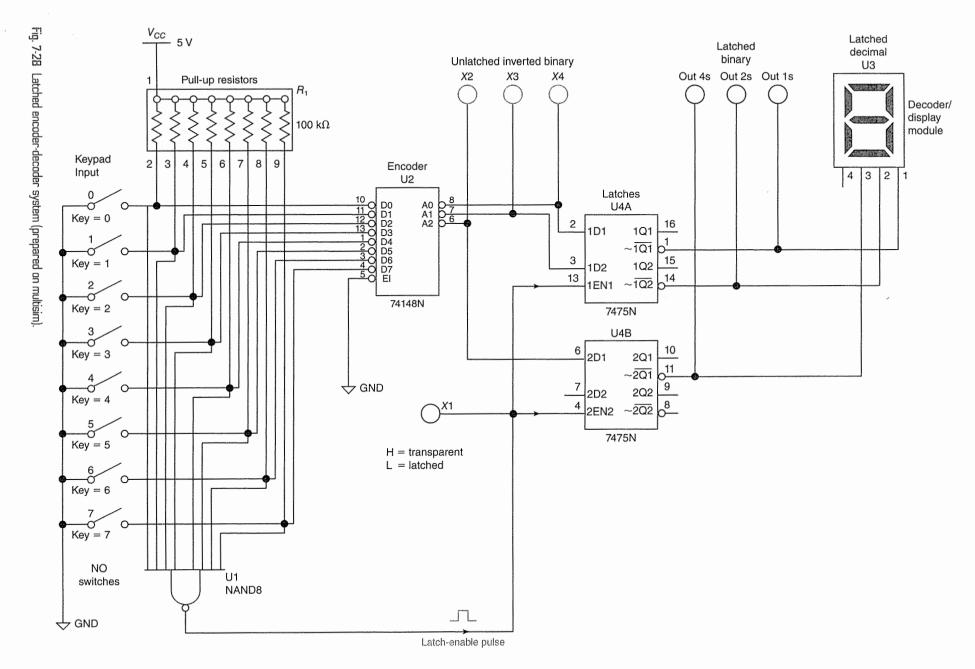

- Encoder: 74148 8-line-to-3-line priority encoder with active LOW inputs and active LOW outputs. Eight pull-up resistors hold the eight encoder inputs HIGH until driven LOW by keypad input(s).
- Decoder: A binary-to-seven-segment display decoder/driver with active HIGH inputs is embedded in the decoder/ display module.
- Outputs: (1) 3-bit-unlatched inverted binary display, (2) 3-bit-latched binary display, and (3) seven-segment LED display embedded in the decoder/display module.
- Memory: 7475 4-bit transparent latch with active HIGH inputs and active LOW outputs. Only three of the four latches are used in this circuit. Data latched with enable (EN) inputs are LOW. Data pass from inputs to outputs when EN inputs are pulsed HIGH. The latch is said to be transparent during the HIGH pulse.
- Latch-enable circuits: The eight-input NAND logic gate emits a HIGH, only when one or more inputs go LOW. With all inputs HIGH, the output of the NAND is LOW, which causes the 7475 latches to remain latched (not transparent).

Example: Power ON. **Press decimal 1** on the keypad, activating input *D*1 of the encoder IC. The 74l48 IC generates the inverted binary 110 (1s complement of binary 001). The 110 (inverted binary) is passed on to the data inputs of the 7475 4-bit latch IC (3 bits used in this circuit).

Pressing decimal 1 on the keypad in this example also causes the eight-input NAND gate (latch-enable circuitry) to output a HIGH. This HIGH activates transparent mode of the 7475 IC as it enters the EN inputs. The positive latch-enable pulse causes the 7475 latch IC to become transparent for an instant and transfer the inverted binary 110 to the complementary outputs (Q), where it becomes the true binary value of 001. As input switch 1 returns to its open position, it outputs HIGH. All inputs to the eight-input NAND gate are now HIGH because of the eight pull-up resistors (R_1) causing the gate's output to go LOW. When the EN input to the 7475 goes LOW, binary data 001 are latched at the complementary outputs (\overline{Q}) and held at the inputs of the decoder/display module.

The seven-segment decoder translates the 001 binary to seven-segment code, activating both segments a and b. This drives the LED display, forming the decimal 1.

The 74148 IC is referred to as a *priority* encoder. The priority feature means that if two or more inputs are activated at one time, the higher-value input will be output. In other words, if both the 2 and 4 inputs to the 74148 encoder go LOW, the IC will generate the 011 (1s complement for binary 100), which will read 4 on the seven-segment display.

The latched encoder-decoder in Fig. 7-28 is an experimental circuit. This circuit uses components and digital devices that you have used in earlier experiments.

-√v- Self-Tesi

Answer the following questions.

- 36. Refer to Fig. 7-28. If all switches on the keypad are open, then the output from the eight-input NAND gate is ______(HIGH, LOW).
- 37. Refer to Fig. 7-28. The 74148 encoder has both active LOW inputs and active LOW outputs. (T or F)
- 38. Refer to Fig. 7-28. If input key 6 is pressed and released, the latched binary

- will be _____ [3-bit binary] and the seven-segment display will read decimal _____ (decimal number).
- 39. Refer to Fig. 7-28. In this circuit, the latches are used as a type of temporary (memory, multiplexer).
- 40. Refer to Fig. 7-28. The ______ (74148, 7475) IC converts the inverted binary to true binary.



Chapter 7 Summary and Review



Summary

- Logic circuits are classified as combinational or sequential. Combinational logic circuits use AND, OR, and NOT gates and do not have a memory characteristic. Sequential logic circuits use flipflops and involve a memory characteristic.
- 2. Flip-flops are wired together to form counters, registers, and memory devices.
- 3. Flip-flop outputs are opposite, or complementary.
- 4. The table in Fig. 7-29 summarizes some basic flip-flops.

- 5. Waveform (timing) diagrams are used to describe the operation of sequential devices.
- 6. Flip-flops can be edge-triggered or master/slave types. Flip-flops can be pulse- or edge-triggered.
- 7. Special flip-flops called latches are widely used in most digital circuits as temporary buffer memories.
- 8. Schmitt triggers are special devices that are used for signal conditioning.
- 9. Figure 7-26 compares traditional flip-flop/latch symbols with the newer IEEE logic symbols.

Circuit	Logic Symbol	Truth Table	Remarks
R-S flip-flop	-OS Q - FF -OR Q -	S R Q 0 0 prohibited 0 1 1 set 1 0 0 reset 1 1 hold	R-S latch Set-reset flip-flop (asynchronous)
Clocked R-S flip-flop	- S Q - FF Q - CLK - R Q -	CLK S R Q 0 0 hold 0 1 0 reset 1 0 1 set 1 1 prohibited	(synchronous)
D flip-flop	→ D Q → FF → CLK Q →	$ \begin{array}{c cccc} CLK & D & Q \\ & \uparrow & 0 & 0 \\ \hline & \uparrow & 1 & 1 \end{array} $ $ \uparrow = \text{L-to-H transition of clock} $	Delay flip-flop Data flip-flop (synchronous)
J-K flip-flop	J Q FF Q CLK K Q	CLK J K Q ↓ 0 0 hold ↓ 0 1 0 reset ↓ 1 0 1 set ↓ 1 1 toggle # = H-to-L transition of clock	Most universal FF (synchronous)

Fig. 7-29 Summary of basic flip-flops.

Chapter Review Questions

Answer the following questions.

- 7-1. Logic ______ are the basic building blocks of combinational logic circuits; the basic building blocks of sequential circuits are devices called ______.
- 7-2. List one type of asynchronous and three types of synchronous flip-flops.
- 7-3. Draw a traditional logic symbol for the following flip-flops:
 - a. J-K
- c. Clocked R-S
- b. D
- d. R-S
- 7-4. Draw a truth table for the following flip-flops:
 - a. J-K (with negative-edge triggering)
 - b. D (with positive-edge triggering)
 - c. Clocked R-S
 - d. R-S
- 7-5. If both synchronous and the asynchronous inputs on a J-K flip-flop are activated, which input will control the output?
- 7-6. When we say the flip-flop is in the set condition, we mean output ______ is at a logical _____.
- 7-7. When we say the flip-flop is in the reset, or clear, condition, we mean output _______ is at a logical ______.
- 7-8. On a timing, or waveform, diagram the horizontal distance stands for _____ and the vertical distance stands for _____.

- 7-9. Refer to Fig. 7-7. This waveform diagram is for a(n) _____ flip-flop. This flip-flop is _____ -edge triggered.
- 7-10. List two types of edge-triggered flip-flops.
- 7-11. The "D" in a "D flip-flop" stands for ______, or data.
- 7-12. D flip-flops are widely used as temporary memories called
- 7-13. If a flip-flop is in its toggle mode of operation, what will the output act like upon repeated clock pulses?
- 7-14. Identify these acronyms used on traditional flip-flop logic symbols:
 - a. CLK
- e. PS
- b. CLR
- f. R
- c. D
- g. S
- d. FF
- 7-15. Give a descriptive name for the following TTL ICs:
 - a. 7474
 - b. 7475
 - c. 74LS112
- 7-16. The 7474 IC is a(n) ______ -edge-triggered unit.
- 7-17. List the modes of operation of the 7474 IC.
- 7-18. List the mode of operation of the 7476 J-K flip-flop for each input pulse shown in Fig. 7-30.
- 7-19. List the binary outputs at the normal output (Q) of the J-K flip-flop after each time period (t_1 - t_7) shown in Fig. 7-30.

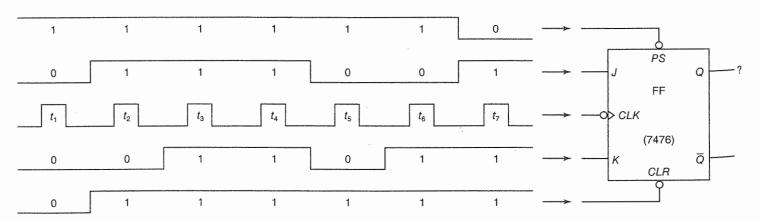


Fig. 7-30 Pulse-train problem.

Chapter Review Questions...continued

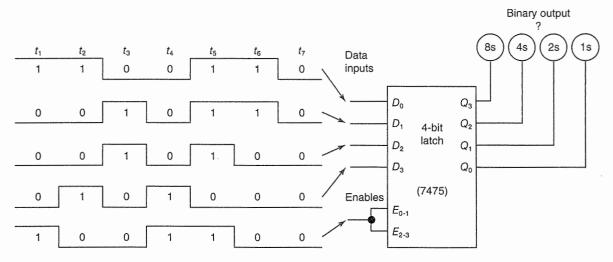


Fig. 7-31 Pulse-train problem.

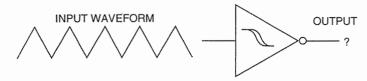


Fig. 7-32 Sample problem.

- 7-20. List the mode of operation of the 7475 4-bit latch for each time period (t_1 through t_7) shown in Fig. 7-31.
- 7-21. List the binary output (4-bit) at the output indicators of the 7475 4-bit latch for each time period (t_1 through t_2) shown in Fig. 7-31.

- 7-22. Refer to Fig. 7-32. The output waveform on the right of the logic symbol will be a _____ (sine, square) wave.
- 7-23. The inverter in Fig. 7-32 is being used as a signal _____ (conditioner, multiplexer) in this circuit.
- 7-24. The logic symbol in Fig. 7-32 is for a symbol _____ [two words] inverter IC.
- 7-25. Identify these markings found inside and on the leads of the IEEE flip-flop/latch logic symbols.
 - a. *C*
- e. J
- b. *S*
- f. *K*
- c. R
- g. ¬
- d. D
- h. >C

Critical Thinking Questions

- 7-1. List two other names sometimes given for an R-S flip-flop.
- 7-2. Explain the difference between asynchronous and synchronous devices.
- 7-3. Draw the traditional and IEEE logic symbols for a D flip-flop (7474 IC) and a J-K flip-flop (7476 IC).
- 7-4. Refer to Fig. 7-3. Notice that line 4 is listed two times across the bottom. Why does output Q = 0 in the first case and then 1 in the second case when inputs R and S are both 1 in each case?
- 7-5. Explain how the 74LS112 J-K flip-flop is triggered.

- 7-6. What is the fundamental difference between a combinational logic and a sequential logic circuit?
- 7-7. List several devices that are built using J-K flip-flops.
- 7-8. Explain why Schmitt-trigger devices tend to "square up" inputs with slow rise times.
- 7-9. At the option of your instructor, use circuit simulation software to (1) draw the flip-flop circuit sketched in Fig. 7-33; (2) test the operation of the flip-flop circuit; (3) make a truth table for the flip-flop (something like Table 7-1) listing the modes of operation as "set," "reset," "hold,"

Critical Thinking Questions ...continued

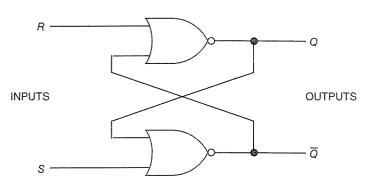


Fig. 7-33 Flip-flop circuit.

and "prohibited"; and (4) determine if it acts more like an R-S or a J-K flip-flop.

7-10. At the option of your instructor, use circuit simulation software to (a) draw the circuit shown in Fig. 7-34 using a generic J-K flip-flop with negative-edge triggering, (b) test the operation of the circuit trying to determine the function of the circuit (such as adder, counter, shift register), and (c) show your instructor your circuit simulation.

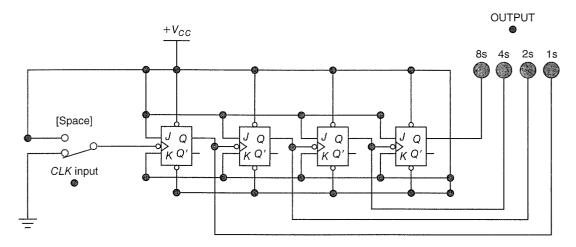


Fig. 7-34 Circuit showing the application of J-K flip-flops.



Answers to Self-Tests

- 1. LOW
- 2. pulse $t_1 = \text{set}$
 - pulse t_2 = reset
 - pulse $t_3 = \text{hold}$
 - pulse $t_{4} = set$
 - pulse $t_5 = \text{hold}$
 - pulse t_6 = reset
- 3. pulse $t_1 = 1$
 - pulse $t_2 = 0$

 - pulse $t_3 = 0$
 - pulse $t_{A} = 1$
 - pulse $t_5 = 1$
 - pulse $t_6 = 0$
- 4. HIGH
- 5. pulse $t_1 = \text{set}$ pulse t_2 = hold


- pulse t_3 = reset
- pulse $t_4 = \text{hold}$
- pulse $t_5 = \text{set}$
- 6. pulse $t_1 = 1$
- pulse $t_2 = 1$

 - pulse $t_3 = 0$
 - pulse $t_{A} = 0$
 - pulse $t_5 = 1$
- 7. HIGH
- 8. enable
- 9. pulse t_1 = asynchronous set
 - (or preset)
 - pulse t_2 = reset
 - pulse $t_3 = \text{set}$
 - pulse t_4 = asynchronous reset (or clear)
 - pulse $t_5 = \text{set}$

- 10. pulse $t_1 = 1$
 - pulse $t_2 = 0$
 - pulse $t_3 = 1$

 - pulse $t_{4} = 0$
 - pulse $t_5 = 1$
- 11. T
- 12. active LOW
- 13. pulse t_1 = asynchronous set (or preset)
 - pulse $t_2 = \text{toggle}$
 - pulse t_3 = reset
 - pulse t_4 = asynchronous reset (or clear)
 - pulse $t_5 = \text{set}$
 - pulse $t_6 = \text{toggle}$
 - pulse $t_7 = \text{toggle}$
 - pulse $t_{g} = \text{hold}$
- 14. pulse $t_1 = 1$
 - pulse $t_2 = 0$
 - pulse $t_3 = 0$
 - pulse $t_4 = 0$
 - pulse $t_5 = 1$
 - pulse $t_6 = 0$
 - pulse $t_7 = 1$
 - pulse $t_8 = 1$
- 15. toggle
- 16. HIGH-to-LOW
- 17. pulse $t_1 = 00$
- pulse $t_2 = 01$
 - pulse $t_3 = 10$
 - pulse $t_4 = 11$
 - pulse $t_5 = 00$

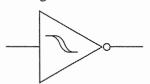- 18. counter
- 19. *Q* (normal)
- 20. LOW
- 21. no effect on the outputs
- 22. latch
- 23. LOW-to-HIGH
- 24. HIGH-to-LOW
- 25. edge-triggering
- 26. negative-edge triggering
- 27. positive-edge triggering
- 28. T
- 29. Schmitt trigger
- 30. See figure below



- 31. hysteresis
- 32. signal conditioning
- 33. clock
- 34. triangle
- 35. LOW, reset
- 36. LOW
- 37. T
- 38. 110,, 6
- 39. memory
- 40. 7475



Counters

Learning Outcomes

This chapter will help you to:

- **8-1** *Draw* a circuit diagram of a ripple counter using J-K flip-flops.
- **8-2** Convert a 4-bit ripple counter to mod-10 (decade) counter.
- **8-3** Analyze the circuit action of any mod-3 through mod-8 synchronous counter.
- **8-4** Analyze the circuit action of ripple down counters.
- **8-5** Explain the action of down counters with a self-stopping feature.
- **8-6** *Understand* the operation and *draw* a block diagram of a frequency divider circuit.
- **8-7** Interpret the data sheets for two TTL counter ICs (7493 4-bit counter and 74192 up/down decade counter). Characterize the operation of several circuits using TTL counters.
- 8-8 Interpret the data sheets for two CMOS counter ICs (74HC393 4-bit binary counter and 74HC193 4-bit binary up/down counter). Summarize the operation of several circuits using CMOS counters.
- 8-9 Investigate the features of the 4553 three-digit BCD counter. Analyze the operation of a three-digit decimal counter with multiplexed displays (using 4553 BCD counter and 4543 BCD-to-seven-segment decoder/driver ICs).
- **8-10** Determine the operation of an optical sensor used as input transducer. Demonstrate knowledge of a counter system using optical encoding of a shaft encoder disk.
- **8-11** *Predict* the operation of a magnitude comparator (74HC85 4-bit magnitude comparator). *Explain* the operation of a simple electronic game using a magnitude comparator.
- 8-12 Analyze and discuss the operation of a complex electronic tachometer. The experimental tachometer features a Hall-effect switch input, one-shot MV input, three-digit BCD counter (4553 IC), seven-segment decoder/driver (4543 IC), and three multiplexed seven-segment displays.
- **8-13** *Troubleshoot* a simple ripple counter.

lmost any complex digital system contains several counters. A counter's job is the obvious one of counting events or periods of time or putting events into sequence. Counters also do some not so obvious jobs: dividing frequency, addressing, and serving as memory units. This chapter discusses several types of counters and their uses. Flip-flops are wired together to form circuits that count. Because of the wide use of counters, manufacturers also make self-contained counters in IC form. Many counters are available in all TTL and CMOS families. Some counter ICs contain other devices such as signal conditioning circuitry, latches, and display multiplexers.

8-1 Ripple Counters

Counting in binary and decimal is illustrated in Fig. 8-1. With four binary places (D, C, B, and A), we can count from 0000 to 1111 (0 to 15 in decimal). Notice that column A is the 1s binary place, or least significant digit (LSD). The term "least significant bit" (LSB) is usually used. Column D is the 8s binary place, or most significant digit (MSD). The term "most significant bit" (MSB) is usually used. Notice that the 1s column changes state the most often. If we design a counter to count from binary 0000 to 1111, we need a device that has 16 different output states: a modulo-16 (mod-16) counter. The modulus of a counter is the number of different states the counter must go through to complete its counting cycle.

A mod-16 counter using four J-K flip-flops is diagrammed in Fig. 8-2(a). Each J-K flip-flop is in its toggle position (*J* and *K* both at 1). Assume the outputs are cleared to 0000. As clock pulse 1 arrives at the clock (*CLK*) input of flip-flop 1 (FF 1), it toggles (on the negative

LSB

MSB

Modulo-16 counter

Modulus of a counter

E	BINARY C	à		
D	С	В	Α	DECIMAL COUNTING
8s	4s	2s	1s	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

Fig. 8-1 Counting sequence for a 4-bit electronic counter.

edge) and the display shows 0001. Clock pulse 2 causes FF 1 to toggle again, returning output Q to 0, which causes FF 2 to toggle to 1. The count on the display now reads 0010. The counting continues, with each flip-flop output triggering the next flip-flop on its negative-going pulse. Look back at Fig. 8-1 and see that column A (1s column) must change state on every count. This means that FF 1 in Fig. 8-2(a) must toggle for each pulse. FF 2 must toggle only half as often as FF 1, as seen from column B in Fig. 8-1. Each more significant bit in Fig. 8-1 toggles less often.

The counting of the mod-16 counter is shown up to a count of decimal 10 (binary 1010) by waveforms in Fig. 8-2(b). The *CLK* input is shown on the top line. The state of each flipflop (FF 1, FF 2, FF 3, FF 4) is shown on the waveforms below. The *binary count* is shown across the bottom of the diagram. Especially note the vertical lines on Fig. 8-2(b); these lines show that the clock triggers only FF 1. FF 1 triggers FF 2, FF 2 triggers FF 3, and so on.

Binary count

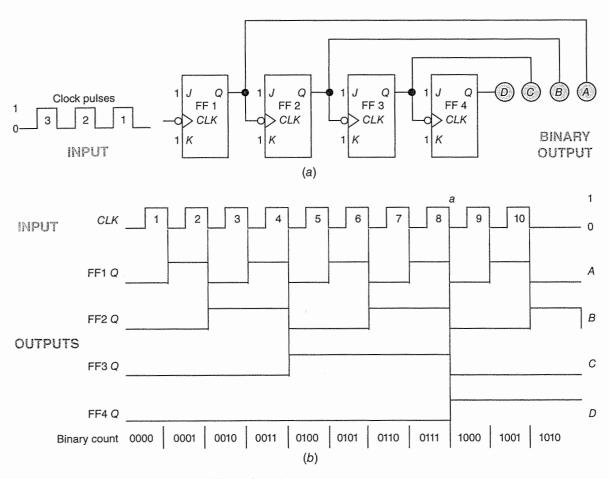


Fig. 8-2 Mod-16 counter. (a) Logic diagram. (b) Waveform diagram.

Asynchronous counter

4-bit counter

Ripple counter

Because one flip-flop affects the next one, it takes some time to toggle all the flip-flops. For instance, at point a on pulse 8, Fig. 8-2(b), notice that the clock triggers FF 1, causing it to go to 0. This in turn causes FF 2 to toggle from 1 to 0. This in turn causes FF 3 to toggle from 1 to 0. As output Q of FF 3 reaches 0, it triggers FF 4, which toggles from 0 to 1. We see that the changing of states is a chain reaction that rip-ples through the counter. For this reason this counter is called a ripple counter.

The counter we studied in Fig. 8-2 could be described as a ripple counter, a mod-16 counter, a 4-bit counter, or an asynchronous counter. All these names describe something about the counter. The ripple and asynchronous labels mean that all the flip-flops do not trigger at one time. The mod-16 description comes from the number of states the counter cycles through. The 4-bit label tells how many binary places there are at the output of the counter.

-{V- Self-Test

Answer the following questions.

- 1. The unit in Fig. 8-3 is a(n) _____-bit ripple counter.
- 2. The unit in Fig. 8-3 is a mod-_____counter.
- 3. Each J-K flip-flop in Fig. 8-3 is in the _____ (hold, reset, set, toggle) mode because inputs *J* and *K* are both HIGH.
- 4. List the binary output after each of the six input pulses shown in Fig. 8-3.

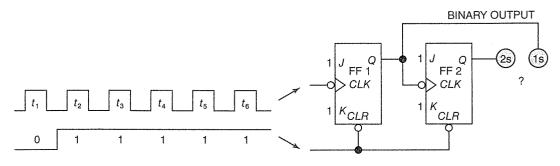


Fig. 8-3 Counter problem for test items 1 through 4.



Mod-10 ripple counter

Decade counter

8-2 Mod-10 Ripple Counters

The counting sequence for a mod-10 counter is from 0000 to 1001 (0 to 9 in decimal). This is down to the heavy line in Fig. 8-1. This mod-10 counter, then, has four place values: 8s, 4s, 2s, and 1s. This takes four flip-flops connected as a ripple counter in Fig. 8-4. We must add a NAND gate to the ripple counter to clear all the flip-flops back to zero immediately after the 1001 (9) count. The trick is to look at Fig. 8-1 and determine what the next count will be after 1001. You will find it is 1010 (decimal 10). You must feed the two 1s in the 1010 into a NAND gate as shown in Fig. 8-4. The

NAND gate then clears the flip-flop back to 0000. The counter then starts its count from 0000 up to 1001 again. We say we are using the NAND gate to reset the counter to 0000. By using a NAND gate in this manner, we can make several other modulous counters. Fig. 8-4 illustrates a mod-10 ripple counter. This type of counter might also be called a *decade* (meaning 10) *counter*.

Ripple counters can be constructed from individual flip-flops. Manufacturers also produce ICs with all four flip-flops inside a single package. Some IC counters even contain the reset NAND gate, such as the one used in Fig. 8-4.

264

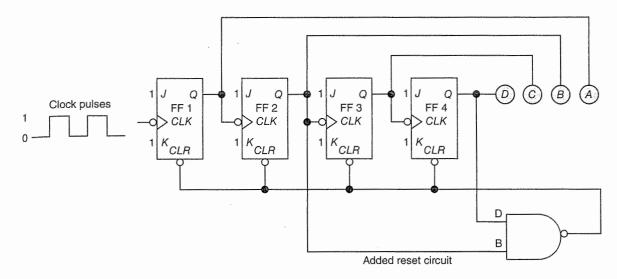


Fig. 8-4 Logic diagram for a mod-10 ripple counter.

-N- Self-Test

Answer the following questions.

- 5. Refer to Fig. 8-4. This is the logic diagram for a mod-10 _____ (ripple, synchronous) counter. Because it has 10 states (counts from 0 through 9), it is also called a(n) _____ counter.
- 6. List the binary output after each of the six input pulses shown in Fig. 8-5.
- 7. The circuit in Fig. 8-5 is a ______ (ripple, synchronous) mod-_____ counter.


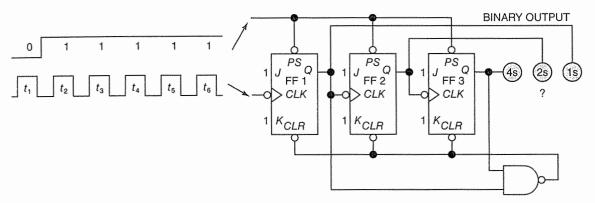


Fig. 8-5 Counter problem for test items 6 and 7.

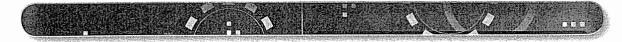


8-3 Synchronous Counters

The ripple counters we have studied are asynchronous counters. Each flip-flop does not trigger exactly in step with the clock pulse. For some high-frequency operations, it is necessary to have

all stages of the counter trigger together. There is such a counter: *a synchronous counter*.

A synchronous counter is shown in Fig. 8-6(a). This logic diagram is for a 3-bit (mod-8) counter. First notice the *CLK* connections. The clock is connected directly to the *CLK* input of each

Synchronous counter

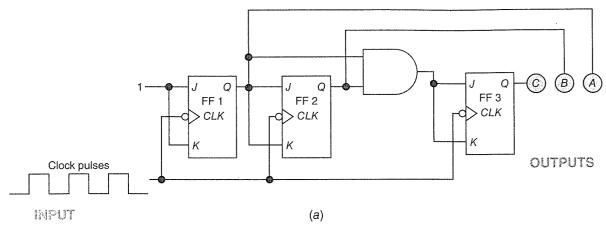

ROW	NUMBER OF		RY COU	DECIMAL COUNT		
	CLOCK PULSES	С	В	Α	000117	
1	0	0	0	0	0	
2	1	0	0	1	1	
3	2	0	1	0	2	
4	3	0	1	1	3	
5	4	1	0	0	4	
6	5	1	0	1	5	
7	6	1	1	0	6	
8	7	1	1	1	7	
9	8	0	0	0	0	
(b)						

Fig. 8-6 A 3-bit synchronous counter. (a) Logic diagram. (b) Counting sequence.

flip-flop. We say that the CLK inputs are connected in *parallel*. Figure 8-6(b) gives the counting sequence of this counter. Column A is the binary 1s column, and FF 1 does the counting for this column. Column B is the binary 2s column, and FF 2 counts this column. Column C is the binary 4s column, and FF 3 counts this column.

Let us study the counting sequence of this mod-8 counter by referring to Fig. 8-6(a) and (b):

Pulse 1-row 2

Circuit action: Each flip-flop is pulsed by the clock.

Only FF 1 can toggle because it is the only one with 1s applied to both J and K inputs.

FF 1 goes from 0 to 1.

Output result: 001 (decimal 1).

Pulse 2—row 3

Circuit action: Each flip-flop is pulsed.

Two flip-flops toggle because they have 1s applied to both J and K inputs.

FF 1 and FF 2 both toggle.

FF 1 goes from 1 to 0.

FF 2 goes from 0 to 1.

Output result: 010 (decimal 2).

Pulse 3—row 4

Circuit action: Each flip-flop is pulsed.

Only one flip-flop toggles.

FF 1 toggles from 0 to 1.

Output result: 011 (decimal 3).

Pulse 4—row 5

Circuit action: Each flip-flop is pulsed.

All flip-flops toggle to opposite state.

FF 1 goes from 1 to 0.

FF 2 goes from 1 to 0.

FF 3 goes from 0 to 1.

Output result: 100 (decimal 4).

Pulse 5—row 6

Circuit action: Each flip-flop is pulsed.

Only one flip-flop toggles.

FF 1 goes from 0 to 1.

Output result: 101 (decimal 5).

Pulse 6-row 7

Circuit action: Each flip-flop is pulsed.

Two flip-flops toggle.

FF 1 goes from 1 to 0.

FF 2 goes from 0 to 1.

Output result: 110 (decimal 6).

Pulse 7-row 8

Circuit action: Each flip-flop is pulsed.

Only one flip-flop toggles.

FF 1 goes from 0 to 1.

Output result: 111 (decimal 7).

Pulse 8-row 9

Circuit action: Each flip-flop is pulsed.

All three flip-flops toggle.

All flip-flops change from 1 to 0.

Output result: 000 (decimal 0).

We now have completed the explanation of how the 3-bit synchronous counter works. Notice that the J-K flip-flops are used in their toggle mode (J and K at 1) or hold mode (J and K at 0).

Synchronous counters are most often purchased in IC form. Synchronous counters are available in both TTL and CMOS.

3-bit synchronous counter

J-K flip-flops in either toggle or hold modes

-VV-

Self-Tes

Supply the missing word in each statement.

- 8. A counter that triggers all the flip-flops at the same instant is called a ______ (ripple, synchronous) counter.
- 10. Refer to Fig. 8-6(a). FF 1 is always in the _____ (hold, reset, set, toggle) mode in this circuit.
- 11. Refer to Fig. 8-6. On clock pulse 4,

 ————— (only FF 1 toggles; both FF 1 and FF 2 toggle; only FF 3 toggles; all the flip-flops toggle), producing a binary count of 100 at the outputs of the counter.
- 12. Refer to Fig. 8-6. The purpose of the AND gate is to place ______ (FF 1, FF 2, FF 3) in the toggle mode two times during the counting cycle [rows 4 and 8 from Fig. 8-6(b)] while this flip-flop stays in the hold mode during other times.




8-4 Down Counters

Up to now we have used counters that count upward $(0, 1, 2, 3, 4, \ldots)$. Sometimes, however, we must count downward $(9, 8, 7, 6, \ldots)$ in digital systems. A counter that counts from higher to lower numbers is called a *down counter*.

A logic diagram of a mod-8 asynchronous down counter is shown in Fig. 8-7(a); the counting sequence for this counter is listed in Fig. 8-7(b). Note how much the down counter in Fig. 8-7(a) looks like the up counter in Fig. 8-2(a). The only difference is in the "carry"

from FF 1 to FF 2 and the carry from FF 2 to FF 3. The up counter carries from Q to the CLK input of the next flip-flop. The down counter carries from \overline{Q} (not Q) to the CLK input of the next flip-flop. Notice that the down counter has a preset (PS) control to preset the counter to 111 (decimal 7) to start the downward count. FF 1 is the binary 1s place (column A) counter. FF 2 is the 2s place (column B) counter. FF 3 is the 4s place (column C) counter. Notice in Fig. 8-7(a) that all three J-K flip-flops are in the toggle mode.

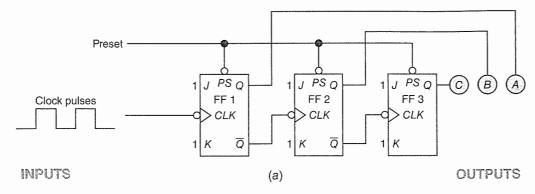Down counters Mod-B asynchronous down counter



NUMBER OF		RY COUI	DECIMAL COUNT			
CLOCK PULSES	С	В	А	000.11		
0	1	1	1	7		
1	1	1	0	6		
2	1	0	1	5		
3	1	0	0	4		
4	0	1	1	3		
5	0	1	0	2		
6	0	0	1	1		
7	0	0	0	0		
8	1	1	1	7		
9	1	0	0	6		
(b)						

Fig. 8-7 A 3-bit ripple down counter. (a) Logic diagram. (b) Counting sequence.

-W- Self-Test

Answer the following questions.

- 13. Refer to Fig. 8-7(*a*). All flip-flops are in the _____ (hold, reset, set, toggle) mode in this counter.
- 14. Refer to Fig. 8-7(*a*). It takes a (HIGH-to-LOW, LOW-to-HIGH) transition of the clock pulse to trigger these J-K flip-flops.
- 15. Refer to Fig. 8-7. On clock pulse 1,
 ______ (only FF 1 toggles; both FF 1
 and FF 2 toggle; only FF 3 toggles; all
 the flip-flops toggle) producing a binary
 count of 110 at the outputs of the counter.
- 16. List the counter's binary output for each of the six input pulses shown in Fig. 8-8.

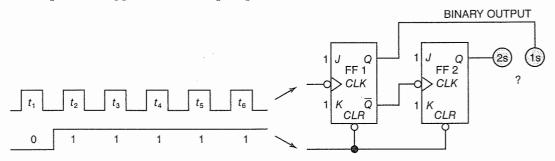


Fig. 8-8 Counter problem for test item 16.



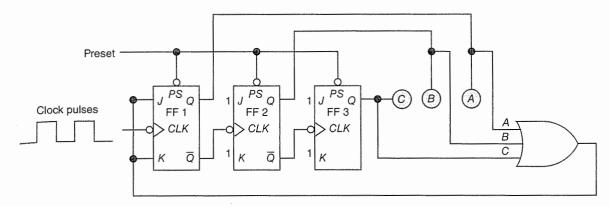


Fig. 8-9 A 3-bit down counter with self-stopping feature.

3-bit down counter with self-stopping feature

8-5 Self-Stopping Counters

The down counter shown in Fig. 8-7(a) recirculates. That is, when it gets to 000 it starts at 111, then 110, and so forth. However, sometimes you want a counter to stop when a sequence is finished. Figure 8-9 illustrates how you could stop the down counter in Fig. 8-7 at the 000 count. The counting sequence is shown in Fig. 8-7(b). In Fig. 8-9 we add an OR gate to place a logical 0 on the J and K inputs of FF 1 when the count at

outputs C, B, and A reaches 000. The preset must be enabled (PS to 0) again to start the sequence at 111 (decimal 7).

Up or down counters can be stopped after any sequence of counts by using a logic gate or combination of gates. The output of the gate is fed back to the J and K inputs of the first flip-flop in a ripple counter. The logical 0s fed back to the J and K inputs of FF 1 in Fig. 8-9 place it in the hold mode. This stops FF 1 from toggling, thereby stopping the count at 000.

Recirculating counter

_AM__

Self-Test

Supply the missing word or words in each statement.

- 17. Refer to Fig. 8-9. This is the logic diagram for a self-stopping 3-bit ______ (down, up) counter.
- 18. Refer to Fig. 8-9. With an output count of 000, the OR gate outputs a ______ (HIGH, LOW). This places FF 1 in the _____ (hold, toggle) mode.
- 19. Refer to Fig. 8-9. With an output count of 111, the OR gate outputs a _____ (HIGH, LOW). This places FF 1 in the _____ (hold, toggle) mode.
- 20. Refer to Fig. 8-10. This is a 3-bit ripple down counter that has a self-stopping feature. (T or F)
- 21. Refer to Fig. 8-10. List the 3-bit binary counts that appear on the output display after input pulses t_1 , t_2 , and t_3 .



Frequency division \mathfrak{a} O BINARY OUTPUT (૪) ધ SS(B)FF 3 CLK PS 10 FF 2 CLK PS × Divide-by-60 circuit G O CLK FF 1 × Clock Digital clock Frequency counter Oscilloscopes STOCK

8-6 Counters as Frequency Dividers

An interesting and common use of counters is for *frequency division*. An example of a simple system using a frequency divider is shown in Fig. 8-11. This system is the basis for a digital clock. The 60-Hz input frequency may be from the power line (formed into a square wave). The circuit must divide the frequency by 60, and the output will be one pulse per second (1 Hz). This is a seconds timer.

A block diagram of a decade counter is drawn in Fig. 8-12(a). In Fig. 8-12(b) the waveforms at the *CLK* input and the binary 8s place (output Q_D) are shown. Notice that it takes 30 input pulses to produce 3 output pulses. Using division, we find that $30 \div 3 = 10$. Output Q_D of the decade counter in Fig. 8-12(a) is a divideby-10 counter. In other words, the output frequency at Q_D is only one-tenth the frequency at the input of the counter.

If we use the decade counter (divide-by-10 counter) from Fig. 8-11 and a mod-6 counter (divide-by-6 counter) in series, we get the *divide-by-60* circuit we need in Fig. 8-11. A diagram of such a system is illustrated in Fig. 8-13. The 60-Hz square wave enters the divide-by-6 counter and comes out at 10 Hz. The 10 Hz then enters the divide-by-10 counter and exits at 1 Hz.

You are already aware that counters are used as frequency dividers in *digital* timepieces, such as electronic *digital clocks*, automobile digital clocks, and digital wristwatches. Frequency division is also used in *frequency counters*, oscilloscopes, and television receivers.


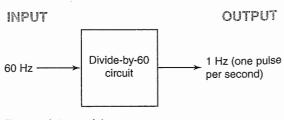


Fig. 8-11 A 1-second timer system.

8-10 Pulse-train problem

É

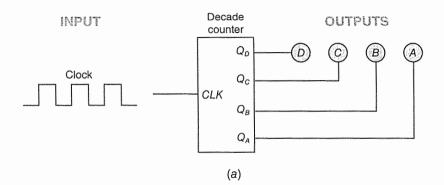




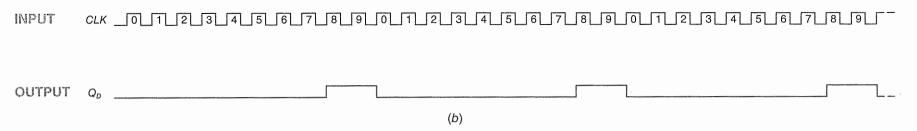


Fig. 8-12 Decade counter used as a divide-by-10 counter. (a) Logic diagram. (b) Waveform diagram.

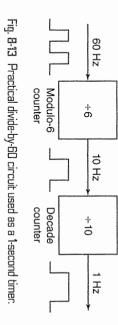

Supply the missing word in each statement.

- 22. Refer to Fig. 8-13. If the input frequency on the left is 60,000 Hz, the output
- frequency from the decade counter is _____ Hz.
- 23. Refer to Fig. 8-12(*a*). Output *A* divides the input clock frequency by ______(number).



8-7 TTL IC Counters

Manufacturers' IC data manuals contain lists of counters. This section covers only two representative types of TTL IC counters.

The 7493 4-Bit Counter

The 7493 TTL 4-bit binary counter is detailed in Fig. 8-14. The block diagram in Fig. 8-14(a) shows that the 7493 IC houses four J-K flip-flops wired as a ripple counter. If you look carefully at Fig. 8-14(a), you will notice that the bottom three J-K flip-flops are prewired internally as a 3-bit ripple counter with output Q_R connected to the clock input of the next lower J-K flip-flop and output Q_c connected internally to the clock input of the bottom J-K flip-flop. Importantly, the top J-K flip-flop does not have its Q_{A} output internally connected to the next lower flipflop. To use the 7493 IC as a 4-bit ripple counter (mod-16), you have to externally connect output Q_A to input B, which is the CLK input of the second flip-flop. A counting sequence for the 7493 IC wired as a 4-bit ripple counter is reproduced in Fig. 8-14(c). Consider the J and K inputs to each flip-flop in Fig. 8-14(a): It is understood that these inputs are permanently held HIGH so the flip-flops are in the toggle mode. Notice that the clock inputs suggest that the 7493 uses negative-edge triggering.

Recall the use of a two-input NAND gate to change the mod-16 ripple counter to a decade counter in Fig. 8-4. Figure 8-14(a) shows that such a two-input NAND gate is built into the 7493 counter IC. Inputs $R_{0(1)}$ and $R_{0(2)}$ are the inputs to the internal NAND gate. The reset/count function table in Fig. 8-14(d) shows that the 7493 counter will be reset (0000) when both $R_{0(1)}$ and $R_{0(2)}$ are HIGH. When either or both reset inputs are LOW, the 7493 IC will count. *Caution:* If

the reset inputs $(R_{0(1)}$ and $R_{0(2)}$) are left disconnected, they will float HIGH and the 7493 IC will be in the reset mode and will not count.

Note B in Fig. 8-14(d) suggests that you can use the 7493 IC as a *biquinary counter* by connecting output Q_D to Q_A with output Q_A becoming the most significant bit. The biquinary number system is used in the hand-manipulated abacus and soroban.

The 7493 4-bit ripple counter is packaged in a 14-pin DIP as shown in Fig. 8-14(b). Note especially the unusual location of the GND (pin 10) and V_{CC} (pin 5) connections to the 7493 counter, which are commonly on the corners of the many ICs.

The 74192 Up/Down Decade Counter

A second TTL IC counter is detailed in Fig. 8-15. It is the 74192 up/down decade counter IC. Read the manufacturer's description of the IC counter in Fig. 8-15(a). Because the 74192 counter is a synchronous counter and has many features, it is quite complex, as shown in the logic diagram reproduced in Fig. 8-15(b). The 74192 IC is packaged in either a 16-pin dual in-line package or a 20-pin surface mount package. The pin configurations of both the DIP and surface mount packages are drawn in Fig. 8-15(c). Both IC packages shown in Fig. 8-15(c) are viewed from the top. Note especially the unusual location of pin 1 on the surface mount package.

The waveform diagram in Fig. 8-15(*d*) details several sequences used on the 74192 counter IC. Useful sequences detailed in the waveform diagram are clear, preset (load), count up, and count down. The clear (*CLR*) input to the 74192 is an active HIGH input while the load is an active LOW input. Counterparts to the 74192 synchronous up/down counter are the 74LS192 and 74HC192.


7493 TTL 4-bit

binary counter

Biquinary counter


74192 up/down decade counter IC

(a) BLOCK DIAGRAM

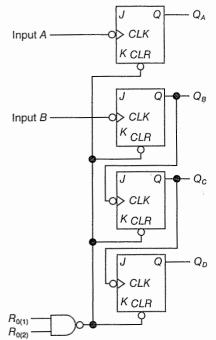

The J and K inputs shown without connection for reference only and are functionally at a high level.

(b) PIN CONFIGURATION

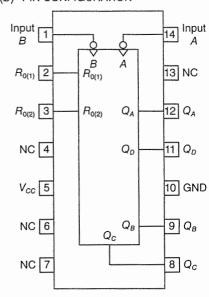

(c) COUNT SEQUENCE: Wired as 4-Bit Counter*

COUNT		OUT	PUT	
COUNT	Q_D	Qc	Q _B	Q_A
0	L	L	L	L
1	L	L	L	Н
2	L	L	Н	L
3	L	L	Н	Н
4	L	Н	L	L
5	L	Н	L	Н
6	L	Н	Н	L
7	L	Н	Н	Н
8	Н	L	L	L
9	Н	L	L	Н
10	Н	L	Н	L
11	Н	L	Н	Н
12	Н	Н	L	L
13	Н	Н	L	Н
14	Н	Н	Н	L
15	Н	Н	Н	Н

Output Q_A is connected to input B.

(d) RESET/COUNT FUNCTION TABLE

RESET	INPUTS		OUTPUT					
$R_{0}(1)$	R ₀ (2)	Q_D	Qc	Q_{B}	Q_A			
Н	Н	L	L	L	L			
L	X	Count						
X	L	Count						

NOTES:

- A. Output Q_A is connected to input B for BCD count (or binary count).
- B. Output Q_D is connected to input A for biguinary count.
- C. H = high level, L = low level, X = irrelevant.

Fig. B-14 A 4-bit binary counter IC (7493). (a) Block diagram. (b) Pin configuration. (c) Count sequence. (d) Reset/count function table.

4-bit binary counter IC (7493)

Applications

You probably have already figured out that some of the features are not used on these IC counters for some applications. Figure 8-16(a) (p. 275) shows the 7493 IC counter being used as a mod-8 counter. Look back at Fig. 8-14, and notice that

several inputs and an output are not being used. Figure 8-16(*b*) shows the 74192 counter being used as a decade down counter. Six inputs and two outputs are not being used in this circuit. Simplified logic diagrams similar to those in Fig. 8-16 are more common than the complicated diagrams in Figs. 8-14(*a*) and 8-15(*b*).

(a) DESCRIPTION

This monolithic circuit is a synchronous reversible (up/down) counter having a complexity of 55 equivalent gates. Synchronous operation is provided by having all flip-flops clocked simultaneously so that the outputs change coincidentally with each other when so instructed by the steering logic. This mode of operation eliminates the output counting spikes which are normally associated with asynchronous (ripple-clock) counters.


The outputs of the four master-slave flip-flops are triggered by a low-to-high-level transition of either count (clock) input. The direction of counting is determined by which count input is pulsed while the other count input is high.

All four counters are fully programmable; that is, each output may be preset to either level by entering the desired data at the data inputs while the load input is low. The output will change to agree with the data inputs independently of the count pulses. This feature allows the counters to be used as modulo-N dividers by simply modifying the count length with the preset inputs.

A clear input has been provided which forces all outputs to the low level when a high level is applied. The clear function is independent of the count and load inputs. The clear, count, and load inputs are buffered to lower the drive requirements. This reduces the number of clock drivers, etc., required for long words.

These counters were designed to be cascaded without the need for external circuitry. Both borrow and carry outputs are available to cascade both the up- and down-counting functions. The borrow output produces a pulse equal to the count-down input when the counter underflows. Similarly, the carry output produces a pulse equal in width to the count-up input when an overflow condition exists. The counters can then be easily cascaded by feeding the borrow and carry outputs to the count-down and count-up inputs respectively of the succeeding counter.

(b) LOGIC DIAGRAM

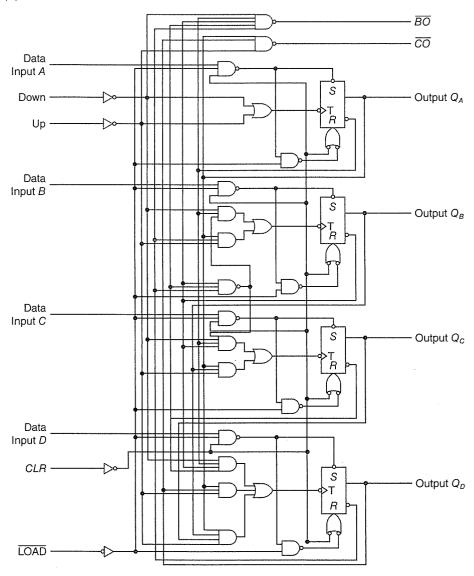

Synchronous decade up/down

counter IC (74192) Fig. 8-15 Synchronous decade up/down counter IC (74192). (a) Description. (b) Logic diagram.

(c) PIN CONFIGURATIONS

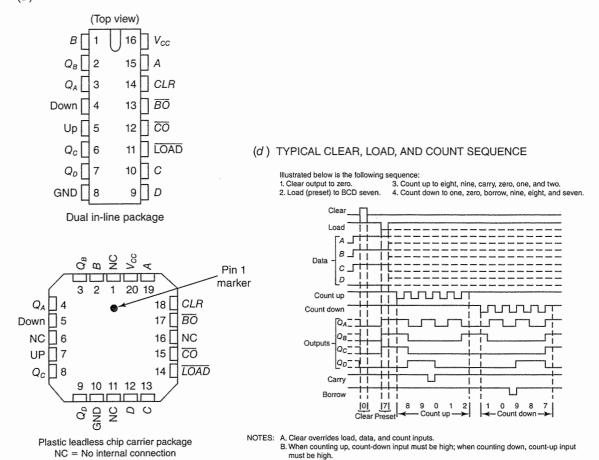


Fig. 8-15 (cont.) (c) Pin configurations. (d) Waveforms.

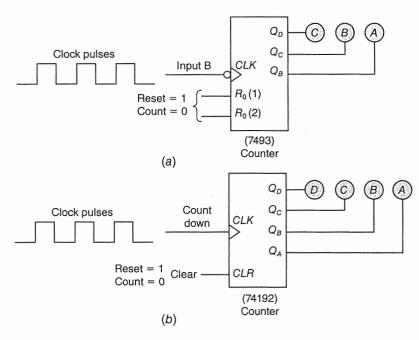


Fig. 8-16 Two applications. (a) 7493 IC wired as a mod-8 up counter. (b) 74192 IC wired as a decade down counter.

Mod-8 counter Decade down counter Answer the following questions.

- 24. Refer to Fig. 8-14. If both inputs to the NAND gate (pins 2 and 3 on the 7493 IC) are HIGH, the output from the 7493 counter will be _____ [4 bits].
- 25. Refer to Fig. 8-14. The 7493 IC is a(n)
 ________-bit _______ (down, up)
 counter.
- 26. Refer to Fig. 8-15. The 74192 IC is a _____(decade, mod-16) up/down _____ (ripple, synchronous) counter.
- 27. Refer to Fig. 8-15. The clock input to the 74192 for counting upward is pin _____ [number] on the DIP IC.
- 28. Refer to Fig. 8-15. The 74192 IC has an active _____ (HIGH, LOW) clear input.

- 29. Refer to Fig. 8-15. The data inputs (D, C, B, and A) of the 74192 IC are used to preset the four outputs $(Q_D, Q_C, Q_B, \text{ and } Q_A)$ along with an ______ (active HIGH carry, active LOW $\overline{\text{LOAD}}$) input.
- 30. Refer to Fig. 8-15. List the *two* clock inputs to the 74192 counter IC.
- 31. Refer to Fig. 8-15. The *borrow* and *carry outputs* from the 74192 IC are used when several counter ICs are cascaded. (T or F)
- 32. List the output frequency at points *B*, *C*, and *D* in Fig. 8-17.
- 33. The 7493 IC is a ripple divide-by-2, divide-by-4, and divide-by- _____ unit in Fig. 8-17.

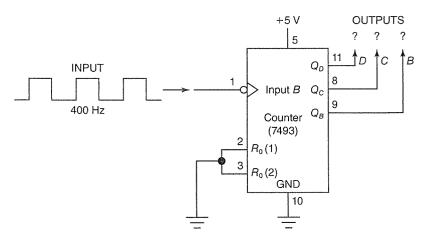


Fig. 8-17 Counter problem for test items 32 and 33.



8-8 CMOS IC Counters

Manufacturers of CMOS chips offer a variety of counters in IC form. This section covers only two types of CMOS counters.


The 74HC393 4-Bit Binary Counter

The diagrams in Fig. 8-18 detail a 74HC393 dual 4-bit binary ripple counter. A function diagram (something like a logic diagram) of the 74HC393 counter IC is shown in Fig. 8-18(a). Note that the IC contains two 4-bit binary

ripple counters. The table in Fig. 8-18(b) gives the names and functions of each input and output pin on the 74HC393 IC. Note that the clock inputs are labeled with the letters \overline{CP} instead of CLK, as used earlier. Pin labels vary from manufacturer to manufacturer. For this reason, you must learn to use manufacturers' data sheets for exact information.


Each 4-bit counter in the 74HC393 IC package consists of four T flip-flops. A *T flip-flop* is any flip-flop that is in the toggle mode. This is shown in the detailed logic diagram drawn in

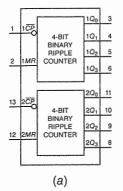74HC393 dual 4-bit binary ripple counter T flip-flop



PIN DESCRIPTION

PIN NO.	SYMBOL	NAME AND FUNCTION
1, 13 2, 12	1 CP , 2 CP 1 <i>MR</i> , 2 <i>MR</i>	clock inputs (HIGH-to-LOW, edge-triggered) asynchronous master reset inputs (active HIGH)
3, 4, 5, 6, 11, 10, 9, 8	$1Q_0$ to $1Q_3$, $2Q_0$ to $2Q_3$	flip-flop outputs
7	GND	ground (0 V)
14	V _{CC}	positive supply voltage
		(b)
		(D)

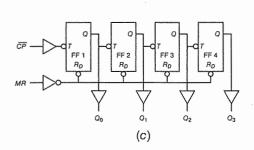

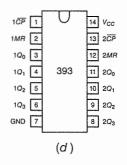


Fig. 8-18 CMOS dual 4-bit binary counter IC (74HC393). (a) Function diagram. (b) Pin descriptions. (c) Detailed logic diagram. (d) Pin diagram.

74HC393 4bit-counter

Fig. 8-18(c). Note that the MR input is an asynchronous master reset pin. The MR pins are active HIGH inputs. In other words, a HIGH at the MR input will override the clock and reset the individual counter to 0000.

A pin diagram for the 74HC393 IC is reproduced in Fig. 8-18(d). This dual in-line package IC is being viewed from the top. The counting sequence for the 74HC393 counter is binary 0000 through 1111 (0 to 15 in decimal).

The functional diagram in Fig. 8-18(a) and logic diagram in Fig. 8-18(c) both suggest that the counters are triggered on the HIGH-to-LOW transition of the clock pulse. The outputs (Q_0, Q_1, Q_2, Q_3) of the ripple counter are asynchronous (not exactly in step with the clock). As with all ripple counters, there is a slight delay in outputs because the first flip-flop triggers the second, the second the third, and so forth. Note that the > symbol at the clock (\overline{CP}) inputs) has been omitted by this manufacturer. Again, many variations occur in both labels and logic diagrams from manufacturer to manufacturer.

The 74HC193 4-Bit Binary Up/Down Counter

The second CMOS IC counter we shall discuss is the 74HC193 presettable synchronous 4-bit binary up/down counter IC. The 74HC193

counter has more features than the 74HC393 IC. Manufacturer's information on the 74HC193 counter IC is detailed in Fig. 8-19.

A function diagram of the 74HC193 IC is drawn in Fig. 8-19(a) with pin descriptions following in Fig. 8-19(b). The 74HC193 has two clock inputs (CP_U and CP_D). One clock input is used for counting up (CP_D) and the other when counting down (CP_D). Figure 8-19(b) notes that the clock inputs are edge-triggered on the LOW-to-HIGH transition of the clock pulse.

A truth table for the 74HC193 counter is drawn in Fig. 8-19(d). The operating modes


74HC193 presettable synchronous 4-bit binary up/down counter IC

ABOUT ELECTRONICS



Devices in the Medical Field

- In the past, blood tests required several vials of blood because testing machines couldn't handle small quantities.
 A new method encapsulates blood within a dime-sized "vial" and moves blood electrically within a computer chip with channels that carry liquid instead of wires. For this procedure, less than a billionth of a liter needs to be sampled.
- Deeply embedded bodily aliments, such as kidney disorders, that cause scar tissue can be located when medical personnel use ultrasound together with touch. When organs do not move freely, the area is scarred.

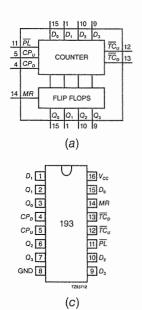

PIN DESCRIPTION

PIN NO.	SYMBOL	NAME AND FUNCTION
3, 2, 6, 7 4 5 8 11 12 13	Q _o to Q _s CP _o CP _u GND PL TC _u TC _p	flip-flop outputs count down clock input* count up clock input* ground (0 V) asynchronous parallel load input (active LOW) terminal count up (carry) output (active LOW) terminal count down (borrow) output (active LOW)
14 15, 1,10, 9 16	MR Do to D3 Vcc	asynchronous master reset input (active HIGH) data inputs positive supply voltage

* LOW-to-HIGH, edge triggered

(b)

OPERATING MODE		INPUTS						OUTPUTS						
	MR	PL	CPu	CP _o	D ₀	D ₁	D ₂	D_3	Q _o	Q,	Q ₂	Q_3	ΤCυ	TCD
reset (clear)	Н	X	X	L	X	Х	Χ	X	L	L	L	L	Н	L
	Н	X	Х	Н	X	Х	Χ	Х	L	L	L	L	Н	Н
	L	L	Х	L	L	L	L	L	L	L	L	L	Н	L
parallel load	L	L	Х	Н	L	L	L	L	L	L	L	L	Н	Н
parallel load	L	L	L	X	Н	Н	Н	Н	н	Н	Н	Н	L	Н
	L	L	Н	X	Н	Н	Н	Н	Н	Н	Н	Н	Н	Н
count up	L	Н	t	н	Х	х	Х	Х		cour	nt up		H⁺	Н
count down	L	Н	Н	1	Х	Х	Х	х		count	down		Н	H [†]

H = HIGH voltage level


* \overline{TC}_U = CP_U at terminal count up (HHHH) † \overline{TC}_D = CP_D at terminal count down (LLLL)

L = LOW voltage level

X = don't care

t = LOW-to-HIGH clock transition

(d)

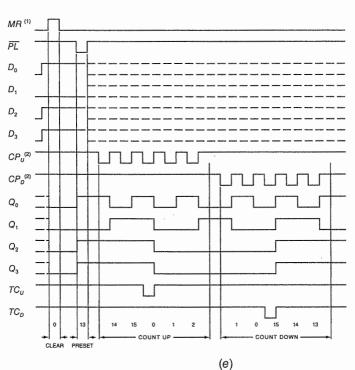

- (1) Clear overrides load, data and count inputs.
- (2) When counting up the count down clock input (CP_D) must be HIGH, when counting down the count up clock input (CP_U) must be HIGH.

Sequence

Clear (reset outputs to zero); load (preset) to binary thirteen; count up to fourteen, fifteen, terminal count up, zero, one

count down to one, zero, terminal count down, fifteen, fourteen and thirteen.

CMOS presettable 4-bit synchronous up/down counter IC (74HC193)

Fig. 8-19 CMOS presettable 4-bit synchronous up/down counter IC (74HC193). (a) Function diagram. (b) Pin descriptions. (c) Pin diagram. (d) Truth table. (e) Typical clear, preset, and count sequence.

for the counter on the left give an overview of the many functions of the 74HC193 counter. Its modes of operation are *reset*, *parallel load*, *count up*, and *count down*. The truth table in Fig. 8-19(d) also makes it clear which pins are inputs and which are outputs.

Typical clear (reset), preset (parallel load), count up, and count down sequences are shown in Fig. 8-19(e). Waveforms are useful when investigating an IC's typical operations or timing.

Applications

Figures 8-20 and 8-21 show two possible applications for the CMOS counter ICs studied in this section. Figure 8-20 shows a logic diagram for a 74HC393 IC wired as a simple 4-bit

binary counter. The MR (master reset) pin must be tied to either 0 or 1. The MR input is an active HIGH input so a 1 clears the binary outputs to 0000. With a logical 0 at the reset pin (MR), the IC is allowed to count upward from binary 0000 to 1111.

The 74HC193 CMOS IC is a more sophisticated counter. Figure 8-21 diagrams a mod-6 counter, which starts at binary 001 and counts up to 110 (1 to 6 in decimal). This might be useful in a game circuit where the rolling of dice is simulated. The NAND gate in the mod-6 counter activates the asynchronous parallel load (\overline{PL}) input with a LOW just after the highest required count of binary 0110. The counter is then loaded with 0001, which is permanently

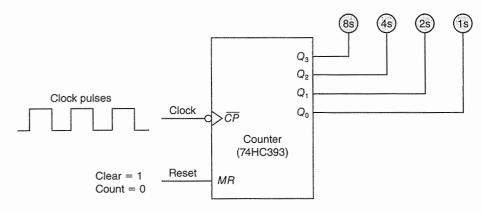


Fig. 8-20 A 74HC393 IC wired as a 4-bit binary counter.

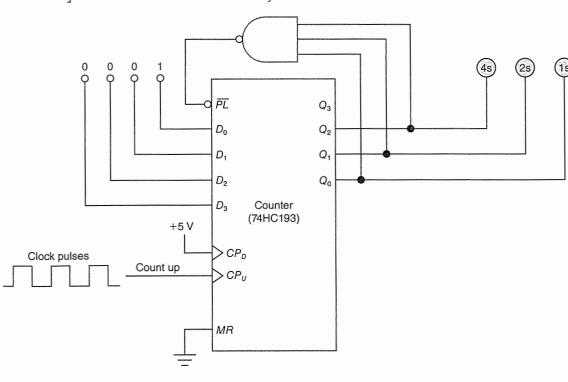


Fig. B-21 A 74HC193 IC wired as a mod-6 counter.

4-bit binary counter

Mod-6 counter

connected to the data inputs $(D_0 \text{ to } D_3)$. Clock pulses enter the count-up clock input (CP_U) . The count-down clock input (CP_D) must be tied to +5 V, and the master reset (MR) pin must be


grounded to disable these inputs and allow the counter to operate. The mod-6 counter circuit in Fig. 8-21 shows the flexibility of the CMOS 74HC193 presettable 4-bit up/down counter IC.

-/№ Self-Test

Answer the following questions.

- 34. Refer to Fig. 8-18. The 74HC393 IC contains two _____ (4-bit binary, decade) counters.
- 35. Refer to Fig. 8-18. The reset pin (*MR*) on the 74HC393 counter is an active _____ (HIGH, LOW) input.
- 36. Refer to Fig. 8-18. The 74HC393 counter's clock inputs are triggered by the _____ (H-to-L, L-to-H) transition of the clock pulse.
- 37. The circuit drawn in Fig. 8-20 is a mod———— [number] ————— (ripple, synchronous) counter.
- 38. Refer to Fig. 8-19. The 74HC193 is a presettable ______ (ripple, synchronous) 4-bit up/down counter IC.

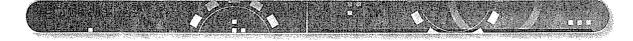- 39. Refer to Fig. 8-19. The reset pin (*MR*) is ______ (asynchronous, synchronous) and overrides all other inputs on the 74HC193 IC.
- 40. Refer to Fig. 8-19. The outputs of the 74HC193 are labeled _____ (D_0 – D_3 , Q_0 – Q_3).
- 41. Refer to Fig. 8-21. List the binary counting sequence for this counter circuit.
- 42. Refer to Fig. 8-21. What is the purpose of the three-input NAND gate in this counter circuit?
- 43. Refer to Fig. 8-18(a). How do you explain the lack of the > symbol near the clock inputs since the 74HC393 counters are edge-triggered?



Internet Connection

Relevant data sheets can be found at www.onsemi.com.

Display multiplexing

8-9 A Three-Digit BCD Counter


Historically more and more electronic functions are being embedded in a single IC. The three-digit BCD counter IC will demonstrate this trend and also feature some devices that you have studied.

The 4553 (MC14553) CMOS three-digit BCD counter will be featured in this section. A simplified functional block diagram of the 4553 IC is sketched in Fig. 8-22(a). You will notice that the 4553 IC contains three cascaded decade counters. Cascading counters means that the 1s BCD counter triggers the 10s counter as it recirculates from 1001_{BCD} to 0000_{BCD}. In like manner, the 10s counter triggers the 100s counter as it recirculates from 1001_{BCD} to 0000_{BCD}. The BCD output from the three counters are fed through the three 4-bit transparent latches. The BCD data are then transferred to a display multiplexer circuit. The display multiplexing circuit will drive three 7-segment displays.

The 4553 BCD counter IC detailed in Fig. 8-22(a) also features a pulse-shaper circuit to square up the incoming clock pulses. The CLK (clock) input to the 4553 is negative-edge-triggered. The display multiplexer circuitry turns on just one of the three decimal displays at a time, feeding the correct BCD output to the display. The multiplexing should occur at a rate of about 40- to 80-Hz. An external capacitor (C_1) can be attached between the C_{1A} and C_{1B} pins of the IC to set the scan oscillator frequency. Capacitor C_1 would typically have a value of about 0.001 μ F.

The disable clock, master reset, and latch enable inputs to the 4553 counter IC are all active HIGH inputs, and the 4-bit BCD outputs (Q_0-Q_3) are active HIGH. The digit select (DS_1,DS_2,DS_3) pins are active LOW outputs.

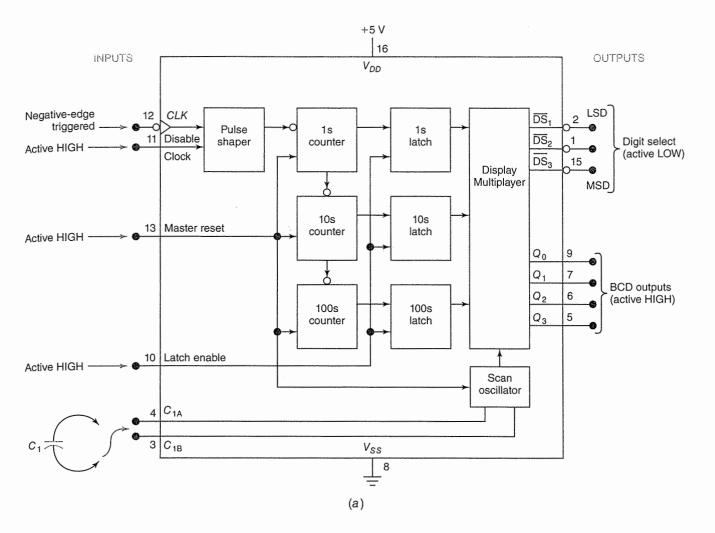A truth table drawn in Fig. 8-22(b) for the 4553 three-digit BCD counter IC shows a few of the modes of operation. These modes of



Partial Truth Table: 4553 3-Digit BCD Counter IC

Mode of		INP			
operation	MR CLK DIS I				OUTPUTS
Master reset	1	Х	Х	0	0000 0000 0000 _{BCD}
Count up	0	\	0	0	Advance count by 1
Disable clock	0	Х	1	0	No change
Latch outputs	0	Х	Х	1	Latches BCD data
	Master reset	Clock	Disable the clock	Latch enable	

0 = LOW

1 = HIGH

¥ = HIGH-to-LOW transition of clock pulse

X = Irrelevant

(b)

Fig. 8-22 4553 three-digit BCD counter IC. (a) Functional block diagram. (b) Partial truth table.

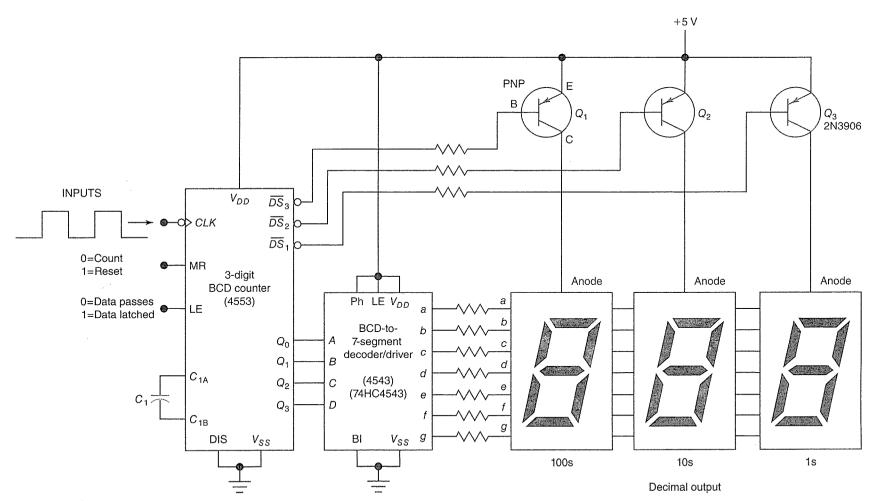


Fig. 8-23 A 3-digit up counter circuit.

operation are the most useful, but several other combinations of inputs are possible. When the MR input pin goes HIGH, the outputs are reset to $0000\ 0000\ 0000_{BCD}$. The master reset mode of operation is shown in line 1 of the truth table in Fig. 8-22(b). The count up mode of operation is detailed in line 2 of the truth table. On the HIGH-to-LOW transition of the clock pulse, the BCD count will advance by 1. Notice from Fig. 8-22(a) that only the 1s counter is triggered by the input clock pulses. The 10s counter is triggered by an output from the 1s counter, while the 100s counter is triggered by the output from the 10s counter (called cascading). The disable clock mode of operation happens when the disable input pin goes HIGH. The input clock pulses are not permitted to reach the 1s counter, and the BCD output remains the same.

The three BCD counters are constructed of 12 T flip-flops that have a memory characteristic. A second layer of memory is provided in the 4553 IC in the form of three 4-bit transparent latches. When the LE (latch enable) input to the 4553 IC is LOW, the three latches pass data directly through to the multiplexer as suggested in the functional block diagram in Fig. 8-22(a). When the latches pass data through, they are said to be transparent. When the LE (latch enable) input to the 4553 IC is activated by HIGH, the last count from the three BCD counters is latched at the inputs to the display multiplexer. It is important to understand that

the BCD counters can continue to count upward even when the LE (latch enable) input is active. However, the BCD output will display the former count frozen in the latches.

Application

One simple application of the 4553 three-digit BCD counter IC is sketched in Fig. 8-23. After activating the MR (master reset) input, the 4553 IC counts the number of input pulses and accumulates the count. The display multiplexer activates one 7-segment LED display at a time in rapid succession. First, as the 1s LED display is turned on by a LOW output from the $\overline{DS1}$ output from the 4553 IC, the correct BCD data from the 1s counter are sent to the 4543 decoder and are translated into seven-segment code, lighting the appropriate segments. Second, as the 10s LED display is turned on by a LOW output from the $\overline{\rm DS2}$ output from the 4553 IC. the new BCD data from the 10s counter are decoded by the 4543 IC and the 10s LED display lights. Third, as the 100s LED display is turned on by a LOW output from the $\overline{DS3}$ output of the 4553 IC, the new BCD data from the 100s counter are decoded by the 4543 IC and the 100s LED display lights. The multiplexer section inside the 4553 IC turns only a single display on at a time in rapid succession. To the human eye, the multiplexed seven-segment displays will appear as being lit continuously even if they are being turned on and off many times per second.

Cascading counter

Self-Test


Answer the following questions.

- 44. The 4553 IC contains a pulse shaper, three BCD ______ (adders, counters), three 4-bit latches, a scan oscillator, and a display _____ (multiplexer, shifter).
- 45. The MR (master reset) pin on the 4553 IC is a(n) ______ (active HIGH, active LOW) input that _____ (resets all counter outputs to 0, sets all counter outputs to 1) when activated.
- 46. The CLK input to the 1s counter on the 4553 IC is triggered on the _____ (H-to-L, L-to-H) transition of the clock pulse.

- 47. All three BCD counters in the 4553 IC use ______ (negative-edge, positive-edge) triggering to increment the count on that counter.
- 48. The LE (latch enable) pin on the 4553 IC is an _____ (active HIGH, active LOW) input.
- 49. Data from the three counters pass through the latches as if they were transparent when the LE input is _____ (HIGH, LOW).
- 50. The DIS (disable clock) pin on the 4553 IC is the same thing as the LE (latch enable) input. (T or F)

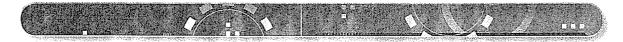- 51. When the LE input is activated with a HIGH, the latest data on the BCD counters are frozen at the output of the latches, but the BCD counters can still count upward with more input pulses. (T or F)
- 52. Refer to Fig. 8-23. The purpose of capacitor C_1 is to _____ (decouple the input from the output, set the scan frequency of the multiplexer).
- 53. Refer to Fig. 8-23. The ______ (4000, 4543) IC serves to translate the BCD

- input to the seven-segment code aiding in turning on the proper segments of the LED displays.
- 54. Refer to Fig. 8-23. The ______ (4543, 4553) IC contains an embedded display multiplexer, which turns on the proper display while routing the correct BCD data to the decoder.
- 55. What is the range (lowest to highest in decimal) for the 4553 counter that could be shown in the seven-segment displays in Fig. 8-23?



8-10 Counting Real-World Events

As we have mentioned before, the processing power of digital circuits is not very useful if we cannot input data and output results. The block diagram in Fig. 8-24(a) is a summary of the systems that we have studied to this point. In the digital processing area, we have studied some combinational and some sequential logic. We have studied several encoders and decoders that

handle interfacing. We have studied many output devices such as LEDs, seven-segment LED, LCD, and VF displays, incandescent bulbs, buzzers, relays, dc motors, and stepper and servo motors. We have worked with a few input devices such as clocks (both astable and monostable), switches, Hall-effect sensors, and pulse-width modulators. In this section we will add a new input device.

A block diagram for the system we are studying in this section is drawn in Fig. 8-24(b). We

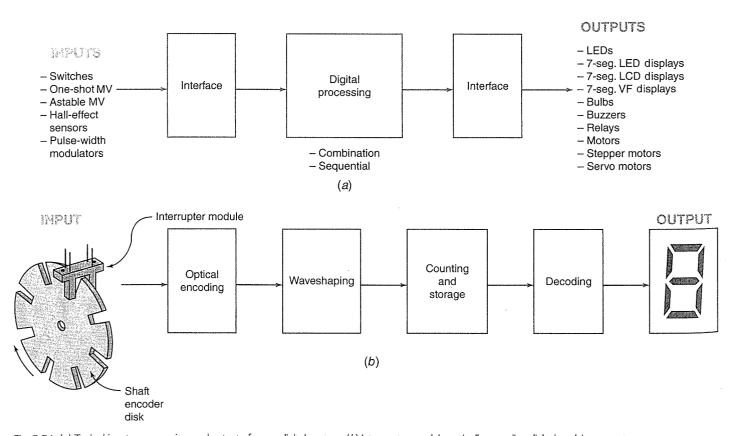


Fig. 8-24 (a) Typical inputs, processing, and outputs from a digital system. (b) Interrupter module optically encoding disk that drives counter.

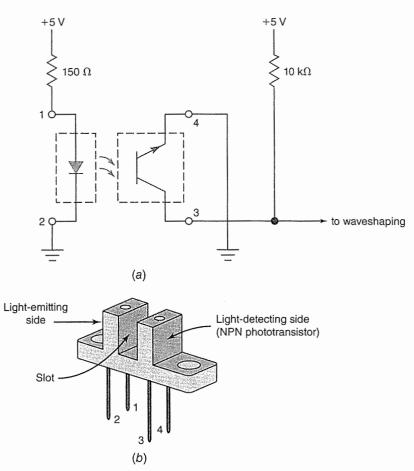


Fig. 8-25 (a) Schematic diagram of optocoupled interrupter module's emitter and light-detecting sides wired.
(b) Drawing of H21A1 optocoupled interrupter module (slot type).

Optocoupled interrupter module

will use optical encoding for input, the counter will accumulate the count, and the seven-segment display will form the output. The optocoupled interrupter module will sense each time the infrared light beam is interrupted and send this as a signal to the waveshaper and then to the decade counter/accumulator. Finally, the BCD count will be decoded, and the number of slots in the shaft encoder disk that have moved by the stationary optocoupled interrupter module will be displayed.

The optocoupled interrupter module or optical sensor is constructed with an infrared light-emitting diode aimed at a phototransistor across the slot. A schematic symbol for the optocoupled interrupter module is reproduced in Fig. 8-25(a). If current flows through the infrared diode on the emitter (E) side, the NPN phototransistor is activated on the detector (D) side of the module. If the light from the LED is blocked, the phototransistor on the detector side of the module is deactivated (turned off).

The H21A1 (ECG3100) optocoupled interrupter module is shown in Fig. 8-25(b). Notice that pins 1 and 2 of the H21A1 interrupter module are for the emitter side or infrared light-emitting diode. Typical wiring of the emitter side of the interrupter module is also detailed in Fig. 8-25(a). Pins 3 and 4 of the H21A1 interrupter module are for the detector side or NPN phototransistor. Typical wiring of the detector side of the interrupter module using an external 10-k Ω pull-up resistor is also shown in Fig. 8-25(a). The signal from the detector side of the interrupter module is then sent on to the waveshaping circuit.

A wiring diagram for a simple system that counts the number of pulses coming from the optocoupled interrupter module is detailed in Fig. 8-26. When an opaque object interrupts the light beam in the module, the phototransistor is deactivated (turned off) and the input to the 7414 Schmitt-trigger inverter is pulled HIGH by the 10-k Ω pull-up resistor. The output of the

Optical sensor

Fig. 8-26 Counter system using optical encoding.

Optical encoding

inverter goes from HIGH to LOW. When the opaque object is removed from the slot of the optocoupled interrupter module, the infrared light crosses the slot, striking the base of the phototransistor. The phototransistor is activated (turned on), and the voltage at pin 3 of the inverter goes from HIGH to LOW. Then the output of the waveshaper goes from LOW to HIGH, which will trigger the 74192 to count upward by 1. The 7447 IC decodes the BCD input to a seven-segment code and lights the appropriate segments on the LED display.

In summary, the optical encoder/counter system in Fig. 8-24(b) increments (one count upward) the count each time an opening in the encoder disk passes through the slot in the interrupter module. The optocoupled interrupted module uses infrared light so the ambient light does not cause false triggering. Remember that the infrared diode emits the correct wavelength of light for the phototransistor to detect.

Two common types of optical sensors are the slot-type module used in the last optical encoder/counter system and the *reflective-type sensor*. A sketch of a common reflective-type optical sensor is shown in Fig. 8-27(a). Notice that it has two holes in the front. One is an infrared-emitting diode, while the other is the receiver part of the optical sensor, which is

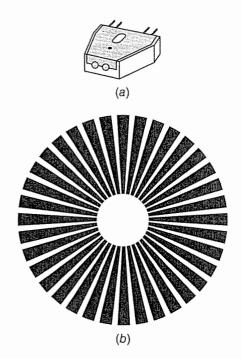


Fig. 8-27 (a) Reflective-type optical encoder. (b) Shaft encoder disk used with reflective-type optical encoder.

Types of optical sensors

a phototransistor. This reflective-type optical sensor is carefully aimed at a target such as the disk shown in Fig. 8-27(b). The white areas reflect light and turn on the output phototransistor, while the dark stripes absorb light and turn off the phototransistor.

-M- Self-Test

Supply the missing word or words in each statement.

- 56. Refer to Fig. 8-24(*b*). The _____ (decoder, interrupter module) is the device that does the job of optical encoding in this circuit.
- 57. Refer to Fig. 8-25(*a*). The diode on the emitter side of the interrupter module gives off _____ (infrared, ultraviolet) light.
- 58. Refer to Fig. 8-25(a). The _____ (phototransistor, germanium transistor) on the detector side of the interrupter module is sensitive to infrared light and does not trigger because of white room light.
- 59. Refer to Fig. 8-24(b). The optical sensor being used in this system is classified as

- a _____ (reflective-type, slot-type) module.
- 60. Refer to Fig. 8-26. The count on the display increments when the output of the Schmitt-trigger inverter goes from _____ (H to L, L to H).
- 61. Refer to Fig. 8-24(*b*). The count on the display increments when the encoder disk opening just ______ (enters, leaves) the interrupter module.
- 62. Refer to Fig. 8-26. The 74192 operates as a ______ (decade, mod-16) counter in this circuit, and it also performs the task of ______ (decoding the count, temporarily storing the count).



8-11 Using a CMOS Counter in an Electronic Game

This section will feature a CMOS counter being used in an electronic game. The game is the classic computer game of "guess the number." In the computer version, a random number is generated, and the player tries to guess the unknown number. The computer responds with one of three responses: correct, too high, or too low. The player can then guess again until he or she zeros in on the unknown number. The player who uses the fewest guesses wins the game.

The schematic for a simple electronic version of this game is drawn in Fig. 8-28. To operate the game, first press the push-button switch (SW_1) . This allows the approximately 1-kHz signal into the clock input of the binary counter. When the push button is released, a random binary number (from 0000 to 1111) is held by the counter at the *B* inputs to the 74HC85 4-bit magnitude comparator. The player's guess is entered at the *A* inputs to the comparator IC. If the random number (*B* inputs) and the guess (*A* inputs) are equal, then the $A = B_{\text{OUT}}$ output will be activated (HIGH) and the green LED will light. This means the guess was correct. After a


correct guess, a new random number should be generated by pressing SW_1 .

If a player's guess (A inputs) is lower than the random number (B inputs), the comparator will activate the $A < B_{\rm OUT}$ output. The yellow LED will light. This means that the guess was too low and the player should try again by entering a somewhat higher number.

Finally, if a player's guess (A inputs) is higher than the random number (B inputs), the comparator will activate the $A > B_{\text{OUT}}$ output. The red LED will light. This means that the guess was too high and the player should try again.

Figure 8-29 provides greater detail on the operation of the 74HC85 4-bit magnitude comparator IC. The pin diagram is shown in Fig. 8-29(a). This is the top view of the DIP 74HC85 CMOS IC. The truth table for the 74HC85 comparator is reproduced in Fig. 8-29(b).

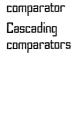The 74HC85 comparator has three "extra" inputs used for *cascading comparators*. Typical cascading of 74HC85 magnitude comparators is shown in Fig. 8-30. This circuit compares the magnitude of the two 8-bit binary words A_7 A_6 A_5 A_4 A_3 A_2 A_1 A_0 and B_7 B_6 B_5 B_4 B_3 B_2 B_1 B_0 . The output from IC_2 is one of three responses (A > B, A = B, or A < B).



74HC85 4-bit

magnitude


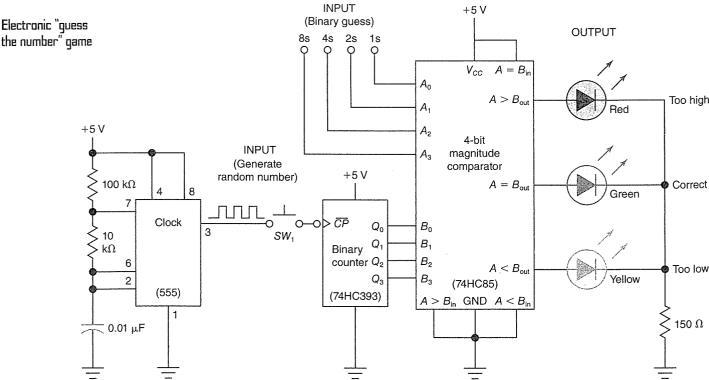


Fig. 8-28 Electronic "quess the number" game.

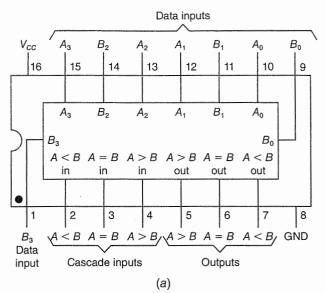

Truth Table-74HC85 Magnitude Comparator IC

A ₃ , B ₃		COMPARING INPUTS					OUTPUTS			
	A_2, B_2	A ₁ , B ₁	A ₀ , B ₀	A > B	A < B	A = B	A > B	A < B	A = B	
$A_3 > B_3$	X	Х	X	Х	X	Х	Н	L	L	
$A_3 < B_3$	Х	Х	Χ	Х	X	X	L	Н	L	
$A_3 = B_3$	$A_2 > B_2$	Х	Х	X	X	X	Н	L	L	
$A_3 = B_3$	$A_2 < B_2$	Х	Χ	X	X	X	L	Н	L	
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	Х	Х	X	X	Н	L	L	
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	Χ	Х	X	Χ	L	Н	L	
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	Х	X	X	Н	L	L	
	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	X	X	X	L	Н	L	
	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	Н	L	L	Н	L	L	
	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	Н	L	L	Н	L	
	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	X	X	Н	L	L	Н	
	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	Н	Н	L	L	L	L	
1	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	L	L	L	Н	Н	L	

Fig. 8-29 CMOS magnitude comparator IC (74HC8S). (a) Pin diagram. (b) Truth table.

74HC85 magnitude comparator IC


-₩- Self-Test

Answer the following questions.

- 63. Refer to Fig. 8-28. If the binary counter holds the number 1001 and your guess is 1011, the ______ [color] LED will light, indicating your guess is _____ (correct, too high, too low).
- 64. Refer to Fig. 8-28. How do you generate a random number before guessing?
- 65. Refer to Fig. 8-28. The 555 timer is wired as a(n) _____ (astable, monostable) multivibrator.
- 66. Refer to Fig. 8-31. List the *color* of the output LED that is lit for each time period $(t_1 \text{ to } t_6)$.



289

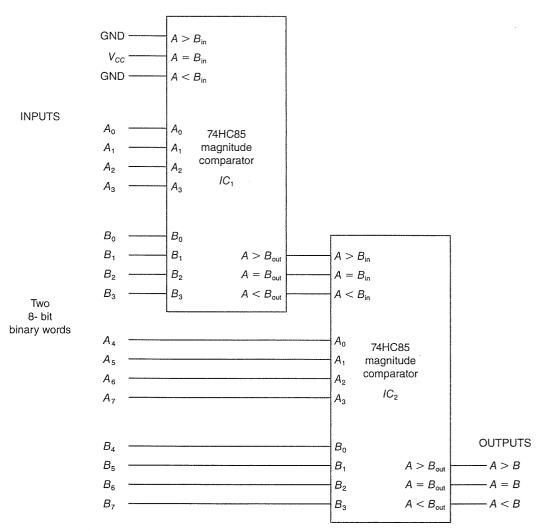

Cascaded magnitude comparators

Fig. 8-30 Cascaded magnitude comparators.

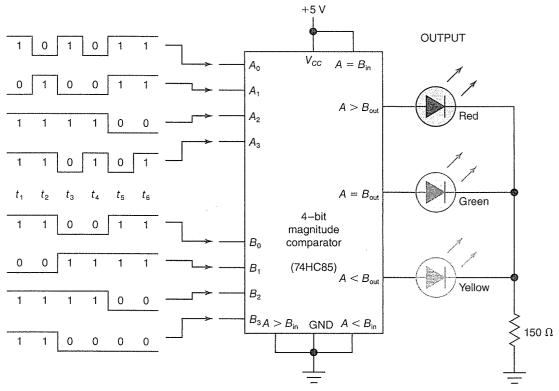


Fig. 8-31 Comparator problem for test item 66.

8-12 Using Counters—An Experimental Tachometer

This section shows how you might integrate subsystems to form an *experimental electronic ta-chometer* system. You will combine known input and output as well as digital devices into a design that will indicate the *angular velocity of a shaft* measured in *rpm* (revolutions per minute).

The first concept drawn of an experimental tachometer using some of the subsystems studied is sketched in Fig. 8-32(a). A 4-digit BCD counter is the heart of the system. The idea is to count each of the input pulses from a Hall-effect

sensor and accumulate that count for a given time such as one minute. The counter would be turned on and count upward in BCD for one minute and then turned off. The count held in the four-digit BCD counter would then be decoded, and the seven-segment display would present the shaft speed in rpm.

The second concept showing the experimental tachometer is sketched in Fig. 8-32(b). This time a three-digit BCD counter becomes the heart of the system. The idea is count the number of input pulses from the Hall-effect sensor in 1/10 of a minute (6 seconds). This would be like counting rpm by 10s. The 1000s, 100s, and

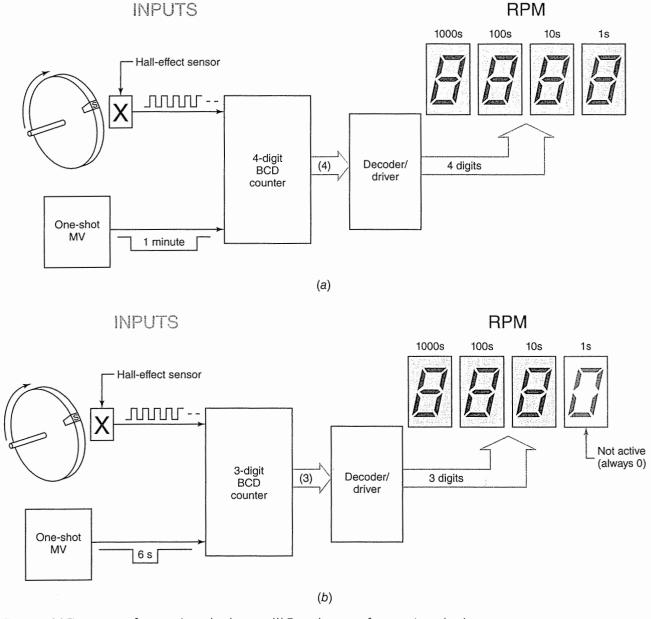


Fig. 8-32 (a) First concept of an experimental tachometer. (b) Second concept of an experimental tachometer.

10s seven-segment displays would present the latest accumulated count from the BCD counters and the 0s place always be considered a 0. Therefore, if the input to the tachometer is 1256 rpm, the three active seven-segment displays would show 125 with the 1s place understood to be 0. This would be interpreted as 1250 rpm.

The second experimental tachometer sketched in Fig. 8-32(*b*) would have a count-up time of only

6 s while the earlier design required a lengthy count time of 1 minute. The sampling time of the second concept experimental tachometer is only 6 seconds. The speed that can be measured by the tachometer in Fig. 8-32(*b*) ranges from 0 to 9990 rpm in increments of 10.

A schematic of an experimental tachometer based on the second concept block diagram [Fig. 8-32(b)] is detailed in Fig. 8-33. This unit

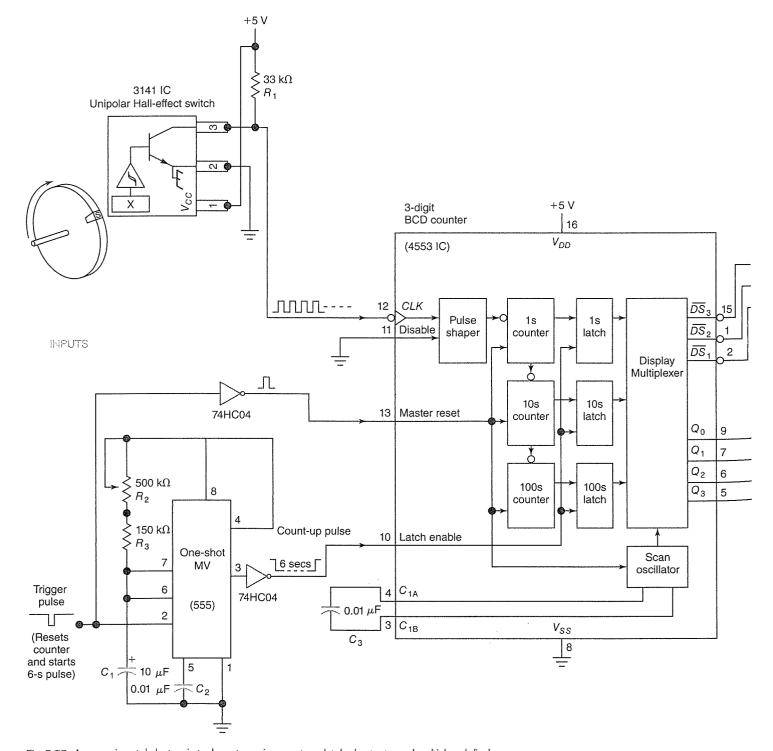



Fig. 8-33 An experimental electronic tachometer using counters, latched outputs, and multiplexed displays.

uses components that you have encountered earlier in your study of electronics.

The input device to the tachometer circuit in Fig. 8-33, which senses the speed of rotation of a shaft, is a Hall-effect switch (3141 IC). A 33 k Ω pull-up resistor (R_1) is required at the output of the 3141 ICs open-collector NPN transistor. The pulses generated by the Hall-effect switch are fed directly into the *CLK* input of the 4553

three-digit BCD counter. Each is pulse from the Hall-effect switch is counted and accumulated in the BCD counter. The three-digit BCD counter can count from $0000\ 0000\ 0000_{BCD}$ to $1001\ 1001\ 1001_{BCD}$ (from 0 to 999 in decimal).

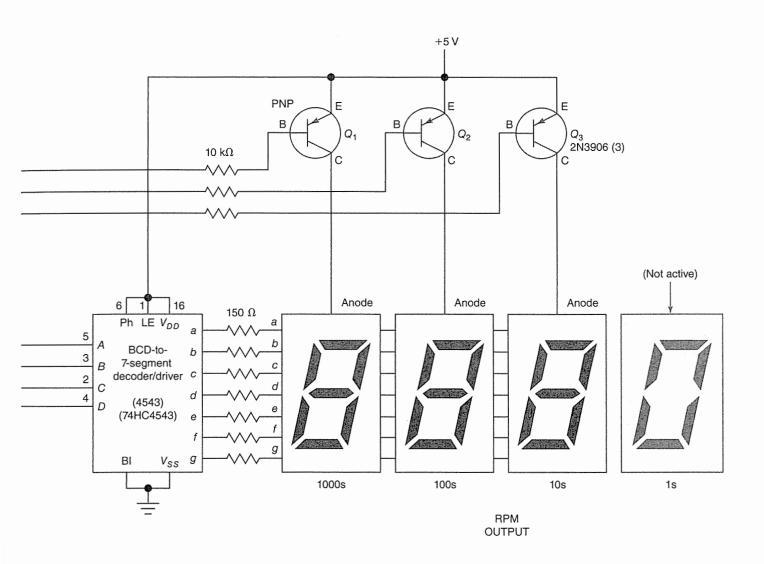A second input shown at the left in Fig. 8-33 is called the trigger pulse. This short negative pulse first clears the counters to 0000 0000 0000 BCD by activating the master reset (MR) with a short



positive pulse emitted by the 74HC04 inverter. Second, the trigger pulse activates the 555 IC wired as a one-shot multivibrator (MV). When triggered, the one-shot MV emits a 6-second (1/10th of a minute) positive pulse, which is inverted by the 74HC04 inverter. The precise length of the count-up pulse can be adjusted using the 500 k Ω potentiometer (R_2). The 6-second negative count-up pulse enters the latch enable (LE) input of the 4553 counter IC. This LOW at the LE input makes the latches transparent, and the outputs of the three BCD counters pass through to the multiplexer. When the count-up pulse is LOW, the displays will be observed counting upward. At the end of the 6-second count-up pulse, the latch enable input is driven active by a HIGH, and the last data accumulated in the three BCD counters are latched at the inputs to the display multiplexer.

The *display multiplexer* section of the 4553 IC shown in Fig. 8-33 lights the three 7-segment LED displays in a rapidly rotating sequence. Details for the lighting sequence are as follows:

1000s Display. The display multiplexer first activates (turns on) PNP transistor Q_1 . This allows +5 V to appear at the anode of the 1000s seven-segment LED display. At this time the display multiplexer sends the segment information for the 1000s display to the 4543 IC for decoding (BCD-to-seven-segment code). The 4543 IC drives the segments of all three LED displays at once with the 1000s data, but only the 1000s display is activated by display driver transistor Q_1 .

100s Display. Second, the display multiplexer activates (turns on) PNP transistor Q_2 . This allows +5 V to appear at the anode of the 100s seven-segment LED display. At this time, the display multiplexer sends the segment information for the 100s display to the 4543 IC for decoding (BCD-to-seven-segment code). The

4543 IC drives the segments of all three LED displays at once with the 100s data, but only the 100s display is activated by display driver transistor Q_2 .

10s Display. Third, the display multiplexer activates (turns on) PNP transistor Q_3 . This allows +5 V to appear at the anode of the 10s seven-segment LED display. At this time, the display multiplexer sends the segment information for the 10s display to the 4543 IC for decoding (BCD-to-seven-segment code). The 4543 IC drives the segments of all three LED displays at once with the 10s data, but only the 10s display is activated by display driver transistor Q_3 .

The display multiplexing in Fig. 8-33 continues at a frequency high enough so the human eye will not detect the displays turning on and off. The display multiplexing frequency is set by the external capacitor C_3 . This frequency is set at about 70 Hz in this circuit. In other words, each seven-segment display turns on and off 70 times each second, but they all appear to be lit continuously.

As a working example, suppose the speed of rotation of input shaft is 1250 rpm. On an external trigger pulse, the experimental tachometer shown in Fig. 8-33 would clear the counters to 000_{10} and the one-shot MV would emit the 6-second count-up pulse. During the 6-second count-up time period, 125 pulses would enter the CLK input and be accumulated in the BCD counters as 0001 0010 0101_{BCD} (125 in decimal). The latch enable input would go HIGH, which would latch the 0001 0010 0101_{BCD} (125 in decimal) at the inputs to the 4553 ICs display multiplexer. The seven-segment displays would be multiplexed with the reading of 125 shown on the left three displays. This would be interpreted as 1250 rpm with the inactive 1s display assumed to be 0.

-\\-\ Self-Test

Answer the following questions.

- 67. An instrument that measures the angular velocity of a rotating shaft in revolutions per minute (rpm) is called a _____ (tachometer, Vu-meter).
- 68. Refer to Fig. 8-33. The interface device used by the tachometer circuit to translate
- from shaft rotation to digital pulses is a(n) _____(Hall-effect switch, optical encoder).
- 69. Refer to Fig. 8-33. The 4553 IC records the number of rotations of the shaft by counting the number of pulses entering the _____ (CLK, master reset) input of the three-digit BCD counter.

- 70. Refer to Fig. 8-33. The negative trigger pulse input first ______ (resets the counter to 000₁₀, sets the counter to 111₁₀) and then causes, the ______ (555, 4543) IC wired as a one-shot MV to generate a 6-second count-up pulse.
- 71. Refer to Fig. 8-33. If the constant rotational speed of the input shaft were 2350 rpm, how many pulses would be counted and accumulated in the BCD counters of the 4553 IC and be displayed after the 6-second count-up pulse goes HIGH?
- 72. Refer to Fig. 8-33. Immediately after the 6-second count-up pulse, the latchenable input is ______ (activated, deactivated) by the HIGH, and the accumulated count is frozen at the inputs to

- the _____ (display multiplexer, pulse shaper) of the 4553 IC.
- 73. Refer to Fig. 8-33. The ______ (counter, display multiplexer) section of the 4553 IC enabled the lighting of the three 7-segment displays in a rapidly rotating sequence.
- 74. Refer to Fig. 8-33. The three PNP transistors $(Q_1, Q_2, \text{ and } Q_3)$ could be described as _____ (digit, segment) drivers during display multiplexing.
- 75. Refer to Fig. 8-33. The external component that sets the frequency of the display multiplexing of the 4553 IC is ______
- 76. Refer to Fig. 8-33. The ______ (4543, 4553) IC decodes and drives the segments of the LED displays.



8-13 Troubleshooting a Counter

Consider the job of troubleshooting the faulty 2-bit ripple counter shown in Fig. 8-34(a). For your convenience, a pin diagram for the 74HC76 IC used in this circuit is shown in Fig. 8-34(b). Note that all of the input and output markings in Fig. 8-34(a) and (b) are not the same. For instance, the asynchronous preset inputs on the logic diagram are labeled PS. The same inputs are labeled PR (for preset) by another manufacturer. The labels on the pins may be different from manufacturer to manufacturer. However, the pins on an IC labeled as a 74HC76 serve the same function even if the labeling is different.

It is found that the faulty 2-bit counter circuit can be cleared to 00 by the reset switch at the left in Fig. 8-34(a). The IC seems to be operating at the correct temperature, and the technician can see or smell no signs of trouble.

A digital logic pulser is used to pulse the *CLK* input on FF 1. According to the pin diagram, the tip of the digital pulser must touch pin 1 of the 74HC76 IC. Upon repeated single pulses, the counting sequence is 00 (reset), 01, 10, 11, 10, 11, 10, 11, and so on. The *Q* output of FF 2 seems to be "stuck HIGH"; however, the asynchronous clear (*CLR*), or reset, switch can drive it LOW.


Power is then turned off in the circuit in Fig. 8-34(a). A logic clip is clipped over the pins on the 74HC76 IC. Power is turned on again. The reset switch is activated. The results displayed on the logic monitor after the reset are shown in Fig. 8-34(c). Compare the logic levels shown on the logic monitor with your expectations. You must use the manufacturer's pin diagram furnished in Fig. 8-34(b). In looking over the logic levels pin by pin, the LOW or undefined logic level at pin 7 should cause concern. This is the asynchronous preset (PS or PR) input and should be HIGH according to the logic diagram in Fig. 8-34(a). If it is LOW or in the undefined region, it can cause the Q output of FF 2 to be in the "stuck HIGH" condition.

A logic probe is used to check pin 7 of the 74HC76 IC. Both LEDs on the logic probe remain off. This means neither a LOW nor a HIGH logic level is present. Pin 7 appears to be floating in the undefined region between LOW and HIGH. The IC is interpreting this as LOW at some times and as HIGH at other times.

The IC is removed from the 16-pin DIP IC socket. It is found that pin 7 of the IC is bent under and not making contact with the IC socket. This caused it to float. The fault is illustrated in Fig. 8-35. This common fault is

Troubleshooting a counter

2-bit ripple counter

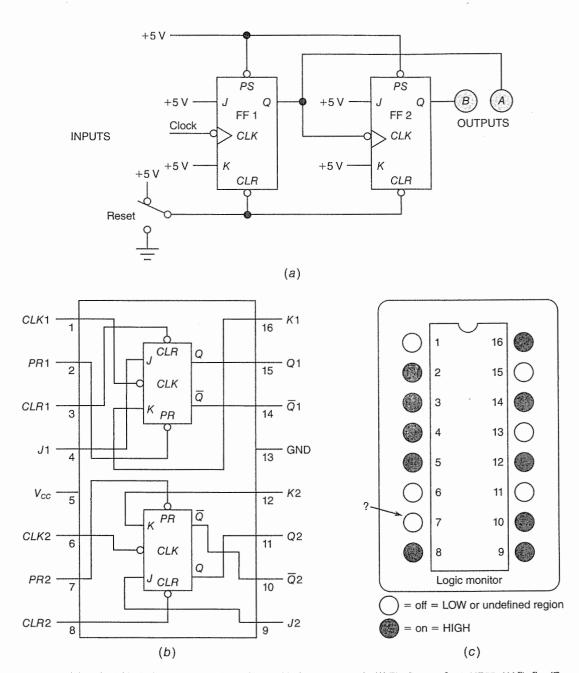

Troubleshooting a faulty counter

Fig. 8-34 (a) Faulty 2-bit ripple counter circuit used in troubleshooting example. (b) Pin diagram for 74HC76 J-K flip-flop IC. (c) Logic clip reading after momentarily resetting the faulty 2-bit counter.

very hard to see when the IC is seated in the IC socket.

In this example, several tools were used in troubleshooting. First, the logic diagram and your knowledge of how it works are most important. Second, a manufacturer's pin diagram was used. Third, a digital logic pulser was used to inject single pulses. Fourth, a logic clip checked the logic level at all pins of the 74HC76 IC. Fifth, a logic probe was used to

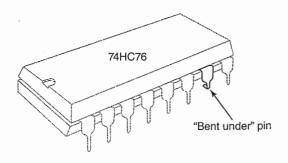


Fig. 8-35 Bent pin caused input to float.

check the suspected pin of the IC. Finally, your knowledge of the circuit and visual observation solved the problem.

Your knowledge of the circuit's normal operation and your powers of observation are probably the most important troubleshooting tools. Logic pulser, logic probes, logic clips, DMMs, logic analyzers, IC testers, and oscilloscopes

are only aids to your knowledge and powers of observation.

The example of a floating input caused by a bent-under pin is a very common problem in student-constructed circuits. It is good practice to make sure all inputs go to the proper logic level. This is true for TTL and especially true for CMOS circuits.

Most important troubleshooting tools


-W-

Self-Test

Supply the missing word or words in each statement.

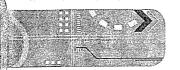- 77. Refer to Fig. 8-34. Pins 4, 9, 12, and 16 to the *J* and *K* inputs of the flip-flops should all be _____ (HIGH, LOW) in this circuit.
- 78. Refer to Fig. 8-34. Pins 3 and 8 to the _____ inputs of the flip-flops should follow the logic state of the reset switch.
- 79. Refer to Fig. 8-34. Pins 2 and 7 to the ______ inputs of the flip-flops should be _____ (HIGH, LOW) in this circuit.
- 80. Refer to Fig. 8-34. The fault in this circuit was located at pin ______ [number]. It was _____ rather than being at a HIGH logic level.





Chapter 8 Summary and Review

Summary

- 1. Flip-flops are wired together to form binary counters.
- 2. Counters can operate asynchronously or synchronously. Asynchronous counters are called ripple counters and are simpler to construct than synchronous counters.
- 3. The modulus of a counter is how many different states it goes through in its counting cycle. A mod-5 counter counts 000, 001, 010, 011, 100 (0, 1, 2, 3, 4 in decimal).
- 4. A 4-bit binary counter has four binary place values and counts from 0000 to 1111 (decimal 0 to 15).
- 5. Gates can be added to the basic flip-flops in counters to add features. Counters can be made to stop at a certain number. The modulus of a counter can be changed.
- 6. Counters are designed to count either up or down. Some counters have both features built into their circuitry.
- 7. Counters are used as frequency dividers. Counters are also widely used to count or sequence events and temporarily store data.
- 8. Manufacturers produce a wide variety of selfcontained IC counters. They produce detailed data sheets for each counter IC. Several TTL and CMOS counter ICs were studied in this chapter.
- 9. Many variations in pin labeling and logic symbols occur from manufacturer to manufacturer.

- 10. A transducer such as an optical sensor can be used to count real-world events such as in shaft encoding. Optical encoders come in slot types and reflective types, and both are based on an infrared diode shining on an output phototransistor.
- 11. A magnitude comparator will compare two binary numbers and decide if A = B, A > B, or A < B. Magnitude comparator ICs can be cascaded to compare larger binary numbers.
- 12. A decade counter counts from 0 through 9 (0000–1001 in binary). Decade counters are also commonly called BCD (binary-coded decimal) counters.
- 13. One trend in the manufacture of a digital IC is to include more functions on one chip. As a simple example, the 4553 three-digit BCD counter IC contains three BCD counters, waveshaping, twelve transparent latches, and display multiplexing.
- 14. A transducer such as a Hall-effect switch may be used to sense rotations of a shaft which can be counted in a given time period, yielding an output in revolutions per minute. An instrument that measures speed of rotation of a shaft is called a tachometer.
- 15. The technician's knowledge of the circuit and powers of observation are the most important tools in troubleshooting. The logic probe, voltmeter, DMM, logic clip, digital pulser, logic analyzer, IC tester, and oscilloscope aid the technician's observations when troubleshooting sequential logic circuits.

Chapter Review Questions

Answer the following questions.

- 8-1. Draw a logic symbol diagram of a mod-8 ripple up counter. Use three J-K flip-flops. Show input *CLK* pulses and three output indicators labeled *C*, *B*, and *A* (*C* indicator is MSB).
- 8-2. Draw a table (similar to Fig. 8-1) showing the binary and decimal counting sequence of the mod-8 counter in question 8-1.
- 8-3. Draw a waveform diagram [similar to Fig. 8-2(*b*)] showing the eight *CLK* pulses and the outputs (*Q*) of FF 1, FF 2, and FF 3 of the mod-8 counter from question 8-1. Assume you are using negative-edge-triggered flip-flops.
- 8-4. A(n) _____ (asynchronous, synchronous) counter is the more complex circuit.

- 8-5. Synchronous counters have the *CLK* inputs connected in _____ (parallel, series).
- 8-6. Draw a logic symbol diagram for a 4-bit ripple down counter. Use four J-K flip-flops in this mod-16 counter. Show the input *CLK* pulses, *PS* input, and four output indicators labeled *D*, *C*, *B*, and *A*.
- 8-7. If the ripple down counter in question 8-6 is a recirculating type, what are the next three counts after 0011, 0010, and 0001?
- 8-8. Redesign the 4-bit counter in question 8-6 to count from binary 1111 to 0000 and then *stop*. Add a four-input OR gate to your existing circuit to add this self-stopping feature.
- 8-9. Draw a block diagram (similar to Fig. 8-13) showing how you would use two counters to get an output of 1 Hz with an input of 100 Hz. Label your diagram.
- 8-10. Refer to Fig. 8-14 for questions **a** to **f** on the 7493 IC counter:
 - a. What is the maximum count length of this counter?
 - b. This is a _____ (ripple, synchronous) counter.
 - c. What must be the conditions of the reset inputs for the 7493 to count?
 - d. This is a(n) _____ (down, up) counter.
 - e. The 7493 IC contains ______ [number] flip-flops.

- 8-11. Refer to Fig. 8-15 for questions **a** to **f** on the 74192 counter:
 - a. What is the maximum count length of this counter?
 - b. This is a _____ (ripple, synchronous) counter.
 - c. A logical ______(0, 1) is needed to clear the counter to 0000.
 - d. This is a(n) _____ (down, up, both up and down) counter.
 - e. How could we preset the outputs of the 74192 IC to 1001?
 - f. How do we get the counter to count downward?
- 8-12. Draw a diagram [similar to Fig. 8-16(*a*)] showing how you would wire the 7493 counter as a 4-bit (mod-16) ripple counter. Refer to Fig. 8-14.
- 8-13. Refer to Fig. 8-36. The 74192 counter is in the _____ (clear, count up, load) mode during pulse t_1 .
- 8-14. List the binary output from the 74192 counter IC after each of the eight input pulses shown in Fig. 8-36. Start with t_1 and end with t_2 .
- 8-15. Refer to Fig. 8-18 for questions **a** to **e** on the 74HC393 IC counter:
 - a. This is a _____ (ripple, synchronous) counter.
 - b. This is a(n) _____ (down, up, either up or down) counter.

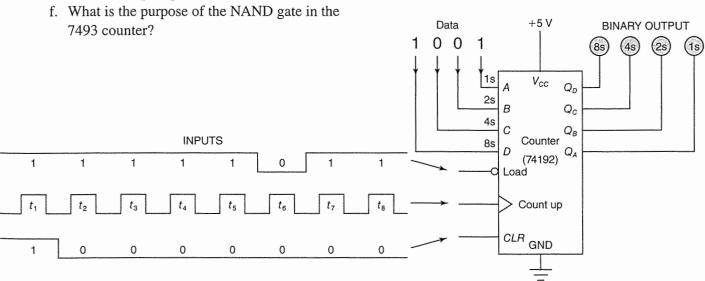


Fig. 8-36 Counter pulse-train problem.

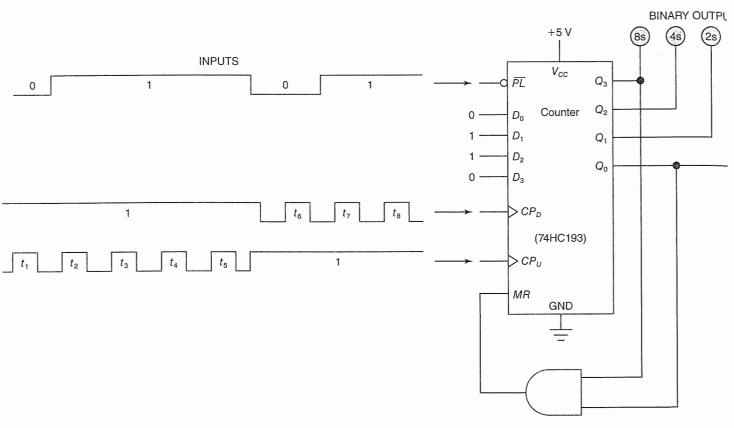


Fig. 8-37 Counter pulse-train problem.

- c. The MR pins are ______ (asynchronous, synchronous) active _____ (HIGH, LOW) inputs that clear the outputs.
- d. Each counter contains four _____ (R-S, T) flip-flops.
- e. This is a _____ (CMOS, TTL) counter.
- 8-16. Refer to Fig. 8-19 for questions **a** to **e** on the 74HC193 IC counter:
 - a. When the MR pin is activated with a _____ (HIGH, LOW), all outputs are reset to _____ (0, 1).
 - b. This is a _____ (ripple, synchronous) counter.
 - c. Parallel data from the data inputs $(D_0 \text{ to } D_3)$ flow through to the outputs $(Q_0 \text{ to } Q_3)$ when the _____ input is activated with a LOW.
 - d. When a clock signal enters pin CP_{υ} , the CP_{D} pin must be tied to _____ (+5 V, GND).

- 8-17. Refer to Fig. 8-37. List the mode of operation for the 74HC193 counter during each pulse t_1 to t_8 (use answers *parallel load, count up, count down*).
- 8-18. Refer to Fig. 8-37. List the binary output for the 74HC193 counter IC after each pulse t_1 to t_8 .
- 8-19. Refer to Fig. 8-22. The CLK input to the 4553 counter IC is triggered on the ______ (H-to-L, L-to-H) transition of the input pulse.
- 8-20. Refer to Fig. 8-22. List whether the following inputs to the 4553 counter IC are active HIGH or active LOW.
 - a. Disable input
 - b. Master reset input
 - c. Latch-enable input
- 8-21. Refer to Fig. 8-22. List whether the following outputs from the 4553 counter IC are active HIGH or active LOW.
 - a. DS, output
 - b. DS, output
 - c. DS₃ output
 - d. BCD outputs $(Q_0 Q_3)$

- 8-22. Refer to Fig. 8-23. If the MR input to the 4553 IC goes HIGH, what happens to the contents of the counters?
- 8-23. Refer to Fig. 8-23. External capacitor C_1 is associated with the ______ (counter, scan oscillator and display multiplexer) section of the 4553 IC.
- 8-24. Refer to Fig. 8-23. The 12 latches in the 4553 IC are said to be ______ (latched, transparent) when the LE input is LOW.
- 8-25. Refer to Fig. 8-23. The 4543 IC is closely associated with segment driving while the three PNP transistors are associated with display driving.

 (T or F)
- 8-26. Refer to Fig. 8-24(*b*). The device optically sensing the opening in the shaft encoder disk and sending a signal to the waveshaping circuit is a(n) ______.
- 8-27. Refer to Fig. 8-24(*b*). The optical encoder at the top of the shaft encoder disk is of the _____ (reflective type, slot type).
- 8-28. Refer to Fig. 8-25(*b*). The H21A1 interrupter module contains a(n) ______ on the

- emitter side and a phototransistor on the detector side of the optical sensor.
- 8-29. Refer to Fig. 8-26. The device that performs wave-shaping in this circuit is the _____ (7414, 74192) IC.
- 8-30. Refer to Fig. 8-26. The device that performs as a decade counter in this circuit is the ______ (7447, 74192) IC.
- 8-31. Refer to Fig. 8-26. The 7447 IC is a decoder/driver that translates BCD data to _____ code and drives the display.
- 8-32. Refer to Fig. 8-27(*b*). The disk shown (black and white strips) would be an encoder disk used by a ______ (reflective-type, slot-type) optical sensor.
- 8-33. Refer to Fig. 8-30. The two 74HC85 magnitude comparator ICs are said to be _____ (cascaded, subdivided) so they can compare two _____ [number]-bit binary numbers.
- 8-34. Refer to Fig. 8-38. List the *color* of the output LED that is lit for each time period $(t_1 \text{ to } t_6)$.
- 8-35. A tachometer is an instrument that measures the speed of rotation of a shaft in revolutions per minutes. (T or F)

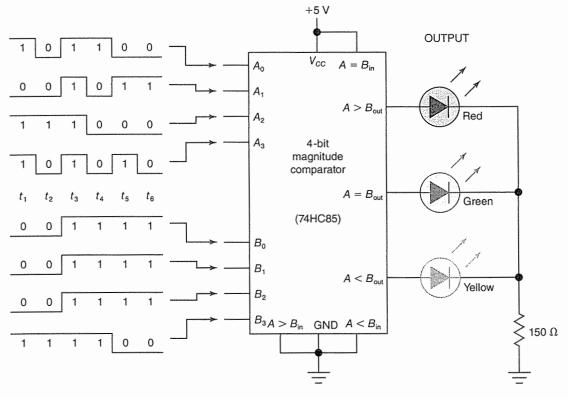


Fig. 8-38 Magnitude comparator pulse-train problem.

- 8-36. Refer to Fig. 8-33. Each rotation of the input shaft will be converted into four pulses that enter the *CLK* input of the 4553 counter IC. (T or F)
- 8-37. Refer to Fig. 8-33. What two things happen when the negative input trigger pulse occurs?
- 8-38. Refer to Fig. 8-33. When the output of the one-shot MV goes LOW for 6 seconds, the 4553 IC _____ (counts the input pulses, latches [freezes] the outputs of the counters).
- 8-39. Refer to Fig. 8-33. The _______ (display multiplexing, pulse-shaper) section of the 4553 IC coordinates the lighting of the three 7-segment LED displays in a rapidly rotating sequence so only one display is turned on at a time.
- 8-40. Refer to Fig. 8-33. If the 4543 decoder/driver IC is called the *segment driver*, then the three PNP

- transistors $(Q_1, Q_2, \text{ and } Q_3)$ would be called the _____ (display, scanner) drivers.
- 8-41. Refer to Fig. 8-33. The purpose of the external capacitor C_1 is to decouple the internal circuitry of the 4553 counter IC from ground (GND). (T or F)
- 8-42. Refer to Fig. 8-33. At a given instant, only one DS output from the 4553 counter IC is ______ (HIGH, LOW) at a given time to turn on its respective PNP transistor and display.
- 8-43. Refer to Fig. 8-33. When the ______ (*CLK*, latch-enable) input goes HIGH, the data accumulated in the BCD counters are frozen at the inputs to the display multiplexer while the counters can continue to count pulses.
- 8-44. A digital ______ (IC tester, pulser) is an instrument for injecting a signal into a circuit.

Critical Thinking Questions

- 8-1. What types of flip-flops are useful in wiring counters because they have a toggle mode?
- 8-2. Draw a logic symbol diagram of a mod-5 ripple up counter. Use three J-K flip-flops and a two-input NAND gate. Show input *CLK* pulses and three output indicators labeled *C*, *B*, and *A* (*C* indicator is MSB).
- 8-3. Draw a logic diagram for a mod-10 counter using a 7493 IC.
- 8-4. Draw a logic diagram of a divide-by-8 counter using a 7493 IC. Show which output of the 7493 IC is the divide-by-8 output.
- 8-5. Refer to Fig. 8-36. List the mode of operation during each of the input pulses t_1 to t_0 .
- 8-6. Refer to Fig. 8-18. Why are the master reset inputs (1MR and 2MR) referred to as asynchronous?
- 8-7. Refer to Fig. 8-19. The 74HC193 IC counter is called presettable because of what operating mode?
- 8-8. Refer to Fig. 8-37. Give the modulus and list the counting sequence for this counter.
- 8-9. Design a decade up counter (0 to 9 in decimal) using a 74HC193 IC and a two-input AND gate.

- 8-10. On a(n) ______ (asynchronous, synchronous) counter, all outputs change to their new states at the same instant.
- 8-11. What is another name for an asynchronous counter?
- 8-12. If we refer to a divide-by-6 counter, the circuit will probably be used for what purpose?
- 8-13. Refer to Fig. 8-26. The counter and display will increase by one when the output of the inverter goes from ______ (H to L, L to H).
- 8-14. Refer to Fig. 8-26. The counter and display will increment when the beam of infrared light across the slot ______.
 - a. is broken (from light to no light)
 - b. begins again (from no light to light)
- 8-15. Compare the shaft encoder disks in Figs. 8-24(*b*) and 8-27(*b*). Which disk will provide the greater resolution?
- 8-16. Refer to Fig. 8-22(*a*). How many T flip-flops are probably used to implement the three BCD counters in the 4553 IC?
- 8-17. Refer to Fig. 8-22(*a*). How many transparent latches are probably used in the 4553 IC to latch the data from the three BCD counters?

Critical Thinking Questions...continued

- 8-18. Refer to Fig. 8-33. How would you adjust the time duration of the *count up pulse* emitted from the one-shot multivibrator?
- 8-19. Refer to Fig. 8-33. How many pulses are emitted
- from the Hall-effect switch for each rotation of the shaft?
- 8-20. Refer to Fig. 8-33. Explain why the 1s display is not active and is considered to be a zero (0).



Answers to Self-Tests

- 1. two
- 2. 4
- 3. toggle
- 4. pulse $t_1 = 00$
 - pulse $t_2 = 01$
 - pulse $t_3 = 10$
 - pulse $t_4 = 11$
 - pulse $t_5 = 00$
 - pulse $t_6 = 01$
- 5. ripple, decade
- 6. pulse $t_1 = 111$, then cleared to 000 just
 - before pulse t_2
 - pulse $t_{2} = 001$
 - pulse $t_3 = 010$
 - pulse $t_{4} = 011$
 - pulse $t_{5}^{4} = 100$
 - pulse $t_{6} = 000$
- 7. ripple, 5
- 8. synchronous
- 9. parallel
- 10. toggle
- 11. all the flip-flops toggle
- 12. FF 3
- 13. toggle
- 14. HIGH-to-LOW
- 15. only FF 1 toggles
- 16. pulse $t_1 = 00$
 - pulse $t_2 = 11$
 - pulse $t_3 = 10$
 - pulse $t_{A} = 01$
 - pulse $t_5 = 00$
 - pulse $t_6 = 11$
- 17. down
- 18. LOW, hold
- 19. HIGH, toggle

- 20. T
- 21. $t_4 = 100$
 - $t_5 = 011$
 - $t_6 = 010$
 - $t_7 = 010$
 - $t_{8} = 010$
- 22. 1000
- 23. 2
- 24. 0000 (reset)
- 25. four, up
- 26. decade, synchronous
- 27. 5
- 28. HIGH
- 29. active LOW LOAD
- 30. down and up
- 31. T
- 32. point B = 200 Hz
 - point C = 100 Hz
 - point D = 50 Hz
- 33. 8
- 34. 4-bit binary
- 35. HIGH
- 36. H-to-L
- 37. 16, ripple
- 38. synchronous
- 39. asynchronous
- 40 0 0
- 40. $Q_0 Q_3$
- 41. 0001, 0010, 0011, 0100, 0101, 0110 (1 to 6 in decimal)
- 42. To preset the counter to 0001 after the highest count of 0110.
- 43. Manufacturers use different standards when drawing logic symbols and labeling.
- 44. counters, multiplexer
- 45. active HIGH, resets all counter outputs to 0

- 46. H-to-L
- 47. negative-edge
- 48. active HIGH
- 49. LOW
- 50. F
- 51. T
- 52. set the scan frequency of the multiplexer
- 53. 4543
- 54. 4553
- 55. 000 to 999
- 56. interrupter module
- 57. infrared
- 58. phototransistor
- 59. slot-type
- 60. L to H (LOW to HIGH)
- 61. enters
- 62. decade, temporarily storing the count
- 63. red, too high
- 64. press and release switch SW_1
- 65. astable

- 66. $t_1 = green$
 - $t_2 = \text{red}$
 - t_3 = yellow
 - $t_{\Delta} = \text{red}$
 - t_5 = green
 - $t_6 = \text{red}$
- 67. tachometer
- 68. Hall-effect switch
- 69. CLK
- 70. resets the counter to 000_{10} , 555
- 71. 235
- 72. activated, display multiplexer
- 73. display multiplexer
- 74. digit
- 75. C_3 or capacitor C_3
- 76. 4543
- 77. HIGH
- 78. clear
- 79. preset (asynchronous), HIGH
- 80. 7, floating



Shift Registers

Learning Outcomes

This chapter will help you to:

- **9-1** Define shift register operations such as shift right, shift left, parallel load, and serial load. Draw a circuit diagram of a serial-load shift register using D flip-flops.
- **9-2** *Understand* the operation of a parallelload shift register, including modes of operation such as asynchronous clear, shift right, and parallel load. *Predict* the operation of a 4-bit shift register with a recirculating feature.
- **9-3** Interpret the many modes of operation of the TTL 74194 4-bit bidirectional universal shift register IC.
- **9-4** Predict the actions of the 74194 shift register when used in its various modes of operation (clear, parallel load, shift right, shift left, and inhibit).
- **9-5** *Interpret* the operation of the CMOS 74HC164 8-bit serial-load shift register.
- 9-6 Study the operation of a simple system (a digital roulette game). Analyze the operations of the subsystems including (a) clock input with a voltage-controlled oscillator, (b) audio output with a simple audio amplifier, (c) LED outputs with eight LEDs driven by the 74HC164 shift register wired as a ring counter, and (d) power-up initializing circuit with auto clearing and loading a ring counter with a single HIGH.
- **9-7** *Troubleshoot* a faulty 4-bit serial-load shift register circuit.

register is a group of memory cells grouped together and considered a single unit. For example, an 8-bit register could be used to store a byte of data. The register can be used to simply store information for later use, or the register can be designed to act on the data as is the case of a shift register. A shift register may modify the contents by shifting data right or left.

The term *latch* may be used to describe the register used to store data. You may have used several transparent latches in previous chapters and know that they are commonly constructed using flip-flops (such as D flip-flops). A *buffer register* is a specific use of a storage device that holds data that are waiting to be transferred. For instance, a buffer is used to temporarily store data while they are waiting to be used by a printer.

A typical example of a shift register at work is found within a calculator. As you enter each digit on the keyboard, the numbers shift to the left on the display. In other words, to enter the number 268 you must do the following. First, you press and release the 2 on the keyboard; a 2 appears at the extreme right on the display. Next, you press and release the 6 on the keyboard, causing the 2 to shift one place to the left and allowing 6 to appear on the extreme right; 26 appears on the display. Finally, you press and release the 8 on the keyboard; 268 appears on the display. This example shows two important characteristics of a shift register: (1) It is a *temporary memory* and thus holds the numbers on the display (even if you release the keyboard number) and (2) it shifts the numbers to the left on the display each time you press a new digit on the keyboard.

Memory and shifting characteristics These *memory* and *shifting characteristics* make the shift register extremely valuable in most digital electronic systems. This chapter introduces you to shift registers and explains their operations.

Shift registers Serial in–serial out

Serial in-parallel out

Parallel in-serial out

Parallel in-parallel out

Shift registers are constructed by wiring flip-flops together. We mentioned before that flip-flops have a memory characteristic. This memory characteristic is put to good use in a shift register. Instead of wiring shift registers by using individual gates or flip-flops, you can buy shift registers in IC form. In larger-scale digital devices (microcontrollers, microprocessors), the registers are integrated into the chip design.

One method of describing shift register characteristics is by how data are *loaded into* and *read from* the storage units. Four categories of shift registers are illustrated in Fig. 9-1. Each storage device in Fig. 9-1 is an 8-bit register. The registers are classified as:

- 1. Serial in–serial out [Fig. 9-1(a)]
- 2. Serial in–parallel out [Fig. 9-1(b)]
- 3. Parallel in–serial out [Fig. 9-1(c)]
- 4. Parallel in–parallel out [Fig. 9-1(*d*)]

The diagrams in Fig. 9-1 illustrate the fundamental idea of each type of register. These classifications are often used in a manufacturer's literature.

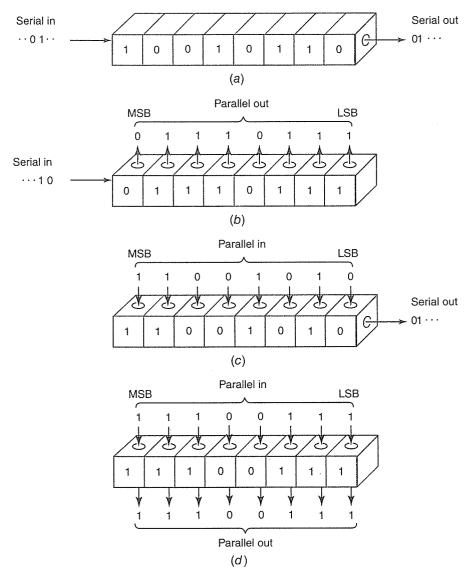


Fig. 9-1 Shift register characteristics. (a) Serial in—serial out. (b) Serial in—parallel out. (c) Parallel in—serial out. (d) Parallel in—parallel out.

9-1 Serial-Load Shift Registers

A basic shift register is shown in Fig. 9-2. This shift register is constructed from four D flip-flops. This register is called a 4-bit shift register because it has four places to store data: A, B, C, D.

With the aid of Table 9-1 and Fig. 9-2, let us operate this shift register. First, clear (*CLR* input to 0) all the outputs (*A*, *B*, *C*, *D*) to 0000. (This situation is shown in line 1, Table 9-1.) The outputs remain 0000 while they await a clock pulse. Pulse the *CLK* input once; the output now shows 1000 (line 3, Table 9-1) because

the 1 from the *D* input of FF *A* has been transferred to the *Q* output on the clock pulse. Now enter 1s on the data input (clock pulses 2 and 3, Table 9-1); these 1s shift across the display to the right. Next, enter 0s on the data input (clock pulses 4 to 8, Table 9-1); you can see the 0s being shifted across the display (lines 6 to 10, Table 9-1). On clock pulse 9 (Table 9-1) enter a 1 at the data input. On pulse 10 the data input is returned to 0. Pulses 9 to 13 show the single 1 on display being shifted to the right. Line 15 shows the 1 being shifted out the right end of the shift register and being lost.

Serial-load shift registers

4-bit shift register

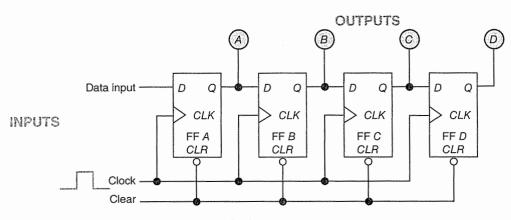


Fig. 9-2 A 4-bit serial-load shift register using O flip-flops.

	Inp	uts	011-	Output					
Line			Clock Pulse	FF A	FF B	FF C	FF D		
Number Clear Data		Number	Α	В	С	D			
1, 11,	0	0	0	0	0	0	0		
2	1	1	0	0	0	0	0		
3	1	• 1	1	1	0	0	0		
4	1	1	2	1	1	0	0		
5	1	1	3	1.	1	1	0		
6	1	0	4	0	1	1	1		
7	ja – 1 54 ju	0	5	0	0		1		
8	1	0	6	0	0	0	1		
9	1	0	7	0	0	0	0		
10	1	0	8	0	0	0	0		
. 11	1		9		0	0	0		
12	1	0	10	0	1	0	0		
13		0	11	0	0	1	0		
14	1	0	12	0	0	0	1		

Remember that the D flip-flop is also called a *delay* flip-flop. Recall that it simply transfers the data from input D to output Q after a delay of one clock pulse.

The circuit diagrammed in Fig. 9-2 is referred to as a *serial-load shift register*. The term "serial load" comes from the fact that only one bit of data at a time can be entered in the register. For instance, to enter 0111 in the register, we had to go through the sequence from lines 3 through 6 in Table 9-1. It took four steps to serially load 0111 into the serial-load shift register. To enter 0001 in this serial-load shift register,

we need four steps, as shown in Table 9-1, lines 11 to 14. According to the classifications in Fig. 9-1, this would be a serial in–parallel out register. However, if data were taken from only FF *D*, it becomes a serial in–serial out register.

The shift register in Fig. 9-2 could become a 5-bit shift register just by adding one more D flip-flop. Shift registers typically come in 4-, 5-, and 8-bit sizes. Shift registers also can be wired using other flip-flops. J-K flip-flops and clocked R-S flip-flops are also used to wire shift registers.

-W- Self-Test

Answer the following questions.

- 1. The unit shown in Fig. 9-3 is a shift-right _____ (parallel, serial)-load shift register.
- 2. List the contents of the register in Fig. 9-3 after each of the six clock pulses starting with t_1 (A = left bit, C = right bit).
- 3. A(n) ______ (entire 3-bit group, single bit) is loaded on each clock pulse in the serial-load shift register in Fig. 9-3.
- 4. The clear (*CLR*) input to the shift register in Fig. 9-3 is active _____ (HIGH, LOW).
- 5. The clear input in Fig. 9-3 must be _____ (HIGH, LOW) and a ____ (H-to-L, L-to-H) clock pulse at the *CLK* input will trigger a right shift in this register.

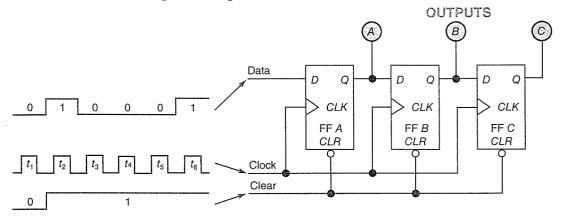


Fig. 9-3 A shift register problem for test items 1 through 5.



Parallel-load shift registers

Recirculating feature

9-2 Parallel-Load Shift Registers

The serial-load shift register we studied in the last section has two disadvantages: It permits only one bit of information to be entered at a time, and it loses all its data out the right side when it shifts right. Figure 9-4(a) illustrates a

system that permits parallel loading of four bits at once. These inputs are the data inputs A, B, C, and D in Fig. 9-4. This system could also incorporate a recirculating feature that would put the output data back into the input so that they are not lost.

A wiring diagram of the 4-bit parallelload recirculating shift register is drawn in Fig. 9-4(b). This shift register uses four J-K flip-flops. Notice the recirculating lines leading from the Q and \overline{Q} outputs of FF D back to the J and K inputs of FF A. These feedback lines cause the data that would normally be lost out of FF D to recirculate through the shift register. The CLR input clears the outputs to 0000 when enabled by a logical 0. The parallel-load data inputs A, B, C, and D are connected to the active LOW preset (PS) inputs of the flip-flops to set 1s at any output position (A, B, C, D). If the switches attached to the parallel-load data inputs are even temporarily switched to a 0, that output will be preset to a logical 1. The clock pulsing the CLK inputs of the J-K flipflops will cause data to be shifted to the right. The data from FF D will be recirculated back to FF A.

Table 9-2 will help you understand the operation of the parallel-load shift register. As you turn on the power, the outputs may assume any combination. Line 2 shows the register being cleared with the *CLR* input. Line 3 shows 0100 being loaded into the register using the parallel-load data switches. An asynchronous parallel load occurs whenever a parallel-load input goes LOW. Notice in line 3, input *B* is at 0 causing the corresponding output *B* to be set to 1.

Lines 4 through 8 in Table 9-2 show five clock pulses (t_1-t_5) shifting data to the right. Examine the outputs in lines 5 and 6. The 1 from FF D (on right) in line 5 is being recirculated back to the left FF A in line 6.

Line 9 shows the register being cleared again by the *CLR* input. New information (0110) is being loaded in the data inputs in line 10. Lines 11 to 15 illustrate the register being

4-bit parallel-load recirculating shift register

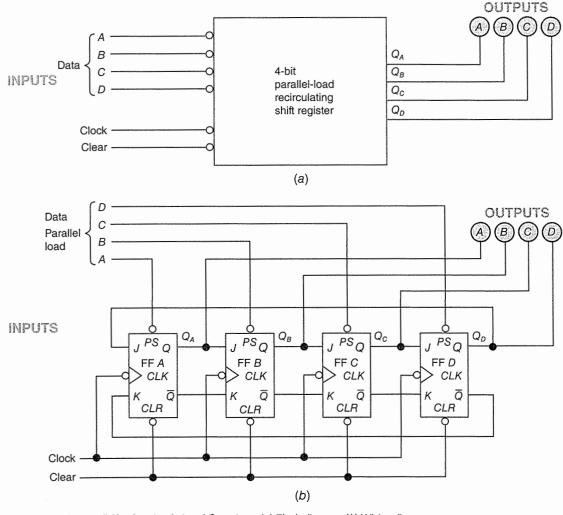


Fig. 9-4 A 4-bit parallel-load recirculating shift register. (a) Block diagram. (b) Wiring diagram.

Table 9-2 Operation of	a 4-Bit Paralle	Load Reci	culatio	g Shift I	Register						
				Inp	uts				Outp	ut	
Mode of	Line			Paralle	l Load		Clock	FF A	FF B	FF C	FF D
Operation	Number	Clear	Α	В	С	D	Pulse	Α	В	С	D
Power up	1	1	1	1	1	1			(Random	outputs)	
Clear (asynchronous)	2	0	. 1	1	1	1		0	. 0	0.,	0
Parallel load (asynchronous)	3	1	1	0	1	1		0	1	0	0
Shift right	4	1	1	1	1	1	t,	. 0	0	1	0
Shift right	5	1	1	1	1	1	t ₂	0	0	0	1
Shift right	6	1.	. 1	1	1	1	t ₃	1	0	0	0
Shift right	7	1	1	1	1	1	t ₄	0	1	0	0
Shift right	8	1	1	1	1	1	t ₅	0	0	1	0
Clear (asynchronous)	9	0	1	1	1	1		0	0	0	0
Parallel load (asynchronous)	10	1	1	. 0	0	. 1		0	1	1	0
Shift right	11	1	1	1	1	1	t ₆	0	0	1	1
Shift right	12	1	1	1	1	1	t ₇	· 1	0	0	
Shift right	13	1	1	1	1	1	t ₈	1	1	0	0
Shift right	14	1 .	1	1 -	1	. 1	t ₉	0	1	1,0	0
Shift right	15	1	1	1	1	1	t ₁₀	0	0	1	1

shifted five times by clock pulses. Note that it takes four clock pulses to come back to the original data in the register (compare lines 11 and 15 or lines 4 and 8 in Table 9-2). The register in Fig. 9-4 could be classified as a parallel in–parallel out storage device.

The recirculating feature of the shift register in Fig. 9-4(b) can be disabled by disconnecting the two recirculating lines. The register is then a parallel in–parallel out register. However, if only the output from FF D is considered, this register is a parallel in–serial out storage device.

-N- Self-Test

Answer the following questions.

- 6. The unit in Fig. 9-5 is a shift-right
 _____ (serial, parallel)-load recirculating shift register.
- Refer to Fig. 9-5. List the mode of operation of the shift register during each of the eight clock pulses (start with pulse t₁). Use as answers the terms "clear," "parallel load," and "shift right."
- 8. List the contents of the register in Fig. 9-5 immediately after each of the eight clock pulses (start with pulse t_1) (A = left bit, C = right bit).

- 10. Refer to Fig. 9-5. The parallel-load inputs are _____ (asynchronous, synchronous) on this shift register.
- 11. Refer to Table 9-2. The shift register is in the clear mode during what two lines on the table?
- 12. Refer to Table 9-2. The shift register is in the parallel-load mode during what two lines on the table?


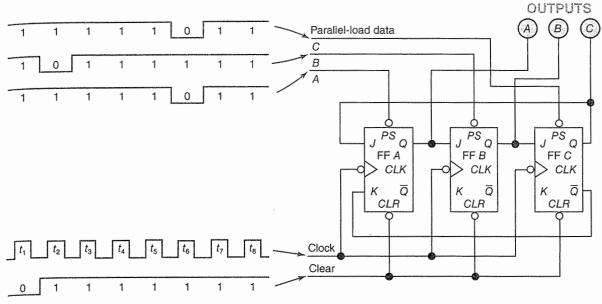


Fig. 9-5 A shift register problem for test items 6 through 10.

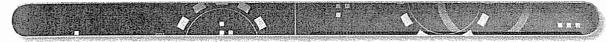

9-3 A Universal Shift Register

When reviewing data manuals, you will see that manufacturers produce many shift registers in IC form. In this section, one such IC shift register will be studied: the 74194 4-bit bidirectional universal shift register.

The 74194 IC is a very adaptable shift register and has most of the features we have seen so far in one IC package. A 74194 IC register can shift right or left. It can be loaded serially or in parallel. Several 4-bit 74194 IC registers can be cascaded to make an 8-bit or longer shift register. And this register can be made to recirculate data.

Read the description of the 74194 shift register in Fig. 9-6(a) for a good overview of what this shift register can do.

A logic diagram of the 74194 shift register is reproduced in Fig. 9-6(b). Because it is a 4-bit register, the circuit contains four flip-flops. Extra gating circuitry is needed for the many features of this universal shift register. The pin configuration in Fig. 9-6(c) will help you determine the labeling of each input and output. Of course, the pin diagram is also a must when actually wiring a 74194 IC.

The truth table and waveform diagrams in Fig. 9-6(d) and (e) are very helpful in determining exactly how the 74194 IC register works because they illustrate the clear, load, shift-right, shift-left, and inhibit modes of operation. When you use the 74194 universal shift register, you will have occasion to look quite carefully at the truth table and waveform diagrams.

74194 4-bit bidirectional universal shift register

-\\- Self-Test

Answer the following questions.

- 13. List the five modes of operation for the 74194 universal shift register IC.
- 14. Refer to Fig. 9-6. If both mode control inputs (S_0, S_1) to the 74194 are HIGH, the unit is in the _____ mode.
- 15. Refer to Fig. 9-6. If both mode control

inputs (S_0, S_1) to	the 74194 IC are LOW,
the unit is in the	mode.

16. Refer to Fig. 9-6. Shift right on the 74194 IC is accomplished when S_0 is ______ (HIGH, LOW) and S_1 is _____ (HIGH, LOW) and when the clock pulse goes from ______ to _____.



This bidirectional shift register is designed to incorporate virtually all of the features a system designer may want in a shift register. The circuit contains 45 equivalent gates and features parallel inputs, parallel outputs, right-shift serial inputs, operating-mode-control inputs, and a direct overriding clear line. The register has distinct modes of operating, namely:


Parallel (broadside) load Shift right (in the direction Q_A toward Q_D) Shift left (in the direction Q_D toward Q_A) Inhibit clock (do nothing)


Synchronous parallel loading is accomplished by applying the four bits of data and taking both mode control inputs, S_0 and S_1 , high. The data are loaded into the associated flip-flops and appear at the outputs after the positive transition of the clock input. During loading, serial data flow is inhibited.


Shift right is accomplished synchronously with the rising edge of the clock pulse when S_0 is high and S_1 is low. Serial data for this mode are entered at the shift-right data input. When S_0 is low and S_1 is high, data shifts left synchronously and new data are entered at the shift-left serial input.

Clocking of the flip-flop is inhibited when both mode control inputs are low. The mode of the S54194/N74194 should be changed only while the clock input is high.

(a) Description

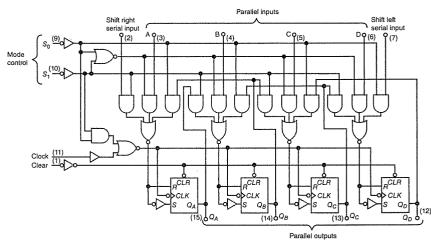

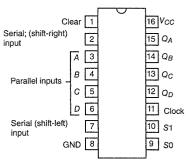

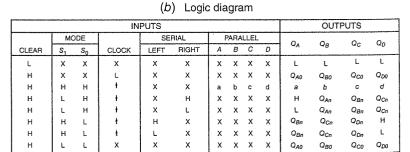

(c) Pin configuration

(d) Function table

- H = high level (steady state)
- L = low level (steady state)
- X = irrelevant (any input, including transitions)
- transition from low to high level
- a,b,c,d, = the level of steady state input at inputs A,B,C, or D, respectively
- $Q_{AO}, Q_{BO}, Q_{CO}, Q_{DO}$ = the level of Q_A, Q_B, Q_C, Q_D , respectively, before the indicated steady standard input conditions were established
- Q_{An}, Q_{Bn}, Q_{Cn}, Q_{Dn} = the level of Q_A, Q_B, Q_C, Q_D, respectively before the most recent ↑ transition of the clock

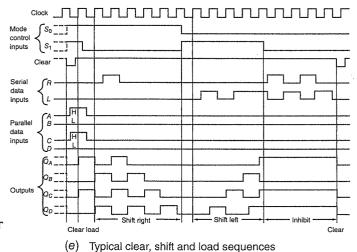


Fig. 9-6 A 4-bit TTL universal shift register (74194). (a) Description. (b) Logic diagram. (c) Pin configuration. (d) Function (truth) table. (e) Waveforms.

74194 shift register

9-4 Using the 74194 IC Shift Register

In this section we shall use the 74194 universal shift register in several ways. Figure 9-7(a) and (b) shows the 74194 IC being used as serial-load registers. A serial-load shift-right register is shown in Fig. 9-7(a). This register operates exactly like the serial shift register in Fig. 9-2. Table 9-1 could also be used to chart the performance of this new shift register. Notice that the mode control inputs (S_0, S_1) must be in the positions shown for the 74194 IC to operate in its shift-right mode. Shifting to the right is


defined by the manufacturer as shifting from Q_A to Q_D . The register in Fig. 9-7(a) shifts data to the right, and as they leave Q_D the data are lost.

The 74194 IC circuit has been revised slightly in Fig. 9-7(b). The shift-left serial input is used, and the mode control inputs have been changed. This register enters data at $D(Q_D)$ and shifts them toward $A(Q_A)$ with each pulse of the clock. This register is a serial-load shift-left register.

In Fig. 9-8 the 74194 IC is wired as a parallel-load shift-right/left register. With a single clock pulse, the data from the parallel load

Serial load shiftright register

Mode control inputs

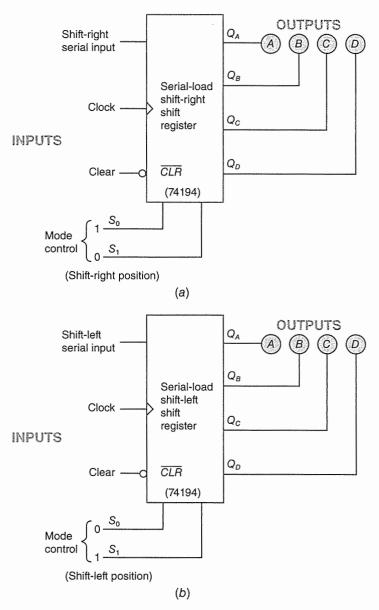

Serial-load shiftleft register

Fig. 9-7 (a) A 74194 IC wired as a 4-bit serial-load shift-right register. (b) A 74194 IC wired as a 4-bit serial-load shift-left register.

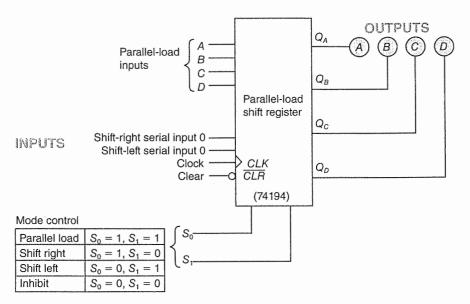


Fig. 9-8 A 74194 IC wired as a parallel load shift-right/left register.

inputs A, B, C, and D appear on the display. The loading happens only when the mode controls (S_0, S_1) are set at 1, as shown. The mode control can then be changed to one of the three types of operations: shift right, shift left, or inhibit. The shift-right and shift-left serial inputs both are connected to 0 to feed in 0s to the register in the shift-right or shift-left mode of operation. With the mode control in the inhibit position $(S_0 = 0, S_1)$

 S_1 = 0), the data do not shift right or left but stay in position in the register. When using the 74194 IC, you must remember the mode control inputs because they control the operation of the entire register. The \overline{CLR} input clears the register to 0000 when enabled by a 0. The asynchronous \overline{CLR} input overrides all other inputs.

Two 74194 IC shift registers are connected in Fig. 9-9 to form an 8-bit parallel-load

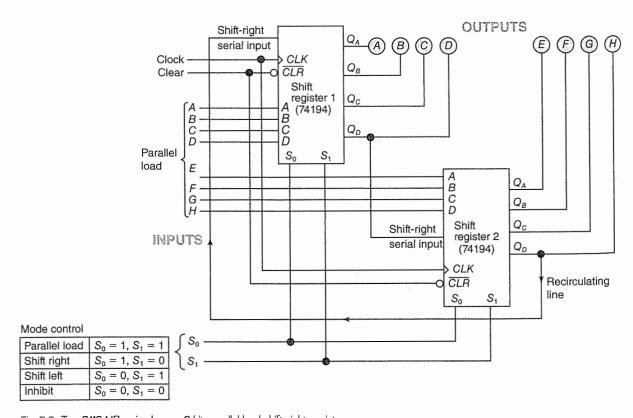


Fig. 9-9 Two 74194 ICs wired as an 8-bit parallel load shift-right register.

8-bit parallel-load shift-right register

shift-right register. The \overline{CLR} input clears the outputs to 0000 0000. The parallel-load inputs A to H allow entry of all 8 bits of data on a single clock pulse (mode control: $S_0=1$, $S_1=1$). With the mode control in the shift-right position ($S_0=1$, $S_1=0$), the register shifts right for each clock pulse. Notice that a recirculating line has been placed from output H (output Q_D of register 2) back to the shift-right serial input of shift register 1. Data that normally would be lost out of output H are recirculated back to position A in the register. Both inputs S_0 and S_1 at 0 will inhibit data shifting in the shift register.

As you have just seen, the 74194 IC 4-bit bidirectional universal shift register is very

useful. The circuits in this section are some examples of how the 74194 IC can be used. Remember that all shift registers use as their basis the memory characteristic of a flip-flop. Shift registers often are used as temporary memories. Shift registers also can be used to convert serial data to parallel data or parallel data to serial data. And shift registers can be used to delay information (delay lines). Shift registers are also used in some arithmetic circuits. Microprocessors and microprocessor-based systems make extensive use of registers similar to the ones used in this chapter. Counterparts to the 74194 are the 74S194, 74LS194A, 74F194, and 74HC194 ICs.

W

Self-Test

Supply the missing word or words in each statement.

- 17. The 74194 IC is in the parallel-load mode when both mode control inputs (S_0, S_1) are _____ (HIGH, LOW). The four bits of data at the parallel-load inputs are loaded into the registers by applying _____ [number] clock pulse(s) to the CLK input.
- 18. If the mode control inputs (S_0, S_1) to the 74194 IC are both LOW, the shift register is in the _____ mode.
- 19. For the 74194 IC to shift right, the mode controls are $S_0 =$ and $S_1 =$

- and the serial data enter the input.
- 20. Refer to Fig. 9-8. If $S_0 = 1$, $S_1 = 1$, shiftleft serial input = 1, and clear input = 0, then the outputs are ______.
- 21. Refer to Fig. 9-6. The 74194 IC is triggered on the _____ (H-to-L, L-to-H) transition of the clock pulse.
- 22. Refer to Fig. 9-6. An active ______ (clear, shift-left serial) input overrides all other inputs and resets the register outputs to 0000 on the 74194 IC.
- 23. Refer to Fig. 9-6. To ______ (shift left, shift right) means to shift data from Q_D toward the Q_A output on the 74194 IC.





9-5 An 8-Bit CMOS Shift Register

This section will detail the operation of one of many CMOS shift registers available from manufacturers. A manufacturer furnished the technical information in Fig. 9-10 on the 74HC164 8-bit serial in–parallel out shift register.


The 74HC164 CMOS IC is an 8-bit edge-triggered register with serial data entry. Parallel outputs are available from each internal D flip-flop. The detailed logic diagram in Fig. 9-10(a)

shows the use of eight D flip-flops with parallel data outputs (Q_0 to Q_7).

The 74HC164 IC featured in Fig. 9-10 is described as having a serial input. Data are entered serially through one of two inputs (D_{sa} and D_{sb}). Observe on Fig. 9-10(a) that the data inputs (D_{sa} and D_{sb}) are ANDed together. The data inputs may be tied together as a single input or one may be tied HIGH using the other for data entry.

The master reset input (\overline{MR}) to the 74HC164 IC is shown at the lower left in Fig. 9-10(a).

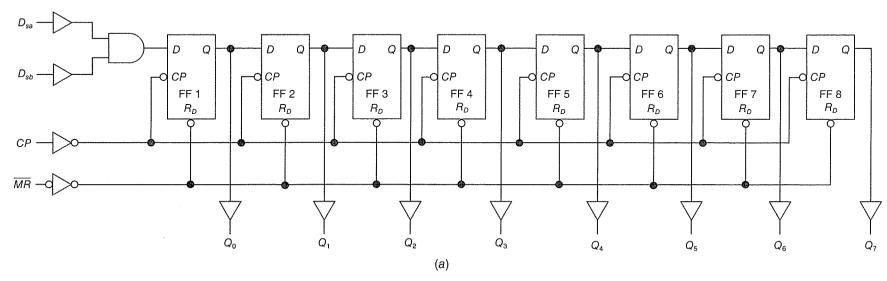74HC164 8-bit serial in–parallel out shift register 74HC164 8-bit shift register IC




Truth table-74HC164 Shift Register

Operating modes		INPUTS				OUTPUTS	
Operating modes	MR	CP	D_{sa}	D_{sb}	Q_0	Q ₁ -Q ₇	
Reset (clear)	L	Х	Х	Х	L	L-L	
Shift right	H H H	† † †	l h h	l h h	コココエ	q₀–q ₆ q₀–q ₆ q₀–q ₆ q₀–q ₆	

- H = HIGH voltage level
- h = HIGH voltage level one set-up time prior to the LOWto-HIGH clock transition
- L = LOW voltage level
- LOW voltage level one set-up time prior to the LOWto-HIGH clock transition
- q = lowercase letters indicate the state of the referenced input one set-up time prior to the LOW-to-HIGH clock transition
- ↑ = LOW-to-HIGH clock transition

(b)

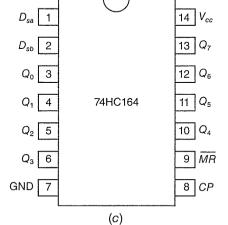

PIN DESCRIPTION

PIN NO.	SYMBOL	NAME AND FUNCTION		
1,2	D_{sa} , D_{sb}	Data inputs		
3, 4, 5, 6, 10, 11, 12, 13	Q_0 to Q_7	Outputs		
7	GND	Ground (0 V)		
8	CP	Clock input (Low-to-HIGH, edge-triggered)		
9	MR	Master reset input (active LOW)		
14	V _{cc}	Positive supply voltage		
(d)				

Fig. 9-10 An 8-bit CMDS serial in-parallel out shift register (74HC164). (a) Detailed logic diagram. (b) Truth table. (c) Pin diagram. (d) Pin descriptions.

It is an active LOW input. The truth table in Fig. 9-10(b) shows that the \overline{MR} input overrides all other inputs and clears all flip-flops to 0 when activated.

The 74HC164 IC shifts data one place to the right on each LOW-to-HIGH transition of the clock (*CP*) input. The clock pulse also enters

data from the ANDed data inputs (D_{sa} and D_{sb}) into output Q_0 of FF 1 [see Fig. 9-10(a)].

For your reference, a pin diagram for the 74HC164 shift register IC is reproduced in Fig. 9-10(c). The helpful table in Fig. 9-10(d) describes the function of each pin on this CMOS IC.

ABOUT ELECTRONICS



Vision Enhancement

The NOMAD Personal Display System is a "see-through" high-resolution head-worn
display that allows mobile viewing of electronic information in all lighting conditions. The
Nomad system superimposes high contrast images on the user's field of vision—from
schematics, maintenance records, or manuals to situational awareness data to interactive training manuals. A crew can now access information while on scaffolding or working
in other difficult positions, all the time, working with their hands while viewing critical
information.



**//**/

Self-Test

Answer the following questions.

- 24. The 74HC164 IC's master reset pin is an active _____ (HIGH, LOW) input.
- 25. The clock input to the 74HC164 IC responds to a(n) _____ (H-to-L, L-to-H) transition of the clock pulse.
- 26. Refer to Fig. 9-11. List the shift register's mode of operation for each clock pulse $(t_1 \text{ through } t_6)$.
- 27. Refer to Fig. 9-11. List the 8-bit output $(Q_0 \text{ bit on left, } Q_7 \text{ bit on right)}$ after each of the six clock pulses.

- 28. The 74HC164 is a _____ (CMOS, TTL) shift register IC.
- 29. The 74HC164 is a(n) _____ (4-bit, 8-bit) ____ (parallel-load, serial-load) shift register IC.
- 30. On the 74HC164 IC, the serial data inputs $(D_{sa} \text{ and } D_{sb})$ are _____ (ANDed, ORed) together inside the chip to form the serial data input.

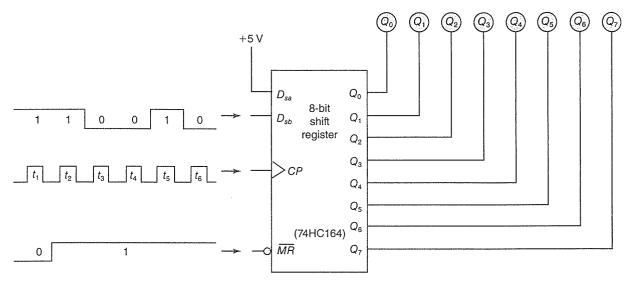


Fig. 9-11 Shift register problem for test items 26 and 27.



9-6 Using Shift Registers: Digital Roulette

The roulette wheel holds great fascination for people of all ages. Variations are used in game shows and in gaming. This section explores an

electronic version of the mechanical roulette

wheel. Digital roulette is a favorite project for many students.

A block diagram of a *digital roulette wheel* is sketched in Fig. 9-12. This simple roulette wheel design uses only eight number markers. The number markers are LEDs in this electronic version of roulette. Only a single LED (number

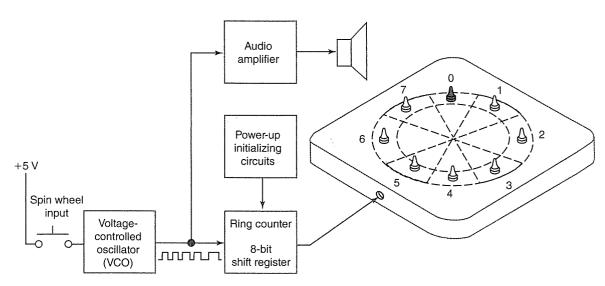


Fig. 9-12 Block diagram for simplified electronic digital roulette wheel.

Digital roulette wheel

marker) must light at a time. A *ring counter* is a circuit that will cause the LEDs to light, one at a time, in sequence. A ring counter is simply a shift register with some added circuitry.

When turning on the power, the shift register in Fig. 9-12 must first be cleared to all zeros. Note that the system ON-OFF switch is not represented in the block diagram. Second, when the "spin wheel" switch is pressed, a single HIGH must be loaded into position 0 on the display lighting LED 0. The voltage-controlled oscillator (VCO) emits a string of clock pulses that gradually decrease in frequency and stops. The clock pulses are directed to the ring counter (shift register) and the audio amplifier sections of the digital roulette game. Each clock pulse entering the ring counter will shift the single light around the roulette wheel. The lighting sequence should be 0, 1, 2, 3, 4, 5, 6, 7, 0, 1, and so forth, until the VCO stops emitting clock pulses. When clock pulses stop, a single LED should remain lit on the roulette wheel in some random position.

The VCO in Fig. 9-12 also sends clock pulses to the audio amplifier section. Each clock pulse is amplified to sound like the click of a roulette wheel. The frequency gradually decreases and stops, simulating a mechanical wheel coasting to a stop.

The ring counter block of the digital roulette game is detailed in Fig. 9-13(a). Notice that the ring counter makes use of the 74HC164 8-bit serial in-parallel out shift register IC studied earlier. When power is turned on, the circuits in the power-up initializing block clear all outputs to zero (all LEDs are off). Upon pressing the "spin wheel" input switch, the first pulse loads a single HIGH into the shift register. This situation is illustrated in Fig. 9-13(a). The clock pulses that follow move the single light across the display. This is illustrated in Fig. 9-13(b). Notice that on each L-to-H transition of the clock, the single HIGH in the 74HC164 8-bit register shifts one position to the right. When the HIGH reaches output Q_7 [after clock pulse 8 in Fig. 9-13(b)], a recirculating line (feedback) is run back to the data inputs to transfer the HIGH back to the left LED (output Q_0). In the example in Fig. 9-13(b), the switch is opened after the twelfth pulse. This stops the light at Q_3 . This is the "winning number" on the roulette wheel for this spin.

The 74HC164 8-bit shift register IC is wired as a ring counter in Fig. 9-13(a). The circuit has the two characteristics that make it a ring counter. First, it has feedback from the last flip-flop (Q_7) to the first FF (Q_0) . Second, it is loaded with a given pattern of 1s and 0s, and these recirculate as long as clock pulses reach the CP input of the shift register. In this case, a single 1 is loaded into the shift register and is recirculated.

In summary, the circuit in Fig. 9-13(a) is a very simple *electronic roulette wheel*. Pressing the spin wheel input causes the single light to be circulated through the LEDs. When the switch opens, the shifting stops.

For added appeal, the simple digital roulette circuit in Fig. 9-13 can be changed by adding a clock that will continue to run for a time after the push button is released. Sound could also be added for a more realistic simulation. Figure 9-14 adds both features to the digital roulette wheel.

The versatile 555 timer IC is wired as a VCO in Fig. 9-14. Pressing the spin wheel input switch turns on transistor Q_1 . The 555 timer operates as a free-running MV. This square-wave output from the VCO drives both the clock input (CP) of the *ring counter* and the *audio amplifier*. Pulses from the VCO alternately turn transistor Q_2 on and off, clicking the speaker.

When the spin wheel input switch is opened, the 47- μ F capacitor holds a positive charge for a time, which is applied to the base (B) of transistor Q_1 . This keeps the transistor turned on for several seconds before the capacitor becomes discharged. As the 47- μ F capacitor discharges, the voltage at the base of Q_1 becomes less and the resistance of the transistor (from emitter to collector) increases. This decreases the frequency of the oscillator. This causes the shifting light to slow down. The clicking from the speaker also decreases in frequency. This simulates the slowing of a mechanical roulette wheel.

To review, the *power-up initializing circuitry* block in Fig. 9-14 must first clear the shift register and then set only the first output HIGH. These two circuits have been added to the digital roulette wheel in Fig. 9-15.

An automatic clear circuit has been added to the roulette wheel in Fig. 9-15. It consists of the resistor-capacitor combination $(R_7 \text{ and } C_4)$.

Ring counter 74HC164 B-bit shift register IC

Voltage-controlled oscillator (VCD)

Audia amplifier

Power-up initializing circuitry

Recirculating line (feedback)

Automatic clear circuit

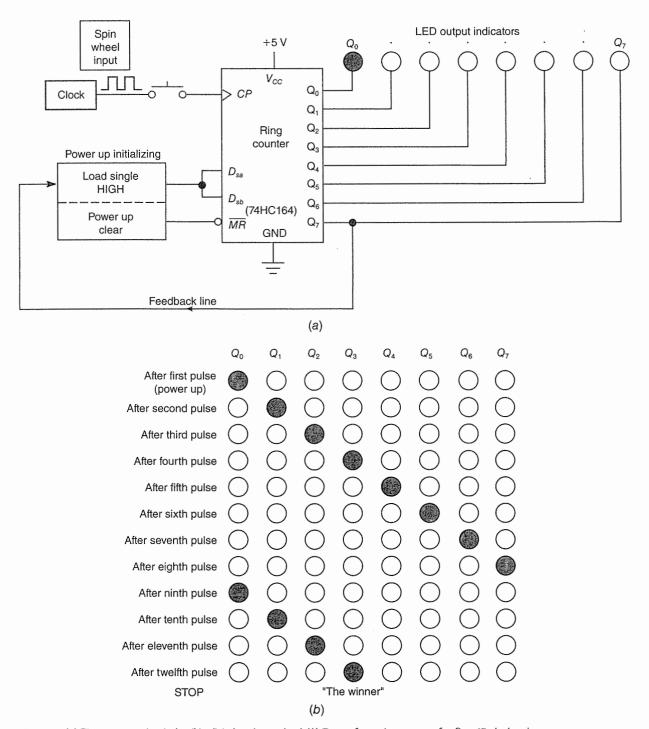


Fig. 9-13 (a) Ring counter circuit detail in digital roulette wheel. (b) Output from ring counter for first 12 clock pulses.

When power is turned on, the voltage at the top of the 0.01- μ F capacitor starts LOW and increases quickly to a HIGH as it charges through resistor R_7 . The master reset (\overline{MR}) input to the 74HC164 register is held LOW just long enough for the output of the shift register to be cleared to 00000000. At this point all the LEDs are off.

The circuit that loads a single 1 into the ring counter consists of the four NAND gates and

two resistors (R_5 and R_6). The NAND gates are wired as an R-S latch. The two resistors (R_5 and R_6) force the output of the NAND gate (IC_a) HIGH when the power is first turned on. This HIGH is applied to the data inputs (D_{sa} and D_{sb}) of the ring counter. On the very first L-to-H transition of the clock, the HIGH at the data inputs is transferred to output Q_0 of the 74HC164 IC. Immediately this HIGH is

Ring counter

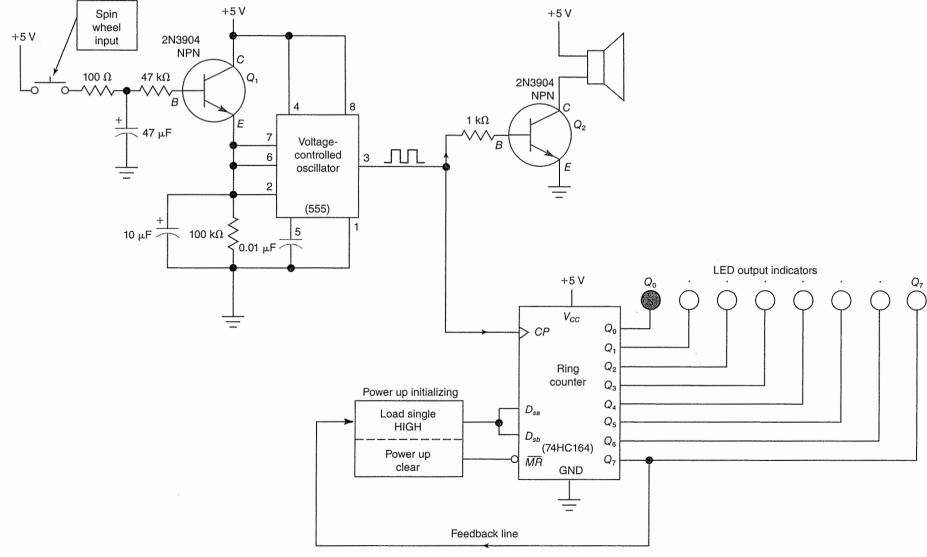


Fig. 9-14 Voltage-controlled oscillator circuit detail in digital roulette wheel.

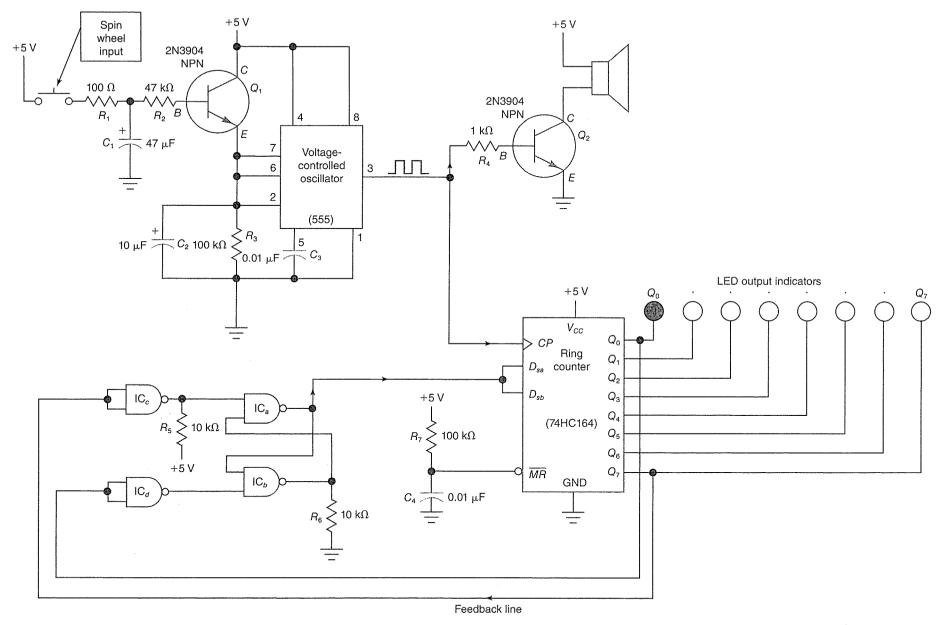


Fig. 9-75 Completed digital roulette wheel. Power-up initializing circuits have been added.

fed back to the input of IC_d and resets the latch so that a LOW now appears at the data inputs $(D_{sa}$ and $D_{sb})$. Only a single HIGH was loaded into the ring counter. Repeated clock pulses move the HIGH (light) across the display until

 Q_7 of the ring counter goes HIGH. This HIGH is fed back to the input of IC_c setting the latch so that a 1 appears at the data inputs of the ring counter. The single HIGH has been recirculated back to Q_0 .




Self-Test

Answer the following questions.

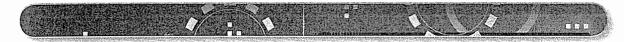- 31. Refer to Fig. 9-15. Components R_4 , speaker, and Q_2 form the _____ block of the digital roulette wheel circuit.
- 32. Refer to Fig. 9-15. The 74HCl64 8-bit shift register is wired as a(n) ______ in this circuit.
- 33. Refer to Fig. 9-15. What components cause the 74HCl64 IC to reset all

- outputs to 0 when the power is first turned on?
- 34. Refer to Fig. 9-15. Clock pulses are fed to the ring counter by the output of the 555 timer IC wired as a(n) _____.
- 35. Refer to Fig. 9-15. The four NAND gates used for loading a single 1 in the ring counter are wired as a(n) _____ circuit.



9-7 Troubleshooting a Simple Shift Register

Consider the faulty serial-load shift-right register drawn in Fig. 9-16. Four D flip-flops (two 7474 ICs) have been wired together to form this 4-bit register.

After checking for obvious mechanical and temperature problems, the student or technician runs the following sequence of tests to observe the problem:

- Action: Clear input to 0 and back to 1.
 Result: Output indicators = 0000 (not lit).
 Conclusion: Clear function operating correctly.
- 2. Action: Data input = 1.
 Single pulse to CLK of flip-flops from logic pulser.

Result: Output indicators = 1000.

Conclusion: FF A loading 1s properly.

3. Action: Data input = 1.
Single pulse to CLK of flip-flops from logic pulser.

Result: Output indicators = 1100.

Conclusion: FF A and FF B loading 1s correctly.

4. Action: Data input = 1.
Single pulse to CLK of flip-flops from logic pulser.

Result: Output indicators = 1110.

Conclusion: FF A, FF B, and FF C loading 1s correctly.

5. Action: Data input = 1.
Single pulse to CLK of flip-flops from logic pulser.

Result: Output indicators = 1110.

Conclusion: Suspect problem near or in FF D since it did not load a HIGH properly.

6. Action: Logic probe at D input to FF D to see if D = 1.

Result: D = 1 on FF D.

Conclusion: HIGH data at D of FF D is correct.


7. Action: One pulse to CLK (pin 11) of FF D from logic pulser.

Result: Output indicator remains at 1110.

Conclusion: Data not being transferred from input D of FF D to output Q on a clock pulse.

8. Action: Logic probe to output Q of FF D (pin 9).

Troubleshooting

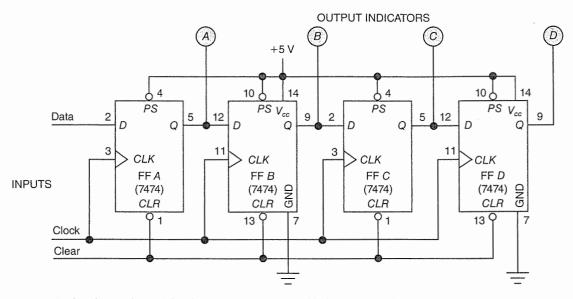

Faulty 4-bit serialload shift-right register

Fig. 9-16 Faulty 4-bit serial load shift-right register used as a troubleshooting example.

Result: Neither HIGH nor LOW indicator lights on logic probe.

Conclusion: Output Q (pin 9) of FF D floating between HIGH and LOW. Probably a faulty FF D in second 7474 IC.

9. *Action:* Remove and replace second 7474 IC (FF *C* and FF *D*) with exact replacement.

Action: Retest circuit, starting at step 1.
 Result: All flip-flops load 1s and 0s.
 Conclusion: Shift register circuit is now operating properly.

According to the sequence of tests, the Q output of FF D seemed to be stuck LOW, while it was actually floating between LOW and

HIGH. This fact made our conclusion in step 1 incorrect. This fault was caused by an open circuit within the second 7474 IC itself. Again, the technician's knowledge of how the circuit operates along with observations helped locate the fault. The logic probe and digital logic pulser aided the technician in making observations.

Sometimes the technician is not exactly sure of the appropriate logic level. In a circuit with redundant circuitry (circuits repeated over and over), the technician could go back to FF A and FF B and compare these readings with those on FF C and FF D. Digital circuits have much redundant circuitry, and at times this technique is helpful in troubleshooting.

Redundant circuitry


-√M- Self-Test

Answer the following questions.

- 36. Refer to Fig. 9-16. Describe the observed problem in this circuit.
- 37. Refer to Fig. 9-16. What is wrong with this circuit?
- 38. Refer to Fig. 9-16. How can the fault in this circuit be repaired?
- 39. What test equipment can be used to troubleshoot this shift register circuit?



Chapter 9 Summary and Review

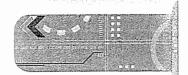

Summary

- 1. Register is a generic name for a group of memory cells (such as flip-flops) that are considered as a single unit. A few other names used for registers are buffer registers, shift registers, and latches.
- 2. Flip-flops are wired together to form shift registers.
- 3. A shift register has both a memory and a shift characteristic.
- 4. A serial-load shift register is one that permits only 1 bit of data to be entered per clock pulse.
- 5. A parallel-load shift register is one that permits all data bits to be entered at one time (one clock pulse).

- 6. A recirculating register feeds output data back into the input.
- 7. Shift registers can be designed to shift either left or right.
- 8. Manufacturers produce many adaptable universal shift registers.
- Shift registers are widely used as temporary memories and for shifting data. They also have other uses in digital electronic systems.
- 10. A ring counter is a shift register that (1) has a recirculating line and (2) is loaded with a pattern of 0s and 1s, which is repeated over and over as the unit is clocked.

Chapter Review Questions

Answer the following questions.

- 9-1. Draw a logic symbol diagram of a 5-bit serial-load shift-right register. Use five D flip-flops. Label inputs data, *CLK*, and *CLR*. Label outputs *A*, *B*, *C*, *D*, and *E*. The circuit will be similar to the one in Fig. 9-2.
- 9-2. Explain how you would clear to 00000 the 5-bit register you drew in question 9-1.
- 9-3. After clearing the 5-bit register, explain how you would enter (load) 10000 into the register you drew in question 9-1.
- 9-4. After clearing the 5-bit register, explain how you would enter (load) 00111 into the register you drew in question 9-1.
- 9-5. Refer to the register you drew in question 9-1. List the contents of the register after each clock pulse shown in \mathbf{b} to \mathbf{e} (assume data input = 0).
 - a. Original output = 01001 (A = 0, B = 1, C = 0, D = 0, E = 1)
 - b. After one clock pulse =
 - c. After two clock pulses =
 - d. After three clock pulses =
 - e. After four clock pulses =

9-6.	Refer to Fig. 9-8. The parallel-load register
	using the 74194 IC needs(no
	one, three, four) clock pulse(s) to load data
	from the parallel-load inputs.
0.7	A (serial perallel) load shift

- 9-7. A ______ (serial, parallel)-load shift register is the simplest circuit to wire.
- 9-8. A ______ (serial, parallel)-load shift register is the easiest to load.
- 9-9. Refer to Fig. 9-6 for questions **a** to **i** on the 74194 IC shift register:
 - a. How many bits of information can this register hold?
 - b. List the four modes of operation for this register.
 - c. What is the purpose of the mode control inputs (S_0, S_1) ?
 - d. The _____ input overrides all other inputs on this register.
 - e. What type are the flip-flops, and how many are used in this shift register?
 - f. The register shifts on the _____ (negative-, positive-) going edge of the clock pulse.

Chapter Review Questions...continued

- g. What does the inhibit mode of operation mean?
- h. By definition, to shift left means to shift data from _____ to ____ (use letters).
- i. This register can be loaded _____ (serially, in parallel, either serially or in parallel).
- 9-10. Refer to Fig. 9-17. List the 74194 shift register's mode of operation during each of the eight clock pulses. Use as answers "clear," "inhibit," "shift right," "shift left," and "parallel load."
- 9-11. Refer to Fig. 9-10 for questions **a** to **f** on the 74HC164 shift register.
 - a. How many bits of information can this register store?
 - b. This shift register is a ______ (CMOS, TTL) IC.
 - c. This is a _____ (parallel, serial)-load shift register.
 - d. The master reset is an active _____ (HIGH, LOW) input.
 - e. The register shifts data on the _____ (H-to-L, L-to-H) transition of the clock pulse.

- f. The register has two data inputs, which are _____ (ANDed, ORed) together for loading data into FF 1.
- 9-12. Refer to Fig. 9-18. List the contents of the register during each of the eight clock pulses $(Q_0 = \text{left bit}, Q_7 = \text{right bit}).$
- 9-13. Refer to Fig. 9-12. The device that generates clock pulses in the digital roulette circuit is called a(n) ______.
- 9-14. Refer to Fig. 9-13(a). The 74HC164 shift register is wired as a(n) ______ in this circuit
- 9-15. Refer to Fig. 9-15. The frequency of the VCO decreases as the voltage at the top of capacitor (C_1, C_2, C_4) decreases.
- 9-16. Refer to Fig. 9-15. What is the purpose of resistor R_7 and capacitor C_4 ?
- 9-17. Refer to Fig. 9-15. Resistors R_5 and R_6 force the output of IC_a (HIGH, LOW) when the power is first turned on.
- 9-18. Refer to Fig. 9-15. If only Q_0 of the ring counter is HIGH (as shown), the R-S latch forces the output of IC_a (HIGH, LOW).

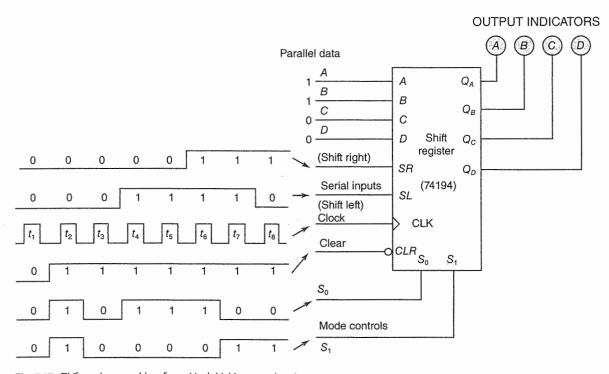


Fig. 9-17 Shift register problem for critical thinking question 4.

Chapter Review Questions...continued

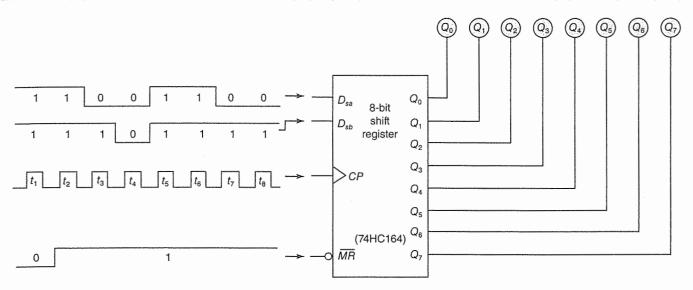


Fig. 9-18 Shift register problem for review question 12.

Critical Thinking Questions

- 9-1. The shift register in Fig. 9-4(*b*) needs
 _____ (no, one, four) clock pulse(s)
 to load data from the parallel data inputs.
- 9-2. The shift register in Fig. 9-4(b) can only load _____ (0S, 1s) using the parallel-load inputs.
- 9-3. List several uses of shift registers in digital systems.
- 9-4. List the contents of the register in Fig. 9-17 after each of the eight clock pulses (A = left bit, D = right bit).
- 9-5. Describe in general terms the nature of the output from the VCO in Fig. 9-12.
- 9-6. Refer to Fig. 9-4. Describe the procedure you would follow when loading the data 1101 into this 4-bit parallel-load shift register.

 Hint: Remember to clear the register to 0000 before activating the asynchronous parallel inputs.
- 9-7. Refer to Fig. 9-8. Parallel loading of data is a(n)
 ______ (asynchronous, synchronous)
 operation when using the 74194 shift register IC.

- 9-8. A ring counter is classified as a type of _____ (shift register, VCO).
- 9-9. Draw a block diagram of a 16-bit electronic roulette wheel with VCO, audio amplifier, power-up initializing circuits, and ring counter blocks. It should look something like the 8-bit electronic roulette wheel in Fig. 9-12.
- 9-10. At the option of your instructor, use Electronics Workbench or Multisim circuit simulation software to (1) draw the 8-bit serial-load shift register shown in Fig. 9-19, (2) test the operation of the shift register, and (3) save the circuit and show your instructor your design.
- 9-11. At the option of your instructor, use Electronics Workbench or Multisim circuit simulation software to (1) add a recirculating line to your 8-bit shift register you designed in question 9-10 (*Hint*: OR recirculating line and data input), (2) test the operation of the shift register with recirculating feature, and (3) save the circuit and show your instructor your design.

Critical Thinking Questions...continued

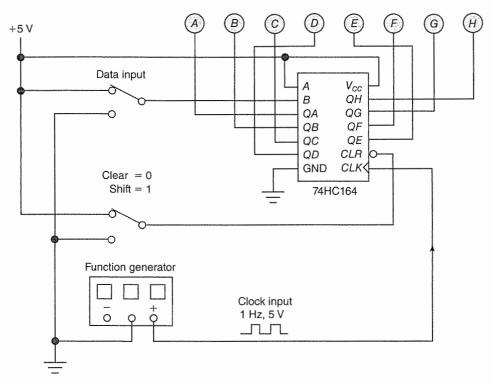


Fig. 9-19 EWB or multisim circuit problem.



Answers to Self-Tests

- 1. serial
- 2. after pulse $t_1 = 000$
 - after pulse $t_2 = 100$
 - after pulse $t_3 = 010$
 - after pulse $t_4 = 001$
 - after pulse $t_5 = 000$
 - after pulse $t_6 = 100$
- 3. single bit
- 4. LOW
- 5. HIGH, L-to-H
- 6. parallel
- 7. pulse $t_1 = \text{clear}$
 - pulse t_2 = parallel load
 - pulse t_3 = shift right
 - pulse t_4 = shift right
 - pulse t_5 = shift right
 - pulse t_6 = parallel load
 - pulse t_7 = shift right
 - pulse t_8 = shift right

- 8. after pulse $t_1 = 000$
 - after pulse $t_2 = 010$
 - after pulse $t_3 = 001$
 - after pulse $t_4 = 100$
 - after pulse $t_5 = 010$
 - after pulse $t_6 = 101$

 - after pulse $t_7 = 110$
 - after pulse $t_8 = 011$
- 9. recirculating
- 10. asynchronous
- 11. lines 2 and 9
- 12. lines 3 and 10
- 13. 1. clear
 - 2. parallel load
 - 3. shift right
 - 4. shift left
 - 5. inhibit (do nothing)
- 14. parallel load
- 15. inhibit

- 16. HIGH, LOW, LOW, HIGH
- 17. HIGH, one
- 18. inhibit
- 19. 1, 0, shift right serial
- 20. 0000 (cleared)
- 21. L-to-H
- 22. clear
- 23. shift left
- 24. LOW
- 25. L-to-H or LOW-to-HIGH
- 26. during pulse t_1 = reset during pulse t_2 = shift right during pulse t_3 = shift right during pulse t_4 = shift right during pulse t_5 = shift right
- 27. during pulse $t_1 = 00000000$ during pulse $t_2 = 10000000$

during pulse t_6 = shift right

- during pulse $t_3 = 01000000$ during pulse $t_4 = 00100000$ during pulse $t_5 = 10010000$ during pulse $t_6 = 01001000$
- 28. CMOS
- 29. 8-bit, serial-load
- 30. ANDed
- 31. audio amplifier
- 32. ring counter
- 33. R_7 and C_4
- 34. voltage-controlled oscillator or VCO
- 35. R-S latch or latch
- 36. will not shift a HIGH into the D position
- 37. Output *Q* (pin 9) of FF *D* floating; 7474 IC that contains FF *C* and FF *D* faulty
- 38. A new 7474 IC should be inserted, replacing FF *C* and FF *D*.
- 39. logic pulser, logic probe





Arithmetic Circuits

Learning Outcomes

This chapter will help you to:

- 10-1 Solve binary addition problems.
- **10-2** *Predict* the outputs from a half-adder circuit.
- 10-3 Predict the outputs from a full-adder circuit.
- **10-4** *Draw* a block-style logic diagram of 3-bit parallel adder and *predict* its operation.
- **10-5** Solve binary subtraction problems. Draw half-subtractor and full-subtractor circuits and predict their operation.
- **10-6** *Draw* a block-style logic diagram of 4-bit parallel adder/subtractor circuit and *predict* its operation.
- 10-7 Use the TTL 7483 IC (or CMOS 4008 IC) as a 4-bit adder and cascade two adder ICs to form an 8-bit binary adder circuit.

 Predict the operation of both 4-bit and 8-bit adder circuits.
- **10-8** Solve binary multiplication problems. Summarize binary multiplication using repeated addition. Solve binary multiplication problems using the add-and-shift method of calculating.
- 10-9 Explain the operation of a simple repeated addition-type multiplication circuit.
 Analyze the operation of an add-and-shift-type multiplier circuit.
- 10-10 Understand 2s complement numbers used by some digital circuits that handle signed numbers. Convert decimal and binary to 2s complement notation and 2s complement to decimal and binary numbers. Solve both addition and subtraction problems using 2s complement numbers.
- 10-11 Add and subtract signed numbers using 2s complement addition and subtraction. Predict the operation of a 4-bit adder/subtractor system using 2s complement numbers.
- **10-12** *Troubleshoot* a faulty full-adder circuit. *List* several hints that aid in successful troubleshooting.

the public's imagination has been captured by computers and modern-day calculators, probably because these machines perform arithmetic tasks with such fantastic speed and accuracy. This chapter deals with some logic circuits that can add and subtract. (Of course, the adding and subtracting is done in binary.) Regular logic gates will be wired together to form *adders* and *subtractors*. Basic adder and subtractor circuits are combinational logic circuits, but they are commonly used with various latches and registers to hold data.

In the central processing unit (CPU) of a computer, arithmetic is handled in a section commonly called the arithmetic-logic unit (ALU). This section within the CPU can usually add and subtract, multiply and divide, complement, compare, shift and rotate, increment and decrement, and perform logic operations such as AND, OR, and XOR. Many older microprocessors and several modern microcontrollers (a miniature microprocessor used mainly for control purposes) do not have multiply and divide commands in their instruction set.

Central processing unit (CPU) Arithmetic-logic unit (ALU)

Microcontroller

10-1 Binary Addition

Remember that in a binary number, such as 10101100, the leftmost digit is the *MSB* and the rightmost digit is the *LSB*. Also remember the place values given to the binary number is: 1s, 2s, 4s, 8s, 16s, 32s, 64s, and 128s.

You probably still recall learning your addition and subtraction tables when you were in elementary school. This is a difficult task in the decimal number system because there are so many combinations. This section deals with the simple task of adding numbers in binary. Because they have only Binary addition

MSB LSB

Fig. 10-1 (a) Binary addition tables. (b) Sample binary addition problems.

Binary addition tables

two digits (0 and 1), the binary addition tables are simple. Figure 10-1(a) shows the binary addition tables. Just as in the case of adding with decimals, the first three problems are easy. The next problem is 1 + 1. In decimal that would be 2. In binary a 2 is written as 10. Therefore, in binary 1 + 1 = 0, with a carry of 1 to the next most significant place value.

Figure 10-1(b) shows some examples of adding numbers in binary. The problems are also shown in decimal so that you can check your understanding of binary addition. The first problem is adding binary 101 to 10, which equals 111 (decimal 7). This problem is simple using the addition tables in Fig. 10-1(a). The second problem in Fig. 10-1(b) is adding binary 1010 to 11. Here you must notice that a 1 + 1 = 0 plus a carry from the 2s place to the 4s place, as shown in the diagram. The answer to this problem is 1101 (decimal 13). In the third problem in Fig. 10-1(b), the binary number 11010 is added to 1100. In the figure, note two carries with the solution as 100110 (decimal 38).

Another sample addition problem is shown in Fig. 10-2(a). The solution looks simple until we get to the 2s column and find 1+1+1 in binary. This equals 3 in decimal, which is 11 in binary. This one situation we left out of the first group of binary addition tables. Looking carefully at Fig. 10-2, you see that the 1+1+1 situation can arise in any column except the 1s column. So the binary addition table

in Fig. 10-1(a) is complete for the *1s column* only. The new short-form addition table in Fig. 10-2(b) adds the other possible combination of 1 + 1 + 1. The addition table in Fig. 10-2(b), then, is for all the place values (2s, 4s, 8s, 16s, and so on) except the 1s column.

To be an intelligent worker on digital equipment, you must master binary addition. Several practice problems are provided in the first test. You may want to check your answers with a calculator that will perform binary arithmetic.



Fig. 10-2 (a) Sample binary addition problem. (b) Short-form addition table.

Answer the following questions.

- What is the sum of binary 1010 + 0100? (Check your answer using decimal addition.)
- 2. What is the sum of binary 1010 + 0111?
- 3. What is the sum of binary 1111 + 1001?
- 4. What is the sum of binary 10011 + 0111?
- 5. What is the sum of binary 0110 0100 + 0011 0010? (Check your answer using decimal addition.)
- 6. What is the sum of binary 1010 0111 + 0011 0011? (Check your answer using decimal addition.)
- 7. What is the sum of binary 01111111 + 01111111? (Check your answer using decimal addition.)




Half adder

10-2 Half Adders

The addition table in Fig. 10-1(a) can be thought of as a truth table. The numbers being added are on the input side of the table. In Fig. 10-3(a),

Half-adder circuit

INPUTS		OUTPUTS		
В	A	Σ	Co	
0	0	0	0	
0	1	1	0	
1	0	1	0	
1	1	0	1	
Binary digits to be		Sum	Carry out	
adde	ed 	XOR	AND	

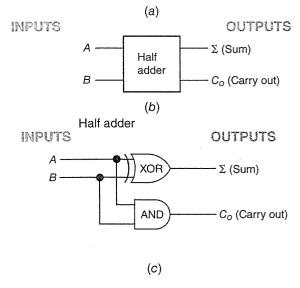

Full adder

Fig. 10-3 Half adder. (a) Truth table. (b) Block symbol. (c) Logic diagram.

these are the A and B input columns. The truth table needs two output columns, one column for the sum and one column for the carry. The sum column is labeled with the summation symbol Σ . The carry column is labeled with a C_o . The C_o stands for carry output or carry out. A convenient block symbol for the adder that performs the job of the truth table is shown in Fig. 10-3(b). This circuit is called a half-adder circuit. The half-adder circuit has two inputs (A, B) and two outputs, (Σ, C_o) .

Take a careful look at the half-adder truth table in Fig. 10-3(a). What is the Boolean expression needed for the C_o output? The Boolean expression is $A \cdot B = C_o$. You need a two-input AND gate to take care of output C_o .

Now what is the Boolean expression for the sum (Σ) output of the half adder in Fig. 10-3(a)? The Boolean expression is $\overline{A} \cdot B + A \cdot \overline{B} = \Sigma$. Two AND gates, two inverters, and one OR gate will do the job. If you look closely, you will notice that this pattern is also that of an XOR gate. The simplified Boolean expression is then $A \oplus B = \Sigma$. In other words, we find that only one 2-input XOR gate is needed to produce the sum output.

Using a two-input AND gate and a two-input XOR gate, a logic symbol diagram for a half adder is drawn in Fig. 10-3(c). The half-adder circuit adds only the LSB column (1s column) in a binary addition problem. A circuit called a *full adder* must be used for the 2s, 4s, 8s, and 16s, and higher places in binary addition.



Self-Test

Answer the following questions.

- 8. Draw a block diagram of a half adder. Label inputs A and B; label outputs Σ and C_o .
- 9. Draw a truth table for a half adder. Label the two inputs B and A. Label the two outputs Σ and C_a .
- 10. A half-adder circuit is used for adding only the _____ (1s, 2s, 4s, 8s) column of a binary addition problem.
- 11. Refer to Fig. 10-4. List the outputs from both the sum (Σ) and carry out (C_0)

terminals of the half-adder circuit for each input pulse $(t_1 \text{ to } t_4)$.

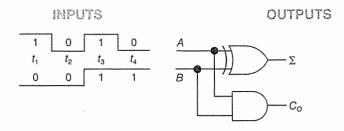


Fig. 10-4 Half-adder pulse-train problem for test question 11.




10-3 Full Adders

Figure 10-2(b) is the short form of the binary addition table, with the 1+1+1 situation shown. The truth table in Fig. 10-5(a) shows all the possible combinations, of A, B, and C_{in} (carry in). This truth table is for a full adder. Full adders are used for all binary place values except the 1s place. The full adder must be used when it is possible to have an extra carry input. A block diagram of a full adder is shown in Fig. 10-5(b). The full adder has three inputs: C_{in} , A, and B. These three inputs must be added to get the Σ and C_{o} outputs.

One of the easiest methods of forming the combinational logic for a full adder is diagrammed in Fig. 10-5(c); two half-adder circuits and an OR gate are used. The expression for this arrangement is $A \oplus B \oplus C = \Sigma$. The expression for the carry out is $A \cdot B + C_{in} \cdot (A \oplus B) = C_{O}$. The logic circuit in Fig. 10-6(a) is a full adder. This circuit is based upon the block diagram using two half adders shown in Fig. 10-5(c). Directly below this logic diagram is a logic circuit that is somewhat easier to wire. Figure 10-6(b) contains two XOR gates and three NAND gates, which makes the circuit fairly easy to wire. Notice that the circuit in Fig. 10-6(b) is exactly the same as the one in Fig. 10-6(a), except that NAND gates have been substituted for AND and OR gates.

	INPUTS	OUTI	PUTS	
C _{in}	В	Α	Σ	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
Carry + B + A			Sum	Carry out

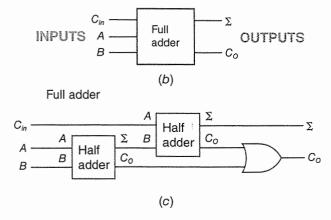

(a)

Fig. 10-5 Full adder. (a) Truth table. (b) Block symbol. (c) Constructed from half adders and an OR gate.

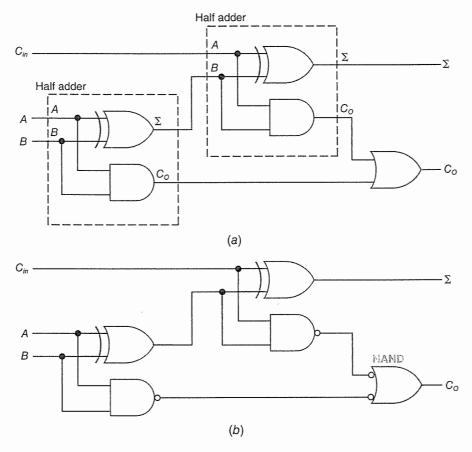


Fig. 10-6 Full adder. (a) Logic diagram. (b) Logic diagram using XDR and NAND gates.

Half and full adders are used together. For the problem in Fig. 10-2(a) we need one half adder for the 1s place and two full adders for the 2s place and the 4s place value. Half and full adders are rather simple combinational logic circuits. However, many of these circuits are needed to add longer problems (more binary digits). Many circuits similar to half and full adders are part of a microprocessor's *arithmetic-logic unit (ALU)*. These circuits are then used for adding 8-, 16-, 32-, or 64-bit binary numbers in a microcomputer system. The microprocessor's ALU can also subtract using the same half- and full-adder circuits. Later in this chapter, you will use adders to perform binary subtraction.

-₩- Self-Test

Answer the following questions.

- 12. Draw a block diagram of a full adder. Label inputs A, B, and C_{in} ; label outputs Σ and C_{o} .
- 13. Draw a truth table for a full adder.
- 14. Adder circuits are widely used in the _____ section of a microprocessor.
- 15. A ______ (half-adder, full-adder) circuit must be used for the 2s, 4s, 8s, and more significant bits in a binary addition problem.
- 16. Refer to Fig. 10-7. List the outputs from both the sum (Σ) and carry out (C_o) terminals of the full-adder circuit for each of the input pulses (t_1 to t_8).



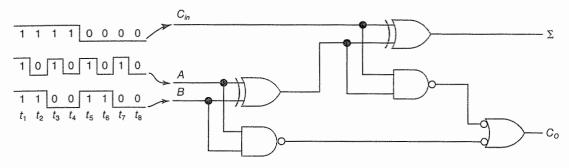


Fig. 10-7 Full-adder pulse-train problem for test question 16.

10-4 3-Bit Adders

Half and full adders are connected to form adders that add several binary digits (bits) at one time. The system in Fig. 10-8, adds two 3-bit numbers. The numbers being added are written as $A_2A_1A_0$ and $B_2B_1B_0$. Numbers from the 1s place value column are entered into the 1s adder which is a half adder. The inputs to the 2s adder are the carry from the half adder and the new bits A_1 and B_1 from the problem. The 4s adder adds A_2 and B_2 and the carry from the 2s adder. The total sum is shown in binary at the lower right. The output also has an 8s place value to take care of any binary number over

111 in the sum. Notice that the 4s adder's output (C_o) is connected to the 8s sum indicator.

The 3-bit binary adder is organized as you would *add and carry* by hand. The electronic adder in Fig. 10-8 is very much faster than doing the same problem by hand. Notice that multibit adders use a half adder for the 1s column only; all other bits use a full adder. This type of adder is called a *parallel adder*.

In a parallel adder, all bits are applied to the inputs at the same time. The sum appears at the output almost immediately. The parallel adder shown in Fig. 10-8 is a *combinational logic circuit* and typically needs various registers to latch data at the inputs and outputs.

3-bit adders

Parallel adder

Combinational logic circuit

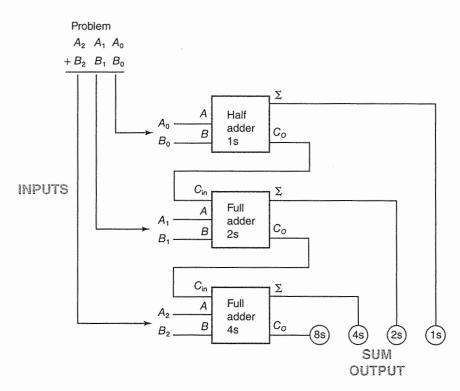


Fig. 10-8 A 3-bit parallel adder.

-W- Self-Test

Supply the missing word (or words) in each statement.

- 17. The unit in Fig. 10-8 uses a(n) ______ for adding the 1s column and _____ for the more significant columns.
- 18. Parallel adders are _____ (combinational, sequential) logic circuits.
- 19. If the inputs to the 3-bit binary adder in Fig. 10-8 are 110₂ and 111₂, the output indicators will show a sum of _____ in binary.
- 20. If the inputs to the 3-bit binary adder in Fig. 10-8 are 010₂ and 110₂, the output indicators will show a sum of _____ in binary.

- 21. If the inputs to the 3-bit binary adder in Fig. 10-8 are 111₂ and 111₂, the output indicators will show a sum of ______ in binary.
- 22. Draw a logic diagram (XOR and AND gates) that would substitute for the *Is half-adder block* in Fig. 10-8. Label inputs with A and B. Label outputs with Σ and C_0 .
- 23. Draw a logic diagram (XOR and NAND gates) that would substitute for the 2s or 4s full-adder blocks in Fig. 10-8. Label inputs with A, B, and C_{in} . Label outputs with Σ and C_{o} .



Binary subtraction

10-5 Binary Subtraction

Half subtractors
Full subtractors

You will find that adders and subtractors are very similar. You use half subtractors and full subtractors just as you use half and full adders. Binary subtraction tables are shown in Fig. 10-9(a). Converting these rules to truthtable form gives the table in Fig. 10-9(b). On the input side, B is subtracted from A to give output D_i (difference). If B is larger than A, such as in line 2, we need a borrow, which is shown in the column labeled B_0 (borrow out).

A block diagram of a half subtractor is shown in Fig. 10-9(c). Inputs A and B are on the left. Outputs D_i and B_o are on the right side of the diagram. Looking at the truth table in Fig. 10-9(b), we can determine the Boolean expressions for the half subtractor. The expression for the D_i column is $A \oplus B = D_i$. This is the same as for the half adder [see Fig. 10-3(a)]. The Boolean expression for the B_o column is $\overline{A} \cdot B = B_o$. Combining these two expressions in a logic diagram gives the logic circuit in Fig. 10-9(d). This is the logic circuit for a half subtractor; notice how much it looks like the half-adder circuit in Fig. 10-4.


When you subtract several columns of binary digits, you must take into account the borrowing. Suppose you are subtracting the numbers

in Fig. 10-10(a). You might keep track of the differences and borrows as shown in the figure. Look over the subtraction problem carefully, and check if you can do binary subtraction by this longhand method. (You can check yourself on the next test.)

A truth table that considers all the possible combinations in binary subtraction is shown in Fig. 10-10(*b*). For instance, line 5 of the table is the situation in the 1s column in Fig. 10-10(*a*). The 2s column equals line 3, the 4s column line 6, the 8s column line 3, the 16s column line 2, and the 32s column line 6 of the truth table.

A block diagram of a full subtractor is drawn in Fig. 10-11(a). The inputs A, B, and B_{in} are on the left; the outputs D_i and B_O are on the right.

Like the full adder, the full subtractor can be wired using two half subtractors and an OR gate. Figure 10-11(b) is a full subtractor showing how half subtractors are used. A logic diagram for a full subtractor is shown in Fig. 10-11(c). This circuit performs as a full subtractor as specified in the truth table in Fig. 10-10(b). The AND-OR circuit on the B_o output can be converted to three NAND gates if you want. The circuit would then be similar to the full-adder circuit in Fig. 10-6(b).

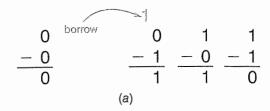


INPUTS		OUTPUTS		
Α	В	D_i	Bo	
0	0	0	0	
0	1	1	1	
1	0	1	0	
1	1	0	0	
Α -	- B	Difference	Borrow out	

(b)

32s 16s 8s 4s 2s 1s

1
10 10 0 10
1 0 1 A
- 1 0 1 0 1 A
Di
(a)

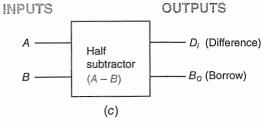

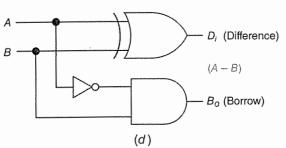


Fig. 10-9 (a) Binary subtraction tables. (b) Truth table for the half subtractor. (c) Block symbol of half subtractor. (d) Logic diagram for half subtractor.

	INPUTS			OUTF	PUTS
	A	В	B _{in}	D _i	Bo
Line 1	0	0	0	0	0
Line 2	0	0	1	1	1
Line 3	0	1	0	1	1
Line 4	0	1	1	0	1
Line 5	1	0	0	1	0
Line 6	1	0	1	0	0
Line 7	1	1	0	0	0
Line 8	1	1	1	1	1
	А	– B –	- B _{in}	Difference	Borrow out

Fig. 10-10 (a) Sample binary subtraction problem. (b) Truth table for a full subtractor.

Binary subtraction tables

Truth table for a full subtractor

-₩- Self-Test

Answer the following questions.

24. Do the binary subtraction problems in a to f. (Check yourself using decimal subtraction.)

25. Do the binary subtraction problems in a to d. (Check yourself using decimal subtraction)

a.
$$1010\ 1010_2$$

 $-0101\ 0110_3$

$$170_{10} - 86_{10}$$

(b)

$$\begin{array}{r}
 \hline
 252_{10} \\
 -69_{10}
\end{array}$$

$$\begin{array}{c} -0100\ 0101_2 \\ \text{c.} & 1100\ 0111_2 \end{array}$$

-000011111,

$$\frac{-15_{10}^{10}}{161_{10}}$$

- 26. Draw a block diagram of a half subtractor. Label inputs A and B; outputs D_i and B_o .
- 27. Draw a truth table for a half subtractor.
- 28. Draw a block diagram for a full subtractor. Label inputs A, B, and B_{in} ; label outputs D_i and B_o .
- 29. Draw a truth table for a full subtractor.

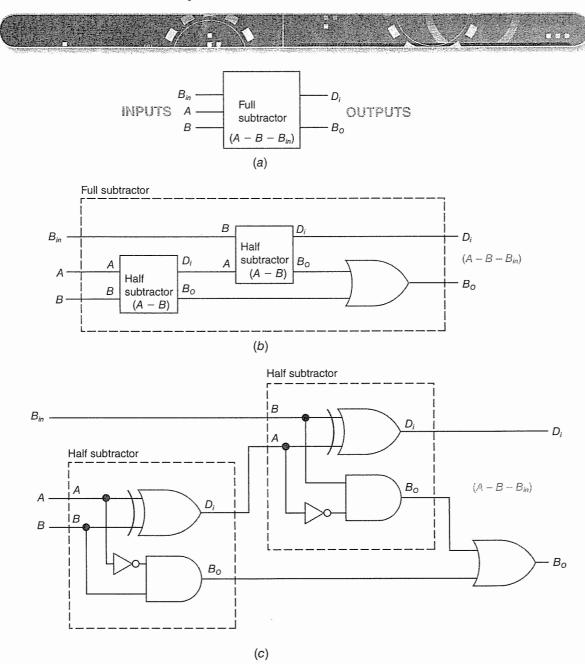


Fig. 10-11 Full subtractor. (a) Block symbol. (b) Constructed with half subtractors and an OR gate. (c) Logic diagram.

Parallel subtractor

10-6 Parallel Subtractors

Half and full subtractors are wired together to perform as a *parallel subtractor*. You have already seen adders connected as parallel adders. An example of a parallel adder is the 3-bit adder in Fig. 10-8. A parallel subtractor is wired in a similar manner. The adder in Fig. 10-8 is

considered a parallel adder because all the digits from the problem flow into the adder at the same time.

Figure 10-12 diagrams the wiring of a single half subtractor and three full subtractors. This forms a 4-bit parallel subtractor that can subtract binary number $B_3B_2B_1B_0$ from binary number $A_3A_2A_1A_0$. Notice in Fig. 10-12 that the top

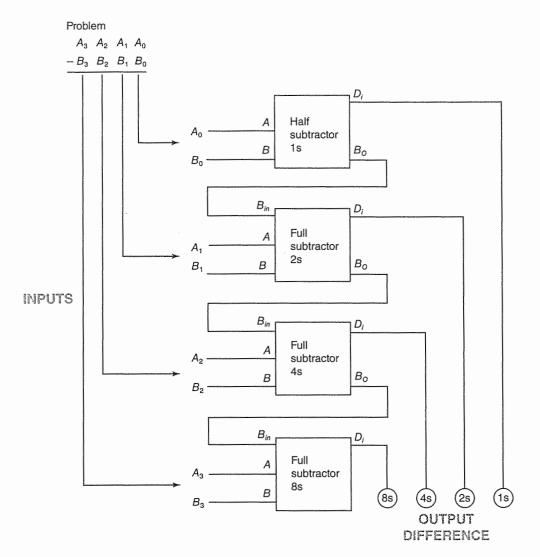


Fig. 10-12 A 4-bit parallel subtractor.

subtractor (half subtractor) subtracts the LSBs (1s place). The B_o output of the 1s subtractor is tied to the B_{in} input of the 2s subtractor. Each subtractor's B_o output is connected to the next more significant bit's borrow input. These borrow lines keep track of the borrows we discussed earlier.

ABOUT ELECTRONICS

Compact Data Storage Information storage is getting smaller and faster. Today, researchers continue to go beyond the limits of silicon to find ways to transmit, store, and retrieve data with molecules. The first step in meshing molecular systems with electronics is to magnetize single molecules.



Answer the following questions.

- 30. Refer to Fig. 10-12. This is a block diagram of a 4-bit ______ (parallel adder, parallel subtractor, serial adder, serial subtractor) circuit.
- 31. Refer to Fig. 10-12. The lines between subtractors (B_O to B_{in}) serve what purpose in this circuit?



Cascading adders

10-7 IC Adders

TTL 7483 4-bit binary full adder 8-bit binary adder IC manufacturers produce several adders. One elementary arithmetic IC is the TTL 7483 4-bit binary full adder. A block symbol for the 7483 IC adder is drawn in Fig. 10-13. The problem of addition of the two 4-bit binary numbers $(A_3A_2A_1A_0)$ and $B_3B_2B_1B_0$) is shown being entered into the eight inputs of the 7483 IC. Notice a difference in numbering systems on the problem and the IC (subscripts don't match). For adding just two 4-bit numbers, the C_o input is held at 0. The C_o input is marked as the C_{in} input by some manufacturers. The sum outputs are shown attached to output indicators. The C_{\star} output is attached to the 16s output indicator. The C_4 output is marked as the C_0 output by some manufacturers. This binary adder can indicate a sum as high as 11110 (decimal 30) when adding binary 1111 to 1111.

The internal organization of the 7483 adder IC is detailed in Fig. 10-14. The 7483 IC is a combinational logic circuit with no memory capabilities. The pin numbers used on DIP 7483 ICs are shown on the logic diagram in Fig. 10-14 with numbers in parentheses. For instance, data input A_1 is pin 10 on the DIP version of the 7483 adder IC. You will observe from the logic diagram in Fig. 10-14 that the circuitry is fairly complex.

The 7483 adder can be cascaded by connecting C_4 (carry out) output of IC1 to the C_0 (carry input) of the next 7483 IC (IC2). The details for cascading of two 7483 adders are shown in Fig. 10-15. This circuit is an 8-bit binary adder. This circuit will add the 8-bit binary inputs $A_7A_6A_5A_4A_3A_2A_1A_0$ to $B_7B_6B_5B_4B_3B_2B_1B_0$ yielding a 9-bit binary sum. The 8-bit binary adder can handle a maximum 9-bit sum of 1111111110₂ (1FE₁₆ or 510₁₀). For instance, if the inputs are 00011100₂ and 11100011₂ then the output will be 11111111₂ (in hexadecimal that would be 1C + E3 = FF).

Counterparts to the 7483 4-bit adder are the 74LS83, 74C83, and 4008 ICs. Other 4-bit adders that function the same as the 7483 IC but have a different pin configuration are the 74283, 74LS283, 74S283, 74F283, and 74HC283.

A more complex arithmetic chip is the 74LS181 IC. The 74LS181 and its relatives, the 74LS381, are described as *arithmetic-logic units/function generators*. These units perform many of the tasks of the ALUs in simple microprocessors and microcontrollers. These functions include add, subtract, shift, magnitude comparison, XOR, AND, NAND, OR, NOR, and other logic operations. The 74LS181 has CMOS relatives including the 74HC181 and MC14581.

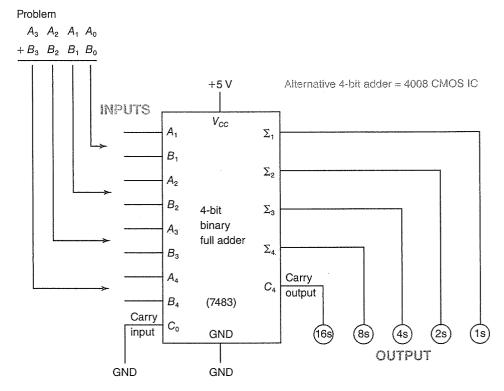


Fig. 10-13 The 7483 4-bit binary adder IC.

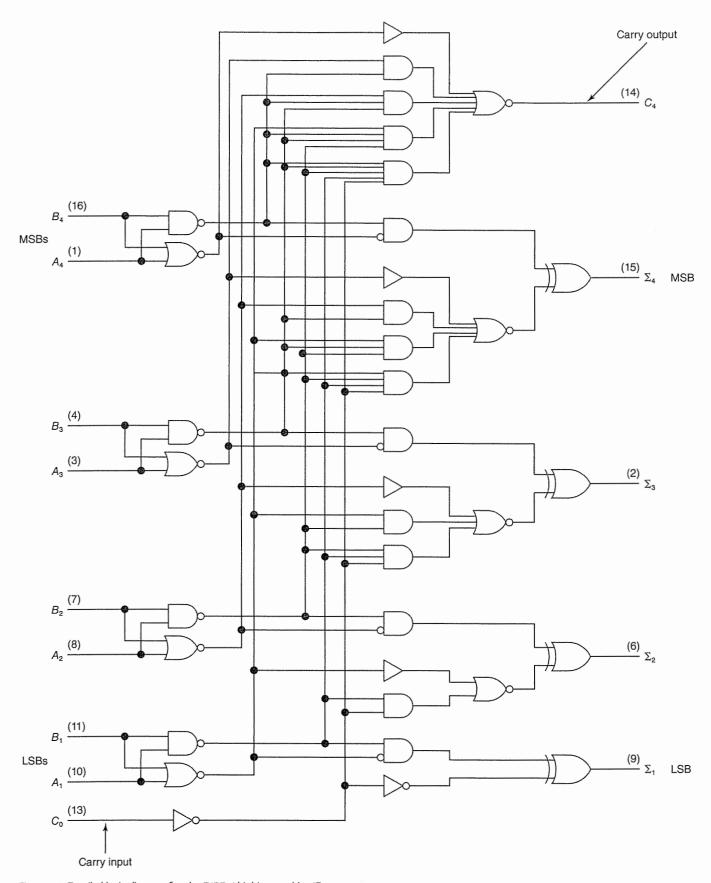


Fig. 10-14 Detailed logic diagram for the 7483 4-bit binary adder IC.

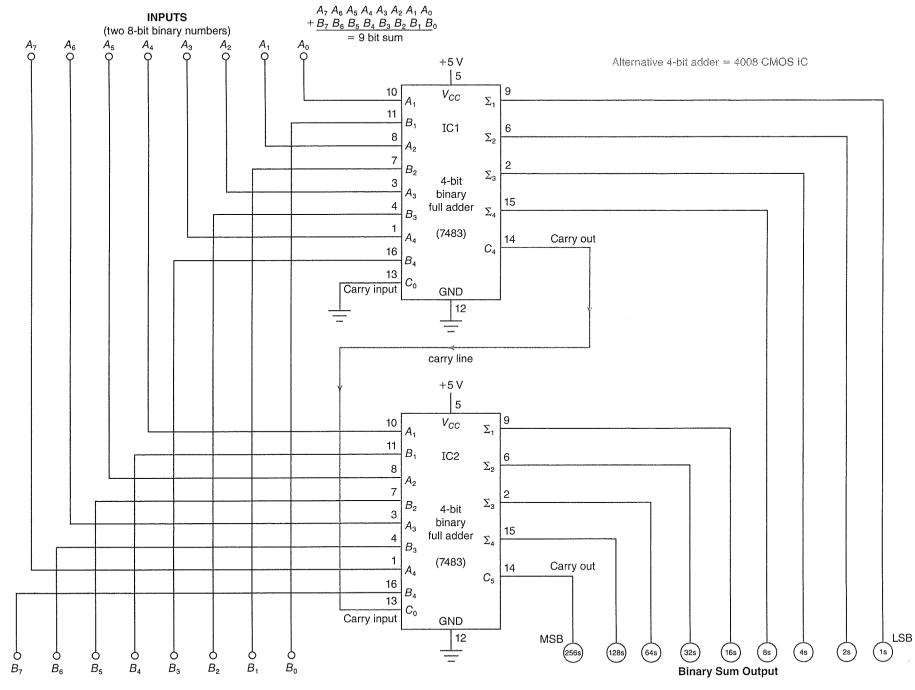


Fig. 10-15 Cascading two 7483 adders to form an 8-bit binary adder circuit.

-₩-

Self-Test

Supply the missing word in each statement.

- 32. The 7483 IC contains a 4-bit binary
- 33. Two 7483 ICs can be ______ to form an 8-bit parallel binary adder.
- 34. An adder such as the 7483 IC does not have a memory device, such a latch, built into the chip and is classified as a _____ (combinational, sequential) logic device.
- 35. The ______ (74LS32, 74LS181) is a more complex IC that performs many of the same operations (such as add, subtract, shift, compare, AND, OR, etc.) as the ALU of a microprocessor or microcontroller.

- 36. Refer to Fig. 10-13. If the binary inputs are 1100₂ and 1001₂, then the binary output will be _____.
- 37. Refer to Fig. 10-14. The 7483 adder IC contains both combinational and sequential logic circuits. (T or F).
- 38. Refer to Fig. 10-15. If the binary inputs are $1100 \ 1100_2$ and $0001 \ 1111_2$, then the binary output will be ______.
- 39. Refer to Fig. 10-15. If the binary inputs are 1111 1111₂ and 1111 1111₂, then the binary output will be _____.
- 40. Refer to Fig. 10-15. This circuit adds _____ (BCD, binary) numbers.



10-8 Binary Multiplication

In elementary school you learned how to multiply. You learned to lay out your multiplication problem similar to that in Fig. 10-16(a). You learned that the top number is called the *multiplicand* and the bottom number is the *multiplier*. The solution to the problem is called the *product*. The product of 7×4 , then, is 28, as shown in Fig. 10-16(a).

Figure 10-16(b) shows that multiplication really is just repeated addition. The problem $7 \times 4 = 28$ is represented by the multiplicand (7) being added four times, because 4 is the multiplier. The product is 28.

$$\begin{array}{c}
 7 \text{ Multiplicand} \\
 \times 4 \text{ Multiplier} \\
 \hline
 28 \text{ Product} \\
 \hline
 (a)
\end{array}$$

$$\begin{array}{c}
 \text{Multiplicand} \\
 7 + 7 + 7 + 7 = 28
\end{array}$$

$$\begin{array}{c}
 \text{Product} \\
 \hline
 \text{Multiplier} = 4
\end{array}$$

Fig. 10-16 (a) Decimal multiplication problem. (b) Multiplying using the repeated addition method.

If you want to multiply 54×14 , the repeated addition system is complicated and takes a long time. The multiplicand (54) must be added 14 times to get a product of 756. Most of us were taught to multiply 54×14 in the manner shown in Fig. 10-17(a). To solve the multiplication problem 54×14 , we first multiply the multiplicand, 54, by 4. This results in the first partial product (216) shown in Fig. 10-17(b). Next we multiply the multiplicand by 1. Actually the multiplicand is multiplied by a multiplier of 10, as shown in Fig. 10-17(c). The second partial product is 540. The first and second partial products (216 and 540) are then added for a final product of 756. It is normal to omit the 0 in the second partial product, as in Fig. 10-17(a).

It is important to notice the *process* in the problem in Fig. 10-17. The multiplicand is first multiplied by the LSD of the multiplier. This gives the first partial product. The second partial product is then calculated by multiplying the multiplicand by the MSD of the multiplier. The two partial products are then added, producing the final product. This same process is used in *binary multiplication*.

Binary multiplication is much simpler than decimal multiplication. The binary system has only two digits (0 and 1), which makes the rules Multiplicand Multiplier Product

Binary multiplication

Rules for binary multiplication

540 Second partial product (c)

Fig. 10-17 (a) Decimal multiplication problem. (b) Calculating the first partial product.

(c) Calculating the second partial product.

Rules for b	inary multiplication	on .
0	0	1 1
$\times 0$	<u>×1</u> >	<u><0</u> <u>×1</u>
0	0	0 1
	(a)	
Decimal	Binary	
7	111	Multiplicand
$\times 5$	<u>×101</u>	Multiplier
35	111	First partial product
	000	Second partial product
	111	Third partial product
	100011	Product
	(b)	

Fig. 10-18 (a) Rules for binary multiplication. (b) Sample multiplication problem.



Search for web pages on binary multiplication.

Decimal	Binary	
27	11011	Multiplicand
<u>×12</u>	<u>× 1100</u>	•
5 4	1101100	Third partial product
27	11011	Fourth partial product
324	101000100	Product

Fig. 10-19 Sample multiplication problem.

for multiplying simple. Figure 10-18(a) shows the rules for binary multiplication.

Multiplication with binary numbers is done just as with decimal numbers. Figure 10-18(b) details a problem where binary 111 is multiplied by binary 101. First, the multiplicand (111) is multiplied by the 1s bit of the multiplier. The result is the first partial product, shown as 111 in Fig. 10-18(b). Next, the multiplicand is multiplied by the 2s bit of the multiplier. The result is the second partial product (0000). Notice that the LSB of the second partial product, 0000, is left off in Fig. 10-18(b). Third, the multiplicand is multiplied by the 4s bit of the multiplier. The result is the third partial product of 11100, shown in Fig. 10-18(b) as 111, with the two blank spaces in the 1s and 2s places. Finally, the first, second, and third partial products are added, resulting in a product of binary 100011. Notice that the same multiplication problem in decimal is shown at the left of Fig. 10-18(b) for your convenience. The binary product 100011 equals the decimal product 35.

Another binary multiplication problem is shown in Fig. 10-19. At the left the problem is in the familiar decimal form; the same problem is repeated in binary form at the right, where binary 11011 is multiplied by 1100. As in decimal multiplication, the Os in the multiplier can simply be brought down to hold the 1s and 2s places in the binary number. The binary product is shown as 101000100, which equals decimal 324.

You will gain experience in solving binary multiplication problems by answering the questions that follow.

Partial product



Self-Test

Answer the following questions.

- 41. Find the product for binary 111×10 .
- 42. Find the product for binary 1101×101 .
- 43. Find the product for binary 1100×1110 .
- 44. Solve these multiplication problems:

a.
$$1111_{2}$$
 15_{10} $\times 1001_{2}$ $\times 9_{10}$

b.	${\overset{1100}{\times}}{\overset{1000}{_{2}}}$	$\times 8_{10}^{12}$
c.	$\begin{array}{c} 1011_2 \\ \times 1011_2 \end{array}$	$\begin{array}{c} 11_{10} \\ \times 11_{10} \end{array}$



10-9 Binary Multipliers

We can multiply numbers by repeated addition, as illustrated in Fig. 10-16(b). The multiplicand (7) could be added four times to obtain the product of 28. A block diagram of a circuit that performs repeated addition is shown in Fig. 10-20. The multiplicand is held in the top register. In our example the multiplicand is a decimal 7, or a binary 111. The multiplier is held in the down counter shown on the left in Fig. 10-20. The multiplier in our example is a decimal 4, or a binary 100. The lower product register holds the product.

The repeated addition technique is shown in operation in Fig. 10-21. This chart shows how the multiplicand (binary 111) is multiplied by the multiplier (binary 100). The product register is cleared to 00000. After one count downward, a partial product of 00111 (decimal 7) appears in the product register. After the second count downward, a partial product of 01110 (decimal 14) appears in the product register. After the third count downward, a partial product of 10101 (decimal 21) appears in the product register. After the fourth downward count, the final product of 11100 (decimal 28) appears in the product register. The multiplication problem (7 \times 4 = 28) is complete. The circuit of Fig. 10-20 has added 7 four times for a total of 28.

This type of circuit is not widely used because of the long time it takes to do the repeated addition when large numbers are multiplied. A more practical method of multiplying in digital electronic circuits is the *add-and-shift method* (also called the shift-and-add method). Figure 10-22 shows a binary multiplication

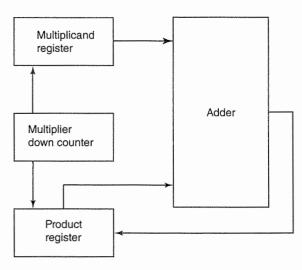


Fig. 10-20 Block diagram of a repeated addition-type multiplier system.

problem. In this problem binary 111 is multiplied by 101 (7×5 in decimal). This hand-done procedure is standard except for the temporary product in line 5. Line 5 has been added to help you understand how multiplication might be done by digital circuits. Close observation of binary multiplication shows the following three important facts:

- 1. Partial products are always 000 if the multiplier is 0 and equal to the multiplicand if the multiplier is 1.
- The product register needs twice as many bits as the multiplicand register assuming the multiplier has the same or a fewer number of bits.
- 3. The first partial product is shifted one place to the *right* (*relative to* the second partial product) when adding.

Add-and-shift method

	Load with binary	After 1 down count	After 2 down counts	After 3 down counts	After 4 down counts
Multiplicand register	111	111	111	111	111
Multiplier counter	100	011	010	001	000
Product register	00000	00111	01110	10101	11100
	Load				Stop

Fig. 10-21 Multiplying binary 111 and 100 using the repeated addition circuit.

Line 1	111	Multiplicand
Line 2	×101	Multiplier
Line 3	111	First partial product
Line 4	000	Second partial product
Line 5	0 1 1 1	Temporary product (line 3 + line 4)
Line 6	111	Third partial product
Line 7	100011	Product

Fig. 10-22 Binary multiplication problem.

You can observe each characteristic by looking at the sample problem in Fig. 10-22.

The important characteristics of longhand multiplication have been given. A binary multiplication circuit can be designed by using these characteristics. Figure 10-23(a) shows a circuit that does binary multiplication. Notice that the multiplicand (111) is loaded into the register at the upper left. The accumulator register is cleared to 0000. The multiplier (101) is loaded into the register at the lower right. Notice, too, that the accumulator and the multiplier are considered together. This is shown by the shading connecting the two registers.


Let us use the circuit in Fig. 10-23(a) to demonstrate the detailed procedure for multiplying. The diagram in Fig. 10-23(b) is a step-by-step review of how binary 111 is multiplied by 101 using the add-and-shift method. The binary 111 is loaded into the multiplicand register. The accumulator and multiplier registers are loaded in step A in Fig. 10-23(b). Step B shows the 0000 and the 111 from the accumulator and multiplicand registers being added when the 1 is applied to the control line. This is comparable to

line 3 of the multiplication problem in Fig. 10-22. Step C shifts both the accumulator and the multiplier register one place to the right. The LSB of the multiplier (1) is shifted out the right end and lost. Step D represents another add step. This time a 0 is applied to the control line. A 0 on the control line means no addition. The register contents remain the same. Step D is comparable to lines 4 and 5, Fig. 10-22. Step E shows the registers being shifted one place to the right. This time the 2s bit of the multiplier is lost as it is shifted out the right end of the register. Step F shows the 4s bit of the multiplier (1) commanding the adder to add. The accumulator contents (0001) and the multiplicand (111) are added. The result of that addition is deposited in the accumulator register (1000). This step is comparable to the left section of lines 5 to 7, Fig. 10-22. Step G is the final step in the add-and-shift multiplication; it shows a single shift to the right for both registers. The 4s bit of the multiplier is lost out of the right end of the register. The final product appears across both registers as 100011. Binary 111 multiplied by 101 resulted in a product of 100011 (7 \times 5 = 35 in decimal). The final product calculated by the multiplier circuit is the same result we got in line 7, Fig. 10-22, when we multiplied by hand.

Two types of multiplier circuits have just been illustrated. The first uses repeated addition to arrive at the product. That system is shown in Fig. 10-20. The second circuit uses the add-and-shift method of multiplying. The add-and-shift system is shown in Fig. 10-23.

In many computers the procedure, such as the add-and-shift method, can be programmed

Add-and-shift method of multiplying

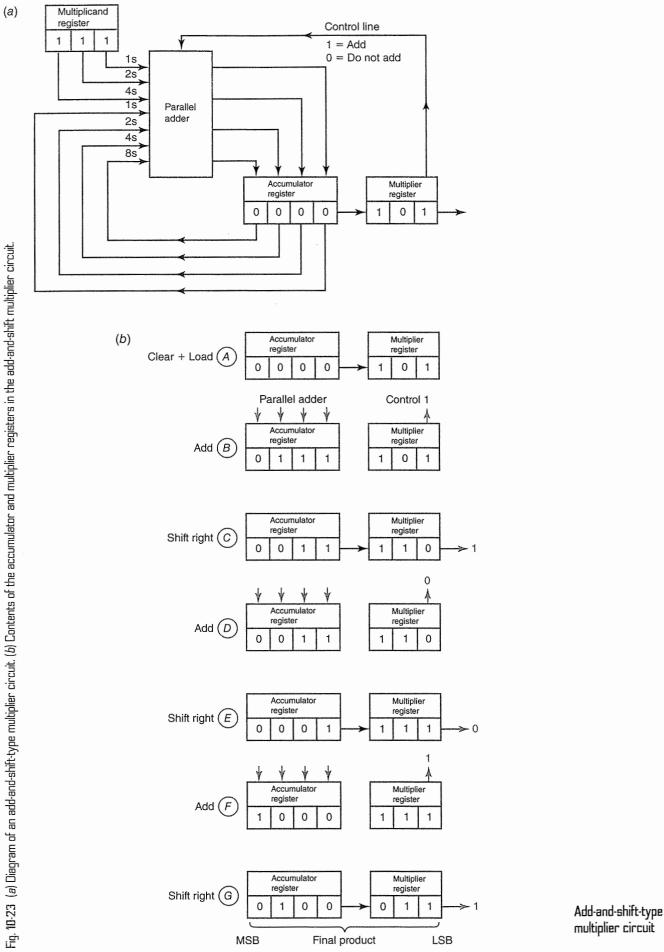

into the machine. Instead of permanently wiring the circuit, we simply *program*, or instruct, the computer to follow the procedure shown in Fig. 10-23(b). We are thus using *software* (a program) to do multiplication. This use of software cuts down on the amount of electronic circuits needed in the CPU of a computer.

Simpler 8-bit microprocessors, such as the obsolete Intel 8080/8085, Motorola 6800, and the 6502/65C02, do not have circuitry in their


ALUs to do multiplication. To perform binary multiplication on these processors, the programmer must write a program (a list of instructions) that multiplies numbers. Either the add-and-shift or the repeated addition method can be used for programming these microprocessor-based machines to do multiplication. Most advanced microprocessors do have multiply instructions. Some more expensive microcontrollers also have a multiply instruction.

Microprocessors



Answer the following questions.

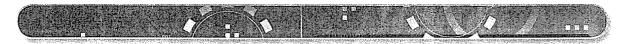- 45. Refer to Fig. 10-20. This circuit uses what method of binary multiplication?
- 46. A widely used technique for multiplying using digital circuits is the _____ method.
- 47. Refer to Fig. 10-23. This circuit uses what method of binary multiplication?
- 48. All microcontrollers have a multiply instruction. (T or F)
- 49. Refer to Fig. 10-23. The *parallel adder* would be classified as a ______ (combinational, sequential) logic device that has no memory characteristic.
- 50. Refer to Fig. 10-23. What three devices in this system are classified as sequential logic devices?



10-10 2s Complement Notation, Addition, and Subtraction

The 2s complement method of representing numbers is widely used in microprocessors. To now, we have assumed that all numbers are positive. However, microprocessors must process both positive and negative numbers. Using 2s complement representations, the sign as well as the magnitude of a number can be determined.

2s Complement 4-bit

For simplicity, assume we are using a 4-bit processor. This means that all data are transferred and processed in groups of four. The MSB is the *sign bit* of the number. This is shown in Fig. 10-24(a). A 0 sign bit means a positive number, while a 1 sign bit means a negative number.

The table in Fig. 10-24(b) shows the 2s complement representation for all the 4-bit positive and negative numbers from +7 to -8. The MSBs in Fig. 10-24(b) of the positive 2s complement numbers are 0s. All negative numbers


(-1 to -8) start with a 1. Note that 2s complement representations of positive numbers are the same as binary. Therefore, +7 (decimal) = 0111 (2s complement) = 0111 (binary).

The 2s complement representation of a negative number is found by first taking the 1s complement of the number and then adding 1. An example of this process is shown in Fig. 10-25(a). The negative decimal number -4 is to be converted to its 2s complement form:

- 1. Convert the decimal number to its binary equivalent. In this example, convert -4₁₀ to 0100₂.
- 2. Convert the binary number to its 1s complement by changing all 1s to 0s and all 0s to 1s. In this example, convert 0100, to 1011 (1s complement).
- 3. Add 1 to the 1s complement number, using regular binary addition. In this example, 1011 + 1 = 1100. The answer (1100 in this example) is the 2s complement representation. Therefore, -4₁₀ = 1100 (2s complement).

2s complement representations

Sign bit

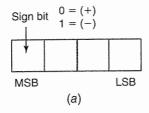

Signed decimal	4-bit 2s complement representation	
+7	0111	
+6	0110	
+5	0101	Compage
+4	0100	Same as binary
+3	0011	numbers
+2	0010	
+1	0001	
0	0000	IJ
-1	1111	
-2	1110	
-3	1101	A Polymer
-4	1100	
-5	1011	
-6	1010	
-7	1001	
-8	1000	
	(b)	

Fig. 10-24 (a) MSB of 4-bit register is a sign bit.

(b) 2s complement representation of positive and negative numbers.

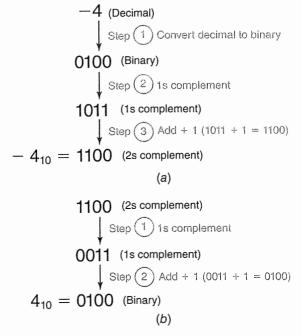


Fig. 10-25 (a) Converting signed decimal numbers to 2s complement form. (b) Converting from 2s complement form to binary numbers.

This answer can be verified by referring to the table in Fig. 10-24(b).

To convert from 2s complement form to binary, follow the procedure shown in Fig. 10-25(b). In this example, the 2s complement number (1100) is being converted to its binary equivalent. Its equivalent decimal number can then be found from the binary.

- 1. Form the 1s complement of the 2s complement number by changing all 1s to 0s and all 0s to 1s. In this example, convert 1100 to 0011.
- 2. Add 1 to the 1s complement number, using regular binary addition. In this example, 0011 + 1 = 0100. The answer (0100 in this example) is in binary. Therefore, $0100_2 = 4_{10}$.

Because the MSB of the 2s complement number (1100) is a 1, the number is negative. Therefore, 2s complement 1100 equals -4_{10} .

2s Complement Addition

2s complement notation is widely employed because it makes it easy to add and subtract signed numbers. Four examples of adding 2s complement numbers are shown in Fig. 10-26. Two positive numbers are added in Fig. 10-26(a). 2s complement addition looks just like adding in binary in this example. Two negative numbers $(-1_{10} \text{ and } -2_{10})$ are added in Fig. 10-26(b). The 2s complement numbers representing -1and -2 are given as 1111 and 1110. The MSB (overflow from 4-bit register) is discarded, leaving the 2s complement sum of 1101, or -3in decimal. Look over examples (c) and (d) in Fig. 10-26 to see if you understand the procedure for adding signed numbers using 2s complement notation.

2s Complement Subtraction

The 2s complement notation is also useful in subtracting signed numbers. Four subtraction problems are shown in Fig. 10-27. The first problem is $(+7) - (+3) = +4_{10}$. The subtrahend (+3) in this case) is converted to its binary form. Next, the 2s complement of this is formed, yielding 1101. Then 0111 is *added* to 1101, yielding 10100. The MSB (overflow from 4-bit register) is discarded, leaving the *difference* of 0100, or $+4_{10}$. Note that an adder is used for subtraction. This is done by converting the subtrahend to its

Add or subtract signed numbers

Converting signed decimal numbers to 2s complement form

$$\begin{array}{c} (+4) \\ + (+3) \\ \hline +7_{10} \\ \hline \end{array} \qquad \begin{array}{c} (-1) \\ + (-2) \\ \hline -3_{10} \\ \hline \end{array} \qquad \begin{array}{c} 1111 \\ + 1110 \\ \hline 11101 \\ \end{array} \qquad \begin{array}{c} (2s \text{ complement SUM)} \\ (2s \text{ complement SUM)} \\ (b) \\ (b) \\ \hline (+1) \\ + (-3) \\ \hline -2_{10} \\ \hline \end{array} \qquad \begin{array}{c} 0001 \\ + 1101 \\ \hline 1110 \\ \hline \end{array} \qquad \begin{array}{c} (2s \text{ complement SUM)} \\ (c) \\ (c) \\ \hline \end{array} \qquad \begin{array}{c} (-5) \\ + (-4) \\ \hline +1_{10} \\ \hline \end{array} \qquad \begin{array}{c} 0101 \\ + 1100 \\ \hline 10001 \\ \end{array} \qquad \begin{array}{c} (2s \text{ complement SUM)} \\ \end{array} \qquad \begin{array}{c} (-5) \\ (-5) \\ \hline \end{array} \qquad \begin{array}{c} (-7) \\ \hline \end{array} \qquad \begin{array}{c} (-$$

Fig. 10-26 Four sample signed addition problems using 4-bit 2s complement numbers.

2s complement and adding. Any carry or overflow into the fifth binary place is discarded.

Look over the sample 2s complement subtraction problems using an adder in Fig. 10-27(b), (c), and (d). See if you can follow the procedure in these remaining subtraction problems.

2s Complement 8-bit

Only 4-bit 2s complement representations have been used in previous examples. Most microprocessors and microcontrollers use 8-, 16-, 32-, or 64-bit groupings. The procedures used with 4-bit 2s complement descriptions of binary numbers also apply to 8-, 16-, 32-, or 64-bit representations.

In an 8-bit 2s complement of a number, the MSB is the sign bit as illustrated in Fig. 10-28(a). This allows both the sign and magnitude of the number to be represented. Some 8-bit 2s complement representations of positive and negative numbers are shown in Fig. 10-28(b). Notice that the range of numbers for an 8-bit 2s complement is from -128 to +127. Notice from the top half of the chart in Fig. 10-28(b) that decimal numbers from 0 through +127 (positive numbers) have 2s complements that are the same as binary

$$\frac{(+7)}{-(+3)} = 0011 \xrightarrow{\text{Form 2s complement}} \frac{0111}{1 \ 0100} + \frac{1101}{1 \ 0100}$$

$$\frac{(-8)}{-(-3)} = 1101 \xrightarrow{\text{Form 2s complement}} \frac{1000}{1 \ 011} + \frac{1011}{1011}$$

$$\frac{(2s \text{ complement DIFFERENCE})}{(2s \text{ complement DIFFERENCE})}$$


$$\frac{(+3)}{-(-3)} = 1101 \xrightarrow{\text{Form 2s complement}} \frac{(b)}{1 \ 0110} + \frac{0011}{0110}$$

$$\frac{(2s \text{ complement DIFFERENCE})}{(2s \text{ complement DIFFERENCE})}$$

$$\frac{(-4)}{-(+2)} = 0010 \xrightarrow{\text{Form 2s complement}} \frac{1100}{1 \ 1010} + \frac{1110}{1 \ 1010}$$

$$\frac{(2s \text{ complement DIFFERENCE})}{(2s \text{ complement DIFFERENCE})}$$

Fig. 10-27 Four sample signed subtraction problems using 4-bit 2s complement numbers.

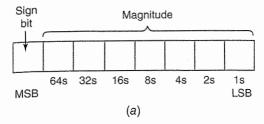

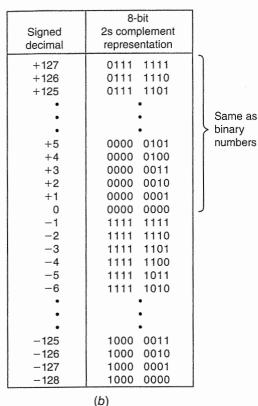


Fig. 10-28 (a) MSB of 8-bit register is a sign bit.
(b) 2s complement representation of selected positive and negative numbers.

numbers. As an example, +125 is represented by 0111 1101 in either binary or 2s complement.

Converting a negative decimal number (from -1 to -128) to its 8-bit 2s complement is accomplished by the same process shown earlier in Fig. 10-25(a). Follow the three-step process in the example below:

- Convert the decimal number −126 to its binary equivalent.
 - Example: $126_{10} = 011111110_{2}$
- 2. Convert the binary number to its 1s complement. Example: 0111 1110, = 1000 0001 (1s c)
- 3. Add 1 to the 1s complement forming the 2s complement. Example: $1000\ 0001\ (1s\ c) + 1 = 1000\ 0010\ (2s\ c)$ Result: $-126_{10} = 1000\ 0010$ in 2s complement

Next convert a 2s complement representation of a negative number to its decimal equivalent. Follow the three-step process in this example:

- 1. Convert the 2s complement to its 1s complement form. Example: 1001 1100 (2s c) = 0110 0011 (1s c)
- 2. Add + 1 to the 1s complement to form the binary number. Example: $0110\ 0011\ (1s\ c) + 1 = 0110\ 0100_{2}$
- 3. Convert the binary number to its decimal equivalent. Example: $0110\,0100_2 = (64 + 32 + 4 = 100) = 100_{10}$ Result: $1001\,1100\,(2s\,c) = -100_{10}$

In the previous examples, you converted a negative decimal number to its 2s complement. Later, you reversed the process and converted a 2s complement to a negative decimal number. Because these conversions are time-consuming and prone to errors, Appendix B includes a 2s complement number conversion chart. Appendix B contains 2s complements of decimal numbers -1 through -128.

Several 8-bit 2s complement addition problems are solved in Fig. 10-29(a). Remember when overflows (more than 8 bits) occur, they are discarded. The sums are in 2s complement notation, but remember that for positive numbers the 2s complement and binary number are the same. Review these addition problems to see if you understand the procedure. You will have practice problems later.

Several 8-bit 2s complement subtraction problems are solved in Fig. 10-29(b). Remember when overflows (more than 8 bits) occur, they are discarded. Notice that only the subtrahends are 2s complemented before they are added to the minuend. The differences are in 2s complement notation, but remember that for positive numbers, the 2s complement and binary number are the same. Review these subtraction problems to see if you understand the procedure. You will have practice problems later.

In summary, 2s complement notation is used because it shows both the sign and magnitude of a number. Remember that 2s complement and binary numbers are identical for positive numbers. Also, 2s complement numbers can be used with adders to either *add* or *subtract signed numbers*. The next section in the text-book will diagram an adder/subtractor system that makes use of 2s complement notation.

2s complement addition

2s complement subtraction

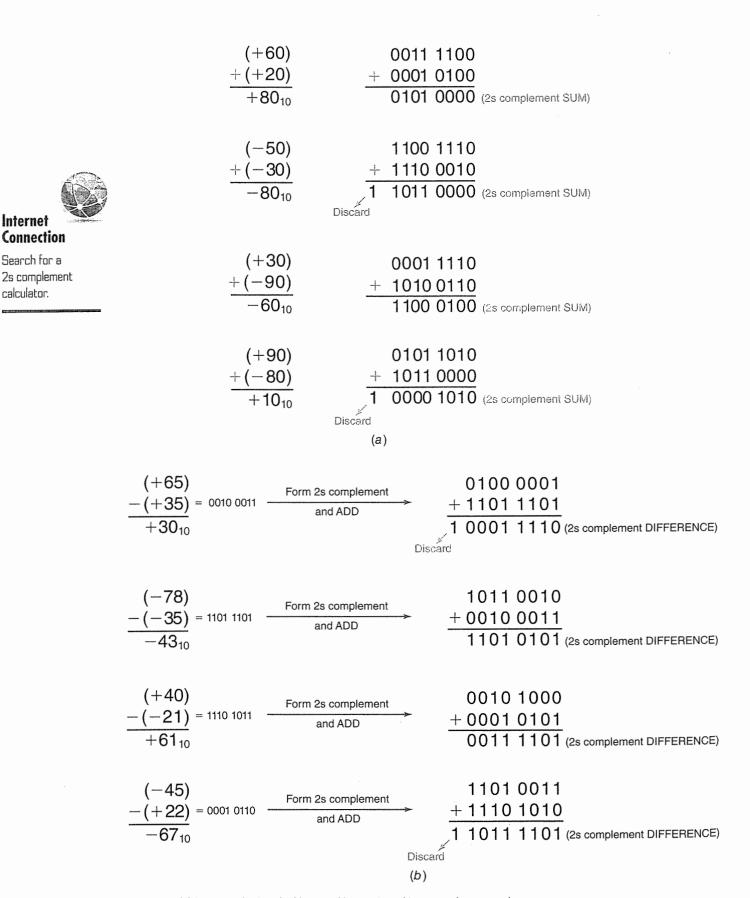


Fig. 10-29 (a) Four sample signed addition problems using 8-bit 2s complement numbers.

(b) Four sample signed subtraction problems using 8-bit 2s complement numbers.



Self-Test

Answer the following questions.

- 51. When microprocessors process both positive and negative numbers, ______ representations may be used.
- 52. The 4-bit 2s complement number 0111 represents ______ in binary and _____ in decimal.
- 53. The 4-bit 2s complement number 1111 represents ______ in decimal.
- 54. In 2s complement representation, the MSB is the ______ bit. If the MSB is 0, the number is _____ (negative, positive), whereas if the MSB is 1, the number is _____ (negative, positive).
- 55. The decimal number –6 equals _____ in 2s complement 4-bit representation.
- 56. The decimal number +5 equals
 _____ in 2s complement 4-bit representation.
- 57. Calculate the sum of the 4-bit 2s complement numbers 1110 and 1101. Give

- the answer in 2s complement and in decimal.
- 58. Calculate the sum of the 4-bit 2s complement numbers 0110 and 1100. Give the answer in 2s complement and in decimal.
- 59. Decimal 90 equals ______ in binary and _____ in 8-bit 2s complement.
- 60. Decimal -90 equals _____ in 8-bit 2s complement.
- 61. Adding 0111 1111 (2s c) and 1111 0000 (2s c) yields _______ in 8-bit 2s complement or ______ in decimal.
- 62. Adding 1000 0000 (2s c) and 0000 1111 (2s c) yields ______ in 8-bit 2s complement or _____ in decimal.
- 63. Subtracting 0001 0000 (2s c) from 1110 0000 (2s c) yields ______ in 8-bit 2s complement or _____ in decimal.
- 64. Subtracting 1111 1111 (2s c) from 0011 0000 (2s c) yields ______ in 8-bit 2s complement or _____ in decimal.



10-11 2s Complement Adders/ Subtractors

A 2s complement 4-bit adder/subtractor system is drawn in Fig. 10-30. Note the use of four full adders to handle the two 4-bit numbers. XOR gates have been added to the B inputs of each full adder to control the mode of operation of the unit. With the mode control at 0, the system adds the 2s complement numbers $A_3A_2A_1A_0$ and $B_2B_2B_1B_0$. The sum appears in 2s complement notation at the output indicators at the lower right. The LOW at the A inputs of the XOR gates permit the B data to flow through the gate with no inversion. If a HIGH enters B_0 input to the XOR gate, then a HIGH exits the gate at Y. The C_{in} input to the top 1s full adder is held at a 0 during the time the mode control is in the add position. In the add mode, the 2s complement

adder operates just like a binary adder except that the carry out (C_o) from the 8s full adder is discarded. In Fig. 10-30, the C_o output from the 8s full adder is left disconnected.

The mode control input is placed at logical 1 for the unit to subtract 2s complement numbers. This causes the XOR gates to invert the data at the B inputs. The C_{in} input to the 1s full adder also receives a HIGH. The combination of the XOR gate's inversion plus adding the 1 at the C_{in} input of the 1s full adder is the same as complementing and adding 1. This is comparable to forming the 2s complement of the subtrahend (B number in Fig. 10-30).

Remember that the system in Fig. 10-30 uses only 2s complement numbers. The 4-bit adder/subtractor system in Fig. 10-30 could be extended to 8, 16, 32, or 64 bits to handle larger 2s complement numbers.

2s complement 4-bit adder/ subtractor system

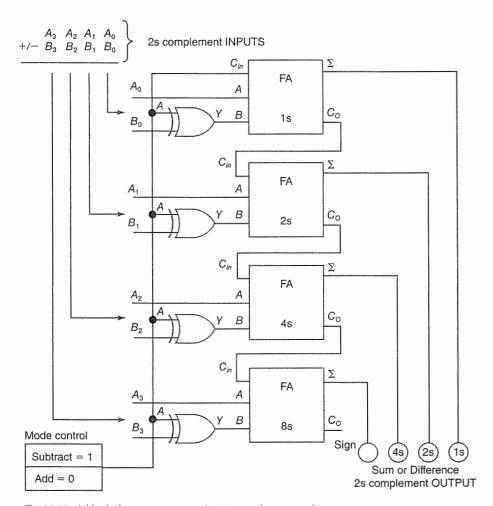


Fig. 10-30 Adder/subtractor system using 2s complement numbers.


-₩- Self-Test

Supply the missing word or words in each statement.

- 65. Refer to Fig. 10-30. The numbers to be added or subtracted in this system must be in ______ (binary, BCD, 1s complement, 2s complement) form.
- 66. Refer to Fig. 10-30. The sum or difference output from this system will be in _____ (binary, BCD, 1s complement, 2s complement) form.
- 67. Refer to Fig. 10-30. This system can add or subtract _____ (signed, only unsigned) numbers.
- 68. Refer to Fig. 10-30. If the system is adding 0011 (2s c) to 1100 (2s c), the output will read _____. This is the 2s

complement representation for decimal

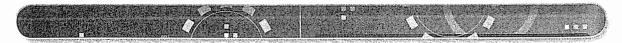- 69. Refer to Fig. 10-30. If the system is subtracting 0010 (2s c) from 0101 (2s c), the output will read ______. This is the 2s complement representation for decimal
- 70. Refer to Fig. 10-30. If the system is adding 1010 (2s c) to 0100 (2s c), the output will read _____. This is the 2s complement representation for decimal
- 71. Refer to Fig. 10-30. If the system is subtracting 1110 (2s c) from 1001 (2s c), the output will read ______. This is the 2s complement representation for decimal _____.



10-12 Troubleshooting a Full Adder

A faulty full adder circuit is sketched in Fig. 10-31(a). The student or technician first checks the circuit visually and for signs of excessive heat. No problems are found.

The full adder is a *combinational logic circuit*. For your convenience, its truth table with normal outputs is shown in Fig. 10-31(b). The student or technician manipulates the full-adder inputs and using a logic probe checks the outputs (Σ and C_o). The actual logic probe outputs are shown in the right-hand columns of the truth table in Fig. 10-31(b). H stands for a HIGH logic level, while L stands for a LOW logic level. Two errors seem to appear in the C_o column in lines 6 and 7 of the truth table. These are noted in Fig. 10-31(b). A look at the truth-table results of the faulty full adder indicates no trouble in the Σ column. The Σ circuitry involves the two XOR gates labeled 1 and 2 in Fig. 10-31(a). It appears that these gates are operating properly.

The troubleshooter expects the problem to be in the OR gate or two AND gates. The bottom line of the truth table suggests that the bottom AND gate and OR gate work. The upper AND gate (labeled 4) is suspect. The technician manipulates the inputs to line 6 on the truth table $(C_{in} = 1, B = 0, A = 1)$. Pins 1 and 2 of the AND gate labeled 4 should both be 1. Both inputs to gate 4 indicate a HIGH logic level when a logic probe is touched to pins 1 and 2. Output 3 of AND gate 4 is checked and remains LOW. This indicates a stuck LOW output at gate 4.

The technician carefully checks the 7408 IC and surrounding circuit board for possible short circuits to GND. None are found. Gate 4 is assumed to have a stuck LOW output, and the 7408 IC is replaced with an exact duplicate.

After replacement of the 7408 IC, the troubleshooter checks the full-adder circuit for proper operation. The circuit works according to its normal truth table. Truth tables help both technicians and students with troubleshooting. Such tables define how a *normal circuit should*

Troubleshooting a full adder

Combinational logic circuit

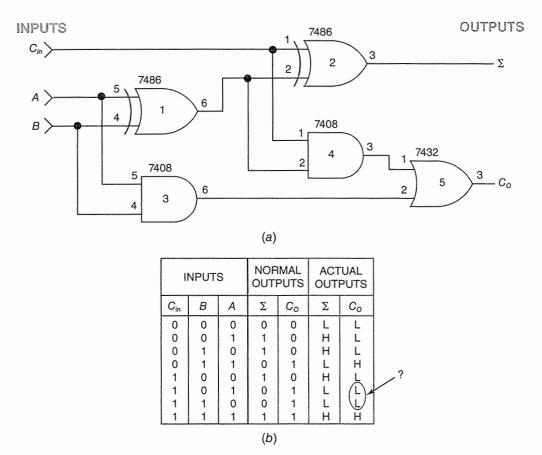


Fig. 10-31 (a) Faulty full-adder circuit used for troubleshooting problem. (b) Full-adder truth table with normal and actual outputs.

respond. The truth table becomes part of the technician's knowledge of the circuit. Knowledge of normal circuit operation is critical to good troubleshooting.


To review, six hints for successful trouble-shooting are:

- 1. *Know* the normal operation of the circuit.
- 2. *Feel* the top of the IC to determine if it is hot.
- 3. *Look* for broken connections or signs of excessive heat.
- 4. *Smell* for overheating.
- 5. *Check* the power source and power to ICs.
- 6. *Trace* the path of logic through the circuit, and isolate the faulty section.


-1/\-	Self-Test	- CALCARD - CALCARD
		2

Supply the missing word or words in each statement.

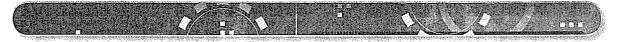- 72. Refer to Fig. 10-31. The fault in the
 ______ (combinational, sequential)
 logic circuit seems to be in the _____
 (carry out, sum) part of the circuit.
- 73. Refer to Fig. 10-31. The fault in the circuit is in gate _____ [number]; the output is stuck _____ (HIGH, LOW).
- 74. Knowledge of normal circuit operation is critical to good troubleshooting. (T or F)
- 75. List several hints for successful troubleshooting.



Chapter 10 Summary and Review

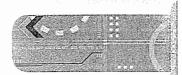

Summary

- Arithmetic circuits, such as adders and subtractors, are combinational logic circuits constructed with logic gates.
- 2. The basic addition circuit is called a half adder. Two half adders and an OR gate can be wired to form a full adder.
- 3. The basic subtraction circuit is called a half subtractor. Two half subtractors and an OR gate can be wired to form a full subtractor.
- 4. Adders can be wired together to form parallel adders.
- 5. A 4-bit parallel adder adds two 4-bit binary numbers at one time. This adder contains a single half adder (1s place) and three full adders.

- 6. Manufacturers produce several arithmetic ICs.
- 7. Adder/subtractor units are often part of the CPU of calculating machines.
- 8. Binary multiplication performed by digital circuits may use repeated additions or the add-and-shift method.
- 9. Microprocessors may use 2s complement notation when dealing with signed numbers. Adders can be used to perform addition and subtraction using 2s complement numbers.
- 10. Truth tables are a great aid in troubleshooting combinational logic circuits since they define the normal operation of the circuits.

Chapter Review Questions

Answer the following questions.

10-1. Do binary addition problems **a** to **h** (show your work):

a.
$$101 + 011 = e. 1000 + 1000 =$$

b.
$$110 + 101 = f. 1001 + 0111 =$$

c.
$$111 + 111 = g. 1010 + 0101 =$$

- 10-2. Draw a block diagram for a half adder (label two inputs and two outputs).
- 10-3. Draw a block diagram for a full adder (label three inputs and two outputs).
- 10-4. Do binary subtraction problems **a** to **h** (show your work):

a.
$$1100 - 0010 =$$

e.
$$10000 - 0011 =$$

b.
$$1101 - 1010 =$$

c.
$$1110 - 0011 =$$

g.
$$10010 - 1011 =$$

d.
$$1111 - 0110 =$$

- 10-5. Draw a block diagram of a half subtractor (label two inputs and two outputs).
- 10-6. Draw a block diagram of a full subtractor (label three inputs and two outputs).

- 10-7. Draw a block diagram of a 2-bit parallel adder (use a half and a full adder).
- 10-8. Use circuit simulation software to (1) construct a full-adder circuit like the one in Fig. 10-6(a),(2) test the circuit, and (3) show your instructor your circuit and results.
- 10-9. Do binary multiplication problems **a** to **h** (show your work). Check your answers using decimal multiplication.

a.
$$101 \times 011 = e. 1010 \times 011 =$$

b.
$$111 \times 011 = f. 110 \times 111 =$$

c.
$$1000 \times 101 = g$$
. $1100 \times 1000 =$

d.
$$1001 \times 010 =$$
 h. $1010 \times 1001 =$

- 10-10. List two methods of doing binary multiplication with digital electronic circuits.
- 10-11. Convert the following signed decimal numbers to their 4-bit 2s complement form:

a.
$$+1 =$$

b.
$$+7 =$$

c.
$$-1 =$$

d.
$$-7 =$$

Chapter Review Questions...continued

- 10-12. Convert the following 4-bit 2s complement numbers to their signed decimal form:
 - a. 0101 =

c. 1110 =

b. 0011 =

- d. 1000 =
- 10-13. Convert the following 8-bit 2s complement numbers to their signed decimal form:
 - a. 0111 0000

c. 1000 0001

b. 1111 1111

- d. 1100 0001
- 10-14. Convert the following signed decimal numbers to their 8-bit 2s complement form:
 - a. +50

c. -50

b. -32

- d. -96
- 10-15. Add the following 4-bit 2s complement numbers. Give each sum as a *4-bit 2s complement number*. Also give each sum as a signed decimal number.
 - a. 0110 + 0001 =

c. 0001 + 1100 =

b. 1101 + 1011 =

- d. 0100 + 1110 =
- 10-16. Subtract the following 4-bit 2s complement numbers. Give each difference as a 4-bit 2s complement number. Also give each difference as a signed decimal number.
 - a. 0110 0010 =

c. 0010 - 1101 =

b. 1001 - 1110 =

- d. 1101 0001 =
- 10-17. Add the following 8-bit 2s complement numbers. Give the sum in 8-bit 2s complement notation. Also give each sum as a signed decimal number.
 - a. $0001\ 0101 + 0000\ 1111 =$
 - b. $1111\ 0000 + 1111\ 1000 =$

- c. 000011111 + 111111100 =
- d. 1101 1111 + 0000 0011 =
- 10-18. Subtract the following 8-bit 2s complement numbers. Give the difference in 2s complement notation. Also give each difference as a signed decimal number.
 - a. $0111\ 0000 0001\ 1111 =$
 - b. $1100\ 1111 1111\ 0000 =$
 - c. $0001\ 1100 1110\ 1111 =$
 - d. $1111\ 1100 0000\ 0010 =$
- 10-19. See Table 10-1. The problem with the faulty half-adder circuit appears to be in the _____ (C_o , sum) output, which seems to be _____ (stuck HIGH, stuck LOW).
- 10-20. See Table 10-1. In an attempt to repair the faulty half-adder circuit, you might start by substituting a good ______ (AND gate IC, XOR gate IC) and then testing the circuit for correct operation.

Half-Adder Circuit					
Inp	outs	Outpu	its		
В	Α	Sum	CO		
·Langega	ery Landing		Н		
L	Н	Н	Н		
H	日間に智能性	計畫的 并 可能	Н		
ш	Ш	l l	Ы		

Table 10-1 Logic Probe Results on Faulty

Critical Thinking Questions

- 10-1. Draw a logic symbol diagram of a 2-bit parallel adder using XOR, AND, and OR gates.
- 10-2. Draw a logic symbol diagram of a full-subtractor circuit using XOR, NOT, and NAND gates. Use Fig. 10-11 as a guide.
- 10-3. Draw a logic diagram of an 8-bit binary adder using two 7483 4-bit adder ICs.
- 10-4. Convert the signed number +127 to its 8-bit 2s complement form. Remember that the leftmost

- bit will be 0, which means the number is positive.
- 10-5. Convert the signed number -25 to its 8-bit 2s complement form. Remember that the left-most bit will be 1, which means the number is negative.
- 10-6. The 2s complement numbers are widely used in digital systems (such as microprocessors)

Critical Thinking Questions...continued

because they can be used to represent _____ numbers.

- 10-7. Describe how you would form a 2s complement from a binary number.
- 10-8. The negative of a binary number is its _ (2s complement, 9s complement).
- 10-9. Why might we say that decimal 0 would be represented as a positive number in 2s complement notation?
- 10-10. At the option of your instructor, use circuit simulation software to (1) construct a 4-bit binary adder using an adder IC (see Fig. 10-13),

- (2) test the circuit by adding several 4-bit binary numbers, and (3) show your instructor your circuit and results. You may substitute a 4008 CMOS 4-bit adder IC in place of the 7483 TTL IC.
- 10-11. At the option of your instructor, use circuit simulation software to (1) construct an adder/ subtractor system using 2s complement numbers (see Fig. 10-30), (2) test the circuit by adding and subtracting 2s complement numbers (see Figs. 10-26 and 10-27 for samples), and (3) show your instructor your circuit and results.



Answers to Self-Tests

1	1	1	1	0

В	\boldsymbol{A}	Σ	C_o
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

11.
$$t_1$$
: sum = 1, $C_o = 0$
 t_2 : sum = 0, $C_o = 0$
 t_3 : sum = 0, $C_o = 1$
 t_4 : sum = 1, $C_o = 0$

12.
$$C_{in} - \Sigma$$
 $A = FA - C_0$

ο.					
	C_{in}	B	\boldsymbol{A}	S	C_o
	0	0	0	0	0
	0	0	1	1	0
	0	1	0	1	0
	0	1	1	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	1	0	0	1
	1	1	1	1	1

- 14. arithmetic-logic unit (ALU)
- 15. full-adder


16.
$$t_1$$
: sum = 1, $C_o = 1$
 t_2 : sum = 0, $C_o = 1$
 t_3 : sum = 0, $C_o = 1$
 t_4 : sum = 1, $C_o = 0$
 t_5 : sum = 0, $C_o = 1$

$$t_6$$
: sum = 1, $C_o = 0$
 t_7 : sum = 1, $C_o = 0$

$$t_8$$
: sum = 0, C_0 = 0

- 17. half adder, full adders
- 18. combinational
- 19. 1101

20. 1000

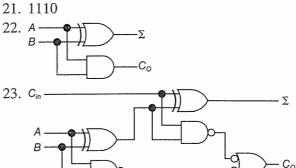

- 24. a. 01
 - b. 10
 - c. 000
 - d. 101
 - e. 1111
 - f. 111
- 25. a. 0101 0100₂, 84₁₀
 - b. 1011 0111₂, 183₁₀
 - c. 1011 1000₂, 184₁₀
 - d. 0100 1110₂, 78₁₀

27.

•	A	B	D_i	B_o
	0	0	0	0
	0	1	1	1
	1	0	1	0
	1	1	0	0

28.
$$B_{in}$$
 FS B_{o}

29.

\boldsymbol{A}	B	B_{in}	$D_{_i}$	B_o
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

- 30. parallel subtractor
- 31. borrow lines
- 32. adder
- 33. cascaded
- 34. combinational

- 35. 74LS181
- 36. 10101
- 37. F
- 38. 1110 1011
- 39. 1 1111 1110
- 40. binary
- 41. 1110
- 42. 1000001
- 43. 1010 1000
- 44. a. 1000 0111₂, 135₁₀
 - b. 0110 0000₂, 96₁₀
 - c. 0111 1001₂, 121₁₀
- 45. repeated addition
- 46. add and shift
- 47. add and shift
- 48. F
- 49. combinational
- 50. multiplicand register multiplier register accumulator register
- 51. 2s complement
- 52. 0111, +7
- 53. -1
- 54. sign, positive, negative
- 55. 1010
- 56. 0101
- 57. 1011, -5
- 58.0010, +2
- 59. 0101 1010, 0101 1010
- 60. 1010 0110
- 61. 0110 1111, +111
- 62. 1000 1111, -113
- 63. 1101 0000, -48
- 64. 0011 0001, +49
- 65. 2s complement
- 66. 2s complement
- 67. signed
- 68.1111, -1
- 69.0011, +3
- 70. 1110, -2
- 71. 1011, -5
- 72. combinational, carry out
- 73. 4, LOW
- 74. T
- 75. Know the normal operation of circuit, feel top of IC, look for broken connections or signs of excessive heat, smell for overheating, check the power sources, trace path of logic, and isolate the faulty section.



Memories

Learning Outcomes

This chapter will help you to:

- 11-1 List and characterize common memory and storage devices used in a microcomputer system. Sketch the general organization of a computer, including CPU, control bus, address bus, data bus, RAM, ROM, NVRAM, and bulk storage memory devices. Associate specific storage devices with their fundamental technology, such as magnetic, mechanical, optical, or semiconductor. Match certain semiconductor memory cell types with specific characteristics and common uses.
- **11-2** Given small semiconductor memory organization, *draw* the memory in table form, *sketch* a logic symbol for the memory, and *explain* the programming of the memory.
- 11-3 Detail the inputs/outputs and predict the operation of a small static RAM IC. Analyze the inputs/outputs and summarize the operation of a larger static RAM.
- **11-4** *Program* a small static RAM with the Gray code.
- **11-5** *Characterize* read-only memories (ROMs). *Analyze* a primitive diode ROM circuit.
- **11-6** *Solve* a counting problem using read-only memory (ROM).
- 11-7 Explain the characteristics of programmable ROMs (such as PROM, EPROM, EEPROM, and flash nonvolatile memory).
- 11-8 Summarize the implementation of nonvolatile read/write memory (such as flash EEPROM, battery backup SRAM, and NVSRAM). Summarize newer non-volatile read/write memory technologies (such as FeRAM and MRAM).
- **11-9** *Identify* several memory packages used in modern computers.
- **11-10** Characterize computer bulk storage devices as to technology (mechanical, magnetic, optical, and semiconductor). Explain advantages of each type of storage device.
- **11-11** Summarize the operation of a digital potentiometer containing NVRAM. Analyze the action of a specific digital potentiometer.

thas been said that the most important characteristic that a digital system has over an analog system is its ability to store data for short or long periods. The availability and use of memory and digital storage devices have fueled what writers have called the *information revolution*. The entire Internet is dependent on the transfer of data from one storage/memory device to another. Of course, computers and telecommunication systems are dependent on large amounts of digital storage.

The *USB flash drive* is one example of an advance in memory technology. The small portable USB flash drive is used by almost everyone. The flash drive does not contain a hard drive but features semiconductor flash memory devices. USB flash drives are commonly available with storage capacities 8, 16, 32, 64, 128, and 256 GB, with larger units available. They have mostly replaced floppy disks. They are also replacing forms of rewritable CD optical storage discs for removable media. Flash drives are portable, rugged, and compatible with computers and other digital devices. Their cost is less than \$2 per gigabyte and decreasing. Flash drives have less storage capacity than external hard drives. It should be noted that flash memory is also employed in many digital devices, including computers, microcontrollers, camcorders, cameras, and game consoles.

The flip-flop, which we have already studied, forms a basic "memory cell" in some *semiconductor memories*. You have already used a simple shift register, latches, and counters, which use the flip-flop as a temporary memory. Several other types of semiconductor memory cells will be

Flash memory

Semiconductor memory investigated in this chapter. Several types of bulk storage devices will also be surveyed. Bulk storage devices are commonly classified as either magnetic, mechanical, optical, or semiconductor in nature.

11-1 Overview of Memory Memory Devices in Computer

The sketch in Fig. 11-1 is an overview of a typical microcomputer system featuring the many types of memory and storage devices used in an everyday machine. The *CPU* is the *central processing unit*, which is the section of a computer or microprocessor that contains the arithmetic, logic, and control sections. The CPU is the focus of most data transfers. Flowing from the CPU in Fig. 11-1 are the *address bus* and *control bus* lines. A *bus* is a group of parallel conductors whose job it is to transfer information to other parts of the computer or microprocessor. The address bus and control bus are one-way communication lines that tell memory, storage, and

other peripheral devices who does what and when. The data bus is a two-way communication channel for sending information to and receiving information from memory, storage, and other peripheral devices. The simplified block diagram in Fig. 11-1 shows some of the common internal semiconductor memory devices used in computers such as the RAM, ROM, and NVRAM. Notice that data from the data bus can flow into (to write in memory) or out of (to read from memory) both random-access memory (RAM) and nonvolatile RAM (NVRAM). The read-only memory (ROM) is different because it is permanently programmed and data can flow out of this semiconductor device only as shown by the arrow in Fig. 11-1. A variety of semiconductor read-only memory devices such as PROMs, EPROMs, or EEPROMs could be substituted for the ROM in this computer system.

Other memory components commonly associated with a modern microcomputer are listed under bulk storage devices in Fig. 11-1. They are divided according to the type of storage

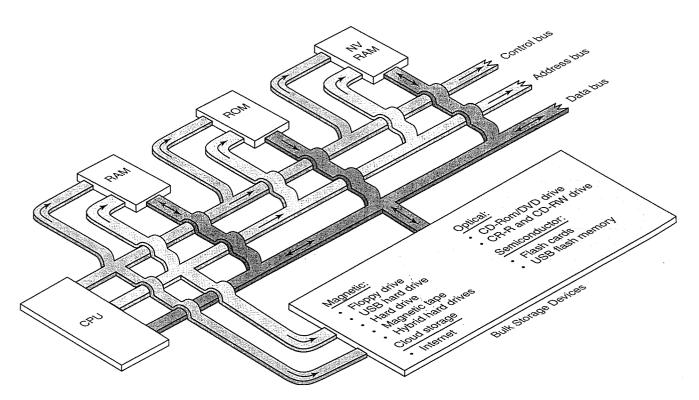


Fig. 33-3 Simplified view of a typical computer system showing types of memory or storage devices.

medium such as magnetic, cloud, optical, or semiconductor.

Magnetic Storage

The hard drive is the most universal magnetic bulk storage device in personal computers. It may also be referred to as a hard disk drive (HDD). Hard drives may also be found in many other digital devices, including camcorders, automobiles, and Internet servers. The hard drive features highly polished rigid disks that spin at high speeds (commonly 7200 rpm). They store data in a thin coating of metal oxide on the surface of the disk. Digital 0s and 1s are represented by the alignment of magnetic domains in one direction or the other in the metal-oxide surface. A write head stores 0s and 1s on the disk, while a read head detects 0s or 1s as the magnetic medium moves at hypersonic speed.

Larger hard disk drives housed in home and school computers may have a capacity of 500 GB (gigabytes) to over a TB (terabyte). To achieve these large capacities, the hard drive mechanism contains many stacked double-sided rigid disks, each with a read/write arm and heads to read and write data. The hard drive mechanism represents extreme precision and is sealed against moisture, smoke, and dust.

Floppy disk drives were standard on many personal computers in the past. The floppy disk material was a flexible plastic coated with a metal oxide. The disk drive would spin the floppy disk and read/write heads would read and write data on the magnetic medium. A typical floppy disk might only have a capacity of 1 to 2 MB.

Optical read/write CDs and USB flash drives have taken over the task of portable data storage because they have greater storage capacities. When larger capacities are required (such as back ups for your computer), then external hard disk drives are common. External hard disk drives usually do not have as large capacities as internal HDDs. External HDDs commonly use the computer's USB port for transferring data.

Internet servers are large-scale computers systems without common user interfaces like keyboards, sound, or monitors. These servers feature high-capacity processors and huge amounts of internal memory. It is common to use stacks of hard disk drives as part of Internet servers.

Optical Storage

Many computer systems contain a CD reader drive capable of reading information from several types of CDs (compact discs). The music industry started using CDs in the early 1980s.

Common optical media include CD-ROM (CD read-only memory), the CD-DA (CD digital audio), CD-R (CD recordable), CD-RW (CD rewritable), and DVD (digital versatile disc). DVDs come in a wide variety including DVD-video (digital video disc), DVD-audio, DVD-ROM, and DVD-RAM.

Manufactured CD-ROM and DVD discs are produced using expensive industrial plastics injection equipment. During manufacture, tiny pits and lands (no pit) are molded into the shiny side of the CD. The CD reader drive aims a laser beam at a track on the spinning CD. The reflected light bounced off the pits and lands are interpreted as logical 0s and 1s.

A high-capacity version of the CD-ROM is the digital versatile disc (DVD). DVDs are most commonly associated with video productions (movies). DVD-video standards are used when the disc holds only audio/video (such as movies). DVD-ROM standards are used when the digital versatile disc is used for data storage as with a computer. The pits and lands are smaller with the DVD, which yields a greater storage capacity than older CD-ROMs. A simple one-sided, single-layer, 4.75-inch DVD has a capacity of about 4.7 GB.

Semiconductor Storage

A single semiconductor type of bulk storage device is listed in the microcomputer system sketched in Fig. 11-1. Flash memories can appear in regular IC packages or in memory card form. A memory card looks something like a thick credit card. Digital cameras commonly use flash memory cards to store photos. A decade ago, flash memories were available only in small sizes, but large-capacity chips have become available. Semiconductor flash memories have become solid-state drives as they replace

the hard drive in some portable computers and other devices such as personal organizers. Flash memories commonly take the form of small *USB flash memory* devices. USB flash memory modules are removable and are commonly used like floppy disks or compact discs.

Semiconductor Storage Cells

Semiconductor storage devices are commonly classified in about six categories: SRAM, DRAM, ROM, EPROM, EEPROM, and flash memory (flash EEPROM). Some of these technologies are better than others for certain jobs in a digital system. Following is a brief description of these technologies:

- SRAM (static random-access memory)—
 high access speed, read or write, requires
 continuous power (volatile memory),
 low density, high cost, associated
 with high-speed cache memory in
 microprocessors.
- DRAM (dynamic random-access memory)—good access speed, read or write, volatile memory plus a need for refresh circuitry, high density, lower cost, RAM type used in most modern PCs.
- ROM (read-only memory)—high density, nonvolatile (cannot be altered), reliable, low cost especially at high volumes.
- EPROM (electrically programmable read-only memory)—high density, non-volatile (can be updated although not easily), ultraviolet light erasable before reprogramming.
- EEPROM (electrically erasable programmable read-only memory)— nonvolatile but electrically erasable by bytes for reprogramming, lower density, high cost.
- Flash Memory—very high density, low power, nonvolatile but rewritable (bit by bit) within the digital system, fairly new and developing technology holding great promise as a solid-state hard drive, can be portable (like floppy disk) in memory card form or USB flash memory.
- FRAM (ferroelectric RAM)—nonvolatile RAM, in-circuit programmable, good access speed (reading and writing), low

- density, high cost, FRAM memory cells based on ferroelectric capacitor and MOS transistor.
- MRAM (magnetoresistive RAM or magnetic RAM)—nonvolatile RAM, incircuit programmable, excellent access speed, high density, nanotechnology used in fabrication; cost has not been determined because it is a new technology.

The diagram in Fig. 11-2 suggests three important characteristics of a semiconductor memory represented by the three large circles: nonvolatility, high density, and the capacity of being electrically updated. Notice in Fig. 11-2 that the flash memory has the best combination of nonvolatility, high density, and read/write capability (electrically updatable). Flash memory is a developing technology, and it can be expected that densities will go up and the price will fall, making the technology widely applied.

Consider the advantage of using flash memory in the system sketched in Fig. 11-1. In a common microcomputer system, the control unit of the computer would direct the disk drive to transfer a file or files to the RAM (probably DRAM in most systems). This takes a bit of time. If the disk drive were replaced with flash memory this seek time (disk-to-DRAM loading) is eliminated making users experience higher-speed operation.

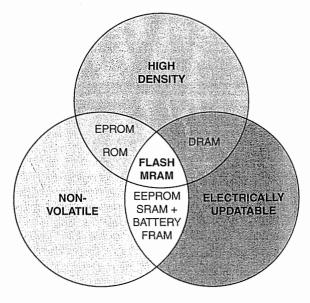


Fig. 11-2 Important semiconductor memory characteristics.



Answer the following questions.

- 1. The section of a computer system that contains the arithmetic, logic, and control section and is the center of many data transfers is called the _____.
- 2. List two one-way buses in a microcomputer system that direct memory, storage, and peripheral devices.
- 3. List three general categories of bulk storage devices based on the technology each uses.
- 4. List at least two bulk storage devices commonly found in microcomputer systems.
- 5. Spell out the full term for each of the following abbreviations.
 - a. RAM
 - b. ROM
 - c. EPROM

- d. EEPROM
- e. SRAM
- f. DRAM
- A DVD is an optical disc that has more storage capacity than a CD-ROM. (T or F)
- 7. A CD writer drive is used on many personal computers to write data on _____ (CD-ROMs, CD-R or CD-RWs).
- 8. Based on the information in Fig. 11-2, which semiconductor memory type would be the best choice if you wanted a nonvolatile memory with read/write capabilities, and high density (memory cells are very small)?



11-2 Random-Access Memory (RAM)

One type of semiconductor memory device used in digital electronics is the random-access memory. The RAM is a memory that you can "teach." After the "teaching-learning" process (called writing), the RAM remembers the information for a while and the RAM's stored information can be recalled, or "remembered," at any time. We say that we can write information (0s and 1s) into the memory and read out, or recall, information. The RAM is also called a read/write memory or a scratch-pad memory.

A semiconductor memory with 64 cells in which to place 0s and 1s is illustrated in Fig. 11-3. The 64 squares (mostly blank) represent the 64 cells that can be filled with data. Notice that the 64 bits are organized into 16 groups called words. Each of the 16 words contains 4 bits of information. This memory is said to be organized as a 16×4 memory. That is, it contains 16 words, and each word is 4 bits long. A 64-bit memory could be organized as a 32×2 memory (32 words of 2 bits each), a 64×1 memory

(64 words of 1 bit each), or an 8×8 memory (8 words of 8 bits each).

The memory in Fig. 11-3 looks very much like a truth table on a scratch pad. On the table

Address	Bit D	Bit C	Bit B	Bit A
Word 0				
Word 1				
Word 2				
Word 3	0	1	1	0
Word 4				
Word 5				
Word 6				
Word 7				
Word 8				
Word 9				
Word 10				
Word 11				
Word 12				
Word 13				
Word 14				
Word 15				

Fig. 11-3 Organization of a 64-bit memory.

Random-access memory

Read/write memory

Memory organization

Write operation

Read operation Address

Volatile memory

Nonvolatile storage devices

after word 3 we have written the contents of word 3 (0110). We say we have stored, or written, a word into the memory; this is the write operation. To see what is in the memory at word location 3, just read from the table in Fig. 11-3; this is the read operation. The write operation is the process of putting new information into the memory. The read operation is the process of copying information from memory. The read operation is also referred to as the sense operation because it senses, or reads, the contents of the memory.

You could write any combination of 0s and 1s in the table in Fig. 11-3 rather like writing on a scratch pad. You could then read any word(s) from the memory, as from a scratch pad. Notice that the information in the memory remains even after it is read. Now it should be obvious why this memory is sometimes called a 64-bit scratch-pad memory. The memory has a place for 64 bits of information, and the memory can be written into or read from very much like a scratch pad.


The memory in Fig. 11-3 is called a random-access memory because you can go directly to

word 3 or word 15 and read its contents. In other words, you have access to any bit (or word) at any instant. You merely skip down to its word location and read that word. A location in the memory, such as word 3, is referred to as the storage location or *address*. In the case of Fig. 11-3, the address of word 3 is 0011_2 (3₁₀). However, the data stored at this address are 0110.

The RAM cannot be used for permanent memory because it loses its data when the power to the IC is turned off. The RAM is considered a *volatile memory* because of this loss of data. Volatile memories are thus used for the *temporary* storage of data. However, some memories are permanent; they do not "forget" or lose their data when the power goes off. Such permanent memories are called *nonvolatile storage devices*.

RAMs are used where only a temporary memory is needed. RAMs are used for calculator memories, buffer memories, and cache memories.

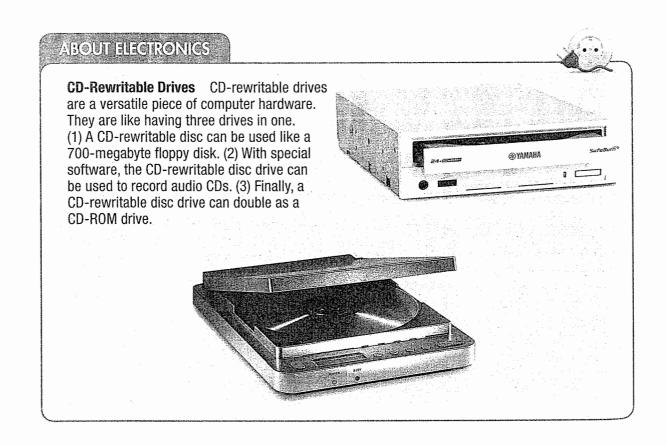Modern personal computers implement random-access memory using both SRAM (static RAM) and DRAM (dynamic RAM).






Self-Test

Supply the missing word or words in each statement.

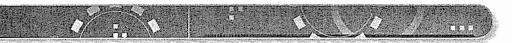- 9. The letters "RAM" stand for
- 10. Copying information into a storage location is called ______ into memory.
- 11. Copying information from a storage location is called _____ from memory.
- 12. A RAM might also called a(n) ______ or scratch-pad memory.
- 13. Refer to Fig. 11-3. This 64-bit unit is organized as a(n) _____ memory.
- 14. A disadvantage of the RAM is that it is _____; it loses its data when the power is turned _____ (off, on).



11-3 Static RAM ICs

The 7489 read/write TTL RAM is a 64-bit data storage unit in IC form. Figure 11-4(a) is a logic symbol for the 7489 RAM. The memory cells are arranged like the layout of the table in Fig. 11-3. The memory can hold 16 words; each word in the 7489 IC is 4 bits wide. The 7489 RAM is said to be organized as a 16×4 -bit memory. A pin diagram for the 7489 IC is given in Fig. 11-4(b).

A simplified truth table for the 7489 RAM is shown in Fig. 11-4(c). The memory enable (\overline{ME}) input is used to "turn on" or "select" the RAM for either reading or writing. The top line in the truth table shows both the \overline{ME} and the write enable (\overline{WE}) inputs LOW. The 4 bits at the data inputs $(D_1$ to D_4) are stored in the memory location selected by the address inputs $(A_3$ to A_0). The RAM is in the write mode.

Let us write data into the 7489 memory chip. Suppose we want to write 0110 into the word 3 location, as shown in Fig. 11-3. The address for word 3 is $A_3 = 0$, $A_2 = 0$, $A_1 = 1$, and $A_0 = 1$. Word 3 is located in the memory by placing a binary 0011 on the address inputs of the 7489 RAM [see Fig. 11-4(a)]. Next, place the correct input data at the data inputs. To enter 0110, place a 0 at input A, a 1 at input B, a 1 at input C, and a 0 at input D. Next, place a LOW at the write enable (\overline{WE}) input. Last, place a LOW at the memory enable (\overline{ME}) input. Data are written into the memory in the storage location called word 3.

Now let us *read*, or *sense*, what is in the memory. If we want to read out the data stored at word 3, we first set the address inputs to

binary 0011 (decimal 3). The write enable (\overline{WE}) input should be in the read position, or HIGH according to the truth table in Fig. 11-4(c). The memory enable (\overline{ME}) input should be LOW. The data outputs will indicate 1001. This output is the *complement* of the actual memory contents, which is 0110. Inverters could be attached to the outputs of the 7489 IC to make the output data the same as that in the memory. This illustrates the use of the *read mode* on the 7489 RAM.

The last two lines in the truth table in Fig. 11-4(c) inhibit both the read and write processes. When both \overline{ME} and \overline{WE} inputs are HIGH, all outputs go HIGH. When the \overline{ME} input is HIGH and the \overline{WE} input is LOW, the outputs are the complement of the inputs, but no reading or writing is taking place.

The 7489 RAM has open-collector outputs. This is suggested by the use of pull-up resistors on the outputs in the diagram in Fig. 11-4(a). A close relative of the 7489 is the 74189 64-bit RAM with the same configuration and pins except its outputs are of the tristate type instead of the open-collector type. A tristate output has three levels: LOW, HIGH, or high impedance.

You will find that although different manufacturers use various labels for the inputs and outputs on this IC, all 7489 ICs have the inputs and outputs shown in Fig. 11-4. IC manufacturers usually include even very small memories like the 7489 RAM in separate data manuals that cover semiconductor memories.

The 7489 RAM is an obsolete IC that is used for experimental purposes in lab experiments to help show how many semiconductor memory 7489 read/write TTL RAM

74189 64 bit RAM

Tristate output

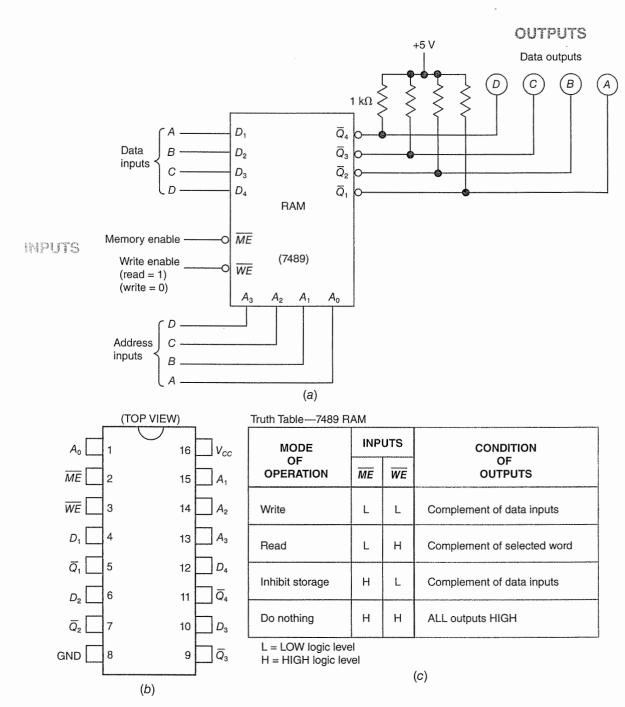


Fig. 11-4 7489 64-bit RAM TTL IC. (a) Logic diagram. (b) Pin diagram. (c) Truth table.

chips are addressed, read from, and written to. Microprocessor-based equipment makes extensive use of semiconductor read/write RAMs in IC form.

Semiconductor RAM ICs are subdivided by manufacturers into static and dynamic types. The *static RAM* stores data in a flip-flop-like element. It is called a static RAM because it holds its 0 or 1 as long as the IC has power. The *dynamic RAM* IC stores its logic state as an electric charge in an MOS device. The stored charge leaks off after a very short time and must

be refreshed many times per second. Refreshing the logic elements of a dynamic RAM requires rather extensive refresh circuitry. Dynamic RAMs come in larger sizes than static RAMs. Dynamic RAMs have the refresh circuitry on the chip. Because of their ease of use, static RAMs will be used in this chapter.

One MOS memory IC is the 2114 static RAM. The 2114 RAM will store 4096 bits, which are organized into 1024 words of 4 bits each. A logic diagram of the 2114 RAM is sketched in Fig. 11-5(a). The 2114 RAM has 10 address

Static RAM 2114 static RAM Dynamic RAM

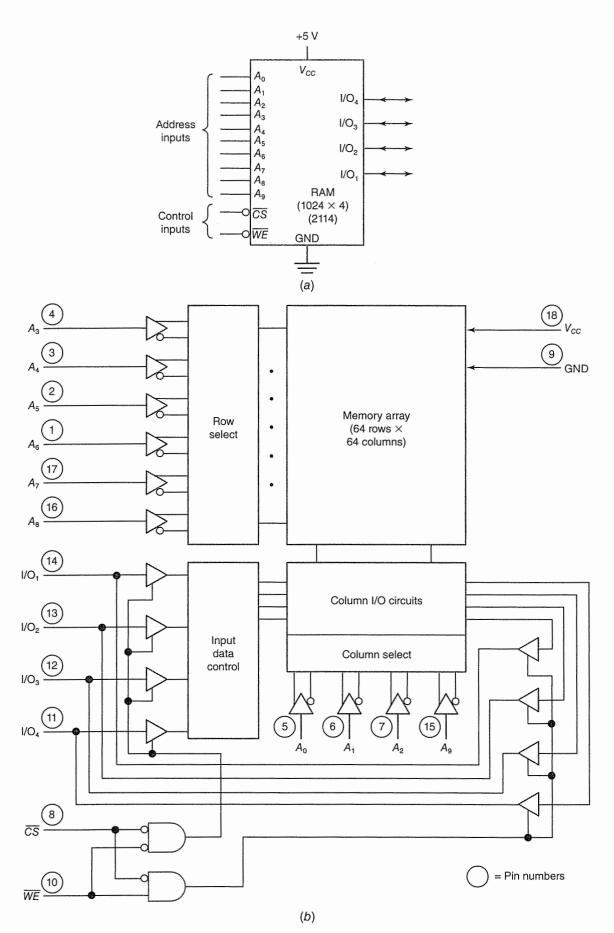


Fig. 11-5 2114 MOS static RAM. (a) Logic diagram. (b) Block diagram of RAM chip.

2114 MDS static RAM. Chip select

Access time

Three-state buffers

lines, which can access $1024~(2^{10})$ words. It has *chip select* (\overline{CS}) and \overline{WE} control inputs. The \overline{CS} input is similar to the \overline{ME} input on the 7489 RAM. The four input/output (I/O₁, I/O₂, I/O₃, I/O₄) pins serve as inputs when the RAM is in the write mode and outputs when the IC is in the read mode. The 2114 RAM is powered by a +5-V power supply.

A block diagram of the 2114 RAM is illustrated in Fig. 11-5(b). Especially note the *three-state buffers* used to isolate the input/output (I/O) pins from a computer data bus. Note that

the address lines are also buffered. The 2114 RAM comes in 18-pin DIP IC form.

An important characteristic of a RAM is its access time. The *access time* is the time it takes to locate and output (or input) a piece of data. The access time of the 7489 TTL RAM is about 33 ns. The access time of the 2114 MOS RAM ranges between 100 and 250 ns depending on what version of the chip you purchase. The TTL RAM is said to be faster than the 2114 memory chip because of its shorter access time.

Supply the missing word in each statement. write) mode. Input data 0011 are being ____ (read from, written into) 16. The 7489 IC is a 64-bit ___ memory location _____ (decimal 17. The 7489 memory IC can hold ____ number). words, each word being _____ bits 19. A_ _ (dynamic, static) RAM wide. must be refreshed many times per second. 18. Refer to Fig. 11-4. If the address inputs = 20. The 2114 RAM IC will store _ 1111, write enable = 0, memory enbits of data, and each of the 1024 words is able = 0, and data inputs = 0011, then bits wide. ___ (read, the 7489 IC is in the __

11-4 Using a SRAM

We need some practice in using the 7489 read/write RAM. Let us *program* it with some usable information. To program the memory is to write in the information we want in each memory cell.

Probably you cannot remember how to count from 0 to 15 in the *Gray code*, so let us take the Gray code and program it into the 7489 RAM. The RAM will remember the Gray code for us, and we can then use the RAM to convert from binary numbers to Gray code numbers.

Table 11-1 shows the Gray code numbers from 0 to 15. For convenience, binary numbers are also included in Table 11-1. The 64 logical 1s and 0s in the Gray code number column of the table must be written into the 64-bit RAM. The 7489 IC is perfect for this job because it contains 16 words; each word is 4 bits long. This is the same pattern we have

in the Gray code column of Table 11-1. The decimal number in the table will be the word number (see Fig. 11-3). The binary number is the number applied to the address input of the 7489 RAM (see Fig. 11-4). The Gray code number is applied to the data inputs of the RAM [see Fig. 11-4(a)]. When the \overline{ME} and \overline{WE} inputs are activated, the Gray code is written into the 7489 RAM. The RAM remembers this code as long as the power is not turned off.

After the 7489 RAM is programmed with the Gray code, it is a *code converter*. Figure 11-6(a) shows the basic system. Notice that we input a binary number. The code converter reads out the equivalent Gray code number. The system is a *binary-to-Gray code converter*.

How do you convert binary 0111 (decimal 7) to the Gray code? Figure 11-6(b) shows the binary number 0111 being applied to the address inputs of the 7489 RAM. The \overline{ME} input is at 0.

Gray code

Programming RAM

Binary-to-Gray code converter

Table 11-1 G	ray Code	
Decimal Number	Binary Number	Gray Code Number
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

The \overline{WE} input is in the read position (logical 1). The 7489 IC then reads out the stored word 7 in inverted form. The four inverters complement the output of the RAM. The result is the correct Gray code output. The Gray code output for binary 0111 is shown as 0100 in Fig. 11-6(*b*). You can input any binary number from 0000 to 1111 and get the correct Gray code output.

The binary-to-Gray code converter in Fig. 11-6 works fine. It demonstrates how you can program and use the 7489 RAM. It is not practical, however, because the RAM is a volatile memory. If the power is turned off for even an instant, the storage unit loses all its memory and "forgets" the Gray code. We say the memory has been *erased*. You then have to again program, or teach, the Gray code to the 7489 RAM.

Each time your home or school computer boots up when it is first started, it loads codes/ programs into its RAM section of memory. This is much like loading the Gray code into the tiny 7489 RAM.

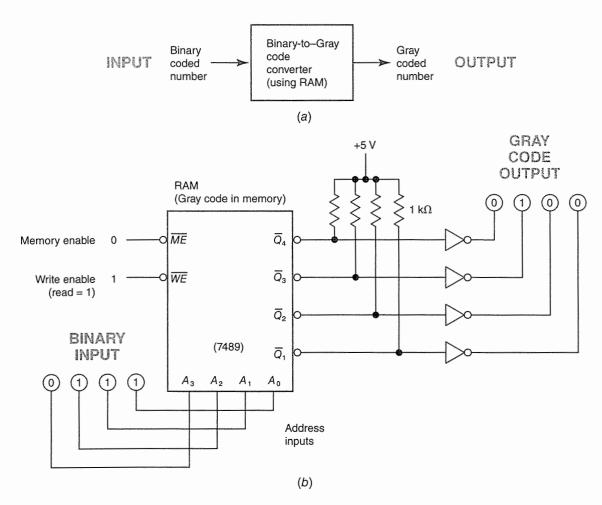


Fig. 11-6 Binary-to-Gray code converter. (a) System diagram. (b) Wiring diagram using RAM.

Supply the missing word or words in each statement.

- 21. Refer to Fig. 11-6. The RAM is programmed as a(n) ____ ____ code converter in this example.
- 22. Refer to Fig. 11-6. If the address inputs = 1000, $\overline{WE} = 1$, and $\overline{ME} = 0$, then the

	output at the displays on the right will be
	This is the code
	equivalent of binary
23.	If power to the 7489 IC in Fig. 11-6 is
	turned off for an instant, the RAM will
	(lose its program and have
	to be reprogrammed, still hold the Gray
	code in its memory cells).



11-5 Read-Only Memory (ROM)

Many digital devices including microcomputers must store some information permanently. This may be stored in a read-only memory or ROM. The ROM is programmed by the manufacturer to the user's specifications. Smaller ROMs can be used to solve combinational logic problems like decoding.

ROMs are classified as nonvolatile memories because they do not lose their data when power is turned off. The read-only memory is also referred to as the mask-programmed ROM. The ROM is used in only high-volume production applications because of the expensive initial setup costs. Programmable read-only memories (PROMs) are used for lower-volume applications where a permanent memory is required.

The primitive diode ROM circuit in Fig. 11-7 can perform the task of translating from binary to Gray code. The Gray code along with decimal and binary equivalents is listed in Table 11-1.

If the rotary switch in Fig. 11-7(a) has selected the decimal 6 position, what will the ROM output indicators display? The outputs (D, C, B, A) will indicate LHLH or 0101. The D and B outputs are connected directly to ground through the resistors and read LOW. The C and A outputs are connected to +5 V through two forward-biased diodes, and the output voltage will read about +2 to +3 V, which is a logical HIGH. Notice that the pattern of diodes in the diode ROM matrix in Fig. 11-7(a) is similar to the pattern of 1s in the Gray code column in Table 11-1. Each new position of the rotary switch will give the correct Gray code output. In a memory, such as the ROM in Fig. 11-7, each position of the rotary switch is referred to as an address.

A refinement in the diode ROM is shown in Fig. 11-7(b). The diode ROM circuit in Fig. 11-7(b) uses a 1-of-10 decoder (7442 TTL IC) and inverters for row selection. This example shows a binary input of 0101 (decimal 5). This activates output 5 of the 7442 with a LOW. This drives the inverter, which outputs a HIGH. The HIGH forward-biases the three diodes connected to the row 5 line. The outputs would be LHHH or 0111. This is the Gray code equivalent for binary 0101 according to Table 11-1.

The diode ROMs suffer many disadvantages. Their logic levels are marginal. The diode ROM also suffers in that it has very limited drive capability. The diode ROMs do not have input and output buffering needed when working with systems that contain data and address buses.

Practical ROMs are available from many manufacturers. These can range from very small bipolar TTL units to quite large capacity CMOS or NMOS ROMs. Commercial ROMs

Read-only memory (RDIVI)


Nonvolatile memories

Mask-programmed ROM Address


1-of-10 decoder

Diode ROM disadvantages

ABOUT ELECTRONICS

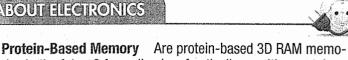

ries in the future? A small cube of optically sensitive protein (such as Rhodopsin), suspended in a transparent plastic, might be the basis for a 20-gigabyte RAM memory. Two laser beams might intersect at a point in the cube of protein to switch that "organic memory cell" from one logic state to another.

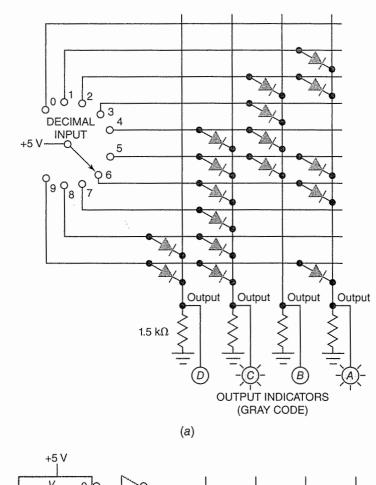

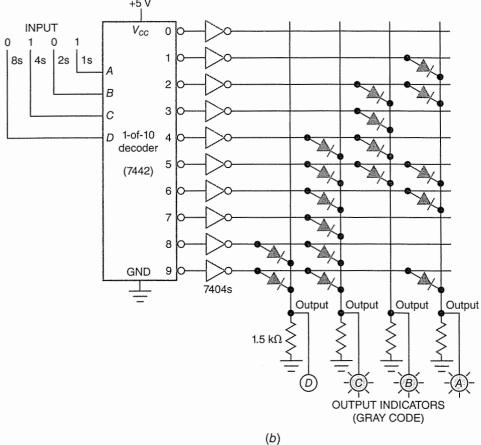


Fig. 11-7 Diode ROMs. (a) Primitive diode ROM programmed with Gray code. (b) Diode ROM with input decoding (programmed with Gray code).


Primitive diade ROM

can be purchased in DIP form. As examples, a very small capacity unit might be the TTL 74S370 2048-bit ROM organized as a 512-word by 4-bit memory. A larger-capacity unit might be CMOS TMS47C512 524,288-bit ROM organized as a 65,536-word by 8-bit memory. The $65,536\times 8$ unit has an access time of from 200 to 350 ns depending on the version you purchase. Personal computers have ROMs of larger capacity.

TMS4764 8192× 8-bit ROM As an example of a commercial product, the TMS4764 ROM will be featured. The TMS4764 is an 8192-word by 8-bit ROM. Its 8192×8 organization makes it useful in systems that might store data in 8-bit groups, or bytes.

A pin diagram for the TMS4764 ROM is reproduced in Fig. 11-8(a). The ROM is housed in a 24-pin DIP. The names and functions of the pins are given in the chart in Fig. 11-8(b). Notice that a total of 13 addresses lines $(A_0 \text{ to } A_{12})$ are needed to address the 8192 (213) memory locations. A_0 is the LSB and A_{12} is the MSB of the word address. The access time of the TMS4764 ROM varies from 150 to 250 ns depending on the version of the chip you purchase. Permanently stored data are output via the pins labeled Q_1 through Q_8 . Q_1 is considered the LSB while \widetilde{Q}_8 is the $\widetilde{\text{MSB}}$. The output pins $(Q_1 \text{ to }$ $Q_{\rm s}$) are enabled by pin 20. Pin 20 may be programmed by the manufacturer to be an active HIGH or active LOW \overline{CS} or \overline{CE} input. When the three-state outputs are disabled, they are in a high-impedance state, which means they may be connected directly to a data bus in a microcomputer system.

Read-only memories are used to store permanent data and programs. Computer system programs, lookup tables, decoders, and character generators are but a few uses of the ROM. ROMs can also be used for solving combinational logic problems. General-purpose microcomputers allocate a larger proportion of their internal memory to RAM. However, dedicated computers allocate more addresses to ROM and usually contain only small amounts of RAM.

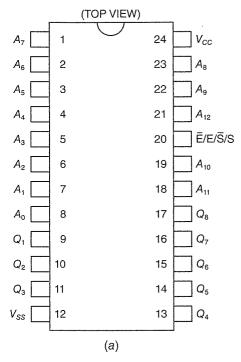

	PIN NOMENCLATURE
A ₀ -A ₁₂	Address inputs
Ē/E/S/S	Chip Enable/Power Down or Chip Select
$Q_1 - Q_8$	Data out
V_{cc}	5-V supply
V_{SS}	Ground
	(b)

Fig. 11-9 TMS4764 ROM IC. (a) Pin diagram. (b) Pin nomenclature.

About 500 different ROMs were available in one recent listing.

A computer program is typically referred to as *software*. However, when a computer program is stored in a ROM, it is called *firmware* because of the difficulty of making changes.

For a summary, look back at Fig. 11-2. Notice that the ROM is a high-density memory device and is nonvolatile. The ROM is a permanent storage device that cannot be reprogrammed.

Software Firmware


-√N- Self-Test

Supply the missing word or words in each statement.

24. The letters "ROM" stand for _____

25. Read-only memories never forget data and are called _____ memories.

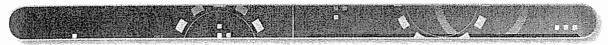- 26. The term _____ is used to describe microcomputer programs that are permanently held in ROM.
- 27. Read-only memories are programmed by the _____ (manufacturer, computer operator) to your specifications.
- 28. A backup battery _____ (is, is not) needed to power the ROM when the computer is turned off so it can retain its programs and data.
- 29. Refer to Fig. 11-7(a). If the input switch is at 3 (binary 0011), the Gray code output will be _____.
- 30. Refer to Fig. 11-7(*b*). If the input is binary 1001, the Gray code output will be _____.
- 31. The typical ROM is a _____ (high-, low-) density memory device.



11-6 Using a ROM

Suppose you have to design a device that will give the decimal counting sequence shown in Table 11-2: 1, 117, 22, 6, 114, 44, 140, 17, 0, 14, 162, 146, 134, 64, 160, 177, and then back to 1. These numbers are to read out on seven-segment displays and must appear in the order shown.

Knowing you will use digital circuits, you convert the decimal numbers to BCD numbers. This is shown in Table 11-2. You find you have 16 rows and 7 columns of logical 0s and 1s. This section forms a truth table. As you look at


the truth table, the problem seems quite complicated to solve with logic gates or data selectors. You decide to try a ROM. You think of the inside of a memory as a truth table. The BCD section of Table 11-2 reminds you that a memory organized as a 16×7 storage unit will do the job. This 16×7 ROM will have 16 words for the 16 rows on the truth table. Each word will contain 7 bits of data for seven columns on the truth table. This will take a 112-bit ROM.

A 112-bit ROM is shown in Fig. 11-9. Notice that it has four address inputs to select one of the 16 possible words stored in the ROM. The 16 different addresses are shown in the left columns of Table 11-3. Suppose the address inputs are binary 0000. Then the first line in Table 11-3 shows that the stored word is 0 000 001 (a to g). After decoding in Fig. 11-9, this stored word reads out on the digital displays as a decimal 1 (100s = 0, 10s = 0, 1s = 1).

Let us consider another example. Apply binary 0001 to the address inputs of the ROM in Fig. 11-9. The second row on Table 11-3 shows us that the stored word is 1 001 111 (a to g). When decoded, this word reads out on the digital display as decimal 117 (100s = 1, 10s = 1, 1s = 7). Remember that the 0s and 1s in the center section of Table 11-3 are *permanently* stored in the ROM. When the address at the left appears at the address input of the ROM, a row of 0s and 1s (7-bit word) appears at the outputs.

You have solved the difficult counting sequence problem. Figure 11-9 diagrams the basic system to be used. The information in Table 11-3 shows the addressing and programming of the 112-bit ROM and the decoded BCD as a decimal readout. You would give the information

Table	11-2 Co	unting	Sequence P	roblem				
Deci	mal Read	out		Binary-Coded Decimal Number				
100s	10s	1s	100s	10s	1s			
	1	1	0	000	001			
1	1 -	7	1	001	111			
	2	2	0	010	010			
		6	0	000	110			
1	1	4	. 1	001	100			
	4	4	0	100	100			
1	4	0	1	100	000			
	1	7	0	001	111			
		0	0	000	000			
	1	4	0	001	100			
1	6	2	1	110	010			
1	4	6	1	100	110			
1	3	4	1	011	100			
	6	4	0	110	100			
1	6	0	1	110	000			
1	7	7	1	111	111			

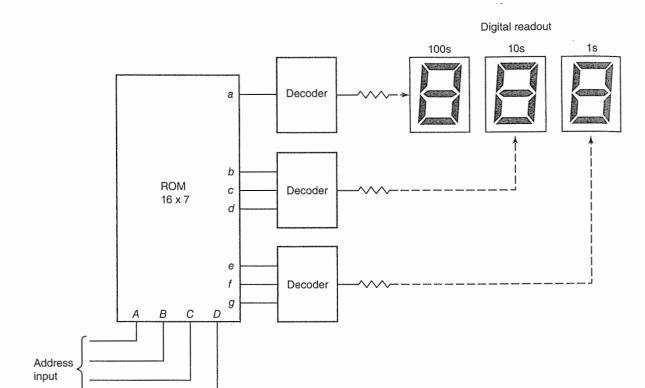

Using a ROM

Fig. 11-9 System diagram for the counting sequence problem using a ROM.

Table	11 E111	aunting	Sequen	ce Proble	m,								
	Inp	uts		ROM Outputs									
	Addre	ss or		100s 10s 1s				Decimal					
Word Location			1s	4s 2s 1s 4s		2s	1s Readout						
D	С	В	Α	а	b	С	d	е	f	g	100s	10s	1 s
0	0	0	0	0	0	0	0	0	0	1			1
0	0	0	1	1	0	0	1	1	1	1	1	1	7
0	0	1	0	0	0	1	0	0	1	0		2	2
0	0	1	1	0	0	0	0	1	1 .	0			6
0	1	0	0	1	0	. 0	1	1	0	0	1	1	4
0	1	0	1	0	1	0	0	1	0	0		4	4
0	1	1	0	1	1	0	0	0	0	0	1	4	0
0	1	1	1	0	. 0	0	. 1	1	1	1		1	7
1	0	0	0	0	0	0	0	0	0	0			0
1	0	0	1	0	0	0	1 :	1 .	0	0		. 1	4
1	0	1	0	1	1	1	0	0	1	0	1	6	2
1	0	1	1	1	1	0	0	1	1	0	1	4	6
1	1	0	0	1	0	1	1	1	0	0	1	3	4
1	1	0	1	0	1	1	0	1	0	0		6	4
1	1	1	0	1	1	1	0	0	0	0	1	6	0
1	1	1	1	1	1	1	1	1	1	1	1	7	7

in Table 11-3 to a manufacturer, who would custom-make as many ROMs as you need with the correct pattern of 0s and 1s.

It is quite expensive to have just a few ROMs custom-programmed by a manufacturer. You probably would not use the ROM if you did not have need for many of these memory units. Remember that this problem also could have been solved by a combinational logic circuit using logic gates.

Semiconductor memories usually come in 2^n sizes or 64-, 256-, 1024-, 4096-, 8192-bit, and

larger units. A 112-bit memory is an unusual size. The 112-bit memory was used in the example because its truth table in Table 11-3 is exactly the truth table of the 7447 IC. You used the 7447 IC as BCD-to-seven-segment decoder earlier. You will want to use the 7447 IC as a ROM in the laboratory.

Read-only memories are used for encoders, code converters, lookup tables, microprograms, character generators, function generators, microcomputer system firmware, and microcontroller firmware.

-M- Self-Test

Supply the missing word or words in each statement.

- 32. Refer to Fig. 11-9. If power is turned off and then back on, the counting sequence programmed into the ROM will _____ (be lost from, remain in) memory.
- 33. Refer to Table 11-3 and Fig. 11-9. If the ROM address input = 1111, the digital readout will be ______.
- 34. Refer to Table 11-3 and Fig. 11-9. If the ROM address input = 1001, the digital readout will be ______.
- 35. A mask-programmable ROM is programmed by the _____ (manufacturer, user).
- A group of programs and data held permanently in a microcomputer's
 ———— (RAM, ROM) would be called firmware.



11-7 Programmable Read-Only Memory [PROM]

Mask-programmable ROMs are programmed by the manufacturer using photographic masks to expose the silicon die. *Mask-programmable ROMs* have long development times, and the initial costs are high. Mask-programmable ROMs are usually simply called ROMs.

Field-programmable ROMs (PROMs) are also available. They shorten development time and many times lower costs. It is also much easier to correct program errors and update products when PROMs can be programmed (burned) by the local developer. The regular PROM can only be programmed once, but its advantage is that it can be made in limited quantities and can be programmed in the local lab or shop. The PROM is also called a fusible-link PROM.

The EPROM (erasable programmable read-only memory) is a variation of the PROM. The EPROM is programmed or burned in the local lab using a PROM burner. If an EPROM needs to be reprogrammed, a special window on the top of the IC is used. Ultraviolet (UV) light is directed at the chip under the window of the EPROM. The UV light erases the EPROM by setting all the memory cells to a logical 1. The EPROM can then be reprogrammed. A 24-pin EPROM DIP IC is shown in Fig. 11-10. The actual EPROM chip is visible through the window on top of the IC. These units are sometimes called UV erasable PROMs or UV EPROMs.

The *EEPROM* is a third variation of a programmable read-only memory. The EEPROM is an *electrically erasable PROM* also referred to as an E^2PROM . Because EEPROMs can be erased electrically, it is possible to erase and

EPROM (erasable programmable read-only memory)

PROM burner

Maskprogrammable ROMs

Field-programmable RDMs (PROMs)

EEPROM

Electrically erasable PRDM

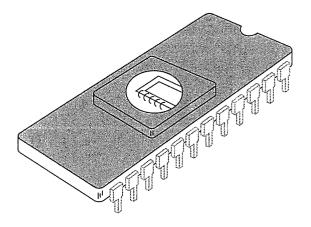


Fig. 11-10 EPROM. Note window in top used to erase EPROM with ultraviolet light.

reprogram them without removing them from the circuit board. The EEPROM can be reprogrammed one byte at a time.

The *flash EEPROM* is a fourth variation of a programmable read-only memory. The newer flash EEPROM is like an EEPROM in that it can be erased and reprogrammed while on the circuit board. Flash EEPROMs are gaining favor because they use a simpler storage cell, thereby allowing more memory cells on a single chip. We say they have greater density. Flash EEPROMs can be erased sector by sector and reprogrammed faster than EEPROMs. While parts of the code can be erased and reprogrammed on an EEPROM, the entire flash EEPROM must be erased and reprogrammed.

The basic idea of a PROM is illustrated in Fig. 11-11. This simplified 16-bit (4×4) PROM is similar to the diode ROM studied in the previous section. In Fig. 11-11(a), each memory cell contains a diode and a good fuse. This indicates that all of the memory cells are storing a logical 1. This is how the PROM might look before programming.

The PROM in Fig. 11-11(b) has been programmed with seven 0s. To program or burn the PROM, tiny fuses must be blown as shown in Fig. 11-11(b). A blown fuse in this case disconnects the diode and means a logical 0 is permanently stored in this memory cell. Because of the permanent nature of burning a PROM, the unit cannot be reprogrammed. A PROM of the type illustrated in Fig. 11-11 can only be programmed once.

A popular *EPROM family* is the *27XXX* series. These are available from many manufacturers. A short summary of some models in the

Table 11-4	27XXX Series EPR	OMs
EPROM 27XXX	Organization	Number of Bits
2708	1024 × 8	8192
2716	2048×8	16384
2732	4096 × 8	32768
2764	8192 × 8	65536
27128	16384×8	131072
27256	32768×8	262144
27512	65536 × 8	524288

27XXX series is shown in Table 11-4. Notice that they are all organized with byte-wide (8-bit-wide) outputs, making them compatible with many digital systems. Many versions of each of these basic numbers are available such as low-power CMOS units, EPROMs with different access times, and even pin-compatible PROMs, EEPROMs, and ROMs.

A sample IC from the 27XXX series EPROM family is illustrated in Fig. 11-12. The pin diagram in Fig. 11-12(a) represents the 2732A 32K $(4K \times 8)$ ultraviolet-erasable PROM. The 2732 EPROM has 12 address pins $(A_0 \text{ to } A_{11})$ which can access 4096 (212) byte-wide words in the memory. The 2732 EPROM uses a 5-V power supply and can be erased using UV light. The CE input is like the chip select CS inputs on some other memory chips. The \overline{CE} input is activated with a LOW. The \overline{OE}/V_{PP} pin serves a dual purpose. It has one purpose during reading and another during writing. Under normal use the EPROM is being read. A LOW at the output enable $(O\bar{E})$ pin during a memory read activates the outputs driving the data bus of the computer system. The eight output pins are labeled O_0 to O_7 on the 2732 EPROM. A block diagram is drawn in Fig. 11-12(b) to show the organization of the 2732 EPROM chip.

When the 2732 EPROM is erased, all memory cells are returned to logical 1. Data are introduced by changing selected memory cells to 0s. The 2732 is in the *programming mode* (writing into the EPROM) when the dual-purpose \overline{OE}/V_{PP} input is at 21 V. During programming (writing), the input data are applied to the data output pins $(O_0$ to O_7). The word to be programmed into the EPROM is addressed using the 12 address lines. A very short (less than 55 ms) TTL

Flash EEPROM

2732A 32K (4K × 8) ultraviolet-erasable PROM

Erasing the UV EPROM

"Burning" a PROM

EPROM family 27XXX-series


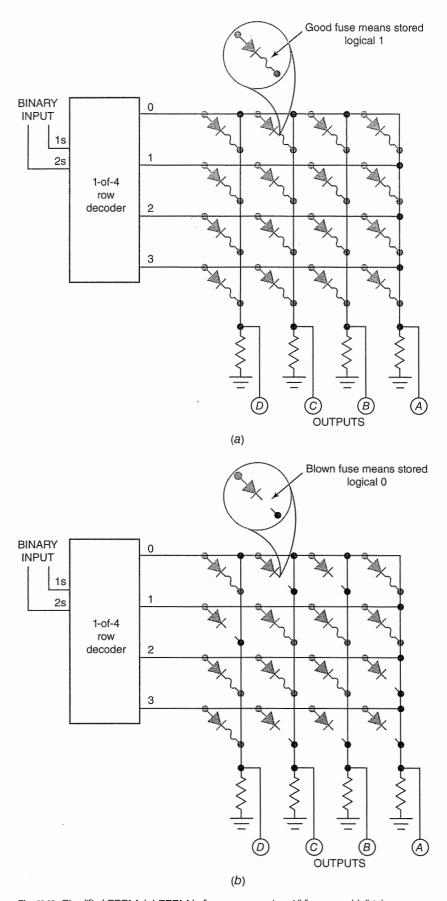


Fig. 11-17 Simplified PROM. (a) PROM before programming. All fuses good (all 1s).
(b) PROM after programming. Seven fuses blown (seven Os programmed).

Simplified PROM

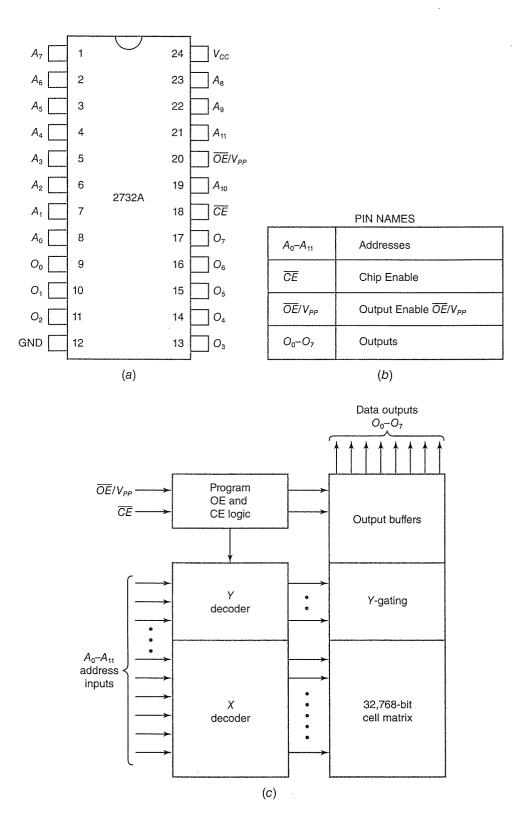

2732 EPROM IC

Fig. 11-12 2732 EPROM IC . (a) Pin diagram. (b) Pin names. (c) Block diagram.

level LOW pulse is then applied to the \overline{CE} input to complete the write process.

Programming an EPROM is handled by special equipment called PROM burners. After erasing and reprogramming, it is common to protect the EPROM window (see Fig. 11-10)

with an opaque sticker. The sticker over the EPROM window protects the chip from UV light from fluorescent lights and sunlight. The EPROM can be erased by direct sunlight in about one week or room-level fluorescent lighting in about three years.



Self-Test

Supply the missing word or words in each statement.

- 37. The letters "PROM" stand for _____
- 38. The letters "EPROM" stand for _____
- 39. The letters "EEPROM" stand for
- 40. Erasing EPROMs can be done by shining _____ light through a special window in the top of the IC.
- 41. See Table 11-4. The 27512 EPROM can store a total of ______ bits of data organized as _____ words, each 8 bits wide.



11-8 Nonvolatile Read/ Write Memory

Both static and dynamic RAMs have the disadvantage of being volatile. When power is turned off, the data are lost. To solve this problem, nonvolatile read/write memories were developed. These are currently implemented by (1) using battery backup for a CMOS SRAM, (2) using a nonvolatile static RAM (NVSRAM), (3) using a flash EEPROM or flash memory, or (4) newer FRAM (ferroelectric random-access memory).

The new MRAM features high speed, high density, nonvolatility, low power, and endurance (unlimited reads and writes).

Battery Backup SRAM

Battery backup is a common method of solving the volatility problem of a SRAM. CMOS RAMs are used with battery backup systems because they consume little power. A long-life lithium battery is typically used to back up data on the CMOS SRAM. Backup batteries have a life expectancy of about 10 years and may be embedded in the memory package. Under normal operating conditions, the SRAM is powered by the equipment's power supply. When the power supply voltage drops to some predetermined lower level, voltage-sensing circuitry switches to backup battery power to maintain the contents of the SRAM until power is restored. Battery backup SRAMs are common in microcomputer systems.

Battery backup SRAM is sometimes referred to as BBSRAM. BBSRAM currently dominates the market. BBSRAM is commonly used,

but some battery-free applications in medicine, aerospace, and distance data logging don't require batteries that may go dead. BBSRAM also has lower data retention than other NVS-RAM devices. Some alternatives to BBSRAM such as NVSRAM, FRAM, and MRAM provide improved access times (they are faster).

NVSRAM

Nonvolatile RAMs can solve the volatility problem. The nonvolatile RAM may be referred to as NVRAM (nonvolatile RAM), NOVRAM (nonvolatile RAM), NVSRAM (nonvolatile static RAM). The NVRAM combines the read/ write capabilities of a SRAM with the nonvolatility of an EEPROM. A block diagram of a small NVSRAM is detailed in Fig. 11-13. Note that the NVSRAM has two parallel memory arrays. The front array is a SRAM, while the back is a shadow EEPROM. During normal operation, the read/write SRAM is used. When the power supply voltage drops, a duplicate of all data in the SRAM is automatically stored in the nonvolatile EEPROM array. The store operation is represented in Fig. 11-13 with an arrow pointing toward the EEPROM array. On powerup, the NVSRAM automatically executes the recall operation, which copies all data from the EEPROM to the SRAM. The recall operation is symbolized in Fig. 11-13 by the arrow pointing toward the front static RAM array.

NVSRAMs seem to have a slight advantage over battery backup SRAMs. NVSRAMs have better access speed and generally better overall life. NVSRAM ICs are smaller than the more bulky battery backup SRAM packages and therefore save PC board space. Currently,


Nonvolatile read/ write memories

Battery backup SRAM

NVSRAM NVSRAM

Battery backup of

CMOS SRAM

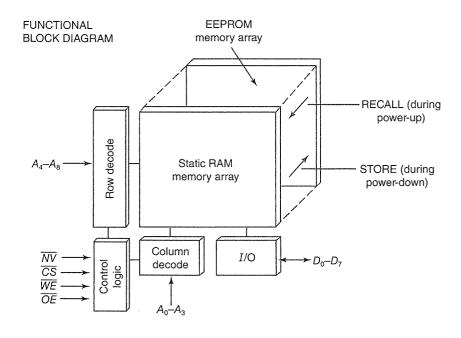

PIN NAMES

A ₀ A ₈	Address inputs	
D ₀ D ₇	Data I/O	
cs	Chip Select	
NV	Nonvolatile Enable	

WE	Write Enable	
ŌĒ	Output Enable	
V _{cc}	+ 5 volts <u>+</u> 10%	

Fig. 11-13 Block diagram and pin names on a typical NVSRAM.

NVSRAMs are more expensive and are manufactured in limited sizes.

Flash memory Flash EEPROM

Flash Memory

Flash EEPROMS may become a low-cost alternative to battery backup SRAMs and NVSRAMs. Flash memories are widely used in laptop computers.

The commercial flash memory by Intel is featured in Fig. 11-14. Intel's $28F512 \ 512K \ (64K \times 8) \ CMOS \ flash \ memory$ will store 524,288 (2¹⁹) bits organized into 65,536 (2¹⁶) words, each 8 bits wide. The block diagram and pin descriptions in Fig. 11-14 give an overview of the flash memory. The 28F512 flash memory reacts like a read-only memory when the V_{pp} erase/program power supply pin is LOW. When the V_{pp} pin goes HIGH (about +12 V), the memory can be quickly erased or programmed based on commands sent to the command register by the attached microprocessor or microcontroller. The 28F512 flash memory uses a 5-V supply to power the chip,

but +12 V is required at the V_{PP} pin during erasing and programming.


In summary, flash EEPROMs or flash memories are an emerging memory technology which will become even more popular in the future. Flash memories have many desirable characteristics including being nonvolatile, in-system rewritable (read/write), highly reliable, and having low power consumption. Flash memories currently boast high densities (the single transistor storage cells are very tiny). Recent developments by Intel suggest that even higher densities will be available in flash memories.

Ferroelectric RAM

Ferroelectric RAM (FeRAM or FRAM) is a high-speed memory similar to SRAM or DRAM, but it is nonvolatile. The FRAM is faster than flash EEPROM memory. The FRAM does not require constant battery power like SRAM with battery backup. Low power consumption makes the ferroelectric RAM an

Internet Connection

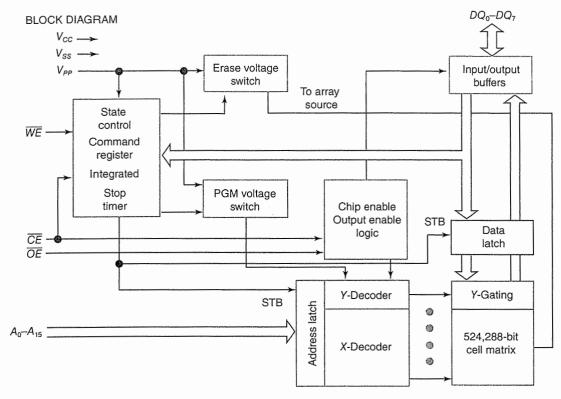Explore Ramtron International's site at www.ramtron.com.



PIN DIRETIONS

Symbol	Туре	Name and Function
A ₀ -A ₁₅	INPUT	ADDRESS INPUTS for memory addresses. Addresses are internally latched during a write cycle.
DQ ₀ -DQ ₇	INPUT/OUTPUT	DATA INPUT/OUTPUT: Inputs data during memory write cycles; outputs data during memory read cycles. The data pins are active high and float to tristate OFF when the chip is deselected or the outputs are disabled. Data is internally latched during a write cycle.
CE	INPUT	CHIP ENABLE: Activates the device's control logic, input buffers, decoders and sense amplifiers. \overline{CE} is active low; \overline{CE} high deselects the memory device and reduces power consumption to standby levels.
ŌĒ	INPUT	OUTPUT ENABLE: Gates the device's output through the data buffers during a read cycle. \overline{OE} is active low.
WE	INPUT	WRITE ENABLE: Controls writes to the command register and the array. Write enable is active low. Addresses are latched on the falling edge and data is latched on the rising edge of the \overline{WE} pulse. Note: With $V_{PP} \le 6.5$ V, memory contents cannot be altered.
V _{PP}		ERASE/PROGRAM POWER SUPPLY for writing the command register, erasing the entire array, or programming bytes in the array.
V _{cc}		DEVICE POWER SUPPLY (5 V ± 10%)
V _{SS}		GROUND
NC		NO INTERNAL CONNECTION to device. Pin may be driven or left floating.

Fig. 11-14 Block diagram and pin descriptions for 28FS12 S12K CMOS flash memory. (Courtesy of Intel Corporation.)

28F512 flash memory IC

excellent choice for portable digital devices. A semiconductor memory like the FRAM may be integrated into microcontrollers and other chips with a few added manufacturing steps. The FRAM memory cell consists of a *ferroelectric capacitor* and MOS transistor. The ferroelectric capacitors (memory cells) do not all need

to be periodically refreshed as in the popular DRAM. A FRAM memory cell *needs refreshing only after a read* of a specific cell.

Currently, ferroelectric RAM densities are somewhat low and prices are high. However, FRAM technology is fairly new, and it is expected that densities will increase and prices

Internet Connection

Find MRAM info at www.freescale.com.



Operation, applications, and benefits of Nanotube RAM (NRAM) are at www.nantero.com. will fall. A major developer and manufacturer of FRAMs is Ramtron International.

Magnetoresistive RAM


Magnetoresistive RAM (MRAM) is an emerging semiconductor memory technology. Magnetoresistive RAM has wonderful characteristics combining the access speed of the SRAM, the density of the DRAM, and the nonvolatility of flash EEPROM memory. The MRAM's small memory cell is based on a single transistor and a magnetic tunnel junction (MTJ) structure.

The cell changes resistance representing different logic states (0 or 1). The MRAM has fast read and write speeds. The MRAM has almost unlimited read and write cycles and has low power requirements. MRAM is compatible with CMOS processes, allowing processors (such as a microcontroller) and memory to be fabricated on the same chip. Some sources suggest that MRAM has the potential to be a "universal semiconductor memory." MRAM is sometimes also referred to as magnetic random-access memory.

Supply the missing word or words in each statement.

- 42. The abbreviation "NVRAM" stands for
- 43. Battery backup SRAMs commonly use a _____ (carbon-zinc, lithium) battery, which has a long life and maintains the data in the memory when power is lost.
- 44. A NVSRAM contains a static RAM array and a shadow _____ (EEPROM, ROM) memory array.
- 45. During power-up using a NVSRAM, the _____ (recall, store) operation automatically occurs, duplicating all the data from the EEPROM into the SRAM memory array.
- 46. Refer to Fig. 11-14. The 28F512 flash memory can be erased/reprogrammed when +12 V is applied to the ______ pin of the IC.

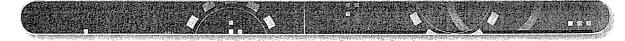- 47. The _____ (ROM, flash memory) has high density, is reliable, and is rewritable.
- 48. The ______ (SRAM, PROM) is a read/write memory that is quite expensive and very fast.
- 49. Flash EEPROMs are a good substitute for a ROM but cannot replace DRAMs because they are not rewritable. (T or F)
- 50. The new ______ (MRAM, ZDRAM) has the potential of replacing many types of semiconductor memory because it is fast, low power, high density, has good endurance, and is nonvolatile.
- 51. In semiconductor memory jargon, the acronym MRAM stands for _____
- 52. In semiconductor memory jargon, the acronym FeRAM stands for ______
- 53. The flash EEPROM is like a SRAM because it is high density, low speed, and a volatile semiconductor memory. (T or F)



11-9 Memory Packaging

A general evolution of memory packaging is depicted in Fig. 11-15. The dual in-line package (DIP) is represented in Fig. 11-15(a). The dual in-line package is the traditional IC package. DIPs occupy a fair amount of surface area on a printed circuit board. The DIP sketched in Fig. 11-15(a) may be either a surface-mount or a through-the-hole type. Small-outline ICs (SOIC) are smaller and reduce the board area

used by the DIP package. In less complex systems (such as microcontroller-based PC boards), DIPs in SOIC form are mounted directly on the main PC board. In larger systems (such as microcomputers), DIP memory ICs are not mounted directly on the main motherboard. Memory modules (boards holding many DIP SOIC memory ICs) are inserted into sockets on the computer's motherboard.

Two types of memory modules used on some older computers are represented in Fig. 11-15(b)

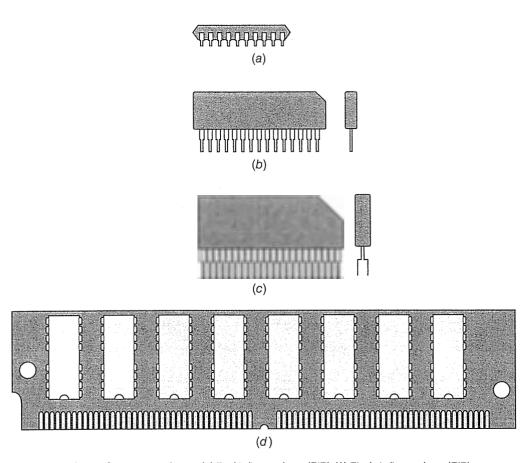


Fig. 11-15 Evolution of memory packages. (a) Dual in-line package (DIP). (b) Single in-line package (SIP). (c) Zig-zag in-line package (ZIP). (d) Single in-line memory module (SIMM).

and (c). These packages are the SIP (single inline package) and the ZIP (zig-zag in-line package). These may be found in older equipment, but not used in new designs.

Some older microcomputers may have SIMM memory modules. The older memory module sketched in Fig. 11-15(d) is a 72-pin SIMM (single in-line memory module). Notice the 72 contacts on the bottom edge of the SIMM. These contacts are located on only one side of the SIMM. An earlier version of this type of memory module was the 30-pin SIMM. Notice the notches on the left side and bottom of the SIMM in Fig. 11-15(d). These notches help the technician install the SIMM in the socket properly.

Newer microcomputers commonly use memory modules that look something like the DIMM (dual in-line memory module) depicted in Fig. 11-16(a). This is a 168-pin DIMM memory module. The DIMM sketched in Fig. 11-16(a) has 84 contacts on each side of the bottom

edge of the pc board for a total of 168 pins. Installation of a typical DIMM is depicted in Fig. 11-16(b). Notice the tabs at each end of the socket. These units help lock the memory module in place when it is pressed firmly downward in the socket, or the levers act as ejectors when removing a seated DIMM. Notice also the notches along the bottom of the memory board in Fig. 11-16(b). These notches slide over solid raised areas in the center of the DIMM socket. This allows the DIMM to fit into the socket in only one direction and ensures the correct memory module is installed.

The DIMM shown in Fig. 11-16(c) is a 184-pin DDR SDRAM (double data rate synchronous DRAM). Currently, the DDR SDRAM is a popular memory module used in PCs. Also widely used in PCs is the 184-pin RDRAM (Rambus DRAM). RDRAM is sometimes referred to as RIMM by its manufacturer Rambus, Inc. The 184-pin RDRAM physically looks somewhat different from the DDR SDRAM,

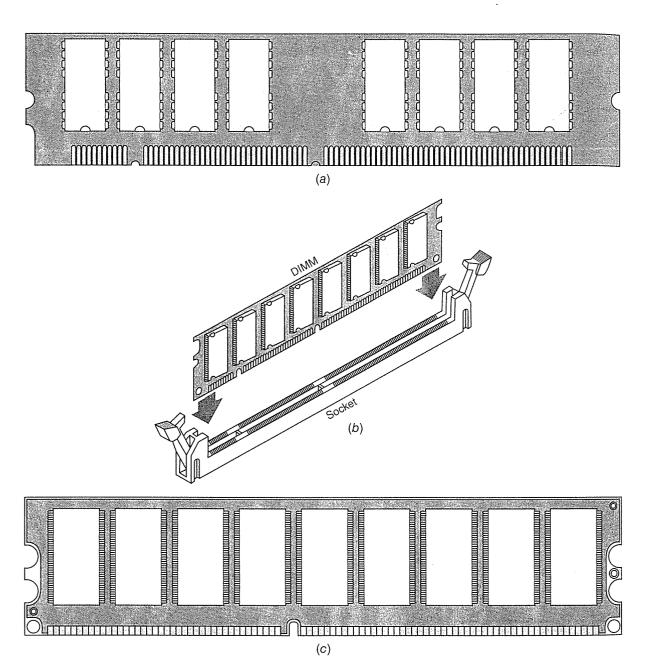


Fig. 11-16 DIMM memory modules. (a) 168-pin DIMM with SDRAM. (b) Installing DIMM in socket. (c) 184-pin DIMM with DDR SDRAM.

and its lower-edge notches have different locations. The 184-pin RDRAM and DDR SDRAM cannot be interchanged because the mother-boards are designed for one style or the other DIMM. A larger-capacity DIMM used in some PCs might be the 240-pin DDR2 SDRAM.

Portable computers use memory modules that are smaller than those pictured in Fig. 11-16. These look different physically. Some DDR SDRAM modules used in laptops might be the small outline 200-pin SO-DIMM or 172-pin micro-DIMM.

DIMMs have many variations including different physical sizes, voltages, speeds, and memory capacities. Replacement or added memory modules *must be ordered for your specific computer*.

Another packaging method is the memory card. The *Personal Computer Memory Card International Association (PCMCIA)* defines standard physical and electrical characteristics of the PCMCIA card. This memory card is about the width and length of a standard credit card; its thickness varies (in four thicknesses)

Internet Connection

Search about installing RAM in a laptop.

from about 3 to 19 mm. The memory card can house arrays of memory chips and other electronics using almost any type of memory device (PROM, DRAM, battery-backed SRAM, flash EEPROM, and so on). The flash memory card is very popular because of its very high density, low power consumption, read/write capabilities, nonvolatility, and modest cost. A PCMCIA device containing flash memory would probably be referred to as a flash memory card. The memory card enables a method of adding memory to laptop and palmtop computing devices or even a copier. Large-capacity flash memory cards can be used as solid-state disk drives. The standard PCMCIA memory card has an edge connector with 68 pins, which are assigned tasks (address lines, data lines, power supply, ground, and so forth). The 68pin PCMCIA memory card allocates 26 pins for address lines, which allows addressing of a large memory ($2^{26} = 64 \text{ MB}$). You should show

some caution when plugging in a memory card because other standards are used, such as the PCMCIA 88-pin interface, the Panasonic 34-pin interface, the Maxwell 36- or 38-pin interface, the Epson 40- or 50-pin interface, and others.

A disk drive is an electromagnetic device that consumes much power and can mechanically wear, thereby causing problems. Disk drives are particularly vulnerable to shock, vibration, dust, and dirt. The *solid-state disk* using flash memory cards or similar devices that appear in portable computers and other equipment must be very small. They use very little power, and withstand shock and vibration. In a *solid-state computer*, the traditional DRAM and magnetic drive combination would be replaced by some fast SRAM and flash memory. The SRAM/ flash memory combination is very fast when transferring data from the solid-state disk to RAM.

-\h- Self-Test

Answer the following questions.

- 54. The memory package in Fig. 11-15(*a*), which is the most traditional, is called the _____(DIP, SIP, ZIP).
- 55. The acronym DIMM stands for what when referring to a computer memory module package?
- 56. The acronym DDR SDRAM stands for what when referring to computer memory modules?
- 57. The acronym SIMM stands for what when referring to computer memory modules?

- 58. The acronym RDRAM stands for what when referring to computer memory modules?
- 59. DIMMs have many variations including different physical sizes, voltages, speeds, and memory capacities. (T or F)
- 60. The letters "PCMCIA" stand for what when referring to a memory card?
- 61. A PCMCIA flash memory card is about the size of a thick _____ (credit card, 5.25-in. floppy disk).
- 62. All memory cards follow the PCMCIA 68-pin standard for electrical connections and physical dimensions. (T or F)

11-10 Computer Bulk Storage Devices

Generally, semiconductor memories are used for internal storage in most modern computers. The computer's internal storage is also called *primary storage*. It is not possible to store all data inside the computer itself. For instance, it is neither necessary nor desirable to store last month's payroll information inside the computer after the checks are printed and cashed. Thus most data are stored outside the computer. External storage is also called *secondary storage*. Several methods are used to

Computer bulk storage devices

Secondary storage Primary storage Magnetic disks

Rigid or floppy disk

Mechanical bulk storage

Hollerith card code



UP-to-date information about hard drives is at www.seagate.com.

Magnetic bulk storage

store information for immediate and future use by a computer. External storage devices are usually classified as either *mechanical*, *magnetic*, *optical*, or *semiconductor*.

Mechanical Devices

Mechanical bulk storage devices include the punched paper card and punched or perforated paper tape. The punched card was developed before 1900 by Herman Hollerith, who adapted them for use in the 1890 United States census. These cards commonly have holes punched in them to represent alphanumeric data. The code used is called the Hollerith card code. A typical Hollerith punched card is made of heavy paper and measures about 3.25×7.5 in. A common punched card can hold 80 characters. Punched paper cards are now obsolete.

Perforated paper tape was another method of mechanically storing data. The paper tape is a narrow strip of paper with holes punched across the tape at places selected according to a code. The paper tape can be stored on reels. This method is also obsolete.

Magnetic Devices

Common *magnetic bulk storage* devices are the magnetic tape, the magnetic disk, and the magnetic drum. Each device operates much like a common tape recorder. Information is recorded (stored) on the magnetic material. Information can also be read from the magnetic material.

Magnetic tape has been widely used for many years as a secondary storage medium. It is still very popular for backing up data because it is quite inexpensive. The main disadvantage of magnetic tapes is that they are sequential-access devices. That is, to find information on the tape, you must search through the tape sequentially, which makes the access time long.

Magnetic drum memory units were used in early computer systems (1950s and 1960s). They featured a spinning magnetic iron-oxide-coated metal drum. Read/write heads recorded and detected binary data. Unlike magnetic tape, drum memory units featured shorter access time because they were random-access devices. Magnetic drum memory was used to store both programs and data (primary storage) before semiconductor memories were available. Drum memory is now obsolete.

Magnetic disks have become particularly popular in recent years. Magnetic disks are random-access devices, which means that any data can be accessed easily and in a short time. Magnetic disks are manufactured in both *rigid* and *floppy* (flexible) disk form. The floppy disk was a popular form of secondary storage used by many microcomputers.

The popular rigid magnetic disk has been combined with very fast nonvolatile RAM (such as flash RAM) to produce hybrid RAM disks. These hybrid hard disk drives (H-HDD) feature increased speed of access and decreased power consumption. Regular hard drives spin the rigid disks continuously, whereas the H-HDD start and stop the platters. Many data transfers to and from the hybrid disk drive use the nonvolatile RAM section. The rigid disk only spins up when needed and then goes to rest as it spins down. Some drawbacks of the hybrid hard disk drives include cost, noise (spin-up and spindown times), and reduced lifetime.

Hard Disks

The hard disk or rigid disk drive is currently the most important bulk storage memory device used on modern computer systems. One of the original sealed dust-free hard disk drives was developed by IBM and was referred to as a Winchester drive (after famous 30-30 Winchester rifle—30 MB with 30-ms access time). The hard disk has proved to be reliable, fast, and today has a very large storage capacity. A picture of a modern hard disk drive by Seagate Technology is reproduced in Fig. 11-17. The cover has been removed from this normally

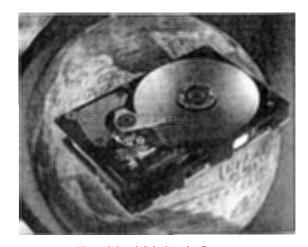


Fig. 11-17 A Cheetah hard disk drive by Seagate.

sealed unit to expose four 3.5-in. rigid disks (called platters) made of aluminum, glass, or ceramic. The platters are probably coated with a thin-film medium, which is a microscopic layer of metal bonded to the disk. The hard drive featured in Fig. 11-17 has eight read/write heads (only one is visible), one on each side of the four platters. When the platters spin, the read/write heads float just above the surface of the disk. The read/write arm pivots to locate a specific circular track on the surface of the platters. The spindle speed on many hard drives is 3600 rpm or faster. Seagate Cheetah hard drives similar to the one pictured in Fig. 11-17 have spindle speeds of 10,000 or 15,000 rpm. The higher spindle speed allows the read/write heads to locate data more quickly.

The specification sheet for a hard disk drive gives information, such as the total storage capacity, number and size of platters, number of read/write heads, average seek time (read/write), average latency, spindle speed, physical dimensions, power requirements, and operating temperatures. The organization of the data on the disks might be given as the number of sectors (a sector commonly holds 512 or multiples of 512 bytes of data plus other information such as an address), number of tracks (concentric circles of data), or number of cylinders (like the number of tracks but three-dimensional, including both sides of all of the platters).

The hard drive pictured in Fig. 11-17 is designed to function as internal storage in a computer system. Currently, internal hard drives in modern PCs have storage capacities ranging from about 100 GB to 3 TB. A portable hard drive, such as the pocket hard drive sketched in Fig. 11-18, is a popular choice. The pocket hard drive unit has a storage capacity of 5 GB

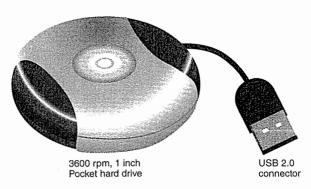


Fig. 11-18 Pocket hard drive.

to 1 TB. It is shirt pocket size, weighing only a few ounces. It has a built-in retractable connector, which can be hot-plugged into a USB port on your PC with data transfers up to 480 Mbps. The pocket hard drive (Fig. 11-18) is powered by the USB port. Other portable hard drives are available, but they are larger in size and may require separate power supplies.

Floppy Disks

Floppy disks were an important portable magnetic storage device. They were read from and written to by a floppy disk drive. For over 50 years they came in 8-in., 5.25-in., and more recently 3.5-in. diameters. A decade ago all home, school, and small business microcomputers featured built-in floppy disk drives. The later 3.5-in. floppy disks had a storage capacity of about 1.4 to 2.0 MB. Floppy disks are still used on many types of older equipment. USB floppy disk drives are available if you choose to use floppy disks for portable storage in newer computer systems. Better portable storage options are available, including USB flash drives, portable external HDDs, optical discs, and memory cards.

A diagram of a common 3.5-in. floppy disk is shown in Fig. 11-19. The drawing shows the bottom view of the disk. It labels the rigid plastic case as well as the sliding metal shutter, both of which help protect the delicate floppy disk housed inside. The sliding metal shutter is shown open, exposing the floppy disk. When released, the cover snaps back to cover the floppy disk inside. The read/write heads of the disk drive can store or retrieve data from both sides of the floppy disk. The center has a metal hub attached to the bottom of the floppy for gripping the disk. The write-protect notch is located at the lower right in Fig. 11-19. If the write-protect hole is closed (as shown in the drawing), you can both write to or read from the disk. If the hole is open (move plastic slider down), the drive can only read the disk; we say that the disk is "write-protected."

Optical Discs

The *optical disc* has become one of the most familiar bulk storage devices used with modern personal computers. Optical disc technology is popular because it is (1) reliable, (2) high capacity, (3) transportable, and (4) inexpensive.

Optical disc

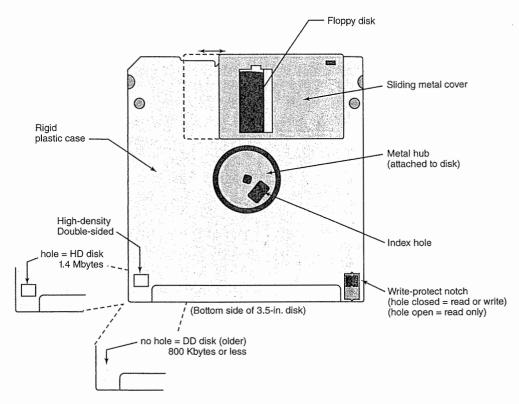


Fig. 11-19 A 3.5-in. floppy disk.

Optical discs are available in many forms and

formats including the popular CD-ROM (com-

pact disc read-only memory), CD-R (compact

disc recordable), and CD-RW (compact disc

rewritable). Newer high-capacity optical discs

include the DVD-ROM (digital versatile disc read-only memory), DVD-R (digital versatile

disc recordable), DVD-RW (digital versatile disc

rewritable), and DVD+RW (another version of

digital versatile disc rewritable). Optical discs are commonly available in the usual 120 mm

(about 4.72 in.)—and the smaller 80 mm (about

3.15 in.)—size. Besides being used for storing

computer data, optical discs are also commonly

The CD was first developed for audio and

CD-ROM

Data transfer rate

then adapted for computer use in the CD-ROM form in the mid-1980s. The CD-ROM is manufactured using a carefully prepared glass master. The master is pressed into injection-molded

used for storing audio and video.

ter. The master is pressed into injection-molded clear polycarbonate plastic, forming the CD-ROM. The resulting CD-ROM contains small pits and lands (no pits). A sketch of a CD-ROM is shown in Fig. 11-20(a). When read by the computer system's CD-ROM drive, a laser is

aimed at the disc from the bottom, and the re-

flection from the pits and lands on the platter

are interpreted by a photodetector and digital circuitry as logical 0s and 1s.

The data transfer rate of a CD-ROM drive is indicated by the manufacturer with a designation such as $1\times$, $2\times$, $16\times$, or $32\times$. A CD-ROM drive with a $1\times$ designation would have a maximum data transfer rate of 150 KB per second. Therefore, a $16\times$ drive would have a maximum data transfer rate of 2400 KB per second (150 KB/s \times 16 = 2400 KB/s or 2.4 MB/s). These data transfer speeds are maximums, and the real data transfer rates are usually less. Currently new PCs are equipped with CD-drives rated at $48\times$ or higher.

The CD-ROMs modern counterpart is the DVD-ROM. CDs and DVDs look alike, both being plastic discs measuring 120 mm in diameter and 1.2 mm in thickness. They both are manufactured using the same technology and read data from a spiral track of pits and lands. The DVD-ROM has a greater storage capacity. A single-layer DVD-ROM can store about seven times more data than the older CD-ROM. The pits and lands on the DVD-ROM are more closely packed, as suggested in the sketch in Fig. 11-20(b) comparing the pit sizes and track pitch (width) for a CD-ROM and for a

DVDs

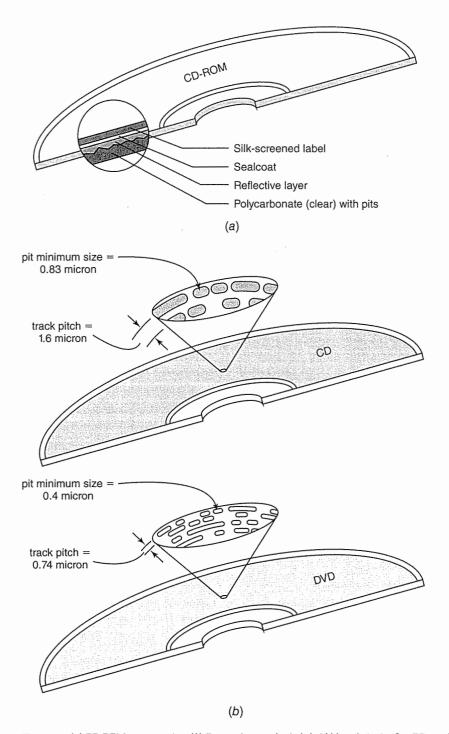


Fig. 11-20 (a) CD-ROM construction. (b) Comparing track pitch (width) and pit size for CDs and DVDs.

DVD-ROM. The tracks on the DVD-ROM are spaced closer together allowing more tracks per disk. The pits and lands are also much smaller. Currently many CD drives have lasers that can read either CD-ROMs or the higher-capacity DVDs. CD drives that can read DVDs will commonly have a DVD logo imprinted on the front.

DVD-ROMs can store 4.7 GB (single-sided, single layer), or 9.4 GB (double-sided, single

layer), or 8.5 GB (single-sided, double layer), or 17 GB (double-sided, double layer) compared to 0.65 GB for a standard CD-ROM. DVD-ROM drives provide a data transfer rate of 1.385 MB per second. This means that a DVD-ROM drive rated at 1× would transfer data at about the same rate as a 9× CD-ROM drive.

CD-R (CD-recordable) discs are popular for permanently storing data (archival storage). CD-Rs are write-once read-many (WORM)

CD-R

storage devices where the PC operator can "burn" a CD-R using a CD-writer drive. Before burning a CD-R disc, the reflective surface appears to a CD reader as a continuous land (no pits). During the burning process a laser heats a gold reflective layer and a dye layer in the CD-R causing it to have a duller appearance. The reflective layer may be gold or silver while the dye layer may be gold, green, or blue depending on the manufacturer. When read by the CD-R drive, the dark burned areas (like the pits on a CD-ROM) reflect less light. The shiny areas (lands) and the dull areas (burned) are interpreted as logical 0s and 1s by the CD-R reader and digital circuitry. The CD-R disc can be burned only once. Most CD-Rs are formatted to have a capacity of about 650 MB.

CD-RW (CD-rewritable) discs were an earlier alternative to floppy disks because of their high capacity and read/write capability. CD-RW discs are sometimes referred to as erasable-CDs or CD-Es. CD-RWs can be rewritten 1000 times or more. When burning a CD-R, the photosensitive dye is permanently changed. When burning a CD-RW, the recording layer (silver-indium-antimony-tellurium alloy) can be recorded and rerecorded, making it rewritable. The recording layer alloy is either very reflective in its polycrystalline state or dull in it amorphous state (like the lands and pits on a CD-ROM). The CD-R/CD-RW drive uses a laser to identify the reflective and dull areas on the CD-RW interpreting them as logical 0s and 1s. Many CD-ROM drives also read CD-Rs and CD-RWs.

Three high-capacity DVD versions of the CD-RW are emerging. They are the *DVD-RW*, DVD+RW, and DVD-RAM. The DVD-RAM disks were developed earlier but were not very compatible with other CD-RW/DVD products. The DVD-RAM with caddy looks like a large floppy disk. DVD-RW (formerly known as DVD-R/W) and DVD+RW discs use phasechange technology for reading, writing, and erasing information. During writing the laser heats a phase-change alloy so it is either crystalline (reflective) or amorphous (dark, nonreflective). The resulting difference between the reflective and dark areas on the disc can be read by a photodetector and interpreted as logical 0s or 1s. DVD+RW discs are more compatible with both the consumer electronics and personal computer environments, which is important in multimedia applications.

It is expected that various forms of optical discs will be used for computer, audio, and video storage for decades due to their reliability, high capacity, low cost and transportability.

USB Flash Memory

The USB flash drive (also known as a USB flash memory stick) has become an important storage device replacing the floppy disk and optical disc for many purposes. A typical USB flash drive is sketched in Fig. 11-21. This unit features 64 MB of flash memory with the common USB standard type A plug. This unit also has an LED indicator showing when the drive is active. Most USB flash drives provide a method of covering the USB plug, such as the cap sketched in Fig. 11-21. The graphic shown on the top of the flash drive housing in Fig. 11-21 is a standard icon used to label USB ports and devices. For most applications, the flash drive draws its power from the computer's USB port and therefore needs no battery.

The USB flash drive is somewhat misnamed because it does not contain any moving parts (as in a hard drive or an optical drive). It is a solid-state flash memory device with appropriate digital interface circuitry. The flash memory is based on EEPROM memory cells. USB flash drives have greater capacity than either a floppy disk or optical disc. USB flash drives are available in capacities from 4 MB to 1 TB. The cost of USB flash drives continues to drop dramatically. The access times and data transfer rates are superior to either the floppy disk or optical disc storage units. The maximum transfer speed of a USB 2.0 port might be as high as 480 MB per second, while newer

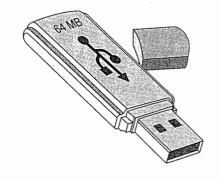


Fig. 11-21 USB flash drive featuring 64 MB of memory and a USB standard type A plug.

CD-RW



Connection

Look for information on the holographic versatile disc (HVD).

Phase-change technology

USB 3.0 ports may have data transfer rates almost 5 GB per second.

USB flash drives are also known as memory sticks and key, pen, thumb, finger, or jump drives. USB flash drives are used with many digital devices including all computers (desktops, laptops, notebooks), some games, phones, and instrumentation.

Access Time

Various bulk storage devices are compared on an access time/storage capacity basis in Fig. 11-22. Whereas access time is given in seconds, storage capacity is graphed in MB. Access time is the time in seconds it takes to retrieve a piece of data from memory. The highest-performance (shortest access time) device on the chart is the flash memory card.

Mechanical methods of storing data (paper tape and punched cards) have the lowest performance and, as such, have been phased out for most applications. Magnetic tape and digital audiotape (DAT) have poor access time but have very large storage capacity at low cost. Hard disks are extremely popular because of their ease of use, large storage capacities, good

access times, reasonable cost, and universal usage. Floppy disks were popular because they are easy to use, are available for a very low cost, are portable, have medium access times, and were used universally.

Optical discs, such as CD-ROMs, CD-Rs, and CD-RWs, have become standard bulk storage media on personal computers. The higher-capacity versions of optical discs, such as DVDs, have gained popularity. Optical storage is popular because of high storage capacities, low cost, transportability, and reliability.

Semiconductor memory used for external storage is shown in Fig. 11-22 to have great speed and storage capacity characteristics. The USB flash drive would be one such storage device that has become extremely popular. A hybrid hard disk drive (H-HDD) is a recent type of hard drive that contains both a traditional hard disk drive with nonvolatile semiconductor memory. The H-HDD would then have the characteristics of a hard drive for some applications. For most routine data transfers, the H-HDD increases its access speed by using the nonvolatile semiconductor memory.



Explore cloud storage.

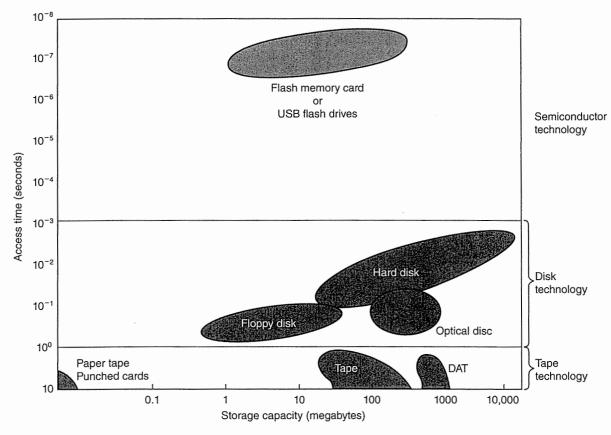


Fig. 11-22 Comparison of several bulk storage devices.

-√- Self-Test

72. The _____ (USB flash drive, mag-Answer the following questions. netic tape) is a bulk storage device that 63. External computer bulk storage devices is low cost, reliable, high capacity, and can be classified as mechanical, transportable. ., _____, or __ 73. The popular digital video disc is referred 64. List several computer bulk storage to as a DVD. The acronym DVD also devices. stands for ______ 65. Magnetic disks are manufactured in both floppy (flexible) and _____ (amor-74. Both CDs and DVDs are classified as phous, rigid) form. ____ (mechanical, optical) bulk 66. The most important bulk storage device storage devices. used in almost all computer systems is the 75. The acronym WORM stands for what in _(magneto-optical disk drive, reference to an optical disc? hard disk drive). 76. The acronym CD-RW stands for what in _ (floppy disk, rigid disk) 67. The _____ reference to an optical storage disc? is faster and has much greater storage _____(CD-ROM, CD-RW) disc capacity. is manufactured with small pits and lands 68. Refer to Fig. 11-17. The rigid disks are which are interpreted by the CD drive as commonly called ___ _ (platters, logical 0s and 1s. spindles) on this disk drive. 78. Floppy disks have lost favor because 69. A gigabyte equals _____ bytes. they feature low-storage capacities and 70. A Winchester drive was an early name for _ (slower, very fast) access times. _ (optical disc drive, hard 79. Hard disk drives are not used in modern disk drive) developed by IBM. computers. (T or F) 71. Modern personal computers are being 80. Optical discs come in a wide variety of shipped with hard disk drives have storage forms to store video, audio, or digital



data. (T or F)

11-11 Digital Potentiometer: Using NV Memory

250 GB and up).

Many products and electronic devices contain embedded semiconductor memory. One such device is the *digital potentiometer* or *solidstate potentiometer*.

capacities of about _____ (30 MB,


Recall that a regular potentiometer, sketched in Fig. 11-23(a), is an analog device. If the wiper is moved over the resistive element, the measured resistance between the wiper and the bottom terminal *gradually changes*. If the resistance of the fixed element is $1 \text{ k}\Omega$, then the measured resistance between points A and B can be any value between 0 and $1 \text{ k}\Omega$.

The concept of a digital potentiometer is shown in Fig. 11-23(b). Here the fixed resistive

element is ten $100-\Omega$ resistors wired in series. The entire resistive element equals $1 \text{ k}\Omega$. The wiper in this model can only connect to the ends of the resistors. Therefore, as you move the wiper upward from the bottom of the digital potentiometer, the measured resistance jumps in discrete steps $(100-\Omega)$ steps in this case). For instance, the ohmmeter could read only in discrete steps of 0, 100, 200, 300, 400, 500, 600, 700, 800, 900, or 1000 ohms.

The block diagram for a digital potentiometer is sketched in Fig. 11-24(a). The DIP pin diagram with pin descriptions is detailed in Fig. 11-24(b). These are diagrams for the *DS1804 NV trimmer potentiometer IC* or digital potentiometer by Dallas Semiconductor. Notice the three outputs labeled H, L, and W much like those on

Solid-state potentiometer

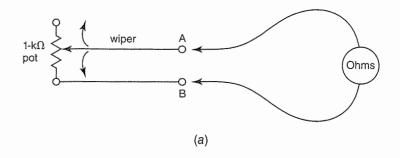

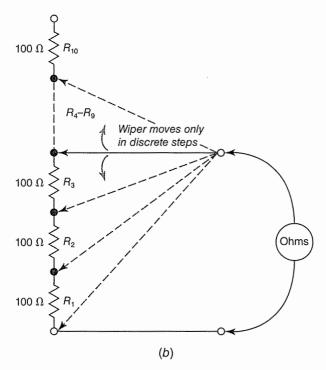


Fig. 11-23 (a) Analog output from a potentiometer. (b) Digital output from solid-state potentiometer (10 steps, 100 Ω each).

a regular potentiometer. On the output side of the block diagram shown in Fig. 11-24(a), note that the DS1804 IC contains series resistances labeled R_1 through R_{99} . The W (wiper) output of the digital potentiometer can be connected to one of 100 different points on the series ladder of resistances. These are labeled position 0 through position 99 on the block diagram. If this unit is a 100-k Ω potentiometer, then each series resistance will be 1 k Ω . If the wiper were at position 1, then the resistance between outputs L and W will be 1 k Ω . If the wiper were at position 98, then the resistance between outputs L and W will be 98 k Ω .

When the DS1804 IC, shown in Fig. 11-24, is first powered up, an *initial wiper position*, stored in nonvolatile EEPROM, is automatically loaded into the control logic section of the

chip. This is passed to the multiplexer to locate the starting position of the wiper. The wiper position can be altered by applying signals to the inputs $(\overline{CS}, \overline{INC}, \text{ and } U/\overline{D})$.

Consider changing the wiper position of the DS1804-100 IC (100-k Ω digital pot) using the logic diagram in Fig. 11-25. The first example [Fig. 11-25(a)] shows a LOW at the chip select (\overline{CS}) input and a HIGH at the up/down (U/\overline{D}) input. This will allow the wiper position to move upward one position for each negative pulse entering the increment (\overline{INC}) input. In this example, three negative pulses enter the \overline{INC} input; therefore, the wiper will move upward three positions from its initial setting. In this example each position is 1 k Ω ; therefore, the three pulses will increase the resistance between outputs L and W by 3 k Ω .

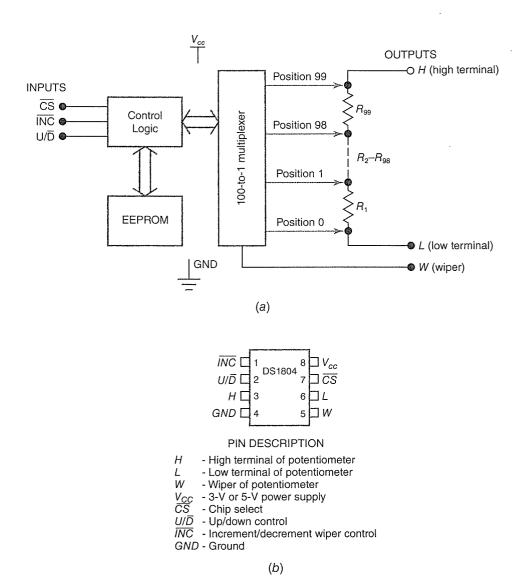


Fig. 11-24 (a) Block diagram of DS1804 digital potentiometer. (b) Pin diagram and pin descriptions for DS1804 digital potentiometer (DIP IC). (Courtesy of Maxim Integrated Products.)

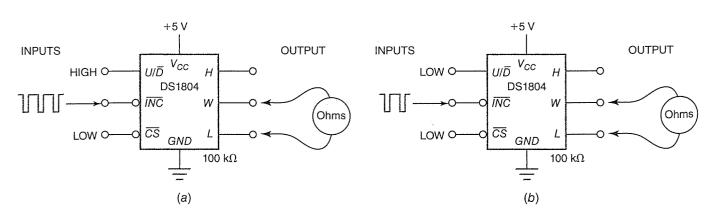


Fig. 11-25 Changing the wiper position on the DSI804-100 digital potentiometer.

Disabling the chip select input (\overline{CS} = HIGH) will disable all inputs to the DS1804 IC. This allows for one-time programming (OTP) of the chip. With the \overline{CS} input HIGH, the EEPROM is not written to during power-down. The EEPROM still holds the last programmed wiper position, and this position is read from the nonvolatile memory during power up.

A second example is shown in Fig. 11-25(b). This example shows the chip select (\overline{CS}) input activated with a LOW, and the up/down (U/\overline{D}) input is LOW selecting the down mode. Two negative pulses are entering the \overline{INC} pin of

the IC. This would cause the wiper position to decrease by two, which decreases the resistance from outputs W to L by $2~\mathrm{k}\Omega$.

The last wiper position is stored in EEPROM using the \overline{INC} and \overline{CS} inputs. Storage of the wiper position occurs whenever the \overline{CS} input changes from LOW to HIGH while the \overline{INC} input is HIGH. The DS1804 IC can accept at least 50,000 writes to EEPROM before a wear-out condition occurs. After wear out, the DS1804 will still function, and the wiper position can be changed when the IC is powered. However, after wear out, the wiper position may be random on power-up.

-∖N- Self-Test

Answer the following questions.

- 81. The DS1804 IC is described by the manufacturer as a(n) ______ also sometimes known as a solid-state potentiometer.
- 82. Refer to Fig. 11-24(a). During power-up (power first turned on to IC), the initial position of the wiper is retrieved from _____ (RAM, EEPROM) and the _____ (multiplexer, XOR gate) adjusts the wiper to stored wiper position.
- 83. Refer to Fig. 11-26. Assume the initial output resistance is 50 k Ω . The measured output resistance after input pulse t_1 is _____ ohms.

- 84. Refer to Fig. 11-26. The measured output resistance from the DS1804 IC after input pulse t_2 is ______ ohms.
- 85. Refer to Fig. 11-26. The measured output resistance from the DS1804 IC after input pulse t_2 is ______ ohms.
- 86. Refer to Fig. 11-26. The measured output resistance from the DS1804 IC after input pulse t_4 is _____ ohms.
- 87. Refer to Fig. 11-26. The measured output resistance from the DS1804 IC after input pulse t_s is ______ ohms.
- 88. Refer to Fig. 11-26. The measured output resistance from the DS1804 IC after input pulse t_s is ______ ohms.


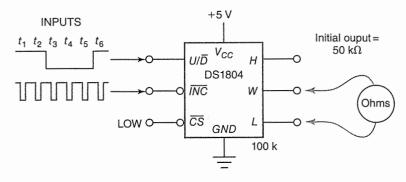


Fig. 11-26 Digital potentiometer pulse-train problem.

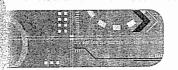



Chapter 11 Summary and Review

Summary :

- 1. The availability of memory and data storage is why many electronic devices are designed using digital instead of analog circuitry.
- Internal memory devices in a computer are usually in the form of RAM, ROM, and NVRAM. The CPU also contains other smaller memory devices like registers, counters, and latches.
- External bulk storage devices are commonly classified as to their basic technology: magnetic, mechanical, optical, or semiconductor.
- 4. Bulk storage devices include floppy disks, hard disks, magnetic tape, CD-ROMs, DVDs, and flash memory modules.
- 5. Semiconductor storage cells are classified as SRAM, DRAM, SDRAM, ROM, EPROM, EEPROM, flash EEPROM, MRAM, and FRAM. Some important characteristics of semiconductor memory devices are density, reliability, cost, power consumption, read only or read/write, nonvolatile/ volatile, and electrically updatable.
- 6. A RAM is a semiconductor read/write randomaccess memory device. RAM comes in two primary forms including SRAM (static RAM) and DRAM (dynamic RAM). Faster SRAM and slower DRAM are both classified as volatile memory.
- 7. A ROM is considered a permanent storage unit that has a read-only characteristic.
- 8. A PROM operates like a ROM. PROMs are onetime write devices. PROMs come in many varieties, generally known as EPROM, EEPROM, and NVSRAM. These "E" prefixed PROMs can be erased electrically or by shining ultraviolet light through a special transparent "window" on the top of the IC.
- 9. The write process stores information in the memory. The read, or sense, process detects the contents of the memory cell.

- 10. NVRAM (nonvolatile RAM) is implemented in microcomputers using SRAM with battery backup, flash EEPROM, FRAM (ferroelectric RAM), or the newer MRAM (magnetoresistive RAM).
- 11. A flash memory is a low-cost EEPROM that can be quickly erased and reprogrammed while in the circuit. Flash memory chips can be packaged as removable flash memory cards or as USB flash drives.
- Computer external storage methods include magnetic tapes, floppy disks, rigid disks, optical discs and flash memory cards or USB flash drives.
- 13. Microcomputers typically use various types of RAM, ROM and NVRAM for internal main memory. Floppy disks, hard disks, CD/DVDs, and flash memory cards and modules are the most common popular bulk storage devices used on smaller computer systems.
- 14. A byte is an 8-bit word. One terabyte (1 TB or 1 Tbyte) of memory means 1 trillion bytes (actually 2⁴⁰). One gigabyte (1 GB or 1 Gbyte) of memory means 1 billion bytes (actually 2³⁰). One megabyte (1 MB or 1 Mbyte) of memory means 1 million bytes (actually 2²⁰). One kilobyte (1 KB or 1 Kbyte) of memory means 1000 bytes (actually 2¹⁰ or 1024).
- 15. DIP, SIP, ZIP, SIMM, DIMM, and RIMM are common memory packages. Memory cards are commonly packaged as a PCMCIA (Personal Computer Memory Card International Association) device.
- 16. A digital potentiometer, featuring an EEPROM, allows changing the output wiper's position digitally and storing the wiper position in NV memory during power-down.

Chapter Review Questions

Answer	the following questions.	11-17.	Press the store key on a calculator. This acti-
			vates the (read, write) process
11-1.	The most important characteristic of a digital		in the memory section.
	system compared to an analog system is its	11-18	Press the recall key on a calculator. This acti-
	(ability to store data, ease of	11 10.	vates the (read, write) process
	interfacing with real-world events).		· · · · · · · · · · · · · · · · · · ·
11-2.	The CD-RW is an example of a bulk storage	11 10	in the memory section.
	device using (mechanical,	11-19.	The following abbreviations stand for what?
	optical) technology.		a. RAM e. EEPROM
11-3.	The (CPU, RAM) is the sec-		b. ROM f. NVRAM
	tion of the computer system that contains the		c. PROM g. FRAM
	arithmetic, logic, and control sections and is		d. EPROM h. MRAM
	the focus of many data transfers.	11-20.	A (RAM, ROM) has both read
11-4.	Three common internal semiconductor memory		and write capability.
	devices used in most computer systems are the	11-21.	A (RAM, ROM) is a permanent
	(floppy, rigid disk, and CD-		memory.
	ROM; RAM, ROM, and NVRAM).	11-22.	A (RAM, PROM) is a nonvola-
11-5	Semiconductor RAM is a		tile memory.
11 5.	(read-only, read/write) type memory device.	11-23.	A (RAM, ROM) has a read/
11-6	Semiconductor ROM is a		write input control.
11 0.	(read-only, read/write) type memory device.	11-24.	A (RAM, ROM) has data
11.7	Semiconductor RAM is a		inputs.
11-7.	(nonvolatile, volatile) memory device.	11-25.	A 32 × 8 memory can hold
11_0	Semiconductor ROM is a		words. Each word is bits long.
11-0.	(nonvolatile, volatile) memory device.	11-26.	List at least three advantages of semiconductor
11_0	Semiconductor NVRAM is a		memories.
11-2.	(read-only, read/write) memory device.	11-27.	A (RAM, ROM) can be erased
11-10	Name the three buses used in a typical personal		easily.
11-10.	computer system.	11-28.	A (flash memory, ROM) can
11.11	The (address, data) bus in		be quickly erased and reprogrammed.
11-11.	a typical PC system is a one-way bus used	11-29.	A(flash memory, UV
	for selecting a specific memory location or		EPROM) can be erased electrically in a very
	peripheral.		short time.
	The USB flash drive is an example of a bulk	11-30.	A (flash memory, ROM) is a
11-12.	storage device using		read/write nonvolatile memory device.
	(mechanical, semiconductor) technology.	11-31.	A(n) (EEPROM, UV EPROM)
11 12	Both floppy and rigid disks use		can be erased and reprogrammed byte by byte
11-13.			without being removed from the equipment.
11 14	(magnetic, optical) technology for storing data.	11-32.	A(DRAM, SRAM with
11-14.	Compared to the typical floppy disk, the hard		battery backup) is a nonvolatile read/write
	disk drive can store much (less,		memory device.
11 15	more) data.	11-33.	A (MRAM, SRAM) semi-
11-15.	The CD-ROM is an optical memory device		conductor memory is a newer type nonvolatile
	that can store about(30 MB,		RAM.
11 17	650 MB) of data.	11-34	A (FRAM, SRAM) semicon-
11-10.	List at least five semiconductor memory		ductor memory is classified as NVRAM.

Chapter Review Questions...continued

11-35.	Memory or data storage is much easier to implement using (analog, digital) electronic circuitry.	11-48.	Replacement or added memory modules (such as DIMMs) are universal and will fit any PC. (T or F)
	The 2114 IC is a (dynamic, static) RAM.	11-49.	A laptop (portable) computer uses the exact same DIMMs and RIMMs as larger desktop
11-37.	The access time of the TTL 7489 RAM is (faster, slower) than that of the MOS 2114 RAM.	11-50.	PCs. (T or F) CD-R and CD-RW discs store data using (magnetic, optical) media.
11-38.	Refer to Fig. 11-7(<i>b</i>). If the input to the decoder is binary 0010, the output from the ROM will be in Gray code.	11-51.	The acronym DVD may stand for digital video disc or
11-39.	Computer programs that are permanently held in ROM are called	11-52.	A (CD-R, CD-RW) is an example of a WORM optical disc.
11-40.	Refer to Table 11-4. Which 27XXX series EPROM could be used to implement a 16K ROM in a microcomputer?	11-53.	The floppy disk used for portable storage in the past had a capacity of about 1 to 2 (KB, MB).
11-41.	Refer to Fig. 11-14. The 16-address line inputs to the 28F512 flash memory IC can address (number) words, each 8 bits	11-54.	Refer to Fig.11-21. The USB flash drive uses magnetic technology (1/2-inch hard drive) to store data. (T or F)
11-42.	wide. Refer to Fig. 11-14. To erase and/or re-	11-55.	Nonvolatile SRAM inside a computer is commonly implemented using battery backup
	program the 28F512 flash memory IC, the (CE, V_{pp}) input must be pulled to a high of about (+5, +12)	11-56.	SRAM (BBSRAM). (T or F) Hybrid hard disk drives contain hard disk platters as well as NVSRAM semiconductor
11-43.	volts. List at least five common types of computer bulk (external) storage.	11-57.	memory. (T or F) The bulk storage device with the best access time (fastest speed) is the
11-44.	Magnetic disks have much (faster, slower) access time than magnetic tapes.	11-58.	(floppy disk, USB flash drive). One gigabyte (1 GB) of memory means a storage capacity of about
11-45.	Short access time in a memory device is a measure of (good, poor) performance.	11-59.	(1 billion, 1 million) bytes. A modern personal computer might feature a hard disk drive with a storage capacity of
11-46.	Refer to Fig 11-16(b). The 168-pin DIMM being installed in the socket on the PC's motherboard contains (ROM, SDRAM) memory chips.	11-60.	(1 MB, 1 TB). A digital potentiometer, such as the DS1804 IC features a(nonvolatile, volatile) memory for storing the wiper position for
11-47.	A RIMM refers to a memory module used in modern PCs that contains semiconductor memory chips of the (RDRAM, ROM BIOS) type.	11-61.	later retrieval during power-down conditions. Generally, an analog input (gradually changing voltage) controls the digital output of a solid-state potentiometer such as the DS1804 IC. (T or F)

Critical Thinking Questions

- 11-1. Draw a diagram of how a 32×8 memory might look in table form. The table will be similar to the one in Fig. 11-3.
- 11-2. List at least three uses of read-only memories.
- 11-3. If a computer has 4 GB of SRAM, how many bytes of read/write memory does it contain?
- 11-4. Explain the difference between software and firmware.
- 11-5. Explain the difference between a mask-programmable ROM and a fusible-link PROM.
- 11-6. Explain the difference between a UV EPROM and an EEPROM.

- 11-7. Why have hard disks become almost standard bulk storage devices on most microcomputers?
- 11-8. List several types of nonvolatile read/write memory.
- 11-9. Internet research: Why might you order a solidstate drive instead of a hard disk drive in a new computer?
- 11-10. Internet research: What is a hybrid hard disk drive?
- 11-11. Internet research: What is a holographic versatile disc (HVD)?
- 11-12. Internet research: What are the uses of Blu-ray discs?



Answers to Self-Tests

- 1. CPU or central processing unit
- 2. address bus, control bus
- 3. magnetic, optical, semiconductor, or mechanical
- 4. floppy disk drive, hard (rigid) disk drive, CD-ROM, DVD, USB flash drive.
- 5. a. random-access memory
 - b. read-only memory
 - c. electrically programmable read-only memory
 - d. electrically erasable programmable read-only memory
 - e. static RAM
 - f. dynamic RAM
- 6. T
- 7. CD-R or CD-RWs
- 8. flash memory or MRAM
- 9. random-access memory
- 10. writing
- 11. reading
- 12. read/write
- 13. 16×4 bit
- 14. volatile, off
- 15. DRAM
- 16. RAM
- 17. 16, 4
- 18. write, written into, 15
- 19. dynamic
- 20. 4096, 4
- 21. binary-to-Gray

- 22. 1100, Gray, 1000
- 23. lose its program and have to be reprogrammed
- 24. read-only memory
- 25. nonvolatile
- 26. firmware
- 27. manufacturer
- 28. is not
- 29. 0010
- 30. 1101
- 31. high-
- 32. remain in
- 33. 177
- 34. 14
- 35. manufacturer
- 36. ROM
- 37. programmable read-only memory
- 38. erasable programmable read-only memory
- 39. electrically erasable programmable read-only memory
- 40. ultraviolet
- 41. 524,288, 65,536
- 42. nonvolatile RAM
- 43. lithium
- 44. EEPROM
- 45. recall
- 46. V_{pp}
- 47. flash memory
- 48. SRAM

- 49. F
- 50. MRAM
- 51. magnetoresistive RAM
- 52. ferroelectric RAM
- 53. F
- 54. DIP
- 55. dual in-line memory module
- 56. double data rate synchronous DRAM
- 57. single in-line memory module
- 58. Rambus DRAM
- 59. T
- 60. Personal Computer Memory Card International Association
- 61. credit card
- 62. F
- 63. magnetic, optical, semiconductor
- 64. magnetic tapes, magnetic disks (floppy and rigid), magnetic drum, optical discs, flash memory or cards, paper tapes, paper punched cards, USB flash drive
- 65. rigid
- 66. hard disk drive

- 67. rigid disk
- 68. platters
- 69. one billion
- 70. hard disk drive
- 71. 250 GB and up
- 72. USB flash drive
- 73. digital versatile disc
- 74. optical
- 75. write-once read-many
- 76. compact disc rewritable
- 77. CD-ROM
- 78. slower
- 79. F
- 80. T
- 81. NV trimmer potentiometer
- 82. EEPROM, multiplexer
- 83. 51 k Ω
- 84. $52 \text{ k}\Omega$
- 85. 51 k Ω
- 86. 50 kΩ
- 87. 49 kΩ
- 88. $50 \text{ k}\Omega$



Simple Digital Systems

Learning Outcomes

This chapter will help you to:

- in most systems. *Classify* parts of the BS2 microcontroller module as to input, output, storage, control, processing or transmission.
- 12-2 Describe each of the five scales of integration of digital ICs (SSI, MSI, LSI, VLSI, and ULSI).
- **12-3** Analyze the operation of two digital dice game circuits.
- 12-4 Diagram the organization of a digital clock system. Analyze the block diagram of a digital clock. Use your knowledge of counters and Schmitt triggers in explaining the operation of several sections of a digital clock.
- **12-5** Analyze the operation of an LSI digital clock system, including frequency dividing circuits and display multiplexing.
- 12-6 Analyze the operation of a digital frequency counter system. Predict the operation of divide-by-x circuits, counters, decoder/drivers for LED displays, control circuitry, and waveshaping circuits.
- 12-7 *Interpret* the detailed schematic of an experimental frequency counter system.
- 12-8 Analyze the operation of an LCD timer system. Predict the operation on time base circuits/clocks, down counters, magnitude comparators, and LCD latch/decoder/drivers.
- 12-9 Classify technologies used in distance sensors. Summarize the operation types of infrared and ultrasonic distance sensors. Test a digital distance sensor. Envision, invent, sketch, and predict of operation of noncontact distance sensor, like an automatic paper-towel dispenser using components you have formerly used in class.
- **12-10** Answer selected questions about terms used in boundary scan technology (JTAG).

any devices we use every day, such as calculators, alarm clocks, digital wristwatches, cellular telephones, MP3 players, and computers, are digital systems. Calculators, digital clocks, and computers are assemblies of subsystems. Typical subsystems include counters, RAMs, ROMs, encoders, decoders, clocks, and display decoders/drivers. You have already used many of these subsystems. This chapter discusses several digital systems, how they transmit data, and how they can be tested for proper system operation. Digital systems are formed by the proper assembly of digital subsystems.

12-1 Elements of a System

Most mechanical, chemical, fluid, and electrical systems have certain features in common. Systems have an input and an output for their product, power, or information. Systems also act on the product, power, or information; this is called *processing*. The entire system is organized and its operation directed by a control function. The transmission function transmits products, power, or information. More complicated systems also contain a storage function. Figure 12-1 illustrates the overall organization of a system. Look carefully, and you can see that this diagram is general enough to apply to nearly any system, whether it is transportation, fluid, school, or electronic. The transmission from device to device is shown by the colored lines and arrows. Notice that the data or whatever is being transferred always moves in one direction. It is common to use double arrows on the control lines to show that the control unit is directing the operation of the system as well as receiving feedback from the system.

Elements of a system

Input Output

Processing Control Transmission

Storage

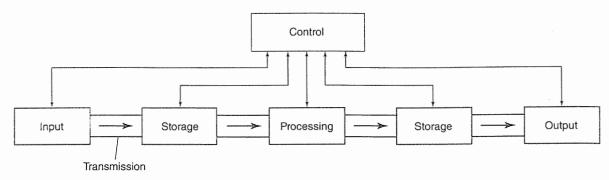


Fig. 12-1 The elements of a system.

Digital systems deal with transmitting digital data, usually as numbers or codes. The general system shown in Fig. 12-1 will help explain several digital systems discussed in this chapter.

BASIC Stamp 2 Module

The BASIC Stamp 2 (BS2) Microcontroller Module by Parallax is a digital system some in your class have used. Figure 12-2(a) represents the BS2 module in 24-pin dual in-line package (DIP) form. Mounted on top of the 24-pin DIP are several electronic devices. The largest IC is the custom PIC16C57 microcontroller, which is housed in a SOIC surface-mount 28-pin IC. The IC labeled *U2* is a SOIC 8-pin, 2-KB EEPROM

used for storing downloaded programs. Other surface-mount parts including a 5-V regulator, reset circuitry, a 20-MHz ceramic resonator, and serial input/output circuitry.

A more detailed schematic of the BS2 module is drawn in Fig. 12-2(b). This shows the components mentioned above along with details on input/output ports (P_0 to P_{15}), serial communication ports (RA_0 to RA_3), power connections V_{DD} , V_{SS} (ground), and V_{in} .

Can we classify the parts of the BS2 module shown in Fig. 12-2(b) as input, storage, processing, output, or control? We can *only partially classify* the parts in the BS2 module because it is a programmable device.

-√M- Self-Test

Answer the following questions.

- There is a two-way path from the _____ section of a system to all other parts.
- 2. The keyboard of a microcomputer is classified as what part of the system?
- 3. Digital systems deal with transmitting
- 4. Refer to Fig. 12-2. The 24LC16 EEPROM would be classified as a _____ (processing, storage) device in this system.
- 5. Refer to Fig. 12-2. The microcontroller (custom PIC16C57 chip) has many functions, including storage, processing, control, input, and output in most applications. (T or F)
- 6. Refer to Fig. 12-2(a). Pins 1 and 2 of the 24-pin DIP BS2 module are used for

- serial transmission of data to and from the host computer (PC). (T or F)
- 7. Refer to Fig. 12-2(b). The component that sets the clock frequency of the PIC16C57 microcontroller is the _____.
- 8. Refer to Fig. 12-2(b). The MCLR pin (pin 28) is an _____ (input, output) linked to the reset (RES) pin of the BS2 module.
- Refer to Fig. 12-2(b). The general-purpose input/output ports become either an input or output as directed by the downloaded PBASIC program. (T or F)
- 10. Refer to Fig. 12-2. List the power connections to the BS2 microcontroller module.
- 11. Refer to Fig. 12-2(*b*). The programs downloaded by the user of the microcontroller are stored in the EEPROM,

while the PBASIC interpreter is housed in _____ (firmware, RAM) in the PIC16C57 microcontroller.

12. Refer to Fig. 12-2(*b*). The communication between the EEPROM and

microcontroller chip appear to be in the form of ______ (8-bit parallel, serial) data transmission.



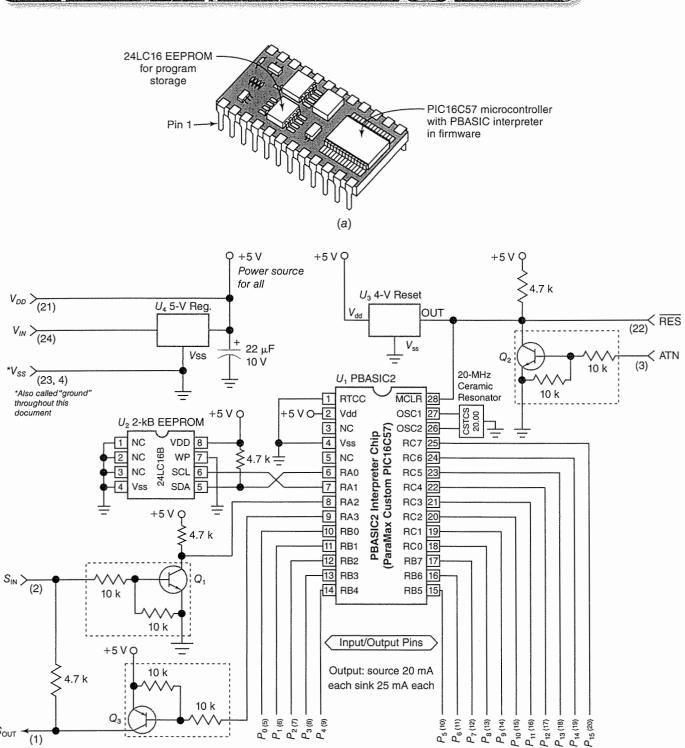


Fig. 12-2 BASIC Stamp 2 module. (a) Housed in 24-pin DIP. (b) Schematic diagram of housing.

Internet Connection

Search Wikipedia for current info on processors.

Ultra large-scale integration (ULSI) Small-scale integration (SSI)

Medium-scale integration (MSI) Calculator chips Microprocessor

Large-scale integration (LSI)

Very large-scale integration (VLSI) Microcontroller

12-2 A Digital System on an IC

We have learned that all digital systems can be wired from individual AND and OR gates and inverters. We have also learned that manufacturers produce subsystems on a single IC (counters, registers, and so on). Now manufacturers have gone a step further: some ICs contain entire digital systems.

The least complex digital integrated circuits are classified as a *small-scale integration (SSI)*. An SSI contains circuit complexity of less than 12 gates or circuitry of similar complexity. Small-scale integrations include the logic gate and flip-flop ICs you have used.

A medium-scale integration (MSI) has a complexity ranging from 12 to 99 gates. ICs that are classified as MSIs belong to the small subsystem group. Typical examples include adders, registers, comparators, code converters, counters, data selectors/multiplexers, and small RAMs. Most of the ICs you have studied and used so far have been either SSIs or MSIs.

A large-scale integration (LSI) has the complexity of 100 to 9999 gates. A major subsystem or a simple digital system is fabricated on a single chip. Examples of LSI chips are digital clocks, calculators, microcontrollers, ROMs, RAMs, PROMs, EPROMs, and some flash memories.

A very large-scale integration (VLSI) has the complexity of 10,000 to 99,999 gates. VLSI ICs are usually digital systems on a chip. The term "chip" refers to the single silicon die (perhaps

 $\frac{1}{4}$ -in. square or larger) that contains all the electronic circuitry in an IC. Large memory chips and advanced microprocessors are examples of VLSI ICs.

An ultra-large-scale integration (ULSI) is the next higher level of circuit complexity and contains more than 100,000 gates on a single chip. Various manufacturers tend to define SSI, MSI, LSI, VLSI, and ULSI differently.

In the 1960s, families of digital ICs were being developed using SSI and MSI technology. Late in the 1960s, large-scale integration technology developed many specialized ICs. Higher-production LSIs included single-chip clocks, calculators, and memories. After the development of *calculator chips*, the architecture of a computer was designed into a single chip called the microprocessor. The *microprocessor* forms the CPU of a computer system. Improvements in CPU design and chip manufacturing have produced the latest generation of microprocessors that contain the equivalent of billions of transistors.

In the 1980s, manufacturers combined some of the separate sections of a computer system (CPU, RAM, ROM, and input/output) into a single inexpensive IC. These "tiny computers on a chip" were used mainly for control purposes and were not used in general-purpose computers. These inexpensive computers on a chip are generally referred to as *microcontrollers*. The BS2 microcontroller module in Fig. 12-2 features one such device.

-N- Self-Test

Supply the missing word in each statement.

- 13. A medium-scale integration is an IC that contains the equivalent of _____ gates.
- 14. A VLSI is an IC that contains the equivalent of more than _____ gates.
- 15. Using SSI and MSI technology, digital families of ICs (like TTL) were
- developed in the _____ (1940s, 1960s).
- 16. A(n) _____ (adder IC, microcontroller IC) could be described as a digital system on a chip.
- 17. Identify an ULSI device that forms the CPU of modern general-purpose computers.



12-3 Digital Games

Electronics has been a popular hobby for more than a half century. A favorite task for many electronic hobbyists, young and old, is to construct electronic games. Electronic games and toys are also very popular with students studying electronics in high schools, technical schools, and colleges.

Electronic games may be classified as simple self-contained, computer, arcade, or TV games. The simple self-contained type includes the games and toys most often constructed by students and hobbyists. Several simple digital electronic games using SSI and MSI digital ICs will be surveyed in this section. These are examples of simple digital systems.

Simple Dice Game

A block diagram of a simple digital dice game is sketched in Fig. 12-3. When the push button is pressed, a signal from the clock is sent to the counter. The counter is wired to have a counting sequence of 1, 2, 3, 4, 5, 6, 1, 2, 3, and so on. The binary output from the counter is translated to seven-segment code by the decoder block. The decoder block also contains a seven-segment LED display driver. The output device in this circuit is an LED display. When the push-button switch is opened, the counter stops at a random number from 1 through 6. This simulates the roll of a single die. The binary number stored in the counter is decoded and shown as a decimal number on the display. This circuit could be doubled to simulate the rolling of a pair of dice.

A wiring diagram for the digital dice game is detailed in Fig. 12-4. Pressing the input switch causes the counter to sequence through the binary numbers 001, 010, 011, 100, 101, 110, 001, 010, 011, etc. When the switch is opened, the last binary count is stored in the flip-flops of

the 74192 counter. It is decoded by the 7447 IC and lights the seven-segment LED display.

The 555 timer IC is wired as an as table MV in Fig. 12-4. It generates a 600-Hz rectangular-wave signal.

The 74192 IC is wired as a mod-6 (1 to 6) up counter. The three-input NAND gate is activated when the count reaches binary 111. The LOW signal from the NAND gate loads the next number in the count sequence, which is binary 001. It should be noted that the three outputs of the counter (Q_A, Q_B, Q_C) all go HIGH for only an extremely short time (less than a microsecond) while the counter is being loaded with 0001. Therefore, the temporary count of binary 111 never appears as a 7 on the LED display.

The 7447 BCD-to-seven-segment decoder chip translates the binary inputs (A, B, C) to seven-segment code. The 7447 IC drives the LED segments with active LOW outputs (a to g). The seven $150-\Omega$ resistors serve to limit the current flow through the LEDs to a safe level. Note that the seven-segment LED display used in Fig. 12-4 is a common-anode type.

Another Dice Game

The digital dice game featured in Fig. 12-4 used TTL ICs with an unrealistic seven-segment display. A more realistic dice simulation is implemented in the circuit shown in Figs. 12-5 and 12-6.

A block diagram for a second digital dice game is sketched in Fig. 12-5(a). This unit uses individual LEDs for the output device.

Depressing the push button in Fig. 12-5(a) causes the clock to generate a square-wave signal. This signal causes the down counter to cycle through the count sequence 6, 5, 4, 3, 2, 1, 6, 5, 4, and so on. The logic block lights the proper LEDs to represent various decimal counts. The LED pattern for each possible decimal output is diagrammed in Fig. 12-5(b).

Digital dice game

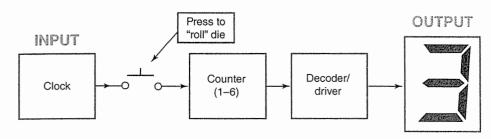


Fig. 12-3 Simple block diagram of a digital dice game.

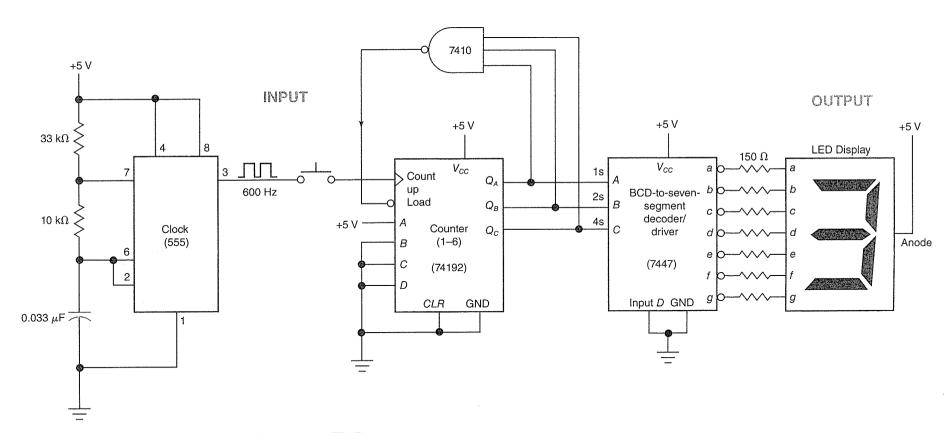


Fig. 12-4 Wiring diagram for an experimental digital dice game using TTL ICs.

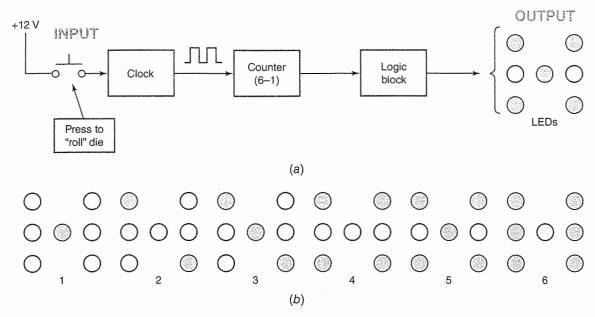


Fig. 12-5 Electronic dice simulation game. (a) Simple block diagram. (b) LED patterns used for representing dice rolls 1 through 6.

Electronic dice simulation game

The wiring diagram for the second digital dice game is detailed in Fig. 12-6. The circuit features the use of 4000 series CMOS ICs and a 12-V dc power supply. The push-button switch on the left is the input device, while the LEDs (D1 to D7) on the right form the output. Physically, the LEDs are arranged as shown at the lower right in Fig. 12-6.

When the "roll dice" switch is closed, the two NAND Schmitt-trigger gates at the left in Fig. 12-6 produce a 100-Hz square-wave signal. The two NAND gates and associated resistors and capacitors are wired to form a stable MV. The 100-Hz signal is fed into the clock input of the 4029 presettable binary/decade up/down counter. In this circuit, the 4029 IC is wired as a down counter whose outputs produce binary 110, 101, 100, 011, 010, 001, 110, 101, 100, etc.

Consider the situation when the down counter in Fig. 12-6 reaches binary 001. On the next LOW-to-HIGH transition of the clock pulse, the carry out output (pin 7) of the 4029 IC drops LOW. This signal is fed back and turns on transistor Q_1 . This causes the preset enable input of the 4029 counter to go HIGH. When the preset enable input goes HIGH, the data at inputs J4, J3, J2, and J1 (the "jam inputs") are asynchronously loaded into the counter's flip-flops. In this example, binary 0110 is loaded on the preset pulse. Once the flip-flops have been loaded, the carry out pin goes back HIGH and transistor Q_1 turns off.

The final sections of the dice game at the right in Fig. 12-6 contain many components. The table in Fig. 12-7 will help explain the complexities of the *logic* and *output* sections of this dice game.

The input section of the table in Fig. 12-7 indicates the logic levels present at the output of the 4029 counter. The top line of the table shows a binary 110 (HHL) stored in the 4s, 2s, and 1s flip-flops of the counter. The middle column of the table lists only the components that are activated to light the proper LEDs.

Consider the first line of the table in Fig. 12-7. The output of the NAND gate goes LOW, which turns on the PNP transistor Q_2 . The transistor conducts and all six LEDs (D2 to D7) on the right in Fig. 12-6 light. This would simulate a dice roll of 6.

Consider line 2 of the table in Fig. 12-7. The binary data equal 101 (HLH). The HIGH on the 1s line (pin 6) turns on transistor Q_5 . Transistor Q_5 conducts and lights LED D1. The output of the NAND gate is HIGH, which causes both bilateral switches to be in the closed condition (low impedance from in/out to out/in). The bilateral switches pass the logic level from the 2s and 4s lines to the base of transistors Q_4 and Q_3 . Transistor Q_3 is turned on by the HIGH and conducts. Light-emitting diodes D2, D3, D4, and D5 light. A decimal 5 is represented when these five LEDs (D1 to D5) are lit.

ambiación gama

Logic and output sections of dice game

4029 presettable binary/decade up/down counter Electronic dice game circuit

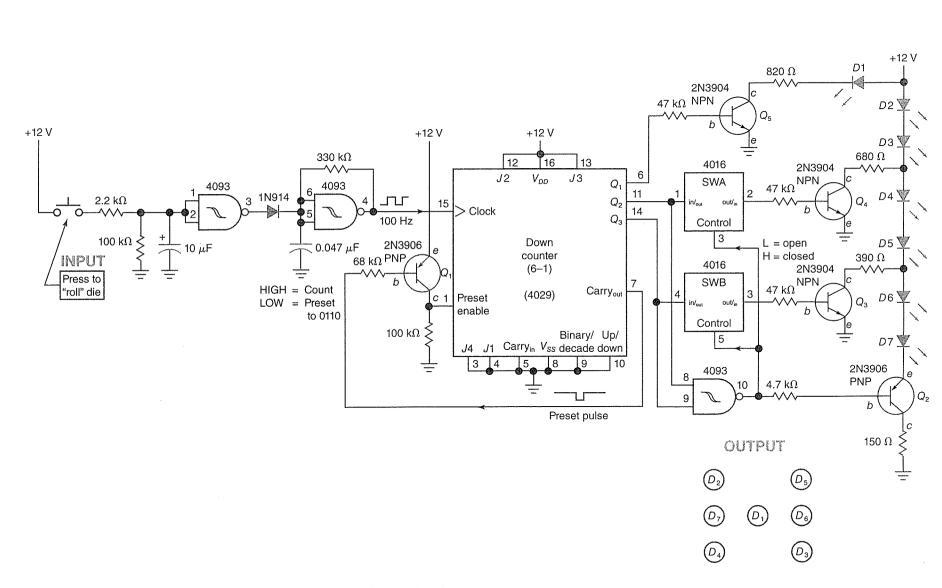


Fig. 12-6 Wiring diagram for an electronic dice simulation game. (Courtesy of Graymark, Inc.)

	INPUTS			ОИТРИТ	
4s (pin 14)	2s (pin 11)	1s (pin 6)	ACTIVE COMPONENTS	LEDs LIT	DECIMAL
Н	Н	L	NAND output LOW Transistor Q₂ turned on	D2, D3, D4, D5, D6, D7	6
			Transistor Q_5 turned on	D1	
Н	L	Н	Bilateral switch SWB closed Transistor Q_3 turned on	D2, D3, D4, D5	5
Н	L	L	Bilateral switch SWB closed Transistor Q_3 turned on	D2, D3, D4, D5	4
L	Н	Н	Transistor Q_5 turned on Bilateral switch SWA closed Transistor Q_4 turned on	D1 D2, D3	3
L	Н	L	Bilateral switch SWA closed Transistor Q ₄ turned on	D2, D3	2
L	L	Н	Transistor Q₅ turned on	D1	1

Fig. 12-7 Explaining the logic and output sections of the electronic dice simulation game.

You may look over the remaining lines of the table in Fig. 12-7 to determine the operation of the logic and output sections of this CMOS digital dice game.

The 4016 IC used in Fig. 12-6 is described by the manufacturer as a *quad bilateral switch*. It is an electronically operated SPST switch. A HIGH at the control input of the 4016 bilateral switch causes it to be in the "closed" or "ON"

position. In the closed position the internal resistance from in/out to out/in terminals is quite low (400 Ω typical). A LOW at the control input of the bilateral switch causes it to be in the open or OFF position. The 4016 IC acts like an open switch when the control is LOW. Unlike a gate, a bilateral switch can pass data in either direction. It can pass either dc or ac signals. A bilateral switch is also referred to as a *transmission gate*.

Quad bilateral switch

Transmission gate

-W- Self-Test

Answer the following questions.

- 18. Refer to Fig. 12-4. The 555 timer is wired as a(n) _____ multivibrator in this digital system.
- 19. Refer to Fig. 12-4. When the 74192 IC increases its count from 110 to 111, the output of the NAND gate goes ______ (HIGH, LOW) immediately loading _____ (binary) into the counter.
- 20. Refer to Fig. 12-4. List the possible digits that can appear on the seven-segment LED display when the input switch is released.
- 21. Refer to Fig. 12-6. Two gates packaged in the _____ (4016, 4029, 4093) IC are wired as a free-running MV in this digital dice game circuit.
- 22. Refer to Fig. 12-6. List the binary counting sequence of the 4029 IC in this circuit.
- 23. Refer to Fig. 12-6. When the output of the counter is binary 001, only *D*1 lights because only transistor _______ is turned on and conducts.
- 24. Refer to Fig. 12-6. When the output of the counter is binary 010, LED(s)

- light because the bilateral switch SWA is ______ (closed, open) and transistor _____ is turned on grounding the cathode of light-emitting diodes D_2 and D_3 .
- 25. A(n) ______ is an IC device available in CMOS that acts much like a SPST switch that can conduct either ac or do signals.
- 26. Refer to Fig. 12-4. The 74192 IC is wired as a mod-7 down counter which counts from 6 through 1. (T or F)
- 27. Refer to Fig. 12-6. A short LOW preset pulse temporarily ______ (turns off, turns on) the PNP transistor Q₁ which causes a short ______ (HIGH, LOW) pulse at the preset enable input loading _____ (1000, 0110) in the 4029 counter IC.
- 28. Refer to Fig. 12-6. With the count output from the 4029 IC at 001, only transistor (Q_2, Q_5) conducts, lighting only LED D1.



12-4 The Digital Clock

We introduced a digital electronic clock earlier and noted that various *counters* are the heart of a digital clock system. Figure 12-8(a) is a simple block diagram of a digital clock system.

Some clocks use the power-line frequency of 60 Hz as their input or frequency standard. This frequency is divided into seconds, minutes, and hours by the frequency divider section of the clock. The one-per-second, oneper-minute, and one-per-hour pulses are then counted and stored in the count accumulator section of the clock. The stored contents of the count accumulators (seconds, minutes, hours) are then decoded, and the correct time is shown on the output time displays. The digital clock has the typical elements of a system. The input is the 60-Hz alternating current. The processing takes place in the frequency divider, count accumulator, and decoder sections. Storage takes place in the count accumulators. The control section is illustrated by the *time-set* control, as shown in Fig. 12-8(a). The output section is the digital time display.

It was mentioned that all digital systems consist of logic gates, flip-flops, and subsystems. The diagram in Fig. 12-8(b) shows how subsystems are organized to display time in hours, minutes, and seconds. This is a more detailed diagram of a digital clock. The input is still a 60-Hz signal. The 60 Hz may be from the low-voltage secondary coil of a transformer. The 60 Hz is divided by 60 by the first frequency divider. The output of the first divide-by-60 circuit is 1 pulse per second. The 1 pulse per

second is fed into an *up counter* that counts upward from 00 through 59 and then resets to 00. The seconds counters are then decoded and displayed on the two 7-segment LED displays at the upper right, Fig. 12-8(b).

Consider the middle frequency divider circuit in Fig. 12-8(b). The input to this divide-by-60 circuit is 1 pulse per second; the output is 1 pulse per minute. The 1-pulse-per-minute output is transferred into the 0 to 59 minutes counter. This up counter keeps track of the number of minutes from 00 through 59 and then resets to 00. The output of the minutes count accumulator is decoded and displayed on the two 7-segment LEDs at the top center, Fig. 12-8(b).

Now for the divide-by-60 circuit on the right in Fig. 12-8(*b*). The input to this frequency divider is 1 pulse per minute. The output of this circuit is 1 pulse per hour. The 1-pulse-per-hour output is transferred to the hours counter on the left. This hours count accumulator keeps track of the number of hours from 0 to 23. The output of the hours count accumulator is decoded and transferred to the two 7-segment LED displays at the upper left, Fig. 12-8(*b*). You probably have noticed that this is a 24-h digital clock. It easily could be converted to a 12-h clock by changing the 0 to 23 count accumulator to a 1 to 12 counter.

For setting the time, a time-set control has been added to the digital clock in Fig. 12-8(b). When the switch is closed (a logic gate may be used), the display counts forward at a fast rate. This enables you to set the time quickly. The switch bypasses the first divide-by-60

Frequency divider circuits

Frequency divider

Count accumulator

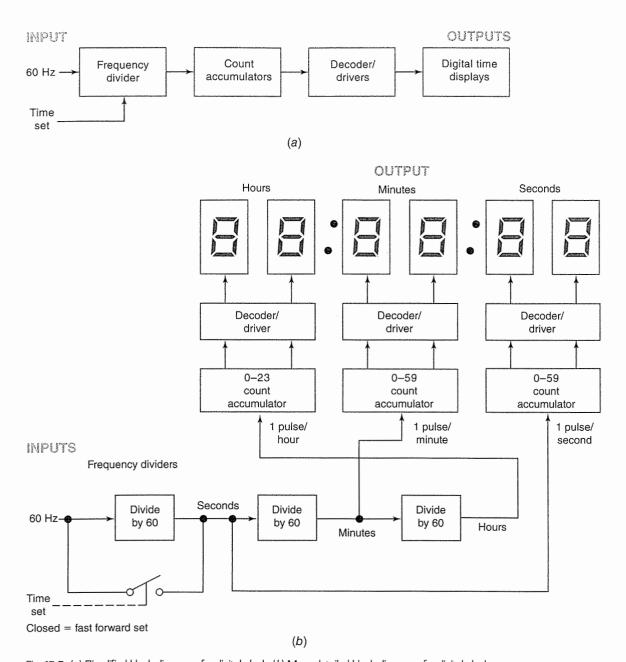


Fig. 12-8 (a) Simplified block diagram of a digital clock. (b) More detailed block diagram of a digital clock.

Digital clock as a system


frequency divider so that the clock moves forward at 60 times its normal rate. An even faster *fast-forward* set could be used by bypassing both the first and the second divide-by-60 circuits. The latter technique is common in digital clocks.

What is inside the divide-by-60 frequency dividers in Fig. 12-8(b)? In Chapter 8 we spoke of a counter being used to divide frequency. Figure 12-9(a) is a block diagram of how a divide-by-60 frequency divider might be organized. Notice that a divide-by-6 counter is feeding a divide-by-10 counter. The entire unit divides

the incoming frequency by 60. In this example, the 60-Hz input is reduced to 1 Hz at the output.

A detailed wiring diagram for a divide-by-60 counter circuit is drawn in Fig. 12-9(b). The three J-K flip-flops and NAND gate form the divide-by-6 counter while the 74192 decade counter performs as a divide-by-10 unit. If 60 Hz enters at the left, the frequency will be reduced to 1 Hz at output Q_D of the 74192 counter.

The seconds and minutes count accumulators in Fig. 12-8(b) are also counters. The 0 to 59 is a decade counter cascaded with a 0 to

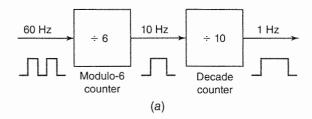

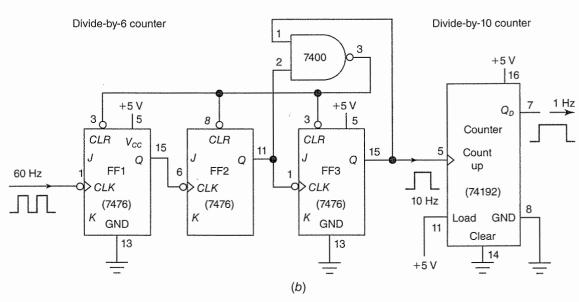


Fig. 12-9 Divide-by-60 counter. (a) Block diagram. (b) Wiring diagram using TTL ICs.

5 counter. The decade counter drives the 1s place of the displays. The mod-6 counter drives the 10s place of the displays. In a like manner, the hours count accumulator is a decade counter cascaded with a 0 to 2 counter. The decade counter drives the 1s place in the hours display. The mod-3 counter drives the 10s place of the hours display.

In many practical digital clocks the output may be in hours and minutes only. Most digital clocks are based upon one of many inexpensive ICs. Large-scale-integrated *clock chips* have all the frequency dividers, count accumulators, and decoders built into a single IC. For only a few extra dollars, clock chips have other features, such as 12- or 24-h outputs, calendar features, alarm controls, and radio controls.

An added feature you will use when you construct a digital timepiece is shown in Fig. 12-10(a). A waveshaping circuit has been added to the block diagram of our digital clock. The IC counters that make up the frequency divider circuit do not work well with a sinewave input. The sine wave [shown at the left in Fig. 12-10(a)] has a slow rise time that does not trigger the counter properly. The sine-wave

input must be converted to a square wave. The waveshaping circuit changes the sine wave to a square wave. The square wave will now properly trigger the frequency divider circuit.

Commercial LSI clock chips have wave-shaping circuitry built into the IC. In the laboratory you may use a *Schmitt-trigger inverter IC* to square up the sine waves as you did in Chapter 7. A simple waveshaping circuit is shown in Fig. 12-10(b). This circuit uses the TTL 7414 Schmitt-trigger inverter IC to convert the sine wave to a square wave. The circuit in Fig. 12-10(b) also contains a *start/stop control*. When the control input is HIGH, the square wave from the Schmitt-trigger inverter passes through the AND gate. When the control input goes LOW, the square-wave signal is inhibited and does not pass through the AND gate. The counter is stopped.

You will want to get some practical knowledge of how counters are used in dividing frequency. Remember that the counter subsystem is used for two jobs in the digital timepiece: first to divide frequency and second to count upward and accumulate or store the number of pulses at its input.

Schmitt-trigger inverter IC

Start/stop control

Waveshaping circuit

Slow rise time Frequency division Count accumulation

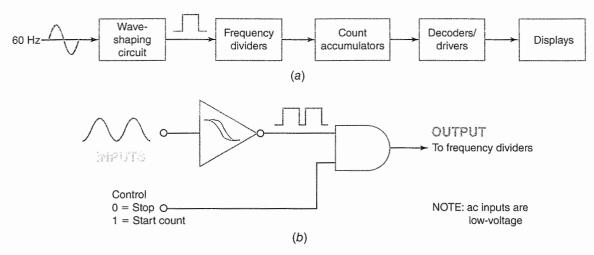


Fig. 12-10 Waveshaping. (a) Adding a waveshaping circuit to the input of the digital clock system. (b) Schmitt trigger inverter used as a wave shaper.

Waveshaping using Schmitt-trigger device

-⁄M- Self-Test

Answer the following questions.

- 29. Refer to Fig. 12-8(a). Counters are used in the ______ and _____ sections of a digital clock.
- 30. Refer to Fig. 12-10. When operating a clock with a sine wave, a(n) ______ circuit is added to the clock.
- 31. Refer to Fig. 12-10(*b*). What is the purpose of the Schmitt-trigger inverter in this circuit?
- 32. Refer to Fig. 12-10(*b*). What is the purpose of the AND gate in this circuit?

- 33. Refer to Fig. 12-8. The seconds 0–59 count accumulator could be wired using _____ (counter, shift register) ICs.
- 34. Refer to Fig. 12-8. The divide-by-60 frequency dividers could be wired using only decade counters. (T or F)
- 35. Refer to Fig. 12-8. The blocks titled "count accumulators" suggest that the embedded counters serve as temporary memory devices. (T or F)



12-5 The LSI Digital Clock

The LSI clock chip forms the heart of modern digital timepieces. These digital clock chips are made as monolithic MOS ICs. Sometimes, the MOS LSI chip, or die, is mounted in an 18-, 24-, 28-, or 40-pin DIP IC. Other times, the MOS LSI chip is mounted directly on the PC board of a *clock module*. The tiny silicon die is sealed under an epoxy coating. Examples of the two packaging methods are shown in Fig. 12-11. An MOS LSI clock IC packaged in a 24-pin DIP is illustrated in Fig. 12-11(a). Pin 1 of the DIP IC is

identified in the normal manner (pin 1 is immediately CCW from the notch). A clock module is sketched in Fig. 12-11(b). The back is a PC board with 22 edge connectors. The numbering of the edge connectors is shown. A four-digit LED display is premounted on the board with all connections complete. Some clock modules have some discrete components and a clock IC mounted on the board. The clock module in Fig. 12-11(b) has the tiny silicon chip, or die, mounted on the PC board. It is sealed with a protective epoxy coating.

Clack module

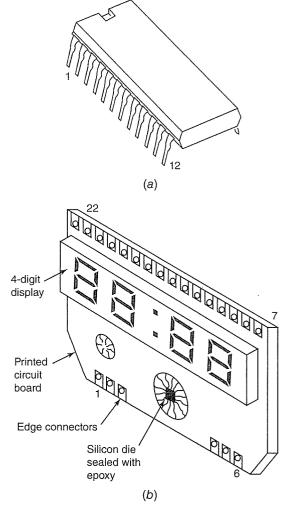


Fig. 12-11 (a) An LSI clock chip in a 24-pin dual in-line package. (b) A typical clock module containing a MOS/LSI die.

A block diagram of National Semiconductor's *MM5314 MOS LSI clock IC* is shown in Fig. 12-12(*a*). The pin diagram is shown in Fig. 12-12(*b*). Refer to Fig. 12-12(*a*) and (*b*) for the following functional description of the MM5314 digital clock IC.

50- or 60-Hz Input [Pin 16]

Alternating current or rectified ac is applied to this input. The *waveshaping circuit* squares up the waveform. The shaping circuit drives a chain of counters which perform the time-keeping job.

Multiplexing and driving displays

MM5314 MD5

LSI clock IC

50- or 60-Hz Select Input [Pin 11]

This input programs the *prescale counter* to divide by either 50 or 60 to obtain a 1-Hz, or

1-pulse-per-second, time base. The counter is programmed for 60-Hz operation by connecting this input to V_{DD} (GND). If the 50/60-Hz select input pin is left unconnected, the clock is programmed for 50-Hz operation.

Time-Setting Inputs (Pins 13, 14, and 15)

Slow- and fast-setting inputs as well as a hold input are provided on this clock IC. These inputs are enabled when they are connected to V_{DD} (GND). Typically, a normally open pushbutton switch is connected from these pins to V_{DD} . The three gates in the counter chain are used for setting the time. For *slow set*, the prescale counter is bypassed. For *fast set*, the prescale counter and seconds counter are bypassed. The *hold* input inhibits any signal from passing through gate A to the prescale counter. This stops the counters, and time does not advance on the output display.

12- or 24-H Select Input [Pin 10]

This input is used to program the hours counter to divide by either 12 or 24. The 12-h display format is selected by connecting this input to V_{DD} (GND). Leaving pin 10 unconnected selects the 24-h format.

Output MUX Operation (Pins 3 to 9 and 17 to 22)

The seconds, minutes, and hours counters continuously reflect the time of day. Outputs from each counter are *multiplexed* to provide digit-by-digit sequential access to the time data. In other words, only one display digit is turned on for a very short time, then the second, then the third, and so forth. By multiplexing the displays instead of using 48 leads to the six displays (8 pins each \times 6 = 48), only 13 output pins are required. These 13 outputs are the multiplexed seven-segment outputs (pins 3 through 9) and the digit enable outputs (pins 17 through 22).

The MUX is addressed by a multiplex divider/decoder, which is driven by a multiplex oscillator. The oscillator uses external timing components (resistor and capacitor) to set the frequency of the multiplexing function.

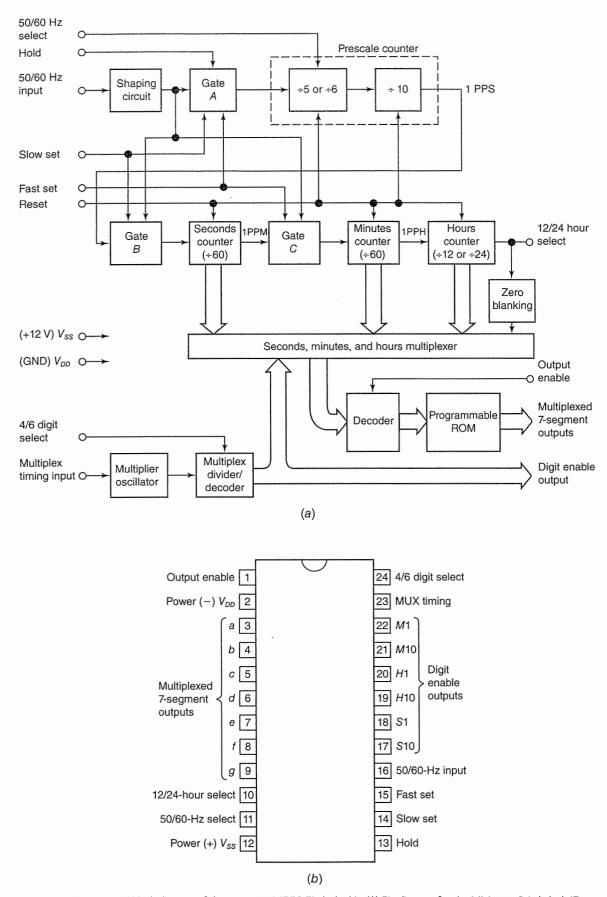


Fig. 12-12 (a) Functional block diagram of the MMS314 MOS/LSI clock chip. (b) Pin diagram for the MMS314 digital clock IC.

MM5314 MOS/ LSI clock chip The four/six-digit select input controls if the MUX turns on all six or just four displays in sequence. The *zero-blanking* circuit suppresses the 0 that would otherwise sometimes appear in the tens-of-hours display. The MUX addresses also become the display digit enable outputs (pins 17 to 22). The MUX outputs are applied to a decoder which is used to address a *PROM*. The PROM generates the final seven-segment output code. The displays are enabled in sequence from the unit seconds through the tens-of-hours display.

PROM

Multiplex Timing Input (Pin 23)

MM5314 clock IC features Relexation oscillator [multiplex oscillator]

Adding a resistor and capacitor to the MM5314 clock IC forms a *relaxation oscillator*. The external resistor and capacitor are connected to the MUX timing input as shown in Fig. 12-13. Typical timing resistor and capacitor values might be 470 k Ω and 0.01 μ F.

Four/Six-Digit Select Input (Pin 24)

The four/six-digit select input controls the MUX. With no input connection, the clock outputs data for a four-digit display. Applying $V_{\scriptscriptstyle DD}$ (GND) to this pin provides a six-digit display.

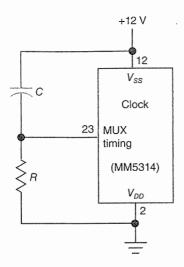


Fig. 12-13 Placement of the external resistor and capacitor used to set the frequency of the multiplex oscillator in the MMS314 clock IC.

Output Enable Input (Pin 1)

With this pin unconnected, the seven-segment outputs are enabled. Switching $V_{\rm DD}$ (GND) to this input inhibits these outputs.

Power Inputs (Pins 2 and 12)


A dc 11- to 19-V nonregulated power supply operates the clock IC. The positive of the power supply connects to the V_{SS} (pin 12), while the negative connects to V_{DD} (pin 2).

-\- Self-Test

Supply the missing word in each statement.

- Digital clock LSI chips are made using ———— (bipolar, MOS) technology.
- 37. Refer to Fig. 12-12. If pin 16 of the MM5314 is at GND, the clock IC is programmed for _____-Hz operation.
- 38. Refer to Fig. 12-12. If the slow set input to the MM5314 IC is grounded, the _____ counter is bypassed.
- 39. Refer to Fig. 12-12. The MM5314 MOS/LSI clock chip requires a(n) _____-\\nonnegulated power supply.

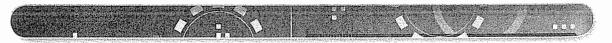- 41. The positive of the 12-V power supply is connected to the _____ (V_{DD}, V_{SS}) pin of the MM5314 clock chip.
- 42. The MM5314 clock chip ______ (has internal, needs external) waveshaping circuitry to square up the incoming 60-Hz signal.
- 43. The MM5314 clock chip needs an external _____ (crystal, resistor and capacitor) connected to the MUX timing pin of the IC.



12-6 The Frequency Counter

An instrument used by technicians and engineers is the *frequency counter*. A digital frequency counter shows in decimal numbers the frequency in a circuit. Counters can measure from low frequencies of a few cycles per second (hertz, Hz) up to very high frequencies of thousands of megahertz (MHz). Like a digital clock, the frequency counter uses decade counters.

As a review, the block diagram for a digital clock is shown in Fig. 12-14(a). The known frequency is divided properly by the counters in the clock. The counter outputs are decoded and displayed in the time display. Figure 12-14(b) shows a block diagram of a frequency counter. Notice that the frequency counter circuit is fed an *unknown* frequency instead of the known frequency in a digital clock. The counter circuit in the frequency counter in Fig. 12-14(b) also contains a *start/stop control*.

The frequency counter has been redrawn in Fig. 12-15(a). Notice that an AND gate has been added to the circuit. The AND gate

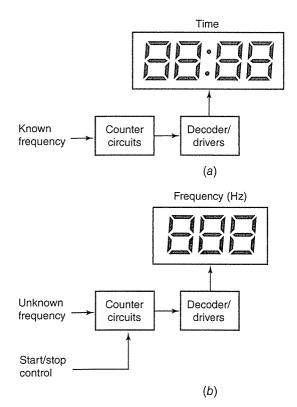


Fig. 12-14 (a) Simplified block diagram of a digital clock.
(b) Simplified block diagram of a digital frequency

controls the input to the decade counters. When the start/stop control is at logical 1, the unknown frequency pulses pass through the AND gate and on to the decade counters. The counters count upward until the start/stop control returns to logical 0. The 0 turns off the control gate and stops the pulses from getting to the counters.

Figure 12-15(b) is a more exact timing diagram of what happens in the frequency counter. Line A shows the start/stop control at logical 0 on the left and then going to 1 for exactly 1 s. The start/stop control then returns to logical 0. Line B diagrams a continuous string of pulses from the unknown frequency input. The unknown frequency and the start/ stop control are ANDed together as we saw in Fig. 12-15(a). Line C in Fig. 12-15(b) shows only the pulses that are allowed through the AND gate. These pulses trigger the up counters. Line D shows the count observed on the displays. Notice that the displays start cleared to 00. The displays then count upward to 11 during the 1 s. The unknown frequency in line B in Fig. 12-15(b) is shown as 11 Hz (11 pulses/s).

A somewhat higher frequency is fed into the frequency counter in Fig. 12-15(c). Again line A shows the start/stop control beginning at 0. It is then switched to logical 1 for exactly 1 s. It is then returned to logical 0. Line B in Fig. 12-15(c) shows a string of higher-frequency pulses. This is the unknown frequency being measured by this digital frequency counter. Line C shows the pulses that trigger the decade counters during the 1-s count-up period. The decade counters sequence upward to 19, as shown in line D. The unknown frequency in Fig. 12-15(c) is measured at 19 Hz.


If the unknown frequency were 870 Hz, the counter would count from 000 to 870 during the 1-s count period. The 870 would be displayed for a time, and then the counters would be reset to 000 and the frequency counted again. This reset-count-display sequence is repeated over and over.

Notice that the start/stop control pulse (count pulse) must be *very accurate*. Figure 12-16 shows how a count pulse can be generated by using an accurate known frequency, such as the 60 Hz from the power line. The 60-Hz sine wave is converted to a square wave by the waveshaping

Frequency counter

Start/stop control

Reset-count-display sequence

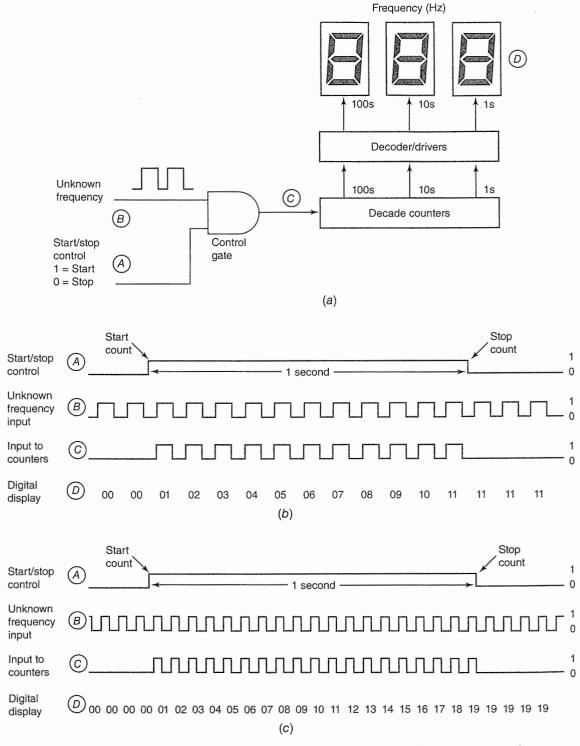

Digital frequency counter

Fig. 12-15 (a) Black diagram of a digital frequency counter showing the start/stop control. (b) Waveform diagram for an unknown frequency of 11 Hz. (c) Waveform diagram for an unknown frequency of 19 Hz.

circuit. The 60-Hz square wave triggers a counter that divides the frequency by 60. The output is a pulse *l* s in length. This *count pulse* turns on the control circuit when it goes HIGH and permits the unknown frequency to trigger the

counters. The unknown frequency is applied to the counters for 1 s.

Remember that the frequency counter goes through the reset-count-display sequence. So far we have shown only the count part of this

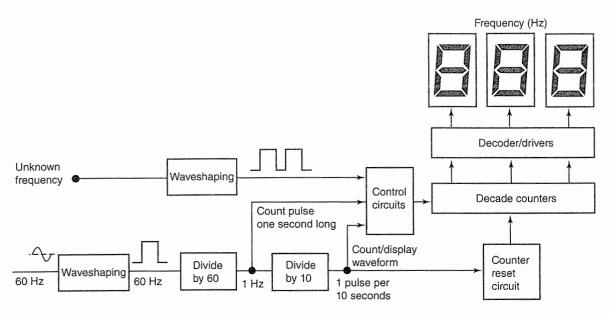


Fig. 12-16 More detailed block diagram of a digital frequency counter.

sequence. The counter reset circuit is a group of gates that reset, or clear, the decade counters to 000 at the correct time—just before the count starts. Next, the 1-s count pulse permits the counters to count upward. The count pulse ends, and the unknown frequency is displayed on the seven-segment displays. In this circuit, the frequency is displayed in hertz. It is convenient to leave this display on the LEDs for a time. To do this, the divide-by-10 counter sends a pulse to the control circuit, which turns off the count sequence for 9 s.

In summary, the events happen like this: (1) *Reset* the counters to 000; (2) *count* upward for a 1 s; and (3) *display* the unknown frequency for 9 s with no counts. This reset-count-display sequence is repeated every 10 s in this experimental frequency counter.

The frequency counter in Fig. 12-16 measures frequencies from 1 to 999 Hz. Notice the extensive use of counters in the divide-by-60, divide-by-10, and three decade counter circuits—hence the name *frequency counter*. The digital frequency counter actually counts the pulses in a given amount of time.

One limitation of the counter diagrammed in Fig. 12-16 is its top frequency; the maximum frequency that can be measured is 999 Hz. There are two ways to increase the top frequency of our counter. The first method is to add one or

more counter-decoder-display units. We could extend the range of the frequency counter in Fig. 12-16 to a top limit of 9999 Hz by adding a single counter-decoder-display unit.

The second method of increasing the frequency range is to count by 10s instead of 1s. This idea is illustrated in Fig. 12-17. A divide-by-6 counter replaces the divide-by-60 unit in our former circuit. This makes the *count pulse* only 0.1 s long. The count pulse permits only one-tenth as many pulses through the control as with the 1-s pulse. This is the same as counting by 10s. Only three LED displays are used. The 1s display in Fig. 12-17 is only to show that a 0 must be added to the right of the three LED displays. The range of this frequency counter is from 10 to 9990 Hz.

In the circuit in Fig. 12-17, the decade counters count upward for 0.1 s. The display is held on the LEDs for 0.9 s. The counters are then reset to 000. The count-display-reset procedure is then repeated. The circuit in Fig. 12-17 has one other new feature: During the count time the displays are blanked out. They are then turned on again when the unknown frequency is on the display. The sequence for this frequency counter is then reset, count (with displays blank), and, finally, the longer display period. This sequence repeats itself once every second while the instrument is being used.

Counter reset circuit

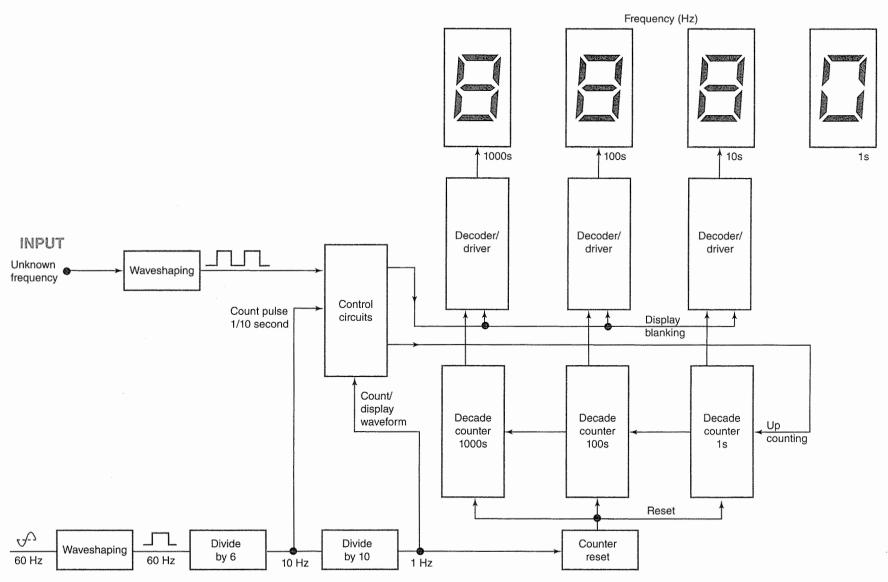


Fig. 12-17 Detailed block diagram of an experimental digital frequency counter with a frequency range from 10 to 9990 Hz.

-₩- Self-Test

Supply the missing word in each statement.

- 44. Refer to Fig. 12-15. This digital frequency counter counts the number of pulses passing through the AND gate in ______s.
- 45. Refer to Fig. 12-15. If the start/stop control to the AND gate is LOW, the signal at output *C* is a _____ (HIGH, LOW, square wave).
- 46. Refer to Fig. 12-16. The waveshaping blocks might be implemented using TTL _____ (XOR gates, Schmitt-trigger inverters).

- 47. Refer to Fig. 12-16. The divide-by-60 block might be implemented using _____ (counters, shift registers).
- 48. Refer to Fig. 12-17. The count pulse is ______ s long in this frequency counter.
- 49. Refer to Fig. 12-17. The unknown frequency input waveform is conditioned by a(n) _____ circuit before entering the control circuitry of the counter.
- 50. Refer to Fig. 12-17. The decade counters serve the dual purpose of counting upward and ______ the count for display.



12-7 An Experimental Frequency Counter

This section is based on an experimental frequency counter circuit purposely designed using only components you have already used earlier in the book. This experimental instrument is not as accurate or stable as commercial units. Its maximum frequency is also limited to 9990 Hz, and its inputs are somewhat primitive. A schematic diagram of the primitive frequency counter is detailed in Fig. 12-18.

The purposes for including the experimental frequency counter are as follows:

- To show how SSI and MSI chips may be used to build digital subsystems and systems.
- To demonstrate the concepts involved in the design and operation of a frequency counter.

Figure 12-17 is a block diagram of the frequency counter. Most components in the wiring diagram are in the same general position as in the block diagram.

At the lower left in Fig. 12-18, a 60-Hz sine wave is shaped into a square wave. The 60-Hz signal may come from the secondary of a

low-voltage power transformer. The *waveshaping* is done by the 7414 Schmitt-trigger inverter. Remember that the divide-by-6 counter needs a square-wave input to operate properly.

To the right of the lower 7414 inverter is a divide-by-6 counter. Three flip-flops (FF1, FF2, and FF3) and a NAND gate are wired to form the mod-6 counter. The frequency going into the divide-by-6 counter is 60 Hz; the frequency coming out of the counter (at Q of FF3) is 10 Hz. The 10 Hz is fed into the 7493 IC wired as a decade or divide-by-10 counter.

Figure 12-18 shows that the four outputs from the 7493 counter are NORed together (OR gate and inverter). The four-input NOR gate generates a 1-Hz signal. This 1-Hz signal is called the count/display waveform. The count/ display waveform is HIGH for exactly 0.1 s and low for 0.9 s. The count/display waveform is fed back into the 7400 control gate. When the counter/display waveform is HIGH for 0.1 s, the unknown frequency passes through the NAND gate on to the clock input of the 10s counter. When the count/display waveform is LOW for 0.9 s, the unknown frequency is blocked from passing through the NAND control gate. It is during the 0.9 s that you may read the frequency off the seven-segment LED displays.

Experimental frequency counter Waveshaping

Divide-by-6 counter

Divide-by-10 counter

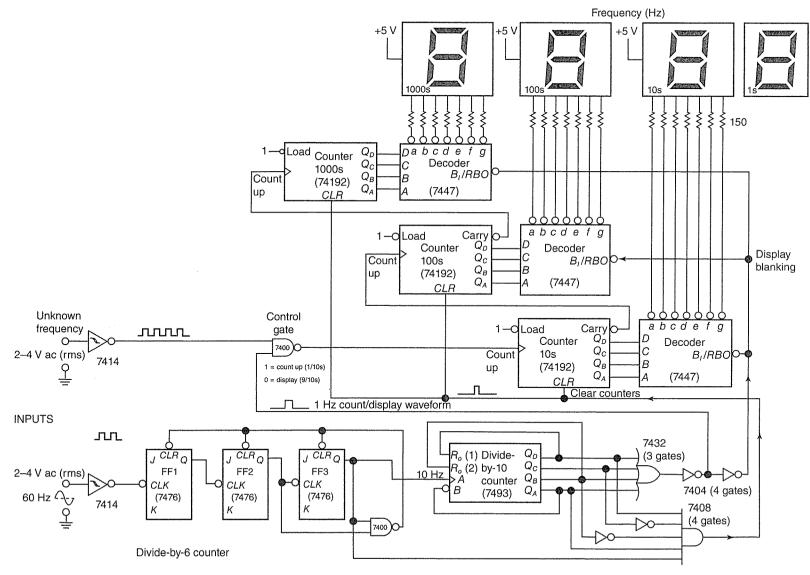


Fig. 12-18 Wiring diagram for an experimental digital frequency counter.

The frequency counter goes through a reset-count-display sequence. The reset pulse is generated by the five-input AND gate near the lower right in Fig. 12-18. It clears the 10s, 100s, and 1000s counters to zero. The reset (or counter clear pulse) is a very short positive pulse that occurs just before the counting occurs.

Next in the reset-count-display sequence is the *count* or *sampling time*. When the count/ display waveform goes HIGH, the control gate is enabled and the unknown frequency passes through the NAND gate to the clock input of the 10s counter. Each pulse during this *sampling time* increments the 10s counter. When the 10s counter goes from 9 to 10, it carries the 1 to the 100s counter. After 0.1 s the count/ display waveform goes LOW. This is the end of the sampling time. You will notice that the unknown frequency that was sampled causes the frequency to increase by 10s.

Last in the reset-count-display sequence is the *display time*. When the count/display waveform goes LOW, the control gate is disabled. It is during this time that a stable frequency display may be read from the LEDs. Notice that an extra 1s display has been added in Fig. 12-18 to remind you that a 0 must be added to the right of the three active displays for a readout in hertz.

To make the displays look better, display blanking occurs during the count time of the reset-count-display sequence. The displays

light normally with a stable readout during the display time. The display blanking waveform is a 0.1-s negative pulse generated by a 7404 inverter off the count/display waveform line. It causes the three displays to blank out for 0.1 s during the count time. The blanking does cause the displays to flicker. This problem could be cured by the use of latches to hold data on the inputs of the decoders.

For the most part commercial frequency counters operate like the one in Fig. 12-18. Commercial counters usually have more displays and read out in kilohertz and megahertz. The experimental frequency counter needs an input signal of about 3 to 8 V to make it operate. Commercial counters usually have an amplifier circuit before the first waveshaping circuit to amplify weaker signals to the proper level. Overvoltage protection is also provided with a zener diode. To get rid of the blinking of the display, commercial counters usually use a slightly different method of storing and displaying the contents of the counters. We used the power-line frequency of 60 Hz as our known frequency. Commercial frequency counters usually use an accurate high-frequency crystal oscillator to generate their known frequency.

Some of the important specifications of commercial frequency counters are the *frequency* range, input sensitivity, input impedance, input protection, accuracy, gate intervals, and display time.

Reset-count-display sequence

Sampling time (count time)

Display blanking

-W- Self-Test


Supply the missing word(s) or number in each statement.

- 51. Refer to Fig. 12-18. FF1, FF2, FF3, and the NAND gate form a(n) ______ counter.
- 52. Refer to Fig. 12-18. The count time for this frequency counter is ______s, while the display time is _____s.
- 53. Refer to Fig. 12-18. The sampling time of the frequency counter is also called the _____ (count, display) time.
- 54. Refer to Fig. 12-18. The five-input AND gate generates a counter clear or

pulse. This is a
(negative, positive) pulse.

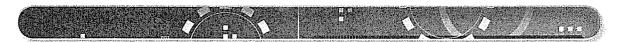- 55. Refer to Fig. 12-18. The display blanking pulse is generated during the _____ (count, display) time. This is a _____ (negative, positive) pulse.
- 56. Refer to Fig. 12-18. The 7414 IC is called a(n) _____ inverter. The 7414 inverters are used for _____ shaping in this circuit.
- 57. Refer to Fig. 12-18. Each pulse from the unknown frequency that reaches the

- counter increases the frequency reading by ______(1, 10, 100) Hz.
- 58. Refer to Fig. 12-18. The frequency range of this experimental counter is from a low of ______ Hz to a high of _____ Hz.
- 59. Refer to Fig. 12-18. The gate interval for the experimental frequency counter is 0.1 s while the display time is ______ seconds.
- 60. Refer to Fig. 12-18. The known frequency entering the experimental counter is _____ Hz.
- 61. Refer to Fig. 12-18. The ______ (7447 decoder ICs, 74192 counter ICs) function as temporary memory devices to hold the highest count during the display time.




Display

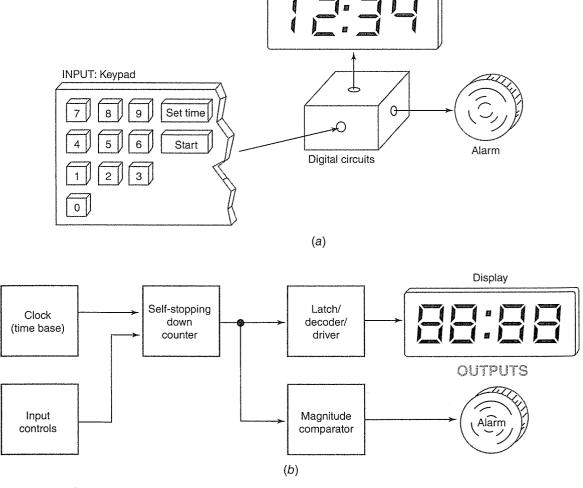12-8 LCO Timer with Alarm

Most microwave ovens and kitchen stoves feature at least one timer with an alarm. Older appliances used mechanical timers, but modern

microwaves and ranges feature electronic timers using digital circuitry. The concept of a timer system is sketched in Fig. 12-19(a). In this system, the keypad is the input and both



LCD timer circuit

Fig. 12-19 Digital timer system. (a) Concept sketch of timer with alarm. (b) Simple block diagram of timer with alarm.

the digital display and alarm buzzer are the output devices. The processing and storage of data occur within the digital circuits block in Fig. 12-19(a).

A somewhat more detailed block diagram of a digital timer is shown in Fig. 12-19(b). The digital circuits block has been subdivided into four blocks. They are the time-base clock, the self-stopping down counter, the latch/decoder/ driver, and the magnitude comparator. The input controls block presets the time held in the down counter. The time base is an astable multivibrator which generates a known frequency. In this case, the signal is a 1-Hz square wave. The accuracy of the entire timer depends on the accuracy of the time-base clock. Activating the start input control causes the down counter to decrement. Each lower number is latched and decoded by the latch/decoder/driver. This block also drives the display.

The illustrations in Fig. 12-19 might be preliminary sketches used by a designer in visualizing a timer system. The designer might next decide on what type of input, output, and processing technologies to use to implement the system.

A somewhat more detailed block diagram of a digital electronic timer system is drawn in Fig. 12-20. The designer decided to use a two-digit LCD along with low-power CMOS ICs. This system was designed with your lab trainers in mind, so the inputs are logic switches to simplify the input section. The designer decided on seconds as the time interval. Notice that each block roughly corresponds to an MSI digital IC or input/output device. A wiring diagram could then be developed from the detailed block diagram in Fig. 12-20.

The block diagram in Fig. 12-20 represents an experimental LCD timer with alarm that you might construct in the laboratory. The timer is operated as follows:

- 1. Set the load/start control to 0 (load mode).
- 2. Load the 1s counter by setting a BCD number using the top four switches.
- 3. Load the 10s counter by setting a BCD number using the bottom four switches.
- A two-digit number should now be displayed on the LCD.

5. Move the load-start control to 1 (start down count mode).

The timer will start counting downward in seconds. The LCD shows the time remaining before the alarm sounds. When both counters reach zero, the LCD reads 00 and the alarm will sound. The final step is to disconnect the power to the circuit to turn off the alarm.

A wiring diagram for the *experimental LCD* timer circuit is detailed in Fig. 12-21. Notice that each IC is placed in the same relative position on the wiring diagram as in the block diagram in Fig. 12-20.

Detailed operation of the LCD timer circuit in Figs. 12-20 and 12-21 follows.

Time Base

The *time-base clock* is a 555 timer IC wired as a free-running MV. It is designed to generate a 256-Hz square wave. The time-base clock in this experimental timer is not very accurate or stable. It can be calibrated by adjusting the value of resistor R_1 . The nominal value of R_1 should be about 20 k Ω .

The second part of the time base is the divide-by-256-counter block. The function of this block is to output a 1-Hz signal. The divide-by-256-counter block is actually two 4-bit counters wired together. Figure 12-22 shows the two 4-bit units wired as divide-by-16 counters. Note that the \overline{CP} inputs are clock inputs and only the Q_D outputs are used. The first divide-by-16 counter divides the frequency from 256 to 16 Hz (256/16 = 16 Hz). The second counter divides the frequency down to the required 1-Hz output (16/16 = 1 Hz).

Self-Stopping Down Counters

The two 74HC192 decade counters are the 74HCXXX series equivalent to the 74192 TTL IC detailed in Chapter 8. When the load inputs to the 74HC192 counters are activated by a LOW, data at the data inputs (A, B, C, D) are immediately transferred into the counter's flip-flops. They then appear at the outputs of the counter (Q_A, Q_B, Q_C, Q_D) . The data loaded should be in BCD (binary-coded decimal) form. When the load/start control goes HIGH, the 1-Hz signal activates the count down input

Experimental timer circuit

Time-base clock

Divide-by-256counter block

Down counters

Experimental LCD timer

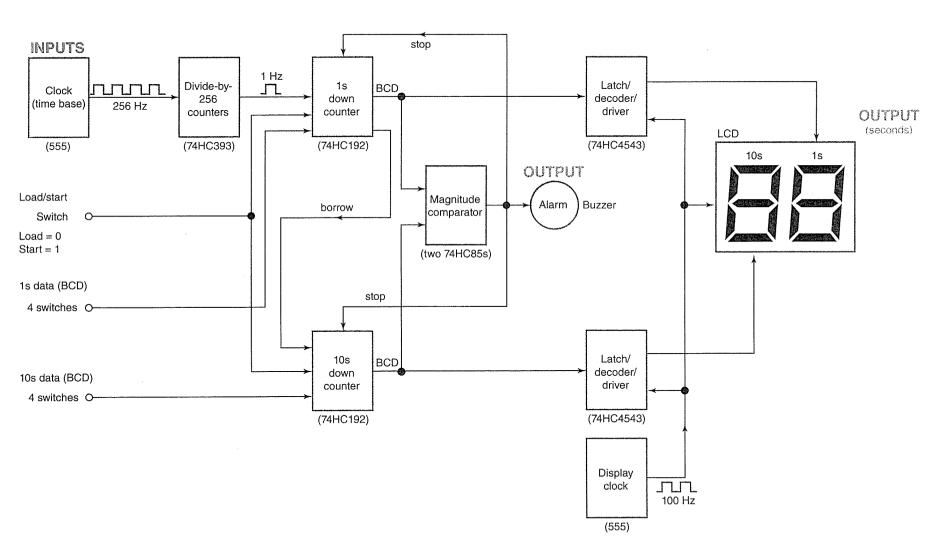


Fig. 12-20 Detailed block diagram of an experimental LCD timer with alarm.

of the 1s counter. The count decreases by 1 on each L-to-H transition of the clock pulse. The *borrow out* output of the 1s down counter goes from L to H when the 1s counter goes from 0 to 9. This decrements the 10s counter. The down counters are actually wired as a self-stopping down counter because of the *counter stop line* fed back to the CLR input of both 74HC192 counters. When this line goes HIGH, both counters stop at 0000.

8-Bit Magnitude Comparator

The 74HC85 4-bit comparators are shown cascaded in Fig. 12-21 to form an 8-bit-magnitude comparator. Their purpose in this circuit is to detect when the outputs of the counters reach $0000\ 0000_{\rm BCD}$. When both counters reach zero, the output of the 8-bit magnitude comparator ($A=B_{\rm out}$) goes HIGH. This serves two purposes. First, it stops both 74HC192 counters at 0000. Second, the HIGH at the output of the comparator turns transistor Q_1 on. This allows current to flow up through the transistor, sounding the buzzer. The diode across the buzzer suppresses

transient voltages that may be generated by the buzzer.

Decoder/Driver

The two 74HC4543 ICs used in the timer circuit serve three purposes. The functions of the 74HC4543 IC are summarized in Fig. 12-23. The latch disable (*LD*) input is permanently tied HIGH in the timer circuit (Fig. 12-21), which disables the latches. The BCD data flows through the latch to the BCD-to-seven-segment decoder. The decoder translates the BCD input to seven-segment code. Finally, the driver circuitry in the 74HC4543 chip energizes the correct segments on the LCD.

The *display clock* shown at the lower right in Fig. 12-21 generates a 100-Hz square wave. This is sent to the common (backplane) connection on the LCD and the *Ph* inputs of the 74HC4543 ICs. The LCD driver in the 74HC4543 chip sends inverted or 180° out-of-phase signals to the LCD segments that are to be activated. Segments that are not activated receive an in-phase square-wave signal from the LCD driver section of the 74HC4543 IC.

Decoder/driver


8-bit magnitude comparator

-√\- Self-Test

Answer the following questions.

- 62. Refer to Fig. 12-21. The accuracy of the entire timer depends on the frequency generated by the _____ clock.
- 63. Refer to Fig. 12-21. The initial numbers to be loaded into the counters in the timer must be entered in ______ (BCD, binary, decimal) form.
- 64. Refer to Fig. 12-21. What two components are considered output devices in this timer circuit?
- 65. Refer to Fig. 12-21. When the count reaches zero, the output $(A = B_{out})$ of the 8-bit magnitude comparator goes _____ (HIGH, LOW). This causes the counter stop line to go _____

- (HIGH, LOW), stopping the counters. This also turns _____ (off, on) the transistor causing it to conduct electricity and sound the buzzer.
- 66. Refer to Fig. 12-21. The driver section of the 74HC4543 IC sends an ______ (in-phase, out-of-phase) square-wave signal to the LCD segments that are to be activated.
- 67. Refer to Fig. 12-21. The display clock sends a 100-Hz square-wave signal to the ______ inputs of both 74HC4543 ICs and the _____ connection on the LCD.
- 68. The timer circuit in Fig. 12-21 is calibrated in (minutes, seconds, tenths of a second).

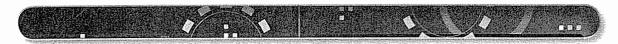


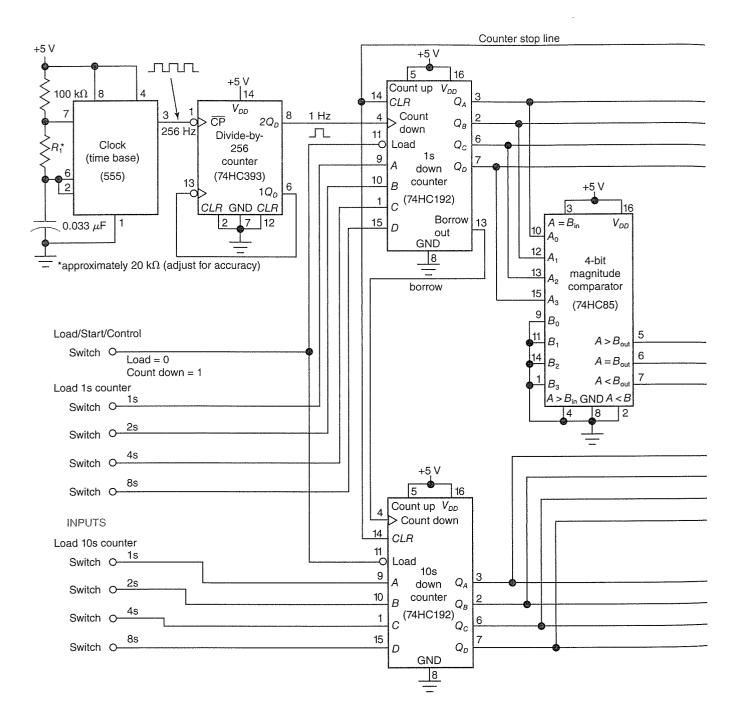


Fig. 12-21 Wiring diagram for an experimental LCD timer with alarm.

Experimental LCD timer with alarm

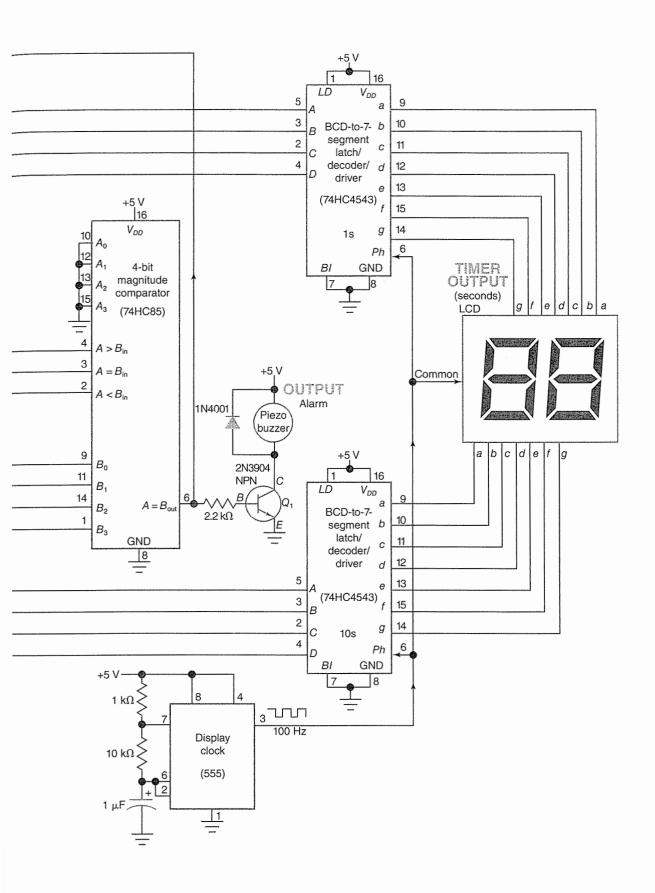

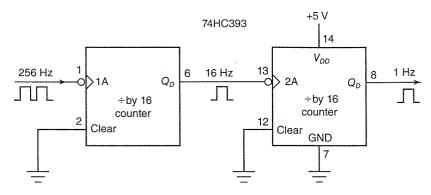


Fig. 12-22 Wiring a divide-by-256 block using two divide-by-16 counters.

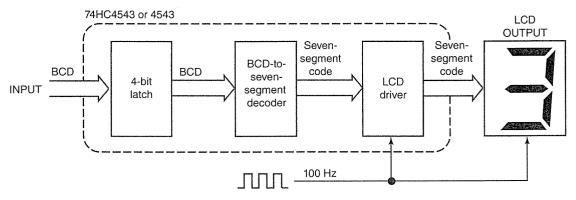


Fig. 12-23 Internal organization of the 74HC4S43 IC including latch, decoder, and driver sections.

12-9 Simple Distance Sensing

Electronic distance sensors may be categorized by the technology used in the device. Five common distance-sensing technologies are (1) infrared light, (2) ultrasonic sound, (3) laser narrow light beam, (4) sonar (sound navigation and ranging), and (5) radar (radio detection and ranging). Both infrared and ultrasonic technologies are used in simpler low-cost distance sensors.

Infrared-light Distance Sensor

An infrared-light distance sensor can measure distance to an object using one of the methods sketched in Fig. 12-24. The method shown on the left in Fig. 12-24(a), uses pulses from an IR LED emitting infrared light which reflect off the target surface. The reflected light enters the lens of the IR detector (phototransistor). The lens shines IR light on the base of the IR phototransistor. More IR light means the transistor will have greater conduction, while less light means less emitter-to-collector current flow. With a pull-up resistor added to the collector of the phototransistor, the change in

emitter-to-collector resistance will be converted in a change in output voltage (a signal).

The method shown on the right in Fig. 12-24(b) uses an IR LED emitting pulses of infrared light which reflect off the target surface. The reflected light enters the lens of the special IR detector. The light striking the sensor is fed to a signal processor. The signal processor inside the DIP distance sensor unit uses the triangulation method of calculating the distance to the target (reflective surface). As diagrammed in Fig. 12-24(b), the smaller the angle between the IR light beam and the perpendicular, the greater the distance to the target. In like manner, a greater angle between the IR light beam and perpendicular is interpreted as a shorter distance to the target. The special IR detector linked to the signal processor generates an output. Depending on the model of distance measuring sensor, the output signal may be either analog or digital.

Ultrasonic Distance Sensor

An ultrasonic distance sensor, sketched in Fig. 12-25, emits a burst of sound energy. The

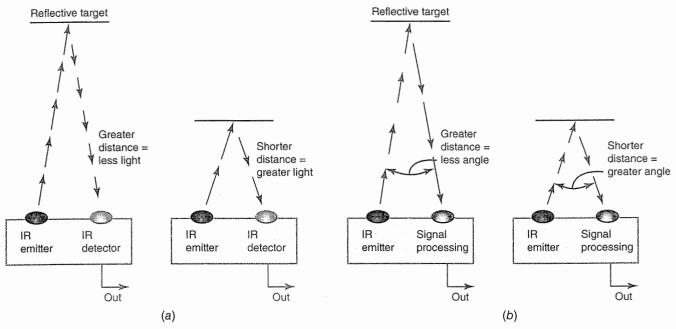


Fig. 12-24 IR distance sensor operation. (a) Traditional IR emitter and IR detector (IR phototransistor). (b) Distance-measuring sensor using the triangulation method of measurement.

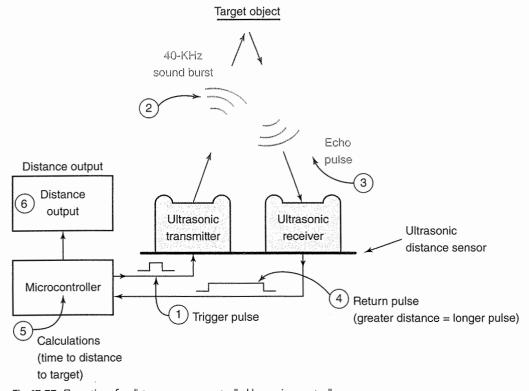


Fig. 12-25 Operation of a distance sensor controlled by a microcontroller.

sound burst bounces off the target and returns as an echo, activating the ultrasonic receiver. The amount of time it takes for the ultrasonic burst to reach the target and return to the receiver is passed on to the control unit (commonly a microcontroller). A control unit then calculates the distance and outputs the information (to an operator or as feedback to a machine).

A more detailed view of the operation of an ultrasonic distance sensor is enumerated in Fig. 12-25. Notice that the ultrasonic distance sensor is under the control of a microcontroller.

The sequence of events to measure the distance from the sensor to the target object is as follows:

1. The microcontroller outputs a short trigger pulse to the transmitter.

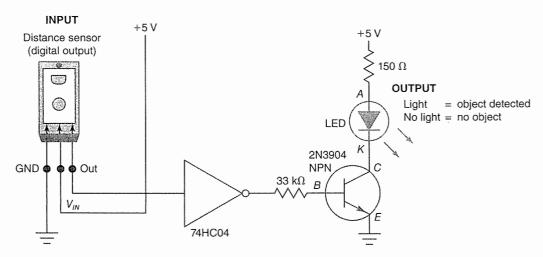


Fig. 12-26 Test circuit for the Pololu 1134 digital distance sensor.

- 2. The ultrasonic transmitter emits a short burst of sound energy.
- 3. After the sound bounces off the target, it is referred to as the echo pulse and returns to be interpreted by the ultrasonic receiver.
- 4. The ultrasonic receiver emits a pulse that represents the time it took the sound to travel from the transmitter, to bounce off the target, and for its echo to return to the receiver. The greater the sensorto-target distance, the greater the time duration of this pulse. Note that the sound has traveled twice the distance from the sensor to the target.
- 5. The microcontroller calculates the sensor-to-target distance based on constants, such as the speed of sound in air (about 1100 ft/s). The calculation must also reflect the fact that the sound burst traveled twice the distance from the sensor to the target.
- The microcontroller generates an appropriate distance output (on a display device or it is used to control the action of a machine such as a robot).

The BASIC Stamp 2 module by Parallax can be used with an ultrasonic distance sensor to measure distances. The unit commonly used with the microcontroller is the PINGTM ultrasonic distance sensor by Parallax.

Testing a Distance Sensor

Two technologies used in an infrared distance sensor are summarized in Fig. 12-24. The first

is the traditional method (IR LED as emitter and IR phototransistor as detector). The second sensor uses the triangulation method of measurement. The IR distance sensor to be tested will be the newer type that operates like the unit in Fig. 12-24(b).

The simple test circuit drawn in Fig. 12-26 will detail the operation of the Pololu Corporation sensor 1134. The unit is described as *Pololu carrier with sharp GP2Y0D810Z0F digital distance sensor 10 cm*. This sensor detects objects between 2 and 10 cm (0.8 and 4 in.) away. Because it only has a digital (HIGH or LOW) output it will detect an object in its range but cannot be used to calculate the exact distance. It could be useful as a break-beam sensor, noncontact bumper or obstacle as used on mobile robots, or counter/timer of objects as they pass in front of the sensor.

The Pololu distance sensor module is shown in Fig. 12-26 in its physical form (not a schematic diagram). The output from the distance sensor is HIGH when it is not detecting on object in its range. When an object is detected in the sensor's range (2–10 cm), the output pin will go LOW. The test circuit in Fig. 12-26 uses the 74HC04 inverter to drive the NPN transistor. When the output of the inverter is LOW, the transistor is turned off and the LED does not light. An object detected by the distance sensor causes a LOW output that is passed on to the inverter. The inverter's output goes HIGH, turning on the transistor and lighting the LED.

Noncontact Operation with Distance Sensor

Imagine a device that operates like the automatic paper-towel dispenser found in many public bathrooms. Can you *envision* a simple system that might operate an electric motor or stepper motor for only a short period of time using a distance sensor? Can you *invent* the simple system you imagined? An *idea sketch* in block diagram form will help clarify your imagined system. A few requirements of the system might be listed below each block in your

system. Limit yourself to components that you have experienced (in the textbook and experiments manual).

The sketch in Fig. 12-27(a) outlines the simple system that was envisioned. Brief notes below each block help define the details needed to construct the simple system. Some of the useful notes under blocks include:

- 1. Detector: Distance sensor with digital outputs, short range.
- 2. Trigger timing circuit to stay on for 2 to 4 s. Turn off. Wait for next trigger. Clock

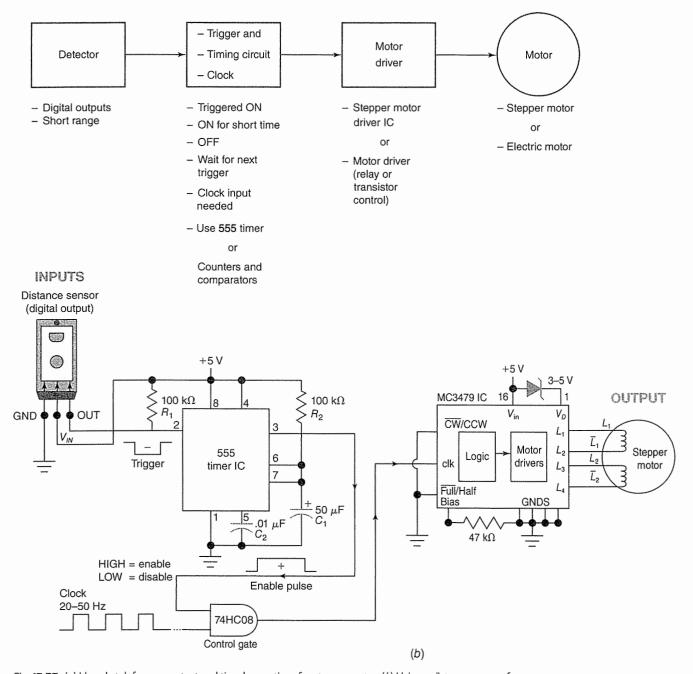


Fig. 12-27 (a) Idea sketch for noncontact and timed operation of a stepper motor. (b) Using a distance sensor for noncontact operation of a stepper motor.

- input needed for timing circuit. Easiest solution for timing circuit seems to be the 555 timer.
- 3. Motor driver: Decide type of output (electric motor or stepper motor). Stepper motor is chosen.
- 4. Motor: Stepper or regular electric motor. Stepper motor is chosen.

A schematic diagram of a circuit using a digital distance sensor for noncontact operation of a stepper motor is detailed in Fig. 12-27(b). This circuit simulates the operation of a noncontact paper-towel dispenser found in many public bathrooms.

The digital distance sensor used in Fig. 12-27(b) is the Pololu 1134 unit tested in Fig. 12-26. The distance sensor generates a LOW output when an object is detected in its range (2 cm to 10 cm). The LOW trigger pulse at the input to the 555 timer IC (pin 2) causes its output (pin 3) to go HIGH for a few seconds. The HIGH at the top input of the control gate (AND gate) allows the 20- to 50-Hz clock pulses to be passed on to the clock input of the MC3479 stepper motor controller IC. The stepper motor rotates in a CW direction as long as clock pulses enter the clk input of the MC3479

IC. The stepper motor would engage the mechanics of the dispenser and cause the paper towels to be delivered. The 555 timer IC circuit is designed to disable the control gate with a LOW after about 2 to 4 s. The rotation of the stepper motor can be increased by increasing clock frequency. This rotation could also be adjusted by changing the value of capacitor C_1 in the timer circuit. Decreasing the value of C_1 would decrease the time that the output (pin 3) of the 555 timer IC remains HIGH.

Another solution to the automatic papertowel dispenser is detailed in Fig. 12-28. In this simple solution, the distance sensor triggers the same 555 timer circuit used in Fig. 12-27. When activated by an object, such as the wave of a hand, the digital distance sensor emits a negative pulse, triggering the 555 timer IC. This generates a 2- to 4-s positive pulse, turning on the NPN transistor. The transistor conducts through the coil of the relay, the NO contacts of the relay snap closed, and the dc motor is energized and rotates. After a delay of about 2 to 4 s, the output of the 555 timer IC (pin 3) returns to LOW. This turns off the NPN transistor. The coil of the relay is no longer energized. The NO relay contacts spring open, causing the dc motor to stop rotating.

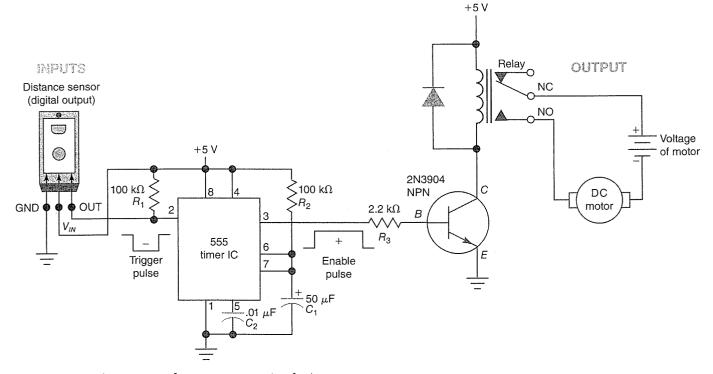


Fig. 12-28 Using a distance sensor for noncontact operation of a dc motor.

The distance sensor used in this circuit is the same one used in Fig. 12-27(b). It is enabled by sensing an object in range (2 to 10 cm). The Pololu 1134 sensor module features a digital output (enabled = LOW, disabled =


HIGH). The time the motor runs can be adjusted by changing the value of capacitor C_1 in the timer circuit. Decreasing the capacitance value of C_1 will decrease the time the motor rotates.

Self-Test

Answer the following questions.

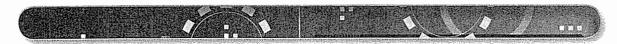- 69. Five common distance-sensing technologies include RADAR, SONAR, Y-modulus, ultrasonic sound, and blue-ray. (T or F)
- 70. Refer to Fig. 12-24(a). The IR emitter applies an infrared diode, while the IR detector uses an IR ______ (phototransistor, ring counter).
- 71. Refer to Fig. 12-24(b). This distance-measuring sensor applies the ______ (9s complement, triangulation) method for calculating the distance to the reflecting target.
- 72. Refer to Fig. 12-24(*b*). The special IR detector's output feeds a _____ (demodulator, signal processing) circuit, generating either an analog or digital output signal.
- 73. Refer to Fig. 12-25. The ultrasonic distance sensor is used with a control unit. The control unit is commonly a _____ (laptop computer, microcontroller).
- 74. Refer to Fig. 12-25. With an ultrasonic sensor, the distance is measured by using the *volume of sound* returned to the ultrasonic receiver. (T or F)
- 75. Refer to Fig. 12-26. The range of the Pololu 1134 distance sensor is about

- _____ (4, 36) in. maximum and its output is _____ (analog, digital).
- 76. Refer to Fig. 12-26. When the distance sensor detects an object in its range, the output goes ______ (HIGH, LOW), the output of the inverter goes _____ (HIGH, LOW), the transistor is turned on, and the LED _____ (lights, does not light).
- 77. Refer to Fig. 12-27(b). A negative trigger pulse from the distance sensor causes the output of the 555 timer IC (pin 3) to go
 ______ (HIGH, LOW), enabling the AND control gate.
- 78. Refer to Fig. 12-27(b). Clock pulses are _____ (blocked, passed through) when the control gate is enabled, causing the MC3479 IC to drive the stepper motor.
- 79. Refer to Fig. 12-28. When the distance sensor module is activated, its output goes _____ (HIGH, LOW), which triggers the 555 timer IC to output a HIGH enable pulse.
- 80. Refer to Fig. 12-28. The motor operates as long as the enable pulse at the output of the 555 timer IC is HIGH, turning the transistor on and snapping the _____ (NC, NO) contacts of the relay closed.



12-10 JTAG/Boundary Scan

It is important to be able to test digital systems and subsystems for proper operation, both at place of manufacture and in the field. Semiconductor manufacturers continue to increase the complexity of digital circuitry built into ICs. Many ICs

contain complete digital systems on a single chip. Other technologies such as surface-mount technology and multilevel PC boards have both increased the number of components on printed circuit boards and shrunk their size. This miniaturization has resulted in a loss of access points for testing system and subsystem operation.

In the mid-1980s, the Joint Test Action Group developed a solution to this problem of loss of test point access on PC boards. The solution it developed was a new testing architecture that added testing ability and test access points into integrated circuits. The Institute for Electrical and Electronic Engineers (IEEE) later formalized this solution as Standard 1149.1 Test Access Port and Boundary-Scan Architecture. The boundary-scan architecture is commonly referred to as *boundary scan* or *JTAG*. JTAG is in reference to the group (Joint Test Action Group) that developed the system. Some ICs and printed circuit boards now have this additional testing subsystem built into them.

Boundary scan or JTAG

A simplified JTAG compliant IC is shown in Fig. 12-29. The main JTAG elements are shown in yellow, pink, and red. The black lines in the drawing represent the IC's regular input and output lines. The red lines at the bottom of Fig. 12-29 are the chip's test access port (TAP). The four solid red lines, TDI (test data input), TDO (test data output), TMS (test mode select), and TCK (test clock), provide a standard four-wire serial interface for test access to the chip. The dashed line represents the test reset (TRST) input, which is an optional fifth wire for resetting the test access port. The other

required boundary-scan elements are the instruction register, the bypass register, the TAP controller, and at least one test data register. JTAG compliant ICs may have more than one test data register; however, one of the test data registers must be the boundary-scan register. The boundary-scan register is made up of a series of boundary-scan cells (BSCs). The ten square yellow boxes in Fig. 12-29 represent the boundary-scan cells that make up the boundary-scan register in this example IC. The right side of Fig. 12-29 shows an exploded view of a boundary-scan cell. Notice that a boundaryscan cell may consist simply of two 2-input multiplexers and two flip-flops. The chip's TAP controller controls the multiplexers and flipflops in the boundary-scan cells.

The TAP controller and the *instruction register* shown at the left in Fig. 12-29 make up the control section of the boundary-scan architecture. Serial data at the TMS input pin, read during the rising edge of the clock input to TCK, sets the TAP controller into one of many possible *states*. The state of the TAP controller determines if (1) the boundary-scan test system is reset, (2) if the test specified by the instruction in the instruction register is run, (3) if the serial data at the TDI input pin are shifted into the

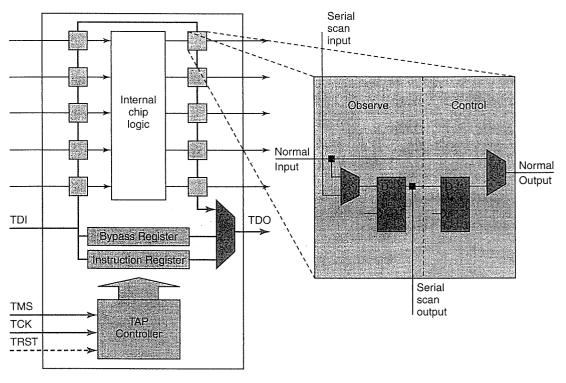


Fig. 12-29 JTAG compliant IC.

instruction register, with the previous instruction in the register shifted out through the TDO output pin, or (4) if the serial data at the TDI input pin are shifted through one of the test data registers and the previous data in the register shifted out through the TDO output pin. If the instruction register is loaded with the bypass instruction and the TAP controller is in the run test state, then data at the TDI input pin instead pass through the 1-bit bypass register. The 1-bit bypass register shortens the shifting path of data from other ICs through the chip when the chip is not part of the test being run on a circuit board containing many JTAG ICs. This can significantly speed up the testing of systems and subsystems on pc boards.

JTAG-compliant ICs must also implement two other required instructions. The extest (external test) instruction allows testing of components and interconnections external to the chip to be tested without the risk of damaging the internal chip logic. When the extest instruction is run, boundary-scan cells at the chip's input pins sample the incoming data, and the BSCs at the output pins output their data to the chip's output pins. During the extest instruction, the TAP controller may prevent the data at the chip's input pins from reaching the internal chip logic in order to prevent damage to the IC. The other required instruction, sample/preload, has two functions. The first function is to take a snapshot, or sample, of the data flowing into or out of the internal chip logic without interrupting the normal operation of the chip. The second function of the sample/preload instruction is to preload known test data into the boundaryscan cells of the IC before running other tests. Semiconductor manufacturers may also build in other test types that can be decoded by the instruction register in their JTAG-compliant ICs. The additional tests specified by the manufacturer may test the entire system on the IC or specific subsystems of the IC.

Figure 12-30 shows a simplified circuit board that makes use of the boundary-scan architecture. The TAP connector at the bottom of the circuit board in Fig. 12-30 is typically connected to a computer. Test data from the computer can be loaded in parallel, possibly through a UART, and passed to the TAP serially. Serial data out from TDO (test-data output) are converted back to parallel data and read back into

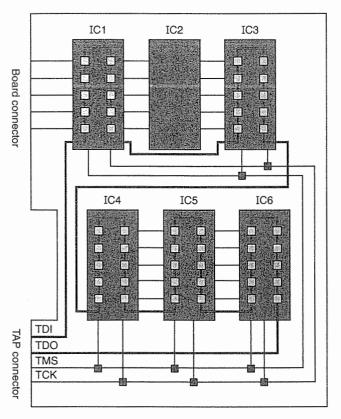


Fig. 12-30 Simplified PC board with six ICs. Five of the ICs are JTAG-compliant using boundry-scan architecture.

the computer. All of the digital subsystems on this circuit board can be tested using automated tests run by a computer. This testing is quicker, more accurate, and less expensive than conventional testing of circuit boards.

The yellow squares on IC1 and IC3 through IC6 in Fig. 12-30 represent the boundary-scan cells (BSCs) built into the chips, the same as they are represented in the single IC shown in Fig. 12-29. The boundary-scan cells can be used to control or observe the values at each IC's inputs and outputs. Serial test data are shifted in through test data input (TDI) on the rising edge of the clock input at TCK. Serial output is observed at the test data output (TDO) on the falling edge of the clock pulse.

Notice that this circuit board has five JTAG ICs and one non-JTAG IC. The placement of JTAG ICs IC1 and IC3 on either side of the non-JTAG IC allows IC2 (the non-JTAG IC) to be tested for proper operation. To test IC2 for proper system operation, a series of input test data values known as *test vectors* is loaded into the output boundary-scan cells of IC1. IC1 and IC3 are then instructed to run the extest instruction, and the output of IC2 is observed

at the input BSCs of IC3. Comparison of the observed inputs at IC3 to the expected outputs of IC2 will confirm the proper operation of IC2. Some other types of tests that might be performed on this circuit board include (1) verifying the proper operation of each of the JTAG-compliant ICs on the board (IC1, IC3–IC6), (2) checking the interconnections (*nets*) between IC4 and IC5 as well as between IC5 and IC6, and (3) observing how the entire system is reacting to the normal system inputs from the board connector.


To summarize, testing is an important part of any complex system. The loss of test access points on printed circuit boards has made boundary scan an important subsystem of many digital systems. The boundary-scan architecture makes testing and correcting problems in digital systems both quicker and easier. Boundary scan is likely to become more widely used as digital systems continue to get more complicated and testing of those systems becomes more difficult because of their miniature size.

-√- Self-Test


Answer the following questions.

- 81. Boundary-scan testing is commonly known as _____ [four letters] referring to the name of the original group that worked on this method.
- 82. A series of test values used during a boundary-scan test procedure might be called ______ (arguments, test vectors).
- 83. The nickname for interconnections in the vocabulary of boundary-scan technology would be ______ (ICs, nets).
- 84. The test access port input/output connection to a JTAG-compliant pc board uses the acronym _____ [three letters].
- 85. JTAG is an acronym for _____ in the field of boundary-scan technology.

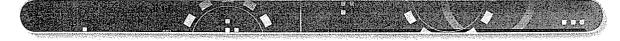- 86. JTAG-compliant PC boards are soaked in a special varnish to make them resistant to chemical vapors and moisture. (T or F)
- 87. JTAG-compliant PC boards are becoming more important as digital ICs become _____ (less complex, more complex) and _____ (larger in size, smaller in size).
- 88. Refer to Fig. 12-30. The small yellow squares on IC1 and IC3–IC6 are called ______ (boundary-scan cells, carbonzinc cells).
- 89. On a printed circuit board containing both JTAG and non-JTAG ICs, it may be possible to test non-JTAG ICs for proper operation using boundary scan. (T or F)



Chapter 12 Summary and Review

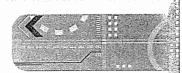

Summary

- 1. An assembly of digital subsystems connected correctly forms a digital system.
- 2. Digital systems have six common elements: input, transmission, storage, processing, control, and output.
- 3. Manufacturers produce ICs that are classified as small-, medium-, large-, very large-, and ultra-large-scale integrations.
- Electronic games are popular construction projects.
 Many are simulations of older games like throwing dice.
- 5. A digital clock and a digital frequency counter are two closely related digital systems. Both make extensive use of counters.
- Many LSI digital clock chips are available. Most clock ICs need other components to produce a working digital clock.
- 7. Multiplexing is a commonly used method of driving seven-segment LED displays.
- 8. All digital systems are basically constructed from AND gates, OR gates, and inverters.
- 9. A frequency counter is an instrument that accurately counts input pulses in a given time interval and

- displays it in digital form. It constantly cycles through a reset-count-display sequence.
- 10. Block diagrams communicate the organization of a digital system. The most detailed block diagrams break the system down to the chip level.
- 11. The IEEE Standard 1149.1 Test Access Port and Boundary-Scan Architecture (commonly known as either JTAG or boundary scan) specifies standards for embedding testing and access points in complex, miniature, high-density ICs and PC boards. Testing can be automated for quality-control testing and field troubleshooting.
- 12. Distance sensors use various technologies, including infrared light, ultrasonic sound, laser, sonar, and radar. Distance sensors are selected by technology, cost, ease of interfacing, and range.
- 13. Outputs from distance sensors are classified as either analog or digital. The sensors with analog outputs are usually linked to a control unit such as a microcontroller for needed calculations and to generate useful outputs.

Chapter Review Questions

Answer the following questions:			Refer to Fig. 12-4. When the push button is
12-1. List the six elements found in most digital systems.			(closed, opened), the display will stop and indicate a random number from 1 to [number], simulating the roll
	What do the following letters stand for when referring to ICs?		of a single die.
	a. IC b. SSI c. MSI d. LSI e. VLSI f. ULSI	1	Refer to Fig. 12-4. This circuit uses(CMOS, TTL) ICs.
		12-7	Refer to Fig. 12-4. If a "1" shows on the
12-3.	The term "chip" usually is taken to (IC, sliver of plas	, ,	seven-segment LED display, then outputs [letters] of the 7447 IC are ac-
12-4.	electronics. A (computer, digitivatch) is usually based upon a single	ital wrist-	tivated with a (HIGH, LOW). 2-8. Refer to Fig. 12-4. When the 74192 IC tries to count upward from 110 to 111, the

Chapter Review Questions...continued

	NAND gate is activated driving the load input	12-22.	What IC(s) are being used as waveshaping cir-
	(HIGH, LOW). This immedi-		cuits in the frequency counter in Fig. 12-18?
	ately loads[binary number]	12-23.	Refer to Fig. 12-18. The unknown frequency
	into the counter's flip-flops.		is allowed to pass through the control gate for
12-9.	Refer to Fig. 12-6. Two trigger		0.1 s when the count/display waveform goes
	NAND gates and associated resistors and		(HIGH, LOW).
	capacitors form the clock section of this digital	12-24.	Refer to Fig. 12-18. The displays are blanked
	dice game.		during the portion of the count
12-10.	Refer to Fig. 12-6. Grounding pin 10 of the 4029		display waveform.
	IC converts this unit to a(n)	12-25.	Refer to Fig. 12-21. List two ICs that form the
	(down, up) counter.		time-base clock section of the LCD timer.
12-11.	Refer to Fig. 12-6. When the counter's outputs	12-26.	Refer to Fig. 12-21. List the IC(s) that detect
	are 110 (HHL), LEDs light.		when the count of the timer reaches 00.
	This is caused by the output of the NAND gate	12-27.	Refer to Fig. 12-21. When the count on the
	going (HIGH, LOW) and tran-		timer reaches 00, the output of the magnitude
	sistor Q_2 being turned (on, off).		comparator goes (HIGH,
12-12.	A bilateral switch is also called a(n)		LOW). This turns on transistor Q_1 , sounding
	gate.		the alarm, and activates the
12-13.	A digital clock makes extensive use of		line.
	(counter, shift register)	12-28.	Refer to Fig. 12-21. When the LCD reads 88,
	subsystems.		the signals on all of the lines from the
12-14.	A known frequency is the main input to a digi-		74HC4543 drivers to the displays are
	tal (clock, frequency counter)		(in phase, 180° out of phase)
	system.		with the signal at the output of the display
12-15.	Counters are used for counting upward and		clock.
	(shifting data, storing data) in	12-29.	Refer to Fig. 12-21. The accuracy of the
	the digital clock system.		entire timer depends on the accuracy of the
12-16.	The National Semiconductor MM5314 clock		clock.
	chip (directly drives, multi-	12-30.	Refer to Fig. 12-19(b). A commercial timer
	plexes) the output displays.		would probably use a(n) con-
12-17.	The multiplex oscillator's frequency in		trolled oscillator (astable MV) for the time-base
	Fig. 12-12(<i>a</i>) is set by		clock to ensure maximum accuracy.
	(connecting an external capacitor and resistor	12-31.	Refer to Fig. 12-21. The 74HC4543 ICs have
	to the correct IC pins; the factory and cannot be		the (decoder, driver, latch)
	changed).		section of the chip disabled in this circuit.
12-18.	Counters are used for counting upward and	12-32.	List five common distance-sensing
	(counting downward, dividing		technologies.
	frequency) in a digital frequency counter.	12-33.	Refer to Fig. 12-24(<i>a</i>). The IR emitter is an
12-19.	The three J-K flip-flops (FF1, FF2, FF3) and		infrared diode, while the IR detector uses a IR
	the NAND gate in Fig. 12-18 function as a		phototransistor. (T or F)
	(down counter, frequency	12-34.	Refer to Fig. 12-24(b). This distance-measuring
	divider).		sensor applied the triangulation method for cal-
12-20.	The 7408 AND gate in Fig. 12-18 serves to		culating the distance to the reflecting target.
	(clear, inhibit) the counters.		(T or F)
12-21.	The frequency counter in Fig. 12-18 counts	12-35.	Refer to Fig. 12-25. List the sequence of events
	from a low of Hz to a high of		after the trigger pulse in the operation of this
	Hz.		ultrasonic distance sensor circuit.

Chapter Review Questions...continued

12-36. Refer to Fig. 12-26. When the digital distance 12-40. In common usage, JTAG is also referred to sensor detects an object in its range, the output as _____ (boundary scan, joule thermal agent) in the field of digital of the sensor goes _____ (HIGH, LOW), causing the output of the inverter to go electronics. _____ (HIGH, LOW), turning on the 12-41. A testing architecture that includes automated transistor and causing the LED to light. testing and test access points for miniaturized 12-37. Refer to Fig. 12-27(b). The negative trigger complex PC boards is covered under IEEE pulse entering the input (pin 2) of the 555 timer _ (Standard 1149.1, Standard IC is generated by the _____ when it 2000), also sometimes called JTAG. is activated. 12-42. Boundary-scan technology is an aftermarket 12-38. Refer to Fig. 12-27(b). The positive enable item that can be added to any complex PC pulse _____ (disables, enables) the board after it has been manufactured. AND control gate, allowing clock pulses to (T or F) enter the MC3479 driver IC, which causes 12-43. A JTAG-compliant IC would have boundaryscan cells embedded in the chip. (T or F) the stepper motor to rotate _____ (CCW, CW). 12-44. JTAG is an acronym for _____ in the 12-39. Refer to Fig. 12-28. Starting with the digital field of boundary-scan technology. distance sensor, list the events needed to turn on

Critical Thinking Questions

12-1. List at least five common pieces of equipment that are considered digital systems.

the dc motor for a few seconds.

- 12-2. List at least four devices you used or studied about that are considered digital subsystems.
- 12-3. Why was the experimental frequency counter shown in Fig. 12-18 included for study when it is not a practical piece of equipment?
- 12-4. What are some differences between the conceptual version of the digital timer in Fig. 12-19 and the working experimental timer in Fig. 12-21?
- 12-5. Why would the digital dice game shown in Fig. 12-6 probably be preferred over the simpler version in Fig. 12-4?
- 12-6. Refer to Fig. 12-6. When the preset pulse line goes _____ (HIGH, LOW), PNP transistor Q_1 turns on and the preset enable input to the 4029 counter is activated with a ____ (HIGH, LOW).

- 12-7. Refer to Fig. 12-6. When the counter's outputs are 100 (HLL), LEDs _______ light. The bilateral switches are closed because of the ______ (HIGH, LOW) on their control inputs. Only transistor ______ (Q_3 , Q_4) is turned on grounding the cathode of LED D_5 .
- 12-8. Refer to Fig. 12-27(*b*). Starting with the digital distance sensor, list the events needed to turn on the stepper motor for only a few seconds.
- 12-9. The BASIC Stamp 2 module by Parallax is commonly used to operate which ultrasonic distance sensor?
- 12-10. Describe how parking sensors might operate on a newer automobile (use an Internet search and/or interview users).
- 12-11. Describe how blind-spot monitoring systems might operate on a newer automobile (use an Internet search and/or interview users).



Answers to Self-Tests

- 1. control
- 2. input
- 3. data or digital data
- 4. storage
- 5. T
- 6. T
- 7. ceramic resonator
- 8. input
- 9. T
- 10. V_{ss} , V_{in} , V_{DO}
- 11. firmware
- 12. serial
- 13. 12 to 99
- 14. 10,000
- 15. 1960s
- 16. microcontroller IC
- 17. microprocessor
- 18. astable (free-running)
- 19. LOW, 0001
- 20. 1, 2, 3, 4, 5, 6
- 21. 4093
- 22. 110, 101, 100, 011, 010, 001
- 23. O.
- 24. D_2 and D_3 , closed, Q_4
- 25. bilateral switch or transmission gate
- 26. F
- 27. turns on, HIGH, 0110
- 28. Q_{5}
- 29. frequency divider, count accumulator
- 30. waveshaping
- 31. waveshaping
- 32. control gate (start/stop control)
- 33. counter
- 34. F
- 35. T
- 36. MOS
- 37. 60
- 38. prescale
- 39. 11 to 19
- 40. multiplexes
- 41. V_{ss}
- 42. has internal
- 43. resistor and capacitor
- 44. 1.0
- 45. LOW

- 46. Schmitt-trigger inverters
- 47. counters
- 48. 0.1
- 49. waveshaping
- 50. storing or
 - accumulating
- 51. divide-by-6
- 52. 0.1, 0.9
- 53. count
- 54. reset, positive
- 55. count, negative
- 56. Schmitt-trigger, wave-
- 57. 10
- 58. 10, 9990
- 59. 0.9
- 60.60
- 61. 74192 counter ICs
- 62. time-base
- 63. BCD
- 64. piezo buzzer, LCD (liquid-crystal display)
- 65. HIGH, HIGH, on
- 66. out-of-phase
- 67. Ph (phase), common (backplane)
- 68. seconds
- 69. F
- 70. phototransistor
- 71. triangulation
- 72. signal processing
- 73. microcontroller
- 74. F
- 75. 4, digital
- 76. LOW, HIGH, lights
- 77. HIGH
- 78. passed through
- 79. LOW
- 80. NO
- 81. JTAG
- 82. test vectors
- 83. nets
- 84. TAP
- 85. Joint Test Action Group
- 86. F
- 87. more complex, smaller in size
- 88. boundary-scan cells
- 89. T



Computer Systems

Learning Outcomes

This chapter will help you to:

- **13-1** Diagram the classic organization of a computer. Trace the flow of data in a block diagram of a computer.
- **13-2** Draw a basic block diagram of a microcomputer. Trace the flow of data. Catagorize peripheral devices as inputs, outputs, or storage.
- **13-3** Analyze an input-store-output program sequence in a simplified microprocessor (featuring only input and output ports, MPU, program memory, and data memory).
- 13-4 Determine the operation of a simple microcomputer address decoding system and characterize the use of three-state buffers with a data bus.
- **13-5** Explain the difference between serial and parallel data transmission. Analyze several simple data transmission examples.
- **13-6** *Understand* the use of parity bits in detecting errors in data transmissions.
- **13-7** Recognize the ports available in several computers. Identify several USB characteristics and uses. Analyze a simplified transmission example.
- **13-8** *Discuss* the use and advantages of PLCs in industrial settings.
- **13-9** Define the use for microcontrollers. Detail primary characteristics and survey several examples of microcontrollers.
- **13-10** Recognize several types of BASIC Stamp microcontroller modules, their characteristics, and the fundamentals of programming. Program a BASIC Stamp 2 module using the PBASIC language.
- **13-11** *Understand* the conceptual features of digital signal processing (DSP).
- 13-12 Describe the use of a DSP in a digital camera.
- **13-13** Solve a mechanical slide mechanism applying a BASIC Stamp 2 microcontroller with photocell input and servo motor output. Analyze the circuit and PBASIC program used to solve the mechanical problem.


desktop or laptop personal computer is probably the first device you think of when you think of a computer system. However, computer systems are found in many other devices that we use every day. Automobile engines have embedded computer chips to make them run more efficiently and to help mechanics diagnose problems. Digital cameras, video cameras, and MP3 players have computer processors in them to compress and decompress video and audio signals. Even your cell phone uses computer chips to send and receive your telephone calls, take pictures, play ringtones, and be a modem for a personal computer. This chapter examines several types of computer systems, some digital subsystems of computer systems, and data transmission.

13-1 The Computer

The most complex digital systems include *computers*. Most digital computers can be divided into the five functional sections shown in Fig. 13-1. The input device may be a keyboard, mouse, joystick, graphics tablet, card reader, magnetic tape unit, scanner, network connection, or telephone line. This equipment lets us pass information from *person to machine* (or machine to machine). The input device often must *encode* human language into the binary language of the computer.

The memory section is the storage area for both data and programs. This storage can be supplemented by storage outside the processing unit.

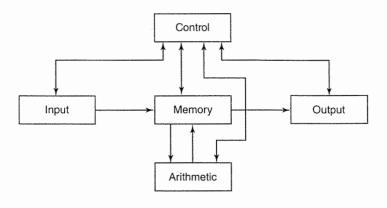The arithmetic unit is what many people think of as being inside a computer. The arithmetic unit adds, subtracts, multiplies, divides, compares, and performs other logic functions. Notice that a two-way path exists between



Central processing unit (CPU) Central processing unit

Fig. 13-1 Sections of a digital computer.

the memory and arithmetic sections. In other words, data can be sent to the arithmetic section for action and the results sent back to storage in the memory. The arithmetic unit is sometimes referred to as the ALU (arithmetic-logic unit).

The control section is the nervous system of the computer. It directs all other sections to operate in the proper order and tells the input when and where to place information in the memory. It directs the memory to route information to the arithmetic section and tells the arithmetic section to add. It routes the answer back to the memory and to the output device. It tells the output device when to operate. This is only a sampling of what the control section can do.

The output section is the link between the machine and a person (or to a device or network). It can communicate to humans through a printer. It can output information on a LED or LCD display. Output information can also be placed on bulk storage devices, such as memory cards, disks, or optical discs. The output section often must decode the language of the computer into human language.

The three middle blocks of Fig. 13-1 are often called the CPU. The arithmetic and memory sections and most of the control section are frequently found on a single circuit board. Devices located outside the CPU are often called *peripheral devices*.

The block diagram of the computer in Fig. 13-1 could well be the diagram for a calculator. Up to this point the basic systems operate the same. The basic difference between the calculator and computer is *size* and the use

of a stored program in a computer. Computers are also faster and are multipurpose machines. Figure 13-2 shows that two types of information are put into a computer. One is the program (instructions) telling the control unit how to proceed in solving the problem. This program, which has to be carefully written by a programmer, is stored in the central memory while the problem is being solved. The second type of information fed to the computer is data, to be acted on by the computer. Data include the facts and figures needed to solve the problem. Notice that the program information is placed in storage in the memory and used only by the control unit. The data information, however, is directed to various positions within the computer and is processed by the ALU. The data need never go to the control unit. The auxiliary memory is extra memory that may be needed to store partial results in some complex problems. It may not be located in the CPU. Data may be stored in peripheral devices such as a hard drive.

In summary, the computer is organized into five basic functional sections: input, memory, control, ALU, and output. Information fed into the CPU is either program instructions or data to be acted upon. The computer's stored program and size make it different from a calculator.

Computers, one of the most complex of digital systems, are not covered in depth in this section. There are entire volumes written about the organization and architecture of computers. Remember, however, that all the circuits in the digital computer are constructed from logic gates, flip-flops, memory cells, and subsystems.

Computer organization

Peripheral devices

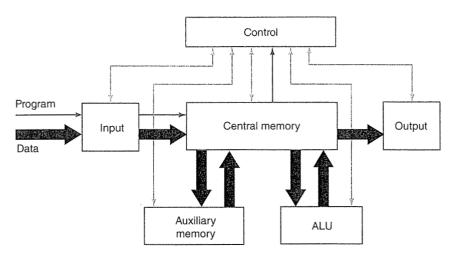


Fig. 13-2 Flow of program instructions and data in a computer system.



Answer the following questions.

- 2. List several of the fundamental differences between a computer and a calculator.
- 3. List the two types of information fed into a digital computer.



Microprocessor (MPU) Stored-program digital computer Microcomputer organization

13-2 The Microcomputer


Computers have been in general use since the 1950s. Formerly, digital computers were large, expensive machines used by governments or large businesses. The size and shape of the digital computer have changed in the past decades as a result of a device called the microprocessor. The *microprocessor* (MPU, for "microprocessing unit") is an IC that contains much of the processing capabilities of a larger computer. The MPU is a small but extremely complex device that is *programmable*. The MPU IC forms the heart of a microcomputer. The *microcomputer* is a *stored-program digital computer*.


The organization of a very tiny microcomputer system is diagrammed in Fig. 13-3. This microcomputer contains all the five basic sections of a computer: the *input* unit, the *control* and *arithmetic* units contained within the MPU, the *memory* units, and the *output* unit.



History of Electronics

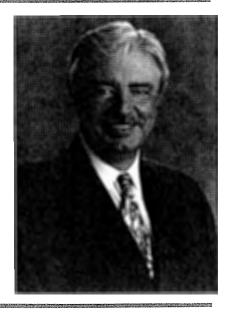Dennis C. Hayes
In 1978, 28-year-old Dennis
C. Hayes formed what became Hayes Microcomputer
Products, Inc. When he began,
Hayes hand-assembled and
soldered products on a borrowed dining room table in
his home. Then, in 1981 the
Hayes Smartmodem, which
was easily integrated into
the computer environment,
started a communications
revolution.



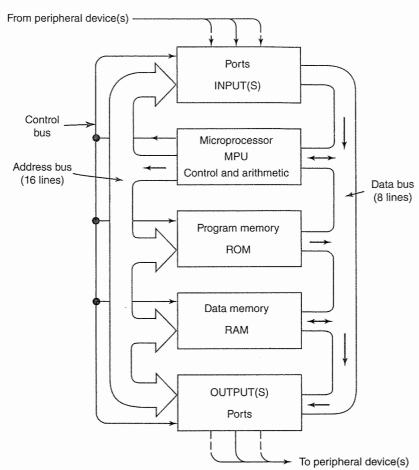



Visit the Intel website to learn about history and developments in microprocessors.

Microcomputer system

MPU

Peripheral devices

Fig. 13-3 Block diagram of a microcomputer system.

The MPU controls all the units of the system using the control lines shown at the left in Fig. 13-3. Besides the control lines, the *address bus* (16 parallel conductors) selects a certain memory location, input port, or output port. The *data bus* (eight parallel conductors) on the right in Fig. 13-3 is a *two-way path* for transferring data into and out of the MPU. It is important to note that the MPU can send data to memory or an output port or receive data from memory or an input port.

The microcomputer's ROM commonly contains a program. A *program* is a list of specially coded instructions that tell the MPU *exactly* what to do. The ROM in Fig. 13-3 is the place where the program resides in this example. In actual practice, the ROM (or perhaps NVSRAM) contains a start-up or initializing program and perhaps other programs. Separate programs can also be loaded into RAM from auxiliary memory. These are user programs.

The RAM area in Fig. 13-3 is identified in this example as the data memory. Data used in the program reside in this memory.

The CPU and memory sections of the micro-computer are not very useful by themselves. The CPU must be interfaced with *peripheral devices* for input, output, and storage. Typical peripheral devices used for input, output, and storage on modern microcomputers are diagrammed in Fig. 13-4. The keyboard, mouse, and joystick are probably the most common input devices connected to most microcomputers. Several other input devices connected to microcomputers are shown at the left in Fig. 13-4.

The optical disc drive is a popular secondary storage device connected to most microcomputers. Other popular secondary storage devices interfaced with microcomputers are hard disk drives and USB flash drives. The monitor, printer, and sound systems are the most common output peripheral devices used with typical microcomputers. Other output devices include TVs, plotters, and laser printers.

Computer connections to networks such as the Internet are almost universal. Individual computer users commonly implement these

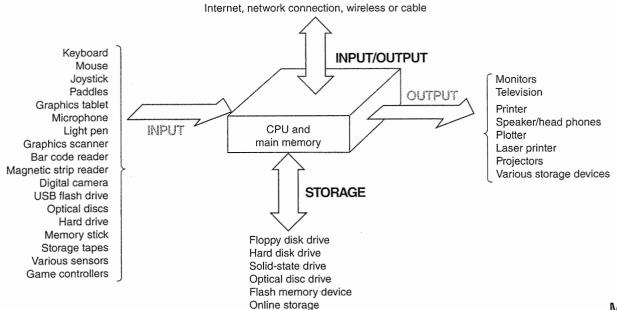


Fig. 13-4 Peripheral devices commonly attached to the CPU of a microcomputer.

network connections using a modem (modulator/demodulator) which communicates with an Internet service provider over regular home telephone or cable TV lines. The modem is classified as an input/output peripheral device in Fig. 13-4. The modem provides two-way communication over the public network called the Internet. The modem serves as an output device when transmitting data and an input device when receiving data. The Internet is a huge network that links millions of computers worldwide. Users of the Internet can find and exchange information, buy and sell products, and play games.

Another method of securing a connection to the Internet is using a *DSL* (digital subscriber line). A DSL connection may be 10 to 100 times faster than a phone connection and is commonly used by some individuals, telecommuters, and small businesses. Cable TV companies can also provide high-speed Internet service in many areas.

Larger organizations commonly use *LANs* (*local area networks*) for two-way communication within a building or campus. LANs use private lines and may use one of several protocols for two-way communication between the

Microcomputer peripheral devices

Modem

DSL

LAN

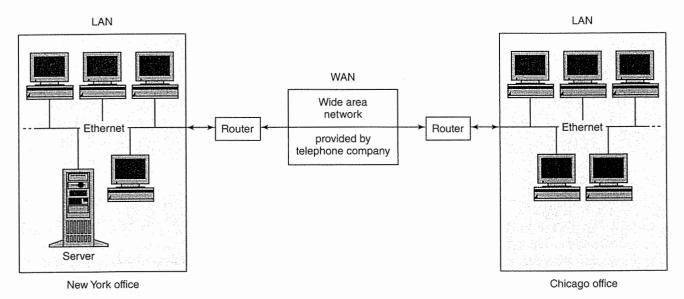


Fig. 13-5 Use of both LANs and WANs for business communication.

desk computers and a server (computer with more processing power and memory). A LAN is shown at the left in Fig. 13-5 showing computers connected to the server using the *Ethernet* protocol. A server might be called on for processing, to retrieve/update a file, or for an application. Larger organizations with remote offices may use a *WAN* (wide area network) to communicate with computers in other cities.

The diagram in Fig. 13-5 shows the WAN supplied by a public telephone company being used for two-way business communication. The *router* (formerly called gateways) shown in Fig. 13-5 is a device that determines the optimal path along which long-range communications traffic should follow to reach its destination. The router may also translate from one transmission protocol to another.

Wan

-M- Self-Test

Supply the missing word in each statement.

- Refer to Fig. 13-3. The address bus is a one-way path, whereas the ______ bus is a two-way pathway for information.
- 5. Refer to Fig. 13-3. The ROM typically holds _____ (data, programs).
- 6. Refer to Fig. 13-3. The exact memory location, or input/output port, is selected by the MPU's output on the ______ bus and _____ bus.
- 7. A ______ (modem, scanner) is an input/output peripheral device that enables the microcomputer to send and receive data over telephone lines.
- 8. Refer to Fig. 13-4. The ______ is probably the most popular peripheral

- output device used with low-cost microcomputers.
- 9. Refer to Fig. 13-4. The _______ is a hand-operated input device used to control the direct movement of the cursor on the monitor's screen.
- 10. An organization's computer network within a single building that might include a server and the Ethernet protocol is referred to as a ______ (LAN, WAN).
- 11. A method of accessing the Internet used by small businesses and individuals that is 10 to 100 times faster than a phone connection might be ______ (DSL, SPL).



13-3 Microcomputer Operation

As an example of microcomputer operation, refer to Fig. 13-6. In this example, the following things are to happen:

- 1. Press the "A" key on the keyboard.
- 2. Store the letter "A" in memory.
- 3. Print the letter "A" on the screen of the monitor.

The input-store-output procedure outlined in Fig. 13-6 is a typical microcomputer system operation. The electronic hardware used in a system like that in Fig. 13-6 is complicated. However, the transfer of data within the system will help explain the use of several different units within the microcomputer.

The more detailed diagram in Fig. 13-7 will aid understanding of the typical microcomputer input-store-output procedure. First, look carefully at the *contents* section of the program memory in Fig. 13-7. Note that instructions have already been loaded into the first six memory locations. From Fig. 13-7, it is determined that the instructions currently listed in the program memory are:

- 1. Input data from input port 1.
- 2. Store data from port 1 in data memory location 200.
- 3. Output data to output port 10.

Note that there are only three instructions in the above program. It appears that there are six instructions in the *program memory* in

Program memory


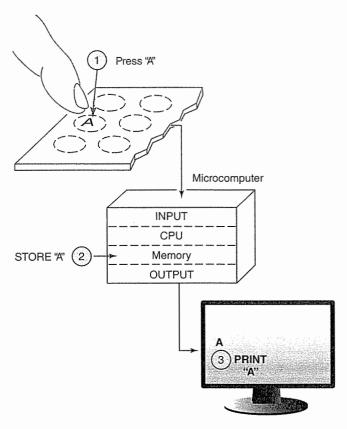


Fig. 13-6 An example of a common input-store-output microcomputer operation.

Fig. 13-7. The reason for this is that instructions are sometimes broken into parts. The first part of instruction 1 above is to input data. The second part tells where the data come from (from port 1). The first, *action* part of the instruction is called the *operation* and

the second part the *operand*. The operation and operand are located in separate memory locations in the program memory in Fig. 13-7. For the first instruction in Fig. 13-7, program memory location 100 holds the input operation while memory location 101 holds the operand

Parts of instruction: operation and operand

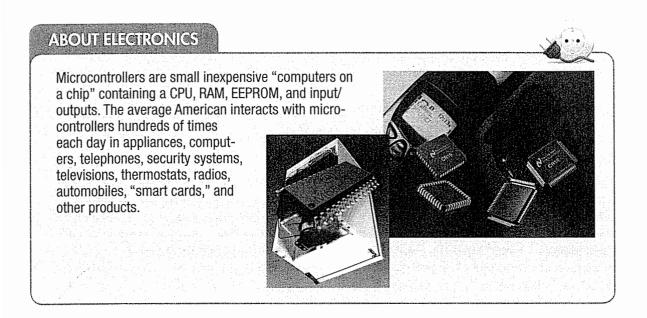

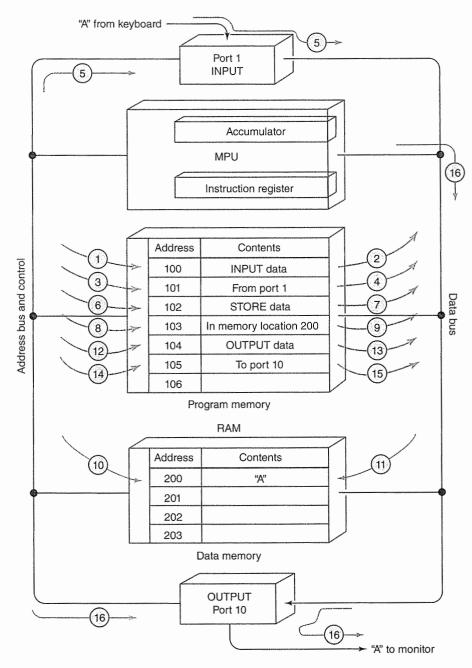


Fig. 13-7 Sequence of microcomputer operations in executing the input-store-output program.

MPU

(port 1) telling where information will be input from.

Two new sections are identified inside the MPU in Fig. 13-7. These two sections are called registers. These special registers are the accumulator and the instruction register.

The sequence of events happening within the microcomputer in the input-store-output "A" example is outlined in Fig. 13-7. The flow of instructions and data can be followed by keying on the circled numbers in the diagram. Remember

that the MPU is the center of all data transfers and operations. Refer to Fig. 13-7 for all steps below.

- 1. The MPU sends out address 100 on the address bus. A control line *enables* the read input on the program memory IC. This step is symbolized in Fig. 13-7 by the encircled number 1.
- 2. The program memory sends the first instruction (input data) on the data bus, and the MPU receives this coded

Accumulator

Instruction register

- message. The instruction is transferred to a special memory location within the MPU called the instruction register. The MPU *decodes*, or interprets, the instruction and determines that it needs the operand to the input data instruction.
- 3. The MPU sends out address 101 on the address bus. The control line enables the read input of the program memory.
- 4. The program memory places the operand (from port 1) on the data bus. The operand was located at address 101 in program memory. This coded message (the address for port 1) is received off the data bus and transferred to the instruction register. The MPU now decodes the entire instruction (input data from port 1).
- 5. The MPU uses the address bus and control lines to the input unit to cause port 1 to open. The coded form for "A" is transferred to and stored in the accumulator of the MPU.

It is important to note that the MPU always follows a *fetch-decode-execute sequence*. It first fetches the instruction from program memory. Second, the MPU decodes the instruction. Third, the MPU executes the instruction. Try to notice this fetch-decode-execute sequence in the next two instructions. Continue with the program listed in the program memory in Fig. 13-7.

- 6. The MPU addresses location 102 on the address bus. The MPU uses the control lines to enable the read input on the program memory.
- 7. The code for the store data instruction is sent on the data bus and received by the MPU, where it is transferred to the instruction register.
- 8. The MPU decodes the store data instruction and determines that it needs the operand. The MPU addresses the next memory location (103) and enables the program memory read input.
- The code for "in memory location 200" is placed on the data bus by the program memory. The MPU accepts this operand and stores it in the instruction register.
 The entire "store data in memory location 200" has been fetched from memory and decoded.

- 10. The execute process now starts. The MPU sends out address 200 on the address bus and enables the *write* input of the data memory.
- 11. The MPU sends the information stored in the accumulator on the data bus to data memory. The "A" is received off the data bus and is written into location 200 in data memory. The second instruction has been executed. This store process does not destroy the contents of the accumulator. The accumulator still also contains the coded form of "A."
- 12. MPU must fetch the next instruction. It addresses location 104 and enables the read input of the program memory.
- 13. The code for the output data instruction is sent to the MPU on the data bus. The MPU receives the instruction and transfers it to the instruction register. The MPU decodes the instruction and determines that it needs an operand.
- 14. The MPU places address 105 on the address bus and enables the read input of the program memory.
- 15. The program memory sends the code for the operand (to port 10) to the MPU via the data bus. The MPU receives this code in the instruction register.
- 16. The MPU decodes the entire instruction "output data to port 10." The MPU activates port 10, using the address bus and control lines to the output unit. The MPU sends the code for "A" (still stored in the accumulator) on the data bus. The "A" is transmitted out of port 10 to the monitor.

Most MPU-based systems transfer information in a fashion similar to the one detailed in Fig. 13-7. The greatest variations are probably in the input and output sections. Several more steps may be required to get the input and output sections to operate properly.

It is important to notice that the MPU is the center of and controls all operations. The MPU follows the fetch-decode-execute sequence. The actual operations of the MPU system, however, are dictated by the instructions listed in program memory. Instructions are usually performed in sequence (100, 101, 102, and so on).

All three instructions in the example would be fetched, decoded, and executed in a few Fetch-decadeexecute sequence

MPU-based systems microseconds or less by most small microcomputers. The advantage of MPU-based systems is their fast operation and flexibility. They are flexible because they can be reprogrammed to perform many tasks.

Microcomputers are complex digital systems containing an MPU IC (or set of ICs), some memory, and inputs and outputs. The

MPU chip itself is a complex, highly integrated subsystem that can process instructions at a high rate of speed. It is expected that microcomputers will be a growth industry for decades to come. The last two sections gave only a brief overview of the basic operation and organization of a microcomputer.

₩.

Self-Test

Supply the missing word or words in each statement.

- 12. The action part of a microcomputer instruction is called the _____. The second part of the instruction is called the _____.
- 13. Refer to Fig. 13-7. Program memory location ______ holds the operation part of the first instruction, whereas location _____ holds the operand part of the instruction.
- 14. Refer to Fig. 13-7. In this microcomputer, the ______ is the center of all data transfers and operations.
- 15. The microcomputer's MPU always follows a fetch-_____sequence when running.
- 16. Program instructions are usually performed in _____ (random, sequential) order in a microcomputer.



Microcomputer address decoding

Three-state buffer

High-impedance state

Address decader

13-4 Microcomputer Address Decoding

Consider the simple 4-bit MPU-based system shown in Fig. 13-8(a). This system uses only eight conductors in the address bus and four conductors in the data bus. The RAMs are tiny, 64-bit (16 \times 4) units. These RAMs are like the 7489 RAMs you studied earlier.

Two problems become apparent when working with a system like the one shown in Fig. 13-8(a). First, how does the MPU select which RAM to read data from when it sends the same 4-bit address to each? Second, how can several devices send data over a common data bus if, generally, outputs of logic devices cannot be tied together? The solutions to both these problems are shown in Fig. 13-8(b).

The address decoder shown in Fig. 13-8(b) decodes which RAM is to be used and sends the enabling signal over the chip select line. Only one chip select line is activated at a time. The

address decoder block consists of familiar combinational logic gates. RAM 0 is selected when the address is 0 through 15. However, RAM 1 is selected when the address is 16 through 31.

The three-state buffers shown in Fig. 13-8(b) disconnect the RAM outputs from the data bus when the memory is not sending data. Only one device is allowed to send on the shared data bus at a given time. For this reason, the chip select line is also used to control, or turn on, the three-state buffers. When the three-state buffers are in the turned off mode, it is said that the buffer outputs are in their high-impedance state and are effectively disconnected from the four data lines at the inputs of the buffers.

The logic circuits used in a simple address decoder are shown in Fig. 13-9. In this example, only when the four address lines $(A_7 \text{ to } A_4)$ are all zero is the output of the bottom four-input OR gate LOW. When address lines A_7 to A_4 are 0000, then RAM 0 is enabled with a LOW at its memory enable (\overline{ME}) input.

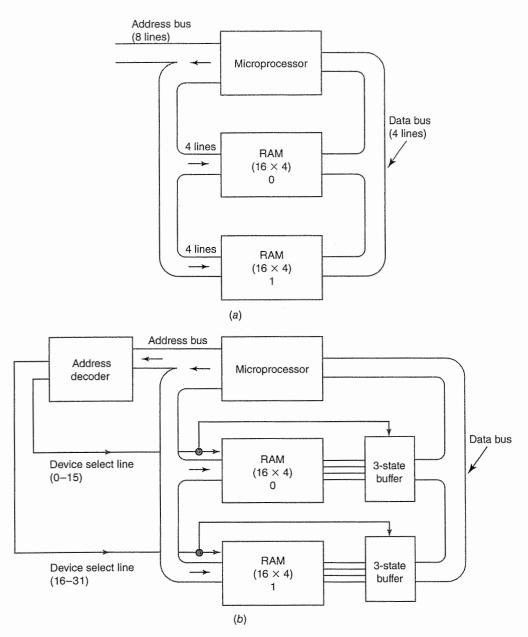


Fig. 13-8 (a) Simplified 4-bit microprocessor interfaced with two 64-bit RAMs.

(b) Address decoder and three-state buffers added to 4-bit microprocessor-based system.


4-bit microprocessorbased system

When the four address lines going into the address decoder in Fig. 13-8 are 0001 ($A_7=0$, $A_6=0$, $A_5=0$, $A_4=1$), the top OR gate is activated. The 0001 causes the top OR gate in the address decoder to generate a LOW output, which activates the bottom device-select line. This enables the bottom RAM (RAM 1).

The address decoder in Fig. 13-9 decodes only the four most significant address lines to generate the correct (\overline{ME}) logic level. The RAMs internally decode the four least significant address lines $(A_0 \text{ to } A_3)$ to locate the exact 4-bit word in RAM.


The MPU-based system in Figs. 13-8 and 13-9 uses eight address lines. This means that the MPU can generate 256 (28) unique addresses. In the systems in Figs. 13-8 and 13-9, the first 16 addresses are used by RAM 0 while the next 16 addresses are used by RAM 1. It is customary to draw a *memory map* of an MPU-based system. The memory map of our sample system is drawn in Fig. 13-10. This shows that the first 16 (0F in hexadecimal) addresses are used by RAM 0. These addresses range from 0 to 15 (00 to 0F in hexadecimal). The second 16 addresses are used by RAM 1. These

Memory map

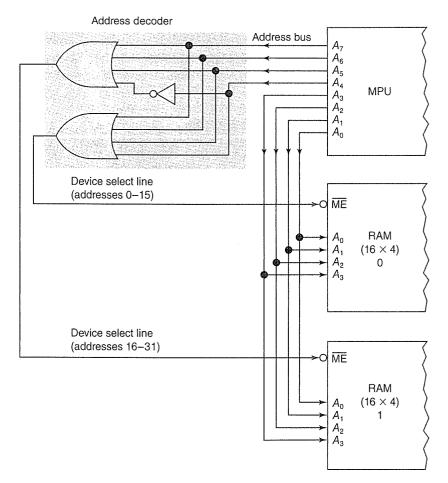

Address decoder

Fig. 13-9 Address decoder gating to generate correct device select signals.

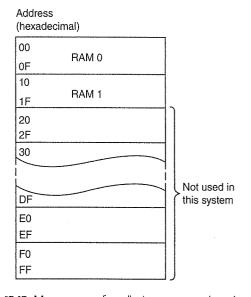

74125 three-state buffer TTL IC

Fig. 13-10 Memory map of small microprocessor-based system using two 16 imes 4 RAMs.

addresses range from 16 to 31 (10 to 1F in hexadecimal). The third through sixteenth groups of addresses are not used in this very tiny system. It is customary to use hexadecimal

notation in specifying addresses in an MPU-based system.

In Fig. 13-8(b), two blocks are labeled three-state buffers. The symbol for a buffer is drawn in Fig. 13-11(a). It has a data input (A) and non-inverted output (Y). When the control input (C) is deactivated with a 1, output Y goes to its high-impedance (high-Z) state and is effectively disconnected from the input.

A commercial version of the three-state buffer is shown in Fig. 13-11(*b*). This is the pin diagram for the *74125 quad three-state buffer TTL IC*. The truth table for the *74125 IC* is shown in Fig. 13-11(*c*).

In summary, an address decoder is used to select *which* device will be connected to the data bus in an MPU-based system. *Address decoders* are usually constructed of combinational logic circuits (simple gating circuits).

To permit many devices to use a common data bus, three-state buffers are used. A three-state buffer has a control input that, when disabled, places the output in the high-impedance (high-Z) state. Both address decoders and three-state buffers are widely used in microcomputers and most other digital products. The three-state buffers are usually part of MPUs, larger RAMs, ROMs, and peripheral interface adapter ICs.





Self-Test

Supply the missing word or words in each statement.

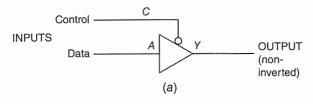- 17. Refer to Fig. 13-8. The ______ in this system selects which RAM will be used.
- 18. Refer to Fig. 13-8. When not in use, RAMs are isolated from the data bus by
- 19. Refer to Fig. 13-9. If the MPU outputs 00001000 on the address bus, RAM
- _____ [number] will be activated and storage area _____ [decimal number] located in the RAM will be accessed.
- 20. Refer to Fig. 13-11. If the control input on the three-state buffer is HIGH, output *Y* is ______ (connected to input *A*; in its high-impedance state).





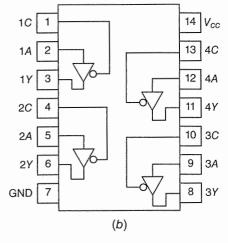

TRUTH TABLE

INP	UTS	OUTPUT
С	Α	Y
L	L	L
L	Н	Н
Н	X	· (Z)

L = LOW voltage level H = HIGH voltage level

X = Don't care

(Z) = High impedance (off)

(c)

Fig. 13-11 (a) Logic symbol for a three-state buffer (b) Pin diagram for commercial 74125 quad three-state buffer IC. (c) Truth table for 74125 three-state buffer IC.

13-5 Data Transmission

Most data in digital systems are transmitted directly through wires and PC boards. Many times bits of data must be transmitted from one place to another. Sometimes the data must be transmitted over telephone lines or cables to points far away. If all the bits in each word were sent at one time over *parallel* wires, the cost and size of these cables would be too expensive and large. Instead, the data are sent over a single wire in *serial* form and reassembled into parallel data at the receiving end. Devices used for sending and receiving serial data are called *multiplexers* (MUXs) and demultiplexers (DEMUXs).

The basic idea of a MUX and DEMUX is shown in Fig. 13-12. Parallel data from one digital device are changed into *serial* data by the MUX. The serial data are transmitted by a single wire. The serial data are reassembled into parallel data at the output by the DEMUX. Notice the control lines that must also connect the MUX and DEMUX. These control lines keep the MUX and DEMUX synchronized. Notice that the 16 input lines are cut down to only a few transmission lines.

The system in Fig. 13-12 works in the following manner. The MUX first connects input 0 to the serial data transmission line. The bit is then transmitted to the DEMUX, which places this bit of data at output 0. The MUX and DEMUX

Data transmission

Serial data

Multiplexer [MUX]
Demultiplexer
[DEMUX]

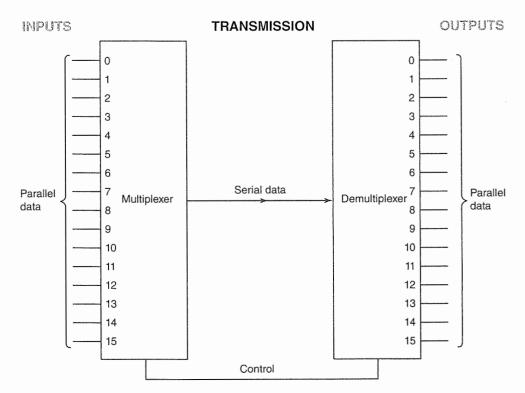


Fig. 13-12 Serial data transmission using a multiplexer and demultiplexer.

proceed to transfer the data at input 1 to output 1, and so on. The bits are transmitted one bit at a time.

A MUX works much like a single-pole, many-position rotary switch, as shown in Fig. 13-13. Rotary switch 1 shows the action of a MUX. The DEMUX operates like rotary switch 2 in Fig. 13-13. The mechanical control in this diagram makes sure input 5 on SW 1 is delivered to output 5 on SW 2. Notice that the mechanical switches in Fig. 13-13 permit data to travel in either direction. Being made from logic gates, MUXs and DEMUXs permit data to travel only from input to output, as in Fig. 13-12.

You may have used a MUX before. The other name for MUX is *data selector*. DEMUXs are sometimes called *distributors* or *decoders*. The term "distributor" describes the action of SW 2 in Fig. 13-13, as it distributes the serial data first to output 1, then to output 2, then to output 3, and so forth.

Figure 13-14 is a detailed wiring diagram of a simple experimental transmission system using the MUX/DEMUX arrangement. A word (16 bits long) is entered at the inputs (0 to 15) of the 74150 MUX IC. The 7493 counter starts at binary 0000. This would be shown as 0 on the seven-segment display. With the data select

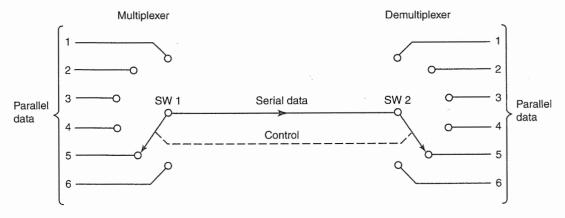


Fig. 13-13 Rotary switches act like multiplexers and demultiplexers.

74150 MUX IC

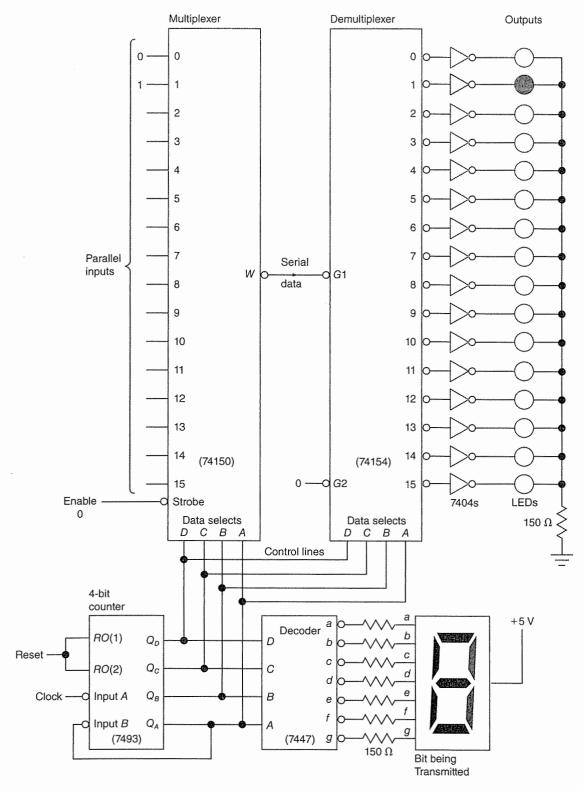


Fig. 13-14 Wiring diagram for an experimental transmission system.

inputs (D, C, B, A) of the 74150 MUX at 0000, the data are taken from input 0, which is shown as a logical 0. The logical 0 is transferred to the 74154 DEMUX IC, where it is routed to output 0. Normally the output of the 74154 IC is inverted, as shown by the invert bubbles. A

7404 inverter complements the output back to the original logical 0.

The counter increases to binary 0001. This is shown as a 1 on the decimal readout. This binary 0001 is applied to the data select inputs of both ICs (74150 and 74154). The logical 1 at

74154 DEMUX IC

Handshaking

Buffer memory

PPI (programmable peripheral interface)

UART (universal asynchronous receivertransmitter)

Data links

Parallel interface

Peripheral interface adapter [PIA] the input of the 74150 MUX is transferred to the transmission line. The 74154 DEMUX routes the data to output 1. The 7404 inverter complements the output, and the logical 1 appears as a lighted LED, as shown in the diagram. The counter continues to scan each input of the 74150 IC and transfer the contents to the output of the 74154. Notice that the counter must count from binary 0000 to 1111 (16 counts) to transfer just one parallel word from the input to the output of this system. The seven-segment LED readout provides a convenient way of keeping track of which input is being transmitted. If the clock is pulsed very fast, the parallel data can be transmitted quite quickly as serial data to the output.

Notice from Fig. 13-14 that we have saved many pieces of wire by sending the data in *serial* form. This takes somewhat more time, but the rate at which we send data over the transmission line can be very high.

One common example of data transmission is the link between a microcomputer and a peripheral device such as a printer or modem. The computer's interface may send data either in parallel or serial format depending on the design of the printer.

A parallel interface transmits 8 bits (1 byte) of data at one time. Figure 13-15 shows how the microcomputer's CPU controls a special IC called a peripheral interface adapter (PIA). The PIA IC communicates with the printer through

the handshaking line to check if it is ready to receive data. If the printer signals the PIA that it is ready, bytes are transmitted from the CPU to the PIA and then on to the printer's buffer memory. The CPU can send data much faster than the printer can print the information. For this reason, the printer signals the PIA when its buffer memory is full. The PIA then signals the CPU to stop sending data temporarily until there is more room for data in the printer's buffer memory.

Peripheral interface adapters are not standardized. For instance, Motorola calls its unit a 6820 PIA, while Intel's name for a similar input/output adapter unit is the 8255 *PPI (programmable peripheral interface)*. The PIAs are general-purpose ICs that can be programmed for either input or output. They have several parallel 8-bit I/O ports.

A serial interface transmits data 1 bit at a time. ICs called *UARTs* (universal asynchronous receiver-transmitters) may be used as the interface between the CPU and the data lines (also called data links). A UART consists of three sections as shown in Fig. 13-16. They are a receiver, a transmitter, and a control block. The receiver converts serial to parallel data. The transmitter section converts parallel data (as from the data bus of the CPU) to serial data. The control section manages the UART's functions and handles communications with the CPU and the peripheral device. The UART also encodes and decodes the serial signal including start, stop, and parity bits.

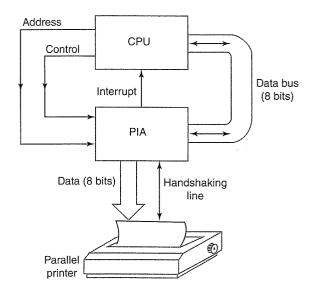


Fig. 13-15 Parallel data transmission from the CPU to printer using a peripheral interface adapter (PIA) IC.

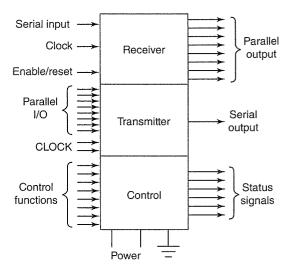


Fig. 13-16 Block diagram of a typical UART.

The speed at which serial data are transmitted is called the baud rate. The *baud rate* is the number of bits per second being transmitted through a data link. The baud rate is *not* the same as the number of characters or words transmitted per second. Common baud rates might be 2400, 9600, 19,200, and 38,400.

The signal levels found in data lines are many times defined by standards. Two serial

interface standards are the EIA RS-232C standard and the older 20-mA current loop teletype standard.

Two common *parallel interfaces* are the Centronics standard and the IEEE-488 standard. The Centronics standard is used between many microcomputers and printers. The IEEE-488 interface is used between computers and scientific instrumentation.

Baud rate

Parallel interface

Serial interface standards



Self-Test

Answer the following questions.

- 21. Refer to Fig. 13-12. A(n) _____ changes parallel data to serial data, whereas a(n) _____ changes serial data to parallel data for transmission.
- 22. Refer to Fig. 13-14. The 7493 IC is used to sequence the data selects from 0000 through ______ (binary number).
- 23. Refer to Fig. 13-15. A complex chip called a(n) ______ is used to output

- parallel data to the printer in some microcomputer systems.
- 24. An LSI IC used for asynchronous data transmission is called a(n) ______.
- 25. A measure of the speed of serial data transmission is called the _____ rate
- 26. The EIA RS-232C standard might be used for _____ (parallel, serial) interfacing between a microcomputer and a peripheral device.



13-6 Detecting Errors in Data Transmissions

Digital equipment, such as a computer, is valuable to people because it is fast and *accurate*. To help make digital devices accurate, special *error detection* methods are used. You can well imagine an error creeping into a system when data are transferred from place to place.

To detect errors, we must keep a constant check on the data being transmitted. To check accuracy, we can generate and transmit an extra parity bit. Figure 13-17 shows such a system. In this system three parallel bits (A, B, and C) are being transmitted over a long distance. Near the input they are fed into a parity bit generator circuit. This circuit generates what is called a parity bit. The parity bit is transmitted with

Parity bit

Error detection

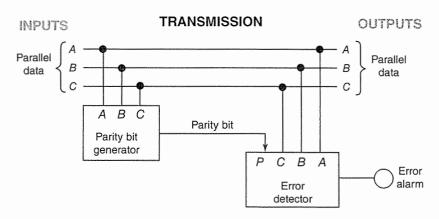


Fig. 13-17 Error detection system using a parity bit.

XOR gate used for parity bit generation and error detection

Table 13-1 Truth Table for Parity Bit Generator

	Inputs		Output
	Parallel data		Parity bit
С	В	Α	Р
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0,5,5	1:	0
1	1	0	0
1	1	1	1

the data, and near the output the results are checked. If an error occurs during transmission, the *error detector* circuit sounds an alarm. If all the parallel data are the same at the output as it was at the input, no alarm sounds.

Table 13-1 will help you understand how the error detection system works. This table is really a truth table for the parity bit generator in Fig. 13-17. Notice that the inputs are labeled A, B, and C for the three data transmission lines. The output is determined by looking across a horizontal row. We want an even number of 1s in each row (zero 1s, or two 1s, or four 1s). Notice that row 1 has no 1s. Row 2 has a single 1 plus the parity bit 1. Row 2 has two 1s. As you look down Table 13-1, you will notice that each horizontal row contains an even number of 1s. Next, the truth table is converted to a logic circuit. The logic circuit for the parity bit generator is drawn in Fig. 13-18(a). You

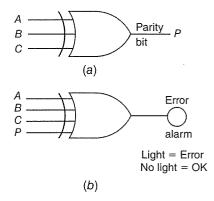


Fig. 13-18 (a) Parity bit generator circuit. (b) Error detector circuit.

can see that a three-input XOR gate will do the job for generating a parity bit. The three-input XOR gate in Fig. 13-18, then, is the logic circuit you would substitute for the parity bit generator block in Fig. 13-17.

Look at the entire truth table in Table 13-1. We can see that under normal circumstances each horizontal row contains an *even number* of 1s. Were an error to occur, we might then have an *odd number* of 1s appear. A circuit that gives a logical 1 output any time an odd number of 1s appear is shown in Fig. 13-18(b). A four-input XOR gate would detect an odd number of 1s at the inputs and turn on the alarm light. Figure 13-18(b) diagrams the logic circuit that can substitute for the error detector block in Fig. 13-17.

The parity bit can be generated for longer words such as a 7-bit ASCII character. For instance, the ASCII code for T is 1010100 (from Table 6-3). If transmitted using an even parity bit, an extra 1 would have to be added (to get an even number of 1s or four 1s). Another example, the ASCII code for S is 1010011 (from Table 6-3). If transmitted using an even parity bit, an extra 0 would have to be added (four 1s already). A seven-input XOR gate would generate the correct even parity bit for 7-bit ASCII characters. An 8-bit XOR gate at the receiver end would serve as an error detector circuit (H = error, L =no error). Either an even or odd parity bit may be transmitted or received. An XNOR gate is used to generate an odd parity bit.

The parity bit system is a simple way to detect an error in a data transmission. However, the parity bit system can only detect errors if an odd number of bits changes. If an even number of bits changes during the data transmission, the parity bit system will not detect the error.

For example, if the ASCII code 1010100 for the letter T changed during transmission to 1010111 (letter W), this error would *not be detected* by the parity bit system. Notice that both 1010100 (ASCII for T) and 1010111 (ASCII for W) have an odd number of 1s. The parity bit system would generate no error message in this example.

One common system used to check for multiple bit errors during transmission is the *cyclic redundancy check*, or *CRC*. The CRC system adds several extra bits to the end of the transmitted data. The extra bits enable the system to

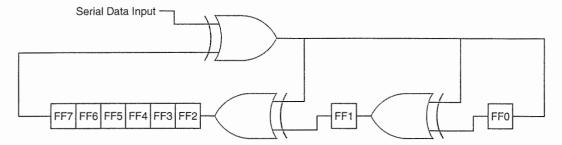


Fig. 13-19 A CRC-8 checksum generator circuit.

detect almost all transmission errors. Systems that use the CRC to detect errors may add 8, 16, or 32 bits to the data. These are commonly referred to as CRC-8, CRC-16, or CRC-32 systems.

The cyclic redundancy check creates a unique code, or *checksum*, for the data by shifting the data through a special shift register circuit made up of flip-flops with XOR gates inserted at specific locations. The example in Fig. 13-19 shows a circuit for generating one possible CRC-8 checksum. After all the data have been shifted into the serial data input of the circuit, the shift register (FF0–FF7) holds the 8-bit checksum for the data.

In a CRC error detection system, both the transmitter and the receiver implement the same circuit. The transmitter uses the circuit to generate the checksum. At the receiver, the received data are passed through the checksum circuit. After all the data have been received, the checksum at the receiver is compared to the checksum sent by the transmitter. If the checksums match, the data were successfully transmitted. If the checksums do not match, the receiver requests the transmitter to resend the data.

The use of parity bits or CRCs in a system only warns if there was an error during transmission. These systems do not automatically correct errors. Some systems such as the *Hamming code* both detect and correct errors in transmission. Codes such as the Hamming code are known as *error-correcting codes*. Other methods of ensuring accuracy in data transmissions have also been developed.

Checksum

-\h- | Self-Test

Supply the missing word or words in each statement.

- 27. Refer to Table 13-1. This is the truth table for an _____ (even, odd) parity bit generator.
- 28. Refer to Fig. 13-17. The parity bit generator block could be replaced with a three-input ______ gate, whereas the error detector block could be replaced with a four-input _____ gate.
- 29. Using even parity, what bit would be transmitted with the 7-bit ASCII code 1011000 as a parity bit?
- 30. Using odd parity, what bit would be transmitted with the 7-bit ASCII code 1011000 as a parity bit?
- 31. A seven-input ______ (AND, XOR) gate will generate an even parity bit for a 7-bit ASCII code.
- 32. When dealing with error detection in data transmissions, the acronym CRC stands for



13-7 Data Transmission in a Computer System

For a computer system to operate, data must be transmitted between the computer and the peripheral devices connected to the computer. If you look at the back of a desktop computer, you will find many different types of connectors for connecting devices to the computer. These connectors are often called *ports*. Some of the most common ports are:

Keyboard Port

A dedicated port specifically for connecting a keyboard. Many PCs use the mini-DIN PS/2 connector (6 pins).

More compact computers commonly use USB (universal serial bus) ports. Some keyboard information is sent in wireless form. The wireless transfer to data may be via RF (radio frequency) or IR (infrared) means. Wireless transmission can pose more of a security risk in business, military, and government offices.

Mouse Port

A dedicated port specifically for connecting a mouse. Many PCs use the mini-DIN connector. Some use the USB connector.

Video Port

The port used for connecting the computer to a display monitor, often an LED or LCD display. This may be an older 15-pin VGA (video graphics adapter) port or a new DVI (digital visual interface) port.

The DVI is a common video standard that can transmit either analog or digital signals using the same connector. The DVI connector can have up to 29 pins and has a unique shape. The DVI connector can be configured to send an analog signal (VGA) to older cathode-ray tube (CRT) monitors (DVI-A). The DVI connector can also be configured to send digital signals to newer LED or LCD monitors (DVI-D).

Expect to see the newer *DisplayPort* digital display interface. The 20-pin connector has a unique shape and can transmit digital video, audio, USB, and other forms of data.

Serial Port

This port has a 9-pin D-shaped connector. It is one of the oldest ports on a computer and is used for connecting many types of devices.

The serial port is not available on most newer PCs.

Parallel Port

This port has a 25-pin DB (data bus) connector. It is also one of the oldest ports on a computer. It was often used to connect printers to the computer. It sends data 8 bits at a time.

Audio Ports

A computer may have two or more of these ports. These are commonly 3.5-mm audio connectors. At least one port is typically used for audio output to headphones or speakers. Another port is often used to connect a microphone for audio input.

USB Port

The universal serial bus (USB) port is found on most modern computers. It has become the standard port for interfacing with a variety of peripheral devices. The USB port has replaced older serial and parallel ports on many computers. The USB port is adaptable enough, with the appropriate software drivers, to interface with the following:

Printers: Inkjet printer, laser printer, and CNC machine

Images: Camera, camcorder, webcam, and scanner

Human interface: Mouse, keyboard, tablet, game controllers, and joystick

Audio: Microphone, speaker, and sound card Bulk storage: USB hard disk drive, USB optical drive, USB flash drive, and memory cards (such as an SD card)

Communications: Modem and other data communications

At this time, the USB 2.0 receptacle is the most common port available on modern computers. The smaller 2.0 mini- or 2.0 micro-USB cables are unique and used on tiny computers such as notebooks and tablets. The 2.0 mini- or 2.0 micro-USB cables are also used on calculators, phones, cameras, and readers. A much faster USB 3.0 is starting to appear on computers. The cables for USB 3.0 are much different.

The standard type A and B plugs are sketched in Fig. 13-20. The type A plug is used to connect "upstream" to the USB ports (called *receptacles*) on the host computer. Type B plugs

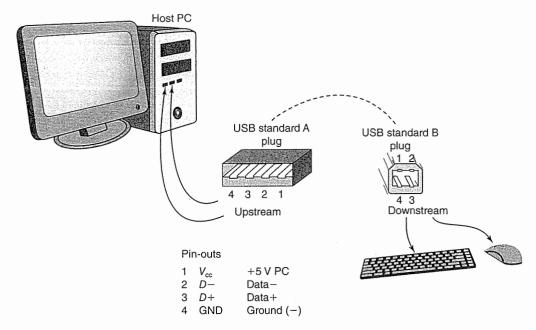


Fig. 13-20 USB 2.0 cables. Standard A plug and standard B plug.

are used to connect "downsteam" to the USB ports (called *receptacles*) on the peripheral devices (mouse and keyboard). Notice the difference in shape of the A and B plugs.

Pin-out information for the standard A and B plugs is detailed in Fig. 13-20. Notice that the USB cables carry power (+5 V and -GND) to the device connected to the computer. Voltage from the USB cable can power some devices. USB cables can even be used to charge batteries on some handheld devices. USB 2.0 ports can provide power up to 500 mA, at 5 V dc.

USB transmission rates are generally classified as:

- USB 1.0 low-speed rate of 1.5 megabits/s.
 Could be used with keyboards and mice.
- USB 1.1 full-speed rate of 12 megabits/s (about 1.4 MB/s). Its basic rate is defined by USB 1.0.
- USB 2.0 high-speed rate of 480 megabits/s (about 57 MB/s). High-speed devices are capable of full-speed operation (USB 1.1). The high-speed transmission rate is currently widely used. Remember these are maximum speeds. Half-duplex differential signaling is used with a LOW being 0 to 0.3 V and HIGH being 2.8 to 3.6 V.

 USB 3.0 superspeed rate of 5 gigabits/s (about 596 MB/s). Transmission rates are higher because of full-duplex operation.

USB transmission was designed with low cost and ease of use in mind. Other transmission technologies such as *FireWire* are for higher performance, especially when dealing with audio and video.

Ethernet Port

This port is used to connect computers to networks at high speed. Many PCs use a RJ-45 jack to connect to a network. The RJ-45 looks something like the RJ-11 jack used to connect modems to home telephone lines.

Transmission Example

A look at how data are moved between the computer and peripheral devices through a simplified serial port will help you to understand data transmission through a computer system. Section 13-5 introduced the UART as an IC commonly used as a serial interface to the CPU. In personal computers, the UART is the IC used to control the serial port. UARTs are *full-duplex* devices because they can send and receive data at the same time.

Fig. 13-21 is a block diagram of a UART used in a simple computer system for both the input and output ports. Data coming into



Discover more on PC ports at www .howstuffworks.com.

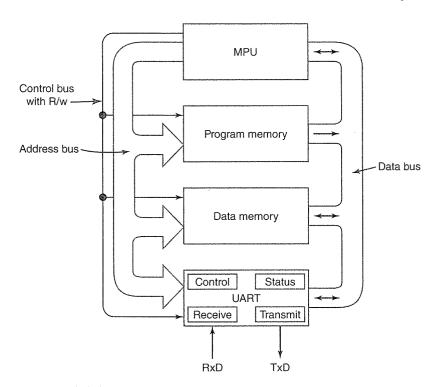


Fig. 13-21 Block diagram of a UART in a computer system.

the UART are the input data to the computer system. Data sent out of the UART are the output data. Notice that the UART in this sketch shows four registers within it. They are the transmit data register, the receive data register, the control register, and the status register. By reading and writing values to these registers, the MPU is able to control data flowing in and out of the UART. The UART makes it easier for the MPU to send and receive data to peripheral devices because it allows the MPU to treat reading and writing data to peripheral devices almost the same as reading and writing data to RAM memory. In microcomputer systems, registers in chips used to control data flowing in and out of ports are mapped into a memory space, the same as the RAM memory is mapped in Fig. 13-10. Although the UART in Fig. 13-21 shows four registers, it is common for the transmit data register and receive data register to share the same memory location. Thus, the memory map for the UART in this figure requires only three memory locations. The MPU signals the UART which data register it wants to use via the R/W control line. If the MPU signals a WRITE operation on the data register memory location of the UART, then data are sent to the transmit data register. If a READ operation is signaled to the same


Table 13-2	10-10-0
Register	Offset
Receive data	00h
Transmit data	00h
Status	01h
Control	02h

memory location, then data are read from the receive data register.

Table 13-2 details where the registers of the UART of Fig. 13-21 exist relative to a base memory location. As an example, let's say the designer of the computer system of Fig. 13-21 placed the UART at a base memory location of 300. In this configuration, the MPU accesses the status register by reading from memory location 301 and accesses the control register by reading or writing to memory location 302. Figure 13-22 provides more details about the control and status registers. Each of these two registers is subdivided into a number of bits, and each bit has special meaning. The special meanings assigned to each bit of these registers are also shown in Fig. 13-22.

Now let's walk through an example of the computer system of Fig. 13-21, setting up the UART and sending the ASCII code for the letter

Control Register

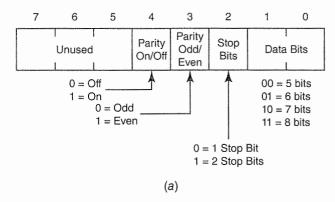

Status Register

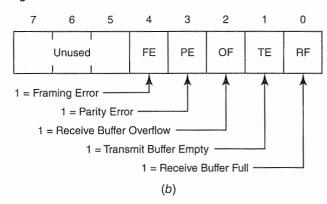


Fig. 13-22 (a) UART control register details. (b) UART status register details.

"A" (1100001 binary) to a peripheral attached to the serial port. The data are to be sent using even parity and one stop bit. Following the same fetch-decode-execute sequence described in Sec. 13-3, the MPU runs a program that instructs the MPU to do the following:

Load the value 00011010 binary (1A in hex) into the MPU's accumulator from program memory.

Place the memory address of 302 on the address bus.

Place the value in the accumulator on the data bus.

Place the WRITE signal on the R/W control line.

A look at the bits of the value (00011010) just sent to the control register of the UART by the instructions above shows that the UART is now configured to transmit and receive data using seven data bits with even parity and one stop bit. Bit 1 of the control register is 1 and bit 0 is 0. From Fig. 13-22(a), we see that this combination of bits instructs the UART to transmit and

receive seven bits of data at a time. Bit 2 of the control registers is set to 0 for one stop bit. Bit 4 is 1, which instructs the UART to use parity encoding, and bit 3 is set to 1 for even parity. Continuing on, the program being run instructs the MPU to:

Load 01100001 binary (the ASCII code for the letter "A") into the accumulator from program memory.

Place the memory address of 300 on the address bus.

Place the value of the accumulator on the data bus.

Place the WRITE signal on the R/W control line.

The UART now has enough information to begin transmitting the character "A" without any further action from the MPU. However, the instructions from the program that the MPU is running still instructs the MPU to read the status register (memory location 301) occasionally to check to see that the data were sent. The program performs this check by looking at bit 1 of

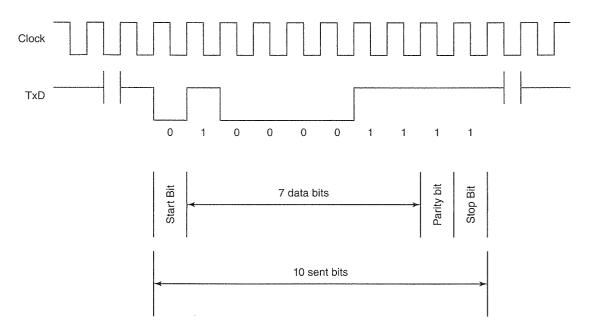


Fig. 13-23 Serial data sent out on TxD of the UART.

the status register. If bit 1 of the status register is 1, the transmit data buffer is empty, indicating that the data were sent.

Figure 13-23 shows the serial data sent out on the TxD (transmit data) line of the UART. Notice that 10 bits were transmitted. The UART did the work of adding the start bit, parity bit, and stop bit and transmitting the data without any further instruction from the MPU. Also notice that the seven bits representing the letter "A" are reversed. Data sent out from the UART are sent least significant bit first. The UART also receives data with the least significant bit first.

When the UART receives data, it automatically strips off the start, stop, and parity bits. The UART also checks the parity of the data received. If the parity does not match the expected parity, the error is indicated, or *flagged*, in the parity error bit of the status register. In fact, four of the five *flags* in the status register are for use when receiving data. In addition to the parity error (PE) flag, there are the receive-bufferfull (RF) flag, the overflow (OF) flag, and the

framing-error (FE) flag. When the UART has received a byte of data, it sets the receive-bufferfull flag to 1, indicating that it has data ready to be read by the MPU. If the UART receives another byte of data before the MPU has read the previously received byte, then it sets the overflow flag to 1, indicating that data were lost. A framing error occurs when the UART doesn't receive the expected number of bits for its current configuration. In our example, this might happen if the peripheral device were configured to send two stop bits instead of one. In this case, the UART would receive 11 bits instead of the expected 10 bits and would notify the MPU of the error by setting the framing-error flag.

The UART in this example was intentionally kept simple to show you how data flow through the computer system to peripherals. UARTs used in personal computers typically have additional registers that allow for greater control over things such as the baud rate. However, the steps used to set up and control those UARTs are the same as what was presented here.



Answer the following questions.

- 33. Connectors on computers that are used to connect to external devices are often called ______.
- 34. The USB port on personal computers replaced the older parallel port and is used *only* to drive printers. (T or F)

- 35. The USB ports on modern personal computers were designed with low cost and ease of use in mind. (T or F)
- 36. The newer and faster USB 3.0 ports on some computers require the exact same plugs and cables used by USB 2.0 ports. (T or F)
- 37. _____ are ICs that are used to control data flowing into and out of the serial port of a personal computer.
- 38. UARTs are _____ (half, full)-duplex devices.
- 39. Registers in ICs that are used for interfacing external devices to a computer are special, so they are not mapped into the computer's memory space. (T or F)
- 40. The MPU must do the work of adding the start, stop, and parity bits to the data before sending them to the UART for transmission. (T or F)
- 41. A ______ (port, flag) is another name of a bit used to indicate status or an error condition.



13-8 Programmable Logic Controllers (PLCs)

A programmable logic controller (PLC) is a specialized computerlike device used to replace banks of electromagnetic relays in industrial process control. The PLC is also known as a programmable controller (PC). The title "PC" for programmable controller could be confused in common usage with "PC" used to mean personal computer. To avoid this confusion, we shall refer to the programmable controller as a programmable logic controller, or PLC.

You can think of the programmable logic controller as a heavy-duty computer system designed for machine control. Like a generalpurpose computer, the PLC is based on digital logic and can be field-programmed. The programming language is a bit different because the purpose of the PLC is to control machines. The PLC is used to time and sequence functions that might be required in assembly lines, robots, and chemical processing. It is designed to deal with the harsh conditions of the industrial environment; some of the physical environment problems could include vibration and shock, dirt and vapors, and temperature extremes. The PLC commonly has to interface with a wide variety of both input and output devices. Some input devices include limit and pressure switches, temperature and optical sensors, and analog-to-digital converters (ADCs). Output devices include relays, motors, solenoids, pneumatic valves, hydraulic valves, digital-to-analog

converters, and indicators (both visual and aural).

A simple block diagram of a programmable logic controller is sketched in Fig. 13-24. As a system, it looks much like classic computer architecture. What makes the PLC different from a general-purpose computer, however, is the type of inputs and outputs connected to the system. A PC system commonly has a keyboard or mouse for primary input, while the PLC must interface with sensors, which detect the machine's action. The primary output from a PC is a monitor or printer, whereas the PLC must drive motors and solenoids. Notice from Fig. 13-24 that the programmer is shown as a separate module, which may or may not be connected to the processing unit. The programming device in Fig. 13-24 can be connected when an update is needed in the PLC and disconnected when the task is finished. Semiconductor memory devices within the processing unit of the PLC hold the machine or process control program. In small PLCs, the input and output modules can be part of the device. In larger systems, the processing module, input module, output module, and power supplies are housed in separate heavy-duty, industrial-style enclosures. The programmer can be a dedicated terminal, general-purpose computer, or handheld programming device.

The processing unit of the PLC typically contains a CPU (a microprocessor) and semi-conductor memory devices such as RAM and EEPROM or EPROM. The CPU communicates with memory and input/output (I/O) modules

Programmable logic controller (PLC)

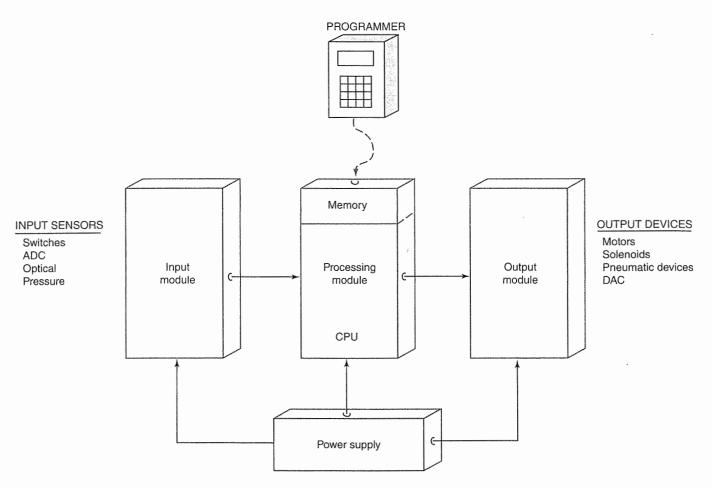


Fig. 13-24 Organization of a programmable logic controller (PLC).

Relay ladder diagram

Ladder logic diagram via the typical address, control, and data buses. The input sensors and output devices are hard-wired to the input and output modules. The architecture of the PLC and a PC look very much alike. Many PLCs have a simple machine-control language built permanently into their memory. The PLC programming language is simpler than the languages used to program general-purpose computers. Programmable logic controllers can be reprogrammed by the electricians and technicians that maintain the other industrial electrical-electronic devices in a factory or plant. The instruction set for a specific PLC may contain as few as 15 to as many as 100 instructions. Besides the normal arithmetic and logic functions associated with computer CPUs, specialized instructions are needed to sense and control output devices and to do the following tasks:

Examine an input bit for ON condition. Examine an input bit for OFF condition. Turn on and latch an output. Turn off and latch an output.

Turn on for a certain time, then turn off.

Programmable logic controllers are closely associated with relay logic or hardwired logic used prior to their introduction in the 1970s. A relay ladder diagram is a graphic method of describing how a circuit works. A ladder logic diagram is a graphic programming language developed from the relay ladder diagram and is useful in programming a PLC. Some examples of equivalent relay ladder diagrams, relay logic diagrams, and logic gate diagrams are illustrated in the following examples. These examples are from the excellent textbook, Programmable Logic Controllers, 4th edition by Frank Petruzella, McGraw-Hill. Notice that each of the three types of diagrams has its own symbols and conventions. Each of the types of diagrams was developed by various manufacturers and users to suit their needs. For instance, the relay schematics were developed before digital logic as we know it became popular. The Two limit switches (LS) connected in series are used to control a solenoid (SOL) (from Frank Petruzella, Programmable Logic Controllers, 4th ed., New York: McGraw-Hill, 2011).


ladder logic diagrams were developed directly from the relay schematics used earlier.

Example 13-1 shows two input switches in series, and the output device is a solenoid valve. The relay schematic is shown at the top, the ladder logic diagram in the center, and the familiar logic gate diagram near the bottom. We recognize that two switches in series is an AND situation as shown at the bottom with a Boolean expression of AB = Y. Note the symbols used in the relay schematic, ladder logic diagram, and gate logic are different but each represents the same task—the AND function.

Example 13-2 shows two input switches in parallel, and the output device is a solenoid valve. The relay schematic is shown at the top, the ladder logic diagram in the center, and the logic gate diagram near the bottom. We recognize that two switches in parallel is an OR situation as shown near the bottom with a Boolean expression of A + B = Y.

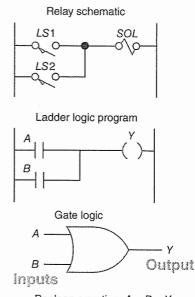Example 13-3 shows two input switches in parallel with a normally open relay contact in series with both, and the output device is a green pilot light. The relay schematic is shown at the top, the ladder logic diagram in the center, and the logic gate diagram near the bottom. We recognize that two switches


Two limit switches (LS) connected in parallel are used to control a solenoid (SOL) (from Frank Petruzella, Programmable Logic Controllers, 4th ed., New York: McGraw-Hill, 2011).



Boolean equation: A + B = Y

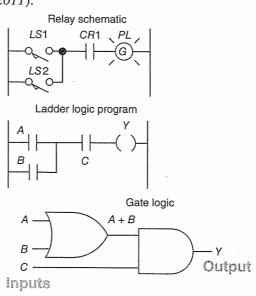EXAMPLE 13-3

Two limit switches (LS) connected in parallel are placed in series with a relay contact (CR) are used to control pilot lamp (PL) (from Frank Petruzella, Programmable Logic Controllers, 4th ed., New York: McGraw-Hill, 2011).




Boolean equation: (A + B)C = Y


Example 13-4 shows two input switches (A and B) in series with each other, and both are in parallel with a single switch (C). The output device in this example is a warning horn. The relay schematic is shown at the top, the ladder logic diagram in the center, and the familiar logic gate diagram near the bottom. We recognize that two switches (A and B) are in series, which is an AND situation, while switch C is parallel with the two switches. Again, remember that the relay schematic, ladder logic diagram, and gate logic diagrams all represent the same logic function as described by the Boolean expression (AB) + C = Y.


In summary, a programmable logic controller (PLC) is a heavy-duty computer system used to replace older relay logic. PLCs are used in factories and plants to control machines, material handling, and chemical processing. PLCs are built to withstand the more harsh environment of a factory, warehouse, or processing plant. The language used to program a PLC has specialized instructions for evaluating inputs and generating outputs. Some PLC languages are based directly on relay ladder diagrams. Because the processing unit (CPU) of the PLC is a microprocessor, it can also perform arithmetic and logic functions as well as data handling and branch and subroutine calls typical of general-purpose computer languages. Some manufacturers of PLCs are Allen-Bradley

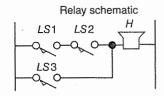EXAMPLE 13-4

Two limit switches (LS) connected in series with each other and in parallel with a third limit switch are used to control a warning horn (H) (from Frank Petruzella, Programmable Logic Controllers, 4th ed., New York: McGraw-Hill, 2011).



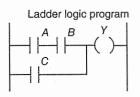

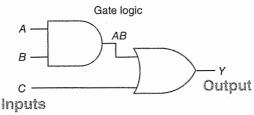

Boolean equation: (AB) + C = Y

Company, Cincinnati Milcron Company, Eaton Corporation (Cutler-Hammer products), Gould Inc., Honeywell, Inc., Square D Company, Texas Instruments, and Westinghouse Electric Company.

-1/1-

Self-Test

Answer the following questions.

- 42. The programmable controller (PC) is also commonly known as the ______ or PLC.
- 43. A programmable logic controller (PLC) is a heavy-duty computer system designed for ______ (general-purpose office use, machine control in factories).
- 44. Once programmed, inputs to a PLC would probably come from devices such as _____ (keyboard and mouse; limit

- switches, pressure switches, temperature and optical sensors).
- 45. Typically a PLC has a programming module connected to it _____ (always, occasionally during reprogramming).
- 46. Refer to Fig. 13-24. The power supply, processing, input, and output sections are referred to as modules because they are sometimes physically housed in separate enclosures in larger systems. (T or F)
- 47. The programming language used with PLCs is commonly _____ (less,

- more) complex than general-purpose computer languages.
- 48. Given the relay schematic in Fig. 13-25, draw the ladder logic program that might be used with a PLC for this circuit.
- 49. Given the relay schematic in Fig. 13-25, draw a logic gate equivalent of this circuit using AND and OR symbols.
- 50. Given the relay schematic in Fig. 13-25, write the Boolean expression that describes the logic function of this circuit.

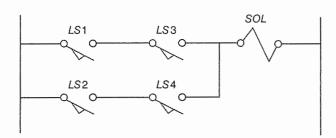


Fig. 13-25 Relay schematic diagram.



13-9 Microcontrollers

A microcontroller is considered to be a "computer on a chip." A single-package microcontroller contains a central processing unit (CPU), semiconductor memory (RAM for data memory and read-only memory for program memory), a clock generator, and input/output capabilities. The read-only memory used to store programs in a microcontroller can take the form of ROM, EPROM, EEPROM, or even flash EEPROM. Microcontrollers are low-cost, programmable, electronic devices that can be embedded in inexpensive appliances. Microcontrollers are popular in consumer products because of their extremely low cost: A simple microcontroller IC may cost only a few dollars. The features of microcontrollers vary widely; some are faster, some contain more memory, some have more input/output ports, and some have other characteristics that may be necessary for a specific application. The term "microcomputer" or "small computer" might be used to describe the microcontroller but is not common usage. The term "microcontroller" fits the jobs these small "computers on a chip" perform, which are control functions. Microcontrollers are not used as general-purpose computers.

Microcontrollers were developed shortly after their larger relatives, microprocessors. The same companies that developed microprocessor chips (for instance Intel and Motorola) also developed a line of microcontrollers. The first 8-bit microcontrollers appeared in the late 1970s, and some of these are still in use today. Microcontrollers sell in huge volumes (many billions per year). Microcontrollers are embedded in many everyday consumer products, such as cars, toys, TVs, VCRs, microwave ovens, and PC keyboards. For instance, a modern automobile may contain 10 to 30 microcontrollers, whereas a high-tech home may contain more than that.

Many younger students may get firsthand experience with microcontrollers through technology classes and robotics competitions. You have probably already used the BASIC Stamp microcontroller modules introduced earlier in this textbook.

Microcontrollers Compared to Microprocessors

When compared to a microprocessor-based system, a microcontroller has less semiconductor memory (RAM, ROM, EPROM, and/ or EEPROM), is lower in cost, and uses less printed circuit board space. Microcontrollers commonly address only a limited size memory. Microcontrollers usually have fewer commands in their instruction set than microprocessors. Microcontrollers typically are programmed to do several limited tasks efficiently and are

Microcontroller

usually not reprogrammed. Microcontroller programs are commonly held in read-only memory. Microcontroller-based systems rarely have complex input/output devices attached, such as keyboards, disk drives, printers, and monitors. Manufacturers support both their microcontroller and microprocessor product with software development tools and application notes (examples of typical applications).

Manufacturers of microcontrollers produce a wide variety of low-cost programmable devices. Some microcontrollers integrate features such as analog-to-digital converters and programmable interval timers. Others include dedicated pulse-width modulation blocks or serial ports of various types.

Microcontrollers are very inexpensive onepackage solutions to complex control and logic problems. Common devices you interact with that seem to have some intelligence probably contain at least one microcontroller.

SOIC package SSOP package

A Family of Microcontrollers

The chart in Fig. 13-26 illustrates a "family of microcontrollers" from Microchip Technology, Inc. This family of devices is described by the manufacturer as the EPROM/ROM-based 8-bit

CMOS microcontroller series. The PIC16C5X device is listed on the left side of the chart with columns showing some of the important characteristics of these low-cost microcontrollers. The operating frequencies of these units allow them to execute instructions very quickly. The program memory size is given in words (word size equals 12 bits for the 16C5X series) and is stored in either ROM or EPROM. The data memory or RAM size is very small, ranging from 24 to 73 bytes. Because microcontrollers are control devices, they typically have many IC pins dedicated to either input or output (I/O pins). The number of I/O pins for the PIC16C5X microcontrollers range from 12 to 20. These I/O pins can be programmed to be either inputs or outputs.

The PIC16C5X series of microcontroller ICs are CMOS devices and operate on low voltages. All of the ICs are available in a variety of packages including the traditional DIP (dual in-line package), SOIC (small-outline IC), and SSOP (shrink small-outline package). The SOIC and SSOP packages are small surface-mount packages. Remember that microcontrollers are embedded CPUs in everyday devices and the small package ICs are ideal for "hiding" them inside of products.

				C	Clock	Mem	ory	Periphera	ls Features
	ntol nto	the free the state of the state	on action	Production by State of State o	The rord of the ro	nodule (s)	Pin ^{ts} Voltage	Etange Moltes	er of Instructions Pastages
PIC16C52	4	384		25	TMR0	12	2.5-6.25	33	18-pin DIP, SOIC
PIC16C54	20	512	_	25	TMR0	12	2.5–6.25	33	18-pin DIP, SOIC; 20-pin SSOP
PIC16C54A	20	512		25	TMR0	12	2.0-6.25	33	18-pin DIP, SOIC; 20-pin SSOP
PIC16CR54A	20	_	512	25	TMR0	12	2.0-6.25	33	18-pin DIP, SOIC; 20-pin SSOP
PIC16C55	20	512		24	TMR0	20	2.5-6.25	33	28-pin DIP, SOIC; SSOP
PIC16C56	20	1K	_	25	TMR0	12	2.5-6.25	33	18-pin DIP, SOIC; 20-pin SSOP
PIC16C57	20	2K	_	72	TMR0	20	2.5-6.25	33	28-pin DIP, SOIC; SSOP
PIC16CR57B	20		2K	72	TMR0	20	2.5-6.25	33	28-pin DIP, SOIC; SSOP
PIC16C58A	20	2K		73	TMR0	12	2.0-6.25	33	18-pin DIP, SOIC; 20-pin SSOP
PIC16CR58A	20	_	2K	73	TMR0	12	2.5-6.25	33	18-pin DIP, SOIC; 20-pin SSOP

All PIC 16/17 Family devices have Power-On Reset, selectable Watchdog Timer, selectable code protect and high I/O current capability.

Fig. 13-25 General specifications for the PIC16CSX family of microcontrollers. (Caurtesy of Microchip Technology, Inc.)

The PIC16C5X series of microcontrollers features RISC architecture using only 33 instructions in their instruction set. RISC means reduced instruction set computing as opposed to CISC (complex instruction set computing). RISC CPUs have fewer instructions but execute them faster. CISC CPUs have more instructions in their instruction set with some of these instructions executing complex tasks. The RISC architecture was developed to speed up the processors, but for complex operations many instructions are needed.

The PIC16C55 Microcontroller

As an example, the 28-pin DIP diagram for the PIC16C55 microcontroller is reproduced in Fig. 13-27(a). A description of the IC's pins is detailed in the chart in Fig. 13-27(b). Note especially from the pin diagram and pin-out descriptions the great number of I/O pins. They are organized into three ports (A, B, and C). Port A (4-bit port) consists of I/O pins RA0-RA3, while ports B and C are each 8-pin ports. Individual I/O pins can be programmed to be either an input or output.

RISC

CISC

-M- Self-Test

Answer the following questions.

- 51. A ______ (microcontroller, microprocessor) can be described as a "computer on a chip" because it contains a CPU, RAM, read-only memory, clock, and I/O pins within a single IC.
- 52. The microcontroller is most likely to appear in a _____ (CPU section of a PC, VCR).
- 53. The microcontroller is noted for its small size and extremely low cost. (T or F)
- 54. All microcontrollers from different manufacturers are alike in size, speed, packaging, instruction set, and function. (T or F)
- 55. Microcontrollers can address _____ (very large, very small) amounts of RAM as compared to microprocessors.

- 56. A ______ (microcontroller, microprocessor) is the device that is considered the CPU of a personal computer.
- 57. The PIC16C55 IC is a ______ (mi-crocontroller, PLC) featuring an EPROM program memory that holds ______ words and a RAM data memory that will hold ______ bytes.
- 58. The PIC16C55 IC would probably cost _____ (less than 5, more than 50) dollars if purchased in small quantities.
- 59. The PIC16C55 IC features a RISC architecture using _____ (33, 72) instructions in its instruction set.
- 60. The programs held in read-only memory in the 16C55 microcontroller are called ______ (firmware, hardware).

13-10 The BASIC Stamp Microcontroller Modules


One of the most popular microcontrollers used in technical training is the BASIC Stamp by Parallax, Inc. The popularity of the BASIC Stamp modules is due to their ease of programming especially for beginners. BASIC Stamp modules are small (about the size of a postage stamp) and fairly inexpensive. Parallax also encourages the educational use of the BASIC Stamp modules with free downloads of both PBASIC editor software and

educational materials from its website (www .parallax.com).

Two versions of BASIC Stamp modules are sketched in Fig. 13-28. The modules are the BASIC Stamp 1 and BASIC Stamp 2. Programming of either of the BASIC Stamp modules is accomplished employing a modern PC using the correct *PBASIC* (Parallax BASIC) editor program. When the student has finished typing the PBASIC program on the PC, it is then downloaded via the proper output port of the PC to the BASIC Stamp module. The *PBASIC interpreter* software translates from

BASIC Stamp

PBASIC interpreter

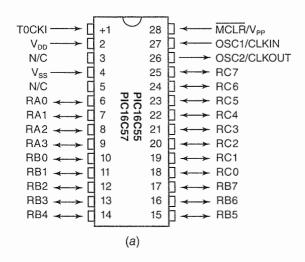

PIC16C55/C57 PIN-OUT DESCRIPTION

	DIP, SOIC	SSOP	I/O/P	Input	
Name	No.	No.	Туре	Levels	Description
RA0 RA1 RA2 RA3	6 7 8 9	5 6 7 8	I/O I/O I/O	TTL TTL TTL TTL	Bidirectional I/O port
RB0 RB1 RB2 RB3 RB4 RB5 RB6 RB7	10 11 12 13 14 15 16	9 10 11 12 13 15 16	1/O 1/O 1/O 1/O 1/O 1/O 1/O	TTL	Bidirectional I/O port
RC0 RC1 RC2 RC3 RC4 RC5 RC6 RC7	18 19 20 21 22 23 24 25	18 19 20 21 22 23 24 25	I/O I/O I/O I/O I/O I/O I/O	TTL	Bidirectional I/O port
TOCKI	1	2	1	ST	Clock input to Timer0. Must be tied to V_{SS} or V_{DD} , if not in use, to reduce current consumption.
MCLR/V _{PP}	28	28	I	ST	Master clear (reset) input/programming voltage input. This pin is an active low reset to the device. Voltage on \overline{MCLR}/V_{PP} must not exceed V_{DD} to avoid unintended entering of programming mode.
OSC1/CLKIN	27	27	ı	ST	Oscillator crystal input/external clock source input.
OSC2/CLKOUT	26	26	0		Oscillator crystal output. Connects to crystal or resonator in crystal oscillator mode. In RC mode, OSC2 pin outputs CLKOUT which has 1/4 the frequency of OSC1, and denotes the instruction cycle rate.
V _{DD}	2	3,4	Р		Positive supply for logic and I/O pins.
V _{SS}	4	1,14	Р		Ground reference for logic and I/O pins.
N/C	3,5	_	_		Unused, do not connect

Legend: I = input, O = output, I/O = input/output,
P = power, — = Not Used, TTL = TTL input,
ST = Schmitt trigger input

(b)

Fig. 13-27 PIC16CSS microcontroller IC. (a) Pin diagram (DIP or SDIC packages only). (b) Pin-out description. (Courtesy of Microchip Technology, Inc.)

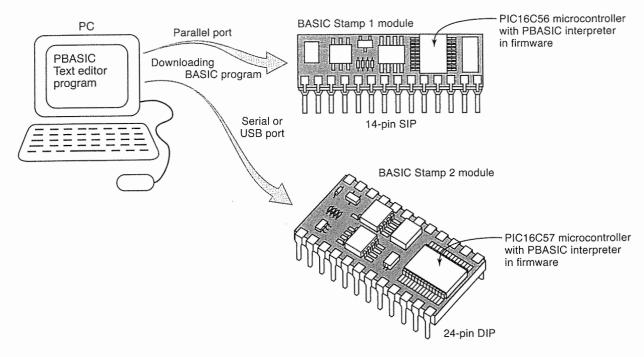


Fig. 13-28 Downloading PBASIC programs to BS1 or BS2 modules.

the downloaded code to machine code to operate the microcontroller. The cable from the PC can then be disconnected, and the program remains in memory on the BASIC Stamp module. The downloaded program then resides in EEPROM where it is executed starting from the beginning of the program each time the power is turned on to the BASIC Stamp module. The downloaded program is held in EE-PROM even if the power to the BASIC Stamp module is turned off. An old program in EE-PROM will be written over if a new program is downloaded from the PC. After programming the BASIC Stamp module, the microcontroller unit would operate independently. Notice that the simple BASIC Stamp 1 uses the parallel port (printer port) of the PC. The larger BASIC Stamp 2 receives downloading from the serial or USB port of the PC.

The BASIC Stamp 1 module (BS1) shown in Fig. 13-28 is a small printed circuit board packaged as a 14-pin SIP (single in-line-package) IC measuring about 0.4 in. wide by 1.4 in. long. The BS1 module is powered by a 9-V battery. An onboard dc voltage regulator drops the voltage to 5 V dc for use by the microcontroller and memory ICs. The main IC on the BS1 module is a custom PIC16C56 microcontroller chip with the PBASIC 1 interpreter in firmware. Because the PIC16C56's memory is used by the PBASIC interpreter, a separate 256-byte program memory is provided. The program memory, implemented using an EEPROM, can hold about 75 instructions. The BASIC Stamp 1 module has eight input/output (I/O) pins. The I/O pins used to control your device are digital in nature. Several special inputs/outputs include those for pulses, sound, PWM (pulsewidth modulation) output, and potentiometer input. Besides the microcontroller, 256-byte EEPROM, and voltage-regulator ICs, the BS1 module also houses a ceramic resonator and a special reset IC.

The BASIC Stamp 2 module (BS2) shown in Fig. 13-28 is a small printed curcuit board packaged as a 24-pin DIP IC. The BS2 module is powered by a 9-V battery. An onboard dc voltage regulator drops the voltage to 5 V dc for use by the microcontroller and memory ICs. The main IC on the BS2 module is a custom PIC16C57 microcontroller chip with the PBASIC 2 interpreter in firmware. Because the PIC16C57's memory is used by the PBA-SIC interpreter, a separate 2048-byte program memory is provided. The program memory, implemented using an EEPROM, can hold about 500 instructions. The BASIC Stamp 2 module has 16 input/output pins. The I/O pins used to



Internet

BASIC Stamp information and downloads are available at www .parallax.com.

control your device are digital in nature. Special inputs/outputs include those for pulses, PWM (pulse-width modulation) output, potentiometer input, X-10 appliance control, touch-tone output, sound, and frequency measurement. Besides the microcontroller, 2048-byte EEPROM, and voltage-regulator ICs, the BS2 module also houses a ceramic resonator and a special reset IC along with some transistor buffers.

DB9 connector

The current-drive capabilities of the BASIC Stamp modules are good ranging from 20 mA to 30 mA. This is enough to drive digital logic or even devices such as LEDs, piezo buzzers, or servo motors. Higher-current devices such as relays or incandescent lamps can be controlled with the use of a driver IC or transistor.

Many beginning students start working with the BASIC Stamp 2 module because it comes in an easy-to-use 24-pin DIP form, can be programmed from MS Windows from a PC, uses an inexpensive serial or USB cable to connect to the module, and its EEPROM can hold approximately 500 instructions. As a practical matter, Parallax produces a useful starter kit called its "Board of Education (BOE)," which is a development board with a DB9 connector for programming and serial communication, a socket for the BS2 IC, 9-V battery snaps, onboard voltage regulator, and breadboarding area. A drawing of the BOE is shown in Fig. 13-29, with several key sections identified. The BOE can be powered with either a standard

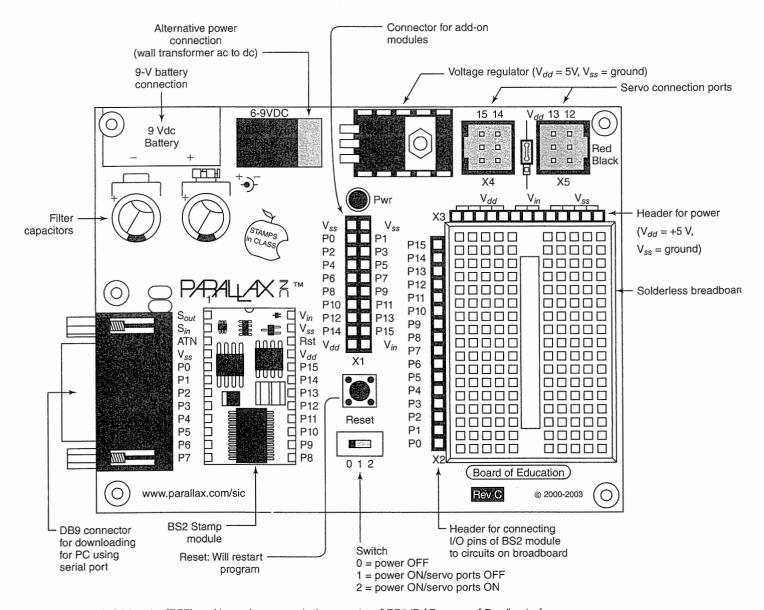


Fig. 13-29 Board of Education (BOE) used by students to study the operation of BS2 IC. (Courtesy of Parallax, Inc.)

9-V dc battery using the snaps at the upper left or an ac-to-dc wall transformer. The solder-less breadboarding area is used by students to wire their projects. I/O port connections from the BS2 IC are available just left of the solderless breadboard for easy connection using 22-gauge solid wire. Power connections ($V_{dd} = +5 \text{ V}$ dc, and $V_{ss} = \text{ground}$) are available above the solderless breadboard in Fig. 13-29. Serial downloading of PBASIC programs from your PC gain access to the BOE through the DB9 connector at the lower left.

The voltage regulator near to the top of the BOE in Fig. 13-29 shifts the input voltage level to +5 V (labeled $V_{\it dd}$) and negative ground (labeled V.). The connectors 12, 13, 14, and 15 are hobby servo connectors. The three-position slide switch near the bottom turns power off (position 0), power on with servo ports OFF (position 1), or power on with servo ports ON (position 2). The reset button will restart the program that is held in the program memory of the BS2 IC module. A top view of the BS2 IC is shown at the lower left on the BOE development board. The DB9 connector at the lower left in Fig. 13-29 is used from downloading from a PC via the serial or USB port. The header X2 is for connecting the I/O ports of the BS2 IC to circuits on the solderless breadboard using 22-gauge wire. The XI header is a connector for add-on modules that are available from Parallax, Inc.

A less expensive version of the BOE is called the BASIC Stamp HomeWork board by Parallax. The HomeWork board features the BS2 module, accepts power from only a 9-V battery, and has fewer features.

Simple BASIC Stamp Programming

Consider using the BOE development board to flash an LED on and off. The wiring of an LED in series with a 220- Ω resistor on the breadboard section of the BOE is sketched in Fig. 13-30. Notice that port 7 (P7) of the BS2 IC will be used to power the LED circuit. The procedure for programming, downloading, and running the program would be as follows:

- 1. Wire the LED circuit with the power off.
- 2. Start the MS Windows *PBASIC editor* on your PC.

- 3. Type the program shown in Fig. 13-31.
- 4. Power on the BOE.
- 5. Download the PBASIC program using the serial port or USB port of the PC.
- Disconnect the download cable.
- 7. Turn BOE power off and then on.
- 8. The program will start at the beginning which will (1) make port 7 of the BS2 an output, (2) turn the LED on, (3) pause 1 second (1000 ms), (4) turn the LED off, (5) pause 1 second (1000 ms), and go to the beginning of the loop titled blink: The LED will blink continuously until the power is turned off.

The simple PBASIC blink program from Fig. 13-31 (and duplicated within Fig. 13-30) is explained below. Notice the use of *remark* statements. In PBASIC, remark statements start with an apostrophe ('). These remark statements are not executed by the BS2 module but appear in the PBASIC editor listing to help humans understand the program.

The first line of the program starts with an apostrophe marking it is a remark statement. In this case 'Blinking LED 1 is the name of the program. Line 2 of the program is output 7 which causes I/O port 7 to be configured as an output. This is clarified in the remark section of line 2. Line 3 (blink:) of the program is the name of the upcoming loop. The colon (:) after a word (such a blink: in this program) is interpreted by the microcontroller to be a label. The label (blink: in this example) is a reference point in the programming that can be referred to by other PBASIC commands. Line 4 (out7 = 0) causes the BS2 module to drive output P7 LOW which turns on the student wired LED shown in Fig. 13-30. Line 5 (pause 1000) causes the BS2 module to do nothing for about 1 second (1000 ms). This means the LED is ON for about 1 second. Line 6 (out7 = 1) causes the BS2 module to drive output P7 HIGH, which turns off the LED. Line 7 (pause 1000) causes another 1-s delay, which means the LED is OFF during this time. Line 8 (goto blink) causes the program jump back to beginning of the loop labeled blink: and repeat the sequence. Remark statements are not required in PBASIC programs but are customary for titles and explaining program operation. Remark statements are very useful for beginners.

PBASIC editor

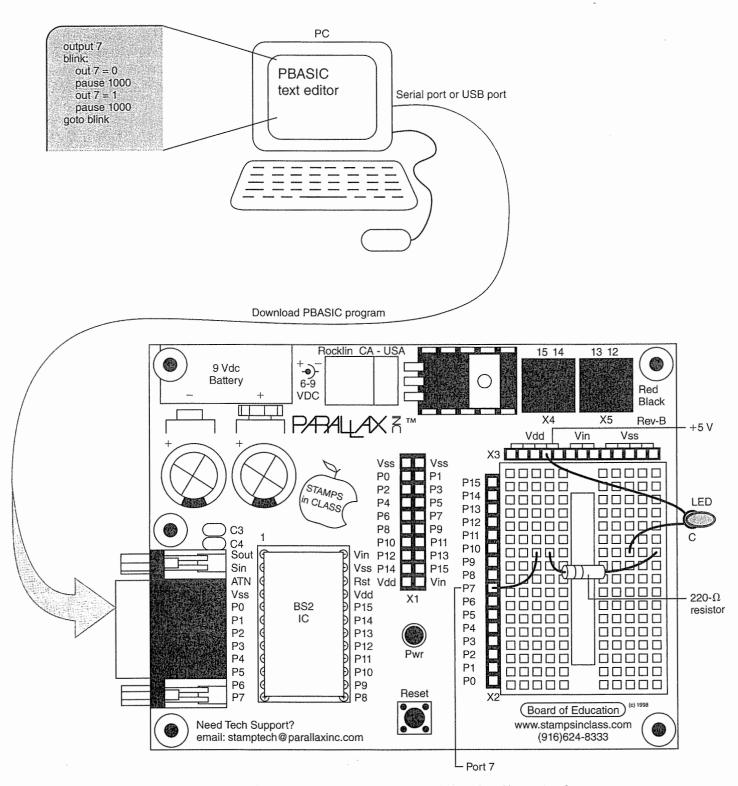


Fig. 13-30. Downloading a PBASIC program to cause the BS2 IC to blink the LEO circuit. Note the use of an older version of BOE.

An LED and $220-\Omega$ resistor were wired between the P7 I/O pin of the BS2 module and the positive rail (V_{dd}) of the power supply in Fig. 13-30. A simplified schematic diagram of this arrangement is shown in Fig. 13-32(a). The LED shown in Fig. 13-32(a) will be used as an output device in the next program.

A push-button switch is being used as an input device (sensor) to I/O pin P3 of the BS2 module in Fig. 13-32(b). You will notice that the push button is wired as an active LOW switch. When the switch is open, I/O port P3 is HIGH, and when the switch is closed, input P3 goes LOW.

'Blinking LED 1

blink: out7 = 0 pause 1000

output7

pause 1000 goto blink

out7 = 1

Fig. 13-31 Listing of the blinking LED 1 program.

'Title of PBASIC program (See Fig. 13.31.)

'Configure I/O port 7 as an output

'Label for loop

'Output 7 to logical 0 which turns on LED

'Pause (do nothing) for 1000 milliseconds

'Output 7 to logical 1 which turns off LED

'Pause for 1000 ms

'Go back to beginning of loop called blink

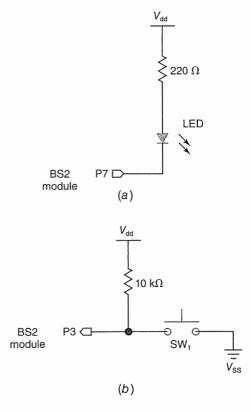


Fig. 13-32 (a) Output LED wired to P7 port of BS2 module. (b) Input switch wired to P3 of BS2 module.

A program using both the LED output and push-button switch input connected to a BS2 module (hardware is diagrammed in Fig. 13-32) is listed in Fig. 13-33. When downloaded into a BS2 module, the PBASIC program constantly checks if the switch is closed. If the switch is open, the **switchcheck:** loop repeats. However, if the switch is closed the microcontroller will jump to the **blink:** routine and flash the LED. After flashing the LED on and off once, the

program returns to the **switchcheck:** routine. The LED will flash on and off the entire time the input switch SW1 is closed.

The IF-THEN statement in the switchcheck: routine might need some explanation. In this example the condition if in3 = 0 (if input 3 is LOW) is evaluated by the microcontroller as either true or false. If the condition (if in3 = 0 or in English if switch SW1 is closed) is true, then the microcontroller causes a jump to the routine labeled blink. However, if the condition (if in3 = 0 or in English if switch SW1 is closed) is false, then the microcontroller continues to the next line of the program, which is the goto switchcheck command. IF-THEN commands are very important in the operation of microcontroller programs because they are the decision-making statements.

Microcontrollers, such as the BASIC Stamp modules, can respond to a variety of inputs such as switches, or variations in light, temperature, position, voltage, or resistance. The microcontroller's outputs can drive a variety of devices such as LEDs, piezo buzzers, speakers, displays (LED or LCD), relays, servos, or stepper motors. BASIC Stamp modules, especially when premounted on a work surface such as Parallax's Board of Education (BOE), allow for an easy introduction to programming and using microcontrollers.

Remember that microcontrollers are tiny computerlike devices that are embedded into products. Microcontrollers can respond to a limited number of inputs and control several output devices. After initial programming, most microcontrollers are single-use controllers as opposed to general-purpose personal computers.

'Input switch-output LED 1 'Title of PBASIC program (See Fig. 13-32.) output7 'Configure I/O P7 as output out7 = 1'Output 7 to 1 turning off LED input3 'Configure I/O P3 as input switchcheck: 'Label for switch checking routine if in 3 = 0 then blink 'If input 3 = 0 (switch closed), then go to blink routine goto switchcheck 'Check switch again (if input 3 = 1) blink: 'Label for LED blink routine out7 = 0'Output 7 to 0 which turns on LED pause 500 'Pause for 500 ms out7 = 1'Output 7 to 1 which turns off LED 'Pause for 500 ms pause 500 goto switchcheck 'Go back and check switch again

Fig. 13-33 Listing of the input switch-output LEO 1 program.

₩ Self-Test

Answer the following questions.

- 61. A BASIC Stamp module contains at least a _____ (microcontroller, microprocessor), voltage regulator, ceramic resonator, reset IC, and EEPROM chip for holding downloaded programs.
- 62. A BASIC Stamp 2 IC is programmed using a PBASIC editor program on your PC and downloaded to the module via the _____ (parallel, serial) port of your computer.
- 63. BASIC Stamp modules accept programs downloaded from a PC while a(n) ______ (interpreter, sequencer) program in firmware translates from the PBASIC high-level language to machine language used by the microcontroller.
- 64. Refer to Fig. 13-29. The $V_{\rm dd}$ pin of the BASIC Stamp 2 module is connected to

- _____ (+5 V, ground), while a pin labeled P7 would be a(n) _____ (I/O port, power connection).
- 65. Refer to Fig. 13-31. This program along with the circuit in Fig. 13-30 will blink the LED _____(continuously until power is turned off, once and stop).
- 66. Refer to Fig. 13-33. and the associated circuits in Fig. 13-32. If switch SW1 is closed, then the condition in the IF-THEN statement (if in3 = 0 then blink) will be ______ (false, true) and next line executed by the microcontroller will be _____ (blink:, goto switchcheck).
- 67. Once programmed, microcontrollers (like the BASIC Stamp modules) are _____ (single-purpose, general-purpose) devices that are commonly embedded in products.

13-11 Digital Signal Processing

Digital signal processing (DSP) has become a very popular field in digital electronics. DSP is used in many pieces of equipment such modems, DVD players, MP3 players, and cell

phones. While these are similar to the microcomputer systems you have just studied, DSP systems are more specialized.

Earlier you learned about analog and digital signals. Digital signal processing is used to analyze and modify digital signals. Many digital

DSP

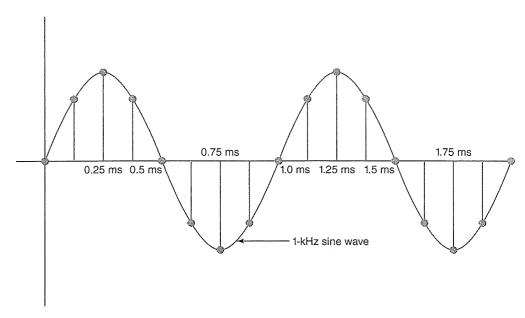


Fig. 13-34 Sampling a 1-kHz sine wave during analog-to-digital conversion.

signals used in DSP systems are acquired from analog signals using a process known as sampling. Sampling can be thought of as taking snapshots of an analog signal's voltage at fixed or discrete points in time. For this reason, digital signals are also called discrete-time signals. An example of a discrete-time signal acquired by sampling a 1-kHz analog sine wave is shown in Fig. 13-34. The blue line represents the analog signal, while the green dots and vertical lines describe the digital signal. The green dots/vertical lines are a "snapshot" of the analog signal at a given time and are digitized (converted into a number).

A simplified block diagram of a DSP system is shown in Fig. 13-35. The A/D converter (analog-to-digital converter) performs the sampling and converts the analog signal into a digital signal. The binary numbers from the A/D converter are stored in memory and used by the digital signal processor. The DSP performs many calculations which modifies the signal. The output of the DSP section is routed to the D/A converter (digital-to-analog converter). The D/A converter alters the signal from its digital to an analog form.

The most common type of calculation performed by the digital signal processor is

known as the sum-of-products. An example of a sum-of-products calculation is detailed in Fig. 13-36(a). In each row, the number from column A is multiplied by the number in column B to yield the result (product) in the product column. The right column in Fig. 13-36(a) is the sum of the products. Notice that for each row, the product of the multiplication for that row is added together, or summed, with the sum of the previous products. In DSP, the word accumulate is used for the process of adding the new product to the total of the previous products. This process of multiplying and accumulating is known as MAC. DSP systems need to perform thousands if not millions of these calculations per second. The mathematical equations that represent the calculations for each row of Fig. 13-36(a) are written in Fig. 13-36(b). Engineers who work with DSP use a shortened form of these equations shown in Fig. 13-36(c). You may encounter equations like one in Fig. 13-36(c) if you work in the DSP field.

Digital signal processors are specialized microprocessors that are optimized to quickly perform the repetitive calculations required by the MAC process. DSPs can perform many millions of instructions per second (MIPS).

Sum-of-products calculation

MAC A/D converter

D/A converter

MIPS

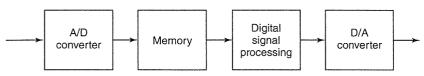


Fig. 13-35 Simplified block diagram of a DSP system.

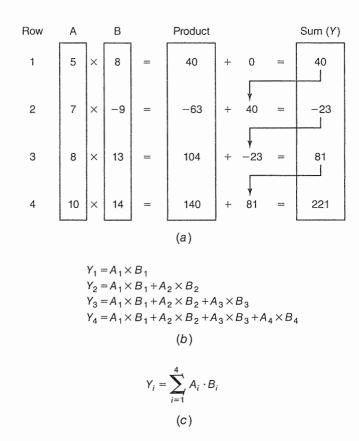


Fig. 13-36 Sum-of-products DSP calculations. (a) An example. (b) Formulas. (c) Another formula.

The basic architecture of a DSP is detailed in Fig. 13-37. Data are read into the separate program memory and data memory sections of the DSP. Samples from the A/D converter (see Fig. 13-35), which were stored in memory, are read into the data memory of the DSP. Fixed numbers called coefficients, which are designed to change the digital signal in a specific way, are read into the program memory. The numbers from program and data memory are multiplied together in the multiplier and stored in the *P register*. The accumulator then adds the results of the products stored in the P register with the previous sum of the products and stores the new result in the R register. Each output of the accumulator, stored in the R register, is a new output sample of the processed digital signal. The output is sent to the D/A converter to be changed back to an analog signal.

Digital signal processors use special registers such as the P and R registers so they can work on more than one task at a time. In an elementary MPU, such as the one in Fig. 13-4, each fetch-decode-execute sequence must finish before the next one can begin. DSPs, however, can fetch a new instruction while the

previous instruction is being decoded and another instruction is being executed. This process of starting a new task before the current one is finished is known as *pipelining*. Due to pipe-lining, the DSP in Fig. 13-37 will be performing all of the following tasks at the same time:


- 1. Writing the contents of the R register to the D/A converter.
- 2. Accumulating a new resulting sum of previous products.
- 3. Multiplying two numbers from the program and data memories.
- 4. Fetching a new sample into the data memory.

Pipelining is also used in most modern microprocessors. Pipelining may take various forms in microprocessors or DSPs but its purpose is to speed up the execution of instructions.

Digital signal processing systems are complex. This section only provides some of the basics of digital signal processing and digital signal processors. The use of DSP has been growing. It is expected that the need for people familiar with DSP will continue to grow.

Pipelining

Coefficients

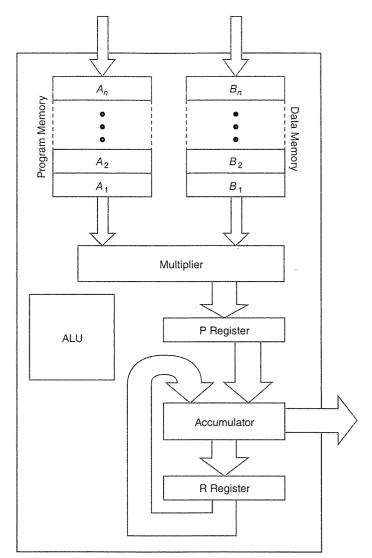

Digital signal processor

Fig. 13-37 Architecture of a digital signal processor.

Self-Test

Answer the following questions.

- 68. In the DSP field, another name that might be used for a digital signal is a(n) ______ signal.
- 69. During digital signal processing, what type of calculation is common?
- 70. In the DSP field, MAC stands for the process of ______
- 71. In a digital signal processor or other microprocessor, starting a task before the previous one is finished is called
- 72. A digital signal processor (DSP) is an IC designed for high-speed data manipulation used in audio, communications, image manipulation and other data acquisition and data control applications. (T or F)



13-12 DSP in a Digital Camera

Digital cameras have become very popular and are rapidly replacing film cameras for photography. Both types of cameras use lenses to focus light in order to record an image. Unlike film cameras, digital cameras make use of digital signal processing to store the image electronically.

Figure 13-38 shows a block diagram of the image capture section of a digital camera. The camera lens focuses the light of the image through a filter to either a charged coupled device (CCD) or a CMOS image sensor. The CCD or CMOS image sensor in the camera is the analog-to-digital converter of this system. Both types of light sensors use an array of photodiodes, one for each pixel in the image, to convert light energy into electric energy. CCDs and CMOS image sensors measure the

electric energy from the photodiode at each pixel location and convert it to a digital number. The big difference between CCDs and CMOS image sensors is where the analog-to-digital conversion is performed. CMOS image sensors perform the analog-to-digital conversion at each photodiode location. CCDs transport the stored electric charge from each photodiode across the array of photodiodes to one corner of the device where the analog-to-digital conversion is performed. You will learn more about analog-to-digital conversion in Chapter 14.

The purpose of the *filter* shown in Fig. 13-38 is to reduce the cost and complexity of the digital camera. Light is composed of three primary colors: red, green, and blue. Each pixel in a digital image stores three 8-bit values, one for each primary color of light. To properly create a digital image, the digital

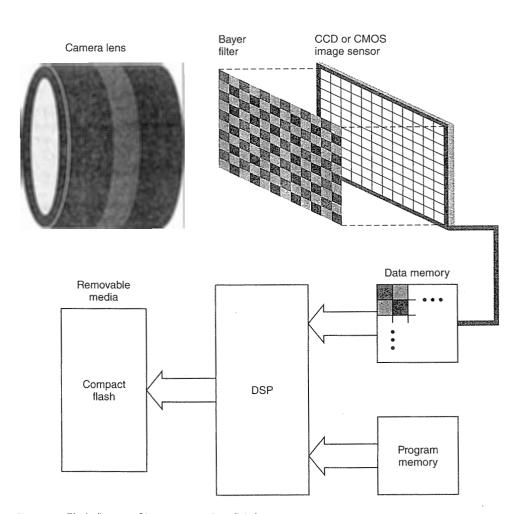


Fig. 13-38 Block diagram of image capture in a digital camera.

Charged coupled device (CCD)

CMOS image sensor

camera has to create samples for all three colors of light at each pixel location. However, CCDs and CMOS image sensors measure overall light intensity; they do not know anything about color. Instead of sampling the intensity of all three colors for each pixel, most digital cameras sample only one color for each pixel and the system later inserts values for the other two colors by looking at the values from neighboring pixels. The special Bayer filter shown in Fig. 13-38 filters the incoming light so that each photodiode in the image sensor sees only one color of light. The color of each square in the Bayer filter is the color of light that is allowed to pass through that filter to the photodiode of the image sensor behind it. You can see from Fig. 13-38 that the pattern of the Bayer filter is rows of red and green filters alternating with rows of blue and green filters. The reason that there are more green filters than red and blue filters is that the human eye is more sensitive to the green component of light than it is to the other two colors.

The output of the image sensor block of Fig. 13-38 is a series of bytes containing the sampled digital values from each photodiode in the image sensor. This series of sampled bytes is the digital signal input to the rest of the system. The samples are stored in temporary memory and read into the data input of the digital signal processor. Recall that a stored digital image needs three values, one for each primary color, for each pixel. At this point in the system, the digital signal has only one sampled value for each pixel. The digital signal processor in Fig. 13-38 runs an algorithm, or sequence of steps, to calculate the two missing color values for each pixel based on the sampled values from neighboring pixels. The process of calculating and inserting new data values from known existing values is called interpolation. Coefficients for the interpolation algorithm are the input to the program memory of the digital signal processor. The output from the digital signal processing block of Fig. 13-38 is a series of three 8-bit values for the red, green, and blue components of each pixel in the image. When the image is viewed, these three values are recombined to re-create the image.

Some cameras may store this RGB (for red, green, blue) output of the DSP block directly to a removable memory card in the camera, as shown in Fig. 13-38. However, digital images can be very large. For example, a 5-megapixel digital camera has 5 million image sensors, each measuring only one color of light for each pixel of the image. So each picture taken with a 5-megapixel camera would require 15 megabytes of memory. For this reason, most digital cameras also do some further processing of the digital signal. Digital cameras often compress the digital image so that it takes up less space when stored on the compact flash or other removable media card in the camera. The most common compression algorithm used by digital cameras is called JPEG after the group that created it, the Joint Photographic Experts Group. When compression is done, the original RGB output of the DSP block may once again be stored in temporary memory and read back into the DSP's data memory path. The program memory for the DSP is changed so that it contains coefficients used by the JPEG compression algorithm. The output of the DSP block is the JPEG compressed image that is then stored on the removable memory card.

The digital-to-analog conversion block of a digital signal processing system is not shown in Fig. 13-38. The digital-to-analog conversion for this system may happen in many places once the digital camera stores the image. The D/A conversion happens when the image is viewed on the LCD screen of the camera. If the image is moved to a personal computer, the D/A conversion will happen when the image is viewed on a monitor attached to the computer. The D/A conversion will also occur when the image is printed on a printer or taken to a photo developer that can print digital images.


This section examined some digital signal processing that occurs within a digital camera. Digital cameras use several digital signal processing algorithms to provide many features. Many other devices, such as cell phones, digital video cameras, and MP3 players, also use digital signal processing. Digital signal processing has become a part of many systems that we use in our everyday lives.

Bayer filter

JPEG

Algorithm

Interpolation

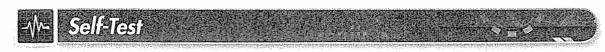


Answer the following questions.

- 73. Image sensors in digital cameras use
 _____ (solar cells, photodiodes) to
 convert light energy into electric energy.
- 74. Green light is ______ (blocked from passing through, allowed to pass through) a green light filter.

75.	(Inspiration, Interpolation) is
	the process of calculation and inserting
	new values from known existing values.

76.	Digital images store values for the
	three primary colors of light, which are
	and

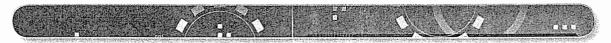

13-13 Microcontroller: Photo Input and Servo Motor Output

Robots come to mind when visualizing modern manufacturing. However, some simple mechanical actions can be controlled locally by embedded electronics. The control might take the form of an inexpensive microcontroller.

The concept of a valve used to control the flow of liquid, air flow, or light intensity is sketched in Fig. 13-39(a). This valve is being activated using a servo motor. A microcontroller could be used to manage the actions of the motor, thus opening and closing the valve. For more precise control a stepper motor could be used, which could also be controlled by a microcontroller.

The concept of developing back-and-forth (reciprocating) motion is diagrammed in Fig. 13-39(b). The reciprocating slide is activated by the back-and-forth motion of the servo motor arm in this sketch. A wire links the servo motor arm to the slide. A microcontroller could be used to manage the actions of the reciprocating slide.

Wiring the BASIC Stamp Circuit

Consider the circuit in Fig. 13-40. The BASIC Stamp 2 module is at the heart of the circuit with photocell input and a single output. With the proper programming, the BASIC Stamp 2 module can operate a mechanism like that shown in Fig. 13-39(b). The physical locations of the servo motor, slide mechanism, photocell, and wire linkage are sketched in Fig. 13-40(b).

The photocell in Fig. 13-40(a) is an inexpensive CdS photoresistive cell. You will recall that the CdS cell changes resistance when more or less light strikes its surface. More light striking the CdS cell means less resistance. Less light striking the photocell means it will have a higher resistance.

The photoresistive cell in Fig. 13-40(a) is wired in a *voltage divider circuit*. With more light striking the surface of the CdS cell its resistance is lowered. The low resistance photocell causes a low voltage input to port 7 of the microcontroller. This low voltage is interpreted by the microcontroller (input port 7) as a LOW logic level. When less light strikes the CdS cell, its resistance is higher. The high-resistance CdS cell causes a higher voltage input to port 7. The higher voltage is interpreted by the microcontroller (input port 7) as a HIGH logic level. The $10-k\Omega$ potentiometer can be adjusted to slightly increase or decrease the input voltages to the microcontroller for proper operation.

If you arrange the servo motor and input CdS photocell as in Fig. 13-40(*b*), the slide will slowly slide back and forth. The photocell will alternately exhibit low resistance and then high resistance to generate the logical LOW and HIGH inputs to the BASIC Stamp 2 module.

BASIC Stamp Programming

The procedure for programming, downloading, and running the BASIC Stamp program would be as follows:

1. Wire the circuit and arrange the servo motor and input photocell as shown in Fig. 13-40.

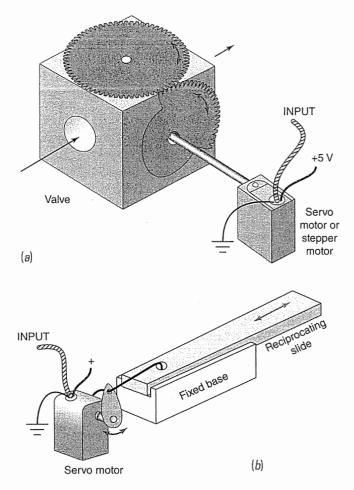


Fig. 13-39 Ideas for microcontroller use. (a) Valve opening and closing. (b) Reciprocating slide mechanism.


- 2. Start the MS Windows PBASIC editor on your PC.
- 3. Type the program shown in Fig. 13-41 and titled 'Read light-rotate servo.
- 4. Power on the BASIC Stamp board (such as BOE).
- 5. Download the PBASIC program using the serial port (or USB port) of the PC.
- 6. Disconnect the download cable.
- 7. Turn the BOE power off and then on.
- 8. The program will start as the servo motor arm, which alternately cycles the slide back and forth. You may have to adjust the exact location of the photocell. You may also have to adjust the 10-k Ω potentiometer for the light intensity.

The PBASIC 'Read light-rotate servo program is listed in Fig. 13-41.

Recall that in PBASIC the *remark* statements begin with an apostrophe ('). Remark statements are not executed by the BS2 module. They appear in the PBASIC editor listing to help understand the program.

Line 1 ('{\$STAMP BS2}) is a remark statement showing the version of BASIC Stamp module. Line 2 ('Read light-rotate servo) is a remark statement and the title of the program. Line 3 (x var byte) declares that variable x has a range from 0 to 255 in decimal or 00000000 to 111111111 in binary. Line 4 (output12) configures port 12 (P12) as an output (drives the servo). Line 5 (input7) configures port 7 (P7) as an input (voltage divider photocell).

Line 6 (**ckphotocell**:) is a *label* for the beginning of the *main routine* (checking input at P7 for HIGH or LOW). Line 7 (**if in7=0 then CW**) checks the logic level at input port 7. If the input is 0 (LOW logic level), the statement is true and

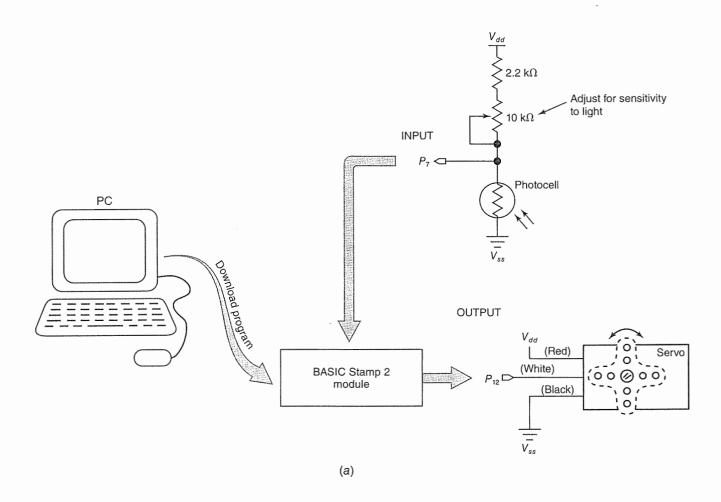

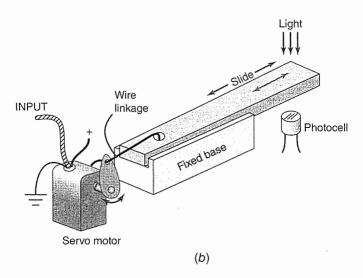


Fig. 13-40 (a) BASIC Stamp 2 microcontroller with photo input and servo motor output. (b) Physical arrangement of servo motor, photocell, and slide mechanism.

' { \$ STAMP BS2} 'Read light-rotate servo	'Title of PBASIC program (See Fig. 13-40.)	L1 L2
x var byte	'Declare variable x, range=0-255	L3
output12 input7	'Configure P12 as output (servo) 'Configure P7 as input (photocell-voltage divider)	L4 L5
mputi	Configure 17 as input (photocen-voltage divide)	ال الساد
ckphotocell:	'Label for checking photocell input (P7)	L6
if in7=0 then CW	'If input P7=LOW then go to CW routine	L7
IF IN7=1 then CCW	'If input P7=HIGH then go to CCW routine	L8
goto ckphotocell	'Go back to start of main routine	L9
CW:	'Label for CW rotation of servo routine	L10
for $x=1 \text{ TO } 30$	'Rotate servo CW	L11
pulsout 12,500	'PWM=1msec pulse	L12
pause 20	'PAUSE for 20 ms	L13
next	'Repeat loop till x=31	. L14
pause 2000	'Pause for 2000 ms	L15
goto ckphotocell	'Go back to main routine	L16
CCW:	'Label for CCW rotation of servo routine	L17
for x=1 TO 30	'Rotate servo CCW	L18
pulsout 12, 1000	'PWM=2msec pulse	L19
pause 20	'Pause for 20 ms	L20
next	'Repeat loop till x=31	L21
pause 2000	Pause for 2000 ms	L22
goto ckphotocell	'Go back to main routine	L23

Fig. 13-41 Listing of the read light-rotate servo program.

the program jumps to the CW subroutine (CW:). However, if input P7 is 1 (HIGH logic level), the statement is false and the program jumps to next line in the program. Line 8 (if in7=1 then CCW) checks the logic level at input port 7. If the input is 1 (HIGH logic level), the statement is true and the program jumps to the CCW subroutine.

One of the two subroutines (CW: or CCW:) is executed, powering the servo motor in either the clockwise or counterclockwise direction. Line 11 (for x = 1 to 30) starts a FOR-NEXT counting loop. The FOR-NEXT loop cycles 30 times as defined by the first statement (line 11). Each time through the CW: loop, the microcontroller generates a 1-ms pulse. This is sent to the servo motor via port 12

(pulsout12, 500). Recall that the small hobbytype servo motors we have used respond to the pulses of 1 ms by rotating clockwise. Thirty 1-ms pulses cause the servo motor to rotate fully clockwise. The (pause 20) adds a short pause of 20 ms between pulses. After exiting the FOR-NEXT counting loop, line 15 (pause 2000) causes a 2-second (2000-ms) pause. Line 16 (goto ckphotocell) sends the program back to the label ckphotocell:, starting the main routine again.

The CCW: subroutine (lines 17–23) operates like the CW: subroutine, except the pulsout 12, 1000 statement (line 19) generates 2-ms pulses. A series of thirty 2-ms pulses by the CCW: subroutine will cause the hobby-type servo motor to rotate fully counterclockwise.




Answer the following questions.

- 77. Refer to Fig. 13-40. The resistance of the CdS photocell _____ (decreases, increases) when exposed to brighter light.
- 78. Refer to Figs. 13-40 and 13-41. Port 7 of the microcontroller is configured as an _____ (input, output).
- 79. Refer to Figs. 13-40 and 13-41. The single output from the microcontroller is _____ (port 7, port 12).
- 80. Refer to Figs. 13-40 and 13-41. The hobby-type servo motor is driven by a technique called ______ (amplitude modulation, pulse-width modulation).
- 81. Refer to Figs. 13-40 and 13-41. When low light strikes the CdS photocell, its resistance is ______ (higher, lower),

- causing a ______ (higher, lower) voltage to enter port P7. This is interpreted by the microcontroller as a _____ (HIGH, LOW) logic level.
- 82. Refer to Figs. 13-40 and 13-41. The task of the main routine (lines 6-9) is to read input port P7 and execute either the **CW**: or **CCW**: subroutines. (T or F)
- 83. Refer to Figs. 13-40 and 13-41. The microcontroller senses a HIGH logic level at port 7. The next line of the 'Read light-rotate servo program to be executed after line 7 (if in7=0 then CW) will be line _______ (8, 10).



Chapter 13 Summary and Review

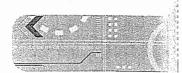

Summary

- 1. The computer is one of the most complex digital systems. It is unique because of its huge capacity, high speed, and stored programs.
- 2. The microcomputer is slower and less expensive than its larger counterparts. The microcomputer is a microprocessor-based digital system.
- 3. The microcomputer makes extensive use of both ROM and RAM for internal storage. Flash memory, optical, and hard disks are widely used for secondary bulk storage. Microcomputers support many peripheral input and output devices including networks.
- 4. Microprocessing unit instructions are composed of the operation and operand parts. The MPU follows the fetch-decode-execute sequence when running a program.
- 5. Combinational logic gates can be used for microcomputer address decoding.
- 6. Three-state devices, such as buffers, must be used when several memories and microprocessors transfer information over a common data bus.
- 7. Multiplexers and demultiplexers can be used for data transmission. More complex UARTs may also be used for serial data transmission.
- 8. Data transmission can be either serial or parallel. Various interface ICs are available for sending and receiving parallel and serial data. The USB standard is one of the most common used systems.
- Errors occurring during data transmission can be detected using parity bits or cyclic redundancy checks.

- A programmable logic controller (PLC) is a rugged computer system used in factories, warehouses, and chemical plants to control machines. PLCs are replacing hardwired relay logic for machine control.
- 11. Ladder relay schematics, ladder relay logic diagrams, logic gate diagrams, and Boolean expressions can all be used to describe a control logic problem.
- 12. A microcontroller is a "computer on a chip" embedded in many everyday devices. Microcontrollers contain a CPU, a small RAM (data memory), read-only memory (program memory containing firmware), a clock, and I/O pins.
- 13. Microcontrollers are produced in huge quantities at very low prices.
- 14. BASIC Stamp modules allow students and others to easily program and download code for directing the action of a microcontroller.
- 15. The PBASIC high-level language is used to program BASIC Stamp modules.
- 16. A digital signal processor (DSP) is a specialized microprocessor designed for high-speed data manipulation used in audio, communications, image manipulation, and other data acquisition and data control applications.
- 17. DSP devices are commonly used as part of a system including A/D converters, memory, DSP, and D/A converters.

Chapter Review Questions

Answer the fol	lowing	questions.
----------------	--------	------------

- 13-1. The CPU of a computer contains what three sections?
- 13-2. The ______ (ALU, MUX) section of a computer performs calculations and logic functions.
- 13-3. The more complex digital system is a _____ (computer, digital multimeter).
- 13-4. An IC called a(n) _____ is the heart of the CPU of a microcomputer.
- 13-5. Refer to Fig. 13-3. The parts of a microcomputer system are connected by control lines,

Chapter Review Questions...continued

	a(n) bus, and a two-way		(general-purpose office use; machine control in factories, warehouses, and
12.6	The input store print energies shown in		
13-6.	The input-store-print operation shown in	12 10	chemical plants).
	Fig. 13-6 required three instructions, which	13-19.	Once programmed, inputs to a
	use bytes of program memory.		(microcomputer, PLC) would probably come
13-7.	Classify these microcomputer peripheral de-		from devices such as limit switches, pressure
	vices as input, output, storage, or input/output		switches, and temperature and optical sensors.
	units:	13-20.	A programming module is always connected
	a. LCD monitor f. Laser printer		to a programmable logic controller, because
	b. Floppy disk drive g. Hard disk drive		program changes need to be made frequently.
	c. Keyboard h. Plotter		(T or F)
	d. Mouse i. Ethernet	13-21.	Refer to Fig. 13-24. The power supply, process-
	e. Modem		ing, input, and output sections are referred to as
13-8.	Microcomputer memory addresses are com-		modules because they are sometimes physically
	monly listed in (Gray code,		housed in separate enclosures in larger systems.
	hexadecimal).		(T or F)
13-9.	What do the following letters stand for when	13-22.	Given the relay schematic in Fig. 13-42, draw
	referring to a microcomputer system?		the ladder logic program that might be used
	a. CPU		with a PLC for this circuit.
	b. PIA	13-23.	Given the relay schematic in Fig. 13-42, write
	c. PPI		the Boolean expression that describes the logic
	d. UART		function of this circuit.
13-10.	The baud rate is the number of	13-24.	A (microcontroller, program-
	per second being transmitted serially through a		mable logic controller) can be described as
	data link.		a "computer on a chip" because it contains a
13-11.	The IEEE-488 standard is a common		CPU, RAM, read-only memory, clock, and I/O
	(parallel, serial) interface stan-		pins within a single IC.
	dard for the data link between a computer and	13-25.	Microcontrollers are most likely to appear
	scientific instrumentation.		(in the CPU section of a
13-12.	Draw the logic symbol and truth table for a		PC, embedded in electronic devices in your
	three-state buffer.		automobile).
13-13.	A MUX/DEMUX system converts parallel	13-26.	The microcontroller is noted for its small size
	input data to (asynchronous,		and (high, very low) cost.
	serial) data for transmission.	13-27.	Program memory in a microcontroller is
13-14.	A MUX/DEMUX system operates somewhat		held in a read-only memory device and
	like two (rotary, three-way)		is (constantly, rarely)
	switches.		reprogrammed.
13-15.	Errors in transmission can be detected by using		
10 10.	a (parity bit, rotary switch).	İ	SOL LS1 LS3 A
13-16.	An(AND, XOR) gate can	-	<u> </u>
15 10.	detect an odd number of 1s at its input.		× × V
13-17	The programmable controller is also		LS2 LS4
15 17.	commonly known as the	_	
	, or PLC.		
13-18	A programmable logic controller (PLC) is	I	
15-10.	a heavy-duty computer system designed for	F	iq. 13-42 Relay schematic diagram.
	a nour j dat j compator o jotom dobighou to		3

Chapter Review Questions...continued

13-28.	Microcontrollers are manufactured in (large, small) volumes.	13-42.	Refer to Fig. 13-29. Parallax's Board of Education development board is used by students
13-29.	Compared to microprocessors, microcontrollers commonly address (very large,		when studying and experimenting with the(BS1 IC, BS2 IC).
	very small) amounts of RAM (data memory).	13_43	Refer to Fig. 13-31. The purpose of the first
13-30	A microcontroller is the device that is consid-	15-45.	pause 1000 line of code would be to wait 1
15-50.	ered the CPU of a personal computer. (T or F)		second (1000 ms) for an input from an attached
13-31	The PIC16C55 IC is a (micro-		switch. (T or F)
15-51.	controller, PLC) featuring an EPROM program	13-44	The acronym DSP stands for
	memory that holds 512 words and a RAM data		In DSP, a digital signal might be referred to as
	memory that will hold 24 bytes.	15 15.	a (discrete-time, random-time)
13-32	The PIC16C55 IC would probably cost less		signal.
15-52.	than five dollars if purchased in small quanti-	13-46	Refer to Fig. 13-35. Sampling should be per-
	ties. (T or F)	15 10.	formed by the(A/D converter,
13_33	The PIC16C55 IC features a(n)		DSP) section of the system.
15-55.	(CISC, RISC) architecture employing only	13-47	The most common type of calculation per-
	33 commands in its instruction set.	15 17.	formed by a digital signal processor is known
13-34	Refer to Fig. 13-17. A three-input		as (multiply-and-shift left,
15 51.	(AND, XOR) gate could be		sum-of-products).
	used in place of the parity bit generator block.	13-48	Digital signal processors can perform
13-35	Refer to Fig. 13-17. A four-input	15 10.	(a few thousand, millions of)
10 00.	(NAND, XOR) gate could be used in place of		instructions per second.
	the error detector circuit.	13-49.	Refer to Fig. 13-35. The output of the DSP
13-36.	Refer to Fig. 13-15. The PIA block is sending	10 .,,	block is digital in nature and the D/A converter
10 00.	byte-wide (8 bits wide) data to the printer. This		changes this to a(n) (analog,
	is an example of(parallel,		multiplexed) signal.
	serial) transmission of data.	13-50.	The light sensors in a digital camera consist of
13-37.	Refer to Fig. 13-27. The PIC16C55 microcon-		a large array of (light-emitting
20 0 7 1	troller has a total ofI/O pins.		diodes, photodiodes), which convert light en-
	The master clear input is an		ergy into electric energy.
	(active HIGH, active LOW) reset pin that is also	13-51.	The image sensor in a digital camera may con-
	used during programming.		tain (many hundreds, many
13-38.	The BASIC Stamp 2 is packaged as a 24-pin		millions) of pixels or sensors.
	DIP and contains several components including	13-52.	To add color to a photo in a digital camera
	a custom PIC16C57 (micro-		a checkerboardlike-colored filter called a
	controller, PLC) with PBASIC interpreter in		(Bayer, UV) filter is placed
	firmware.		between the lens of the camera and the image
13-39.	The (EEPROM, ROM) IC on		sensor.
	the BASIC Stamp module is used for program	13-53.	The DSP block in a digital camera is a special-
	memory.		ized very fast microprocessor that can handle
13-40.	Programming in PBASIC is done on a		enormous amounts of processing in a very short
	(PC, small 12-key keypad) and		time. (T or F)
	then downloaded to the BASIC Stamp module.	13-54.	The CdS photocell, used as a light sensor in
13-41.	The (parallel, serial) port of		Fig. 13-40, exhibits lower resistance as the light
	a PC is used for downloading to the BASIC		striking the cell (decreases,
	Stamp 2 module.		increases).

Chapter Review Questions...continued

- 13-55. The hobby-type servo motor used in Fig. 13-40 rotates counterclockwise (CCW) when the dc voltage increases and CW as the dc voltage decreases. (T or F)
- 13-56. Refer to Fig. 13-40. With no light striking the surface of the CdS photocell, the voltage entering port 7 of the microcontroller increases. This is interpreted as a logical ______ (HIGH, LOW) by the BS2 module.
- 13-57. Refer to Figs. 13-40 and 13-41. If input 7 to the BS2 module is HIGH, the main routine (L6–L9) sends the program to the _____ (CW:, CCW:) subroutine.
- 13-58. Refer to Figs. 13-40 and 13-41. If input 7 to the BS2 module is LOW, the main routine (L6–L9) sends the program to the ______ (CW:, CCW:) subroutine. This causes the slide on the mechanism in Fig. 13-40(*b*) to _____ (extend, retract).
- 13-59. Refer to Figs. 13-40 and 13-41. Line 12

 (pulsout 12, 500) of the PBASIC program
 generates a(n) _______ (audio, PWM)
 signal of about 1 ms to drive the servo motor in
 a ______ (CW, CCW) direction.
- 13-60. Refer to Figs. 13-40 and 13-41. The group of PBASIC statements (L17–L23) in the BS2 module is referred to as the main routine. (T or F)

Critical Thinking Questions

- 13-1. Draw a block diagram of the organization of the five main sections of a computer. Show the flow of *program* information and *data* through the system.
- 13-2. Why do PLCs simulate relay logic so closely?
- 13-3. Given the relay schematic in Fig. 13-43, draw the ladder logic program that might be used with a PLC for this circuit.
- 13-4. Given the relay schematic in Fig. 13-43, draw the logic gate diagram for this circuit (use AND and OR symbols) and write the Boolean expression that describes the logic of the circuit.



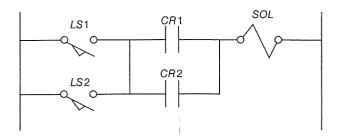


Fig. 13-43 Relay schematic diagram.

- 13-5. Refer to Fig. 13-44. The inputs in this problem are both ______ (active HIGH, active LOW) switches and the output LED is activated (turned on) with a _____ (HIGH, LOW).
- 13-6. Refer to Fig. 13-44. Line 4 in the PBASIC program (input 8) causes I/O port 8 of the BASIC Stamp 2 to be configured as a(n)
 ______ (input, time delay port).
- 13-7. Refer to Fig. 13-44. If the switch SW1 is pressed, the PBASIC program will cause a jump to the ______ (blink:, doubleblink:) routine and the LED will blink ______ (once, twice).
- 13-8. Refer to Fig. 13-44. If the switch SW2 is pressed, the PBASIC program will cause a jump to the ______ (blink:, doubleblink:) routine and the LED will blink _____ (once, twice).
- 13-9. Refer to Fig. 13-44. Remark statements shown in a PBASIC program are not executed by the microcontroller in the BASIC Stamp module. (T or F)

Critical Thinking Questions...continued

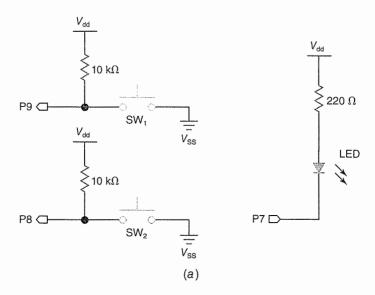

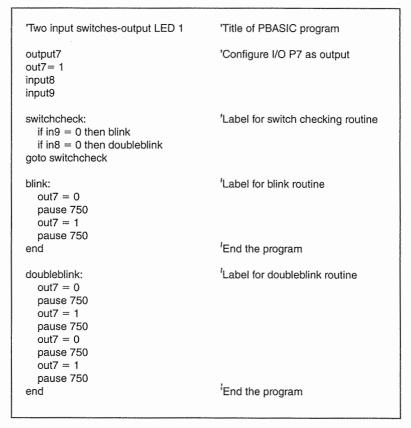

(b)


Fig. 13-44 Problem using BASIC Stamp 2. (a) External inputs and output. (b) PBASIC program listing.



Answers to Self-Tests

- 1. peripheral
- 2. size, stored program, speed, multipurpose
- 3. program information and data
- 4. data
- 5. programs
- 6. address, control
- 7. modem
- 8. LCD monitor
- 9. mouse
- 10. LAN
- 11. DSL
- 12. operation, operand
- 13. 100, 101
- 14. MPU (microprocessor)
- 15. decode-execute
- 16. sequential
- 17. address decoder
- 18. three-state buffers or tristate buffers
- 19. 0, 8
- 20. in its high-impedance state
- 21. multiplexer, demultiplexer
- 22. 1111
- 23. PIA (peripheral interface adapter)
- 24. UART (universal asynchronous receiver-transmitter)
- 25. baud
- 26. serial
- 27. even
- 28. XOR, XOR
- 29. 1
- 30. 0
- 31. XOR
- 32. cyclic redundancy check
- 33. ports
- 34. F
- 35. T
- 36. F
- 37. UARTs
- 38. full
- 39. F
- 40. F
- 41. flag
- 42. programmable logic controller
- 43. machine control in factories

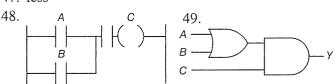- 44. limit switches, pressure switches, and temperature and optical sensors
- 45. occasionally during reprogramming
- 46. T
- 47. less



- 50. (A + B)C = Y
- 51. microcontroller
- 52. VCR
- 53. T
- 54. F
- 55. very small
- 56. microprocessor
- 57. microcontroller, 512, 24
- 58. less than 5
- 59. 33
- 60. firmware
- 61. microcontroller
- 62. serial
- 63. interpreter
- 64. +5 V, I/O port
- 65. continuously until power is turned off
- 66. true, blink:
- 67. single-purpose
- 68. discrete-time
- 69. sum-of-products
- 70. Multiplying and accumulating
- 71. pipelining
- 72. T
- 73. photodiodes
- 74. is allowed to pass through
- 75. Interpolation
- 76. red, green, blue
- 77. decreases
- 78. input
- 79. port 12
- 80. pulse-width modulation
- 81. higher, higher, HIGH
- 82. T
- 83. 8
- 84. 2



Connecting with Analog Devices

Learning Outcomes

This chapter will help you to:

- **14-1** Survey the concepts of A/D conversion and D/A conversion. Answer selected questions about a simple D/A converter.
- **14-2** Design an op-amp circuit with a given voltage gain.
- **14-3** Analyze the operation of a basic D/A converter composed of a resistor network and summing amplifier.
- **14-4** Analyze the operation of a ladder-type D/A converter composed of an R-2R ladder network and summing amplifier.
- **14-5** *Analyze* the operation of a counter-ramp A/D converter.
- **14-6** *Understand* the use of an operational amplifier as a voltage comparator.
- **14-7** Analyze the operation of an elementary digital voltmeter. Answer selected questions on the operation of the digital voltmeter.
- **14-8** *Understand* the theory of operation of a ramp-type A/D converter. *Analyze* the operation of a successive-approximation A/D converter. *Diagram* the logic used in successive-approximation A/D converters.
- **14-9** *Survey* important specifications of A/D converters. *Answer* selected questions about A/D converter specifications.
- **14-10** *Test* the operation the ADC0804 8-bit A/D converter IC. *Answer* selected questions about the ADC0804 A/D converter IC.
- **14-11** Analyze the operation of two different light meter circuits using a CdS photocell sensor as input. Answer selected questions on the A/D circuitry and CdS photocell input.
- **14-12** *Test* the operation of a thermistor temperature sensor. *Digitize* the output of the thermistor using a Schmitt-trigger inverter IC. *Survey* several more expensive linear thermal sensors.

tering or leaving a digital system have been digital information. Many digital systems, however, have analog inputs that vary continuously between two voltage levels. In this chapter, we discuss the interfacing of analog devices to digital systems.

Interfacing

Most real-world information is analog. For instance, time, speed, weight, pressure, light intensity, and position measurements are all analog in nature.

The digital system in Fig. 14-1 has an analog input. The voltage varies continuously from 0 to 3 V. The *encoder* is an electronic device that converts the analog signal to digital information. The encoder is called an *analog-to-digital converter* or *A/D converter*. The A/D converter, then, converts analog information to digital data.

The digital system diagrammed in Fig. 14-1 also has a *decoder*. This decoder is a special type: It converts the digital information from the digital processing unit to an analog output. For instance, the analog output may be a continuous voltage change from 0 to 3 V. We call this decoder a *digital-to-analog converter* or *D/A converter*. The D/A converter, then, decodes digital information to analog form.

The entire system in Fig. 14-1 might be called a *hybrid system* because it contains both digital and analog devices. The encoders and decoders that convert from analog to digital and digital to analog are called *interface devices* by engineers and technicians. The word "interface" is generally used when referring to a device or circuit that converts from one mode of operation to another. In this case we are converting between analog and digital data.

Note that the input block in Fig. 14-1 refers to an analog voltage ranging from 0 to 3 V. This voltage could be produced by a transducer. A

Analog-to-digital converter

A/D converter

D/A converter

Hybrid system

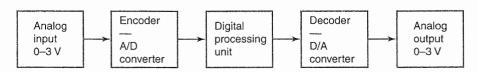


Fig. 14-1 A digital system with analog input and analog output.

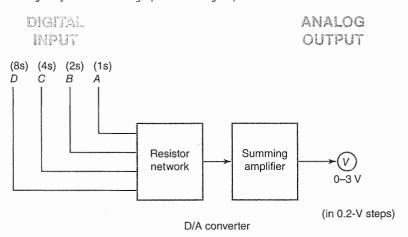


Fig. 14-2 Block diagram of a D/A converter.

Transducer

Resistor network Summing amplifier (scaling amplifier)

transducer is defined as a device that converts one form of energy to another. For instance, a photocell could be used as an input transducer to give a voltage proportional to light intensity. In this example, light energy is being converted into electric energy by the photocell. Other transducers might include microphones, speakers, strain gauges, photoresistive cells, temperature sensors, potentiometers, distance sensors, and Hall-effect sensors.

D/A Conversion 14-1

Refer to the D/A converter in Fig. 14-1. Let us suppose we want to convert the binary from the processing unit to a 0- to 3-V output. As with any decoder, we must first set up a truth table of all the possible situations. Table 14-1 shows four inputs (D, C, B, A) into the D/A converter. The inputs are in binary form so the exact value of the inputs is not important. Each 1 is about +3 to +5 V. Each 0 is about 0 V. The outputs are shown as voltages in the rightmost column in Table 14-1. According to the table, if binary 0000 appears at the input of the D/A converter, the output is 0 V. If binary 0001 is the input, the output is 0.2 V. If binary 0010 appears at the input, then the output is 0.4 V. Notice that for each row you progress downward in Table 14-1, the analog output increases by 0.2 V.

A block diagram of a D/A converter is shown

	Troton diagram of a birrorder is one with
i	in Fig. 14-2. The digital inputs (D, C, B, A) are
2	at the left. The decoder consists of two sections:
t	the resistor network and the summing amplifier.

Table 14-1 Truth Table for D/A Converter

	ALL SILVANIA	Dig Inp			Analog Output
	\overline{D}	С	В	Α	Volts
Row 1	0	0	0	0	0
Row 2	0	0	0	1	0.2
Row 3	0	0	1	0	0.4
Row 4	0	0	1	1	0.6
Row 5	0	1	0	0	8.0
Row 6	0	1	0	1	1.0
Row 7	0 `	1	1	0	1.2
Row 8	0	1	1	1	1.4
Row 9	1	0	0	0	1.6
Row 10	. 1	0	0	1	1.8
Row 11	1	0	1	0	2.0
Row 12	1	0	1	1	2.2
Row 13	1	1	0	0	2.4
Row 14	1	1	0	1	2.6
Row 15	1	1	1	0	2.8
Row 16	1	1	1	1	3.0

The output is shown as a voltage reading on the voltmeter at the right.

The resistor network in Fig. 14-2 must take into account that a 1 at input B is worth twice as much as a 1 at input A. Also, a 1 at input C is worth four times as much as 1 at input A. Several arrangements of resistors are used to do this job. These circuits are called *resistive ladder networks*.

The summing amplifier in Fig. 14-2 takes the output voltage from the resistor network

and amplifies it the proper amount to get the voltages shown in the rightmost column of Table 14-1. The summing amplifier typically uses an IC unit called an *operational amplifier*. An operational amplifier is often simply called an *op amp*. The summing amplifier is also called a *scaling amplifier*.

The special decoder called a D/A converter consists of two parts: a group of resistors forming a resistive ladder network and an op amp used as the summing amplifier.

Operational amplifier (op amp)

-{\}-

Self-Test

Supply the missing word in each statement.

- A special encoder that converts from analog to digital information is called a(n) ______.
- A special decoder that converts from digital to analog information is called a(n) ______.
- 3. A D/A converter consists of a(n)
 _____ network and a(n) _____
 amplifier.
- 4. The name "op amp" stands for

- 5. Refer to Fig. 14-2 and Table 14-1. If the binary input to the D/A converter is 0111₂, the analog output will be ______ volts.
- Refer to Fig. 14-2 and Table 14-1. If the binary input to the D/A converter is 1111₂, the analog output will be ______ volts.
- 7. Refer to Fig. 14-2 and Table 14-1. If the binary input increases from 0001 to 0010, the analog output will increase by ______ volts.



14-2 Operational Amplifiers

The special amplifiers called *op amps* are characterized by high input impedance, low output impedance, and a variable voltage gain that can be set with external resistors. The symbol for an op amp is shown in Fig. 14-3(a). The op amp shown has two inputs. The top input is labeled an *inverting input*. The inverting input is shown by the minus sign (–) on the symbol. The other input is labeled a *noninverting input*. The noninverting input is shown by the plus sign (+) on the symbol. The output of the amplifier is shown on the right of the symbol.

The operational amplifier is almost never used alone. Typically, the two resistors shown in Fig. 14-3(b) are added to the op amp to set the voltage gain of the amplifier. Resistor R_{in}

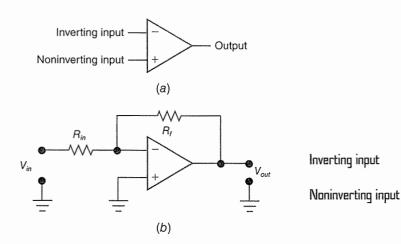


Fig. 14-3 Operational amplifier. (a) Symbol. (b) With input and feedback resistors for setting gain.

is called the input resistor. Resistor R_f is called the feedback resistor. The *voltage gain* of this amplifier is found by using the simple formula

$$A_{\nu}$$
 (voltage gain) = $\frac{R_f}{R_{in}}$

Suppose the values of the resistors connected to the op amp are $R_f = 10 \text{ k}\Omega$ and $R_{in} = 10 \text{ k}\Omega$. Using our voltage gain formula, we find that

$$A_{\nu} = \frac{R_f}{R_{in}} = \frac{10,000}{10,000} = 1$$

The gain of the amplifier is 1. In our example, if the input voltage at V_{in} in Fig. 14-3(b) is 5 V, the output voltage at V_{out} is 5 V. The inverting input is being used, and so if the input voltage is +5 V, then the output voltage is -5 V. The voltage gain of the op amp can also be calculated using the formula

$$A_{v} = \frac{V_{out}}{V_{in}}$$

The voltage gain for the circuit above is then

$$A_{v} = \frac{V_{out}}{V_{in}} = \frac{5}{5} = 1$$

The voltage gain is again found to be 1.

Suppose the *input and feedback resistors* are 1 k Ω and 10 k Ω , as shown in Fig. 14-4. What

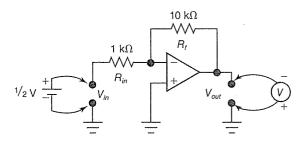


Fig. 14-4 Amplifier circuit using an op amp.

is the voltage gain for this circuit? The voltage gain is calculated as

$$A_{\nu} = \frac{R_f}{R_{in}} = \frac{10,000}{1,000} = 10$$

The voltage gain is 10. If the input voltage is +0.5 V, then the voltage at the output is how many volts? If the gain is 10, then the input voltage of 0.5 V times 10 equals 5 V. The output voltage is -5 V, as measured on the voltmeter in Fig. 14-4.

You have seen how the voltage gain of an opamp can be changed by changing the ratio between the input and feedback resistors. You should know how to set the gain of an operational amplifier by using different values for R_{in} and R_{f}


In summary, the op amp is part of a D/A converter; it is used as a *summing amplifier* in the converter. The gain of the op amp is easily set by the ratio of the input and feedback resistors.

Summing amplifier Input and feedback resistors

-N- Self-Test

Answer the following questions.

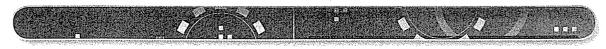- 8. Refer to Fig. 14-3(b). The resistor labeled R_f in this op-amp circuit is called the _____ resistor.
- 9. Refer to Fig. 14-3(*b*). The resistor labeled R_{in} in this op-amp circuit is called the _____ resistor.
- 10. What is the voltage gain (A_{ν}) of an op amp such as the one shown in Fig. 14-3(b) if $R_{in} = 1 \text{ k}\Omega$ and $R_{f} = 20 \text{ k}\Omega$?
- 11. What is the output voltage (V_{out}) from the op amp in question 10 if the input voltage is +0.2 V?
- 12. What is the voltage gain (A_{ν}) of an op amp such as the one shown in Fig. 14-3(b) if $R_{in} = 5 \text{ k}\Omega$ and $R_{\epsilon} = 20 \text{ k}\Omega$?
- if $R_{in} = 5 \text{ k}\Omega$ and $R_f = 20 \text{ k}\Omega$? 13. What is the output voltage (V_{out}) from the op amp in question 12 if the input voltage is +1.0 V?



14-3 A Basic D/A Converter

A simple D/A converter is shown in Fig. 14-5. The D/A converter is made in two sections. The *resistor network* on the left is made up of

resistors R_1 , R_2 , R_3 , and R_4 . The summing amplifier on the right consists of an op amp and a feedback resistor. The input (V_{in}) is 3 V applied to switches D, C, B, and A. The output voltage

Resistor network

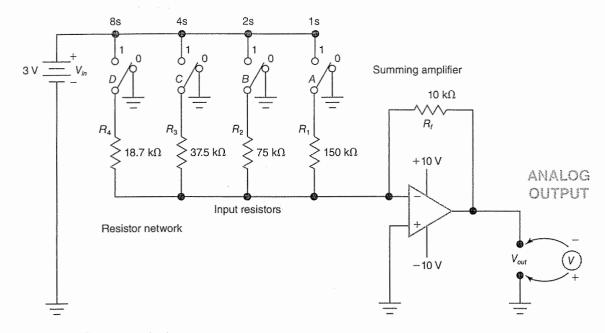


Fig. 14-5 A D/A converter circuit.

Basic D/A converter

 (V_{out}) is measured on a voltmeter. Notice that the op amp requires a dual power supply: a +10-V supply and a -10-V supply.

With all switches at GND (0 V), as shown in Fig. 14-5, the input voltage at point A is 0 V and the output voltage is 0 V. This corresponds to row 1, Table 14-1. Suppose we move switch A to the logical 1 position in Fig. 14-5. The input voltage of 3 V is applied to the op amp. We next calculate the gain of the amplifier. The gain is dependent upon the feedback resistor (R_i), which is 10 k Ω , and the input resistor (R_i), which is the value of R_1 , or 150 k Ω . Using the gain formula, we have

$$A_{\nu} = \frac{R_f}{R_{in}} = \frac{10,000}{150,000} = 0.066$$

To calculate the output voltage, we multiply the gain by the input voltage as shown here:

$$V_{out} = A_{v} \times V_{in} = 0.066 \times 3 = 0.2 V$$

The output voltage is 0.2 V when the input is binary 0001. This satisfies the requirements of row 2, Table 14-1.

Let us now apply binary 0010 to the D/A converter in Fig. 14-5. Only switch *B* is moved to the logical 1 position, applying 3 V to the op amp. The gain is

$$A_{\nu} = \frac{R_f}{R_{\odot}} = \frac{10,000}{75,000} = 0.133$$

Multiplying the gain by the input voltage gives us 0.4 V. The 0.4 V is the output voltage. This satisfies row 3, Table 14-1.

Notice that for each binary count in Table 14-1, the output voltage of the D/A converter increases by 0.2 V. This increase occurs because of the increased voltage gain of the op amp as we switch in different resistors (R_1 , R_2 , R_3 , and R_4). If only resistor R_4 from Fig. 14-5 were connected by activating switch D, the gain would be

$$A_{\nu} = \frac{R_f}{R_{in}} = \frac{10,000}{18,700} = 0.535$$

The gain multiplied by the input voltage of 3 V gives 1.6 V at the output of the op amp. This is what is required by row 9, Table 14-1.

When all switches are activated (at logical 1) in Fig. 14-5, the op amp puts out the full 3 V because the gain of the amplifier has increased to 1.

Any input voltage up to the limits of the operational-amplifier power supply ($\pm 10~V$) maybe used. More binary places may be added by adding switches. If a 16s place value switch is added in Fig. 14-5, it needs a resistor with half the value of resistor R_4 . Its value would then have to be 9350 Ω . The value of the feedback resistor would also be changed to 5 k Ω . The input would then be a 5-bit binary

number; the output would still be an analog output varying from 0 to -3.1 V (in 0.1 V steps).

Trying to expand D/A converter in Fig. 14-5 to many bits results in an impractical range of resistor values and poor accuracy.

-Ņ- Self-Test

Answer the following questions.

- 14. Calculate the voltage gain of the op amp in Fig. 14-5 when only switch *C* (the 4s switch) is at logical 1.
- 15. Using the voltage gain from question 14, calculate the output voltage of the D/A converter in Fig. 14-5 when only switch *C* is at logical 1.
- 16. List two limitations of the basic D/A converter shown in Fig. 14-5 for large binary words.
- 17. Calculate the voltage gain of the op amp in Fig. 14-5 when both switches A and B are at logical 1 [Hint: Use parallel resistance formula $R_T = (R_1 \times R_2)/(R_1 + R_2)$].
- 18. Using the voltage gain from question 17, calculate the output voltage from the D/A converter in Fig. 14-5 when both input switches A and B are at logical 1.



Ladder-type D/A converters

R-2R ladder network

14-4 Ladder-Type D/A Converters

Digital-to-analog converters consist of a resistor network and a summing amplifier. Figure 14-6 diagrams a type of resistor network that provides the proper weighting for the binary inputs. This resistor network is sometimes called the R-2R ladder network. The advantage of this arrangement of resistors is that only two values of resistors are used. Resistors R_1 , R_2 , R_3 , R_4 , and R_5 are 20 k Ω each. Resistors R_6 , R_7 , R_8 , and R_6 are each 10 k Ω . Notice that all the horizontal resistors on the "ladder" are exactly twice the value of the vertical resistors, hence the title R-2R ladder network.

The summing amplifier in Fig. 14-6 is the same one used in the last section. Again notice the use of the dual power supply on the op amp.

The operation of this D/A converter is similar to the basic one in the last section. Table 14-2 details the operation of this D/A converter. Notice that we are using an input voltage of 3.75 V on this converter. Each binary count increases the analog output by 0.25 V, as shown

Table 14-2 Truth Table for D/A Converter

_	Binary	Inputs		
8s	4s	2s	1s	Analog Output
D	С	В	Α	Volts
.0	0	0	0	0 ,
0	0	0	1	0.25
0	0	1	0	0.50
0	0	1	1	0.75
0	1	0	0	1.00
0	1	0	1	1.25
0	1	1	0	1.50
0	1	1	1	1.75
\1	0	0	0	2.00
1	0	0	1	2.25
1	0	1	0	2.50
1	0	1	1	2.75
1	1	0	0	3.00
1	1	0	1	3.25
1	1	1	0	3.50
1	1	1	1	3.75

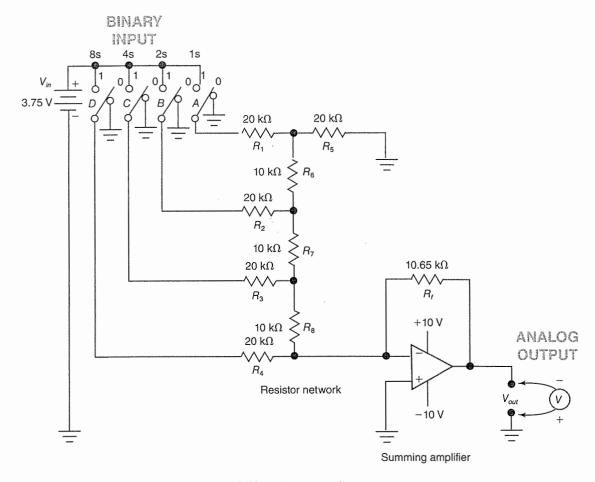


Fig. 14-6 A D/A converter circuit using an R-2R ladder resistor network.

in the rightmost column of Table 14-2. Remember that each 0 on the input side of the table means 0 V applied to that input. Each 1 on the input side of the table means 3.75 V applied to that input. The input voltage of 3.75 V is used because this is very close to the output of TTL counters and other ICs you may have used. The inputs (*D*, *C*, *B*, and *A*) in Fig. 14-6, then, could be connected directly to the outputs of a TTL IC and operate according to Table 14-2. In actual practice, however, the outputs of a TTL IC are not accurate enough; they have to be put

through a level translator to get a very precise voltage output.

More binary places (16s, 32s, 64s, and so on) can be added to the D/A converter in Fig. 14-6. Follow the pattern of resistor values shown in this diagram when adding place values.

Two types of special decoders called digital-to-analog converters have been covered. The R-2R ladder-type D/A converter has some advantages over the more basic unit. The heart of the D/A converter consists of the resistor network and the summing amplifier.

-N- Self-Test

Answer the following questions.

- 19. The digital-to-analog converter in Fig. 14-6 is a(n) ______ -type D/A converter.
- 20. Refer to Fig. 14-6. The gain of the op amp is greatest when all input switches are at logical ______(0, 1).
- 21. Refer to Fig. 14-6 and Table 14-2. The gain of the op amp is *least* when switch

- A, B, C, D) is the only switch at logical 1.
- 22. Refer to Fig. 14-6 and Table 14-2. If the binary input to the D/A converter is 1011, the analog output voltage is ______ volts.
- 23. Refer to Fig. 14-6 and Table 14-2. If the binary input to the D/A converter increases from 0111 to 1000, the analog output voltage increases by _______ volts.



A/D converter

Voltage comparator

14-5 An A/D Converter

An analog-to-digital converter is a special type of encoder. A basic block diagram of an A/D converter is shown in Fig. 14-7. The input is a single variable voltage. The voltage in this case varies from 0 to 3 V. The output of the A/D converter is in binary. The A/D converter translates the analog voltage at the input into a 4-bit binary word. As with other encoders, it is well to define exactly the expected inputs and outputs. The truth table in Table 14-3 shows how the A/D converter should work. Row 1 shows 0 V being applied to the input of the A/D converter. The output is binary 0000. Row 2 shows a 0.2-V input. The output is binary 0001. Notice that each increase of 0.2 V increases the binary count by 1. Finally, row 16 shows that when the maximum 3 V is applied to the input, the output reads binary 1111. Notice that the truth table in Table 14-3 is just the reverse of the D/A converter truth table in Table 14-1; the inputs and outputs have just been reversed.

The truth table for the A/D converter looks quite simple. The electronic circuits that perform

the task detailed in the truth table are somewhat more complicated. One type of A/D converter is diagrammed in Fig. 14-8. The A/D converter contains a *voltage comparator*, an AND gate, a binary counter, and a D/A converter. All the sections of the A/D converter except the comparator are familiar to you.

The analog voltage is applied at the left of Fig. 14-8. The comparator checks the voltage coming from the D/A converter. If the analog input voltage at A is greater than the voltage at input B of the comparator, the clock is allowed to increase the count of the 4-bit counter. The count on the counter increases until the feedback voltage from the D/A converter becomes greater than the analog input voltage. At this point the comparator stops the counter from advancing to a higher count. Suppose the input analog voltage is 2 V. According to Table 14-3, the binary counter increases to 1010 before it is stopped. The counter is reset to binary 0000, and the counter starts counting again.

Now for more detail on the A/D converter in Fig. 14-8. Let us assume that there is a logical 1 at point X at the output of the comparator. Also

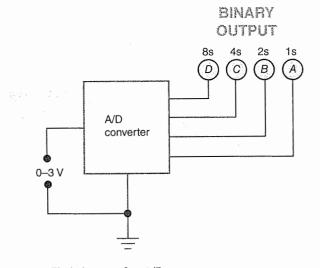


Fig. 14-7 Block diagram of an A/D converter.

Table 14-3 Truth Table for A/O Converter

			Bina Outp		
	Analog Input	8s	4s	2s	1s
	Volts	D	С	В	Α
Row 1	0	0	0	0	0
Row 2	0.2	0	0	0	1
Row 3	0.4	0	0	1	0
Row 4	0.6	0	0	1	1
Row 5	0.8	0	1	0	0
Row 6	1.0	0	1	0	1
Row 7	1.2	0	1	1	0
Row 8	1.4	0	1	1	1
Row 9	1.6	1	0	0	0
Row 10	1.8	1	0	0	1
Row 11	2.0	1	0	1	0
Row 12	2.2	1	0	1	1
Row 13	2.4	1	1	0	0
Row 14	2.6	1	1	0	1
Row 15	2.8	1	1	1	0
Row 16	3.0	1	1	1	1

assume that the counter is at binary 0000. Assume, too, that 0.55 V is applied to the analog input. The 1 at point X enables the AND gate, and the first pulse from the clock appears at the CLK input of the counter. The counter advances its count to 0001. The 0001 is displayed on the lights in the upper right of Fig. 14-8. The 0001 is also applied to the D/A converter.

According to Table 14-1, a binary 0001 produces 0.2 V at the output of the D/A converter. The 0.2 V is fed back to the *B* input of the comparator. The comparator checks its inputs. The *A* input is higher (0.55 V as opposed to 0.2 V), and so the comparator outputs a logical 1. The 1 enables the AND gate, which lets the next clock pulse through to the counter. The counter advances its count by 1. The count is now 0010. The 0010 is applied to the D/A converter.

According to Table 14-1, a 0010 input produces a 0.4-V output. The 0.4 V is fed back to the *B* input of the comparator. The comparator again checks the *B* input against the *A* input; the *A* input is still larger (0.55 V as opposed to 0.4 V). The comparator outputs a logical 1. The AND gate is enabled, letting the next clock pulse reach the counter. The counter increases its count to binary 0011. The 0011 is applied back to the D/A converter.

According to Table 14-1, a 0011 input produces a 0.6 V output. The 0.6 V is fed back to

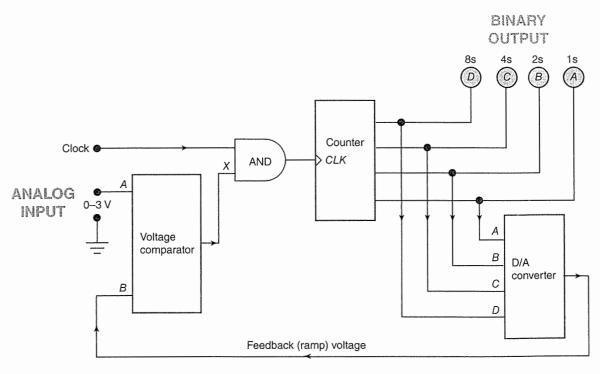


Fig. 14-8 Block diagram of a counter-ramp-type A/D converter.

the *B* input of the comparator. The comparator checks input *A* against input *B*; for the first time the *B* input is larger than the *A* input. The comparator outputs a logical 0. The logical 0 disables the AND gate. No more clock pulses can reach the counter. The counter stops at binary 0011. A look at row 4, Table 14-3, shows that 0.6 V gives the readout of binary 0011. Our A/D converter has worked according to the truth table.

Counter-ramp A/D converter Ramp

If the input analog voltage were 1.2 V, the binary output would be 0110, according to Table 14-3. The counter would have to count from binary 0000 to 0110 before being stopped by the comparator. If the input analog voltage were 2.8 V, the binary output would be 1110. The counter would have to count from binary

0000 to 1110 before being stopped by the comparator. Notice that it does take some time for the conversion of the analog voltage to a binary readout. However, in most cases the clock runs fast enough so that this time lag is not a problem.

You now should appreciate why we studied the D/A converter before the A/D converter. This *counter-ramp A/D converter* is fairly complex and needs a D/A converter to operate. The term "ramp" in the name for this converter refers to the gradually increasing voltage from the D/A converter that is fed back to the comparator. A 4-bit converter produces a staircase waveform. When enough bits are used, the waveform approaches a smooth ramp.

-W-

Self-Test

Supply the missing word or words in each statement.

- 24. An A/D converter will translate a(n)
 ______ input voltage into a(n)
 _____ output.
- 25. Refer to Table 14-3. If the analog input voltage is 1 V, the binary output will be
- 26. Refer to Fig. 14-8. When the voltage at point *B* is less than *A*, the output of the comparator at point *X* is ______ (HIGH, LOW). This causes the clock pulses to ______ (be blocked by, pass through) the AND gate.

- 27. The unit diagrammed in Fig. 14-8 is a(n) _______-type A/D converter.
- 28. Refer to Fig. 14-8. The feedback voltage from the D/A converter to input *B* of the _____ (counter, comparator) would appear as a ramp or "stair-step shape" waveform if observed on an oscilloscope.
- 29. Refer to Fig. 14-8. The comparator compares the ______ (binary values, voltages) at inputs *A* and *B*.
- Refer to Fig. 14-8. The _______(AND, XOR) gate blocks clock pulses from getting to the counter when the output of the comparator goes ______(HIGH, LOW).



14-6 Voltage Comparators

Voltage comparator In the last section we used a *voltage comparator*. We found that a comparator compares two voltages and tells us which is the larger of the two. Figure 14-9 is a basic block diagram of a comparator. If the voltage at input A is larger than at input B, the comparator gives a logical 1 output. If the voltage at input B is larger than at input A, the output is a logical 0. This is written A > B = 1 and B > A = 0 in Fig. 14-9.

The heart of a voltage comparator is an op amp. Figure 14-10(a) shows a comparator

circuit. Notice that input A has 1.5 V applied and input B has 0 V applied. The output voltmeter reads about 3.5 V, or a logical 1.

Figure 14-10(b) shows that the input B voltage has been increased to 2 V. Input A is still at

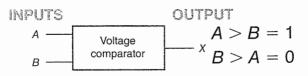


Fig. 14-9 Block diagram of a voltage comparator.

Op amp

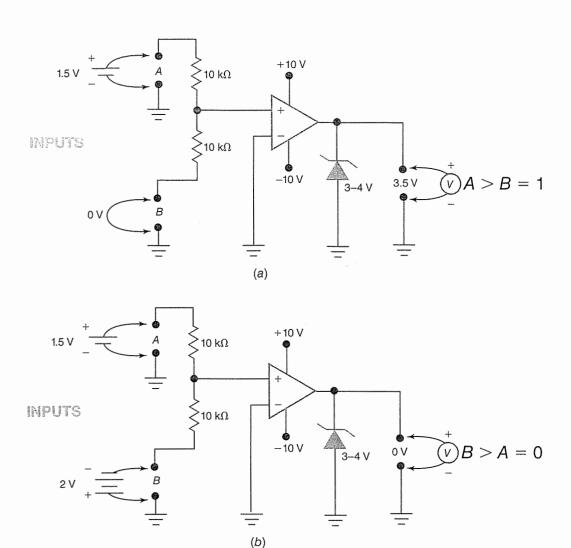


Fig. 14-10 Voltage comparator circuit. (a) With greater voltage at input A. (b) With greater voltage at input B.

1.5 V. Input B is larger than input A. The output of the comparator circuit is about 0 V (actually the voltage is about -0.6 V), or a logical 0.

The comparator in the A/D converter in Fig. 14-8 works exactly like this unit. The *zener*

diode in the comparator in Fig. 14-10 is there to clamp the output voltage at about +3.5 or -0.6 V. Without the zener diode the output voltages would be about +9 and -9 V. The +3.5 and -0.6 V are more compatible with TTL ICs.

Voltage comparator circuit

Zener diode

-√V- Self-Test

Answer the following questions.

- 31. The comparator block shown in Fig. 14-8 compares two _____ (binary numbers, decimal numbers, dc voltages).
- 32. A voltage comparator circuit can be constructed using a(n) ______ IC, several resistors, and a zener diode.
- 33. Refer to Fig. 14-10. When input B

increases and becomes higher than input A, the output of the op amp will change from ______ (HIGH, LOW) to _____ (HIGH, LOW).

34. Refer to Fig. 14-10. The _____ (10-k Ω resistor, zener diode) "clamps" the output voltages of the op amp to about 3.5 V (HIGH) or 0.6 V (LOW).



Elementary digital voltmeter

14-7 An Elementary Digital Voltmeter

One use for an A/D converter is in a digital voltmeter. You have already used all the subsystems needed to make an elementary digital voltmeter system. A block diagram of a simple digital voltmeter is shown in Fig. 14-11. The A/D converter converts the analog voltage to binary form. The binary is sent to the decoder, where it is converted to a seven-segment code. The seven-segment readout indicates the voltage in decimal numbers. With 7 V applied to the input of the A/D converter, the unit outputs binary 0111, as shown. The decoder activates lines a to c of the seven-segment display; segments a to c light on the display. The display reads as a decimal 7. Note that the A/D converter is also classified as an encoder; it encodes from an analog input to a binary output.

A wiring diagram of an elementary digital voltmeter is shown in Fig. 14-12. Notice the voltage comparator, the AND gate, the counter, the decoder, the seven-segment display, and the D/A converter. Several power supplies are needed to set up this circuit. A dual ±10-V supply (or two individual 10-V supplies) is used for the 741 op amps. A 5-V supply is used for the 7408, 7493, and 7447 TTL ICs and the seven-segment LED display. A 0- to 10-V variable dc power supply is also needed for the analog input voltage.

Let us assume a 2-V input to the analog input of the digital voltmeter in Fig. 14-12. Reset the counter to 0000. The comparator checks inputs A and B; A is larger (A = 2 V, B = 0 V). The comparator's output is a logical 1. This 1 enables the AND gate. The pulse from the clock passes through the AND gate. The pulse causes the counter to advance one count. The count is

now 0001. The 0001 is applied to the decoder. The decoder enables lines b and c of the seven-segment display; segments b and c light on the display, giving a decimal readout of 1. The 0001 is also applied to the D/A converter. About 3.2 V from the counter is applied through the $150-k\Omega$ resistor to the input of the op amp. The voltage gain of the op amp is

$$A_{\nu} = \frac{R_f}{R_{in}} = \frac{47,000}{150,000} = 0.31$$

The gain is 0.31. The voltage gain times the input voltage equals the output voltage:

$$V_{out} = A_{v} \times V_{in} = 0.31 \times 3.2 = 1 \text{ V}$$

The output voltage of the D/A converter is -1 V. The 1 V is fed back to the comparator.

Now, with 2 V still applied to the input, the comparator checks A against B; input A is larger. The comparator applies a logical 1 to the AND gate. The AND gate passes the second clock pulse to the counter. The counter advances to 0010. The 0010 is decoded and reads out as a decimal 2 on the seven-segment display. The 0010 also is applied to the D/A converter. The D/A converter puts out about -2 V, which is fed back to the B input of the comparator.

The display now reads 2. The 2 V is still applied to input A of the comparator. The comparator checks A against B; B is just slightly larger. Output X of the comparator goes to logical 0. The AND gate is disabled. No clock pulses reach the counter. The count has stopped at 2 on the display. This is the voltage applied at the analog input.

The digital voltmeter in Fig. 14-12 is an experimental circuit. The circuit is included because it demonstrates the fundamentals of how a digital voltmeter works. It shows how SSI and MSI ICs can be used to build more complex

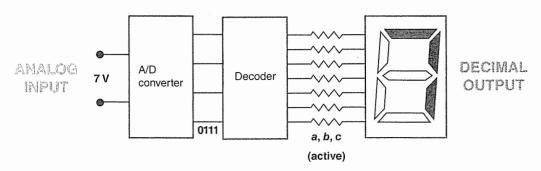


Fig. 14-11 Block diagram of an elementary digital voltmeter.

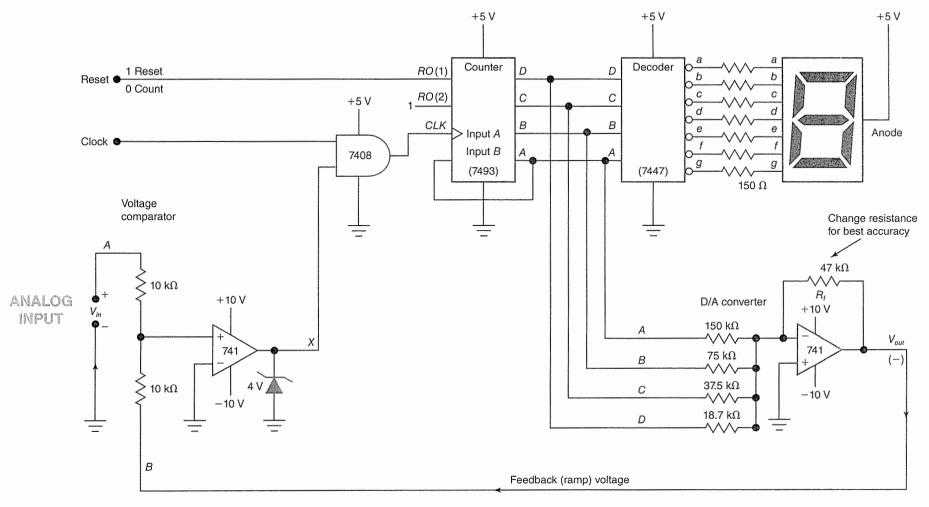


Fig. 14-12 Wiring diagram of an elementary digital voltmeter.

Hybrid electronic system

LSI digital voltmeter IC



Research Intersil ICL 7106 and ICL 7107 functions. It is a simple example of a *hybrid* electronic system containing both digital and analog devices.

Modern digital voltmeters and DMMs are based on LSI ICs. These specialized A/D converters are available from many manufacturers. Large-scale integration digital voltmeter chips include all the active devices on a single CMOS IC. Included are the A/D converter, seven-segment decoders, display drivers, and a

clock. The ICL7106 and ICL7107 3½-digit A/D converters are two examples of these complex devices. They will directly drive either LCD (7106 IC) or LED (7107 IC) 3½-digit displays. They feature a built-in clock, voltage references, accurate A/D converter, auto-zero, high input impedance, decoders, and direct display drivers for 3½-digit seven-segment displays. These chips can be used in digital voltmeters or digital thermometers.

Self-Test

Answer the following questions.

- 35. One application for an A/D converter is in a(n) _____.
- 36. Refer to Fig. 14-12. The elementary digital voltmeter is considered a _____ (digital, hybrid) system because it contains both digital and analog ICs.
- 37. Refer to Fig. 14-12. With the counter *reset* to 0000, the feedback (ramp) voltage will be about _______ V.
- 38. Refer to Fig. 14-12. If the analog input voltage is 3.5 V and the counter is reset, how many clock pulses reach the 7493 IC before the counter stops?
- 39. Refer to Fig. 14-12. If the analog input voltage is 4.6 V, the display will read

- _____ V after the reset/count sequence.
- 40. Refer to Fig. 14-12. The op amp on the right is wired as a(n) _____ while the operational amplifier at the left functions as a voltage comparator.
- 41. Refer to Fig. 14-12. If the analog input voltage is 8.5 V, the display will read ______ V after the reset/count sequence.
- 42. Refer to Fig. 14-12. When input *B* of the voltage comparator becomes _____ (greater than, less than) the input voltage at *A*, the output goes LOW and the AND gate _____ (does not pass, passes) the clock pulses to the counter.



14-8 Other A/O Converters

In Sec. 14-5 we studied the counter-ramp A/D converter. Several other types of A/D converters are also used; in this section we shall discuss two other types of converters.

A ramp A/D converter is shown in Fig. 14-13. This A/D converter works very much like the counter-ramp A/D converter in Fig. 14-8. The ramp generator at the left in Fig. 14-13 is the only new subsystem. The ramp generator produces a sawtooth waveform, which is shown in Fig. 14-14(a).

Suppose 3 V is applied to the analog voltage input of the A/D converter in Fig. 14-13. This situation is diagrammed in Fig. 14-14(a). The

ramp voltage starts to increase but is still lower than input A of the comparator. The comparator output is at a logical 1. This 1 enables the AND gate so that a clock pulse can pass through. In Fig. 14-14(a) the diagram shows three clock pulses getting through the AND gate before the ramp voltage gets larger than the input voltage. At point Y in Fig. 14-14(a), the comparator output goes to a logical 0. The AND gate is disabled. The counter stops counting at binary 0011. The binary 0011 means 3 V is applied at the input.

Figure 14-14(b) gives another example. The input voltage to the ramp-type A/D converter is 6 V in this situation. The ramp voltage begins to increase from left to right. The comparator

Ramp A/D converter

Ramp generator

Sawtooth waveform

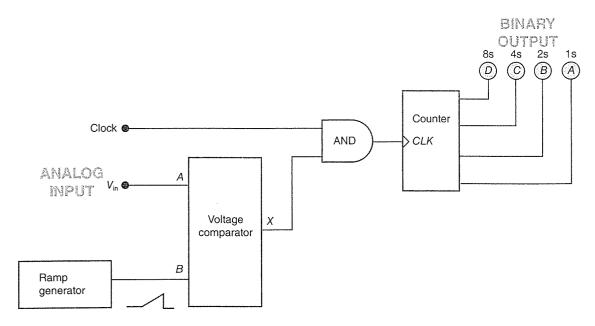


Fig. 14-13 Block diagram of a ramp-type A/O converter.

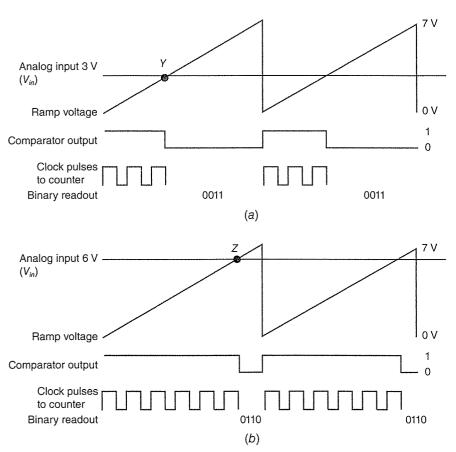


Fig. 14-14 Ramp-type A/D converter waveforms (a) With 3 V applied. (b) With 6 V applied.

Ramp-type A/D converter

output is at a logical 1 because input A is larger than the ramp-generator voltage at input B. The counter continues to advance. At point Z on the ramp voltage, the ramp-generator voltage is larger than V_{in} . At this point the comparator output goes to a logical 0. This 0 disables the AND gate. The clock pulses no longer reach the counter. The counter is stopped at binary 0110. The binary 0110 represents the 6-V analog input.

The difficulty with ramp-type A/D converters is the long time it takes to count up to higher voltages. For instance, if the binary output were eight binary places, the counter might have to count up to 255. To eliminate this slow conversion time, we use a different type of A/D converter. A converter that cuts down on conversion time is a *successive-approximation A/D converter*.

A block diagram of a successive-approximation A/D converter is shown in Fig. 14-15. The converter consists of a voltage comparator, a D/A converter, and a new logic block. The new logic block is called the successive-approximation logic section.

Suppose we apply 7 V to the analog input. The successive-approximation A/D converter first makes a "guess" at the analog input voltage. This guess is made by setting the MSB to 1. This is shown in block 1, Fig. 14-16. This job is performed by the successiveapproximation logic unit. The result (1000) is fed back to the comparator through the D/A converter. The comparator answers the question in block 2, Fig. 14-16, Is 1000 high or low compared with the input voltage? In this case the answer is "high." The successiveapproximation logic then performs the task in block 3. The 8s place is cleared to 0, and the 4s place is set to 1. The result (0100) is sent back to the comparator unit through the D/A converter. The comparator next answers the question in block 4, Is 0100 high or low compared with the input voltage? The answer is "low." The successive-approximation logic then performs the task in block 5. The 2s place is set to 1. The result (0110) is sent back to the comparator. The comparator answers the question in block 6, Is 0110 high or low compared with the input voltage? The answer

Successiveapproximation A/D converter

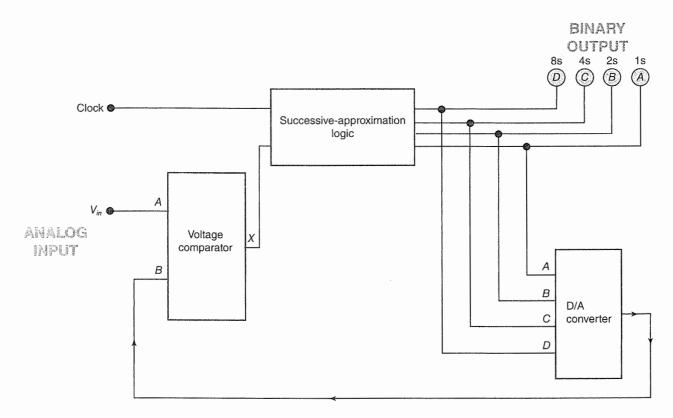


Fig. 14-15 Block diagram of a successive-approximation A/D converter.

is "low." The successive-approximation logic then performs the task in block 7. The 1s place is set to 1. The final result is binary 0111. This stands for the 7 V applied at the input of the A/D converter.

Notice in Fig. 14-16 that the items in the blocks are performed by the successive-approximation logic unit. The questions are answered by the comparator. Also notice

that the task performed by the successive-approximation logic depends upon whether the answer to the previous question is "low" or "high" (see blocks 3 and 5).

The advantage of the successive-approximation A/D converter is that it takes fewer guesses to get the answer. The *digitizing* process is thus faster. The successive-approximation A/D converter is very widely used.

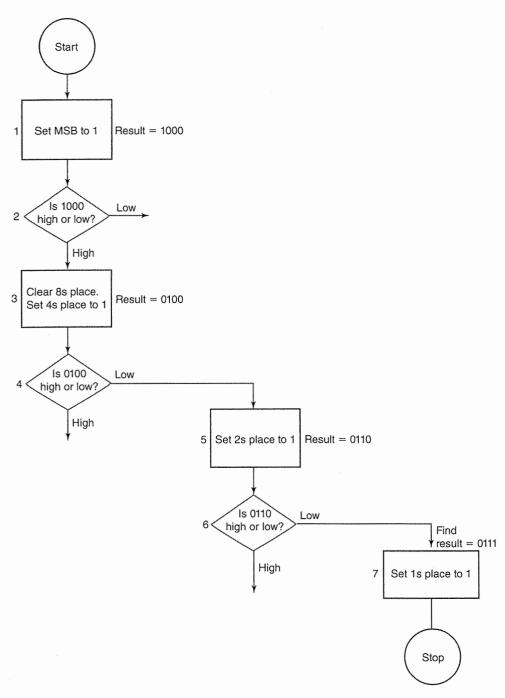



Fig. 14-16 Flowcharting the operation of the successive-approximation A/D convertor.

Flowcharting

-W- Self-Test

Answer the following questions.

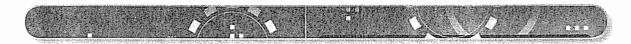- 43. List three types of A/D converter circuits.
- 44. The counter-ramp A/D converter uses a D/A converter to generate the ramp voltage fed back to the comparator, whereas the ramp type uses a(n) ______ to do this job.
- 45. The successive-approximation A/D converter is ______ (faster, slower) than ramp-type units.
- 46. Refer to Fig. 14-13. The ramp generator produces a _____ (sawtooth, square) waveform.
- 47. Refer to Fig. 14-14. If the input voltage (V_{in}) is 2 V and the ramp voltage is 0 V, the output of the voltage comparator is _____ (HIGH, LOW) and the AND gate allows clock pulses to pass to the counter.
- 48. Refer to Fig. 14-15. When starting a new conversion, the ______ first sets the MSB to 1 and the voltage comparator checks to see if the input voltage (V_{in}) is higher than the feedback voltage at B.



A/D converter specifications

Resolution

iconocian

μP-type A/D converters

14-9 A/D Converter Specifications

Manufacturers produce a wide variety of A/D converters. One recent publication lists over 300 different A/D converters fabricated by many manufacturers.

Some of the more common specifications of A/D converters are detailed below.

Type of Output

Generally, A/D converters are classified as having either binary or decimal outputs. Analog-to-digital converters with decimal outputs are commonly used as digital voltmeters and used in digital panel meters and DMMs.

Analog-to-digital converters with binary outputs have from 4 to 16 outputs. Analog-to-digital converters with binary outputs are common input devices to microprocessor-based systems. The latter are sometimes referred to as μP -type A/D converters.

Microcontroller inputs are commonly digital in nature. Many input sensors used with microcontrollers are analog in nature. A traditional A/D converter can be used to interface between analog sensors and digital microcontroller inputs.

Traditional A/D converters are sometimes replaced with simpler circuits when using low-cost microcontrollers. Many of these feature the

use of *RC* circuits (resistive/capacitive circuits) where the time of charging (or discharging) a capacitor through a resistance is measured by the microcontroller.

Resolution

The resolution of an A/D converter is given as the number of bits at the output for a binary-type unit. For decimal-output A/D converters (used in DMMs), the resolution is given as the number of digits in the readout (such as 3½ or 4½). Typical A/D converters with binary outputs have resolutions of 4, 6, 8, 10, 12, 14, and 16 bits. The errors that occur due to the use of discrete binary steps to represent a continuous analog voltage are called quantizing errors.

A 16-bit A/D converter has much finer resolution than a 4-bit unit because it divides the input or reference voltage into smaller discrete steps. For instance, each step in a 4-bit A/D converter would be one-fifteenth $(2^4 - 1 = 15)$ of the input range. This would be a resolution of 6.7 percent $(1/15 \times 100 = 6.7 \text{ percent})$. An 8-bit A/D converter has finer increments. An 8-bit unit has 255 $(2^8 - 1 = 255)$ discrete steps. This provides a resolution of 0.39 percent $(1/255 \times 100 = 0.39 \text{ percent})$. The 8-bit unit has better resolution than the 4-bit A/D converter. The resolution of a 16-bit converter is 0.0015 percent.

Accuracy

The resolution of an A/D converter can be thought of as the inherent "digital" error due to the discrete steps available at the output of the IC. Another source of error in an A/D converter might be an analog component, such as the comparator. Other errors might be introduced by the resistor network. The overall precision of an A/D converter is called the *accuracy* of the A/D converter IC.

The accuracies of typical A/D converter ICs with binary outputs range from $\pm \frac{1}{2}$ LSB to \pm 2 LSB. Those with decimal outputs might range from 0.01 to 0.05 percent accuracy.

Conversion Time

The conversion time is another important specification of an A/D converter. It is the time it takes for the IC to convert the analog input

voltage to binary (or decimal) data at the outputs. Typical conversion times range from 0.05 to 100,000 µs for A/D converter ICs with binary outputs. Conversion times for A/D converters with decimal outputs are somewhat longer and might typically be 200 to 400 ms.

Decimal-output A/D converters

Other Specifications

Four other common characteristics given for A/D converters are the power supply voltage, output logic levels, input voltage, and maximum power dissipation. Power supply voltages are commonly +5 V. However, some A/D converter ICs operate on voltages from +5 to +15 V. The output logic levels are either TTL, CMOS, or tristate. The input voltage range is commonly 5 V. Maximum power dissipation for an A/D converter IC might be in a range from about 15 to 3000 mW.

Accuracy

Conversion time

-/₩- Self-Test

Supply the missing word or number in each statement.

- 49. An A/D converter with binary outputs is sometimes referred to as a _____ (meter, μP)-type unit.
- 50. The _____ of an A/D converter is given as the number of bits at the output of a binary-type unit.
- 51. An 8-bit A/D converter has greater resolution than a _____ (4, 12)-bit chip.
- 52. A typical conversion time for an A/D converter might be about ______ (110 mus, 1 s).

- 53. A typical A/D converter might have a maximum power dissipation of about _____ (850 mW, 10 μW).
- 54. The conversion time for meter-type A/D converters is _____ (longer, shorter) than for μ P-type units.
- 55. Microcontrollers may collect analog sensor information using a traditional A/D converter or by using lower-cost circuits commonly based on RC timing circuits. (T or F)


14-10 An A/D Converter IC

A commercial A/D converter IC is featured in this section. Figure 14-17(a) shows the pin diagram for an ADC0804 8-bit A/D converter IC. The table in Fig. 14-17(b) lists the name and function of each pin on the ADC0804 IC.

The ADC0804 A/D converter was designed to interface directly with older 8080, 8085, or Z80 microprocessors. Some pin labels on the

ADC0804 IC correspond to pins on popular microprocessors. For instance, the ADC0804 uses \overline{RD} , \overline{WR} , and \overline{INTR} as pin labels, which correspond to the RD, WR, and INTR pins on the older 8085 microprocessor. The ADC0804 can also be interfaced with other older 8-bit microprocessors such as the 6800 and 6502. The \overline{CS} control input to the ADC0804 A/D converter receives its signal (chip select) from the microprocessor address-decoding circuitry.

ADCO804 8-bit A/D converter IC

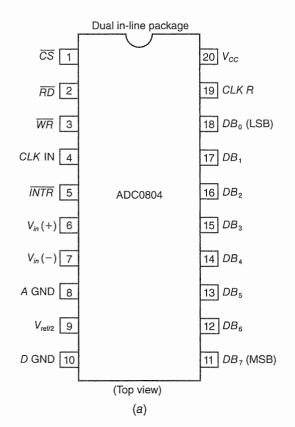

ADC0804 A/D Converter IC

Pin No.	Symbol	Input/Output or Power	Description
1	<u>cs</u>	Input	Chip select line from μP-control
2	RD	Input	Read line from µP-control
3	WR	Input	Write line from μP-control
4	CLK IN	Input	Clock
5	INTR	Output	Interrupt line goes to µP interrupt input
6	V _{in} (+)	Input	Analog voltage (positive input)
7	V _{in} (-)	Input	Analog voltage (negative input)
8	A GND	Power	Analog ground
9	V _{ref/2}	Input	Alternate voltage reference (+)
10	D GND	Power	Digital ground
11	DB ₇	Output	MSB data output
12	DB ₆	Output	Data output
13	DB₅	Output	Data output
14	DB₄	Output	Data output
15	DB ₃	Output	Data output
16	DB ₂	Output	Data output
17	DB ₁	Output	Data output
18	DB_0	Output	LSB data output
19	CLK R	Input	Connect external resistor for clock
20	V _{cc} (or ref)	Power	Positive of 5-V power supply and primary reference voltage

ADCO804 A/D converter IC

(b)

Fig. 14-17 ADCOBO4 A/D converter IC. (a) Pin diagram. (b) Pin labels and functions.

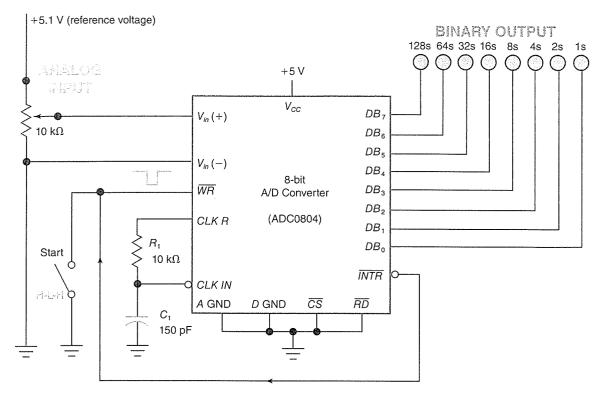


Fig. 14-18 Wiring diagram for a test circuit using the ADCO804 CMOS A/D converter IC.

Testing the AOCO8O4 A/D converter IC

Successiveapproximation A/D converter

The ADC0804 is a CMOS 8-bit successive-approximation A/D converter. It has three-state outputs so that it can interface directly with a microprocessor-based system data bus. The ADC0804 has binary outputs and features a short conversion time of only 100 µs. Its inputs and outputs are both MOS- and TTL-compatible. It has an on-chip clock generator. The on-chip generator does need two external components (resistor and capacitor) to operate. The ADC0804 IC operates on a standard +5-V dc power supply and can encode input analog voltages ranging from 0 to 5 V.

The ADC0804 A/D converter IC can be tested using the circuit shown in Fig. 14-18. The function of the circuit is to encode the difference in voltage between $V_{in}(+)$ and $V_{in}(-)$ compared to the reference voltage (5.12 V in this example) to a corresponding binary value. The resolution of the ADC0804 IC is 8 bits or 0.39 percent. This means that for each 0.02-V (5.1 V \times 0.39 percent = 0.02 V) increase in voltage at the analog inputs, the binary count increases by 1.

The "start switch" in Fig. 14-18 is first closed and then opened to start this free-running A/D converter. It is "free-running" because it continuously converts the analog input to digital outputs. The start switch should be left open

once the A/D converter is operating. The \overline{WR} input can be thought of as a clock input with the interrupt output (\overline{INTR}) pulsing the \overline{WR} input at the end of each analog-to-digital conversion. A L-to-H transition of the signal at the \overline{WR} input starts the A/D converter process. When the conversion is finished, the binary display is updated and the \overline{INTR} output emits a negative pulse. The negative interrupt pulse is fed back to clock the \overline{WR} input, and it initiates another A/D conversion. The circuit in Fig. 14-18 will perform about 5,000 to 10,000 conversions per second. The conversion rate of the ADC0804 is high because it uses the successive-approximation technique in the conversion process.

The resistor (R_1) and capacitor (C_1) connected to the *CLK R* and *CLK IN* inputs to the ADC0804 IC in Fig. 14-18 cause the internal clock to operate. The data outputs (DB7–DB0) drive the LED binary displays. The data outputs are active HIGH three-state outputs.


What is the binary output in Fig. 14-18 if the analog input voltage is 1.0 V? Recall that each 0.02 V equals a single binary count. Dividing 1.0 V by 0.02 V equals 50 in decimal. Converting decimal 50 to binary equals 00110010₂. The output indicators will show binary 00110010 (LLHHLLHL).

-M- Self-Test

Supply the missing word in each statement.

- 56. The ADC0804 A/D converter is manufactured using _____ (CMOS, TTL) technology.
- 57. The ADC0804 IC is a _____ (meter, microprocessor)-type A/D converter.
- 58. The ADC0804 is an A/D converter with a resolution of ______.
- The ADC0804 IC's inputs and outputs meet both MOS and ______ voltagelevel specifications.
- 60. The conversion time for the ADC0804 IC is about ______ (100 μs, 400 ms).

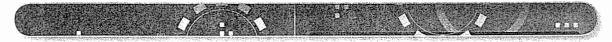- 61. Refer to Fig. 14-18. Components R_1 and C_1 are used by the ADC0804 IC's internal _____ (clock, comparator).
- 62. Refer to Fig. 14-18. If the analog input voltage is 2.0 V, the binary output is
- 63. Refer to Fig. 14-18. A(n) ______ (H-to-L, L-to-H) signal at the \overline{WR} input to the ADC0804 IC starts a new A/D conversion.
- 64. Refer to Fig. 14-18. What output terminal of the ADC0804 IC produces a negative pulse immediately after each A/D conversion?



14-11 Digital Light Meter

The A/D converter is the electronic device used to encode analog voltages to digital form. These analog voltages are often generated by transducers. For instance, light intensity may be converted to a variable resistance using a photocell.

A schematic diagram for a basic digital light meter is drawn in Fig. 14-19. The ADC0804 IC is wired as a free-running A/D converter as in the last section. The push-button switch is pressed only once to start the A/D converter. The analog input voltage is being measured across resistor R_2 . The photocell (R_3) is the light sensor or transducer in this circuit. As the light intensity increases, the resistance of the photocell (R_2) decreases. Decreasing the resistance of R_3 causes an increase in current through series resistances R_2 and R_3 . The increased current through R_2 causes a proportional increase in the voltage drop across the resistor. The voltage drop across R_2 is the analog input voltage to the A/D converter. An increase in the analog input voltage causes an increase in the reading at the binary outputs.

The *cadmium sulfide photocell* used in Fig. 14-19 is a variable resistor. As the intensity of the light striking the photocell increases, its resistance decreases. The photocell shown in

Fig. 14-19 might have a maximum resistance of more than $100 \text{ k}\Omega$ and a minimum of less than $1 \text{ k}\Omega$. The cadmium sulfide photocell is most sensitive in the green-to-yellow portion of the light spectrum. The photocell is also referred to as a photoresistor, CdS photocell, a photoresistive cell or a light-dependent resistor (LDR).

CdS photocells vary widely in their minimum and maximum resistances. If the substitute photocell has different resistance specifications, you can change the value of resistor R_2 in the light meter circuit (Fig. 14-19) to scale the binary output as desired.

A second digital light meter circuit is drawn in Fig. 14-20. This light meter indicates the relative brightness of the light striking the photocell in decimal (0 to 9). The new light meter is similar to the circuit in Fig. 14-19. The new light meter has a clock added to the circuit. The clock consists of a 555 timer IC, two resistors, and a capacitor wired as an astable MV. The clock generates a TTL output with a frequency of about 1 Hz. This means the analog input voltage is only converted into digital form one time per second. The very low conversion rate keeps the output from "jittering" between two readings on the seven-segment LED display.

The 7447A IC decodes the four MSBs (DB_7 , DB_6 , DB_5 , and DB_4) from the output of the

Photoresistor Photoresistive cell Digital light meter

Transducer



Search for photocells and LORs.

Cadmium sulfide photocell

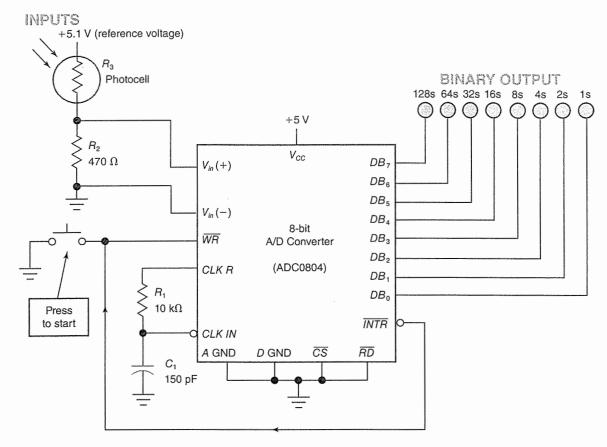


Fig. 14-19 Wiring diagram for a digital light meter using binary outputs.

ADC0804 A/D converter. The 7447A IC also drives the segments on the seven-segment LED display. The seven $150-\Omega$ resistors between the 7447A IC and seven-segment LED display limit the current through an "on" segment to a safe level.

As in the previous circuit (Fig. 14-19), the output of the new light meter may have to be

scaled so that low light reads 0 and high light intensity reads 9 on the seven-segment LED display. The value of resistor R_2 can be changed to scale the output. If R_2 is substituted with a lower-value resistor, the decimal output will read lower for the same light intensity. However, if the resistance value of R_2 is increased, the output will read higher.

-M- Self-Test

Supply the missing word or number in each statement.

- 65. Refer to Fig. 14-19. As the light intensity striking the surface of the photocell increases, the binary value at the output of the light meter circuit _____ (decreases, increases).
- 66. Refer to Fig. 14-19. As the light intensity striking the surface of the photocell increases, the resistance of the photocell _____ (decreases, increases).
- 67. Refer to Fig. 14-20. If current through series resistances R_2 and R_3 increases, the analog input voltage to the A/D converter _____ (decreases, increases).
- 68. Refer to Fig. 14-20. The conversion rate of the ADC0804 IC in this digital light meter circuit is about _______ (1, 400 A/D conversion(s) per second.
- 69. Refer to Fig. 14-20. Substituting R_2 with a resistor of a lower ohmic value would cause the output display to read

Digital light meter circuit

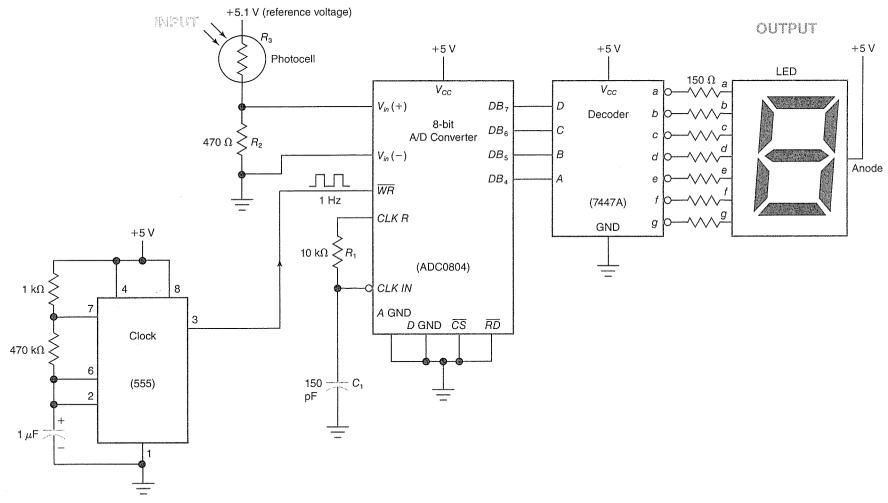


Fig. 14-20 Wiring diagram for a digital light meter circuit using a decimal display.

_____ (higher, lower) for the same light intensity.

- 70. Refer to Fig. 14-20. The part labeled R_3 in the light meter circuit is a _____ (transducer, transformer) that converts light intensity into a variable resistance.
- 71. Refer to Fig. 14-20. The component labeled R_3 is a cadmium ______.
- 72. The conversion time of the A/D converter is much less frequent in the digital light meter circuit (Fig. 14-20) than in the light meter in Fig. 14-19. (T or F)
- 73. Another name used for a CdS photocell is a light-dependent resistor (LDR). (T or F)



14-12 Digitizing Temperature

The A/D converter could be used to convert an analog temperature to a digital quantity. A digital thermometer is one example of the use of an A/D converter in digitizing temperature. Devices other than an A/D converter might also be used to convert an analog temperature to a digital form.

As a general definition, to *digitize* means to convert an analog measurement into digital units or digital pulses. The A/D converter is one example of a *digitizer*. In this section the digitizer will be an elementary Schmitt-trigger inverter.

A simple circuit for digitizing temperature is shown in Fig. 14-21. The digitizing device is a simple Schmitt-trigger inverter (74LS14 IC). A *thermistor* is the temperature transducer. A

thermistor is a *temperature-sensitive resistor*. As the temperature of the thermistor increases, its resistance will decrease. Thermistors are said to have a *negative temperature coefficent*, while most metals (like copper) have a positive temperature coefficent.

Recall that the switching threshold of the 74LS14 Schmitt-trigger inverter is about 1.7 V when the input voltage is increasing. Because of hysteresis, the switching threshold of the Schmitt-trigger inverter is lower or about 1 V when the input voltage is decreasing.

As the temperature of the thermistor in Fig. 14-21 increases, its resistance will decrease. This will cause the voltage at the input of the Schmitt-trigger inverter to increase (see voltmeter). When the temperature increases the voltage at the input of the inverter will finally exceed about +1.7 V and the output of the

Digitize

Thermistor

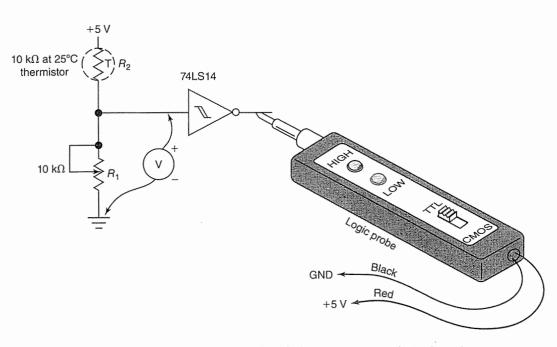


Fig. 14-21 Using a thermistor to sense temperature and a Schmitt-trigger inverter to digitize the analog input.

inverter will snap from HIGH to LOW as indicated on the logic probe.

Furthermore, as the temperature of the thermistor in Fig. 14-21 decreases its resistance will increase. This causes the voltage at the input of the inverter to decrease (see voltmeter in Fig. 14-21). When the temperature decreases below the threshold voltage of about +1 V, the output of the Schmitt-trigger inverter will snap from LOW to HIGH, as indicated on the logic probe. The potentiometer shown in Fig. 14-21 allows the user some adjustment as to what temperatures the digitizer circuit triggers to HIGH or to LOW. In other words, potentiometer R_i is used for calibration.

In the example in Fig. 14-21, it is said that we have digitized the temperature. In this example digitizing takes the form of generating either a HIGH or LOW. This example is like the sensing function of a thermostat. The I/O pins of a microcontroller (like the BASIC Stamp) can digitize analog data much like the circuit in Fig. 14-21 when I/O pins are used as inputs. After sensing the HIGH or LOW input, a microcontroller can then be programmed to respond to the higher or lower temperature.

A thermistor, such as the one used in Fig. 14-21, is constructed by sintering combinations of metallic oxides into different shapes. A common shape for a thermistor is a small teardrop to which leads are attached. The metallic oxides commonly used in manufacturing thermistors include those of titanium, iron, copper, cobalt, and nickel. A common thermistor you may use in lab will have a resistance value of 10 k Ω at a temperature of 25°C. This same thermistor might have a resistance of 28 k Ω at 0°C and 1 k Ω at 100°C.

The advantage of the thermistor is that it is simple, inexpensive, and easy to interface. One disadvantage of the thermistor is that it has a nonlinear temperature-vs.-resistance characteristic. This nonlinear characteristic makes the thermistor difficult to use as the thermal sensor in a thermometer application.

Many more expensive *linear thermal sensors* are available in IC form that can be used as sensors in thermometers. These include the threeterminal LM34 and LM35 temperature sensors from National Semiconductor and the twoterminal AD592 precision IC temperature transducer from Analog Devices. More complex ICs like the 8-pin DIP DS1620 digital thermometer and thermostat IC include more functions, including sensing temperature, converting the temperature into a 9-bit word, a three-wire serial interface, and programmable thermostatic controls. The DS1620 is especially useful when used in conjuction with a microcontroller (such as the BASIC Stamp). The DS1620 is manufactured by Dallas Semiconductor.

Monlinear

Linear thermal sensors




Connection

Research the term sintering.

Answer the following questions.

- 74. Refer to Fig. 14-21. The device that can be classified as a temperature transducer __ (Schmitt-trigger inverter, thermistor).
- 75. Refer to Fig. 14-21. The device that can be classified as the digitizer is the (Schmitt-trigger inverter, thermistor).
- 76. Refer to Fig. 14-21. Potentiometer R_1 can be used to calibrate the digitizer circuit. (T or F)

77.	Refer to Fig. 14-21. If the temperature
	of the thermistor is greatly increased,
	its resistance (decreases,
	increases, stays the same) and the volt-
	age at the input to the inverter
	(decreases, increases). This increasing
	thermistor temperature causes the output
	of the Schmitt-trigger inverter to snap
	from(HIGH to LOW, LOW to
	HIGH).

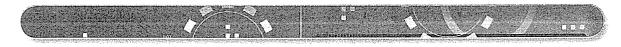

Chapter 14 Summary and Review



Summary

- Special interface encoders and decoders are used between analog and digital devices. These are called D/A converters and A/D converters.
- 2. A D/A converter consists of a resistor network and a summing amplifier.
- 3. Operational amplifiers are used in D/A converters and voltage comparators. Gain can be easily set with external resistors on the op amp.
- 4. Several different resistor networks are used for weighting the binary input to a D/A converter.
- 5. Common A/D converters are the counter-ramp, rampgenerator, and successive-approximation types.
- A voltage comparator compares two voltages and determines which is larger. An operational amplifier is the heart of the comparator.
- Common specifications used for A/D converters include such characteristics as type of output, resolution, accuracy, conversion time, power supply

An

- voltage, output logic levels, input voltage, and power dissipation.
- 8. The ADC0804 IC is a CMOS 8-bit A/D converter. It features fast conversion times, microprocessor compatibility, three-state outputs, TTL level inputs and outputs, and an on-chip clock.
- 9. A photocell, or light-dependent resistor (LDR), can be used as a transducer to drive an A/D converter in a digital light meter circuit.
- A thermistor (temperature-sensitive resistor) can be used as temperature transducer. The thermistor has a nonlinear temperature-vs.-resistance characteristic.
- 11. A Schmitt-trigger device can be used as a very elementary digitizer.
- 12. An A/D converter is at the heart of a digital voltmeter. Most commercial digital voltmeters and DMMs use complex meter-type A/D converter LSI ICs.

Chapter Review Questions

swer	the following questions.		of (R_f, R_{in}) by the value of
14-2.	An A/D converter is a special type of (decoder, encoder). A D/A converter is a(n) (decoder, encoder). The (A/D, D/A) converter digitizes analog information.	14-8.	Draw a symbol for an operational amplifier. Label the inverting input with a minus sign and the noninverting input with a plus sign. Label the output. Label the $+10\text{-V}$ and -10-V power supply connections.
14-4.	The (A/D, D/A) converter translates from binary to an analog voltage.		Refer to Fig. 14-4. What is the gain (A_v) of the op amp in this diagram if $R_{in} = 1 \text{ k}\Omega$ and $R_f = 20 \text{ k}\Omega$. Refer to Fig. 14-4. With the input voltage at
	A D/A converter consists of a(n)network and a summing		+½ V, the output voltage is (+, -)5 V. This is because we are using the (inverting, noninverting) input of the op amp.
14-6.	The term "operational amplifier" is frequently shortened to	14-11.	Refer to Fig. 14-5. What is the voltage gain of
14-7.	The voltage gain of the operational amplifier in Fig. 14-3(<i>b</i>) is determined by dividing the value		the op amp in this circuit with only switch A at logical 1?

Chapter Review Questions...continued

	en man come est	caratex	
sistance	Fig. 14-5. What is the combined re- of parallel resistors R_1 and R_2 if both	14-27.	Conversion times are somewhat longer for (meter, microprocessor)-type
	s A and B are at logical 1?		A/D converters.
14-13. Refer to	Fig. 14-5. What is the gain (A_{ν}) of the	14-28.	The ADC0804 (Fig. 14-17) has
op amp	with switches A and B at logical 1?		(binary, decimal) outputs.
(Use the	e resistance value from question 14-12.)	14-29.	The A/D converter wired in Fig. 14-18 performs
14-14. Refer to	Fig. 14-5. What is the output voltage		about (3, 5,000 to 10,000) A/D
when bi	nary 0011 is applied to the D/A con-		conversions per second.
verter?	(Use the A_{ν} from question 14-14.)	14-30.	Refer to Fig. 14-18. If the analog input voltage
14-15. The arra	angement of resistors in Fig. 14-6 is		is 3.0 V, the binary output is
called th	neladder network.	14-31.	Refer to Fig. 14-20. Decreasing the light inten-
14-16. A HIGH	H, or logical 1, from a TTL device is		sity striking R_3 causes the resistance of the pho-
about _	(0, 3.75, 8.5) V.		tocell to (decrease, increase).
14-17. The	(A/D, D/A) converter is	14-32.	Refer to Fig. 14-20. Decreasing the light inten-
the mor	e complicated electronic system.		sity striking the photocell causes the decimal
14-18. Refer to	Fig. 14-8. If point X is at a logical		output to (decrease, increase).
Market Control of the	(0, 1), the counter advances	14-33.	Refer to Fig. 14-20. If current through series
one cou	nt as a pulse comes from the clock.		resistances R_2 and R_3 decreases, the analog inpu
14-19. Refer to	Fig. 14-8. If input B of the comparator		voltage to the A/D converter
has a hi	gher voltage than input A, the AND gate		(decreases, increases).
is	(disabled, enabled).	14-34.	Thermistors can be used as temperature trans-
14-20. The prin	mary component in a voltage comparator		ducers but have a nonlinear temperature-vs
is a(n) _	(counter, op amp).		resistance characteristic, which makes them
14-21. Refer to	Fig. 14-12. This digital voltmeter uses		difficult to use as a thermal sensor in a ther-
a	(counter-ramp, successive-		mometer. (T or F)
approxi	mation) A/D converter.	14-35.	Refer to Fig. 14-21. As the temperature of the
14-22. The	(ramp, successive-		thermistor decreases, the voltage at the input to
approxi	mation) A/D converter is faster at		the 74LS14 inverter (decreases
digitizir	ng information.		increases) due to the
14-23. Devices	s such as microphones, speakers, strain		(decreased, increased) resistance of the thermal
gauges,	photocells, temperature sensors, and po-		sensor R_2 .
tentiom	eters convert one form of energy to an-	14-36.	Refer to Fig. 14-21. As the temperature of
other ar	nd are generally called		the thermistor decreases greatly, the output
14-24. An A/D	converter with binary outputs might		of the Schmitt-trigger inverter will snap from
be class	sified as a (meter,		(HIGH to LOW, LOW to
micropi	rocessor)-type unit.		HIGH).
	Fig. 14-18. What is the resolution of	14-37.	Refer to Fig. 14-21. Potentiometer R_1 is used for
	C0804 A/D converter?		(digitizing, calibration) in this
	(8, 16)-bit A/D converter		simple A/D converter circuit.
has a lo	wer quantization error and is considered		
more "s	accurate"		

Critical Thinking Questions

- 14-1. Calculate the gain of the op-amp circuit in Fig. 14-4 if $R_{in}=1~{\rm k}\Omega$ and $R_{f}=5~{\rm k}\Omega$. Using the calculated gain, what is the output voltage (V_{out}) if $V_{in}=0.5~{\rm V}$?
- 14-2. Refer to Fig. 14-5.
 - a. What is the combined resistance of parallel resistors R_2 and R_3 if both switches B and C are at logical 1?
 - b. Using the calculated resistance, what is the gain (A_{ν}) of the op amp with switches B and C at a logical 1?
 - c. What is the output voltage when binary 0110 is applied to the inputs of the D/A converter (use calculated A_)?
- 14-3. Compare Tables 14-1 and 14-2. Explain the difference between the data in the two tables.
- 14-4. List the four sections of a counter-ramp A/D converter circuit.
- 14-5. List the four sections of a ramp-type A/D converter circuit.
- 14-6. Compare the D/A converter resistor networks in Figs. 14-5 and 14-6. Why would the R-2R ladder resistor network in Fig. 14-6 be easier to expand from four to eight binary inputs?

- 14-7. Refer to Fig. 14-8. What would be the *resolution* of this A/D converter?
- 14-8. A digital voltmeter is one application of a(n) _____(A/D, D/A) converter.
- 14-9. At the option of your instructor, use circuit simulation software to (1) draw the 4-bit D/A converter using the R-2R ladder resistor network and op amp detailed in Fig. 14-22, (2) operate the 4-bit D/A converter circuit, and (3) show instructor your working D/A converter.
- 14-10. At the option of your instructor, use circuit simulation software to (1) draw a 5-bit D/A converter using the R-2R ladder resistor network and op amp something like the unit in Fig. 14-22, (2) operate the 5-bit D/A converter circuit, and (3) show the instructor your working 5-bit D/A converter.
- 14-11. At the option of your instructor, use circuit simulation software to (1) draw the generic 8-bit A/D converter circuit (with binary output) detailed in Fig. 14-23,(2) operate the 8-bit A/D converter circuit, and (3) show the instructor your working A/D converter.

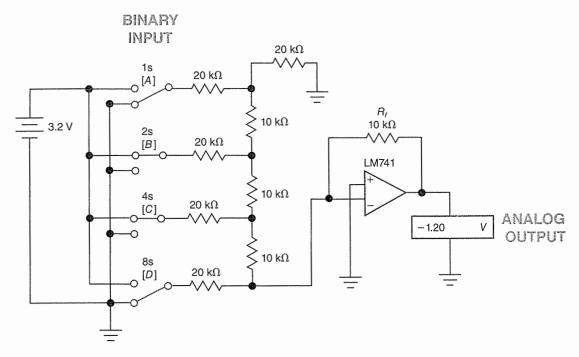


Fig. 14-22 Electronics Workbench simulation circuit of a D/A converter circuit using R-2R resistor network and op amp (scaling amplifier).

Critical Thinking Questions...continued

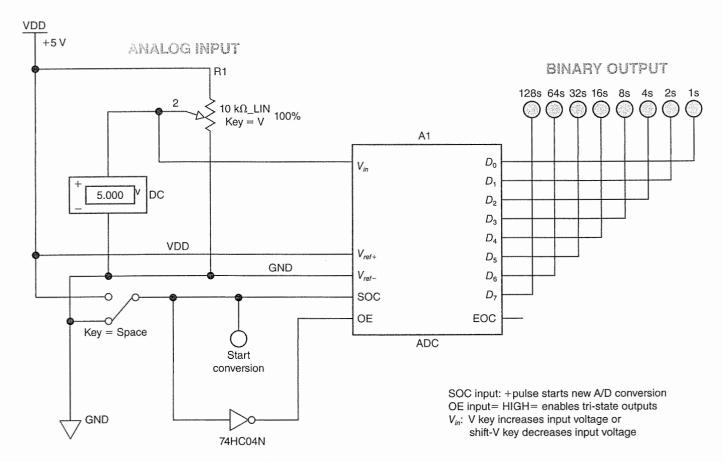


Fig. 14-23 A/D converter circuit with 8-bit binary readout.



Answers to Self-Tests

- 1. analog-to-digital converter (A/D converter)
- 2. digital-to-analog converter (D/A converter)
- 3. resistor, summing (scaling)
- 4. operational amplifier
- 5. 1.4
- 6. 3.0
- 7. 0.2
- 8. feedback
- 9. input
- 10. $A_{y} = 20$
- 11. $V_o = -4 \text{ V}$
- 12. $A_{\nu} = 4$
- 13. $V_o = -4 \text{ V}$
- 14. $A_{\nu} = 0.266$
- 15. $V_{o} = -0.8 \text{ V}$

- 16. 1. low accuracy
 - 2. a large range of resistor values needed
- 17. $A_{y} = 0.2$
- 18. $V_{out} = -0.6$
- 19. ladder (R-2R ladder)
- 20. 1
- 21. A
- 22. 2.75
- 23. 0.25
- 24. analog, digital (binary)
- 25. 0101
- 26. HIGH, pass through
- 27. counter-ramp
- 28. comparator
- 29. voltages


- 30. AND, LOW
- 31. dc voltages
- 32. op amp
- 33. HIGH, LOW
- 34. zener diode
- 35. digital voltmeter
- 36. hybrid
- 37. 0
- 38. four
- 39. 5
- 40. D/A converter
- 41. 9
- 42. greater than, does not pass
- 43. 1. counter-ramp
 - 2. ramp
 - 3. successive-approximation
- 44. ramp generator
- 45. faster
- 46. sawtooth
- 47. HIGH
- 48. successive-approximation logic
- 49. μP (microprocessor)
- 50. resolution
- 51. 4
- 52. 110 μs

- 53. 850 mW
- 54. longer
- 55. T
- 56. CMOS
- 57. microprocessor
- 58. 8 bits (0.39 percent)
- 59. TTL
- 60. $100 \mu s$
- 61. clock
- 62. 01100100, (decimal 100)
- 63. L-to-H
- 64. *ĪNTR*
- 65. increases
- 66. decreases
- 67. increases
- 68. 1
- 69. lower
- 70. transducer
- 71. sulfide photocell
- 72. T
- 73. T
- 74. thermistor
- 75. Schmitt-trigger inverter
- 76. T
- 77. decreases, increases, HIGH to LOW



Appendix A

Solder and the Soldering Process

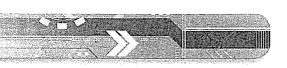

From a Simple Task to a Fine Art

Soldering is the process of joining two metals together by the use of a low-temperature melting alloy. Soldering is one of the oldest-known joining techniques, first developed by the Egyptians in making such weapons as spears and swords. Since then it has evolved into what is now used in the manufacturing of electronic assemblies. Soldering is far from the simple task it once was; it is now a fine art, one that requires care, experience, and a thorough knowledge of the fundamentals. With the advent of lead-free solder, even more care is needed to achieve good results and high reliability. The importance of having high standards of workmanship cannot be overemphasized. Faulty solder joints remain a cause of equipment failure, and because of that, soldering is a critical skill.

The material contained in this appendix is designed to provide the student with both the fundamental knowledge and the practical skills needed to perform many of the high-reliability soldering operations encountered in today's electronics. Covered are the fundamentals of the soldering process, the proper selection of irons, tips, and materials and the use of the soldering station. Wave soldering and reflow soldering are techniques used in the manufacture of electronic equipment. This appendix focuses on rework soldering, which is usually a part of the repair process.

The key concept in this appendix is high-reliability soldering. Much of our present technology is vitally dependent on the reliability of countless, individual soldered connections. High-reliability soldering was developed in response to early failures with space equipment. Since then the concept and practice have spread to military and medical equipment. We have now come to expect it in everyday electronics as well.

The Advantages of Soldering

Soldering is the process of connecting two pieces of metal together to form a reliable electrical path. Why solder them in the first place? The two pieces of metal could be put together with nuts and bolts, or some other kind of mechanical fastening. The disadvantages of these methods are threefold. First, the reliability of the connection

Adapted from material provided by PACE, Inc., Southern Pines, NC.

cannot be ensured because of vibration and shock. Second, because oxidation and corrosion are continually occurring on the metal surfaces, electric conductivity between the two surfaces would progressively decrease. A soldered connection does away with both these problems. There is no movement in the joint and no interfacing surfaces to oxidize. A continuous conductive path is formed, made possible by the characteristics of the solder itself. Third, during manufacturing, hundreds or thousands of joints can be realized at the same time.

The Nature of Solder

Solder used in electronics is a low-temperature melting alloy made by combining various metals in different proportions. The most common types of solder were made from tin and lead. When the proportions are equal, it is known as 50/50 solder—50 percent tin and 50 percent lead. Similarly, 60/40 solder consists of 60 percent tin and 40 percent lead. The percentages are usually marked on the various types of solder available; sometimes only the tin percentage is shown. The chemical symbol for tin is Sn; thus Sn 63 indicates a solder that contains 63 percent tin.

Pure lead (Pb) has a melting point of 327°C (621°F), and pure tin has a melting point of 232°C (450°F). When they are combined into a 60/40 solder, the melting point drops to 190°C (374°F)—lower than either of the two metals alone. Today, lead-free solders are mandated for many manufacturing and repair procedures. Table A-1 shows both lead and lead-free alloys. All the alloys listed are available in wire form for repair work, and two are available in paste form. Paste solders are used in the reflow process for manufacturing printed circuits with surface-mount devices. Paste solder is also sometimes used in rework.


As listed in Table A-1, 60/40 solder begins to melt at 183°C (351°F), but is not fully melted until the temperature reaches 190°C (374°F). Between these two temperatures, the solder exists in a plastic (semiliquid) state—some, but not all, of the solder has melted. The same is true for the tin-silver-copper alloy shown in Table A-1. Two of the solder alloys have no plastic range. They transition directly from solid to liquid (or from liquid to solid) as they are heated (or cooled). These are called *eutectic* alloys or *eutectic* solders.

Table A-1 Some Comi	non Lead and Lead-F	ree Solders
Alloy	Melting Temperature	Available In Paste Form
63% tin, 37% lead	361°F (183°C)	Yes
60% tin, 40% lead	361–374°F (183–190°C)*	No
96.5% tin, 3% silver, 0.5% copper	422-428°F (217-220°C)*	Yes
96.5% tin, 3.5% silver	430°F (221°C)	No

"This alloy has a plastic range between its liquid and solid transition temperatures.

When using solders with a plastic range, it is especially important to avoid vibration or movement of the joint during the cool-down period. When any movement happens, the joint tends to have a dull, grainy appearance. Such joints are unreliable and are rejected by careful workers and quality inspectors. However, lead-free solder joints are *inherently dull and grainy*, as shown in Fig. A-1. Thus, workers and inspectors must learn new visual inspection guidelines for lead-free soldering.

In some situations, it is difficult to maintain a stable joint during cooling, for example, when wave soldering is used with a moving conveyor line of circuit boards during the manufacturing process. In other cases, it may be necessary to use minimal heat to avoid damage to heat-sensitive components. In both these situations, eutectic solder is the preferred choice, since it changes from a liquid to a solid during cooling with no plastic range.

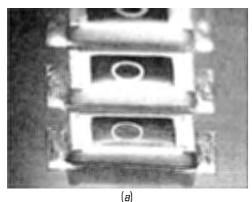

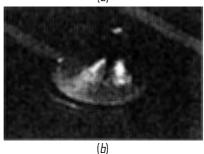


Fig. A-1 Appearance of (a) a lead alloy solder joint and (b) a lead-free joint.

The Wetting Action

To someone watching the soldering process for the first time, it looks as though the solder simply sticks the metals together like a hot-melt glue, but what actually happen is far different. A chemical reaction takes place when the hot solder comes into contact with the copper surface. The solder dissolves and penetrates the surface. The molecules of solder and copper blend together to form a new metal alloy, one that is part copper and part solder and that has characteristics all its own. This reaction is called *wetting* and forms the intermetallic bond between the solder and copper.

Proper wetting can occur only if the surface of the copper is free of contamination and from oxide films that form when the metal is exposed to air. Also, the solder and copper surfaces need to have reached the proper temperature. Even though the surface may look clean before soldering, there may still be a thin film of oxide covering it.

When applied to a contaminated surface, the solder acts like a drop of water on an oily surface because the oxide coating prevents the solder from coming into contact with the copper. No reaction takes place, and the solder can be easily scraped off. For a good solder bond, surface oxides must be removed during the soldering process.

The Role of Flux

Reliable solder connections can be accomplished only on clean surfaces. Some sort of cleaning process is essential in achieving successful soldered connections, but in most cases it is insufficient. This is due to the extremely rapid rate at which oxides form on the surfaces of heated metals, thus creating oxide films, which prevent proper soldering. To overcome these oxide films, it is necessary to utilize materials, called *fluxes*, which consist of natural or synthetic rosins and sometimes additives called *activators*.

It is the function of flux to remove surface oxides and keep them removed during the soldering operation. This is accomplished because the flux action is very corrosive at or near solder melt temperatures and accounts for the flux's ability to rapidly remove metal oxides. It is the fluxing action of removing oxides and carrying them away, as well as preventing the formation of new oxides, that allows the solder to form the desired intermetallic bond.

Flux must activate at a temperature lower than solder so that it can do its job prior to the solder flowing. It volatilizes very rapidly; thus it is mandatory that the flux be activated to flow onto the work surface and not simply be volatilized by the hot iron tip if it is to provide the full benefit of the fluxing action.

There are varieties of fluxes available for many applications. For example, in soldering sheet metal, acid fluxes

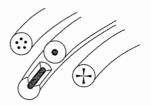


Fig. A-2 Flux-cored wire solders.

are used; silver brazing (which requires a much higher temperature for melting than that required by tin-lead alloys) uses a borax paste. Each flux removes oxides and, in many cases, serves additional purposes. The fluxes used in electronic hand soldering are the pure rosins; rosins combined with mild activators to accelerate the rosin's fluxing capability; low-residue, no-clean fluxes; or water-soluble fluxes. Acid fluxes or highly activated fluxes should *never* be used in electronic work. Various types of flux-cored solder are in common use. They provide a convenient way to apply and control the amount of flux used at the joint (see Fig. A-2).

Soldering Irons

In any kind of soldering, the primary requirement, beyond the solder itself, is heat. Heat can be applied in a number of ways—conductive (e.g., soldering iron, wave, or vapor phase), convective (hot air), or radiant (IR). Here, we are mainly concerned with the conductive method, which uses a soldering iron.

Soldering stations come in a variety of sizes and shapes but consist basically of three main elements: a resistance heating unit; a heater block, which acts as a heat reservoir; and the tip, or bit, for transferring heat to the work. The standard production station is a variable-temperature, closed-loop system with interchangeable tips and is made with ESD-safe plastics.

Controlling Heat at the Joint

Controlling tip temperature is not the real challenge in soldering; the real challenge is to control the heat cycle of the work—how fast the work gets hot, how hot it becomes, and how long it stays that way. This is affected by so many factors that, in reality, tip temperature is not the critical one.

The first factor that needs to be considered is the relative thermal mass of the area to be soldered. This mass may vary over a wide range. Consider a single land on a single-sided circuit board. There is relatively little mass, so the land heats up quickly. But on a double-sided board with plated-through holes, the mass is more than doubled. Multilayered boards may have an even greater mass, and

that's before the mass of the component lead is taken in to consideration. Lead mass may vary greatly, since some leads are much larger than others. Further, there may be terminals (e.g., turret or bifurcated) mounted on the board. Again, the thermal mass is increased, and will further increase as connecting wires are added.

Each connection to be soldered, then, has its own particular thermal mass. How this combined mass compares with the mass of the iron tip, the "relative" thermal mass, determines the time and temperature rise of the work. With a large work mass and a small iron tip, the temperature rise will be slow. With the situation reversed, using a large iron tip on a small work mass, the temperature rise of the work will be much more rapid—even though the temperature of the tip is the same.

Now consider the capacity of the iron itself and its ability to sustain a given flow of heat. Essentially, irons are instruments for generating and storing heat, and the reservoir is made up of both the heater block and the tip. The tip comes in various sizes and shapes; it's the pipeline for heat flowing into the work. For small work, a conical (pointed) tip is used, so that only a small flow of heat occurs. For large work, a large chisel tip is used, providing greater flow. Table A-2 shows some various tip styles and sizes.

The heat reservoir is replenished by the heating element, but when an iron with a large tip is used to heat massive work, the reservoir may lose heat faster than it can

Table A-2 Examples of Soldering Iron Tips				
Drawing	Size in Inches	Description		
	0.031	30° chisel		
	0.047	30° bent chisel extended		
MB	0.063	30° bent chisel		
	0.063	60° chisel		
	0.078	60° chisel		
	0.094	30° chisel		
DI II3	0.125	90° chisel extended		
	0.203	chisel		
	0.250	Single-sided chisel		

be replenished. Thus, the size of the reservoir becomes important: A large heating block can sustain a larger outflow longer than a small one. An iron's capacity can be increased by using a larger heating element, thereby increasing the wattage of the iron. These two factors, block size and wattage, are what determine the iron's recovery rate.

If a great deal of heat is needed at a particular connection, the correct temperature with the right size tip is required, as is an iron with a large enough capacity and an ability to recover fast enough. Relative thermal mass, then, is a major consideration for controlling the heat cycle of the work.

A second factor of importance is the surface condition of the area to be soldered. If any oxides or other contaminants cover the lands or leads, there will be a barrier to the flow of heat. Then even though the iron tip is the right size and has the correct temperature, it may not supply enough heat to the connection to melt the solder. In soldering, a cardinal rule is that a good solder connection cannot be created on a dirty surface. Before attempting to solder, the work should always be cleaned with an approved solvent to remove any grease or oil film from the surface. In some cases, pretinning may be required to enhance solderability and remove heavy oxidation of the surfaces prior to soldering.

A third factor to consider is *thermal linkage*—the area of contact between the soldering iron tip and the work. Figure A-3 shows a tip touching a round lead. The contact occurs only at the point indicated by the "+," so the linkage area is very small. The contact area can be greatly increased by applying wire solder to the point of contact between the tip and workpiece. This solder heat bridge drastically improves the thermal linkage and ensures rapid heat transfer into the work.

It should now be apparent that there are many more factors than just the temperature of the iron tip that affect how quickly any particular connection is going to heat up. In reality, soldering is a very complex control problem, with a number of variables to it, each influencing the other. And what makes it so critical is time. The general rule for high-reliability soldering on printed circuit boards is to apply heat for no more than 2 seconds from the time solder starts to melt. Applying heat for longer periods may cause damage to the component or board or both.

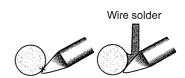


Fig. A-3 Increasing contact area for improved heat flow.

The soldering iron tip should be applied to the area of maximum thermal mass of the connection being made. This will permit the rapid thermal elevation of the parts being soldered. Molten solder always flows toward the heat source of a properly prepared connection.

For soldering and desoldering, a primary workpiece indicator is *heat rate recognition*—observing how fast heat flows into the connection. In practice, this means observing the rate at which solder melts, which should be within 1 to 2 seconds. This indicator encompasses all the variables involved in making a satisfactory solder connection with minimum heating effects, including the capacity of the iron and its tip temperature, the surface conditions, the thermal linkage between the tip and the workpiece, and the relative thermal masses involved.

If the iron tip is too large for the work, the heating rate may be too fast to be controlled. If the tip is too small, it may produce a "mush" kind of melt; the heating rate will be too slow, even though the temperature at the tip is the same. A general rule for preventing overheating is, "Get in and get out as fast as you can." That means using a heated iron you can react to—one giving a 1- to 2-second dwell time on the particular connection being soldered.

Selecting the Soldering Iron and Tip

A good all-around soldering station for electronic soldering is a variable-temperature, ESD-safe station, with a pencil-type iron and tips that are easily interchangeable, even when hot (see Fig. A-4). The soldering iron tip should always be fully inserted into the heating element and tightened. This will allow for maximum heat transfer from the heater to the tip.

The tip should be removed daily to prevent an oxidation scale from accumulating between the heating element and the tip. A bright, thin-tinned surface must be maintained on the tip's working surface to ensure proper heat transfer and to avoid contaminating the solder connection.

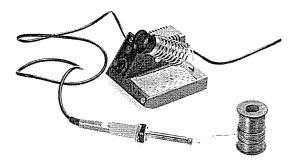


Fig. A-4 Pencil-type iron with interchangeable tips.

The plated tip is initially prepared by holding a piece of flux-cored solder to the face so that it will tin the surface when it reaches the lowest temperature at which solder will melt. Once the tip is up to operating temperature, it will usually be too hot for good tinning, because of the rapid oxidation at elevated temperatures. The hot tinned tip is maintained by wiping it lightly on a damp sponge to shock off the oxides. When the iron is not being used, the tip should be coated with a layer of solder.

Making the Solder Connection

The soldering iron tip should be applied to the area of maximum thermal mass of the connection being made. This will permit the rapid thermal elevation of the parts being soldered. Molten solder always flows toward the heat of a properly prepared connection.

When the solder connection is heated, a small amount of solder is applied to the tip to increase the thermal linkage to the area being heated. The solder is then applied to the opposite side of the connection so that the work surfaces, not the iron, melt the solder. Never melt the solder against the iron tip and allow it to flow onto a surface cooler than the solder-melting temperature.

Solder, with flux, applied to a cleaned and properly heated surface, will melt and flow without direct contact with the heat source and provide a smooth, even surface, feathering out to a thin edge (see Fig. A-5). The resulting

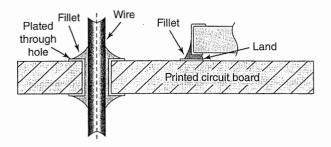


Fig. A-S Solder fillets.

shape is called a *fillet*. Improper soldering will exhibit a built-up, irregular appearance and poor filleting. The parts being soldered must be held rigidly in place until the temperature decreases to solidify the solder. This will prevent a disturbed or fractured solder joint.

Selecting cored solder of the proper diameter will aid in controlling the amount of solder being applied to the connection (e.g., a small-gauge solder for a small connection; a large-gauge solder for a large connection).

Final Inspection and Removal of Flux


The art of soldering requires knowledge of how the process works, the proper tools and materials, lots of practice, and careful inspection. Most solder joints involve fillets, and these take on a characteristic appearance. Figure A-5 shows examples of fillets. Experience dictates how these should appear for high-reliability joints. Generally, a properly shaped fillet indicates clean conditions (good wetting action), proper soldering temperature and duration, and the correct amount of solder.

Cleaning may be required to remove certain types of fluxes after soldering. If cleaning is required, the flux residue should be removed as soon as possible, preferably within 1 hour after soldering. Failure to clean can result in loss of long-term reliability. For example, flux residues can encourage the growth of metal dendrites that can eventually produce short circuits between closely spaced lands.

What the Law Requires


There is not sufficient space here to list the laws that apply to electronic soldering, since they vary by country. In many European countries, restriction of hazardous substances (RoHS) and waste from electrical and electronic equipment (WEEE) standards are enforced.

Appendix B 2s Complement Conversions

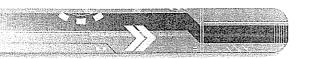

2s Complem	ent Conversion	Charit	and the state of t				
2s Comp	Decimal	2s Comp	Decimal	2s Comp	Decimal	2s Comp	Decimal
11111111	-1	11011111	- 33	10111111	-65	10011111	-97
11111110	-2	11011110	-34	10111110	-66	10011110	-98
11111101	-3	11011101	-35	10111101	-67	10011101	-99
11111100	-4	11011100	-36	10111100	-68	10011100	-100
11111011	-5	11011011	-37	10111011	-69	10011011	-101
11111010	-6	11011010	-38	10111010	- 70	10011010	-102
11111001	-7	11011001	-39	10111001	– 71	10011001	-103
11111000	-8	11011000	-40	10111000	-72	10011000	-104
11110111	-9	11010111	-41	10110111	-73	10010111	-105
11110110	-10	11010110	-42	10110110	-74	10010110	-106
11110101	-11	11010101	-43	10110101	-75	10010101	-107
11110100	-12	11010100	-44	10110100	-76	10010100	-108
11110011	-13	11010011	-45	10110011	-77	10010011	-109
11110010	-14	11010010	-46	10110010	-78	10010010	-110
11110001	-15	11010001	-47	10110001	-79	10010001	-111
11110000	-16	11010000	-48	10110000	-80	10010000	-112
11101111	-17	11001111	-49	10101111	-81	10001111	-113
11101110	-18	11001110	–50	10101110	-82	10001110	-114
11101101	-19	11001101	-51	10101101	-83	10001101	-115
11101100	-20	11001100	-52	10101100	-84	10001100	-116
11101011	-21	11001011	-53	10101011	-85	10001011	-117
11101010	-22	11001010	-54	10101010	-86	10001010	-118
11101001	-23	11001001	-55	10101001	-87	10001001	-119
11101000	-24	11001000	-56	10101000	-88	10001000	-120
11100111	-25	11000111	– 57	10100111	-89	10000111	-121
11100110	-26	11000110	-58	10100110	-90	10000110	-122
11100101	-27	11000101	-59	10100101	-91	10000101	-123
11100100	-28	11000100	60	10100100	-92	10000100	-124
11100011	-29	11000011	-61	10100011	-93	10000011	-125
11100010	-30	11000010	-62	10100010	-94	10000010	-126
11100001	-31	11000001	-63	10100001	–95	10000001	-127
11100000	-32	11000000	-64	10100000	-96	10000000	-128

Glossary of Terms and Symbols

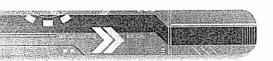

Term	Definition	Symbol or Abbreviation
Access time	In memories, the time it takes to retrieve a piece of data from storage.	
Active HIGH input	Digital input that executes its function when a HIGH is present.	
Active LOW input	Digital input that executes its function when a LOW is present.	
Active-matrix display	A high-quality expensive color LCD using active-matrix technology, which involves the use of thin-film transistors. For contrast see <i>passive-matrix display</i> .	
A/D converter	Device for converting an analog voltage into a proportional digital quantity. Types include a microprocessor-compatible device with binary outputs or meter type with decimal	ADC
Adder	outputs. Combinational logic circuit which generates sum and carry outputs from any set of binary inputs. Half adders and full adders are two fundamental adder circuits.	ADC
Address	In computer systems, a number that represents a unique storage location.	
Alphanumeric	Consisting of numbers, letters, and other characters. ASCII is a common alphanumeric code.	
Ampere	Base unit of current.	A
Analog	A branch of electronics dealing with infinitely varying quantities. Also referred to as <i>linear electronics</i> .	
Analog to digital	Conversion of an analog signal to a digital quantity such as binary.	A/D
AND gate	Basic combinational logic device where all inputs must be HIGH for the output to be HIGH.	A D-Y
Angular velocity	Another method of describing the speed of rotation of a shaft or other object.	
Anade	Positive section of a device such as a diode or LED.	A - \
Arithmetic-logic unit	Part of central processing unit of computer that processes data	
	using arithmetic and logic operations.	ALU
American Standard Code	One of the most widely used alphanumeric codes.	ASCII
for Information Interchange		
Astable multivibrator	Device that oscillates between two stable states. Commonly called a free-running clock or multivibrator.	
Asynchronous	In digital circuits, meaning that operations are not executed in step with the clock.	
Base	Center section of a bipolar transistor used to control current flow from the emitter to collector.	В
BASIC	An easy-to-learn, high-level programming language commonly used to teach beginning programming. An acronym for beginners all-purpose symbolic instruction code.	BASIC
BASIC Stamp 2 module	An easy-to-use microcontroller system including PBASIC software, microcontroller, memory, and interface features (by Parallax, Inc.).	
Baud	Unit of signal transmission speed in telecommunications equal to the number of discrete events per second.	Bd

Term	Definition	Symbol or Abbreviation
BCD counter	A 4-bit counter that commonly counts from binary 0000 to 1001 and resets to 0000.	
Bilateral switch	Switch that operates much like relay, providing good isolation between the control signal and input/output (either digital or analog). A typical bilateral switch is packaged in IC form using CMOS technology and is also called a transmission gate or analog switch.	Control — Out Out —4016 — In
BiMOS	A technology used to manufacturer chips that includes both bipolar and metal-oxide semiconductor (MOS) sections.	
Binary Binary-coded decimal	Base 2 number system using numbers 0 or 1. A common code in which each decimal digit (0–9) is	BCD
Bistable multivibrator	represented by a 4-bit group. A device having two stable states, but it must be triggered to jump from one to the other. Also called a <i>flip-flop</i> .	·
Bit	A single binary digit (0 or 1). Useful in representing ON-OFF switching in digital circuits. An acronym for <i>binary digit</i> .	
Block diagram	A drawing using labeled blocks for functional sections of an electronic system.	
Boolean algebra	Mathematical system for representing logical statements. Very useful in digital electronics.	
Boolean expression	Mathematical representation of a logic function. Function could also be described using a truth table or logic circuit diagram.	AB + C'D = Y
Boundary-scan technology	A system of embedding test points in silicon during the design process for ease of testing for quality control and field testing. See <i>JTAG</i> .	JTAG
Broadside loading	Parallel loading.	-9
Bubble	On logic symbol, it means an active LOW input or output.	
Buffer	Special solid-state device used to increase the drive current at	
	the output. Noninverting buffer has no logical function.	
Bus	In a computer system, parallel conductors used for communication between CPU, memories, and perpherial devices. Most systems have an address bus, data bus, and control bus.	
Byte	An 8-bit group that is commonly used to represent a number or code in computers and digital electronics.	
Cache memory	In computers, an extremely fast, expensive SRAM unit used to store frequently needed or recently used data. The cache memory is the bridge between the ultrafast processor and the much slower main/hard drive/CD-ROM memory. Cache memory is commonly referred as L1 (primary) or L2 (secondary).	
Cascading	Generally, the series connection of electronic devices with the output of the first feeding the input of the second. Term is used in both linear and digital electronics.	
Cathode	Negative section of a device such as a diode or LED.	- >- x
Cathode-ray tube	Vacuum tube used in older televisions, video monitors, and oscilloscopes to display images.	CRT
CD-R	A compact disc that you can record data once using a CD burner on a standard PC. CD-R is an acronym for <i>compact discrecordable</i> .	CD-R
CD-ROM	A read-only mass storage device based on the compact disc.	
CD-RW	A compact disc that you can rewrite data many times using your computer system. CD-RW is an acronym for <i>compact disc-</i>	CD DW
	rewritable.	CD-RW

Term	Definition	Symbol or Abbreviation
Cell	In memories, a single storage element.	
Central processing unit	In computer system, the logic unit that performs logic arithmetic, control functions, and is the center of most data transfers.	CPU
Charge-coupled device	Image sensor using a light-sensitive array of photocells based on capacitorlike semiconductor devices. Used in digital cameras, scanners, camcorders, and scientific imaging equipment. See	
Chin	CMOS image sensor for an alternative technology. An integrated circuit.	CCD
Chip Clack	Signal generated by an oscillator used to provide timing for a digital system such as a computer.	IC
CMOS image sensor	An image sensor using a light-sensitive array of photocells much like the CCD but less expensive to fabricate. Used in less expensive digital cameras and cell phones. See also <i>charge-coupled device</i> .	
Collector	The region of a bipolar transistor that receives the flow of current carriers.	c
Combinational logic	Use of logic gates to produce desired output immediately. No memory or latching characteristics.	\mathcal{A}
Complementary metal-	A popular technology for manufacturing ICs that features	
oxide semicanductor	extremely low power consumption. Uses opposite polarity field-effect transistors in its design.	CMOS
CPLD	A specific programmable logic device much like the GAL only for much larger scale logic problems. An acronym for complex programmable logic device.	CPLD
Current	Movement of charge in a specified direction. Base unit is the	
	ampere.	A
Current sinking	Conventional current flow into LOW output of digital device. Current is "sinking" to ground.	
Current sourcing	Conventional current flow from HIGH output into load. Output is "sourcing" current.	
Cylinder	On a hard disk drive, a series of identical tracks on various platters.	
D/A converter	Device for converting a digital quantity into a proportional analog voltage.	DAC
D flip-flop	Flip-flop with at least set and reset modes of operation. Also called a <i>data</i> or <i>delay flip-flop</i> .	CLK FF Q
Data selector	Combination logic block that selects one-of-x data inputs and connects that information to the output. Also called a <i>multiplexer</i> .	
Decader	A logic device that translates from binary code to decimal. Generally, it translates processed data into a digital system to another format such as alphanumeric.	
Decrement	To decrease the count by 1.	
Demultiplexer	Combination logic block that distributes data from single input	
·	to one-of-x outputs. Also called a <i>distributor</i> . Can change serial to parallel data.	DEMUX
Digital	Branch of electronics dealing with discrete signal levels. Signals are commonly HIGH or LOW and may be represented by binary numbers.	
Digital potentiometer	An electronic device comparable to a traditional potentiometer with resistance outputs variable in discrete steps. The wiper position can be stored in EEPROM when the power is turned off. Digital input pulses control the movement of the wiper. Also referred to as a solid-state potentiometer or nonvolatile (NV) digital potentiometer.	

Term	Definition	Symbol or Abbreviation
Digital signal processor	A specialized microprocessor-like device that can be programmed to condition and enhance signals (eliminate noise, increase frequency response, etc.). Commonly used in conjunction with A/D and D/A converters.	DSP
Digital to analog	Conversion of a digital signal to its analog equivalent, such as a voltage.	D/A
Digital versatile disc	A popular very high capacity optical disc that looks like a traditional CD. It can store from about 4.7 GB to about 17 GB of video, audio, or computer data. Also referred to as a digital video disc.	DVD
Digitize	To convert an analog signal into digital units or pulses. See <i>A/D</i> converter.	
DIMM	In computer technology, a modern RAM memory board holding many SDRAM memory chips used on PCs. An acronym for dual in-line memory module. See also slightly older SIMM.	DIMM
DIN connector	Connectors used on computers following the standards of the	3
Diode	German association DIN (Deutsche Industrie Norm). Two-terminal semiconductor device. They usually allow current to flow in only one direction.	DIN 2
Discrete time signal	Another name for a digital signal especially used in DSP applications where digital inputs are commonly a sampling of an analog input.	
Display multiplexing	To light multiple alphanumeric displays by sequentially activating them one at a time in rapid succession so they appear to be turned on continuously. Display multiplexing saves components and cost.	
Double data rate SDRAM	A synchronous dynamic RAM that is faster than regular SDRAM.	DDR SDRAM
Drive	Generally in computers, it refers to a mass-storage device such as a hard disk drive, optical drive, or solid-state drive. Usually an electromagnetic or optical device which moves mass-storage media under read/write heads.	
Driver	In digital electronics, an IC (or other interface electronics) that is capable of operating at higher currents and suitable voltages to drive an output device (such as a display).	
Oual in-line package	Older packaging method for ICs.	DIP
Dynamic RAM	Extremely common random-access (read/write) memory device whose memory cells need refreshing many times per second. A volatile memory. Compare with <i>SDRAM</i> and <i>RDRAM</i> .	DRAM
Edge triggering	In synchronous devices such as flip-flops, the exact time the device is activated such as on the rising (positive edge) or falling edge (negative edge) of the clock pulse.	
8421 BCD code	Four-bit BCD code with weighting of 8, 4, 2, and 1. See <i>binary-coded decimal</i> .	
Electrically erasable programmable read-only memory	A nonvolatile memory that can be programmed, electrically erased, and reprogrammed. Flash memories are a type of EEPROM.	EEPROM
Electronic control unit	In modern automobiles, one of a variety of embedded electronic control modules. A few of these include (1) engine control module (ECM), (2) body control module (BCM), (3) brake control module (ABS), (4) transmission control module (TCM), (5) airbag control unit (ACU), and (6) instrument	
	panel module.	ECU

Term	Definition	Symbol or Abbreviation
Emitter	The region of a bipolar transistor that sends the current carriers to the collector.	(A)
Enable	To activate a function or input to a digital circuit. The opposite of <i>disable</i> .	Ϋ́E
Encoder	A logic device that translates from decimal to another code such as binary. Generally, it translates input information to a code useful to digital circuits.	
Even parity	In data transmission, sending a parity bit that will make the number of 1s in a group even.	
Extended Binary-Coded	An 8-bit alphanumeric code used mainly on mainframe	EDODIO
Decimal Interchange Code	computers.	EBCDIC
Fan-out	Output drive characteristic of logic device. The number of inputs of the logic family that can be driven by a single output.	
Ferroelectric RAM	A semiconductor nonvolatile RAM with good access speed that allows in-circuit programming. FeRAM memory cells are based on ferroelectric capacitors and MOS transistors.	FeRAM or FRAM
Field-effect transistor	Type of transistor where gate terminal controls the resistance of a semiconducting channel.	
Firmware	Computer programs and data held permanently in nonvolatile memory devices such as ROMs. See also <i>hardware</i> and <i>software</i> .	
Flash memory	A nonvolatile memory similar to the EEPROM. Its outstanding characteristics include very high density (small memory cell), low power, and nonvolatile but rewritable.	
Flip-flop	Basic sequential logic device having two stable states. Can serve as a memory device. Also called a <i>bistable multivibrator</i> .	
Floating input	An input not held HIGH or LOW, which may "float" either HIGH, LOW, or in between. Can cause problems.	
FPLD	A specific programmable logic device something like the CPLD, but containing simpler cells allowing more flexibility during the design process. An acronym for field programmable logic device.	FPLD
Frequency divider	A logic block that divides the input waveform's frequency by a certain number (such as divide by 10). Counters commonly perform this function.	
Full adder	Digital circuit with three inputs for carry in and two bits with sum and carry out outputs.	$C_{\text{in}} - FA - FA - FA - C_{o}$
Gain	A ratio of output to input. May be measured in terms of voltage, current, or power. Also known as <i>amplification</i> .	В —
Gate	Basic combinational logic device which performs a specific logic function (AND, OR, NOT, NAND, NOR).	
Generic array logic	A specific programmable logic device (PLD) with an array of ANDs that can be reprogrammed; a fixed array of ORs gates.	GAL
Glitch	An unwanted current or voltage spike that usually commonly reoccurs but not regularly.	
GND	Label for negative of power supply in TTL ICs and some CMOS ICs. <i>Common ground</i> .	
Gray code	Numeric code for rotary encoders because, unlike binary, as you progress to the next successive value (up or down) only 1 bit changes. The Gray code is also called reflected binary code.	3-Bit Gray Code 0 0 0 0 0 1
Half adder	Digital circuit that will add two bits and output a sum and carry. Cannot handle carry inputs.	$ \begin{array}{cccccccccccccccccccccccccccccccccccc$
Hall-effect sensor	A transducer that converts an increasing or decreasing magnetic field into a proportional varying voltage. These sensors are commonly packaged as <i>Hall-effect switches</i> featuring a digital output (HIGH or LOW).	1 1 1 1 0 1 1 0 0

Term	Definition	Symbol or Abbreviation
Hardware	In computer technology, the physical components of a	
11 .	computer system. See also <i>software</i> and <i>firmware</i> .	**
Hertz	The base unit of frequency. One cycle per second.	Hz
Hexadecimal	Base 16 number system using characters 0 thru 9, A, B, C, D, E, and F. Used to represent binary numbers 0000 through 1111.	Hex
Hybrid hard disk drive	A combination of a hard disk drive and nonvolatile memory (such as flash memory) used as a larger buffer. Hybrid drives have the benefit of greater speed of data access and decreased power consumption (its hard drive does not speed until	
	needed).	H-HDD
Hysteresis	Unequal switching thresholds exhibited by some logic circuits making their outputs "snap action." Schmitt-trigger logic devices exhibit this feature.	<i>J</i>
IEEE	Institute for Electrical and Electronic Engineers.	
Increment	To increase the count by 1.	
Input/Output	A connection to a digital device that can be programmed to	
	serve as either an input or output. Very common on many	
	complex devices including microcontrollers.	I/O
Instruction set	The complete set of commands responded to by a microprocessor, microcontroller, or PLC.	
Integrated circuit	Combination of many electronic components in a compact	
	package that functions as an analog, digital, or hybrid circuit. Classified as to levels of circuit complexity (SSI, MSI, LSI, VLSI, or ULSI).	IC
Interfacing	The design of interconnections between circuits that shift the levels of voltage and current to make them compatible.	
Inverter	Basic logic function where the output is always opposite the	>
	input. Also called the NOT function.	V
JEDEC	Joint Electron Device Engineering Council.	
J-K flip-flop	Flip-flop with at least set, reset, toggle, and hold modes of operation. Very adaptable.	CLK - FF - Q
JTAG	In common use, JTAG refers to the boundary-scan method of embedding test points in silicon during the design process for automated testing. An acronym for Joint Test Action Group, responsible for developing the IEEE STD 1149.1 Test Access Port and Boundary Scan Architecture. See also boundary-	
	scan technology.	JTAG
Karnaugh map	A graphic method of reducing Boolean expressions to simpler forms.	K map
Large-scale integration	Used by some manufacturers to indicate the complexity of an integrated circuit. LSI usually means having a complexity of	-
t t	from 100 to 9999 gates.	LSI
Latch	Fundamental binary storage device. Also called a <i>flip-flop</i> .	T 070
Least significant bit	The bit position in a binary number with the least weight.	LSB
Light-emitting diade	Special PN junction that gives off light when current flows through it. Has lens to focus the light.	LED
Liquid-crystal display	Very low power display technology used in most battery- operated devices. Nematic fluid in display changes reflectivity when energized changing display from silver to black characters. Color LCDs are common.	LCD
Logic analyzer	An expensive test instrument that can sample and store many channels of digital information.	
Lagic diagram	A schematic showing interconnection between logic devices like gates, flip-flops, etc.	

Term	Definition	Symbol or Abbreviation
Logic family	A group of totally compatible digital ICs that can be interconnected with no interfacing problems. Common examples are the 7400 series TTL, 74HC00 series CMOS, and 4000 series CMOS.	
Logic function	The logical task needed to be performed. It might be represented by the name (such as AND), a logic symbol, a Boolean expression (such as $AB = Y$), and/or a truth table.	
Logic levels	In digital electronics, voltage ranges at which inputs to digital devices interpret signal as HIGH, LOW, or undefined. Voltage thresholds may be different for various logic families.	
Logic probe	Simple service tool which indicates logical 0s, logical 1s, or pulses in digital circuits.	
Logic subfamilies	Groups of related digital ICs that have similar characteristics but may vary in speed, power dissipation, and current drive capabilities. Examples might be 7400-, 74LS00-, 74F00-, 74ALS00-, and 74AS00-series TTL ICs. In some applications you may be able to substitute between subfamilies.	
Logic symbols	Two systems are used in the U.S. Traditional representations using the unique shaped logic gate symbols. The newer IEEE symbols using rectangle boxes.	
Low-voltage CMOS	A family of lower-voltage CMOS digital ICs for 3-V applications. LVC has excellent characteristics and is used in portable equipment.	LVC
Magnetoresistive RAM	A semiconductor nonvolatile RAM with excellent access speed, allows in-circuit programming and low power, and features high density. MRAM memory cells are based on a transistor and a magnetic tunnel junction (MTJ).	MRAM
Magnitude comparator	A combinational logic block that compares two binary inputs A and B and activates one of three outputs $(A > B, A = B, \text{ or } A < B)$.	
Maxterm Boolean expression	See product-of-sums.	
Medium-scale integration	Used by some manufacturers to indicate the complexity of an integrated circuit. MSI usually means having a complexity of from 12 to 99 gates.	MSI
Memory card	Packaging method for arrays of memory devices (such as flash memories). The cards are commonly about the size of a thick credit card with edge connectors; other sizes are available. See <i>PCMCIA</i> .	
Metal-axide semicanductor	Technology used in the fabrication of integrated circuits using metal and an oxide (silicon dioxide) as an important part of the device's structure.	
Microcontroller	An inexpensive IC which contains a tiny processor, limited RAM, ROM, and I/O. A small computer on a chip. They are usually embedded in a product.	
Microprocessor	An IC which forms the CPU of most microcomputers.	MPU
Minterm Boalean expression	See sum-of-products.	
Minuend	The number the subtrahend is being subtracted from.	
Monostable multivibrator	Device that emits a single pulse when triggered. Also called a one-shot multivibrator.	
Most significant bit	The bit position in a binary number with the most weight.	MSB

Term	Definition	Symbol or Abbreviation
Multiplex	In driving displays, to turn on/off one of several displays, each for a short time in turn at a high enough frequency so they appear to be lit continuously. In general, transmitting several signals over common lines.	
Multiplexer	Combinational logic block selects one-of-x inputs and directs the information to a single output. Can change parallel to serial data, Also called a <i>data selector</i> :	MUX
Multivibrator circuits	Classified as bistable (flip-flops), monostable (one-shots), and astable (free-running clocks).	MV
NAND gate	Basic combinational logic device where all inputs must be HIGH for the output to be LOW. A not AND circuit.	
Nibble	One half a byte. A 4-bit binary word.	
Noise	In digital electronics, unwanted voltages induced in connecting wires and PC board traces that might affect input logic levels and therefore outputs in circuits.	
Noise immunity	A digital circuit's insensitivity to undesired voltages or noise. Also called <i>noise margin</i> in digital circuits.	
Nonvolatile memory	Memory which retains data even if the power is turned off.	
Nonvolatile RAM	Read/write memory that will hold its data even when the power is turned off.	NVRAM
NOR gate	Basic combinational logic device where all inputs must be LOW for the output to be HIGH. A not OR circuit.	
NDT	Basic combinational logic device where the output is always the opposite from the input. Also called an <i>inverter</i> .	->-
Octal	Base 8 number system using characters 0 thru 7.	
Odd parity	In data transmission, sending a parity bit that will make the number of 1s in a group odd.	
0hm	The base unit of resistance.	Ω
1 s complement	The 1s complement form is formed by inverting each bit of a binary number.	
Open collector	Digital circuit output which has no internal path to the positive of the power supply. Commonly used with an external pull-up resistor.	
Operational amplifier	An adaptable amplifier with inverting and noninverting inputs featuring high input and low output impedance, and very high gain. Gain can be set by external components.	op amp
Optical disc drive	Very high capacity mass-storage device which commonly stores data as surface pits. Reading is done by directing laser bean at pits/no pits and detecting the light bouncing from the reflective disc. Other optical recording methods are also used.	
Optoisolator	An interface device used to electrically isolate input from output by using a light beam to transfer data.	
OR gate	Basic combinational logic device where the output goes HIGH when any or all inputs are HIGH.	
Oscillator	Electronic circuit that generates ac waveforms from a dc source.	
Oscilloscope	Test instrument that plots time against voltage by drawing a graph or waveform on the screen. Oscilloscopes are available in either analog or digital models. Also called a <i>scope</i> .	
Parallel data	Transmission of data in groups at the same time over multiple lines.	
Parity	A system used to detect errors in binary data transmission.	
Parity bit	An extra bit sent with data bits to check for errors in transmission.	

Term	Definition	Symbol or Abbreviation
Passive-matrix display	An low-resolution LCD which is satisfactory for low-cost monochrome displays but not good for high-quality color LCDs. For contrast see active-matrix display.	
PBASIC	A specialized high-level version of BASIC developed by Parallex, Inc., to program BASIC Stamp microcontroller modules.	
PC	Commonly means personal computer but it may also be used to refer to a programmable controller or programmable logic controller.	
PCMCIA	Personal Computer Memory Card International Association (sets standards for memory cards).	
Phase-change technology	Used in DVD-RW and DVD+RW optical discs. A phase-change alloy is employed for reading, writing, and erasing information. The tiny "pit" and "no pit" areas of optical disc are either dark/nonreflective if the alloy is in its amorphous state or reflective if the phase-change alloy is in its crystalline state. These discs are rewritable.	
Photoresistive cell	A photo-sensitive resistor whose resistance decreases as the light striking the unit increases. A cadmium sulfide photo cell or photoresistor.	Cds
Pipelining	In computer terminology, a method of speeding up processing by fetching and decoding instructions ahead of time so the next instruction is waiting to be executed immediately. Also called <i>prefetching</i> .	
Plastic-leaded chip carrier	A type of surface-mount IC package with leads bent under the case.	PLCC
Platter	In a hard disk drive, a single hard disk. The drive may contain a stack of platters to increase storage capacity.	
Part	In computers and microcontrollers, the circuits used to transfer data in and out of the system.	I/O
Product-of-sums	The form of a Boolean expression that looks like this: $(A + B)$ $(C + D) = Y$. Implemented using an OR/AND logic diagram. Also called a <i>maxterm Boolean expression</i> .	
Program	List of instructions which tells computer what to do. May be written in a variety of computer languages.	
Programmable array logic	A specific PLD containing an array of ANDs which are programmable with a fixed OR array.	PAL
Programmable logic controller	A specialized heavy-duty computer system used for process control in factories, chemical plants, and warehouses. Closely associated with traditional relay logic. Also called a	
Programmable logic device	programmable controller (PC). A generic name for a group of specific programmable logic	PLC
Programmable read-only	devices including PALs, GALs, CPLDs, and FPLDs. Nonvolatile memory which is programmed once by the user or	PLD
memory Propagation delay	distributor. The time it takes the output of a digital device to change state after the input is activated. Usually measured in nanoseconds.	PROM
Pull-up resistor	A resistor connected to the positive of the power supply to hold a point in the circuit HIGH when it is inactive.	
Pulse-width modulation	Information placed on a digital signal by increasing and decreasing the width (duration) of pulses. Used to drive hobby servo motors. Also referred to as <i>pulse-duration</i>	
	modulation.	PWM


Term	Definition	Symbol or .	Abbreviation
Quadrature code	The 2-bit code (a type of Gray code) that can be used with a rotary encoder to determine the direction of rotation of a shaft. In terms of shaft rotation, <i>quadrature</i> means being 90 degrees out of phase.		2-Bit Gray Code 0 0 0 1 1 1 1 0
Radix	The base of a number.		, ,
Random-access memory	Memory organization allowing for easy access to each bit, byte, or word. RAM is commonly used to mean semiconductor read/write memory.	RAM	
MARDR	In computer technology, an extremely fast dynamic RAM. Acronym for Rambus dynamic RAM. Compare with <i>DRAM</i> , <i>SDRAM</i> .	RDRAM	
Read	The process of sensing and retrieving data from a memory cell or cells.		
Read-only memory	Nonvolatile memory which is not usually changed once it is programmed. ROM commonly used to refer to mask-programmable read-only memory.	ROM	
Register	A group of temporary memory cells (such as flip-flops) for temporary storage that have a common purpose. For instance, a register might have a name (such as DIRS in a popular microcontroller) and have a specific width (such as 8 or 16 bits).		
Relay	Electrical device which uses the force of an electromagnet to open/close contacts. Used for heavy-duty switching and isolation of circuits.		3
Reset condition	In a flip-flop, the normal output (Q) has been reset or cleared to 0.		
Resistance	Opposition to current flow. Measured in ohms.	R	
Rewritable optical disc	A very large capacity optical disc that can be rewritten to many times. Some versions are called PD rewritable optical disc or CD-E (compact disc erasable).	CD-E	
RIMM	Rambus DRAM memory packaging for use in computers comparable to the DIMM. RIMM cannot be interchanged with DIMM.		
Ring counter	A recirculating shift register which is loaded with a pattern of 1s (such as a single 1) which continue to circulate around in the circle or repeated clock pulses.		
Ripple counter	Simple binary counter where the changing state of the LSB flip-flop triggers the clock input of the next, etc. A time delay results from the rippling of the count from LSB to MSB.		
RoHS	Acronym for the EU directive, restrictions of hazardous substances, and a label used on some electronic components. Sometimes called the <i>lead-free directive</i> , it also restricts the use of lead, mercury, cadmium, chromium, PBB, PBDE, and acrylamide in electronic products.	RoHS	
R-S flip-flop	Flip-flop with at least set, reset, and hold modes of operation. Fundamental latching (memory) circuit.	KOHS	$\begin{array}{cccccccccccccccccccccccccccccccccccc$
Sampling	To measure a signal level at discrete times. Widely used in DSP while digitizing an analog input at discrete times.		
Schmitt trigger	A circuit that exhibits hysteresis and is useful in signal conditioning in digital electronics. May be used to digitize an analog input.		
Schottky diode	A diode whose voltage drop when forward-biased is lower than a silicon diodes; also characterized by its quick response to being reverse-biased. It is used to speed switching times in Schottky TTL ICs. Schottky diodes may also be known as barrier diodes.	Anode	Cathode

Term	Definition	Symbol or Abbreviation
SDRAM	In computer technology, a very fast dynamic RAM. Acronym for synchronous dynamic RAM. Compare with <i>DRAM</i> and <i>RDRAM</i> .	SDRAM
Semiconductor	Elements having four valence electrons and electrical properties between those of conductors and insulators.	
Sensor	A detector that converts a physical quantity into an electric/ electronic signal. Sensors commonly detect and measure light and color, pressure, distance, temperature, humidity, compass headings, GPS, acceleration, tilt, proximity, flow, motion, noise, vibration, magnetic fields, electricity (voltage, current, and resistance), radiation, Hall effect, and chemicals.	
Sequential logic	A logic circuit whose logic states depend on asynchronous and synchronous inputs. Exhibit's memory characteristics.	
Serial data	The transmission of data one bit at a time.	
Servo	General term for a motor whose either angular position or speed can be precisely controlled by a servo loop which uses feedback from the output back to the input for control.	
Set condition	In a flip-flop, the normal output (Q) has been set to 1.	
Seven-segment display	Numeric display with seven segments. May be implemented with LED, LCD, or VF technologies. A few letters can also be displayed for indicating hexadecimal numbers.	$\begin{bmatrix} \underline{a} \\ f \end{bmatrix} b$
Shaft encoder	Encoder that is used to convert the angular position of a wheel or shaft to a digital signal, such as the Gray code. Also called a <i>rotary encoder</i> .	$\frac{1}{d}$
Shift register	A sequential logic block made up of flip-flops that allows parallel or serial loading and serial or parallel outputs as well as shifting bit by bit.	
Signal	The information transmitted within, to, and from electronics circuits.	
Silicon	A semiconductor element used in the manufacture of most solid- state devices such as diodes, transistors, and integrated circuits.	
SIMM	In computer technology, a RAM memory board holding many memory chips used on PCs. An acronym for single in-line memory module. See also more modern <i>DIMM</i> .	SIMM
Small-outline DIMM	Compact memory module packaging for use in laptop-sized computers. One example is the 200-pin DDR SDRAM SO DIMM.	SO DIMM
Small-scale integration	Used by some manufacturers to indicate the complexity of an integrated circuit. SSI usually means having a complexity of	
Software	less than 12 gates. Computer programs that instruct the hardware. Two main classifications of software are applications (like a word processor or game) and operating systems. Other categories might include network software and programming software. See also hardware and firmware.	SSI
SOIC	Smaller package for IC than DIP packaging. Used in SMT. An acronym for small-outline integrated circuit.	Prinni
Salenaid	An actuator which converts electric energy into linear motion. It is constructed as a hollow coil with a sliding iron core. In operation the spring-loaded iron core is "sucked into" the coil when current flows in the coil.	
Solid-state drive	A device with solid-state nonvolatile memory (such as flash memory) that is organized so it appears to the computer as a hard disk drive. SSDs are a bit more costly but are used where fast access speed, low power consumption, small size,	
	and light weight are important (e.g., for handheld devices).	SSD

Term	Definition	Symbol or Abbreviation
Source	Terminal of a field-effect transistor that sends current carriers to the drain.	
Static RAM	Common random-access (read/write) memory device which stores data in a flip-flop-like cell. Volatile memory.	S SRAM
Stepper motor	A dc motor that jogs in short uniform angular movements in either direction given the proper digital signals. Common step angles might be 1.8°, 3.6°, 7.5°, and 15°. Two types are permanent-magnet and variable-reluctance stepper motors.	Stepper
Subtrahend	The number being subtracted from the minuend.	
Successive approximation	In D/A and A/D converters, a technique used to decrease conversion time.	
Sum-of-products	The form of a Boolean expression that looks like this: $AB + CD = Y$. Implemented using an AND/OR logic diagram. Also called a minterm Boolean expression.	Plastic-leaded chip carrier Small-outline Chip
Surface-mount technology	SMT covers all aspects of the manufacturing techniques, equipment, and parts (surface-mount devices or SMDs) used in soldering electronic components to the surface of a printed circuit board.	(PLCC) package (SOT) component Solder Solder Circuit board
Synchronous	In digital circuits, meaning that operations are executed in step with the clock.	
T flip-flop	Short for toggle flip-flop. The output toggles to the opposite logic state on repeated clock pulses. Very useful in digital counter circuits.	
Thermistor	A thermally sensitive resistor used as a heat sensor.	(≥ τ)
Three-state output	Condition of outputs on certain digital ICs which includes three possible states including HIGH, LOW, or high impedance. Also commonly referred to as <i>Tristate</i> (trademark of National Semiconductor).	
Toggle	To change to the opposite logic state. A pulse that changes a logic circuit's state to opposite condition. A mode of operation in a flip-flop where the output goes to the opposite state on each successive clock pulse.	
Transducer	A general name for a device that converts one form of energy to another. Examples include (1) as an input, Hall-effect sensor converting from magnetic to electric energy; (2) as an output, electric motor converting from electric to rotary mechanical energy.	
Transistor	A solid-state amplifying or controlling device which commonly has three leads.	
Transistor-transistor logic	A type of digital IC fabricated using bipolar junction transistors.	TTL
2s complement	Notation commonly used to indicate sign and magnitude of a number using only 0s and 1s. To form 2s complement, take 1s complement of binary and add 1. Helpful when using binary adders for binary subtraction.	
Trigger	A pulse that causes a logic device to be activated or change states.	ABIY
Truth table	Tabular listing of all inputs and resultant output conditions for a logic function or circuit.	0 0 0 0 1 0 1 0 0
2s complement subtraction	Method of subtraction using a 2s complement subtrahend added to the minuend. Used so adders can be used to perform subtraction.	i i i
Ultra-large-scale integration	Used by some manufacturers to indicate the complexity of an integrated circuit. ULSI usually means having a complexity	YII OI
	of 100,000 or more gates.	ULSI

Term	Definition	Symbol or Abbreviation
Universal shift register	Register with many features including serial in/out, parallel in/out, hold, and shift right or left.	
USB port	USB is an acronym for universal serial bus. A general-purpose serial port for transmitting data from a microcomputer to peripherals such as external printer, modem, mouse, keyboard, portable drive (optical, magnetic), or flash memory module. The USB port provides power to the device that can be plugged in or disconnected when the computer is turned on.	
V_{CC}	Label for positive of power supply in TTL ICs and some CMOS ICs (commonly +5 V).	
V_{DD}	Label for positive of power supply in many but not all CMOS ICs $(+3 \text{ to } +18 \text{ V})$.	
$V_{\rm ss}$	Label for negative of power supply on many but not all CMOS ICs.	
Vacuum fluorescent display	Low-voltage triode vacuum tube display which commonly glows green (without filters).	VF
Very large-scale integration	Used by some manufacturers to indicate the complexity of an integrated circuit. VLSI usually means having a complexity of from 10,000 to 99,999 gates.	VLSI
Volatile memory	Memory that can store data only as long as power is applied.	
Valt	Base unit voltage.	V
Voltage	Electric pressure.	V
Voltage comparator	An op-amp circuit that compares a positive voltage input (A) with a negative voltage input (B) and indicates with a logic output which input is higher.	
Waveforms	A graphic representation of voltage versus time as might be viewed on an oscilloscope.	V ‡time
Winchester drive	Historical name for a hard disk drive.	
Ward	In computer terminology, a group of bits that are processed as a single unit. The exact definition of a word depends on the system. Word sizes of 16 or 32 bits are common.	
Write	The process of recording data in a memory cell or cells.	
Write-once read-many	An optical CD recordable disc that can be recorded on once using your PC, and it then is permanent like a CD-ROM.	WORM
XNOR gate	Basic combinational logic device where an even number of HIGH inputs generates a HIGH output. A not XOR gate.	
XOR gate	Basic combinational logic device where an odd number of HIGH inputs generates a HIGH output.	#

Photo Credits

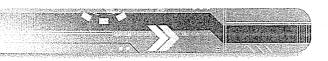

Front Matter

Page xiii (left, middle): Courtesy Apple Computers; p. xiii (right): © Corbis; p. xvi (left): © Cindy Lewis Photography; p. xvi (right): © Lou Jones/Getty Images.

Chapter 1

Figure 1-3a: Courtesy Simpson Electric Co.; **1-3b:** Courtesy Fluke Corporation; **p. 4** (*top left*): file photo; (*top right*): © Fred Wilson/Getty Images RF; (*bottom*): Courtesy Apple Computers; **1-16:** Courtesy of Dynalogic 1.800.246.4907.

Chapter 3

Page 70: International Telecommunication Union & Inmarsat.

Chapter 4

Page 94: Courtesy Braun; p. 125: © Corbis; p. 126: © Bettmann/Corbis.

Chapter 6

Page 211 (left): © Michael Schmelling/AP Photo; 6-19: Courtesy Fluke Corporation.

Chapter 9

Page 317: Courtesy Microvision.

Chapter 11

Page 366: Courtesy Yamaha Consumer Electronics; 11-17: Courtesy Seagate Technology.

Chapter 13

Page 447: © Hayes Microcomputer Products; p. 451: Courtesy Motorola.

Appendix A

Figure A-1a: © AIM Solder; A-1b: © IPC Media Training; A-4: © Zoonar/Bernd Juergen/agefotostock RF.

Index

Symbols	Analog electronic systems, 4, 5	Battery-powered soldering irons, using, 150
& (ampersand), 73	Analog in nature, natural phenomena as, 4-5, 499	Baud rate, 461
'(apostrophe) symbol, 48	Analog input to digital information. See A/D converter	Baudot, 202
(·) multiplication dot, 45	(analog-to-digital converter)	Bayer filter, 486, 487
(⁻) overbar, 48 + symbol, 58	Analog inputs, to digital systems, 499 Analog measuring device, 2	BBSRAM, 381 BCD (binary coded decimal), 27
~ (tilde), 81	Analog meter, 3	BCD code, 197
I (vertical line), 81	Analog-to-digital (A/D) converter. See A/D converter	BCD decoder/driver circuit, wiring diagram of, 224
> symbol, 249, 277	(analog-to-digital converter)	BCD-to-seven-segment decoder, 214, 215, 218, 219
•	AND circuit, using switches, 44	BCD-to-seven-segment decoder/drivers, 208, 209-21
A	AND dot, eliminating, 96	BEL (bell), 202
ABEL software, 116	AND function, 44, 45	"Bent under" pin, 296
Absolute encoders, using Gray code, 200	AND gate, 43-45, 73-74, 419	Bidirectional shift register, 312
AC, in a core part number, 65	And logic function, substituting NAND gates, 56	Bilateral switches, 151
Access time, 370, 393	AND truth table, 44	BiMOS 5804 stepper motor translator/driver, 176–17
AC-CMOS, 148	AND-OR logic circuit, 107	Binary (BCD)-to-decimal decoder circuit, 42
Accumulating, 484	AND-OR pattern, of logic gates, 109	Binary 0, 44
Accumulator, 452, 485	Angular velocity, 291	Binary 1, 44
Accuracy, of an A/D converter, 517	Anode, 221 Antifuse FPGAs, 116	Binary addition, 330–331
Acid fluxes, 531–532	"Any or all gate," 46	Binary and octal representations, for decimal numbers 1 through 17, 36
ACT, in a core part number, 65 Action part, of an instruction, 451	Apostrophe symbol, as alternative NOT symbol, 48	Binary calculator, 331
Activators, 531	Arithmetic circuits, 330–356	Binary code, converting to decimal numbers, 30
Active HIGH input, 74	Arithmetic unit, of a computer, 445–446	Binary coded decimal (BCD). See BCD (binary coded
Active HIGH input switch, 153	Arithmetic-logic unit (ALU), 330, 334, 340, 446	decimal)
Active LOW inputs, 204	AS, in a core part number, 65	Binary count, 263
Active LOW outputs, 204	ASCII (American Standard Code for Information	Binary digit, 37
Active LOW switches, 153	Interchange), 27, 202, 203	Binary equivalents, to decimal numbers, 35
Active-matrix LCDs (AMLCDs), 216-217	Astable multivibrator, 10	Binary multiplication, 343-344, 346
A/D converter (analog-to-digital converter), 5, 6,	Astable MV, 237	Binary multipliers, 345–348
483, 499	AS-TTL (advanced Schottky TTL), 148, 160	Binary number system
example of a digitizer, 523	Asynchronous counter, 264	counting in, 27–28
IC, 517–519	Asynchronous inputs, overriding synchronous inputs,	place value in, 28–29
other, 512–515	242	Binary numbers
specifications, 516–517	Audio amplifier sections, of the digital roulette game, 319	converting from, 229 converting to decimal, 30
translating analog voltage at input, 506 truth table for, 506, 507	Audio ports, 464	converting to decimal, 35
using as a digital voltmeter, 510–512	Automatic clear circuit, 319–320	converting to octal, 36
ADC0804 8-bit A/D converter IC, 517, 519, 520	Automobile	Binary outputs, digital light meter using, 521
Add steps, in binary multiplication, 346, 347	alarm system, 75-77	Binary point, 29, 30
Add-and-shift method, 345, 346	driving experience enhanced by electronics, 8	Binary subtraction, 336-337
Add-and-shift multiplication, 346, 347	fuel indicators, 6	Binary term, 38
Adders, 330	_	Binary-coded decimal numbers, 375
used for subtraction, 349-350	В	Binary-to-Gray code converter, 370-371
Address	B421 BCD code, 196–198	Bipolar stepper motors, 172
rotary switch positions as, 372	Back-and-forth (reciprocating) motion, 488, 489	Bipolar technology, families manufactured using, 62
of a word, 366	Backlighting, added to an active-matrix LCD screen,	Bipolar TTL logic family inverter, 141–142
Address bus, 362, 448	217 Page 2 greaters 27, 24	Biquinary counter, 7493 IC as, 272
Address decoder, 454, 455, 456	Base 2 system, 27, 34 Base 8 numbers, 36	Bistable multivibrator, 10, 237 Bit, 37
Address inputs, of the 7489 RAM, 367 Alarm, LCD timer with, 426–429, 430–432	Base 10 system, 27, 34	Blanking, leading zeros, 211–212
Algorithm, 487	Base 16 system, 34, 35	Blanking input (BI), 209, 210
"All or nothing gate," 43	Basic gate, converting to any other gate, 62	Blinking LED 1 program, listing of, 481
Allegro Microsystem, 3132 Hall-effect switch, 180	BASIC Stamp 1 module (BS1), 477	Block diagrams
Alphanumeric code, 202	BASIC Stamp 2 (BS2) Microcontroller Module by	debounced logic switch, 9
ALS, in a core part number, 65	Parallax, 77, 126, 128, 186-188, 404	digital clock, 413, 419
Alternate NOT symbol, 48	BASIC Stamp 2 module (BS2), 126, 477-478	digital electronic timer system, 427, 428
Alternative NAND symbol, 61	circuit, 488, 490	digital frequency counter, 419, 420, 421
ALU (arithmetic-logic unit), 330, 334, 340, 446	steps in wiring and programming, 186	digital potentiometer, 394, 396
American Standard Code for Information Interchange	using with an ultrasonic distance sensor to measure	digital roulette wheel, 318
(ASCII), 27, 202, 203	distances, 434	of a full adder, 333
AMLCDs (active-matrix LCDs), 216–217	BASIC Stamp program, 488, 480, 401	of a full subtractor, 336, 338
Ammeter, as output indicator, 5	BASIC Stamp program, 488–489, 491 BASIC Stamp programming, 479–482	of a half subtractor, 336, 337 MM5314 MOS LSI clock IC, 416, 417
Ampersand (&) inside the IEEE standard AND gate symbol, 73	Battery backup, for a CMOS SRAM, 381	repeated addition-type multiplier system, 345
in the NAND function in PBASIC, 81	Battery backup SRAM, 381	2732 EPROM chip, 378
Analog circuits, 2	Battery-operated portable devices, CMOS ICs	Blood tests, requiring less blood, 277
Analog devices, 2, 499	ideal for, 150	Board of Education (BOE), 478–479
		* **

Boole, George, 99, 125	Circumflex accent (^), in the XNOR function of	Complementary symmetry metal-oxide semiconductor
Boolean algebra, 45, 99–100, 125 Boolean expressions, 45	PBASIC, 81 CISC (complex instruction set computing), 475	(CMOS) ICs, 160 Complementing, 4-bit binary number, 32
forms of, 91	Clamp diode, 165	Computer bulk storage devices, 387–394
for four-input OR gate, 58	Cleaning, required to remove certain types of fluxes, 534	Computer connections, to networks, 448–449
for the OR function, 51	Clear mode, 74194 shift register, 311, 312	Computer mouse, 211
keyboard versions of, 95, 124	CLK inputs, 239, 266, 293	Computer simulations, logic converter, 108-111
for NAND, 50	Clock, digital circuits in, 10	Computer systems, 445–491
for the output of the XNOR gate, 55	Clock chips, large-scale integrated, 414	data transmission in, 464–468
simplifying, 99–100, 101	Clock circuit, 26	flow of program instructions and data in, 446–447
to truth table, 94	Clock module, 415, 416 Clocked R-S flip flop, 239–240	Computers, 445–446 on a chip, 451, 473
for the XNOR gate, 54 Borax paste, 532	CLR input, of a counter, 74	memory devices in, 362–363
Borrow out output, 429	CMOS (complementary metal-oxide semiconductor), 62	photographic history of, 4
Bounce-free switch, 180, 183	advantages of, 144	Conductive foam, 150
Boundary scan or JTAG, 438	buffers, 156, 162, 163	Contact bounce, in a mechanical switch, 9
Boundary-scan architecture, 438, 440	circuit, troubleshooting, 71	Contents section, of the program memory, 450
Boundary-scan cells (BSCs), 438, 439	counter, 276–280, 288–289, 290	Continuous rotation, of a stepper motor, 174
Braun ThermaScan ear thermometer, 94	counter ICs, 279	Control and arithmetic units, 447
Breadboard wiring, of a free-running clock, 11, 12	devices, 162–163	Control block, in a UART, 460
BS (backspace), 202 BS2 microcontroller module, 406	digital circuits, 16 digital ICs, 65, 66	Control bus, 362 Control devices, microcontrollers as, 474
Buffer memory, printer's, 460	driving an LCD display, 218–219	Control functions
Buffer register, 305	image sensors, 486	of digital systems, 403, 404
Buffers. See Three-state buffers	inverters, 142, 143	performing by microcomputers, 473
Bulk storage devices, 362	logic gates, 65-69	Control input, extra, 49
Bus, 362	noise margin better for, 145	Control register, 466, 467
Bus systems, buffer/driver used with, 49	power dissipation of, 149	Control section
Buzzers, interfacing with, 164	quadruple two-input AND gate IC, 66	of boundary-scan architecture, 438
Byte, 38	RAMs, 381	of a computer, 446
	shift registers, 315 SRAM, 381	Control sequences for sample bipolar stepper motors, 172, 174
С	TMS47C512 TOM, 374	used by the MC3479 IC, 176
C, in a core part number, 65	XOR gates, 214, 215	Conversion options, for a logic converter, 108–109
Cache memory, in microprocessors, 364	CMOS ICs, 62, 150–151	Conversion time, of an A/D converter, 517
Cadmium sulfide photocell, 520	advantages of, 150	Core part number, internal letters in, 65
Calculator	caution against static charges, 68	Corrosion, on metal surfaces, 530
binary, 331	damaged by static charges, 66	Count accumulator section, of a clock, 412
commercial, 37	disadvantages of, 150	Count or sampling time, 425
compared to a computer, 446	families of compatible, 66 handling, 150	Count pulse, 420, 421 Count/display waveform, 423
keys on, 152	interfacing with TTL, 160–163	Count-display-reset procedure, repeating, 421
pocket, 31	storing, 150	Counter stop line, 429
scientific, 37 shift register in, 305	subfamilies, 67–68	Counter subsystem, 414
Calculator chips, 406	with a "T" designator, 142	Counter system, using optical encoding, 286
Carry input, 333	CMOS-to-LED interfacing, 156	Counterclockwise (CCW) rotation, 172, 174
Carry out, 332	Code conversions, with software, 33	Counter-ramp A/D converter, 508
Cascaded decade counters, 280	Code converter, 370	Counters
Cascading adders, 340, 342	Codes, converting from several, 229 Coefficients, 485	described, 262
Cascading comparators, 288, 290	Collector of electrons, in the triode tube, 221	formed by flip-flops, 236 as frequency dividers, 270–271
Cascading counter, 283	Color LCDs, 215–217	as heart of a digital system, 412
Cathode (K), 221 Cathode lead, of an LED, 206, 207	Combinational logic, 90	J-K flip-flop in, 246
Cathode/heater, 221	Combinational logic circuits, 90, 208, 236, 335, 355	troubleshooting, 295-297
Cathode-ray tube (CRT) technology, 215	NAND gates used in wiring, 106	Counting, real-world events, 284-287
CCDs (charged couple devices), 486	using logic gates, 376	Count-up pulse, 294
CD reader drive, 363	Combinational logic designs, PLDs implementing, 121	CPLD (complex programmable logic device), 116
CD4081BE CMOS quad two-input AND gate IC, 66	Combinational logic problems, solving, 90–91, 126	CPU (central processing unit), 5, 330, 362, 406, 446,
CD4081BE part number, 66	Commercial calculators, converting between number systems, 37	448, 449 CR (carriage return), 202
CD-DA (CD digital audio), 363	Commercial frequency counters, 425	CRC-8 system, 463
CD-Es, 392 CD-R (compact disc recordable), 363, 390, 391–392	Commercial grade, 63	CRC-16 system, 463
CD-ROM (compact disc read-only memory), 363,	Commercial LCDs, 214-215, 216	CRC-32 system, 463
390, 391	Commercial monochrome LCDs, 215, 216	CUPL software, 116
CD-RW (CD rewritable), 363, 392	Commercial ROMs, in DIP form, 372, 374	Current sinking, 156–157, 158
CDs (compact discs), 363, 390	Commercial vacuum fluorescent display, 222, 223	Current sourcing, 156–157, 158
CdS photocell, 520	Common cathode form, 207	CW rotation, 172, 174
CdS photoresistive cell, 488, 490	Common-anode seven-segment LED display, 207 Communications, in orbit, 70	Cycles, displaying, 21 Cyclic redundancy check (CRC), 462–463
Central processing unit (CPU), 5, 330, 362, 406, 446,	Compact data storage, 339	Cylinders, number of, 389
448, 449 Centronics standard, 461	Compact low-voltage ICs, 68	Cymiato, namos or, 507
Charged coupled device (CCD), 486	Comparator, 507–508	
Cheetah hard disk drive, by Seagate, 388	Complement, of actual memory contents, 367	
Chip select control input, 370	Complementary metal-oxide semiconductor (CMOS).	D flip-flops, 241–243, 308
Circuit board, 439	See CMOS (complementary metal-oxide	delaying data, 242
Circuit resistance, 6	semiconductor)	serial-load shift register using, 307
Circuit simulation software, 92, 94–98	Complementary outputs, 13, 236 Complementary symmetry metal-oxide semiconductor	use of eight with parallel data outputs, 315
Circuits, constructing from Boolean expressions, 91–92	(CMOS) devices, 150	used to latch data, 248 wiring, 242
2 L 2 M	, , , , , , , , , , , , , , , , , , , ,	

D latch symbol, 249, 250	Digital computers	Divide-by-6 counter, 423
D/A converter (digital-to-analog converter),	as backbone of the Internet, 7	Divide-by-10 counter, 270, 423
483, 499, 500–501	functional sections, 445–446	Divide-by-60 counter circuit, 270, 271, 413, 414
circuit, 503	Digital device, operating with a digital signal, 2	Divide-by-60 frequency divider, 413, 414
parts of, 501	Digital dice game, simple, 407, 408	Divide-by-256-counter block, 427
sections of, 502–503	Digital electronic equipment, codes used in, 196	DM7408N part number, 63
truth table for, 500, 504	Digital electronic timer system, 427, 428	DMM (digital multimeter), using a modern LCD,
	Digital electronics, applications of, 8	213, 214
truth tables, 506		
Dark burned areas, reflecting less light, 392	Digital frequency counter	Double inverting, effect of, 48
DAT (digital audiotape), 393	block diagram of, 419, 420	Double-word, 38
Data	experimental, 422	Down counters, 267–268, 269, 427, 429
ability to store, 361	more detailed block diagram of, 421	Down position, switch in, 63
to be acted on by a computer, 446	Digital games, 407–411	Drain supply, in MOSFET, 151
sent over a single wire in serial form, 457	Digital ICs	DRAM (dynamic random-access memory), 364, 366
Data bus, 362, 448	CMOS technology used in, 151	Drive capabilities, of digital ICs, 146-148
Data flip-flops, 242	data manuals from manufacturers, 65	Drive current, supplying greater at its output, 48
	low-cost reliable, 7	DS1620, in conjunction with a microcontroller, 524
Data inputs, 112, 367	specifications of, 146	DS1804 NV trimmer potentiometer IC, 394–395, 396
Data links, 460		
Data memory, 448, 474, 485	Digital light meter, 520–521	DSL (digital subscriber line), 449
Data selectors, 112, 113–114, 458	Digital light meter circuit, 522	DSP
Data transfer rate, of a CD-ROM drive, 390	Digital logic pulser, 295	architecture of, 484, 485
Data transmission, 457–461	Digital measuring device, 2–3	in a digital camera, 486–487
in a computer system, 464-468	Digital multimeter (DMM), 2–3	DT-1000 digital trainer board, 14
examples of, 460, 465-468	Digital potentiometer, 394–397	D-type latches, 243
Data transmissions, detecting errors in, 461–463	Digital roulette, using shift registers, 318–323	Dual circuitry, advantages and limitations, 7
Data-enabled mode, for 7475 latch IC, 248	Digital roulette wheel, 318, 322	Dual in-line package (DIP), 62-63, 205, 384,
Data-latched mode, for 7475 latch IC, 248	Digital roulette wheel circuit, 321	385, 474
	Digital signal processing (DSP), 482–485, 486–487	DVD (digital versatile disc), 363
DB9 connector, 478, 479		
DB-1000 display board, 14	Digital signal processor (DSP), 483	DVD+RW (digital versatile disc rewritable), 390
Dc motor, noncontact operation of, 436	Digital signals, 2–3	DVD-audio, 363
Dc voltage, across nematic fluid destroying LCDs, 214	displayed on scope, 2	DVD-R (digital versatile disc recordable), 390
De Morgan, Augustus, 126	engine control module sending, 6	DVD-RAM, 363, 392
De Morgan's theorems, 61, 124–128	generating, 2, 9–14	DVD-ROM (digital versatile disc read-only memory),
Debounced logic switch, block diagram of, 9	testing for, 15–18	363, 390–391
Debounced switches, 11–12, 153	waveform, 2	DVD-ROM drives, data transfer rate, 391
Debouncing circuit	Digital subscriber line (DSL), 449	DVD-RW (digital versatile disc rewritable),
adding, 11	Digital systems	390, 392
	elements of, 403–404, 405	DVD-video (digital video disc), 363
eliminating switch bounce, 12		
lack of, 153	on ICs, 406	DVI (digital visual interface) port, 464
use of, 9	inputs and outputs from, 284	DVI-A, 464
Decade counter, 264, 270, 271	measuring amount of liquid in a water tank, 5	DVI-D, 464
Decade down counter, 74192 IC wired as, 275	requirements for, 5	Dynamic RAM IC, 368
Decimal multiplication, compared to binary	using encoders, 204–205	
multiplication, 343–344	Digital timepieces, frequency dividers in, 270	E
Decimal number system, 27, 28, 29	Digital trainer, used during lab sessions, 14	EBCDIC (extended, binary-coded decimal interchange
Decimal numbers	Digital versatile disc (DVD), 363	code), 202
converting from, 229	Digital voltmeter, 510-512	**
converting to BCD numbers, 375	Digital waveform, providing, 9	ECL (emitter-coupled logic), 149
		EDE1200 unipolar stepper motor IC, 176
converting to binary, 30-31	Digital-to-analog (D/A) converter. See D/A converter	Edge-triggered flip-flops, 249
converting to binary, 30-31 converting to hexadecimal, 35	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter)	
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487	Edge-triggered flip-flops, 249
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read-
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable read- only memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display driver, 207	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostal
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display driver, 207	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit xOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostar IC, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167 Electronic circuit simulators, running on a PC
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensing, simple, 432–437	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit xOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167 Electronic circuit simulators, running on a PC (personal computer), 108
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Displays time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensing, simple, 432–437 Distance sensor	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit xOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3 Digital circuitry, 1, 3	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display time, 425 DisplayPort digital display interface, 464 Distance sensing, simple, 432–437 Distance sensor noncontact operation with, 435–437	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary numbers and from binary to decimal, 31
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3 Digital circuits, 2, 4–8 Digital clock, 412–415	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Discrete-time signals, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensor noncontact operation with, 435–437 testing, 434	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary numbers and from binary to decimal, 31 Electronic dice simulation game, explaining logic and
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3 Digital circuits, 2, 4–8 Digital clock, 412–415 block diagram of, 413, 419	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensing, simple, 432–437 Distance sensor noncontact operation with, 435–437 testing, 434 using for noncontact operation of a stepper	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostar IC, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary numbers and from binary to decimal, 31 Electronic dice simulation game, explaining logic and output sections of, 409, 411
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3 Digital circuitry, 1, 3 Digital circuitry, 2, 4–8 Digital clock, 412–415 block diagram of, 413, 419 chips, 415	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display driver, 207 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display prot digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensior, simple, 432–437 Distance sensor noncontact operation with, 435–437 testing, 434 using for noncontact operation of a stepper motor, 435	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostatic, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary numbers and from binary to decimal, 31 Electronic dice simulation game, explaining logic and
converting to binary, 30–31 converting to hexadecimal, 35 converting to octal, 36 having 2s complements same as binary, 350 Decimal-output A/D converters, 516, 517 Decimal-to-binary conversion, 196–197 Decimal-to-binary encoder circuit, 41 Decode (verb), defined, 32 Decoder/driver, 429 Decoders, 31, 32–33, 196, 208–209, 458, 499 Decoding, 196, 412 Decoding circuit, troubleshooting, 227–228 DEL (delete), 202 Delay flip-flop, 241, 242, 308 Delay period, adjusting, 12, 155 Demultiplexers (DEMUXs), 457 Dependency notation, 72 Development software, for PLDs, 116 Dice simulation, more realistic, 407, 409–411 Digital audiotape (DAT), 393 Digital cameras compressing digital images, 487 DSP in, 486–487 solid-state drives, 363–364 using flash memory cards, 363 Digital circuitry, 1, 3 Digital circuits, 2, 4–8 Digital clock, 412–415 block diagram of, 413, 419	Digital-to-analog (D/A) converter. See D/A converter (digital-to-analog converter) Digital-to-analog conversion block, 487 Digitizing, 523 temperature, 523–524 Digitizing process, faster for successive-approximation A/D converter, 515 DIMM (dual in-line memory module), 385, 386 Diode ROM matrix, pattern of diodes in, 372, 373 Diode ROMs, disadvantages of, 372 DIP (dual in-line package), 62–63, 205, 384, 385, 474 Discrete points, in time, 483 Disk drive, electromagnetic device, 387 Display, seven segments of, 205 Display blanking, during the count time, 425 Display clock, 429 Display multiplexer circuit, 280 Display multiplexer section, of the 4553 IC, 293, 294 Display multiplexer section, of the 4553 IC, 293, 294 Display technologies, 206 Display time, 425 DisplayPort digital display interface, 464 Displays, multiplexing, 294, 416 Distance sensing, simple, 432–437 Distance sensor noncontact operation with, 435–437 testing, 434 using for noncontact operation of a stepper	Edge-triggered flip-flops, 249 EEPROM (electrically erasable programmable readonly memory), 364, 377–378, 477 memory cells, 392 program memory, 77, 80 Egyptians, soldering developed by, 530 EIA RS-232C standard, 461 8-bit 2s complement addition problems, 351, 352 of a number, 350 subtraction problems, 351, 352 8-bit binary adder, 340 8-bit CMOS shift register, 315–317 8-bit parallel-load shift-right register, 314–315 8-bit register, 237, 305 8-bit XOR gate, 462 8-bit-magnitude comparator, 429 8-pin DIP DS1620 digital thermometer and thermostar IC, 524 8255 PPI (programmable peripheral interface), 460 8421 BCD code, 197, 229 8421 code, most widely used BCD code, 198 Electromechanical relays, 167 Electronic circuit simulators, running on a PC (personal computer), 108 Electronic devices, translating from decimal to binary numbers and from binary to decimal, 31 Electronic dice simulation game, explaining logic and output sections of, 409, 411

552

Electronic engine control, 8	FAST TTL logic series, 147	propagation delays of, 149
Electronic games	Fast-forward set, 413	voltages for, 66
classifying, 407	FCT, in a core part number, 65	voltages up to 18 V, 224
CMOS counter in, 288–289, 290	Feedback resistor, 502	4029 presettable binary/decade up/down counter, 409
constructing, 407	Ferroelectric capacitor, with a MOS transistor, 383	4050 noninverting buffer, 161
Electronic lock, designing, 97	Ferroelectric RAM (FeRAM or FRAM), 382–384	4081B CMOS IC, 66
Electronic roulette wheel, summary of, 319	Fetch-decode-execute sequence, 453, 467	4511 BCD-to-seven-segment decoder IC, digits
Electronic thermometers, 94	Field-effect LCD, 213, 214	generated by, 225, 226
Electronic translators, 31–33	Field-programmable logic arrays (FPLAs), 116, 121	4511 BCD-to-seven-segment latch/decoder/driver
encoders and decoders, 196	Field-programmable ROMs (PROMs), 377	CMOS IC, 224-226
Electronics technicians and engineers, in great	50/50 solder, 530	4511 BCD-to-seven-segment latch/decoder/driver IC
demand, 8	Filament, 221	pin diagram, 225
Electronics Workbench (EWB), 95	Fillet shape, of solder, 534	4553 (MC14553) CMOS three-digit BCD counter,
Elements, of a digital system, 403-404, 405	Filter, purpose of, 486	280–283
ELPD (electrically programmable devices), 116	FireWire, 465	4553 three-digit BCD counter, CLK input of, 293
Emitter-to-collector resistance, of the power	Firmware, 374	40106 CMOS IC, special inverter, 155
transistor, 167	555 timer IC	Four-variable Karnaugh map, 103
Encode (verb), defined, 32	in a clock, 520	Four-wire bipolar stepper motor, test circuit for hand
	switch debouncing circuit using, 155	checking, 174–175
Encoder, 31, 32–33, 196, 499		
Encoder-decoder system, 32–33	triggering, 436	FPGA (field-programmable gate arrays), 116
Encoders and decoders, in digital systems, 204-205	wired as a VCO, 319, 321	FPL (fuse-programmable logic), 116
Encryption, 32, 196	Five-variable Karnaugh map, 105	FPLAs (field-programmable logic arrays), 116, 121
	Five-variable unsimplified Boolean expression, 105	
Engelbart, Douglas, 211		FRAM (ferroelectric RAM), 364, 381
Engine control module (ECM), 6	Fixed angle, 172, 173	Framing-error (FE) flag, 468
Enhancement-mode MOSFETs, 150	Flagged error, 468	Free-running A/D converter, 519
Eniac, 4	Flags, in the status register, 468	Free-running clock circuit, 11
EPROM (electrically programmable read-only	Flash drives, 361	Free-running multivibrator, 10
memory), 364, 380	Flash EEPROMs, 378, 381, 382	Free-running MV, 10
EPROM (erasable programmable read-only memory), 377	Flash memories, 363	Frequency
EPROM family, 378	Flash memory, 361, 364, 381, 382, 387	of input voltage, 21
•		
EPROM window, protecting, 380	Flip-flops, 9, 13, 236	selecting, 19
EPROM/ROM-based 8-bit CMOS microcontroller	constructing latches using, 305	Frequency counter, 419–422
series, 474	memory characteristics, 240, 306, 315	Frequency counter circuit, 74
Epson 40- or 50-pin interface, 387	operating synchronously, 239	Frequency divider section, of a clock, 412, 413
Erasable PLD units, 121	in semiconductor memories, 361	Frequency dividers, counters as, 270–271
Erasable-CDs, 392	traditional and IEEE symbols for, 253	Frequency division, 270–271
Erasing, memory, 371	triggering, 249–250	Fuel gauge system, traditional analog, 6
Error detector circuit, sounding an alarm, 462	uses of, 248	Full adder circuit, 332
Error-correcting codes, 463	Floating inputs	Full adders, 333–334, 355–356
Errors, detecting in data transmission, 461-463	caused by a bent-under pin, 297	Full subtractors, 336, 338
	on CMOS ICs, 71	
Ethernet port, 465		Full-duplex devices, 465
Ethernet protocol, 450	good design practice for, 211	Full-step mode, 176
Euctectic solders, 530	on TTL, 152	Function diagram, 276, 277
Eutectic alloys, 530	Floating output, from a digital circuit, 18	of the 74HC193 IC, 277, 278
Eutectic solder, as preferred choice, 531	Floppy disk drives, 363, 390	Function generator, 19
Even or odd parity bit, transmitted or received, 462	Floppy disk form, 388	Fuse maps, 120
Excess-3 code, 198-199, 229	Floppy disks, 389, 390	Fusible-link PROM, 377
Exclusive NOR gate, 54–55	Flux	
Exclusive OR gate, 53–54	removal of, 534	G
Experimental frequency counter, 423-425	role of, 531–532	GAL (generic array logic), 116, 122
Experimental LCD timer circuit, wiring diagram for,	FOR-NEXT loops, 188	
427, 430–431	Four full adders, use of, 353	Gallium arsenide (GaAs), LEDs fabricated
427, 430–431		from, 207
Experimental tachometer, 291-294	4-bit adders, functioning the same as the	Gallium arsenide (GaAs) infrared-emitting
Experiments Manual for Digital Electronics, 8	7483 IC, 340	diode, 167
External hard disk drives, 363	4-bit binary counter, logic diagram for a 74HC393 IC	
External pulse width, 170	wired as, 279	Gas-discharge tube, 206
		Gate circuits, troubleshooting, 69–71
External storage, 387–388	4-bit counter, 264	Gates
Extest (external test) instruction, for	4-bit electronic counter, counting sequence for, 263	with more than two inputs, 57–59
JTAG-compliant ICs, 439	4-bit microprocessor-based system, 455	
Trio-compilant 100, 100	•	using inverters to convert, 59–62
	4-bit MPU-based system, 454, 455	Gateways, 450
F	4-bit parallel subtractor, 338–339	GB (gigabytes), 38, 363
	4-bit parallel-load recirculating shift register, 309	
F, in a core part number, 65	4-bit ripple counter, 7493 IC as, 272	Gear-tooth sensing ICs, 182–183
FACT (Fairchild Advanced CMOS Technology)	• •	Generator, producing a square waveform, 2
74AC00 series, 66	4-bit shift register, 307	Geostationary earth orbit (GEO), 70
FACT (Fairchild Advanced CMOS Technology)	4-digit BCD counter, 291	Gigabytes (GB), 38, 363
•	Four-input AND gate, wiring, 58	
CMOS ICs	Four-input NAND circuit, schematic diagram of, 185	GND connection, 151
designed to outperform existing CMOS and most		Graph form, analog and digital signals
bipolar logic families, 151	Four-input NAND gate, wiring, 59	representing, 2
interfacing with other families, 162	Four-input NOR gate, 423	Gray, Frank, 199
	Four-input OR gate, wiring using two-input	
logic series, 67, 151	OR gates, 58–59	Gray code, 27
more tolerant of static discharge, 150		converting from, 229
output drive capabilities, 161, 162	4N25 optoisolator, 167	numbers from 0 to 15, 370
outstanding output drive capabilities of, 147	Four-phase stepper motors, 176	
	14-pin DIP IC, 62	programming into the 7489 RAM, 370
rivaling the best TTL ICs in low propagation delays,		used for input and output devices in digital
149	4000 series, 151	systems, 199
Families, of digital ICs, 62	4000 series CMOS devices, interfacing with simple	Gray code-to-binary decoder, 200
	LED indicator lamps, 156, 157	
Fan-in, of a family of ICs, 147	4000 series CMOS ICs, 66, 142, 143, 155	Green, human eye more sensitive to, 487
Fan-out, of a digital IC, 146		Grid (G), 221
Fast set, 416	fan-out for low-power, 146	Guess the number computer game, 288

Н	Idle mode, in clocked R-S flip-flops, 239	Interpolation, 487
H, in a core part number, 65	IEEE logic symbols, 72–73, 252–253	Invalid BCD inputs, generating unique outputs on the
H21A1 optocoupled interrupter module (slot type),	IEEE-488 standard, 461	7447A decoder, 211
285	IEEE-1149.1 standard, 438	Invert bubbles, 50, 51
	IFL (integrated fuse logic), 116	added to the inputs of the OR gate, 61
Half adders, 332, 334	IGFETs (insulated-gate field-effect transistors), 62	at the input of the AND gate, 61
Half subtractors, 336	Image capture section, of a digital camera, 486	on the left side of the inverter symbol, 48, 49
Half-adder circuit, 332	Incandescent display, 206	at the R and S inputs, 237
Half-byte, 38		•
Half-step mode, 176	Incandescent lamp, interfacing, 159	replaced with a right triangle on IEEE symbols, 73
Hall, E. F., 179	Inclusive OR function, 46	Inverted AND function, 50
Hall effect, 179	Information, put into a computer, 446	Inverted binary form, 254
Hall voltage, proportional to the strength of the	Information revolution, 361	Inverter logic function, substituting NAND gates, 56
magnetic field, 178	Infrared light, optocoupled interrupter module	Inverters, 48
	using, 287	adding to a logic symbol, 61
Hall-effect sensors, 178–184	Infrared-emitting diode, 169, 287	adding to the output of the AND gate, 61
basic, 178–179	Infrared-light distance sensor, 432, 433	attached to the inputs of the OR symbol, 61
with a dc amplifier and voltage regulator, 179	<u> </u>	
input pulses from, 291	Inhibit mode, 74194 shift register, 311, 312	complementing or inverting the input, 48
Hall-effect switch (3141 IC), 293	Initial wiper position, stored in nonvolatile	truth table for, 48
Hall-effect switch IC, 182	EEPROM, 395	using at the inputs and outputs, 62
Hall-effect switches, 179-182, 184	Input	using to convert gates, 59–62
Hamming code, 463	of a digital system, 403, 404	Inverting
Handshaking line, 460	inverting, 59–60	4-bit binary number, 32
	provided by a simple SPDT switch, 15	CMOS buffer, 156
Hard disk drives (HDDs), 363, 448	Input and feedback resistors, 502	outputs of the AND gate, 50
Hard disks, 388–389, 393	Input controls, 426, 427	Inverting input, to an op amp, 501
Hard drives, 363		
Hard logic, using traditional ICs, 90–91	Input devices	IR detector (phototransistor), 432
Hardware	to computers, 445	IR LED, emitting pulses of infrared light, 432
encoding and decoding performed by, 31	connected to microcomputers, 448	
needed to program the BASIC Stamp	for PLCs, 469	J
Microcontroller Module, 77, 78	Input loading characteristics, of several families	J-K flip-flops, 243–247
Hayes, Dennis C., 447	of digital ICs, 147	* * *
	Input resistor, 502	shift register using four, 309
Hayes Microcomputer Products, Inc., 447	Input shaft, speed of rotation of, 294	in toggle mode or hold mode, 267
Hayes Smartmodem, 447	Input signals, 15, 21	J-K master/slave flip-flop, 250
HC, in a core part number, 65		Joint, controlling heat at, 532–533
HCT, in a core part number, 65	Input switch	Joint Test Action Group (JTAG), 438
Heart cycle, controlling, 532	of BS2 module, 481	JPEG (Joint Photographic Experts Group), 487
Heat rate recognition, 533	with a debouncing circuit, 11	JTAG-compliant ICs, 438, 440
Heat reservoir, replenished by the heating	Input unit, 447	,,,
element, 532–533	Input voltage range, 517	17
Heater, 221	Input waveforms, 237, 238	K
	Input/output peripheral device, 449	Karnaugh, Maurice, 100
Heavy-duty computer system, designed for machine	Input-store-output procedure, 450–451	Karnaugh map (K map)
control, 469		considering as a vertical cylinder, 104
Hexadecimal equivalents, to decimal numbers, 35	Installation, of a typical DIMM, 385, 386	filled in, 100
Hexadecimal notation, representing a binary	Institute for Electrical and Electronic Engineers	five-variable, 105–106
number, 34	(IEEE). See IEE specific entries	forming four corners into a ball, 105
Hexadecimal number system, 27, 34	Instruction register, 438, 452	
Hexadecimal numbers, 34–35	Instruction set, for a specific PLC, 470	with four variables, 103
HIGH input, 66–67, 142	Instruments	more sample, 104–105
	simple, 19–21	simplifying a Boolean expression from, 101
HIGH input input, 141	used in the lab, 8	with three variables, 101–102
HIGH logic level, for a CMOS inverter, 142, 143	Insulated-gate field-effect transistors (IGFETs), 62	Keyboard, entering information, 152
HIGH output, 53, 142		Keyboard port, 464
HIGH voltage, 2, 16, 37, 44	Integrated circuits (ICs)	Keyboard versions, of Boolean expressions, 95, 124
High-capacity DVD versions, of the CD-RW, 392	containing entire digital systems, 406	Kilobytes, of storage, 38
High-impedance state, buffer outputs in, 454	digital electronic signals generated and processed	Kilobytes, of storage, 50
High-impedance state (high-Z state), 49	by, 2	
High-reliability soldering, 530	interfacing between TTL and CMOS devices, 142	L
High-speed CMOS (HC), 67	manufacturers producing encoders and decoders, 32	L, in a core part number, 65
Hobby servo motor. See Servo motor	packaging, 62-63, 66	Label, in PBASIC, 79, 128
	part numbers, 63, 65	Ladder logic diagram, graphic programming language
Hold condition, for the flip-flop, 237	from the same logic family interfacing properly, 141	470
Hold input, 416	troubleshooting, 71	Ladder-type D/A converters, 504–505
Hold mode, 239, 243, 244, 267	used to construct digital circuits, 43	
Hollerith, Herman, 388		LANs (local area networks), 449-450
Hollerith card code, 202, 388	wiring, 63, 64, 66–67	Laptop computers, 4
HomeWork board, 479	Integrated fuse logic (IFL), 116	Large-scale integration digital voltmeter chips, 512
Horizontal sweep time knob, on a scope, 20	Intel 4004 4-bit microprocessor, 37	Large-scale integration (LSI), 406
Hybrid electronic system, 512	Interconnections (nets), checking, 440	Laser narrow light beam, for distance sensing, 432
Hybrid hard disk drive (H-HDD), 388, 393	Interface devices, 499	Latch/decoder/driver, 426, 427
	Interfacing	Latched encoder-decoder system, 254-256
Hybrid RAM disks, 388	analog devices to digital systems, 499	Latch-enable circuitry, 254
Hybrid system, 499	with buzzers, 164	Latch-enable pulse, 254
Hysteresis, 251, 523	defined, 141	Latches, 154, 236, 237, 247, 305
1	with servo and stepper motors, 170–177	available in all logic families, 248
IC adders, 340-342	TTL and CMOS ICs, 160–163	flip-flops, 9
IC forms, of MV circuits, 11	TTL and CMOS with LEDs, 156–159	groups of, 237
IC latches, 247–248	TTL and CMOS with switches, 152-155	in IC form, 248
IC programmer, burning open selected fuses, 118	using relays, 165, 166	transparent, 283
ICL7106 3½-digit A/D converters, 512	Internal short circuit, of a chip, 228	LCD decoder/driver system, 218, 219
ICL7100 392-digit A/D converters, 512	Internet, 7, 449	LCD displays, CMOS driving, 218-219
	Internet servers, 363	LCD timer, with alarm, 426–429, 430–432
ICs. See Integrated circuits (ICs)		

LCDs, driving, 214, 215	Looping cylinder, 106	Memory units, 447
Lead (Pb), melting point of pure, 530 Lead mass, variations in, 532	LOW, HIGH, LOW, HIGH waveform, 9, 10 LOW input, 66, 141, 142	Metal-oxide semiconductor circuits, 150 Metal-oxide semiconductor field-effect transistor
Lead-free solder joints, inherently dull and grainy, 531	LOW logic level, for a typical CMOS inverter,	(MOSFET), 150
Lead-free solders, mandated for many manufacturing	142, 143	Metal-oxide semiconductor (MOS) technology,
and repair procedures, 530	LOW voltage, 2, 16, 37, 44	62, 150
Leading zeros, blanking, 211-212	Low-cost PALs, with fusible links, 122	Microchip Technology, family of microcontrollers, 474
Least significant bit (LSB), 197, 262	Low-earth orbit (LEO), satellites in, 70	Microcomputer, 447–450
Least significant digit (LSD), 35, 262	Lower-voltage 3-V chips (ICs), 68	address, decoding, 454–457
LED (light-emitting diode), 15, 156, 206–207	Lower-voltage ICs, 68–69	keyboard on, 152
compared to LCD, 213 flashing on and off, 479	Low-power Schottky (LS), 63 Low-voltage CMOS IC, 143, 144	operations, 450–454 ROM, 448
interfacing TTL and CMOS with, 156–159	Low-voltage civios 1c, 145, 144 Low-voltage digital ICs, subfamilies, 69	Microcontrollers, 330, 406, 451, 473–475
interfacing using a transistor driver circuit, 158	LS, in a core part number, 65	digital inputs, 516
as number markers, 318	LSB (rightmost digit), 330	family of, 474–475
as output indicator, 44	LSI chips, examples of, 406	responding to a variety of inputs, 481
with a series-limiting resistor, 16	LSI digital clock, 415–418	Microprocessor-based systems, hexadecimal notation
LED 1 program, 481, 482	LS-TTL, driving any CMOS gate, 160	widely used in, 34
LED output indicators, 16, 159	LS-TTL gates, fan-out of, 148	Microprocessors, 330, 406, 447. See also MPU microcontrollers compared to, 473–474
LF (line feed), 202 Light-dependent resistor (LDR), 520	Ν.Α	multiplication and, 348
Limit switches (LS), connected in parallel and in	Mahina languaga dagadian ta daginal ayanbara	Military, advanced electronics training programs, 8
series, 471–472	Machine language, decoding to decimal numbers, 205–206	Millions of instructions per second (MIPS), 484
Linear thermal sensors, 524	Machine-control language, for PLCs, 470	Minterm Boolean expression
Liquid-crystal displays (LCDs), 206, 213-217	Magnetic bulk storage devices, 388	constructing a truth table from, 94
Load mode, 74194 shift register, 311, 312	Magnetic devices, 388	forming for the electronic lock circuit, 97
Logic circuits	Magnetic disks, 388	Minterm expressions, creating AND-OR logic
drawing from a maxterm Boolean expression,	Magnetic domains, in metal-oxide surface, 363	circuits, 93 Minterm form, 91–92
92–93 groups of, 236	Magnetic drum memory units, 388	Minterm-to-maxterm form, converting, 124
for the parity bit generator, 462	Magnetic field, characteristics of, 180	MM5314 digital clock IC, functional description of,
troubleshooting simple, 185–186	Magnetic random-access memory (MRAM), 364, 384 Magnetic storage, 363	416, 418
Logic converter, 95, 108	Magnetic tape, 388	MM5314 MOS LSI clock IC, block diagram of,
Logic converter instrument, 95, 97-98	Magnetic tunnel junction (MTJ) structure, 384	416, 417
Logic converter software, 98	Magnetically activated sensors or switches, 178	Mod-6 counter, 270
Logic diagrams	Magnetoresistive RAM (MRAM), 364, 384	74HC193 CMOS IC as, 279
of the 74194 shift register, 311, 312	Magnitude comparator, 288, 426, 427	Mod-8 asynchronous down counter, logic diagram of,
for a full adder, 333, 334 Logic families, availability of, 141	Mainframe computer, 4	267–268 Mod-10 ripple counters, 264–265
Logic functions, 43, 45	Mask-programmed ROM, 372, 377	Mod-16 counter, 262–263
programming, 80–81	Master reset input	Mod-16 ripple counter, 272
using software, 77–81	to the 74HC164 IC, 315, 316 to the 74HC164 register, 320	Mod-B counter, 7493 IC wired as, 275
Logic gates, 43, 44, 45, 236	Master reset mode, of operation, 283	Mode control inputs, 313
applications, 73–77	Master/slave triggering, obsolete, 250	Modem (modulator/demodulator), 449
combining, 90–130	Master/slave type, of flip-flop triggering, 250	Modulo-16 (mod-16) counter, 262
summary of basic, 82 symbols, 72	Maximum frequency, increasing, 421	Modulus, of a counter, 262 Molecules, magnetizing single, 339
Logic levels	Maximum power dissipation, 517	Monochrome LCD, 213–214
CMOS logic families, 142–143	Maxterm Boolean expression, drawing a circuit from,	Monostable multivibrator, 10, 12–14
in graphic form, 16	92–93 Maxterm expressions, 93, 125	Monostable MV, 237
low-voltage CMOS, 143-144	Maxterm form, 92	MOS ICs, 150
TTL logic family, 141–142	Maxterm-to-minterm Boolean expression, converting,	MOS LSI chip, 415
Logic probe, 17, 19–20, 185–186	124	MOS LSI clock IC packaged in a 24-pin DIP, 415, 416
Logic problems, solving using data selectors, 113–114	Maxwell 36- or 38-pin interface, 387	Most significant bit (MSB), 262
Logic switches, using in the laboratory, 10 Logic symbol	MC3479 stepper motor driver IC, 175–176	Most significant digit (MSD), 37, 262 Mouse port, 464
for a clocked R-S flip-flop, 239	Mechanical bulk storage devices, 388	MPU, 452, 453. See also Microprocessors
for commercial D flip-flop, 242	Mechanical devices, 388 Mechanical switches, debouncing, 9	MPU IC, 447–448
common alternative, 61	Medical field, devices in, 277	MPU-based systems, 453, 454
for the D flip-flop, 241	Medium-earth orbit (MEO), satellites in, 70	MRAM (magnetoresistive RAM or magnetic
for a D flip-flop using negative-edged triggering,	Medium-scale integration (MSI), 406	RAM), 364, 384
249, 250	Megabytes, of storage, 38	MSB (leftmost digit), 330
for a D flip-flop with positive-edge triggering, 249,	Memory	MSBs, of positive 2s complement numbers, 348, 349
250 for the OR gate, 46	erasing, 371	μP-type A/D converters, 516 Multidigit LED display, 206
for the inverter (NOT circuit), 48	organization of, 365	Multiple bit errors, checking during transmission, 462
for J-K flip-flop, 243, 244	overview of, 362–364 reading from, 362	Multiplex divider/decoder, 416
for the NOR gate, 51, 52	writing in, 362	Multiplex oscillator, 416, 418
showing the AND gate, 43, 44	Memory cards, 363, 386	Multiplexer section, inside the 4553 IC, 283
for three-state buffer, 49	Memory characteristic, of the clocked R-S	Multiplexers (MUXs), 114, 457
for the XNOR gate, 54	flip-flop, 240	Multiplicand, 343
Logic symbol diagram, for a half adder, 332	Memory devices	Multiplication
Logical ANDing, ways to express, 45 Logical NANDing, expressing, 50	in computers, 362–363	with binary numbers, 344 process of, 343
Logical NORing, expressing, 50 Logical NORing, ways to express, 52	formed by flip-flops, 236	Multiplication dot (·), symbolizing the AND
Logical ORing of two variables, 46	needed to hold BCD code, 247 Memory enable input, 367	function, 45
Logical XNORing, of three variables, 55	Memory map, of an MPU-based system, 455–456	Multiplication problem, sample, 344
Long overbar, 61	Memory packaging, evolution of, 384–387	Multiplier, 343, 485
Looping, on a Karnaugh map, 100	Memory section, of a computer, 445	Multiplying and accumulating, process of, 484

Multisim logic converter 05	Ohm's law, o	P
Multisim logic converter, 95 Multivibrators (MVs)		P register, 485
	On-board diagnostics system (OBD I or OBD II), 178	PAL (programmable array logic), 116
circuits, 10–11	On-chip clock generator, 519	PAL10H8, 121-122
types of, 237	1-of-8 data selector, 112	PAL12H10 IC, 117
MUX, working like a single-pole, many-position	1-of-10 decoder (7442 TTL IC), 372	PAL/GAL IC part identification guidelines, 122
rotary switch, 458	1-of-16 data selector, 114	Panasonic 34-pin interface, 387
	1-second timer system, 270	Paper tape, perforated, 388
N	100s display, 294	Parallel adder, 335, 338
NAND Boolean expression, methods of writing, 51	112-bit memory, 376	Parallel data, changing into serial data, 457
NAND function, 50, 51	112-bit ROM, 375, 376	Parallel in-parallel out register, 306, 310
NAND gates, 50-51	184-pin DDR SDRAM (double data rate synchronous	Parallel in-parallel out storage device, 310
forming an R-S flip-flop, 237	DRAM), 385	Parallel in-serial out shift register, 306
resetting a counter, 264	184-pin RDRAM (Rambus DRAM), 385–386	Parallel in-serial out storage device, 310
steps involving, 107	One-package solution, to a complicated logic	Parallel interfaces, 460, 461
truth table, 50	problem, 112	Parallel loading, of four bits at once, 308
two-input, 272, 273	One-shot multivibrator circuit, push button	Parallel port, 464
unique output from, 51	connected to, 10	Parallel subtractors, 338–339
as universal gates, 56, 106	One-shot multivibrator (MV), wiring, 12–14	Parallel wires, sending bits in each word at
widely available, 56	1000s display, 294	one time, 457
wired as an R-S latch, 320	One-time programming (OTP), of a chip, 397	Parallel-load shift registers, 308-310
wiring to create any of the other basic	Open-collector NAND TTL IC, 155	Parallel-load shift-right/left register, 313-314
logic functions, 56	Open-collector outputs, of 7489 RAM, 367	Parity bit, 461, 462
NAND logic, using, 106–107	Operand, 451	Parity bit generator circuit, 461-462
NAND logic function, 50, 61	Operation, 451	Parity error bit, of the status register, 468
NAND-NAND logic circuit, 107, 109, 111	Operational amplifier (op amp), 501-502, 508	Parity error (PE) flag, 468
Nanotube RAM (NRAM), 384	Optical disc drive, 448	Partial products, 344
National Semiconductor (NS), 63	Optical discs, 389–392, 393	Passive-matrix LCDs, 216
Natural phenomena, analog in nature, 4–5	Optical encoder/counter system, incrementing the	Past solders, 530
Negated input, 48	count, 287	PBASIC (Parallax BASIC) editor program, 475
Negative decimal number, 348–349, 351	Optical encoding	PBASIC 1 interpreter, in firmware, 477
Negative GND (black lead), 17	for input, 284–285	PBASIC blink program, 479
Negative temperature coefficient, of thermistors, 523	of a shaft's angular position, 199-200	PBASIC editor, in MS Windows, 479
Negative-edge triggering, 74LS112 flip-flop using, 244	Optical read/write CDs, 363	PBASIC high-level language, 77
Negative-edge-triggered flip-flop, toggling, 249	Optical sensors, 285, 287	PBASIC interpreter software, 475, 477
Nematic fluid, 213	Optical storage, 363	PBASIC programs
Nibble, 38	Optocoupled interrupter module, 285	2-input AND function, 78, 79–80
NMOS (N-channel MOS), 150	Optocoupler, 167	downloading, 128, 477, 480
NMOS devices, interfacing with CMOS, 161	Optoisloators, 167–169	ServoTest 1, 187–188
No inversion, flowing through a gate with, 353	OR (XOR) logic function, 81	PBASIC text editor program, loading, 78, 128
Noise, 7, 145	OR function	PC boards, loss of test point access on, 438
Noise immunity, 144, 151	in PBASIC, 80	P-channel MOSFET, 150
Noise margin, 144–145	summary of, 46, 47	PCMCIA 88-pin interface, 387
NOMAD Personal Display System, 317	OR gate, 46-47	PCMCIA card, 386–387
Noninverting buffer/driver, 48, 49	inverting to a NAND function, 61	PCMCIA device, containing flash memory, 387
Noninverting CMOS buffer, 156	truth table, 46	PEEL (programmable electrically erasable logic), 116
Noninverting input, to an op amp, 501	OR logic function, substituting NAND gates, 56	Pencil-type solder iron and tips, 533
Nonlinear temperature-vsresistance characteristic,	OR symbol	Peripheral devices, 446, 448, 449
of a thermistor, 524	as another symbol for a NAND gate, 107	Peripheral interface adapter (PIA), 460
Nonvolatile memories, 372	with a small invert bubble, 51	Permanent magnet rotor, 172, 173
Nonvolatile RAM (NVRAM), 362	Organization, of a very tiny microcomputer system,	Personal Computer Memory Card International
Nonvolatile read/write memories, 381	447–448	Association (PCMCIA), 386
and the second s	Oscilloscope, 2, 20–21	Personal computers, 4
Nonvolatile static RAM (NVSRAM), 381 Nonvolatile storage devices, 366	Out-of-phase signals, 218	Petruzella, Frank, 470
NOR Boolean expression, alternative methods of writing, 52	Output	Phase-change alloy, 392
	of A/D converters, 516	Phase-change technology, 392
NOR gate, 51–52	of a digital system, 403, 404	Photocell, 488, 490
NOR logic function, 56	from a PLC driving motors and solenoids, 469	Photodiodes, 486
NOR truth table, 52 Normal circuit, truth tables defining response of,	Output devices, 19, 164	Photoresistive cell, 520
355–356	Output drive characteristics, of several families of	Photoresistor, 520
Normal output, 13, 236	digital ICs, 147	Phototransistor, activating, 167, 287
North pole, of a magnet, 182	Output drive currents, for the standard TTL, 160	Phototransistor detector, 167
NOT AND, 50	Output indicator, 15, 16	PIC16C55 microcontroller, 475, 476
NOT AND, 50 NOT circuit, 48	Output logic levels, 517	PIC16C56 microcontroller chip, 477
NOT OR gate, 51–52	Output peripheral devices, 448	PIC16C57 microcontroller, 404, 405
NOT OK gate, 31–32 NOT symbol, alternative, 48	Output section, of a computer, 446	PIC16C57 microcontroller chip, PBASIC 2 interpreter
Notation system, used with PLDs, 119	Output unit, 447	in firmware, 77, 477
· · · · · · · · · · · · · · · · · · ·	Output voltages	PIC16CSX family of microcontrollers, specifications
NOVRAM (nonvolatile RAM), 381 NPN phototransistor, 285	calculating for op amps, 503	for, 474–475, 476
NPN transistor, driving an LED, 16	for CMOS ICs, 142, 143	Piezo buzzer, 164
	selecting, 19	Pilot lamp (PL), controlling, 471
Numbers, adding in binary, 330–331	Output waveforms, 237, 238	Pin configuration, of the 74194 shift register,
NVRAM (nonvolatile RAM), 381	Outputs	311, 312
NVSRAM (nonvolatile static RAM), 381–382	of digital circuits, 15	Pin descriptions, 74HC164 shift register, 316, 317
5	inverting, 59, 60	Pin diagrams, 63
	Overbar (-) symbol, above the output, 48	74HC164 shift register, 316, 317
Octal number system, 27, 36	Overflow (OF) flag, 468	74HC393 IC, 277
Octal numbers, 36–37	Oxidation, on metal surfaces, 530	74HC85 comparator, 288, 289
"Odd but not even gate," 53	Oxide films, overcoming, 531	741C65 Comparator, 268, 269 7489 IC, 367, 368
	-	. 102 20, 201, 200

CD4081BE CMOS quad two-input AND	described, 117–121	Recirculating down counter, 269
gate IC, 66	fabricating specialized encoders and decoders, 208	Recirculating feature, 308, 310
4511 BCD-to-seven-segment latch/decoder/driver	integrated circuit, 117	Recirculating line (feedback), 319
IC, 225	practical, 121–122	Recording layer (silver-indium-antimony
MM5314 MOS LSI clock IC, 416, 417	programming, 116–117	tellurium alloy), 392
74HC76 IC, 295, 296	specific devices referred to, 116	Redundant circuitry, 324
7408 digital IC, 63	typical equipment for programming, 117	Reflective-type sensor, 287
TMS4764 ROM, 374	Programmable read-only memories (PROMs), 372,	Registered PLDs, 121
2732A 32K (4K X 8) ultraviolet-erasable	377–380	Registers, 237, 305, 452, 466
PROM, 378, 380	basic idea of, 378	Relaxation oscillator, 418
Pin labels and functions, for ADC0804 A/D	burners, 377, 380	Relay ladder diagram, 470
converter IC, 518	generating final seven-segment output code, 418	Remark statements, 79, 128, 187, 479, 489
Pin-out information, for the standard A and	permanent nature of burning, 378	Repeated addition, 343
B plugs, 465	Programming	Repeated addition-type multiplier system, 345
Pixels, 217, 486	a computer, 348	Repeated divide-by-2 method, 197
PLA (programmable logic arrays), 116	an EPROM, 380	Repeated divide-by-2 process, 30-31
Place value, 28–29	Programming mode, 378	Repeated divide-by-8 process, 36-37
Plastic range, using solders with, 531	Prohibited state, for a flip-flop, 237	Repeated divide-by-16 process, 35
Plate (P), 221	Propagation delay, of digital ICs, 148–149	Reset condition, for the flip-flop, 237
Plated tip, preparing for a soldering iron, 534	Propagation delays, for the FACT series, 151	Reset input, 236
Platters, 389	Protein-based memory, 372	Reset mode
PLC programming, 470	Pull-down resistor, 75, 153	for 7476 J-K flip-flop, 244
PLDs. See Programmable logic devices (PLDs)	Pull-up resistor, 74, 152, 160, 182	in clocked R-S flip-flops, 239
Plus (+) sign, Boolean symbol for OR, 46	Pulse duration, 170	Reset pulse, generated, 425
. , .	Pulse generator, 170	Reset/count function table, 272, 273
PMOS (P-channel MOS), 150		
PN-junction diode, 207	Pulse triggering, IEEE symbols for, 253	Reset-count-display sequence, 419, 420, 425
Pocket calculator, encoders and decoders, 31	Pulse width, 14, 170	Resistance, decreasing causing an increase in
Pocket hard drive, 389	Pulses, counting the number of, 285–287	current, 5
Polarity	Pulse-shaper circuit, 280, 281	Resistive ladder network, 501
LED sensitive to, 207	Pulse-width modulation (PWM), 170, 186	Resistor network, 500, 502, 504
of a magnetic field, 180	Punched card, 388	Resolution, of an A/D converter, 516
Pololu carrier with sharp GP2Y0D810ZOF digital	Pure rosins, 532	Restriction of hazardous substances (RoHS)
distance sensor 10 cm, 434	Push-button switch, 152	standards, 534
Pololu Corporation sensor 1134, 434	activating clear (CLR) input of an 8-bit binary	RGB (red, green, blue) output, cameras storing, 487
Pololu distance sensor module, 434	counter IC, 74, 75	Rigid disk form, 388
Portable computers, memory modules, 386	open, 10	Rigid magnetic disk, 388
Portable hard drive, 389	using to make a digital signal, 9	RIMM, 385
Ports, 128, 464	PWM (pulse-width modulation), 170, 186	Ring counter, 319, 320
Positive logic, 44		Ripple counters, 262–264
Positive-edge-triggered flip-flop, toggling, 249	п	Ripple-blanking input (RBI), 209, 210, 212
Potentiometer		Ripple-blanking output (RBO), 209, 210
as analog device, 394, 395	Quad bilateral switch, 411	RISC (reduced instruction set computing), 475
sensing angular position of the output, 170	Quadrature encoder, 200–201	Rise and fall times, fast, 251
used for calibration, 524	Quadruple two-input AND gate, 63	RJ-11 jack, 465
Power consumption, exceptionally low, 150	Quantizing errors, 516	RJ-45 jack, 465
Power dissipation, of digital ICs, 149	Quine-McCluskey method, 100	Roll dice switch, closing, 409
Power supply voltages, 517		ROM (read-only memory), 364, 375-377
Power transistor, attaching to output, 167	R	Rosins, combined with mild activators, 532
Power-up initializing circuitry, 319	R register, 485	Rotary encoder, determining direction of rotation
Prescale counter, programming, 416	R-2R ladder network, 504	of, 201
Pretinning, 533	Radar (radio detection and ranging), 432	Rotary switches, 112-113, 458
Primary storage, 387	Radiation-tolerant FACT ICs, 151	Roulette wheel, 318
Primitive diode ROM circuit, 372, 373	Ramp A/D converter, 512, 513, 514	Router, 450
Primitive frequency counter, schematic	Ramp generator, 512, 513	Rpm (revolutions per minute), 291
diagram, 423, 424	Ramtron International, 384	R-S flip-flops, 236–238
Printed circuit (PC) board, 70	Random number, counter stopping at, 407	RS flip-flops, 154
Priority encoder, 74148 IC as, 256	Random-access memory (RAM), 362, 365–366	R-S latch, 236
Priority feature, of 74147 encoder, 204	Range of voltages, defined HIGH and LOW, 9	
Procedure, programming into a computer, 346, 348	RC circuits (resistive/capacitive circuits), 516	S
Processing, of a digital system, 403, 404	Read light-rotate servo program, listing of, 491	
Processing unit, of the PLC, 469		S, in a core part number, 65
Product, 343	Read mode, on the 7489 RAM, 367	Sample/preload instruction, 439
Product of sums (POS), 91–92	Read operation, 366	Sampling, 483
Program, for a computer, 448	Reading, what is in memory, 367	Sampling time, 425
Program (instructions), 446	Reading from, memory, 362	Satellites, in geostationary earth orbit (GEO), 70
	Reading out, information from RAM, 365	Schematic symbol, for optocoupled interrupter
Program memory	Read-only memory (ROM), 362, 372–374	module, 285
instructions in, 450–451	storing programs in a microcomputer, 473	Schmitt triggers, 251–252
placing the operand on the data bus, 453	used to store permanent data and programs, 374	Schmitt-trigger inverter, 155, 251, 523
sections of, 485	uses of for encoders, 376	Schmitt-trigger inverter IC, 414, 415
separate provided, 477	Read/write memory, 365	Schmitt-trigger threshold detector, 180
Program memory size, 474	Real-world events, counting, 284–287	Schottky diodes, use of, 177
Programmable AND and OR arrays, 121	Real-world information, as analog, 4, 499	Schottky TTL (LS-TTL), fan-out for low-power, 146
Programmable controller (PC), 469	Recall operation, in NVSRAM, 381	Scientific calculators, making number system
Programmable Logic Controllers 4th edition	Receive data register, 466	conversions, 37
(Petruzella), 470–472	Receive-buffer-full (RF) flag, 468	Scope. See Oscilloscope
Programmable logic controllers (PLCs), 469–472	Receiver, in a UART, 460	Scratch-pad memory, 365
Programmable logic devices (PLDs), 91, 116–122	Receptacles, 464, 465	Seagate Technology, 388
advantages of, 116	Reciprocating slide, activated by motion of a servo	Secondary storage, 387–388
burner, 118	motor arm, 489	Seconds timer, 270

74HC4543 BCD-to-seven-segment latch/decoder/ Sectors, 389 Signed numbers, adding or subtracting, 349 driver CMOS IC, 218, 219, 220 74HC4543 IC, functions of, 429, 432 Self-stopping counters, 269 Silicon dioxide layers, inside a CMOS chip, 150 Self-stopping down counters, 426, 427 Silver brazing, 532 for LCD timer circuit, 427, 429 74HC76 IC, pin diagram for, 295, 296 SIMM memory modules, 385 Simple self-contained digital electronic games, 407 Semiconductor flash memory devices, 361 74HC85 4-bit magnitude comparator, 288 Semiconductor memory, 361, 364 Semiconductor RAM ICs, static and dynamic 74HCT00 series, of CMOS ICs, 142, 161 Simplified 16-bit (4 X 4) PROM, 378 74HCT34 noninverting IC, 161 Sine wave, sampling, 483 types, 368 74LS04 inverter, 147-148 Single short, positive pulse, output from the one-shot Semiconductor storage, 363-364 74LS112 TTL-LS J-K flip-flop, 244-246 Sense operation, 366 74LS14 IC, 523 Single-package microcontroller, 473 Sensing, what is in memory, 367 74LS279 Quad S-R Latch IC, 238 Single-pole, double-throw (SPDT) switches, 9, 174 74LVC (low-voltage CMOS), 69 Single-pulse clock, 10 Sensors Sinking current, 157, 158 SIP (single inline package), 385 74LVX00, 143-144 information from, 6 7400 series logic circuits, propagation delays, 150 7400 series of TTL ICs, 63 7404 inverter, complementing the output, 460 measuring analog phenomena, 5 measuring analog pnenomena, 5 PLC interfacing with, 469 Sequential logic circuits, 90, 236 Sequential logic devices, D flip-flops as, 242 60/40 solder, 530 60-Hz signal, input into a digital clock, 412 7404 inverter IC, 32 7406 TTL ICs, 162 60-Hz sine wave, converted to a square wave, 419-420 Serial data 64 MB of flash memory, 392 7408 digital IC, pin diagram for, 63 changing parallel data into, 457 64-bit memory, organization of, 365 out from TDO (test-data output), 439 7414 Schmitt-trigger inverter, 423 64-bit scratch-pad memory, 366 68-pin PCMCIA memory card, 387 sent out on the TxD (transmit data) line of 7414 Schmitt-trigger inverter TTL IC, 251, 252 the UART, 468 7416 TTL ICs, 162 Six-wire unipolar stepper motor, 176-177 at the TMS input pin, 438 7447 BCD-to-seven-segment decoder chip, 407, 408 Slot-type module, 287 7447 binary-to-seven-segment LED decoder/driver Serial data transmission, 458 Slow rise time, for a sine wave, 414 Serial form, 457, 460 IC, 32 Slow set, 416 Serial in-parallel out register, 306, 308 7447A IC, 520-521 Small-outline IC (SOIC), 68, 384, 404, 474 Small-scale integration (SSI), 406 SMT (surface-mount technology) packages, 63 Serial in-serial out register, 306, 308 7474 TTL D flip-flop, 241, 242 7474 TTL *B* hip-flop, 241, 242 7475 TTL 4-bit transparent latch, 248 7475/74LS75/74HC75 4-bit latch, 238 7476 TTL J-K flip-flop, 243–244, 245 Serial interface SN74LVC08, 68-69 standards, 461 transmitting data 1 bit at a time, 460 Snap action, changing to either HIGH or LOW, 155 7483 4-bit adder, counterparts to, 340 Snap-action bounce-free output, 180 Serial load, 308 Serial output, observed at test data output 7489 read/write RAM, programming, 370 Snap-action pushbutton switch, 14 (TDO), 439 7489 read/write TTL RAM, 367 Snapshot or sample, of data flowing into or out of the 7489 TTL RAM, access time of, 370 Serial port, 464 internal chip logic, 439 Serial test data, shifted in through test data input 7493 4-bit ripple counter, packaged in a 14-pin Social networking, 7-8 (TDI), 439 DIP, 272, 273 Software, 32, 374 Serial-load shift register, 308 7493 IC counter, used as a mod-8 counter, 273, 275 doing multiplication, 348 Serial-load shift registers, 307-308 7493 TTL 4-bit binary counter, 272, 273 SOIC (small-outline IC), 68, 384, 404, 474 Serial-load shift-left register, 313 74121 one-shot multivibrator IC, 13 Solder, nature of, 530-531 Serial-load shift-right register, 313, 323, 324 74125 quad three-state buffer TTL IC, 456, 457 Solder connection, making, 534 74147 10-line-to-4-line priority encoder, 204, 205 74147 decimal-to-binary encoder IC, 32 Solder heat bridge, 533 Servo motor connected to the BASIC Stamp 2 module, 186 Soldering 74150 MUX, 459, 460 74154 DEMUX, 460 74154 DEMUX IC, 459 74189 64-bit RAM, 367 controlling using a control pulse, 170, 171 interfacing BASIC Stamp 2 Module with, advantages of, 530 defined, 530 high-reliability, 530 186-188 interfacing with, 170-172 as very complex control problem, 533 rotational characteristics, 172 Soldering irons, 532, 533-534 74192 decade counter, 413 valve activated using, 488 74192 up/down decade counter IC, 272-275 Solderless breadboard, 11, 12, 14 Set condition, for the flip-flop, 237 74194 4-bit bidirectional universal shift register, 311 Solenoid, 165, 166 Set input, 236 74194 IC 4-bit bidirectional universal shift register, 315 Solid-state computer, 387 74194 IC register, 311 Solid-state disk, 387 Set mode for 7476 J-K flip-flop, 244 74194 IC shift register, 313-315 Solid-state potentiometer, 394 in clocked R-S flip-flops, 239 Shaft encoder, 199-200 Solid-state relay, 167, 169 Shaft or wheel, locating angular position of, 200 Shape, of a waveform, 19 Sonar (sound navigation and ranging), 432 Seven-input XOR gate, generating correct even parity bit, 462 Source supply, in a MOSFET, 151 Shape, of a waveforth, 19 Shift registers, 305 categories of, 306 characteristics of, 306 constructing, 306 Seven-segment decoder/drivers, 207 Seven-segment LED, 32 Sourcing current, 157 South pole, of a magnet, 182 Seven-segment LED displays, 205-207 SP (space), 202 Speed versus power graph, comparing several of the TTL and CMOS families, 149 72-pin SIMM (single in-line memory module), 385 converting serial data to parallel data or parallel 74AC00 series, 142, 150 74ACQ00 series, 142 data to serial data, 315 Spindle speed, of hard drives, 389 74ACT00 series, of CMOS ICs, 66, 142, 143 formed by flip-flops, 236 SPST switch, electronically operated, 411 74ACTQ00 series, of CMOS ICs, 142, 143 forming, 242 SPTD switch debouncing circuit, 238 in IC form, 306 74ALVC (advanced low-voltage CMOS), 69 Square waves, useful in digital electronics, 21 74ALVC00 series, 143, 150, 151 memory and shifting characteristics, 305-306 SRAM (static random-access memory), 364, 366, 74AVC (advanced very low voltage CMOS), 69 operating, 307 370-371 74C00 series, 142, 143 of CMOS ICs, 66 SRAM FPGA (static RAM field-programmable gate troubleshooting, 323-324 used as temporary memories, 315 using, 315, 318–323 array), 116 equivalent of 7400 series of TTL ICs, 151 SSOP (shrink small-outline package), 474 74FCT00 series, of CMOS ICs, 66, 142, 143 74FCTA00 series, of CMOS ICs, 142, 143 74HC00 series, 66, 67, 142, 151 Shift-and-add method, 345, 346 Standard logic symbol, for the NAND gate, 50 Shift-left mode, 74194 shift register, 311, 312 Shift-right mode, 74194 shift register, 311, 312 Standard TTL gate, capabilities, 147 Standard TTL inverter, typical propagation delay for, 74HC04 inverter, positive pulse emitted by, 294 Short circuit, dropping power supply voltage, 228 148 74HC164 8-bit serial in-parallel out shift register, Short-form addition table, for binary, 331 Start input control, activating, 427 315-317, 319 Sign bit, of a number, 348 Start/stop control, 414, 415, 419 74HC193 IC, wired as a mod-6 counter, 279-280 Static discharges, protecting from, 150 Signal, defined, 2 74HC193 presettable synchronous 4-bit binary Signal conditioning, 251 Static electricity, resistance to, 151 up/down counter IC, 277-279 Signed decimal numbers, converting to 2s complement Static RAM, 368

Static RAM ICs, 367-370

74HC393 dual 4-bit binary ripple counter, 276-277

Status register, 466, 467	Three-digit BCD counters, 280-283, 291-292	NAND gate, 50
Step angles, for common stepper motors, 172	Three-dimensional Karnaugh map, 105	NAND logic function, 61
Stepper motors	Three-input AND gate, 57	NOR function, 52
control sequence, 172, 174	Three-state buffers, 370, 454	NOR gate, 51
interfacing, 174-177	commercial version of, 456, 457	OR circuit, 46
noncontact and timed operation of, 435	truth table for, 49	as origin of most logic circuits, 93
rotating a fixed angle, 172, 173	Three-terminal LM34 and LM35 temperature	parity bit generator, 462
Storage capacity, graphed in MB, 393	sensors, 524	R-S flip-flops, 237
Storage function, of a digital system, 403, 404	3132 bipolar Hall-effect switch, 179-182	74HC164 shift register, 316, 317
Storage registers, forming, 242	3132 Hall-effect switch, 181, 182	74HC193 counter, 277-278
Store operation, in NVSRAM, 381	3144 unipolar Hall-effect switch, 182	74HC4543 BCD-to-seven-segment latch/decoder/
Stored program, in a computer, 446	Three-variable Karnaugh map, 101-102	driver CMOS IC, 220
Stored-program digital computer, 447	Tilde (~) symbol, 81	74LS112 J-K flip-flop, 244, 246
Strength, of a magnetic field, 180	Time, graphing versus input voltage, 20	7447A decoder/driver IC, 209, 210
Subscripts, indicating the base of a number, 34	Time displays, 412	7474 D flip-flop, 242
Subsystems, assemblies of, 403	Time duration, for a cycle, 21	74125 IC, 456, 457
Subtraction problem, sample binary, 337	Time-base clock, 426, 427	74194 shift register, 311, 312
Subtractors, 330	Time-set control, 412, 413	three-input AND gate, 57
Successive-approximation A/D converter, 514-515, 519	Timing diagrams, given for sequential logic	three-state buffer, 49
Successive-approximation logic unit, 514	circuits, 237	XOR and XNOR gates, 55
Summing amplifier, 500, 501, 502, 504	Tin, melting point of pure, 530	OR and XOR gates, 53
Sum-of-products (SOP) form, 91	Tin-silver-copper alloy, 530	TTL (transistor-transistor logic)
Sum-of-products calculation, 483, 484	Tip styles and sizes, for soldering irons, 532	circuits, 16
Surface condition, of area to be soldered, 533	TMS (test mode select), 438	digital circuit, testing, 17-18
Surface oxides, removing, 531	TMS4664 ROM, access time of, 374	digital ICs, constructing, 62
Switch bounce, caused by a mechanical switch, 12	TMS4764ROM, 8192-word by 8-bit ROM, 374	family of ICs, 9
Switch debouncing circuit, 153, 154–155	Toggle mode, 244, 267	IC counters, 273–275
Switchcheck, IF-THEN statement in, 481	Toggling, 9, 243	input logic levels showing noise margin, 145
Switches, interfacing TTL and CMOS, 152–155	Tracks, number of, 389	inputs floating at a HIGH logic level, 152
Switching threshold	Traditional method of distance sensing, 434	inverter, expected outputs from, 142
of the 7404 IC, 251, 252	Transducer, 500, 520	logic family, 141
voltage increasing, 145	Transistor driver circuit, 159	logic gates, 62–65
Switch-to-CMOS interface circuits, 152, 153	Transistor-transistor logic (TTL). See TTL (transistor-	voltabe profile, 142
Switch-to-TTL interfaces, 152	transistor logic)	voltage levels, 9
Synchronous counters, 265–267, 272	Transmission function, of a digital system, 403, 404	XOR gates, not used, 214
Synchronous flip-flops, 249	Transmission gates, 151, 411	TTL 7414 Schmitt-trigger inverter IC, 414, 415
Synchronous operation, 240	Transmission system, using MUX-DEMUX	TTL 7447A BCD-to-seven-segment decoder/driver,
of a D flip-flop, 242	arrangement, 458–460	209–212
Synchronous parallel loading, of a shift register, 312	Transmit data register, 466	TTL 7483 4-bit binary full adder, 340, 341
Synchronous paramer loading, or a sinte register, 512	Transmitter, in a UART, 460	TTL and CMOS noise margins, comparing, 144
Τ	Transparent latch, 248, 256	TTL digital IC, top of a typical, 63
T	Transparent mode, of 7475 IC, 256	TTL families, families, voltage characteristics of all,
T flip-flop, 246, 276–277	Transponder ECM, 8	148
"T" series CMOS ICs, 143	Triangulation method, 432, 433, 434	TTL ICs
Tabular method of simplification, 100	Trigger pulse, 293–294	interfacing with CMOS ICs, 160–163
Tachometer, 6	Trigger voltage, 13	typical fan-out value for, 146
TAP controller, 438	Triggering, flip-flops, 249–250	TTL-to-CMOS interfacing, 161
TB (terabyte), 363	Triode vacuum tube, 221, 222	TTL-to-LED interfacing, 156, 157
TCK (test clock), 438	Tristate output, 367	TTL-type digital circuit, testing, 19
TDI (test data input), 438	Troubleshooting	"T"-type CMOS gates, having input voltage profile of
TDO (test data output), 438	a CMOS circuit, 71	a TTL IC, 161
Temperature, digitizing, 523–524	counters, 295–297	12-h display format, 416
Temperature-sensitive resistor, 523	a decoding circuit, 227–228	20-mA current loop teletype standard, 461
Temporary memory, in a shift register, 305		
Temporary storage, of data, 366	a full adder, 355–356 ICs, 71	20-pin DIP IC, 121
10-line-to-4-line priority encoder, 204, 205	knowledge of circuit operation key to effective, 18	24LC 16 EEPROM, for program storage, 405
10s display, 294	most important tools, 297	24-pin DIP IC, 77 24-pin EPROM DIP IC, 377, 378
Test access points, loss of, 440	shift registers, 323–324	25-pin DB (data bus) connector, 464
Test access port (TAP), 438	simple gate circuits, 69–71	27XXX series EPROM, 378
Test data register, 438	simple logic circuits, 185–186	
Test reset (TRST) input, 438	six hints for successful, 356	28F512 512K (64K X 8) CMOS flash memory,
Test vectors, loading into output boundary-scan cells,		382, 383
439	Truth tables A/D converter, 506, 507	Twisted-nematic field-effect LCD, 213–214
Testing, as an important part of any complex system,		Twisted-nematic field-effect technology, 215
440	AND, 44 Region expressions 93	2-bit quadrature, 200–201
Texas Instruments, "SN" designating, 63	Boolean expressions, 93	2-bit ripple counter, troubleshooting a faulty,
Texas Instruments digital IC, markings on, 64	clocked R-S flip-flop, 240	295–297
Thermal linkage, 533	and the form Poology avaragions 04	
The same of same 522	constructing from Boolean expressions, 94	Two-digit seven-segment LCD, 215, 216
Thermal mass, 532	D flip-flop, 241	240-pin DDR2 SDRAM, 386
Thermistor, 523, 524	D flip-flop, 241 D/A converter, 500, 504, 506	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program,
Thermistor, 523, 524 Thin-film medium, 389	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172
Thermistor, 523, 524 Thin-film medium, 389	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79-80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system,
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385 3.5-in. floppy disks, 389, 390	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283 four-input OR gate, 58	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354 2s complement 8-bit, 350–352
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283 four-input OR gate, 58 full adder, 333, 355	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354 2s complement 8-bit, 350–352 2s complement addition, 349, 350
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385 3.5-in. floppy disks, 389, 390 3-bit (mod-8) counter, logic diagram for, 265–267 3-bit adders, 335	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283 four-input OR gate, 58 full adder, 333, 355 full subtractor, 336, 337	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354 2s complement 8-bit, 350–352 2s complement addition, 349, 350 2s complement conversions chart, 535
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385 3.5-in. floppy disks, 389, 390 3-bit (mod-8) counter, logic diagram for, 265–267 3-bit adders, 335 3-bit counter, with self-stopping feature, 269	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283 four-input OR gate, 58 full adder, 333, 355 full subtractor, 336, 337 half adders, 332	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354 2s complement 8-bit, 350–352 2s complement addition, 349, 350 2s complement conversions chart, 535 2s complement form, converting to binary, 349
Thermistor, 523, 524 Thin-film medium, 389 Thin-film transistor (TFT) technology, 217 Thin-film transistors, 216–217 30-pin SIMM, 385 3.5-in. floppy disks, 389, 390 3-bit (mod-8) counter, logic diagram for, 265–267 3-bit adders, 335	D flip-flop, 241 D/A converter, 500, 504, 506 described, 93 4511 BCD-to-seven-segment latch/decoder/driver CMOS IC, 225–226 4553 three-digit BCD counter IC, 280, 281, 283 four-input OR gate, 58 full adder, 333, 355 full subtractor, 336, 337	240-pin DDR2 SDRAM, 386 Two-input AND function PBASIC program, 78, 79–80 Two-phase stepper motor, 172 2s complement 4-bit adder/subtractor system, 353–354 2s complement 8-bit, 350–352 2s complement addition, 349, 350 2s complement conversions chart, 535

2s complement representations	USB transmission rates, classified, 465	LOW, HIGH, LOW, HIGH, 9, 10
determining sign and magnitude of a number, 348	UV erasable PROMs, 377	ramp-type A/D converter, 513
of a negative number converting to decimal		showing propagation delays for a standard TTL
equivalent, 351	V	inverter, 148
of negative numbers, 348	Vacuum fluorescent (VF) display, 206, 221–223, 224	Waveshaping, by a 7414 Schmitt-trigger inverter, 423
of positive numbers, 348	Valve, controlling flow of liquid, air flow, or light	Waveshaping circuit, 414, 415, 416
2s complement subtraction, 349–350	intensity, 488, 489	Wear-out condition, for DS1804 IC, 397
Two-terminal AD592 precision IC temperature	Variable, declaring, 187–188	Wetting action, 531
transducer, 524		Winchester drive, 388
2114 static RAM, 368-370	Variable output, on the function generator, 19	Wiper position, in DS1804-100 digital potentiometer,
2732 EPROM chip, block diagram of, 378	Variable reluctance stepper motors, 172	396
2732 EPROM IC, 378, 380	Variable-frequency signal, from vehicle speed sensor, 6	Wiring diagrams
2732A 32K (4K X 8) ultraviolet-erasable PROM, pin	Variable-voltage signal, 6	BCD decoder/driver circuit, 224
diagram, 378, 380	Vehicle speed sensor, engine control module (ECM), 6	clocked R-S flip flop, 240
Two-way path, transferring data into and out of the	Veitch diagrams, 100	digital dice game, 407, 408
MPU, 448	Venn diagrams, 100	digital light meter circuit, 522
TxD (transmit data) line of the UART, 468	Vertical deflection knob, on a scope, 20	divide-by-60 counter circuit, 413, 414
	Vertical line (I) symbol, in the NOR function in	· · · · · · · · · · · · · · · · · · ·
Type A plug, connecting upstream to the USB	PBASIC, 81	elementary digital voltmeter, 510, 511
ports, 464	Very large-scale integration (VLSI), 406	experimental LCD timer circuit, 427, 430–431
Type B plugs, connecting downstream to the	Very small capacity unit, 374	4-bit parallel-load recirculating shift register, 309
USB ports, 464–465	VF display, driving, 224–226	latched encoder-decoder circuit, 254–256
	VGA (video graphics adapter), 464	Words, 38
	Video port, 464	in 64-bit memory, 365
UARTs (universal asynchronous receiver-transmitters),	Vision enhancement, 317	in computer jargon, 37
460, 465-466	VLSI ICs, 406	Work surfaces, melting the solder, 534
Ultra-large-scale integration (ULSI), 406	Volatile memory, RAM as, 366	World Wide Web (WWW), 7
Ultrasonic distance sensor, 432–434	Voltage, output by an analog circuit, 2	Worst-case conditions, 147
Ultrasonic receiver, 433	Voltage characteristics, of both TTL and	Write input, of the data memory, 453
Ultraviolet (UV) light, erasing EPROM, 377	CMOS ICs, 141	Write mode, RAM in, 367
Undefined region, 16	Voltage comparators, 506, 508–509	Write operation, 366
between HIGH and LOW, 9	Voltage divider circuit, 488, 490	Write-once read-many (WORM) storage devices,
pin floating in, 295	Voltage gain, 503	391–392
voltage at, 9	of an amplifier, 502	Write-protect notch, 389, 390
Unipolar Hall-effect switches, 182	of the op amp, 510	Write-protected disk, 389, 390
Unipolar or four-phase stepper motors, 176	Voltage incompatibility, from TTL (NMOS)	Writing
	to CMOS, 161	in memory, 362
Unipolar stepper motors, 172	Voltage levels, for digital signals, 9	to RAM, 365
Unique output, AND truth table, 45		
Universal flip-flop, 246	Voltage profile, of a typical TTL inverter (7404 IC),	X
Universal gate, NAND gates as, 56	251, 252	
Universal serial bus (USB) port, 464–465	Voltage rails, of the power supply, 142	XNOR (exclusive NOR) function, 54, 55, 56
Universal shift register, 311, 312	Voltage regulator, on BOE, 479	XOR function, Boolean expression for, 53
Unknown frequency, measured by a digital frequency	Voltage versus time format, for signals, 2	XOR gates
counter, 419	Voltage-controlled oscillator (VCO), 319	inverting data at, 353
Unused input leads, connecting, 150	Volt-ohm-millimeter (VOM), 2	logic symbol for, 53
Unused outputs, leaving unconnected, 150		output for, 53
Unwanted voltages, 145	W	for parity bit generation and error detection, 462
Up position, switch in, 63	WAN (wide area network), 450	truth tables, 53
USB 1.0 low-speed rate, 465	Warning horn (H), 472	unique characteristic of, 53
USB 1.1 full-speed rate, 465	Waste from electrical and electronic equipment	unique output of, 54
USB 2.0	(WEEE) standards, 534	in a variety of arithmetic circuits, 54
high-speed rate, 465	Waveform diagram	XOR logic function, substituting NAND gates, 56
ports, 392	74192 counter IC, 272, 275	XORing, ways of expressing, 54
receptacle, 464	74194 shift register, 311, 312	X-Y position indicator, for a display system, 211
USB 3.0	for a clocked R-S flip-flop, 239	
ports, 393, 464	graphing analog output, 2	Z
superspeed rate, 465	for an unknown frequency, 419, 420	Zener diode, in a comparator, 509
USB flash drives, 361, 363, 448	Waveforms	Zero-blanking circuit, 418
USB flash memory, 364, 392-393	digital, 9	ZIF (zero insertion force) IC socket, 117
USB floppy disk drives, 389	with fast rise and fall times, 251	Zinc-oxide fluorescent material, 221
USB ports, 392, 393, 464–465	given for sequential logic circuits, 237, 238	ZIP (zig-zag in-line package), 385
USB standard type A plug, 392	input, 237, 238	Zir (Zig-zag iii-iiio package), 303
** * -	mpac, 201, 200	