

**HANDBOOK
OF
ELECTRONICS
FORMULAS,
SYMBOLS
AND
DEFINITIONS**

HANDBOOK
OF
ELECTRONICS
FORMULAS,
SYMBOLS
AND
DEFINITIONS

Second Edition

John R. Brand



VAN NOSTRAND REINHOLD
New York

ISBN-13: 978-1-4684-6493-1
DOI: 10.1007/978-1-4684-6491-7

e-ISBN-13: 978-1-4684-6491-7

Copyright © 1992 by Van Nostrand Reinhold
Softcover reprint of the hardcover 1st edition 1992
Library of Congress Catalog Card Number 91-30692

All rights reserved. Certain portions of this work ©1979 by Van Nostrand Reinhold. No part of this work covered by the copyright hereon may be reproduced or used in any form or by any means --graphic, electronic, or mechanical, including photocopying, recording, taping, or informational storage and retrieval systems -- without written permission of the publisher

Manufactured in the United States of America

Published by Van Nostrand Reinhold
115 Fifth Avenue
New York, New York 10003

Chapman and Hall
2-6 Boundary Row
London, SE 1 8HN

Thomas Nelson Australia
102 Dodds Street
South Melbourne 3205
Victoria, Australia

Nelson Canada
1120 Birchmount Road
Scarborough, Ontario M1K 5G4, Canada

16 15 14 13 12 11 10 9 8 7 6 5 4 3 2

Library of Congress Cataloging-in-Publication Data

Brand, John R.
Handbook of electronics formulas, symbols, and definitions/ John R. Brand. -- 2nd ed.
p. cm.

1. Electronics--Handbooks, manuals, etc. I. Title.
TK7825.B73 1991
621.381--dc20

91-30692
CIP

PREFACE

The *Handbook of Electronics Formulas, Symbols and Definitions* has been compiled for engineers, technicians, armed forces personnel, commercial operators, students, hobbyists, and all others who have some knowledge of electronic terms, symbols, and theory.

The author's intention has been to provide:

A small, light reference book that may be easily carried in an attaché case or kept in a desk drawer for easy access.

A source for the majority of all electronic formulas, symbols, and definitions needed or desired for today's passive and active analog circuit technology.

A format in which a desired formula may be located almost instantly without the use of an index, in the desired transposition, and in sufficiently parenthesized linear form for direct use with any scientific calculator.

Sufficient information, alternate methods, approximations, schematic diagrams, and/or footnotes in such a manner so that technicians and hobbyists may understand and use the majority of the formulas, and that is acceptable and equally useful to engineers and others very knowledgeable in the field.

INTRODUCTION

All formulas in this *Handbook* use only the basic units of all terms. It is especially easy in this age of scientific calculators to convert to and from basic units.

Formulas in all sections are listed alphabetically by symbol with the exception of applicable passive circuit symbols, where, for a given resultant, all series circuit formulas are listed first, followed by parallel and complex circuit formulas.

If the symbol for an electronic term is unknown, a liberally cross-referenced listing of electronic terms and their corresponding symbols may be found in the appendix.

Symbols of all reactive magnitude terms in formulas have been consistently given the signs conventionally associated with them to maintain capacitive or inductive identity. In rectangular quantities, this also allows identification of the complex number as representing a series equivalent impedance/voltage or a parallel equivalent admittance/current.

To prevent possible confusion, all symbols representing vector quantities in polar or rectangular form have been printed in boldface.

A number of formulas have the potential to develop a zero divisor. Conventional mathematics prohibits a division by zero, and calculators will overflow if this is attempted. However, formulas noted $\textcircled{0}$ allow the manual conversion of the reciprocal of zero to infinity and the reciprocal of infinity to zero. Division by zero in formulas noted $\textcircled{\infty}$ is prohibited.

Textbooks conventionally use italic (slanted) type for quantity symbols and roman (upright) type for unit symbols. However, this *Handbook* follows the example of almost all technical manuals, using roman type for both quantity and unit symbols.

ACKNOWLEDGMENTS

Much of the material in this *Handbook* is based upon a small loose-leaf notebook containing formulas and other reference material compiled over many years. With the passage of time, the sources of this material have become unknown. It is impossible therefore to list and give the proper credit.

Special thanks are due to my wife and family for their understanding and acceptance of long periods of neglect, without which this book would not have been possible.

CONTENTS

Preface	iii
Introduction	v
Section 1 Passive Circuits	
1.1 English Letters	1
1.2 Greek Letters	185
Section 2 Transistors	
2.1 Static Conditions	201
2.2 Small Signal Conditions	221
Section 3 Operational Amplifiers	
3.1 Symbols and Definitions	253
3.2 Formulas and Circuits	277
Appendix	
A Table of 5% Value Ratios	363
B Table of 1%, 0.5%, 0.25% and 0.1% Standard Values	369
C Electronics Terms and their Corresponding Symbols	371

SECTION ONE

PASSIVE CIRCUITS

1.1 ENGLISH LETTERS

A

**Ampere,
Amplification
etc.**

A = Symbol for ampere.

A = Basic unit of electric current.

A = Coulombs per second.

A = $6.24 \cdot 10^{18}$ elementary charges per second (electrons or holes).

A = Unit often used with multiplier prefixes.

pA = 10^{-12} A, nA = 10^{-9} A, μ A = 10^{-6} A

mA = 10^{-3} A, kA = 10^3 A, etc.

A = Symbol for area. Area is measured in various unit such as in², ft², cm², m² etc.

Ah = Symbol for ampere-hours. One ampere-hour equals 3600 coulomb (C).

At or A = Symbol for ampere turn, the SI unit of magnetomotive force.

A_i = Symbol for current amplification.

See—Active Circuits

A_v = Symbol for voltage amplification.

See—Active Circuits.

a = Symbol for atto. A multiplier prefix for 10^{-18} .

α = Substitute for greek letter alpha. (Not recommended)

See— α

a = Not recommended as a quantity symbol.

B

Susceptance Definitions

B = Symbol for susceptance

B = The ease with which an alternating current of a given frequency at a given potential flows in a circuit containing only pure capacitive and/or inductive elements. The imaginary part of admittance. The reciprocal of reactance in any purely reactive circuit. The reciprocal of a pure reactance in parallel with other elements.

B = Magnitude of susceptance measured in mho (old) or siemens (new). Siemens (S) and mho (Ω^{-1}) are equal.

B = $|B|$ = $B_{\text{absolute value}}$ = $B_{\text{magnitude}}$

B = Complete description of susceptance

B = $B \angle \pm 90^\circ = 0 \pm jB = 0 - (\pm B)j$

B_C = Capacitive susceptance

B_C = $B \angle +90^\circ = 0 + jB = 0 - (-B)j$

B_L = Inductive susceptance

B_L = $B \angle -90^\circ = 0 - jB = 0 - (+B)j$

B_C = B magnitude identified as capacitive

B_L = B magnitude identified as inductive

-B = B magnitude "given" the sign usually associated with capacitive quantities. **-B** = **B_C**

+B = B magnitude "given" the sign usually associated with inductive quantities. **+B** = **B_L**

±B = Identification of B as capacitive or inductive in many formulas.

±B = Identification of B as capacitive or inductive in the resultant of all formulas in this handbook.

Susceptance, Series Circuits	B	Applicable Notes	Terms
$B_C = -X_C/(X_C^2 + R_s^2)$		① ② ③	R_s, X_C
$B_L = X_L/(X_L^2 + R_s^2)$		① ② ③	R_s, X_L
$\pm B = \pm X_s/(X_s^2 + R_s^2)$		① ② ③	$R_s, \pm X_s$
$B_C = -X_C/Z^2$		① ② ③	X_C, Z
$B_L = X_L/Z^2$		① ② ③	X_L, Z
$\pm B = \pm X_s/Z^2$		① ② ③	$\pm X_s, Z$
$\pm B = -Y[\sin(\pm\theta_Y)]$		① ② ③ ④ ⑬	$Y, \pm\theta_Y$
$\pm B = [\sin(\pm\theta_Z)]/Z$		① ② ③ ④ ⑬	$Z, \pm\theta_Z$

B Notes:

- ① B IS INTRINSICALLY A PARALLEL CIRCUIT QUANTITY. B DERIVED FROM A SERIES CIRCUIT IS THE EQUIVALENT PARALLEL CIRCUIT REACTANCE IN RECIPROCAL FORM.
- ② R_s = Series R, X_s = Series X.
- ③ B and X are magnitudes, however both B and X have been "given" the signs usually associated with capacitive and inductive quantities. B_C therefore "equals" $-B$, B_L "equals" $+B$, X_C "equals" $-X$ and X_L "equals" $+X$. This allows direct identification of a reactive quantity derived from any formula in this handbook.
- ④ The form $(\pm\theta)$ is used as a reminder that the sign of the phase angle determines the sign of B and therefore the identity of B as either capacitive or inductive.

Susceptance, Parallel Circuits	B	Applicable Notes	Terms
$(B_C)_t = (-B_C)_1 + (-B_C)_2 \dots + (-B_C)_n$ $-B_t = (-B_1) + (-B_2) \dots + (-B_n)$		③ ⑩	B_C $-B$
$(B_L)_t = (B_L)_1 + (B_L)_2 \dots + (B_L)_n$ $+B_t = (+B_1) + (+B_2) \dots + (+B_n)$		③ ⑩	B_L $+B$
$(B_C)_t = -\omega(C_1 + C_2 \dots + C_n)$		③ ⑤ ⑩	C
$(B_L)_t = \omega^{-1}(L_1^{-1} + L_2^{-1} \dots + L_n^{-1})$		③ ⑤ ⑥ ⑩	L
$(B_C)_t = (-X_C)_1^{-1} + (-X_C)_2^{-1} \dots + (-X_C)_n^{-1}$ $-B_t = (-X_1)^{-1} + (-X_2)^{-1} \dots + (-X_n)^{-1}$		③ ⑥ ⑩	X_C $-X$
$(B_L)_t = (+X_L)_1^{-1} + (+X_L)_2^{-1} \dots + (+X_L)_n^{-1}$ $+B_t = (+X_1)^{-1} + (+X_2)^{-1} \dots + (+X_n)^{-1}$		③ ⑥ ⑩	X_L $+X$
$ B $ = The magnitude of the imaginary part of Y_{RECT} $\pm B$ = The imaginary part of Y_{RECT} multiplied by $-j$.		③ ⑦ ⑧ ⑨	Y RECT

B Notes:

⑤ $\omega = 2\pi f = \text{angular velocity}$

⑥ $x^{-1} = 1/x$

⑦ $Y_{RECT} = G + j|B| = G - j(\pm B) = G - (\pm B)j$

⑧ $|B|$ = magnitude of B without knowledge of vectorial direction. $|B|$ therefore cannot be identified as either capacitive or inductive.

⑨ $(-j) \cdot (-j) = +1, (-j) \cdot (+j) = -1$

⑩ $(x)_t = \text{total } x = \text{equivalent } x$

Susceptance, Parallel Circuits	B	Applicable Notes	Terms
$\pm B_t = B_L - B_C$		③	B_C, B_L
$\pm B_t = (\pm B_1) + (\pm B_2) \dots + (\pm B_n)$		⑩	$-B, +B$
$\pm B_t = (\omega L)^{-1} - (\omega C)$		③ ⑤	C L
$\pm B_t = (\omega L_1)^{-1} - (\omega C_1) + (\omega L_2)^{-1} - (\omega C_2) \dots$		⑥ ⑩	
$ B = \sqrt{Y^2 - G^2}$		⑧	G, Y
$\pm B = -G [\tan(\pm\theta_Y)]$		③ ④	G, θ_Y
$ B = \sqrt{Z^{-2} - R^{-2}}$		⑧ ⑪ ⑫	R_p, Z
$\pm B = [\tan(\pm\theta_Z)] / R$		③ ④ ⑫	R_p, θ_Z
$\pm B_t = X_L^{-1} - X_C^{-1}$		③ ⑥	X_C, X_L
$\pm B_t = (\pm X_1)^{-1} + (\pm X_2)^{-1} \dots + (\pm X_n)^{-1}$		⑩	$-X + X$
$\pm B = -Y [\sin(\pm\theta_Y)]$		③ ④ ⑬	Y, θ_Y
$\pm B = [\sin(\pm\theta_Z)] / Z$		③ ④ ⑬	Z, θ_Z

B Notes:

⑪ $x^{-2} = 1/x^2$

⑫ R_p = parallel resistance

⑬ If the admittance (Y) or the impedance (Z) and the associated phase angle (θ_Y or θ_Z) are known, it is immaterial if the circuit configuration (i.e., series or parallel) is unknown.

B

Magnetic Flux Density, Bandwidth

B = Symbol for bel. (Rarely used)

B = Ten decibels (dB)

See—dB

B = Symbol for magnetic flux density.

B = The magnetic flux per unit area perpendicular to the direction of flux. (also known as magnetic induction)

B = Magnetic flux density measured in telsa (T), gauss (G), maxwell (Mx) per square centimeter and lines of flux per square inch.

telsa (T) = weber (Wb) per square meter

gauss (G) = 10^{-4} telsa

maxwell (Mx) = lines of flux

weber (Wb) = 10^8 maxwell (Mx) = 10^8 lines of flux

B = ϕ/A where **A** = cross sectional area of magnetic path.
 ϕ = Total magnetic flux in weber, maxwell or lines of flux.

B = μH where μ = permeability
H = magnetic force

B = Symbol for bandwidth (not recommended)

\bar{B} = Symbol for bandwidth (not recommended)

BW or $\bar{B}\bar{W}$ is the preferred symbol for bandwidth.

See—**BW**

B₁ = Symbol for unity gain bandwidth. (**BW**_(Av=1))

See—Active Circuits, Opamp

3 dB Down
Bandwidth

BW

Bandwidth

BW = Symbol for bandwidth

Other symbols for or abbreviations of bandwidth include:
B, \bar{B} , $(f_2 - f_1)$, **B.W.**, $\bar{B}\bar{W}$, $BW_{-3\text{ dB}}$

BW = The difference between the two frequencies of a continuous frequency band where the output has fallen to one half power. (-3 dB is very close to one half power)


BW = Bandwidth expressed in hertz (Hz).

$$BW = (f_2 - f_1)_{-3\text{ dB}}$$

$$BW = f_r/Q$$

$$BW = (f_r R)/X_L(@f_r)$$

$$BW = R/(2\pi L)$$

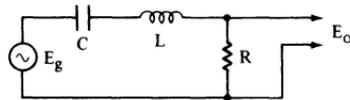


$$f_r = (2\pi\sqrt{LC})^{-1}$$

$$BW = (f_2 - f_1)_{-3\text{ dB}}$$

$$BW = f_r/Q$$

$$BW = (f_r X_C(@f_r))/R$$

$$BW = (2\pi RC)^{-1}$$

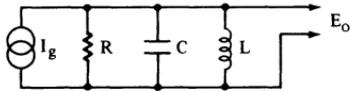

$$f_r = (2\pi\sqrt{LC})^{-1}$$

$BW_{(A_V=1)}$ —See—Active Circuits, Opamp

$\bar{B}\bar{W}$ = Average bandwidth. Effective noise bandwidth.

See also—BW Active Circuits, Opamp

BW Notes:

See—Q for frequency to bandwidth ratio.

See—D for bandwidth to frequency ratio.

See also—d Active Circuits.

C

Capacitance etc. Definitions

C = The symbol for capacitance.

C = 1. In a system of conductors and dielectric or in a capacitor, that property which permits the storage of electrical energy.

2. The property which determines the quantity of electric charge at a given potential.

3. In a system of conductors (plates) and dielectric (insulator) or in a capacitor, the ratio of the quantity of electric charge to the potential developed.

C = Capacitance (also known as capacity) measured in farad (F) units unless noted.

[This extremely large unit is very seldom used except in formulas. The resultant of all capacitance formulas should be converted to more practical units such as microfarads (μF) or picofarads (pF)]

$C \approx 7 \text{ pF per sq in of parallel plates separated by } \frac{1}{32} \text{ in of air.}$

C = The symbol for capacitor on part lists and schematics.

C = The symbol for coulomb (unit of quantity of charge) (Seldom used in electronics)

c = Obsolete symbol for cycles per second. [Use hertz (Hz)]

c = The symbol for the velocity of light or electromagnetic waves (physics). (Not recommended. Use v for velocity in electronics)

Capacitance, Series Circuits	C	Applicable Notes	Terms
$C_t = (C_1^{-1} + C_2^{-1} \dots + C_n^{-1})^{-1}$		①	C
$C_x = (C_t^{-1} - C_1^{-1})^{-1}$		②	
$C_t = \omega^{-1} [(X_C)_1 + (X_C)_2 \dots + (X_C)_n]^{-1}$		① ②	X_C
$C_t = -\omega^{-1} [(-X_1) + (-X_2) \dots + (-X_n)]^{-1}$		③	$-X$
$C = D/(\omega R_s)$	Series reactive element must be capacitive	① ②	D R_s
$C = (\omega R_s Q)^{-1}$	Series reactive element must be capacitive.	① ②	Q R_s
$C = [-\omega R_s (\tan \theta_Z)]^{-1}$	θ_Z must be negative	① ②	R_s θ_Z
$C = [-\omega Z (\sin \theta_Z)]^{-1}$	θ_Z must be negative	① ②	Z θ_Z
Series to Parallel Conversion		① ②	C_s R_s
$C_p = [(\omega^2 R_s^2 C_s) + C_s^{-1}]^{-1}$		④	

C Notes:

- ① C = Capacitance, D = Dissipation Factor, Q = Quality Factor, R = Resistance, X_C and $-X$ = Capacitive Reactance, Z = Impedance, θ = Phase Angle, ω = Angular Velocity
Subscripts: C = capacitive, n = any number, p = parallel, s = series, t = total or equivalent, x = unknown
- ② $x^{-1} = 1/x$, $\omega = 2\pi f$
- ③ B and X are magnitudes, however both B and X are often "given" the signs usually associated with capacitive and inductive quantities.
In all formulas in this handbook $-B = B_C$, $-X = X_C$, $+B = B_L$ and $+X = X_L$
- ④ Equivalent capacitance varies with frequency.

Capacitance, Parallel Circuits	C	Applicable Notes	Terms
$C_t = [(B_C)_1 + (B_C)_2 \dots + (B_C)_n] / \omega$		① ②	B_C
$C_t = [(-B_1) + (-B_2) \dots + (-B_n)] / -\omega$		③ ⑤	$-B$
$C_t = C_1 + C_2 \dots + C_n$		①	C
$C_t = [(X_C)_1^{-1} + (X_C)_2^{-1} \dots + (X_C)_n^{-1}] / \omega$		① ②	X_C
$C_t = [(-X_1)^{-1} + (-X_2)^{-1} \dots + (-X_n)^{-1}] / -\omega$		③	$-X$
$C_p = (\omega R_p D)^{-1}$ Parallel reactive element known to be capacitive		① ②	D, R_p
$C_p = [G(\tan \theta_Y)] / \omega$ θ_Y must be positive		① ② ⑤	G, θ_Y
$C_p = Q / (\omega R_p)$ Parallel reactive element known to be capacitive		① ②	$Q R_p$
$C_p = (\tan \theta_Z) / (-\omega R_p)$ θ_Z must be negative		① ②	R_p, θ_Z
$C_p = [Y(\sin \theta_Y)] / \omega$ θ_Y must be positive		① ② ⑤	Y, θ_Y
$C_p = (\sin \theta_Z) / (-\omega Z)$ θ_Z must be negative		① ②	Z, θ_Z
$C_p = [I_t(\sin \theta_I) / (\omega E)]$ θ_I must be positive		① ② ⑤	$E I \theta_I$
Parallel to Series Conversion			
$C_s = (\omega^2 C_p R_p^2)^{-1} + C_p$		① ② ④	$C_p R_p$

C Notes: ⑤ B = Susceptance, E = rms Voltage, G = Conductance, I = rms Current, Y = Admittance

Capacitance Misc. Formulas	C	Applicable Notes	Terms
$C_r = (\omega^2 L)^{-1}$	C required for resonance. Series or parallel circuits	② ⑥	L
$C = Q/E$	C required for a charge of Q coulombs	⑥	E, Q
$C = Q^2/(2W)$	W = work equiv. stored energy in watt/sec Q = charge in coulombs	⑥	Q, W
$C = T/R$	C required for time constant T and resistor R	⑥	R, T
$C = (It)/E$	I = constant current E = voltage change after time t	⑥	C, E I

Capacitance of two parallel plates (conductors) separated by an insulator (dielectric)

$$C = (Ak)/(4.45d) \text{ approx. pF}$$

A = Useful area of each plate in square inches

d = Spacing or distance between plates in inches

k = Dielectric constant (Air = 1)

Capacitance of concentric cylinders (e.g., coaxial cable)

$$C = (7.354k)/[\log(D/d)] \text{ pF per foot length}$$

D = inside diameter of outside cylinder (inches)

d = outside diameter of inside cylinder (inches)

k = dielectric constant of material between cylinders
(Air = 1)

C Notes:

- ⑥ C_r = Resonant Capacitance, E = dc Voltage, I = dc Current, L = Inductance, Q = Charge in coulombs, t = Time in sec., T = Time Constant, W = Work in joules

D

Dissipation Factor Definitions

D = The symbol for dissipation factor

D = 1. The ratio of energy dissipated to the energy stored in dielectric material, in certain electric elements, or in certain electric structures.

2. The inverse of the quality factor Q. (also known as the storage or merit factor)

3. In certain electric elements or structures, the absolute value of the cotangent of the phase angle of the alternating current with respect to the voltage, the voltage with respect to the alternating current, the impedance, or the admittance.

D = A factor which usually has a numerical value of from zero to one and is expressed in either decimal or percentage form.

D = A factor most commonly associated with capacitor specifications or measurements, however may be used in all Q factor applications.

D \simeq Power factor when $D < .1$

D = A factor which is very useful for the calculation of equivalent series resistance. ($R_s = DX_C = D/(\omega C) = DX_L = D\omega L$)

D Notes:

① B = Susceptance, C = Capacitance, G = Conductance, L = Inductance, Q = Storage Factor, Quality Factor or Merit Factor, R = Resistance, X = Reactance, Y = Admittance, Z = Impedance, θ = Phase Angle, ω = Angular Velocity

Subscripts: p = parallel, s = series

② $\omega = 2\pi f$, $x^{-1} = 1/x$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $x^{-2} = 1/x^2$

③ Not valid for LC circuits.

Dissipation Factor, Series Circuits	D	Applicable Notes	Terms
$D = 1/Q$		①	Q
$D = \cotan \theta$ Exception ③		① ⑥	θ
$D = \omega C_s R_s$		① ②	$C_s R_s$
$D = \sqrt{(Z\omega C_s)^2 - 1}$		① ② ⑧	$C_s Z$
$D = R_s/(\omega L_s)$		① ②	$L_s R_s$
$D = \sqrt{[Z/(\omega L_s)]^2 - 1}$		① ② ⑧	$L_s Z$
$D = R_s/X_s$		① ④	$R_s X_s$
$D = [(Z/R_s)^2 - 1]^{-\frac{1}{2}}$ Exception ③		① ② ⑧	$R_s Z$
$D = \sqrt{(Z/X_s)^2 - 1}$		① ④ ⑧	$X_s Z$
$D_r = \omega C_s R_s = R_s/(\omega L_s)$		① ② ⑦	$C_s L_s R_s$
$D_r = R_s/X_C = R_s/X_L$		① ② ⑦	$X_C X_L R_s$

D Notes:

- ④ X_s may be X_C or X_L but not $(X_L - X_C)$
- ⑤ B may be B_C or B_L but not $(B_L - B_C)$
- ⑥ $\cotan x = 1/(\tan x)$
- ⑦ D_r = Dissipation Factor at Resonance,
 X_C = Capacitive Reactance,
 X_L = Inductive Reactance
- ⑧ If the resultant under the radical sign is negative, a mistake has occurred.

Dissipation Factor, Parallel Circuits	D	Applicable Notes	Terms
$D = 1/Q$		①	Q
$D = \cotan \theta$ Exception ③		① ⑥	θ
$D = G/B$		① ⑤	B G
$D = \sqrt{(Y/B)^2 - 1}$		① ⑤ ⑧	B Y
$D = (R_p \omega C_p)^{-1}$		① ②	C_p R_p
$D = \sqrt{[Y/(\omega C_p)]^2 - 1}$		① ② ⑧	C_p Y
$D = \sqrt{(Z \omega C_p)^{-2} - 1}$		① ② ⑧	C_p Z
$D = [(Y/G)^2 - 1]^{-\frac{1}{2}}$ Exception ③		① ② ⑧	G Y
$D = (\omega L_p)/R_p$		① ②	L_p R_p
$D = \sqrt{(Y \omega L_p)^2 - 1}$		① ② ⑧	L_p Y
$D = \sqrt{[(\omega L_p)/Z]^2 - 1}$		① ② ⑧	L_p Z
$D = X_p/R_p$		① ④	R_p X_p
$D = [(R_p/Z)^2 - 1]^{-\frac{1}{2}}$ Exception ③		① ② ⑧	R_p Z
$D = \sqrt{(X_p/Z)^2 - 1}$		① ④ ⑧	X_p Z

dB

Decibel Definitions and Formulas

dB = The symbol for decibel

dB = 1. The standard logarithmic unit for expressing power gain or loss.

2. One tenth of a bel. (The basic bel unit is very seldom used)

3. A power ratio only—according to the original definition and to a few purists.

4. A commonly used convenient unit for expressing voltage and current ratios. See—dB Note 2

Formulas for Definitions 1, 2, & 3

$$\text{dB} = 10 \log (P_o/P_i)$$

$$\text{dB} = 20 \log (E_o/E_i) \quad \text{only when } (Z_o/\theta_o) = (Z_i/\theta_i)$$

$$\text{dB} = 20 \log (I_o/I_i) \quad \text{only when } (Z_o/\theta_o) = (Z_i/\theta_i)$$

$$\text{dB} = 20 \log \left[\frac{(E_o \sqrt{Z_i \cos \theta_i})}{(E_i \sqrt{Z_o \cos \theta_o})} \right]$$

$$\text{dB} = 20 \log \left[\frac{(I_o \sqrt{Z_o \cos \theta_o})}{(I_i \sqrt{Z_i \cos \theta_i})} \right]$$

Formulas for Definition 4

$$\text{dB} = 10 \log (P_o/P_i)$$

$$\text{dB} = 20 \log (E_o/E_i)$$

$$\text{dB} = 20 \log (I_o/I_i)$$

dB Notes:

- ① log = logarithm to the base 10, P = Power, E = rms Voltage, I = rms Current, θ = Phase Angle, Subscripts: i = Input, o = Output
 - ② When using definition 4, it should be stated as dB voltage or current gain or loss, dB apparent power gain or loss, etc. ---, not as dB gain or loss or as dB power gain or loss.
 - ③ See also—dBm notes, dB editorial—opamp
-

dBm

Power in dB Definitions and Formulas

dBm = Symbol for decibels referenced to one milliwatt.

dBm = Power level expressed in decibels above or below one milliwatt.

$$\text{dBm} = L_{P(\text{mW})}$$

$$\text{dBm} = \text{V.U. (volume units) (sinewave only)}$$

$$\text{dBm} = 10(\log P) + 30$$

$$\text{dBm} = 10[\log(1000 P)]$$

$$\text{dBm} = 10[\log(E^2/R)] + 30$$

$$\text{dBm} = 10[\log(I^2 R)] + 30$$

$$\text{dBm} = 10[\log(EI \cos \theta)] + 30$$

$$\text{dBm} = 10[\log(I^2 Z \cos \theta)] + 30$$

$$\text{dBm} = 10\left(\log\left[\frac{E^2 \cos \theta}{Z}\right]\right) + 30$$

$$\text{dBm} = 10[\log(E^2 Y \cos \theta)] + 30$$

dBm Notes:

- ① P = Power, E = dc or rms Voltage, I = dc or rms Current, Y = Admittance, Z = Impedance, θ = Phase Angle, cos = cosine, log = Logarithm to the base 10.
 - ② When using a calculator to obtain the log of a number smaller than one, the value of both the characteristic and the mantissa are likely to be different than the value obtained from log tables. The calculator value will have both a negative characteristic and a negative mantissa. This is the correct value to use. (Log tables always have a positive mantissa)
-

E

Voltage Definitions

E = Symbol for electromotive force (emf)
(emf is more commonly called voltage or potential)

E = The electric force which causes current to flow through a conductor.

E = Potential measured in volts (V)

$E = E_{dc}$ or $|E_{rms}|$

E = Complete description of voltage

$E = E_{POLAR} = E_{RECTANGULAR}$

$E = E/\theta_E = E_R + (\pm E_X)j$

$E_R = E/0^\circ = E_R + 0j$

$E_C = E/-90^\circ = 0 + (-E_X)j = 0 - jE_X$

$E_L = E/+90^\circ = 0 + (+E_X)j = 0 + jE_X$

$E_R = E_{\text{magnitude}}$ identified as resistive or real

$E_C = E_{\text{magnitude}}$ identified as capacitive

$E_L = E_{\text{magnitude}}$ identified as inductive

$-E_X = E_C$ "given" the sign associated with capacitive quantities.

$+E_X = E_L$ "given" the sign associated with inductive quantities.

$\pm E_X =$ Identification of E_X as capacitive or inductive in the resultant of many formulas.

e = The instantaneous value of voltage

Note: The symbol V is also used for voltage and predominates in active circuits. See—V, Active Circuits

Voltage, DC Circuits	E	Applicable Notes	Terms	Circuit Type
$E_t = (\pm E_1) + (\pm E_2) \dots + (\pm E_n)$		① ②	E	Series Circuits
$E_t = P_t/I$		① ②	I P	
$E_t = (P_1 + P_2 \dots + P_n)/I$		① ②	I P	
$E_t = IR_t$		① ②	I R	
$E_t = I(R_1 + R_2 \dots + R_n)$		① ②	I R	
$E_t = \sqrt{P_t R_t}$		① ②	P R	Parallel Circuits
$E_t = \sqrt{(P_1 + P_2 \dots + P_n)(R_1 + R_2 \dots + R_n)}$		① ②	P R	
$E = I_1/G_1 = I_t/G_t$		① ②	G I	
$E = \sqrt{P_1/G_1} = \sqrt{P_t/G_t}$		① ②	G P	
$E = P_1/I_1 = P_t/I_t$		① ②	I P	
$E = I_1 R_1 = I_t R_t$		① ②	I R	Complex Circuits
$E = \sqrt{R_1 P_1} = \sqrt{R_t P_t}$		① ②	R P	
See—R, complex circuits See—R, delta to Y conversion See also—I and P if necessary Simplify circuit and use above formulas				

**Transient Voltages,
Voltage Ratios**

e E

$e_C := E \left[1 - (\epsilon^{-1})^{\frac{t}{RC}} \right]$ $e_C = .6321 E \quad \text{when } t = RC \text{ (1 time constant)}$ $e_C = (It)/C \quad (I = \text{constant current})$	Capacitor Voltage During Charge thru Resistor
$e_C = E/\epsilon^{\frac{t}{RC}}$ $e_C = .3679 E \quad \text{when } t = RC \text{ (1 time constant)}$ $e_C = E - [(It)/C] \quad (I = \text{constant current})$	Capacitor Voltage During Discharge thru Resistor
$e_L = E/\epsilon^{\frac{Rt}{L}}$ $e_L = .3679 E \quad \text{when } t = L/R \text{ (1 time constant)}$	Inductor Voltage During Energization thru Resistor
$e_L = -L(di/dt) \quad \left[\begin{array}{l} (di/dt) = \text{rate of current change} \\ \text{in (ampere/seconds)} \end{array} \right]$	Inductor Voltage Developed By Current Change
$E = Q/C \quad (Q = \text{Charge in coulombs})$	Voltage Developed by Electric Charge
$E_{av} = \left[\frac{(2\sqrt{2})}{\pi} \right] E_{rms} = .9003 E_{rms}$ $E_{av} = (2/\pi) E_{peak} = .6366 E_{peak}$ $E_{peak} = (\sqrt{2}) E_{rms} = 1.414 E_{rms}$ $E_{p-p} = (2\sqrt{2}) E_{rms} = 2.828 E_{rms}$ $E_{rms} = \left[\frac{\pi}{(2\sqrt{2})} \right] E_{av} = 1.111 E_{av}$ $E_{rms} = E_{eff}$ $E_{rms} = (1/\sqrt{2}) E_{peak} = .7071 E_{peak}$ $E_{rms} = \left[1/(2\sqrt{2}) \right] E_{p-p} = .3535 E_{p-p}$	Voltage Ratios

E Notes:

① General

B = Susceptance ⑥, C = Capacitance, e = Instantaneous Voltage, E = Voltage Magnitude or DC Voltage ⑥, \mathbf{E} = Magnitude and Phase Angle of Voltage, f = Frequency, G = Conductance, I = Current, j = Imaginary Number ③, L = Inductance, P = Power, Q = Quantity of Electrical Charge, R = Resistance, X = Reactance ⑥, Y = Admittance, Z = Impedance, ϵ = Base of Natural Logarithms ③, π = Ratio of Circumference to diameter of a circle ③, θ = Phase Angle ⑥, ω = Angular Velocity ③

② Subscripts

C = capacitive, E = voltage, I = current, L = inductive, n = any number, o = output, p = parallel circuit, r = (of or at) resonance, s = series circuit, t = total or equivalent, X = reactive, Y = admittance, Z = impedance

③ Constants

$j = i$ $j = \sqrt{-1}$ $j = 90^\circ$ multiplier, $\epsilon = 2.718+$ $\epsilon^{-1} = .36788-$, $\pi = 3.1416-$ $2\pi = 6.2832-$, $\omega = 2\pi f$ $\omega = 6.2832f$

④ Algebra

$x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $x^{\frac{1}{2}} = \sqrt{x}$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $|x|$ = absolute value or magnitude of x

⑤ Trigonometry

sin = sine, cos = cosine, tan = tangent, \tan^{-1} = arc tangent

⑥ Reminders

$\pm\theta$ --- use the sign of the phase angle
 $\pm X$ --- $-X$ identifies X as capacitive (X_C)
 $+X$ identifies X as inductive (X_L)
 $\pm B$ --- $-B$ identifies B as capacitive (B_C)
 $+B$ identifies B as inductive (B_L)
 $\pm E_X$ --- $-E_X$ identifies E_X as capacitive (E_C)
 $+E_X$ identifies E_X as inductive (E_L)

Voltage, Series Circuits	E	Applicable Notes	Terms
$(E_C)_t = (E_C)_1 + (E_C)_2 \dots + (E_C)_n$			E_C
$(E_L)_t = (E_L)_1 + (E_L)_2 \dots + (E_L)_n$		① ②	E_L
$(E_R)_t = (E_R)_1 + (E_R)_2 \dots + (E_R)_n$			E_R
$(\pm E_X)_t = (E_L)_1 - (E_C)_1 + (E_L)_2 - (E_C)_2$		① ②	$E_C \quad E_L$
$(\pm E_X)_t = (\pm E_1) + (\pm E_2) \dots + (\pm E_n)$		⑥	$-E_X \quad +E_X$
$E_t = \sqrt{E_R^2 + E_C^2}$		① ②	$E_C \quad E_R$
$E_t = \sqrt{E_R^2 + E_L^2}$		① ②	$E_L \quad E_R$
$(E_C)_t = I\omega^{-1}(C_1^{-1} + C_2^{-1} \dots + C_n^{-1})$		① ② ③ ④	I C
$(E_L)_t = I\omega(L_1 + L_2 \dots + L_n)$		① ② ③	I L
$(E_R)_t = I(R_1 + R_2 \dots + R_n)$		① ②	I R
$(E_C)_t = I [(X_C)_1 + (X_C)_2 \dots + (X_C)_n]$		① ②	I X_C
$(-E_X)_t = I [(-X_1) + (-X_2) \dots + (-X_n)]$		⑥	I -X
$(E_L)_t = I [(X_L)_1 + (X_L)_2 \dots + (X_L)_n]$		① ②	I X_L
$(+E_X)_t = I [(+X_1) + (+X_2) \dots + (+X_n)]$		⑥	I +X
$E = IZ$		①	I Z

Additional E magnitude formulas are included in E formulas starting on page 27.

Voltage, Parallel Circuits	E	Applicable Notes	Terms
$E = I_t / [(B_C)_1 + (B_C)_2 \dots + (B_C)_n]$		① ②	$I_t B_C$
$E = I_t / [(-B_1) + (-B_2) \dots + (-B_n)] $		④ ⑥	$I_t -B$
$E = I_t / [(B_L)_1 + (B_L)_2 \dots + (B_L)_n]$		① ②	$I_t B_L$
$E = I_t / [(+B_1) + (+B_2) \dots + (+B_n)]$		⑥	$I_t +B$
$E = I_t / [(\pm B_1) + (\pm B_2) \dots + (\pm B_n)] $		① ② ④ ⑥	$I_t \pm B$
$E = I_t / [\omega(C_1 + C_2 \dots + C_n)]$		① ② ③	$I_t C_p$
$E = I_t / (G_1 + G_2 \dots + G_n)$		① ②	$I_t G$
$E = I_t \omega [(L_p)_1^{-1} + (L_p)_2^{-1} \dots + (L_p)_n^{-1}]^{-1}$		① ② ③ ④	$I_t L_p$
$E = I_t [(R_p)_1^{-1} + (R_p)_2^{-1} \dots + (R_p)_n^{-1}]^{-1}$		① ② ④	$I_t R_p$
$E = I_t [(X_C)_1^{-1} + (X_C)_2^{-1} \dots + (X_C)_n^{-1}]^{-1}$		① ②	$I_t X_C$
$E = I_t [(-X_p)_1^{-1} + (-X_p)_2^{-1} \dots + (-X_p)_n^{-1}]^{-1} $		④ ⑥	$I_t -X_p$
$E = I_t [(X_L)_1^{-1} + (X_L)_2^{-1} \dots + (X_L)_n^{-1}]^{-1}$		① ②	$I_t X_L$
$E = I_t [(+X_p)_1^{-1} + (+X_p)_2^{-1} \dots + (+X_p)_n^{-1}]^{-1}$		④ ⑥	$I_t +X_p$
$E = I_t [(\pm X_p)_1^{-1} + (\pm X_p)_2^{-1} \dots + (\pm X_p)_n^{-1}]^{-1} $		① ② ④ ⑥	$I_t \pm X_p$
$E = I/Y$		①	$I Y$
$E = IZ$		①	$I Z$

$$E_t = \left\{ \left([E_1 \cos \theta_1] + [E_2 \cos \theta_2] \dots + [E_n \cos \theta_n] \right)^2 \right. \\ \left. + \left([E_1 \sin(\pm\theta_1)] + [E_2 \sin(\pm\theta_2)] \dots + [E_n \sin(\pm\theta_n)] \right)^2 \right\}^{1/2}$$

$$\theta_t = \tan^{-1} \left[\frac{([E_1 \sin(\pm\theta_1)] + [E_2 \sin(\pm\theta_2)] \dots + [E_n \sin(\pm\theta_n)])}{([E_1 \cos \theta_1] + [E_2 \cos \theta_2] \dots + [E_n \cos \theta_n])} \right]$$

Series Sum of $E_1/\theta_1, E_2/\theta_2, \dots, E_n/\theta_n$

$$E_t = \sqrt{([E_1 \cos \theta_1] - [E_2 \cos \theta_2])^2 + ([E_1 \sin(\pm\theta_1)] - [E_2 \sin(\pm\theta_2)])^2}$$

$$\theta_t = \tan^{-1} \left[\frac{([E_1 \sin(\pm\theta_1)] - [E_2 \sin(\pm\theta_2)])}{([E_1 \cos \theta_1] - [E_2 \cos \theta_2])} \right]$$

$E_1/\theta_1, E_2/\theta_2$ Differential



Complex Voltages,
Series & Differential

E

Voltage & Phase Important Notes

1. It should be understood by the reader that the phase angle of voltage and current is the same one and only phase angle of a circuit or of a circuit element. The fact that current leads the voltage while the voltage lags the current in an inductive circuit means only that the signs of the voltage and current phase angles are different.
 2. In a given circuit, the phase angle of voltage, current, impedance and admittance is the same one and only phase angle. The signs of the angle is the only difference. $\pm\theta_E = -(\pm\theta_I) = \pm\theta_Z = -(\pm\theta_Y)$.
 3. The voltage phase angle uses the current phase angle as a reference (0°) while the current phase angle uses the voltage phase angle as a reference (0°). Due to this fact, if the voltage phase angle is expressed, the current phase angle is 0° and if the current phase angle is expressed, the voltage phase angle is 0° . It should be obvious that the voltage and current phase angles cannot be used at the same time.
 4. The same applies to rectangular form voltage and current. Rectangular form current cannot have an imaginary (reactive) component when the rectangular form voltage has an imaginary (reactive) component. The reverse, obviously, is also true.
 5. Due to this confusing situation and the high probability of error, the author DOES NOT RECOMMEND THE USE OF POLAR OR RECTANGULAR FORM VOLTAGE OR CURRENT WHERE EACH USES THE OTHER AS A REFERENCE. THE USE OF THE GENERATOR AS THE PHASE REFERENCE IS RECOMMENDED.
 6. The following polar and rectangular form voltage formulas are listed for reference only. Proceed to the E_o and vector algebra E_o formulas.
-

**Voltage & Phase,
Series Circuits**

E

**Resistive & Reactive
Voltages
In Series**

E = The magnitude and phase angle of the voltage developed by current through a series circuit. ($\theta_1 = 0^\circ$)
See also $-\theta$

$$E_{\text{POLAR}} = E \angle \pm\theta_E$$

$E_{\text{RECT}} = 1$. The 0° and $\pm 90^\circ$ voltages which have a resultant equal to E_{POLAR} .

2. The voltages developed by current through series resistance and net reactance.

$$E_{\text{RECT}} = E_R + (\pm E_X) j$$

$$E_{\text{RECT}} = (E \cos \theta_E) + [E \sin(\pm\theta_E)] j$$

	Applicable Notes	Terms
$E_{\text{POLAR}} = \sqrt{E_R^2 + E_C^2} / \tan^{-1}(-E_C/E_R)$ $E_{\text{RECT}} = E_R - jE_C$	① ② ③ ⑤	E_R E_C
$E_{\text{POLAR}} = \sqrt{E_R^2 + E_L^2} / \tan^{-1}(E_L/E_R)$ $E_{\text{RECT}} = E_R + jE_L$	① ② ③ ⑤	E_R E_L
$E_{\text{POLAR}} = \sqrt{E_R^2 + E_{Xc}^2} / \tan^{-1}(-E_{Xc}/E_R)$ $E_{\text{RECT}} = E_R + (-E_X) j$	① ② ③ ⑤ ⑥	E_R E_{Xc}
$E_{\text{POLAR}} = \sqrt{E_R^2 + E_{XL}^2} / \tan^{-1}(+E_{XL}/E_R)$ $E_{\text{RECT}} = E_R + (+E_X) j$	① ② ③ ⑤ ⑥	E_R E_{XL}
$E_{\text{POLAR}} = \sqrt{E_R^2 + (E_L - E_C)^2} / \tan^{-1}[(E_L - E_C)/E_R]$ $E_{\text{RECT}} = E_R + (E_L - E_C) j$ $E_{\text{RECT}} = E_R + (\pm E_X) j$	① ② ③ ⑤ ⑥	E_R E_C E_L

Voltage and Phase, Series Circuits	E	Applicable Notes	Terms
$E = I\sqrt{R^2 + (\omega C)^{-2}}$ $\theta_E = \tan^{-1}(\omega CR)^{-1}$		① ② ③ ④ ⑤	I C R I C R
$E = I\sqrt{R^2 + (\omega L)^2}$ $\theta_E = \tan^{-1}[(\omega L)/R]$		① ② ③ ⑤	I L R I L R
$E = P/(I \cos \theta_Z)$ $\theta_E = \pm\theta_Z = -(\pm\theta_I)$		① ② ⑤ ⑥	I P $\pm\theta$ I P $\pm\theta$
$E = (IR)/(\cos \theta)$ $\theta_E = \pm\theta_Z = -(\pm\theta_I)$		① ② ⑤ ⑥	I R $\pm\theta$ I R $\pm\theta$
$E = (IX)/(\sin \theta) $ $\theta_E = \pm\theta_Z = -(\pm\theta_I)$		① ② ④ ⑤ ⑥	I X $\pm\theta$ I X $\pm\theta$
$E = IZ$ $\theta_E = \pm\theta_Z = -(\pm\theta_I)$		① ② ⑥	I Z $\pm\theta$ I Z $\pm\theta$
$E = I\sqrt{R^2 + [(\omega L) - (\omega C)^{-1}]^2}$ $\theta_E = \tan^{-1}([(\omega L) - (\omega C)^{-1}]/R)$		① ② ③ ⑤	I C L R I C L R
$E = I\sqrt{R^2 + (X_L - X_C)^2}$ $\theta_E = \tan^{-1}[(X_L - X_C)/R]$		① ② ⑤	I R X _C X _L

See previous page for definitions, **E_{POLAR}** and **E_{RECT}**

**Voltage and Phase,
Parallel Circuits**

E Voltage and Phase
When a parallel circuit
is driven by a current source

E = The magnitude and phase angle of the voltage developed by the total current through a parallel circuit. ($\theta_{IR} = 0^\circ$) See also— θ

$$E_{POLAR} = E \angle \pm \theta_E$$

E_{RECT} = 1. The 0° and $\pm 90^\circ$ voltages which have a resultant equal to **E_{POLAR}**.

2. The series equivalent voltages of a parallel circuit.

3. The voltages developed by current through the series equivalent of a parallel circuit.

$$E_{RECT} = (E \cos \theta_E) + [E \sin(\pm \theta_E)] j$$

$$E_{RECT} = (E_R)_s + [(\pm E_X)_s] j$$

	Applicable Notes	Terms
$E = I_t / \sqrt{G^2 + (B_L - B_C)^2}$ $\theta_E = \tan^{-1} [(B_L - B_C) / G]$	① ② ⑤ ⑥	$I_t \pm B G$
$E = (I_t \sin \theta) / (B_L - B_C) $ $\theta_E = -(\pm \theta_I) = -(\pm \theta_Y)$	① ② ⑤ ⑥ ⑦	$I_t \pm B \pm \theta$
$E = I_t / \sqrt{R^{-2} + [(\omega L)^{-1} - (\omega C)]^2}$ $\theta_E = \tan^{-1} (R [(\omega L)^{-1} - (\omega C)])$	① ② ③ ④ ⑤	$I_t CL R$
$E = (I_t \sin \theta) / [(\omega L)^{-1} - (\omega C)] $ $\theta_E = \pm \theta_Z = -(\pm \theta_I) = -(\pm \theta_Y)$	① ② ③ ④ ⑥	$I_t CL \pm \theta$
$E = (I_t \cos \theta) / G $ $\theta_E = -(\pm \theta_I) = -(\pm \theta_Y) = \pm \theta_Z$	① ② ④ ⑤ ⑥	$I_t G \pm \theta$

Voltage and Phase, Parallel Circuits With Current Source	E	Applicable Notes	Terms
$E = Z \sqrt{I_R^2 + (I_{X_L} - I_{X_C})^2}$ $\theta_E = \tan^{-1} [(I_{X_L} - I_{X_C})/I_R]$		① ② ③ ⑥	$I_X Z$ $I_R \pm I_X$
$E = I_t \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}$ $\theta_E = \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$		① ② ④ ⑤ ⑥	$\pm X$ $I_t R \pm X$
$E = (I_t R) \cos \theta$ $\theta_E = \pm \theta_Z = -(\pm \theta_I) = -(\pm \theta_Y)$		① ② ⑤ ⑥	$\pm \theta$ $I_t R \pm \theta$
$E = I_t \sin \theta / (X_L^{-1} - X_C^{-1}) $ $\theta_E = \pm \theta_Z = -(\pm \theta_I) = -(\pm \theta_Y)$		① ② ③ ④ ⑤ ⑥ ⑦	$\pm \theta$ $I_t \pm X \pm \theta$
$E = I_t / Y$ $\theta_E = -(\pm \theta_Y)$		① ② ⑥	$\pm \theta_Y$ $I Y \pm \theta_Y$
$E = I_t Z$ $\theta_E = \pm \theta_Z$		① ② ⑥	$\pm \theta_Z$ $I Z \pm \theta_Z$
$E = P / (I_t \cos \theta)$ $\theta_E = -(\pm \theta_I) = \pm \theta_Z$		① ② ⑤ ⑥	$\pm \theta$ $P I_t \pm \theta$
$E = \sqrt{(PZ) / (\cos \theta)}$ $\theta_E = \pm \theta_Z = -(\pm \theta_I)$		① ② ③ ⑥	$\pm \theta$ $P Z \pm \theta$

See previous page for definitions, **E_{POLAR}**, and **E_{RECT}**.

Complex Voltages, Series & Differential	E	Terms
$E_t = \sqrt{(E_R)_t^2 + (E_X)_t^2}$ $\theta_t = \tan^{-1} [(\pm E_X)_t / (E_R)_t]$ $(E_R)_t = (E_1 \cos \theta_1) + (E_2 \cos \theta_2) \dots$ $+ (E_n \cos \theta_n)$ $(\pm E_X)_t = [E_1 \sin(\pm \theta_1)] + [E_2 \sin(\pm \theta_2)] \dots$ $+ [E_n \sin(\pm \theta_n)]$		E_1/θ_1 E_2/θ_2 E_n/θ_n
$E_t = \sqrt{(E_R)_t^2 + (E_X)_t^2}$ $\theta_t = \tan^{-1} [(\pm E_X)_t / (E_R)_t]$ $(E_R)_t = (E_1 \cos \theta_1) - (E_2 \cos \theta_2)$ $(\pm E_X)_t = [E_1 \sin(\pm \theta_1)] - [E_2 \sin(\pm \theta_2)]$		E_1/θ_1 E_2/θ_2 Differential
$(\mathbf{E}_{RECT})_t = (\mathbf{E}_{RECT})_1 + (\mathbf{E}_{RECT})_2 \dots + (\mathbf{E}_{RECT})_n$ $\mathbf{E}_{RECT} = E_R \pm jE_X = E_R + (\pm E_X) j$ $(\mathbf{E}_{RECT})_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]$ $+ [(\pm E_X)_1 + (\pm E_X)_2 \dots + (\pm E_X)_n] j$		$(\mathbf{E}_{RECT})_1$ $(\mathbf{E}_{RECT})_2$ $(\mathbf{E}_{RECT})_n$
$(\mathbf{E}_{RECT})_t = (\mathbf{E}_{RECT})_1 - (\mathbf{E}_{RECT})_2$ $\mathbf{E}_{RECT} = E_R \pm jE_X = E_R + (\pm E_X) j$ $(\mathbf{E}_{RECT})_t = [(E_R)_1 - (E_R)_2]$ $+ [(\pm E_X)_1 - (\pm E_X)_2] j$		$(\mathbf{E}_{RECT})_1$ $(\mathbf{E}_{RECT})_2$ Differential

E Notes:

- ① $E/\theta_E = E_{POLAR}$
- ② $E_R = E_{0^\circ} = +E = \text{"Real" numbers}$ ($-E_R = E_{180^\circ}$)
- ③ $E = |E| = E_{polar\ magnitude}$, $\pm E_X = E_{\pm 90^\circ}$
- ④ $+E_X = E_{+90^\circ} = E_L = E \sin(+\theta)$
- ⑤ $-E_X = E_{-90^\circ} = E_C = E \sin(-\theta)$


E_o

Output Voltage & Phase

$$E_o = E_g [(R_2/R_1) + 1]^{-1}$$

$$E_o = (E_g R_2)/(R_1 + R_2)$$
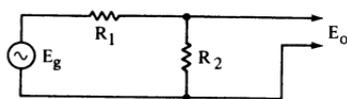
$$\theta_{E_o} = \theta_{E_g} = 0^\circ$$




$$E_o = (E_g R)/\sqrt{R^2 + X_C^2}$$

$$E_o = E_g (\cos \theta_{Z_i})$$

$$\theta_{E_o} = -(-\theta_{Z_i}) = \tan^{-1}(X_C/R)$$

(E_o Leads E_g)

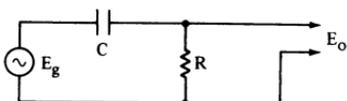


$$E_o = (E_g R)/\sqrt{R^2 + X_L^2}$$

$$E_o = E_g (\cos \theta_{Z_i})$$

$$\theta_{E_o} = -(+\theta_{Z_i}) = \tan^{-1} - (X_L/R)$$

(E_o Lags E_g)

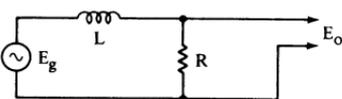


$$E_o = (E_g X_C)/\sqrt{R^2 + X_C^2}$$

$$E_o = |E_g (\sin \theta_{Z_i})|$$

$$\theta_{E_o} = -(-\theta_{Z_i}) - 90^\circ = [\tan^{-1}(X_C/R)] - 90^\circ$$

(E_o Lags)

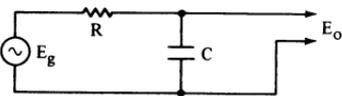

E_o Notes:

- ① E_g = Generator voltage, Z_i = Input impedance, θ_{E_o} = Phase angle of output voltage
 - ② $X_L = \omega L$, $X_C = (\omega C)^{-1}$, $\omega = 2\pi f$
 - ③ $x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $x^{\frac{1}{2}} = \sqrt{x}$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$
 - ④ \tan^{-1} = arc tangent, \sin = sine, \cos = cosine
-

E_o


Output
Voltage & Phase

$$E_o = (E_g X_L) / \sqrt{R^2 + X_L^2}$$

$$E_o = |E_g (\sin \theta_{Zi})|$$

$$\theta_{Eo} = -(\pm \theta_{Zi}) + 90^\circ = 90^\circ - [\tan^{-1}(X_L/R)]$$

θ_{Eo} Leads θ_{Eg}

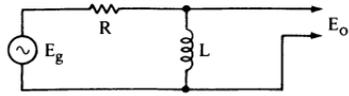


$$E_o = (E_g R) / \sqrt{R^2 + (X_L - X_C)^2}$$

$$E_o = E_g (\cos \theta_{Zi})$$

$$\theta_{Eo} = -(\pm \theta_{Zi}) = \tan^{-1} [(X_C - X_L)/R] = 0^\circ @ f_r$$

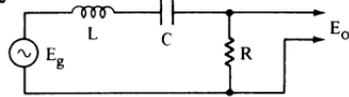
$$\theta_{Eo} = 0^\circ @ f_r, \text{ near } +90^\circ @ \text{ vlf}, \text{ near } -90^\circ @ \text{ vhf}$$



$$E_o = (E_g X_C) / \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta_{Eo} = -(\pm \theta_{Zi}) - 90^\circ = \left(\tan^{-1} [(X_C - X_L)/R] \right) - 90^\circ$$

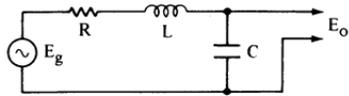
$$\theta_{Eo} = -90^\circ @ f_r, \text{ near } 0^\circ @ \text{ vlf}, \text{ near } -180^\circ @ \text{ vhf}$$



$$E_o = (E_g X_L) / \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta_{Eo} = +90^\circ - (\pm \theta_{Zi}) = 90^\circ - \left(\tan^{-1} [(X_L - X_C)/R] \right)$$
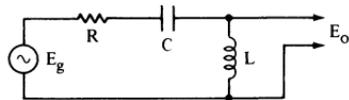
$$\theta_{Eo} = +90^\circ @ f_r, \text{ near } 0^\circ @ \text{ vhf}, \text{ near } 180^\circ @ \text{ vlf}$$



LCR Filter
Networks

E_o

Output
Voltage & Phase

$$E_o = (E_g R) / Z_i$$


$$E_o = E_g (\cos \theta_{Z_i})$$

$$\theta_{E_o} = -(\pm \theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{R^2 + (X_L^{-1} - X_C^{-1})^{-2}} \quad \text{①}$$

$$\theta_{Z_i} = \tan^{-1} [R(X_C^{-1} - X_L^{-1})]^{-1} \quad \text{②}$$
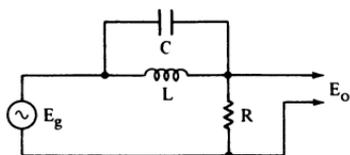
$$\theta_{E_o} = 0^\circ @ f_r, \text{ Lags } \theta_{E_g} \text{ below } f_r, \text{ Leads } \theta_{E_g} \text{ above } f_r$$



$$E_o = (E_g X_C) [R_s^2 + (X_{L_s} - X_C)^2]^{-\frac{1}{2}}$$


$$\theta_{E_o} = \theta_{X_C} - \theta_{Z_i}$$

$$\theta_{E_o} = (-90^\circ) - (\pm \theta_{Z_i})$$

$$\theta_{E_o} = (-90^\circ) - \left(\tan^{-1} [(X_{L_s} - X_C) / R_s] \right)$$

$$\text{where } R_s = [(R/X_L^2) + R^{-1}]^{-1}$$
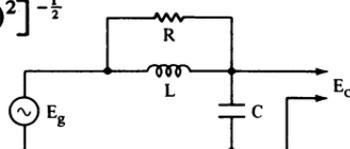
$$X_{L_s} = [(X_L/R^2) + X_L^{-1}]^{-1}$$



$$E_o = (E_g X_L) [R_s^2 + (X_L - X_{C_s})^2]^{-\frac{1}{2}}$$


$$\theta_{E_o} = \theta_{X_L} - \theta_{Z_i}$$

$$\theta_{E_o} = +90^\circ - (\pm \theta_{Z_i})$$

$$\theta_{E_o} = +90^\circ - \left(\tan^{-1} [(X_L - X_{C_s}) / R_s] \right)$$

$$\text{where } R_s = [(R/X_C^2) + R^{-1}]^{-1}$$
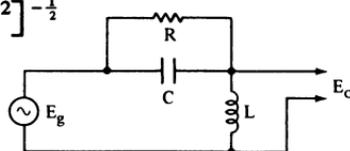
$$X_{C_s} = [(X_C/R^2) + X_C^{-1}]^{-1}$$



**LCR Filter
Networks**

E_o

**Output
Voltage & Phase**

$$E_o = E_g [Z_i (Y_L^{-1} - X_C^{-1})]^{-1} \quad \textcircled{a}$$


$$E_o = |E_g (\sin \theta_{Z_i})^{-1}| \quad \textcircled{a}$$

$$\theta_{E_o} = \pm 90^\circ - (\pm \theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{R^2 + (X_L^{-1} - X_C^{-1})^{-2}} \quad \textcircled{a}$$

$$\theta_{Z_i} = \tan^{-1} [R(X_L^{-1} - X_C^{-1})]^{-1} \quad \textcircled{a}$$
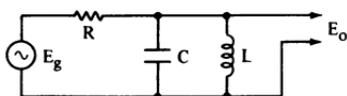
$$\theta_{E_o} = 0^\circ @ f_r, \text{ Leads } \theta_{E_g} \text{ below } f_r, \text{ Lags } \theta_{E_g} \text{ above } f_r$$



$$E_o = (E_g Z_2) / Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$Z_i = [R_s^2 + (X_L - X_{Cs})^2]^{1/2}, \theta_{Z_i} = \tan^{-1} [(X_L - X_{Cs}) / R_s]$$

$$Z_2 = (R^{-2} + X_C^2)^{-1/2}, \theta_{Z_2} = \tan^{-1} (R / X_C)$$

$$\text{where } R_s = [(R / X_C^2) + R^{-1}]^{-1}$$
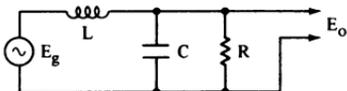
$$X_{Cs} = [(X_C / R^2) + X_C^{-1}]^{-1}$$



$$E_o = (E_g Z_2) / Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$Z_i = [R_s^2 + (X_{Ls} - X_C)^2]^{1/2}, \theta_{Z_i} = \tan^{-1} [(X_{Ls} - X_C) / R_s]$$

$$Z_2 = (R^{-2} + X_L^2)^{-1/2}, \theta_{Z_2} = \tan^{-1} (R / X_L)$$

$$\text{where } R_s = [(R / X_L^2) + R^{-1}]^{-1}$$
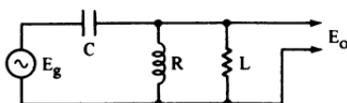
$$X_{Ls} = [(X_L / R^2) + X_L^{-1}]^{-1}$$



**LCR Filter
Networks**

E_o

**Output
Voltage & Phase**

$$E_o = [E_g(X_L - X_C)]/Z_i$$


$$E_o = |E_g(\sin \theta_{Z_i})|$$

$$\theta_{E_o} = \pm 90^\circ - (\pm \theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta_{Z_i} = \tan^{-1} [(X_L - X_C)/R]$$

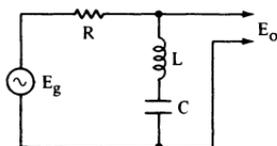$\theta_{E_o} = 0^\circ$ @ f_r , Lags θ_{E_g} below f_r , Leads θ_{E_g} above f_r



$$E_o = (E_g Z_2)/Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$\theta_{E_o} = (-\theta_{Z_2}) - (\pm \theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta_{Z_i} = \tan^{-1} [(X_L - X_C)/R]$$
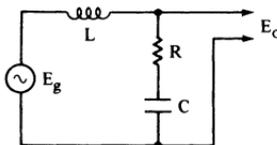
$$Z_2 = \sqrt{R^2 + X_C^2}, \theta_{Z_2} = \tan^{-1} (-X_C/R)$$



$$E_o = (E_g Z_2)/Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$\theta_{E_o} = (+\theta_{Z_2}) - (\pm \theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta_{Z_i} = \tan^{-1} [(X_L - X_C)/R]$$
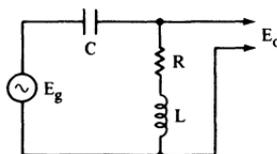
$$Z_2 = \sqrt{R^2 + X_L^2}, \theta_{Z_2} = \tan^{-1} (X_L/R)$$



E_o

Output
Voltage & Phase

$$E_o = (E_g Z_2)/Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$\theta_{E_o} = (-\theta_{Z_2}) - (-\theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{(R_1 + R_2)^2 + X_C^2}$$

$$\theta_{Z_i} = \tan^{-1} [-X_C/(R_1 + R_2)]$$
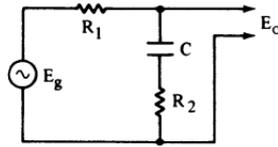
$$Z_2 = \sqrt{R_2^2 + X_C^2}, \theta_{Z_2} = \tan^{-1} (-X_C/R_2)$$



$$E_o = (E_g Z_2)/Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$\theta_{E_o} = (+\theta_{Z_2}) - (+\theta_{Z_i})$$

$$\text{where } Z_i = \sqrt{(R_1 + R_2)^2 + X_L^2}$$

$$\theta_{Z_i} = \tan^{-1} [X_L/(R_1 + R_2)]$$
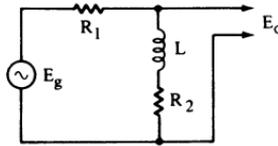
$$Z_2 = \sqrt{R_2^2 + X_L^2}, \theta_{Z_2} = \tan^{-1} (X_L/R_2)$$



$$E_o = (E_g Z_2)/Z_i$$


$$\theta_{E_o} = \theta_{Z_2} - \theta_{Z_i}$$

$$E_o = [E_g (R_2^{-2} + X_{C_2}^{-2})^{-\frac{1}{2}}] / [(R_1 + R_{2s})^2 + (X_{C_1}^{-1} + X_{C_{2s}}^{-1})^{-2}]^{\frac{1}{2}}$$

$$\theta_{E_o} = [\tan^{-1} (R_2 / -X_{C_2})] - (\tan^{-1} [(R_1 + R_{2s}) / -(X_{C_1}^{-1} + X_{C_{2s}}^{-1})])$$

$$\text{where } R_{2s} = [(R_2 / X_{C_2}^2) + R_2^{-1}]^{-1}$$
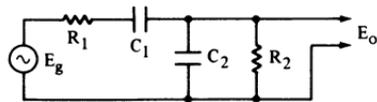
$$X_{C_{2s}} = [(X_{C_2} / R_2^2) + X_{C_2}^{-1}]^{-1}$$




**Networks
Driven By
Current Source**

E_o

**Output
Voltage & Phase**


$$E_o = I_g R$$

$$\theta_{E_o} = 0^\circ$$

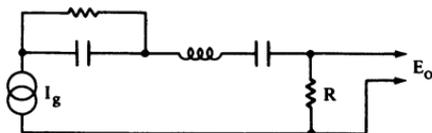


$$E_o = I_g X_C$$
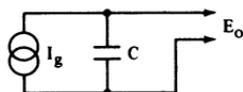
$$\theta_{E_o} = -90^\circ (\theta_{E_o} \text{ Lags } \theta_{I_g})$$



$$E_o = I_g X_L$$
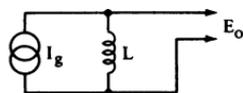
$$\theta_{E_o} = +90^\circ (\theta_{E_o} \text{ Leads } \theta_{I_g})$$




$$E_o = I_g Z$$

$$E_o = I_g \sqrt{R^2 + X_C^2}$$

$$\theta_{E_o} = (-\theta_Z) = \tan^{-1}(-X_C/R)$$

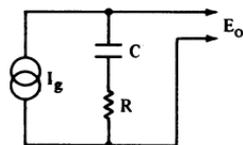$\theta_{E_o} \text{ Lags } \theta_{I_g}$




$$E_o = I_g Z$$

$$E_o = I_g \sqrt{R^2 + X_L^2}$$

$$\theta_{E_o} = (+\theta_Z) = \tan^{-1}(X_L/R)$$

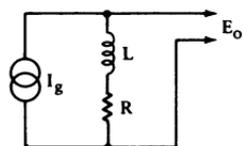$\theta_{E_o} \text{ Leads } \theta_{I_g}$



Note: $\text{---}\text{---}$ = Infinite impedance alternating current source

**Networks
Driven By
Current Source**


E_o

**Output
Voltage & Phase**

$$E_o = I_g Z$$

$$E_o = I_g (R^{-2} + X_C^{-2})^{-\frac{1}{2}}$$
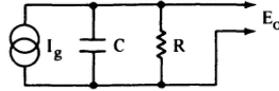
$$\theta_{E_o} = +(-\theta_Z) = \tan^{-1}(R/-X_C)$$




θ_{E_o} Lags θ_{I_g}

$$E_o = I_g Z$$

$$E_o = I_g (R^{-2} + X_L^{-2})^{-\frac{1}{2}}$$
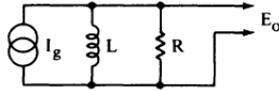
$$\theta_{E_o} = +(+\theta_Z) = \tan^{-1}(R/X_L)$$




θ_{E_o} Leads θ_{I_g}

$$E_o = I_g Z$$

$$\theta_{E_o} = +(\pm\theta_Z)$$

$$E_o = I_g [R^{-2} + (X_L^{-1} - X_C^{-1})^2]^{-\frac{1}{2}} = I_g R @ f_r$$
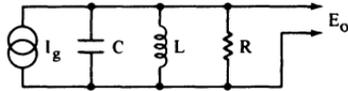
$$\theta_{E_o} = \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$$




$$E_o = I_g Z$$

$$\theta_{E_o} = +(\pm\theta_Z)$$

$$E_o = I_g \sqrt{R^2 + (X_L - X_C)^2}$$
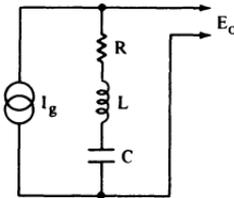
$$\theta_{E_o} = \tan^{-1} [(X_L - X_C)/R]$$



**Networks
Driven By
Current Source**

E_o


**Output
Voltage & Phase**

$$E_o = I_g Z$$

$$\theta_{E_o} = \pm \theta_Z$$

$$E_o = I_g [R^{-2} + (X_L - X_C)^{-2}]^{-\frac{1}{2}}$$
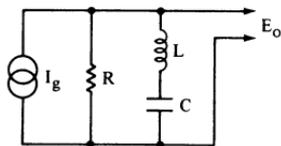
$$\theta_{E_o} = \tan^{-1} [R/(X_L - X_C)]$$




$$E_o = I_g Z$$

$$\theta_{E_o} = \pm \theta_Z = \pm 90^\circ$$

$$E_o = |I_g [X_{C1}^{-1} + (X_L - X_{C2})^{-1}]^{-1}|$$

Ⓐ

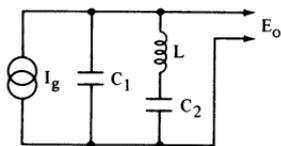


$$E_o = I_g Z$$

$$\theta_{E_o} = \pm \theta_Z = \pm 90^\circ$$

$$E_o = |I_g [X_{L1}^{-1} + (X_{L2} - X_C)^{-1}]^{-1}|$$


Ⓐ

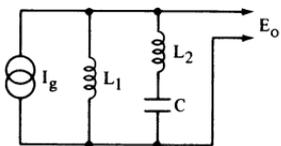

$$E_o = (I_g Z_i X_{C2}) / (X_L - X_{C2})$$

$$\theta_{E_o} = (\pm \theta_{Z_i}) + (-90^\circ) - (\pm 90^\circ)$$
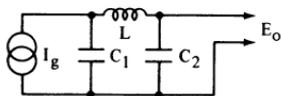
$$E_o = I_g / [X_{C1}^{-1} + X_{C2}^{-1} - (X_L / X_{C1} X_{C2})]$$



See also—Z complex circuits, Y complex circuits

Note Ⓐ

If the reciprocal of zero is presented, $E_o = \infty$.

E

Voltage Vector Algebra

Vector Algebra AC Ohms Law

$$\mathbf{E}_g = E_g / 0^\circ \text{ or } \mathbf{I}_g = I_g / 0^\circ$$

$$\mathbf{E} = \mathbf{I}_g \mathbf{Z} = I_g Z / 0^\circ + \theta_Z = \pm \theta_Z$$

$$\mathbf{I} = \mathbf{E}_g / \mathbf{Z} = E_g / Z / 0^\circ - \theta_Z = -(\pm \theta_Z)$$

$$\mathbf{Z} = \mathbf{E}_g / \mathbf{I} = E_g / I / 0^\circ - \theta_I = -(\pm \theta_I)$$

$$\mathbf{Z} = \mathbf{E} / \mathbf{I}_g = E / I_g / \theta_E - 0^\circ = \pm \theta_E$$

Addition and Subtraction of Rect. Quantities

$$\mathbf{E}_1 + \mathbf{E}_2 = \mathbf{E}_{1(\text{RECT.})} + \mathbf{E}_{2(\text{RECT.})}$$

$$= [\mathbf{E}_R + (\pm \mathbf{E}_X) j]_1 + [\mathbf{E}_R + (\pm \mathbf{E}_X) j]_2$$

$$= [(\mathbf{E}_R)_1 + (\mathbf{E}_R)_2] + [(\pm \mathbf{E}_X)_1 + (\pm \mathbf{E}_X)_2] j$$

$$\mathbf{E}_1 - \mathbf{E}_2 = [(\mathbf{E}_R)_1 - (\mathbf{E}_R)_2] + [(\pm \mathbf{E}_X)_1 - (\pm \mathbf{E}_X)_2] j$$

$$|\pm \mathbf{E}_X| = E_L \quad |-\mathbf{E}_X| = E_C$$

$$\mathbf{I}_1 + \mathbf{I}_2 = \mathbf{I}_{1(\text{RECT.})} + \mathbf{I}_{2(\text{RECT.})}$$

$$= [\mathbf{I}_R - (\pm \mathbf{I}_X) j]_1 + [\mathbf{I}_R - (\pm \mathbf{I}_X) j]_2$$

$$= [(\mathbf{I}_R)_1 + (\mathbf{I}_R)_2] - [(\pm \mathbf{I}_X)_1 + (\pm \mathbf{I}_X)_2] j$$

$$\mathbf{I}_1 - \mathbf{I}_2 = [(\mathbf{I}_R)_1 - (\mathbf{I}_R)_2] - [(\pm \mathbf{I}_X)_1 - (\pm \mathbf{I}_X)_2] j$$

$$|\pm \mathbf{I}_X| = I_L \quad |-\mathbf{I}_X| = I_C$$

Note: The rectangular current of a series circuit represents current through an equivalent parallel circuit.

Note: See \mathbf{Z}_{RECT} for addition and subtraction of impedance

E_o


Output Voltage
Vector Algebra

$$I_g = I_g \angle 0^\circ$$

$$Z_i = Z$$

$$Z_o = Z$$

$$E_o = I_g Z$$

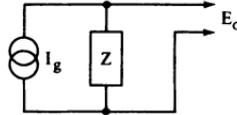



$$E_g = E_g \angle 0^\circ$$

$$Z_i = Z_1 + Z_2$$

$$Z_o = [Z_1^{-1} + Z_2^{-1}]^{-1}$$

$$Y_o = Y_1 + Y_2$$

$$E_o = (E_g Z_1) / Z_i$$

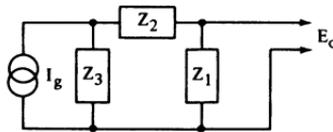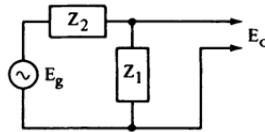

$$I_g = I_g \angle 0^\circ \quad E_g = I_g Z_i$$

$$Z_i = [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1}$$


$$Z_o = [Z_1^{-1} + (Z_2 + Z_3)^{-1}]^{-1}$$

$$Y_o = Y_1 + (Y_2^{-1} + Y_3^{-1})^{-1}$$

$$E_o = I_g Z_1 [1 - (Z_i / Z_3)]$$

E_o

Output Voltage Vector Algebra

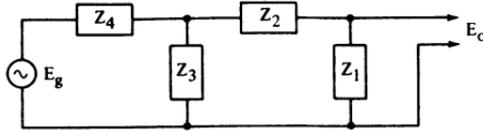


$$E_g = E_g / 0^\circ \quad I_g = E_g / Z_i$$

$$Z_i = Z_4 + [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1}$$

$$Z_o = (Z_1^{-1} + [Z_2 + (Z_3^{-1} + Z_4^{-1})^{-1}]^{-1})^{-1}$$

$$Y_o = Y_1 + [Y_2^{-1} + (Y_3 + Y_4)^{-1}]^{-1}$$
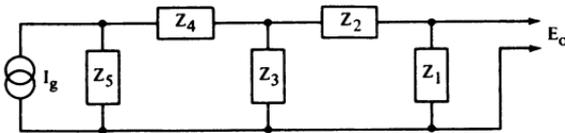
$$E_o = E_g [1 - (Z_4/Z_i)] / [(Z_2/Z_1) + 1]$$



$$I_g = I_g / 0^\circ \quad E_g = I_g Z_i$$

$$Z_i = [Z_5^{-1} + (Z_4 + [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1})^{-1}]^{-1}$$

$$Z_o = [Z_1^{-1} + (Z_2 + [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1})^{-1}]^{-1}$$

$$Y_o = Y_1 + (Y_2^{-1} + [Y_3 + (Y_2^{-1} + Y_1^{-1})^{-1}]^{-1})^{-1}$$


$$E_o = [I_g(Z_i - Z_4)] / [(Z_2/Z_1) + 1]$$

**Output
Voltage**

E_o

**Source
Conversions**

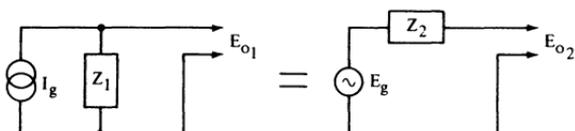Current Source to Voltage Source Conversion




$$E_g = I_g Z_1$$

$$\theta_{E_g} = \theta_{I_g} = 0^\circ$$

$$Z_2 = Z_1 \quad \text{at all frequencies}$$

$$E_{o2} = E_{o1} \quad \text{at all frequencies}$$

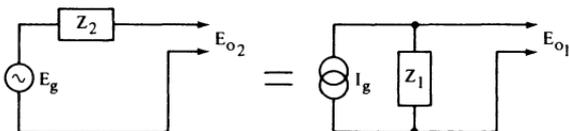Voltage Source to Current Source Conversion



$$I_g = E_g / Z_2$$

$$\theta_{I_g} = \theta_{E_g} = 0^\circ$$

$$Z_1 = Z_2 \quad \text{at all frequencies}$$

$$E_{o1} = E_{o2} \quad \text{at all frequencies}$$

Note: E_o may be loaded in any manner and the two outputs although changed will remain equal to each other.

e_N E_N

Noise Voltage

$e_{N(th)}$ = Thermal noise (white noise) voltage of resistance.
(Other symbols of thermal noise voltage include E_N ,
 E_{TH} , $E_{N(TH)}$, e_n , $e_{N(TH)}$, $e_{N(\sqrt{\sim})}$, $e_{N(\sqrt{Hz})}$, V_N , $V_{N(TH)}$
etc)

Note: Thermal noise voltage is always rms voltage regardless of symbol used.

$$e_{N(th)} = \sqrt{4kT_K R \overline{BW}}$$

k = Boltzmann constant ($1.38 \cdot 10^{-23}$ J/°K)

T_K = Temperature in Kelvin.
(°C + 273.15)

BW = Noise bandwidth in hertz.

(Noise measured with infinite attenuation of frequencies outside of bandwidth)

$e_{N(\sqrt{Hz})}$ = Thermal noise per hertz. (per root hertz)

$e_{N(\sqrt{Hz})} = 1.283 \cdot 10^{-10} \sqrt{R}$ @ 25°C and 1 Hz bandwidth

$E_{N(EX)}$ = The noise (1/f noise) voltage (rms) of a resistor in excess of thermal noise.

$E_{N(EX)}$ = Resistor excess noise voltage (rms) in microvolts per volt of dc voltage drop per decade of frequency.

$$E_{N(EX)} = 10^{-6} E_{dc} [\log^{-1}(\overline{NI}/20)]$$

NI = Noise Index in dB (a specification)

$NI = +10$ to -20 dB (carbon composition)

$NI = -10$ to -25 dB (carbon film)

$NI = -15$ to -40 dB (metal film or wirewound)

E_N Note: $\log^{-1} = \text{antilog}_{10}$

f

**Femto,
Frequency**

f = Symbol for femto.

f = A multiplier prefix meaning 10^{-15} unit.

f = Symbol for frequency.

f = The number of complete cycles per second of alternating current, sound, electromagnetic radiation, vibrations or certain other periodic events.

f = Frequency measured in hertz (Hz). (old cps)

f_c = Crossover or cutoff frequency. (3 dB down)

f_o = Oscillation, output or reference frequency.

f_r = Frequency of resonance.

$f = 1/t$ (t = time of one cycle)

$f = v/\lambda$

Sound in Air

$f \approx 1136/\lambda$ (λ in feet, @25°C)

$f \approx 346.3/\lambda$ (λ in meters, @25°C)

Electromagnetic waves including radio frequency and light in air or vacuum.

$f \approx (9.83 \cdot 10^8)/\lambda$ (λ in feet)

$f \approx (3 \cdot 10^8)/\lambda$ (λ in meters)

$f = 1/(2\pi X_C C)$

$f = X_L/(2\pi L)$


Notes: X = reactance, v = velocity, λ = wavelength, C = Capacitance, L = Inductance

f_c

Crossover Frequency

$$f_c = (2\pi CR)^{-1}$$

$$f_c = \frac{R}{2\pi L}$$

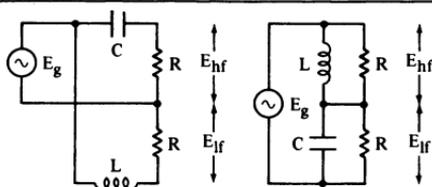

$$X_L = X_C = R \quad \text{when } f = f_c$$

$$Z = R, \quad (E_{if} + E_{hf}) = E_g \quad \text{when } f = 0 \text{ to } \infty$$


$$L = R/(2\pi f_c), \quad C = (2\pi f_c R)^{-1}$$

$$E_{C(\max)} = E_{L(\max)} = E_g$$

$$I_{L(\max)} = I_{C(\max)} = (E_g/R)$$

$$f_c = (2\sqrt{2}\pi CR)^{-1}$$

$$f_c = R/(\sqrt{2}\pi L)$$

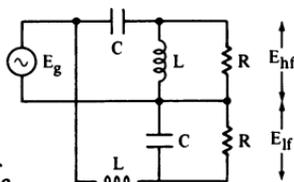

$$X_L = X_C = \sqrt{2} R \quad \text{when } f = f_c$$

$$Z = R, \quad (E_{if} + E_{hf}) = E_g \quad \text{when } f = 0 \text{ to } \infty$$

$$L = R/(2\pi f_c \sqrt{2}), \quad C = (2\pi f_c R \sqrt{2})^{-1}$$

$$E_{C(\max)} = E_{L(\max)} = 1.272 E_g$$


$$I_{L(\max)} = I_{C(\max)} = 1.029 (E_g/R)$$

f_c Notes:

- ① C = Capacitance, E = rms Voltage Magnitude, E = Polar or Rectangular form of Voltage, I = rms Current Magnitude, L = Inductance, R = Resistance, X = Reactance, Z = Polar or Rectangular form of Impedance

 f_c **Crossover
Frequency**
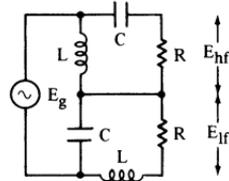
$$f_c = (\sqrt{2}\pi CR)^{-1}$$
$$f_c = \frac{R}{2\pi L\sqrt{2}}$$



$$X_L = X_C = R/\sqrt{2} \quad \text{when } f = f_c$$

$$Z = R, \quad (E_{lf} + E_{hf}) = E_g \quad \text{when } f = 0 \text{ to } \infty$$



$$L = R/(2\pi f_c \sqrt{2}), \quad C = (\sqrt{2}\pi f_c R)^{-1}$$

$$E_{C(\max)} = E_{L(\max)} = 1.029 E_g$$



$$I_{L(\max)} = I_{C(\max)} = 1.272 (E_g/R)$$

**3 dB Down
Frequency** f_c **Cutoff
Frequency**

$f_c = (2\pi CR)^{-1}$

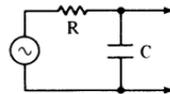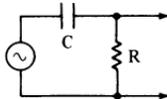

$f_c = R/(2\pi L)$

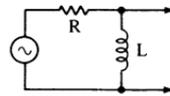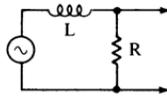 f_c Notes:

② E_C = Capacitor voltage, E_g = Generator voltage, E_L = Inductor voltage, E_{hf} = High freq. voltage, E_{lf} = Low freq. voltage, I_C = Capacitor current, I_L = Inductor current

③ $x^{-1} = 1/x$

④ $\pi = 3.1416$, $\sqrt{2} = 1.414$, $2\pi = 6.2832$, $\sqrt{2}\pi = 4.443$

**Exponential
Horn Formulas**

$$f' f_{FC}$$

**Flare Cutoff
Frequency**

f_{FC} = Symbol for flare cutoff frequency.

f_{FC} = In an exponential horn of infinite length, the frequency below which no energy is coupled through the horn.

f_{FC} = .5 to .8 of the lowest frequency of interest in the usual exponential horn.

$$f_{FC} = v / (18.13 \ell_{2A})$$

$$f_{FC} = v / (18.13 \sqrt{\ell_{2d}})$$

$$f_{FC} = v / (18.13 \sqrt{\ell_{2r}})$$

$$f_{FC} = (mv) / (4\pi)$$

f_{FC} Notes:

ℓ_{2A} , ℓ_{2d} , ℓ_{2r} = Length between points on the horn center line of double cross sectional area, double diameter, and double radius respectively.

m = Flare constant = $.6931/\ell_{2A} = .6931/\sqrt{\ell_{2d}}$

v = Velocity of sound \approx 13,630 in./sec, 1136 ft/sec, 346.3 meters/sec, 34,630 cm/sec at 25°C

f' = The lowest frequency of "satisfactory" horn loading due to area of horn mouth.

f' = Frequency at which:

1. Mouth diameter equals $\frac{1}{4}$ wavelength
2. Mouth circumference equals one wavelength
3. Mouth diameter equals $\frac{1}{3}$ wavelength
4. Mouth diameter equals $\frac{1}{2}$ wavelength
5. Mouth diameter equals $\frac{2}{3}$ wavelength

Low frequency horns are almost always compromised to use criteria 1, 2 or 3. Wavelength—See λ

f_o	Frequency of Oscillation or Output
$f_o \approx (2\pi\sqrt{LC})^{-1}$	(LC Oscillator)
$f_o \approx (2\pi RC\sqrt{6})^{-1}$	(Phase Shift Oscillator with three equal RC stages. May be phase lead or phase lag type)
$f_o \approx (2\pi R_1 C_1)^{-1}$	(Wein Bridge Oscillator) (when $R_1 C_1 = R_2 C_2$) See—Active Circuits

Output frequency of a electromechanical generator

$f_o = N_{pp}(\tau_{ps})$ (Number of pairs of poles times rev./sec)

f_r	Resonant Frequency Definitions
f_r = Symbol for frequency of resonance.	
$f_r = 1$. The frequency at which the circuit acts as a pure resistance. In a series circuit, the frequency at which the impedance is lowest. In a parallel circuit, the frequency at which the impedance is highest.	
2. The frequency at which the inductive reactance equals the capacitive reactance.	
<i>Note:</i> Definition 2 is commonly used due to simpler mathematics, but in many low Q circuits, it is a poor approximation. When Q is high, the difference between the definitions is negligible.	

Series Resonant Frequency


f_r

Resonant Frequency, Series Resonance

$$f_r = (2\pi\sqrt{LC})^{-1} \quad \text{Def. 1 \& 2}$$

$$@ f_r \quad Z = 0$$


$$X_L = X_C, \quad Q = \infty$$

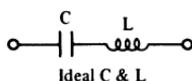

$$f_r = (2\pi\sqrt{LC})^{-1} \quad \text{Def. 1 \& 2}$$

$$@ f_r \quad Z = R$$
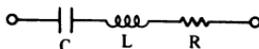
$$\theta_Z = 0^\circ, \quad X_L = X_C, \quad Q = X_L/R$$



$$f_r = \left[\frac{(LC) - (L/R)^2}{(LC > L^2/R^2)} \right]^{-1/2} / (2\pi) \quad \text{Def. 1}$$

$$f_r \approx (2\pi\sqrt{LC})^{-1}$$

$$@ f_r \quad \text{Def. 1}$$

$$@ f_r$$


$$Z = \left[(R/X_L^2) + R^{-1} \right]^{-1}$$

$$Z \approx X_L^2/R$$

$$\theta_Z = 0^\circ$$

$$X_C = \left[(X_L/R^2) + X_L^{-1} \right]^{-1} \quad X_C \approx X_L$$
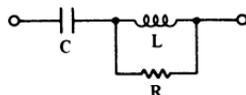
$$Q = X_C \left[(R/X_L^2) + R^{-1} \right] \quad Q \approx R/X_L$$



f_r Notes:

- ① C = Capacitance, L = Inductance, Q = "Q" Factor, R = Resistance, R_C = Resistance in capacitive circuit, R_L = Resistance in inductive circuit, X_C = Capacitive reactance, X_L = Inductive reactance, Z = Impedance, θ_Z = Phase angle of impedance

**Series Resonant
Frequency**

f_r

**Resonant Frequency,
Series Resonance**

$$f_r = \sqrt{(LC)^{-1} - (CR)^{-2}} / (2\pi) \quad \text{Def. 1}$$

exception = $\sqrt{-x}$

$$f_r \approx (2\pi\sqrt{LC})^{-1}$$


@ f_r Definition 1

$$Z = [(R/X_C^2) + R^{-1}]^{-1} \quad Z \approx X_C^2/R$$

$$\theta_Z = 0^\circ$$

$$X_L = [(X_C/R^2) + X_C^{-1}]^{-1} \quad X_L \approx X_C$$
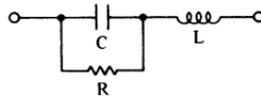
$$Q = X_L [(R/X_C^2) + R^{-1}] \quad Q \approx R/X_C$$



$$f_r = \sqrt{[(R_C^2 C)^{-1} - L^{-1}] / [(L/R_L^2) - C]} / (2\pi) \quad \text{Def. 1}$$

exception = $\sqrt{-x}$

$$f_r \approx (2\pi\sqrt{LC})^{-1}$$


@ f_r (Definition 1)

$$Z = [(R_C/X_C^2) + R_C^{-1}]^{-1} + [(R_L/X_L^2) + R_L^{-1}]^{-1}$$

$$\theta_Z = 0^\circ$$

$$[(X_L/R_L^2) + X_L^{-1}] = [(X_C/R_C^2) + X_C^{-1}]$$
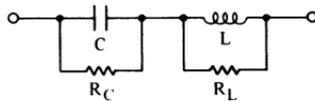
$$Q \approx [X_L(R_L^{-1} + R_C^{-1})]^{-1}$$



Parallel Resonant Frequency


f_r

Resonant Frequency, Parallel Resonance

$f_r = (2\pi\sqrt{LC})^{-1}$ Def. 1 & 2

@ $f_r, Z = \infty, \theta_Z = 0^\circ$


$X_C = X_L, Q = \infty$

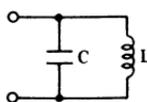

$f_r = (2\pi\sqrt{LC})^{-1}$ Def. 1 & 2

@ $f_r, Z = R, \theta_Z = 0^\circ$

$X_C = X_L, Q = R/X_L$

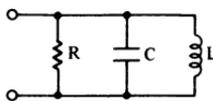

$f_r = \sqrt{(LC)^{-1} - (R/L)^2} / (2\pi)$ Def. 1

exception = $\sqrt{-x}$


$f_r \approx (2\pi\sqrt{LC})^{-1}$

@ $f_r \theta_Z = 0^\circ$

$Z = (X_L^2/R) + R \quad Z \approx X_L^2/R$

$X_C = (R^2/X_L) + X_L \quad X_C \approx X_L$

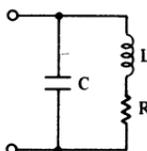$Q = [(X_L^2/R) + R] / X_C \quad Q \approx X_L/R$



f_r Notes:

- ② $x^{-1} = 1/x, x^{\frac{1}{2}} = \sqrt{x}, x^{-\frac{1}{2}} = 1/\sqrt{x}, x^{-2} = 1/x^2$
- ③ Def. 1 = f_r Definition 1 (max or min Z plus $\theta_Z = 0^\circ$)
- ④ $\omega_r =$ Resonant angular velocity = $2\pi f_r$
- ⑤ $L_p, R_{Cp}, R_{Lp} =$ Parallel equivalent quantities of series quantities

See also—Q, Z, Y

Parallel Resonant
Frequency


f_r

Resonant Frequency,
Parallel Resonance

$$f_r = [(LC) - (CR)^2]^{-\frac{1}{2}} / (2\pi) \quad \text{Def. 1} \quad (-x)^{-\frac{1}{2}} \text{ exception}$$

$$f_r \approx (2\pi\sqrt{LC})^{-1}$$

@ f_r Definition 1

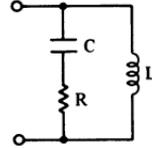

$$\theta_z = 0^\circ$$

$$Z = (X_C^2/R) + R \quad Z \approx X_C^2/R$$

$$X_L = (R^2/X_C) + X_C \quad X_L \approx X_C$$


$$Q = [(X_C^2/R) + R]/X_L \quad Q \approx X_C/R$$

$$f_r = \sqrt{[C^{-1} - (R_L^2/L)] / [L - (R_C^2 C)]} / (2\pi) \quad \text{Def. 1}$$

exception = $\sqrt{-x}$

$$f_r \approx (2\pi\sqrt{LC})^{-1}$$

@ f_r Definition 1

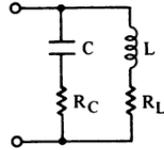

$$\theta_z = 0^\circ$$

$$Z = \left([(X_C^2/R_C) + R_C]^{-1} + [(X_L^2/R_L) + R_L]^{-1} \right)^{-1}$$

$$[(R_C^2/X_C) + X_C] = [(R_L^2/X_L) + X_L] \quad X_C \approx X_L$$

$$Q \approx [\omega_r L_p (R_L^{-1} + R_C^{-1})]^{-1}$$

$$Q \approx \sqrt{L} / [C(R_L + R_C)^2] / (2\pi)$$

$$Q \approx X_C / (R_L + R_C)$$

Frequency of Acoustical Resonance	f_r	Pipes and Tubes	Applicable Notes	
$f_r = v/(2\ell + 1.6d)$ $\ell = (v/2f_r) - (d/1.25)$ $d = (v/1.6f_r) - (1.25\ell)$			① ②	Open Pipe
$f_r = v/(2\ell + 1.8\sqrt{A})$ $\ell = (v/2f_r) - (\sqrt{A}/1.11)$ $A = \sqrt{(v/1.8f_r) - (1.11\ell)}$			③ ⑤	
$f_r = v/(4\ell + 1.6d)$ $\ell = (v/4f_r) - (d/2.5)$ $d = (v/1.6f_r) - (2.5\ell)$			① ②	
$f_r = v/(4\ell + 1.8\sqrt{A})$ $\ell = (v/4f_r) - (\sqrt{A}/2.22)$ $d = \sqrt{(v/1.8f_r) - (2.22\ell)}$			④ ⑤	

Pipe Notes:

- ① A = Cross sectional inside area of pipe
d = Inside diameter of pipe
 ℓ = Length of pipe
v = Velocity of sound in air
- ② $v \approx 13\ 630$ inches per second @ 25°C
 $v \approx 1136$ feet per second @ 25°C
 $v \approx 346.3$ meters per second @ 25°C
- ③ Also has secondary resonances @ $2f_r, 3f_r, 4f_r, 5f_r$, etc.
- ④ Also has secondary resonances @ $3f_r, 5f_r, 7f_r$, etc.
- ⑤ A, d, ℓ and v must all use the same unit of linear measure

Frequency of Acoustical Resonance	f_r	Applicable Notes	
$f_r = 2070[A/V^2]^{\frac{1}{4}}$ $f_r = 1948.7\sqrt{d/V}$ $V = d[1948.7/f_r]^2$ $d = V[f_r/1948.7]^2$		① ⑤ ⑥	Helmholtz Resonator (ported hollow sphere)
$f_r \approx 1424\sqrt{d/V}$ $V \approx d[1424/f_r]^2$ $d \approx V[f_r/1424]^2$	(Assuming speaker resonance is much lower than box resonance)	② ⑥	Closed Box Speaker Cabinet
$f_r \approx 2070[(.285A_1 + A_2)/V^2]^{\frac{1}{4}}$ $V \approx [2070^2\sqrt{.285A_1 + A_2}]/f_r^2$ $A_2 \approx [V^2(f_r/2070)^4] - .285A_1$		③ ⑤ ⑥	Ported Speaker Cabinet (Bass Reflex)
$f_r \approx 1713/\sqrt{(.85d_2 + \ell)} [(V_1/d_2^2) - (.25\pi\ell)]$ $\ell \approx [(1913d_2)^2/(f_r^2V_2)] - .85d_2$		④ ⑥	Ducted Port Speaker Cabinet

Cabinet Notes:

- ① A = Area of opening (port), d = Diameter of opening (port), V = Internal volume of sphere.
- ② d = Diameter of speaker opening, V = Internal volume of cabinet (neglect speaker volume)
- ③ A₁ = Area of speaker opening, A₂ = Area of port, V = Internal volume of cabinet (neglect speaker volume)
- ④ d₂ = Diameter of speaker opening and duct opening, V₁ = Internal volume of cabinet including duct volume. V₂ = Internal cabinet volume excluding duct, ℓ = Duct length.
- ⑤ $x^{\frac{1}{4}} = \sqrt{\sqrt{x}}$, $x^4 = (x^2)^2$
- ⑥ A, d, ℓ and V must all use the same unit of linear measure.

F

Farad,
Force etc

F = Symbol for farad.

F = Basic unit of capacitance.

F = Capacitance required to store one coulomb of charge at one volt potential.

F = Extremely large unit. Seldom used without a prefix symbol.

F = $\mu\text{F} \cdot 10^6$ (Typewriter—use uF)

F = $\text{nF} \cdot 10^9$ (just coming into usage in USA)

F = $\text{pF} \cdot 10^{12}$ ($\mu\mu\text{F}$ is not recommended)

Note: The prefix symbol m (milli) should not be used with F due to long time previous use of m with F to indicate microfarads.

F = Symbol for magnetic, electrostatic and mechanical force.

F = Magnetomotive force when units are in gilberts or ampere turns [gilbert = 1.257 ampere turns (At)]

F = $\phi\mathcal{R}$ where ϕ = total flux and \mathcal{R} = reluctance

Repulsive Electrostatic Force

F = $9 \cdot 10^9 [Q_1 Q_2 / d^2]$ dynes

Q_1, Q_2 = charge in coulombs on two bodies

d = distance in cm separating two bodies

$^\circ\text{F}$ = Symbol for degrees Fahrenheit.

$^\circ\text{F}$ = Unit of temperature. (USA)

F, F_n —See—NF (Noise Figure)

F_p —See—pf (Power Factor)

g G

Conductance Definitions and DC Formulas, Mutual Conductance

<p>G = Symbol for conductance.</p> <p>G = The ease with which direct current flows in a circuit at a given potential. The ease with which alternating current at a given potential flows in a purely resistive circuit. The reciprocal of resistance in any purely resistive circuit. The reciprocal of a pure resistance in parallel with other elements. The real part of admittance. The reciprocal of the equivalent parallel circuit resistance in a series circuit.</p> <p>G = Conductance in units of siemens (S). [old unit mho (Ω^{-1} or \mathcal{U}) is still common usage in USA]</p> <p>G = A parallel circuit quantity which may be used as easily in parallel circuits as resistance is used in series circuits.</p> <p>G = $R_p^{-1} / \underline{O}^\circ$ in terms of polar impedance.</p>	Definitions
<p>$G = 1/R$</p> <p>$G = I/E$</p> <p>$G = P/E^2$</p> <p>$G = I^2/P$</p> <p>$G_t = (R_1 + R_2 \dots + R_n)^{-1}$ Series Circuits</p> <p>$G_t = G_1 + G_2 \dots + G_n$ Parallel Circuits</p> <p>$G_t = R_1^{-1} + R_2^{-1} \dots + R_n^{-1}$ Parallel Circuits</p>	DC Formulas
<p>g_m = Symbol for mutual conductance or transconductance. See—Active Circuits</p> <p>$g_m = \Delta I_p / \Delta E_g$ (Vacuum Tubes)</p>	

Conductance, Series Circuits	G	Applicable Notes	Terms
$G = (R_1 + R_2 \dots + R_n)^{-1}$		① ②	R
$G = R / [R^2 + (\omega C)^{-2}]$		① ② ③	C R
$G = (\omega C Z^2)^{-1}$		① ② ③	C Z
$G = \omega C (\sin \theta)^2$		① ③ ④ ⑦	C θ
$G = I/E_R$		① ⑤	E_R I
$G = P/E_R^2$		① ⑤	E_R P
$G = I^2/P$		①	I P
$G = R / [R^2 + (\omega L)^2]$		① ③	L R
$G = (\omega L)/Z^2$		① ③	L Z
$G = (\sin \theta)^2 / (\omega L)$		① ③ ④ ⑦	L θ

G Notes:

- ① G IS INTRINSICALLY A PARALLEL CIRCUIT QUANTITY. G DERIVED FROM A SERIES CIRCUIT IS THE EQUIVALENT PARALLEL CIRCUIT RESISTANCE IN RECIPROCAL FORM.
- ② $x^{-1} = 1/x$, $x^{-2} = 1/x^2$
- ③ $\omega = 2\pi f = 6.283f =$ angular velocity
- ④ sin, eos, tan = abbr. for sine, cosine and tangent
- ⑤ $E_R =$ Voltage developed by a resistance
- ⑥ $|x| =$ Absolute value of x = Magnitude of x
- ⑦ θ may be θ_E , θ_I , θ_Y or θ_Z , B may be B_C or B_L , X may be X_C or X_L

Conductance, Series Circuits	G	Applicable Notes	Terms
$G = R/[R^2 + X_C^2]$		①	$X_C R$
$G = X_C/Z^2$		①	$X_C Z$
$G = (\sin \theta_Z)^2/X_C$		① ④ ⑦	$X_C \theta$
$G = R/[R^2 + X_L^2]$		①	$X_L R$
$G = X_L/Z^2$		①	$X_L Z$
$G = (\sin \theta)^2/X_L$		① ④ ⑦	$X_L \theta$
$G = R / \left(R^2 + [(\omega L) - (\omega C)^{-1}]^2 \right)$		① ② ③	CLR
$G = [(\omega L) - (\omega C)^{-1}] / Z^2 $		① ② ③ ⑥	CLZ
$G = (\sin \theta)^2 / [(\omega L) - (\omega C)^{-1}] $		① ② ③ ④ ⑥ ⑦	$CL \theta$
$G = R / [R^2 + (X_L - X_C)^2]$		①	$X_C X_L$ R
$G = (X_L - X_C) / Z^2 $		① ⑥	$X_C X_L$ Z
$G = (\sin \theta)^2 / (X_L - X_C) $		① ④ ⑥ ⑦	$X_C X_L$ θ

Conductance, Parallel Circuits	G	Applicable Notes	Terms
$G = G_1 + G_2 \dots + G_n$		⑧	G
$G = R_1^{-1} + R_2^{-1} \dots + R_n^{-1}$		② ⑧	R
$G = \sqrt{Y^2 - B^2}$		⑨	B Y
$G = \sqrt{Z^{-2} - B^2}$		② ⑨	B Z
$G = B/(\tan \theta) $		④ ⑥ ⑦	B θ
$G = \sqrt{Y^2 - (\omega C)^2}$		③ ⑨	C Y
$G = \sqrt{Z^{-2} - (\omega C)^2}$		② ③ ⑨	C Z
$G = (\omega C)/(\tan \theta) $		③ ④ ⑥ ⑦	C θ
$G = P/E^2$			E P
$G = \sqrt{Y^2 - (\omega L)^{-2}}$		② ③ ⑨	L Y
$G = \sqrt{Z^{-2} - (\omega L)^{-2}}$		② ③ ⑨	L Z
$G = [(\omega L) (\tan \theta)]^{-1} $		③ ④ ⑥ ⑦	L θ
$G = \sqrt{Y^2 - X^{-2}}$		② ⑦ ⑨	X Y
$G = \sqrt{Z^{-2} - X^{-2}}$		② ⑦ ⑨	X Z

Conductance, Parallel Circuits	G	Applicable Notes	Terms
$G = [X(\tan \theta)]^{-1} $		② ④ ⑦	X θ
$G = Y(\cos \theta)$		④ ⑦	Y θ
$G = (\cos \theta)/Z$		④ ⑦	Z θ
$G = \sqrt{Y^2 - (B_L - B_C)^2}$		⑨	B _C B _L Y
$G = \sqrt{Z^{-2} - (B_L - B_C)^2}$		② ⑨	B _C B _L Z
$G = (B_L - B_C)/(\tan \theta) $		④ ⑥ ⑦	B _C B _L θ
$G = \sqrt{Y^2 - [(\omega L)^{-1} - (\omega C)]^2}$		② ③ ⑨	C L Y
$G = \sqrt{Z^{-2} - [(\omega L)^{-1} - (\omega C)]^2}$		② ③ ⑨	C L Z
$G = [(\omega L)^{-1} - (\omega C)]/(\tan \theta) $		② ③ ④ ⑥ ⑦	C L θ
$G = \sqrt{Y^2 - (X_L^{-1} - X_C^{-1})^2}$		② ⑨	X _C X _L Y
$G = \sqrt{Z^{-2} - (X_L^{-1} - X_C^{-1})^2}$		② ⑨	X _C X _L Z
$G = (X_L^{-1} - X_C^{-1})/(\tan \theta) $		② ④ ⑥ ⑦	X _C X _L θ

G Notes:

- ⑧ In a purely parallel circuit, the values of parallel reactances are not relevant to the value of G.
- ⑨ A negative resultant under the radical sign indicates an error.

H

Henry Unit, Magnetic Field Strength

H = Symbol for henry.

H = Basic unit of inductance.

H = The inductance which develops one volt from current changing at the rate of one ampere per second.

$$H = \text{mH} \cdot 10^3$$

$$H = \mu\text{H} \cdot 10^6$$

H = Symbol for magnetic field strength.

H = Magnetomotive force per unit length.
Magnetizing force.
Magnetic intensity.

H = Gilberts per centimeter (CGS Oersteds).

H = Ampere turns per meter (SI A/m).

$H = F\ell$ where F = magnetomotive force
 ℓ = length of magnetic path

$H = B/\mu$ where B = magnetic flux density
 μ = permeability

H = B when magnetic path is air

H = B when permeability (μ) = 1

Ampere turns per inch = .495 Oersteds

Oersteds = 2.02 Ampere turns per inch

h

**Hybrid Parameter,
Height,
Hour**

h = Symbol for hybrid parameter.

See—Active Circuits

h = Symbol for height.

h = Symbol for hour.

h = Symbol for planck's constant.

Hz

Hertz

Hz = Symbol for hertz.

Hz = The basic unit of frequency equal to one cycle per second.

Hz = Unit often used with multiplier prefixes.

kHz = 10^3 Hertz (kilohertz)

MHz = 10^6 Hertz (megahertz)

GHz = 10^9 Hertz (gigahertz)

Hz = cps = c/s

Hz = 360° per second

Hz = 2π radians per second

Hz = Vectorial revolutions per second.

|

**Current
Definitions**

I = Symbol for electric current.

- I** = 1. The movement of electrons through a conductor.
2. The rate of flow of electric charge.

I = Current in amperes (A). (Coulombs per sec.)

I = $\pm I_{dc}$ or I_{ac} (effective)

$I_{eff} = I_{rms}$

$I_{ac} = |I| = I_{absolute\ value} = I_{magnitude}$

θ_I = Phase angle of alternating current.

I = Complete description of alternating current.

I = I_{POLAR} or $I_{RECTANGULAR}$ ($I_{POLAR} = I_{RECT}$)

$I_{POLAR} = I/\theta_I = \text{Vectorial current}$

$I_{RECT} = (\pm I_R \pm I_X j) = \text{Complex number current}$

where $\pm I_R$ = Current through a real or an equiv.
parallel circuit resistance and

where $\pm I_X$ = Current through a real or an equiva-
lent parallel circuit reactance.

$I_{RECT} = \text{Complex number form of current which expresses
the } 0^\circ \text{ or } 180^\circ \text{ and the } +90^\circ \text{ or } -90^\circ \text{ vectors which
have a resultant vector equal to } I_{POLAR}.$

$I_{RECT} = I_R - (\pm I_X)j$ in this handbook (one exception)
whereby $+I_X$ identifies I_X as inductive and $-I_X$
identifies I_X as capacitive.

$I_{RECT} = \text{Mathematical equivalent of resistive and reactive
currents in parallel regardless of actual circuit
configuration.}$

i = Instantaneous value of current.

(exception: $i_N = \text{rms noise current}$)

**Direct Current
Formulas**

$I = EG$ $I = P/E$ $I = E/R$ $I = \sqrt{P/R}$	General
$I = P_1/E_1 = P_2/E_2 = P_n/E_n$ $I = E_1/R_1 = E_2/R_2 = E_n/R_n$ $I = (E_1 + E_2 \dots + E_n)/(R_1 + R_2 \dots + R_n)$ $I = \sqrt{P_1/R_1} = \sqrt{P_2/R_2} = \sqrt{P_n/R_n}$ $I = \sqrt{(P_1 + P_2 \dots + P_n)/(R_1 + R_2 \dots + R_n)}$	Series Circuits
$I_t = I_1 + I_2 \dots + I_n$ $I_t = EG_t = E(G_1 + G_2 \dots + G_n)$ $I_t = P_t/E = (P_1 + P_2 \dots + P_n)/E$ $I_t = E(R_1^{-1} + R_2^{-1} \dots + R_n^{-1})$ $I_t = \sqrt{P_t G_t}$ $I_t = \sqrt{P_t(R_1^{-1} + R_2^{-1} \dots + R_n^{-1})}$	Parallel Circuits

I Notes:

① **General**

B = Susceptance, C = Capacitance, e = Instantaneous Voltage, E = Voltage (dc or rms), f = Frequency, G = Conductance, i = Instantaneous Current, I = Current (dc or rms), L = Inductance, P = Power, Q = Quantity of Electric Charge, Q = Quality or Q Factor, R = Resistance, t = Time, T = Time Constant, X = Reactance, Y = Admittance, Z = Impedance, ϵ = Base of Natural Logarithms, θ = Phase Angle, —Continued on page 67



Transient Currents, Current Ratios

$I = Q/t$ (I produced by charge Q for t sec.)	
$i = (E/R) (\epsilon^{\frac{-t}{RC}})$ (E = Applied voltage) $i = .36788 (E/R) @ t = RC$ (one time constant) $I = (e_C C)/t$ (constant current)	Capacitor Charge
$i = (E/R) (\epsilon^{\frac{-t}{RC}})$ (E = Initial voltage) $i = .36788 (E/R) @ t = RC$ (one time constant) $I = (E - e_C) (C/t)$ (constant current)	Capacitor Discharge
$i = (E/R) (1 - \epsilon^{\frac{-Rt}{L}})$ (E = Applied Voltage) $i = .6321 (E/R) @ t = L/R$ (one time constant)	Inductor Energization
$I_{p-p} = (2\sqrt{2}) I_{rms} = 2.828 I_{rms}$ $I_{peak} = (\sqrt{2}) I_{rms} = 1.414 I_{rms}$ $I_{av} = [(2\sqrt{2})/\pi] I_{rms} = .9003 I_{rms}$ $I_{av} = (2/\pi) I_{peak} = .6366 I_{rms}$ $I_{rms} = [\pi/(2\sqrt{2})] I_{av} = 1.111 I_{av}$ $I_{rms} = \text{effective current} = \text{dc equiv. current}$ $I_{rms} = (1/\sqrt{2}) I_{peak} = .707 I_{peak}$ $I_{rms} = [1/(2\sqrt{2})] I_{p-p} = .3535 I_{p-p}$	Current Ratios

I Notes:

① Continued

π = Circumference to Diameter Ratio, ω = Angular Velocity or Angular Frequency.

Series Circuit Current	I	Applicable Notes	Terms
$I = E_C \omega C$		① ② ③	$E_C C$
$I = E_L / (\omega L)$		① ② ③	$E_L L$
$I = E_R / R$		① ②	$E_R R$
$I = E_C / X_C$		① ②	$E_C X_C$
$I = E_L / X_L$		① ②	$E_L X_L$
$I = EY$		①	$E Y$
$I = E/Z$		①	$E Z$
$I = \sqrt{P/R}$		①	$P R$
$I = P/(E \cos \theta)$		① ⑤	$E P \theta$
$I = (E \cos \theta)/R$		① ⑤	$E R \theta$
$I = E / \sqrt{R^2 + [(\omega L) - (\omega C)^{-1}]^2}$		① ③	$E CL R$
$I = E / \sqrt{R^2 + (X_L - X_C)^2}$		① ②	$E X_C X_L R$
$I = \sqrt{P/(Z \cos \theta)}$		① ⑤	$P Z \theta$

I Notes:

② Subscripts

C = capacitive, E = voltage, g = generator, I = current, L = inductive, n = any number, o = output, p = parallel, R = resistive, s = series, t = total or equivalent, X = reactive, Y = admittance, Z = impedance

③ Constants

$j = \sqrt{-1}$, = 90° multiplier, = mathematical i, $\epsilon = 2.718$, $\epsilon^{-1} = .36788$, $\pi = 3.1416$, $2\pi = 6.2832$, $\omega = 2\pi f$

④ Algebra

$x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $x^{\frac{1}{2}} = \sqrt{x}$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $x^{(-y/z)} = 1/x^{(y/z)}$, $|x|$ = absolute value or magnitude of x

Current, Parallel Circuits	Applicable Notes	Terms
$I_t = E(B_{C1} + B_{C2} \dots + B_{Cn})$	① ②	E B _C
$I_t = E(B_{L1} + B_{L2} \dots + B_{Ln})$	① ②	E B _L
$I_t = E\omega(C_1 + C_2 \dots + C_n)$	① ② ③	E C
$I_t = E(G_1 + G_2 \dots + G_n)$	① ②	E G
$I_t = [E(L_1^{-1} + L_2^{-1} \dots + L_n^{-1})] / \omega$	① ② ③ ④	E L
$I_t = E(R_1^{-1} + R_2^{-1} \dots + R_n^{-1})$	① ② ④	E R
$I_t = E(X_{C1}^{-1} + X_{C2}^{-1} \dots + X_{Cn}^{-1})$	① ② ④	E X _C
$I_t = E(X_{L1}^{-1} + X_{L2}^{-1} \dots + X_{Ln}^{-1})$	① ② ④	E X _L
$I = EY$	①	E Y
$I = E/Z$	①	E Z
$I = E(B_L - B_C)$	① ②	E B _C B _L
$I = E(X_L^{-1} - X_C^{-1})$	① ② ④	E X _C X _L
$I = E\sqrt{G^2 + (B_L - B_C)^2}$	① ②	E B _C B _L G
$I = E\sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}$	① ② ④	E X _C X _L R

I Notes:

⑤ Trigonometry

sin = sine, cos = cosine, tan = tangent, tan⁻¹ = arc tangent

⑥ Reminders

±θ --- use the sign of the phase angle

±X, ±B, ±I_X --- identifies X, B and I_X as capacitive or inductive

-X, -B, -I_X are capacitive

+X, +B, +I_X are inductive

⊗ Division by zero is prohibited

1. It should be understood that the phase angle of voltage, current, impedance and admittance is the same, one and only, phase angle in a given circuit. The fact that the sign of the voltage or impedance phase angle differs from the sign of the current or admittance phase angle means only that if the current leads the voltage, the voltage must lag the current by the same angle.
2. $\pm\theta_I = -(\pm\theta_E) = -(\pm\theta_Z) = \pm\theta_Y$
3. When using the phase angle of impedance (or admittance), a phase angle always exists when the circuit is reactive. The phase angle of voltage and current however can only exist for one of the two at the same time. When the voltage phase angle exists, the current phase angle must be 0° and when the current phase angle exists, the voltage phase angle must be 0° . This is explained by the fact the voltage uses the current as a reference and the current uses the voltage as a reference.
4. The same situation exists with voltage and current in rectangular form. When "imaginary" current exists, the voltage must be $E/0^\circ$ or $E + j0$ and when "imaginary" voltage exists, the current must be $I/0^\circ$ or $I + j0$.
5. For practical problems, the best method of minimizing confusion and errors is to use the phase angle of the generator as the 0° reference. If the generator is a current source, the phase angle of the total current is always 0° and if the generator is a voltage source, the phase angle of the total voltage is always 0° .

Note: The rectangular current of a series circuit driven by a voltage source represents the currents through an equivalent parallel circuit. The rectangular voltage of a parallel circuit driven by a current source represents the voltages across elements of the equivalent series circuit.

I = The magnitude and phase angle of the current developed by a voltage applied to a circuit. ($\theta_{E_g} = 0^\circ$)
See also— θ

$$I_{POLAR} = I / \pm \theta_I = I / -(\pm \theta_Z)$$

I_{RECT} = 1. The 0° and $\pm 90^\circ$ currents which produce a resultant equal to **I_{POLAR}**.

2. The current through resistance and net reactance in parallel.

3. The current through the parallel equivalent resistance and net reactance of a series circuit.

(*Note:* Only one current is possible in a series circuit.)

$$I_{RECT} = I_R - (\pm I_X) j$$

$$I_{RECT} = [I \cos \theta_I] - [-I \sin(\pm \theta_I)] j$$

$$I_{RECT} = [I \cos \theta_Z] - [I \sin(\pm \theta_Z)] j$$

Note: The above rectangular form is strongly recommended for most uses. The negative sign will always identify the complex quantity as current or admittance and as a parallel equivalent quantity. The use of θ_Z eliminates the double change of signs often needed and maintains the identity of the reactive quantity at all times.

Note: The rectangular form of current has been used by some as a substitute for rectangular admittance (**Y_{RECT}**) for solving series circuits in parallel. It should be noted that if the assumed voltage is one, **I_{RECT}** and **Y_{RECT}** are identical in meaning and method except for the names of the quantities. When $E = 1/0^\circ$, **I_{POLAR}** = **Y_{POLAR}**, **I_{RECT}** = **Y_{RECT}**, $I_R = G$, $I_C = B_C$, $I_L = B_L$, $-I_X = -B$, $+I_X = +B$ and $\pm I_X = \pm B$.

Note: Use formulas on following page to obtain **I_{POLAR}** then convert to **I_{RECT}** using above formulas.

**I_{POLAR} and I_{RECT}
Series Circuits**

**Current & Phase,
Series Circuits**

All Series Circuit I Formulas

$I_{POLAR} = I / \pm \theta_I$ $I_{POLAR} = I / -(\pm \theta_Z)$ $I_{RECT} = [I \cos \theta_Z] - [I \sin(\pm \theta_Z)] j$ $I_R = I \cos \theta_Z$ $I_C = I \sin(-\theta_Z) \quad (I_C = -I_X)$ $I_L = I \sin(+\theta_Z) \quad (I_L = +I_X)$ $\pm I_X = I \sin(\pm \theta_Z)$ $I_{RECT} = I_R - (\pm I_X) j$	Parallel Equivalent Current or Equiv. parallel circuit current	Applicable Notes	Terms
		$I = P / (E \cos \theta_Z)$	① ② ⑤
$I = (E \cos \theta_Z) / R$	① ② ⑤	$E R \theta_Z$	
$I = E / Z$	①	$E Z \theta_Z$	
$I = E / \sqrt{R^2 + [(\omega L) - (\omega C)^{-1}]^2}$ $\pm \theta_Z = \tan^{-1} [(\omega L) - (\omega C)^{-1}] / R$	① ② ③ ④ ⑤ ⑥	$E C L R$	
$I = E / \sqrt{R^2 + (X_L - X_C)^2}$ $\pm \theta_Z = \tan^{-1} [(X_L - X_C) / R]$	① ② ⑤ ⑥	$E X_C X_L R$	
$I = (E \sin \theta_Z) / (X_L - X_C) $	① ② ④ ③ ⊗	$E X_C X_L \theta$	

**Current & Phase,
Parallel Circuits**

**Resistive & Reactive
Currents
In Parallel**

I = The magnitude and phase angle of the current developed by the application of voltage to a parallel circuit. ($\theta_E = 0^\circ$)

$$I_{\text{POLAR}} = I/\theta_I = I/\theta_Y = I/-(\pm\theta_Z)$$

$I_{\text{RECT}} = 1$. The 0° and $\pm 90^\circ$ currents which have a resultant equal to I_{POLAR} .

2. The resistive current and the reactive current in parallel.

$$I_{\text{RECT}} = I_R - (\pm I_X)j = [I \cos \theta_Z] - [I \sin(\pm\theta_Z)]j$$

$$I_{\text{RECT}} = [I \cos \theta_I] + [I \sin(\pm\theta_I)]j$$

$$I_{\text{RECT}} = [I \cos \theta_Y] + [I \sin(\pm\theta_Y)]j$$

	Applicable Notes	Terms
$I = (EG)/(\cos \theta_Y)$	① ② ⑤	$E G \theta_Y$
$I = P/(E \cos \theta_Z)$	① ② ⑤	$E P \theta_Z$
$I = E/(R \cos \theta_Z)$	① ② ⑤	$E R \theta_Z$
$I = EY$	①	$E Y \theta_Y$
$I = E/Z$	①	$E Z \theta_Z$
$I = \sqrt{I_R^2 + (I_L - I_C)^2}$ $\pm\theta_I = \tan^{-1} [-(I_L - I_C)/I_R]$	① ② ⑤ ⑥	$I_R I_C I_L$
$I = \sqrt{P/(Z \cos \theta_Z)}$	① ② ⑤	$P Z \theta_Z$

Current & Phase, Parallel Circuits	Applicable Notes	Terms
$I = E \sqrt{G^2 + (B_L - B_C)^2}$ $\pm\theta_I = \tan^{-1} [-(B_L - B_C)/G]$	① ② ⑤ ⑥	G B _L B _C
$I = [E(B_L - B_C)] / (\sin \theta_Y) $ $\pm\theta_I = \pm\theta_Y$	① ② ⑤ ⑥ ⊗	θ _Y B _L B _C
$I = E \sqrt{R^{-2} + [(\omega L)^{-1} - (\omega C)]^2}$ $\pm\theta_I = \tan^{-1} (-R [(\omega L)^{-1} - (\omega C)])$	① ② ③ ④ ⑤ ⑥	R L C
$I = (E [(\omega L)^{-1} - (\omega C)]) / (\sin \theta_Z)$ $\pm\theta_I = -(\pm\theta_Z)$	① ② ③ ④ ⑤ ⑥ ⊗	θ _Z L C
$I = E \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}$ $\pm\theta_I = \tan^{-1} [-R(X_L^{-1} - X_C^{-1})]$	① ② ④ ⑤ ⑥	R X _L X _C
$I = [E(X_L^{-1} - X_C^{-1})] / [\sin \theta_Z]$ $\pm\theta_I = -(\pm\theta_Z)$	① ② ④ ⑤ ⑥ ⊗	θ _Z X _L X _C

**Parallel Complex
Currents,
Procedure Method**

Terms — $I_1/\pm\theta_1, I_2/\pm\theta_2, \dots I_n/\pm\theta_n$

Procedure for those who are uncomfortable when working with rectangular form currents. Maintains positive identity of reactive currents.

Procedure:

1. Convert each $I/\pm\theta_I$ to its equivalent parallel resistive current from:

$$I_{R_p} = I \cos \theta_I$$

2. $(I_{R_p})_t = (I_{R_p})_1 + (I_{R_p})_2 \dots + (I_{R_p})_n$

3. Convert each $I/\pm\theta_I$ with a negative angle to its equivalent parallel inductive current from:

$$I_{L_p} = I \sin |-\theta_I|$$

4. $(I_{L_p})_t = (I_{L_p})_1 + (I_{L_p})_2 \dots + (I_{L_p})_n$

5. Convert each $I/\pm\theta_I$ with a positive angle to its equivalent parallel capacitive current from:

$$I_{C_p} = I \sin(+\theta_I)$$

6. $(I_{C_p})_t = (I_{C_p})_1 + (I_{C_p})_2 \dots + (I_{C_p})_n$

7. Convert totals back to a single polar form current from:

$$I_t = \sqrt{(I_{R_p})_t^2 + [(I_{L_p})_t - (I_{C_p})_t]^2}$$
$$\pm\theta_{I_t} = \tan^{-1} \left(- [(I_{L_p})_t - (I_{C_p})_t] / [(I_{R_p})_t] \right)$$


Formula Method	Complex Currents, Sum & Differential
$I_t = \left\{ (I_1 \cos \theta_1) + (I_2 \cos \theta_2) \dots + (I_n \cos \theta_n) \right\}^2$ $+ \left\{ (I_1 \sin(\pm\theta_1)) + [I_2 \sin(\pm\theta_2)] \dots + [I_n \sin(\pm\theta_n)] \right\}^2 \left. \right\}^{1/2}$ $\theta_{I_t} = \tan^{-1} \frac{[I \sin(\pm\theta)]_t}{[I \cos \theta]_t}$ <p>Sum of I_1/θ_1, $I_2/\theta_2 \dots$ and I_n/θ_n</p>	$I_{I_t} = \sqrt{[(I_1 \cos \theta_1) - (I_2 \cos \theta_2)]^2 + ([I_1 \sin(\pm\theta_1)] - [I_2 \sin(\pm\theta_2)])^2}$ $\theta_{I_t} = \tan^{-1} \frac{([I_1 \sin(\pm\theta_1)] - [I_2 \sin(\pm\theta_2)])}{([I_1 \cos \theta_1] - (I_2 \cos \theta_2))}$ <p>Differential of I_1/θ_1 and I_2/θ_2</p>

Current and Phase, Complex Circuits	Vector Algebra and/or Rectangular Form Method	Terms
$I_{\text{POLAR}} = (E_{\text{POLAR}})/(Z_{\text{POLAR}})$ $I/\theta_I = (E/\theta_E)/(Z/\theta_Z)$ $I = E_g/Z, \quad \theta_I = 0^\circ - \theta_Z$		E_{POLAR} Z_{POLAR}
$I_{\text{POLAR}} = (E_{\text{POLAR}}) \cdot (Y_{\text{POLAR}})$ $I/\theta_I = (E/\theta_E) \cdot (Y/\theta_Y)$ $I = E_g Y, \quad \theta_I = 0^\circ + \theta_Y$		E_{POLAR} Y_{POLAR}
$(I_{\text{RECT}})_t = (I_{\text{RECT}})_1 + (I_{\text{RECT}})_2$ $(I_{\text{RECT}})_t = [I_R + (\pm I_{90^\circ})j]_1 + [I_R + (\pm I_{90^\circ})j]_2$ $(I_{\text{RECT}})_t = (I_{R1} + I_{R2}) + [(\pm I_{90^\circ})_1 + (\pm I_{90^\circ})_2]j$		$(I_{\text{RECT}})_1$ $(I_{\text{RECT}})_2$
$(I_{\text{RECT}})_t = [(I_{\text{POLAR}})_1]_{\text{RECT}} + [(I_{\text{POLAR}})_2]_{\text{RECT}}$ $(I_{\text{RECT}})_t = [I_1/\theta_1]_{\text{RECT}} + [I_2/\theta_2]_{\text{RECT}}$ $(I_{\text{RECT}})_t = [(I_1 \cos \theta_1) + (I_2 \cos \theta_2)]$ $+ [(I_1 \sin \pm \theta_1) + (I_2 \sin \pm \theta_2)]j$ $(I_{\text{RECT}})_t = (I_R)_t + [(\pm I_{90^\circ})_t]j$ $I_t = \sqrt{(I_R)_t^2 + (\pm I_{90^\circ})_t^2}$ $(\pm \theta_I)_t = \tan^{-1} [(\pm I_{90^\circ})_t / (I_R)_t]$		$(I_{\text{POLAR}})_1$ $(I_{\text{POLAR}})_2$


I_o

Output Current & Phase

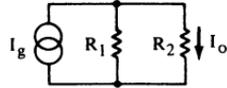
$$I_o = I_g / [(R_2/R_1) + 1]$$
$$\theta_{I_o} = \theta_Z = 0^\circ$$



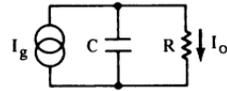
$$I_o = I_g / [R \sqrt{R^{-2} + X_C^{-2}}]$$
$$\theta_{I_o} = \theta_Z = \tan^{-1}(R/-X_C)$$


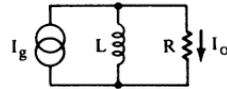
$$I_o = I_g / [R \sqrt{R^{-2} + X_L^{-2}}]$$
$$\theta_{I_o} = \theta_Z = \tan^{-1}(R/+X_L)$$


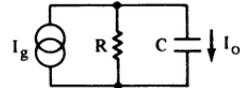
$$I_o = I_g / [X_C \sqrt{R^{-2} + X_C^{-2}}]$$
$$\theta_{I_o} = \theta_Z + 90^\circ$$
$$\theta_{I_o} = [\tan^{-1}(R/-X_C)] + 90^\circ$$



$$I_o = I_g / [X_L \sqrt{R^{-2} + X_L^{-2}}]$$
$$\theta_{I_o} = \theta_Z - 90^\circ$$
$$\theta_{I_o} = [\tan^{-1}(R/+X_L)] - 90^\circ$$




Note: $\text{---}\infty\text{---}$ = Infinite impedance current source


I_o

Output Current & Phase

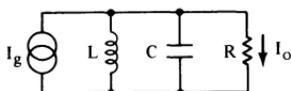
$$I_o = (I_g Z)/R$$
$$\theta_{I_o} = \theta_Z$$
$$I_o = I_g / [R \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}]$$
$$\theta_{I_o} = \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$$



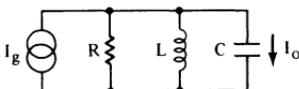
$$I_o = (I_g Z)/X_C$$
$$\theta_{I_o} = \theta_Z - (-90^\circ) = \theta_Z + 90^\circ$$
$$I_o = I_g / [X_C \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}]$$
$$\theta_{I_o} = 90^\circ + \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$$


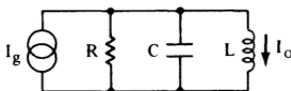
$$I_o = (I_g Z)/X_L$$
$$\theta_{I_o} = \theta_Z - (+90^\circ) = \theta_Z - 90^\circ$$
$$I_o = I_g / [X_L \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}]$$
$$\theta_{I_o} = -90^\circ + \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$$



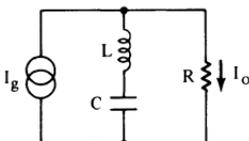
$$I_o = (I_g Z)/R$$
$$\theta_{I_o} = \theta_Z$$
$$I_o = I_g / [R \sqrt{R^{-2} + (X_L - X_C)^{-2}}]$$
$$\theta_{I_o} = \tan^{-1} [R/(X_L - X_C)]$$



I_o


Output Current & Phase
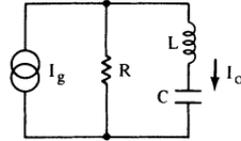
$$I_o = (I_g Z) / (X_L - X_C)$$
$$\theta_{I_o} = \theta_Z - (\pm 90^\circ)$$




$$I_o = I_g / [(X_L - X_C) \sqrt{R^2 + (X_L - X_C)^{-2}}]$$
$$\theta_{I_o} = (\tan^{-1} [R / (X_L - X_C)]) - (\pm 90^\circ)$$

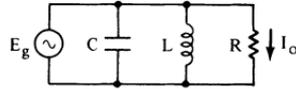
$$I_o = E_g / R$$
$$\theta_{I_o} = 0^\circ$$



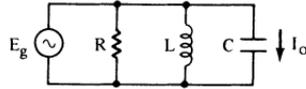
$$I_o = E_g / X_C$$
$$\theta_{I_o} = -(-90^\circ) = +90^\circ$$




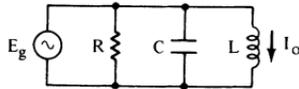
$$I_o = E_g / X_L$$
$$\theta_{I_o} = -(+90^\circ) = -90^\circ$$


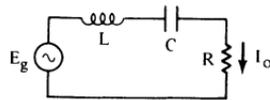
$$I_o = E_g / Z$$
$$\theta_{I_o} = -(\pm \theta_Z)$$


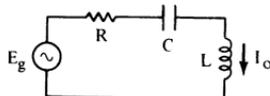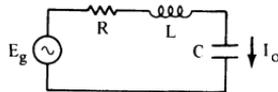
$$I_o = E_g / \sqrt{R^2 + (X_L - X_C)^2}$$
$$\theta_{I_o} = \tan^{-1} [-(X_L - X_C) / R]$$



Vector Algebra AC Ohms Law

$$\begin{aligned} E_g &= E_g / 0^\circ \text{ or } I_g = I_g / 0^\circ \\ I &= E_g / Z = E_g / Z / 0^\circ - \theta_Z = -(\pm \theta_Z) \\ E &= I_g Z = I_g Z / 0^\circ + \theta_Z = \pm \theta_Z \\ Z &= E_g / I = E_g / I / 0^\circ - \theta_I = -(\pm \theta_I) \\ Z &= E / I_g = E / I_g / \theta_E - 0^\circ = \pm \theta_E \end{aligned}$$



Addition and Subtraction of Rect. Quantities
(See also — Z_{RECT} , Addition and Subtraction)

$$\begin{aligned} I_1 + I_2 &= I_{1(RECT)} + I_{2(RECT)} \\ &= [I_R - (\pm I_X)j]_1 + [I_R - (\pm I_X)j]_2 \\ &= [(I_R)_1 + (I_R)_2] - [(\pm I_X)_1 + (\pm I_X)_2]j \\ I_1 - I_2 &= [(I_R)_1 - (I_R)_2] - [(\pm I_X)_1 - (\pm I_X)_2]j \\ & \quad | +I_X | = I_L \quad | -I_X | = I_C \end{aligned}$$

$$\begin{aligned} E_1 + E_2 &= E_{1(RECT)} + E_{2(RECT)} \\ &= [E_R + (\pm E_X)j]_1 + [E_R + (\pm E_X)j]_2 \\ &= [(E_R)_1 + (E_R)_2] + [(\pm E_X)_1 + (\pm E_X)_2]j \\ E_1 - E_2 &= [(E_R)_1 - (E_R)_2] + [(\pm E_X)_1 - (\pm E_X)_2]j \\ & \quad | +E_X | = E_L \quad | -E_X | = E_C \end{aligned}$$

Note: The rectangular current of a series circuit represents current through an equivalent parallel circuit. The rectangular voltage of a parallel circuit represents voltage across elements of an equivalent series circuit.

Output Current Vector Algebra	Applicable Notes
\mathbf{I}_o	
$\mathbf{E}_g = \mathbf{E}_g / 0^\circ$ $\mathbf{Z}_i = \mathbf{Z}$ $\mathbf{I}_o = \mathbf{E}_g / \mathbf{Z}$	I _{VA} Notes ① ② ③
$\mathbf{I}_g = \mathbf{I}_g / 0^\circ$ $\mathbf{Z}_i = [\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1}]^{-1}$ $\mathbf{E}_g = \mathbf{I}_g \mathbf{Z}_i$ $\mathbf{I}_o = [\mathbf{I}_g \mathbf{Z}_i] / \mathbf{Z}_1$	I _{VA} Notes ① ② ③
$\mathbf{E}_g = \mathbf{E} / 0^\circ$ $\mathbf{Z}_i = \mathbf{Z}_3 + [\mathbf{Z}_2^{-1} + \mathbf{Z}_1^{-1}]^{-1}$ $\mathbf{I}_g = \mathbf{E}_g / \mathbf{Z}_i$ $\mathbf{I}_o = \mathbf{E}_g / (\mathbf{Z}_i [(\mathbf{Z}_1 / \mathbf{Z}_2) + 1])$	I _{VA} Notes ① ② ③
I _{VA} Notes: ① \mathbf{E}_g = Generator voltage \mathbf{E}_o = Output voltage \mathbf{I}_g = Generator current \mathbf{I}_o = Output current \mathbf{Z}_i = Input impedance \mathbf{Z}_o = Output impedance	
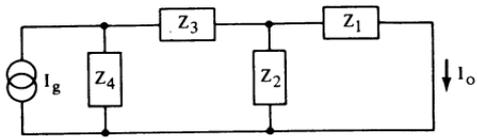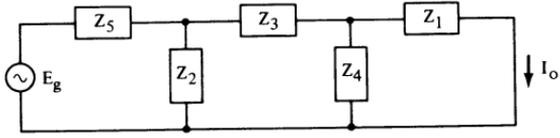
<p>Output Current Vector Algebra</p>	<p>Applicable Notes</p>
<div style="text-align: center;">  </div> <p> $I_g = I_g / 0^\circ \quad E_g = I_g Z_i$ $Z_i = (Z_4^{-1} + [Z_3 + (Z_2^{-1} + Z_1^{-1})^{-1}]^{-1})^{-1}$ $I_o = I_g [1 - (Z_i / Z_4)] / [(Z_1 / Z_2) + 1]$ </p>	<p>IV_A Notes</p> <p>① ② ③</p>
<div style="text-align: center;">  </div> <p> $E_g = E_g / 0^\circ \quad I_g = E_g / Z_i$ $Z_i = Z_5 + (Z_4^{-1} + [Z_3 + (Z_2^{-1} + Z_1^{-1})^{-1}]^{-1})^{-1}$ $I_o = I_g (1 - [(Z_i - Z_5) / Z_4]) / [(Z_1 / Z_2) + 1]$ </p>	<p>IV_A Notes</p> <p>① ② ③</p>

IV_A Notes:

- ② Z, Z_1, Z_2, Z_3, Z_4 and Z_5 may represent resistances, capacitances, inductances, series circuits, parallel circuits, unknown circuits or any combination.
- ③ All mathematical operations involving addition or subtraction must be performed in rectangular form. It is recommended that all mathematical operations involving multiplication or division be performed in polar form.

See also – Z , Vector Algebra See – Z to Z^{-1} Conversion

$i_{N(th)}$

Thermal Noise Current

$i_{N(th)}$ = Symbol for thermal noise current. (other symbols for thermal noise current are I_N , I_{TH} , $I_{N(TH)}$, i_N , i_{th} etc)

$i_{N(th)}$ = Thermal noise (white noise) current of resistance. (thermal noise current is always rms current regardless of symbol)

$$i_{N(th)} = \sqrt{(4kT_K \overline{BW})/R}$$

k = Boltzmann constant ($1.38 \cdot 10^{-23} \text{ J/}^\circ\text{K}$)

T_K = Temperature in Kelvin ($^\circ\text{C} + 273.15$)

R = Resistance generating thermal noise.

BW = Noise bandwidth in hertz. (Bandwidth with zero noise contribution from frequencies outside of bandwidth. See—Active Circuits, Opamp, BW_{NOISE} for correction factors for noise measurement with standard filters.)

$i_{N(\sqrt{Hz})}$ = Symbol for noise current per root hertz. [formerly called root cycle ($\sqrt{\sim}$)]

$$i_{N(th)(\sqrt{Hz})} \approx 1.287 \cdot 10^{-10} \sqrt{1/R} \text{ @ room temperature } (BW_{NOISE} = 1 \text{ Hz})$$

Note: Above formulas do not include the excess noise current of resistors (that noise developed by dc voltage applied to resistors). Excess noise is $1/f$ noise and may be of significance at frequencies below 1 KHz.

j J

Imaginary Number, Joules

$j = \text{Symbol for } \sqrt{-1}$

$j = \text{The imaginary unit of electrical complex numbers. The basic imaginary component of electrical rectangular form quantities. A unit identical to the mathematical imaginary unit } i. \text{ A } 90^\circ \text{ indicator. A } 90^\circ \text{ multiplier. A mathematical quantity which rotates a number from the } x \text{ axis (real numbers) to the } y \text{ axis (imaginary numbers).}$

$j = \text{The imaginary unit used in all electronic calculations (instead of the mathematical unit } i) \text{ to avoid confusion with the symbol for electrical current } I \text{ or } i.$

$$j = \sqrt{-1} = 1 \angle +90^\circ$$

$$-j = -\sqrt{-1} = 1 \angle -90^\circ$$

$$j^2 = -1 = 1 \angle \pm 180^\circ \quad \text{or} \quad 1 \angle +180^\circ$$

$$-j^2 = +1 = 1 \angle 0^\circ$$

$$j^3 = -j = 1 \angle -90^\circ \quad \text{or} \quad 1 \angle +270^\circ$$

$$j^4 = +1 = 1 \angle 0^\circ \quad \text{or} \quad 1 \angle +360^\circ$$

$J = \text{Symbol for joules}$

$J = \text{A unit of work or work equivalent energy.}$

$J = \text{A unit of work equivalent to } 1 \text{ watt} \cdot \text{second.}$

$J = \text{A unit of work equal to } .7376 \text{ foot} \cdot \text{pounds.}$

$J = \text{A unit of work equal to } .102 \text{ kg} \cdot \text{meters or } 10^7 \text{ ergs (dyne} \cdot \text{centimeters).}$

$J = \text{A unit of work equivalent to } 9.478 \cdot 10^{-4} \text{ Btu.}$

k


Coupling Coefficient

k = Symbol for coupling coefficient
(Capital K is sometimes used)

k = The ratio of mutual inductance to the square root of the product of the primary and the secondary inductances. The equivalent coupling coefficient provided by a discrete coupling element between two otherwise independent circuits.

$$k = M/\sqrt{L_1 L_2}$$


$$k = \omega_0^2 M \sqrt{C_1 C_2}$$

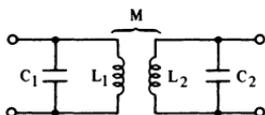

$$k = L_M [(L_M + L_1)(L_M + L_2)]^{-\frac{1}{2}}$$

$$k = \omega_0^2 L_M \sqrt{C_1 C_2}$$


$$k \approx L_M / \sqrt{L_1 L_2}$$

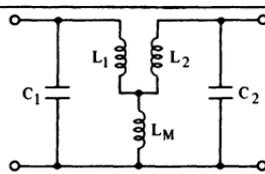

$$k = - \left((C_1 C_2) / [(C_M + C_1)(C_M + C_2)] \right)^{\frac{1}{2}}$$


$$k = - [(X_{C1} X_{CM}^{-1}) + 1]^{-1} \text{ when } C_1 = C_2$$

$$k \approx -\sqrt{C_1 C_2} / C_M$$

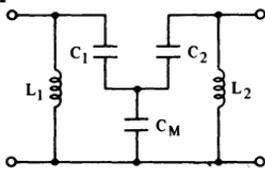

$$k = - [(C_1 / C_M) + 1]^{-1} \text{ when } C_1 = C_2$$
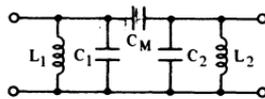
$$k = -C_M / \sqrt{(C_M + C_1)(C_M + C_2)}$$



Note: Circuits exhibit double peaks above critical coupling.

k K

**Kilo,
Dielectric
Constant,
Kelvin**

k = Symbol for kilo

(capital K is also used as a symbol for kilo)

k = A prefix symbol meaning 1000. A multiplier prefix used to indicate 10^3 units. Typical electronic uses include kilovolt (kV), kilowatt (kW), kilohertz (kHz) and kilohm ($k\Omega$). The symbol for kilohms ($k\Omega$) is often further abbreviated to k. In this form, it is most often capitalized. (K)

k = Symbol for dielectric constant (also K)

k = The capacitance multiplying effect of a specific material used as insulation between capacitor "plates" as compared to air. The ratio of capacitance of a given capacitor using a specific dielectric, to the capacitance of the capacitor using air as the dielectric.

k \neq A true constant since k varies somewhat with frequency, temperature, etc.

Typical dielectric constants

Air = 1	Mica = 2.5 - 9.3
Paper = 2 - 3.5	PVC = 2.9
Ceramics = 10 - 10 k+	Polystyrene = 2.6
Fiber = 5.0	Waxes = 2.3 - 3.7

k = Boltzmann constant = $1.3805 \cdot 10^{-23} \text{ J/K}^\circ$

(capital K is also used as a symbol for this constant)

K = Symbol for Kelvin (Kelvin temperature scale)

K = $^\circ\text{C}$ above absolute zero

K = $^\circ\text{C} + 273.15$



Inductance Definitions

L = Symbol for inductance. (self inductance)

L = In an inductor, in a coil, in a transformer, in a conductor or in any circuit where a varying electric current is flowing; that property which induces voltage in the same circuit from the varying magnetic field at a polarity which opposes the change of electric current.

Note that RC circuits and active circuit “inductances” which produce a lagging current do not meet the above definition and therefore cannot always perform in the same manner.

L = Inductance in henry (H) units.

Note that the basic unit is of convenient size for audio frequencies, but that millihenries (mH) and microhenries (μH) are more convenient at higher frequencies.

L = The symbol for an inductor on parts lists and schematics.

L = The symbol for inductive when used as a subscript.

L = One henry when a current change of one ampere per second develops one volt.

L_M = Mutual Inductance

(The symbol for mutual inductance is also M)

L_s = Series Circuit Inductance

L_p = Parallel Circuit Inductance

ℓ = Symbol for length

lf = Abbreviation for low frequency

Inductance, Series Circuits	L	Applicable Notes	Terms
$L_t = L_1 + L_2 \dots + L_n$ $L_2 = L_t - L_1$		①	L
$L_t = [(X_L)_1 + (X_L)_2 \dots + (X_L)_n] / \omega$ $L_t = [(+X_1) + (+X_2) \dots + (+X_n)] / \omega$		①	X_L +X
$L = R / (\omega D)$ Series reactive element must be inductive		①	D R
$L = (QR) / \omega$ Series reactive element must be inductive		①	Q R
$L = (R \tan \theta_Z) / \omega$ θ_Z must be a positive angle		①	R θ_Z
$L = (Z \sin \theta_Z) / \omega$ θ_Z must be a positive angle		①	Z θ_Z
Series to Parallel Conversion			
$L_p = [R_s^2 / (\omega^2 L_s)] + (R_s / \omega)$		①	L_s R_s
$L_p = [\omega(Z^{-1} \sin \theta_Z)]^{-1}$ (θ_Z must be positive)		②	Z θ_Z

L Notes:

- ① B_L = Inductive susceptance, +B = Inductive susceptance, C = Capacitance, D = Dissipation Factor, E = rms Voltage, e = Instantaneous voltage, I = Current, L_M = Mutual inductance, L_p = Parallel circuit inductance, L_s = Series circuit inductance, l = Length, M = Mutual Inductance, N = Number of turns, n (subscript) = Any number, Q = Quality, Merit or Storage Factor, R = Resistance, r = Radius, T = Time constant, W = Work, X_L = Inductive reactance, +X = Inductive reactance, Y = Admittance, Z = Impedance, θ = Phase angle, ω = Angular velocity = $2\pi f$, di/dt = Current rate of change.
- ② $x^{-1} = 1/x$, $|x|$ = Absolute value or magnitude of x

Inductance, Parallel Circuits	L	Applicable Notes	Terms
$L_t = [\omega(B_{L1} + B_{L2} \dots + B_{Ln})]^{-1}$		①	B_L
$L_t = \omega^{-1} [(+B_1) + (+B_2) \dots + (+B_n)]^{-1}$		②	+B
$L_t = [L_1^{-1} + L_2^{-1} \dots + L_n^{-1}]^{-1}$		① ②	L
$L_t = \omega^{-1} [(X_L^{-1})_1 + (X_L^{-1})_2 \dots + (X_L^{-1})_n]^{-1}$		①	X_L
$L_t = \omega^{-1} [(+X_1^{-1}) + (+X_2^{-1}) \dots + (+X_n^{-1})]^{-1}$		②	+X
$L = (DR)/\omega$ Parallel reactive element must be inductive		①	D R_p
$L = [\omega G(\tan \theta_Y)]^{-1} $ θ_Y must be a negative angle		① ②	G θ_Y
$L = R/(\omega Q)$ Parallel reactive element must be inductive		①	Q R
$L = R/(\omega \tan \theta_Z)$ θ_Z must be a positive angle		①	R θ_Z
$L = [\omega Y \sin \theta_Y]^{-1}$ θ_Y must be a negative angle		① ②	Y θ_Y
$L = Z/(\omega \sin \theta_Z)$ θ_Z must be a positive angle		①	Z θ_Z
$L = E/(\omega I \sin \theta_I)$ θ_I must be a negative angle		① ②	E I θ_I
Parallel to Series Conversion			
$L_s = [(\omega^2 L_p/R^2) + L_p^{-1}]^{-1}$		①	L_p R_p
$L_s = (Z \sin \theta_Z)/\omega$ (θ_Z must be positive)		②	Z θ_Z

Inductance, Misc. Formulas	L	Applicable Notes	Terms
$L = 1/(\omega B_L)$		①	B_L
$L_T = 1/(\omega^2 C)$ $L_T = X_C/\omega$	L required for resonance	①	C X_C
$L = X_L/\omega$		①	X_L
$L = (2W)/I^2$	(W = Work equivalent stored energy)	①	I W
$L = R/T$	(T = time constant)	①	R T
$L = -e/(di/dt)$ e = instantaneous voltage di/dt = rate of change in ampere/seconds		①	e $\frac{di}{dt}$
$L \approx (rN)^2/(9r + 10\ell)$ when magnetic path is air r = radius to center of winding N = number of turns ℓ = length of winding		①	ℓ N r
Coupled Series Inductances			
$L_t = L_1 + L_2 + 2M$ (fields aiding)		①	L_1 L_2 M
$L_t = L_1 + L_2 - 2M$ (fields opposing)			
Coupled Parallel Inductances			
$L_t = [(L_1 - M)^{-1} + (L_2 - M)^{-1}]^{-1}$ (fields opposing)		①	L_1 L_2 M

M

Mega, Mutual Inductance

M = Symbol for mega (also meg).

M = A prefix meaning one million. A multiplier prefix used to indicate 10^6 units.

Typical uses in electronics include megahertz (MHz), megawatt (MW), megavolt (MV) and megohm (M Ω).

Note: Megohm is often contracted to Meg and M Ω is often contracted to M.

M = Symbol for mutual inductance
(The symbol L_M is also used)

M = The equivalent inductance common to both the primary and secondary windings of a transformer. In a circuit with two discrete inductors coupled by magnetic field interaction, the equivalent inductance common to both inductors.

$$M = k\sqrt{L_p L_s}$$

$$M = kN_p N_s$$

$$M = (L_{ta} - L_{to})/4$$

M Notes:

k = Coefficient of coupling.

L_p = Primary inductance.

L_s = Secondary inductance.

L_{ta} = Total inductance with primary and secondary windings connected series aiding.

L_{to} = Total inductance with primary and secondary windings connected series opposing.

N_p = Number of primary turns.

N_s = Number of secondary turns.

m

Flare Constant, Exponential Horns

m = Symbol for flare constant (flaring constant)

m = In acoustical horns, a constant used in formulas to determine the area, diameter or radius at any distance from the throat, e.g., $A = A_o \epsilon^{mx}$ or $S = S_o \epsilon^{mx}$. In an exponential horn of infinite length, a constant used in formulas to determine the frequency (flare cutoff frequency f_{FC}) below which no energy is coupled through the horn.

m = Flare constant expressed in units of inverse inches, inverse feet, inverse meters, etc.

$$m = .6931/\ell_{2A}$$

$$m = .6931/\sqrt{\ell_{2d}}$$

$$m = \sqrt{.4804/\ell_{2d}}$$

$$m = \sqrt{.4804/\ell_{2r}}$$

$$m = (2.3025/\ell_{T-M}) [\log(A_M/A_o)]$$

$$m = (4.605/\ell_{T-M}) [\log(d_M/d_o)]$$

$$m = (4\pi)/\lambda_{FC}$$

$$m = (4\pi f_{FC})/v$$

A, A_M , A_o , A_x are in square units. d, ℓ , r, v and x are in same units. m is in inverse of same units (units⁻¹)

m Notes:

ℓ_{2A} , ℓ_{2d} , ℓ_{2r} = Length between centerline points of double area, diameter and radius respectively. ℓ_{T-M} = Throat to mouth length. A, A_M , A_o , A_x = Area, Area of mouth, throat and at distance x from throat respectively. d_o and d_M = Throat and mouth diameter. f_{FC} and λ_{FC} = Flare cutoff frequency and wavelength. ϵ = Base of natural logarithms = 2.718. v = Velocity of sound \approx 13630 in/sec, 1136 ft/sec or 346.3 meters/sec @ 25°C

n N

Nano,
Number,
Newton, Neper

n = Symbol for nano

n = Prefix symbol meaning 10^{-9} unit. One thousandth of a millionth unit.

Typical usage includes nanoamp (nA), nanovolt (nV), nanowatt (nW) and nanosecond (ns).

n = Symbol for an indefinite number

N = Symbol for number, number of turns, etc.

N = A pure number. Symbol for seldom used quantities where the natural symbol is in recognized use for another quantity. N_p = Number of turns of primary winding of a transformer. N_s = Number of turns of secondary winding of a transformer. N_{pp} = Number of pairs of poles in a motor or generator.

$$N_p = (E_p N_s) / E_s \quad N_s = (E_s N_p) / E_p$$

$$N_p = (I_s N_s) / I_p \quad N_s = (I_p N_p) / I_s$$

$$N_{L1} = N_{Lt} \sqrt{L_1 / L_t} \quad (\text{Tapped inductor turns})$$

$$N_p = N_s \sqrt{Z_p / Z_s} \quad N_s = N_p \sqrt{Z_s / Z_p}$$

$$N_{Z1} = N_{Zt} \sqrt{Z_1 / Z_t} \quad (\text{Tapped secondary turns})$$

$$N_{pp} = f / \text{RPS} \quad (\text{Pairs of poles in a generator or sync. motor})$$

N = Symbol for newton (SI unit of force)

N_p = Symbol for neper (logarithmic ratio unit)

$$N_p = \ln \sqrt{P_2 / P_1} = 8.686 \text{ dB}$$

$$N_p = \ln(E_2 / E_1) = \ln(I_2 / I_1) \quad \text{when impedances are equal}$$

NF NI

Noise Figure,
Noise Index

NF = Symbol for noise figure.

(noise figure is also known as noise factor)

NF = The ratio in decibels of device output noise to ideal device output noise with all conditions of operation specified.

See—Active Circuits

NI = Symbol for noise index.

NI = The ratio, in decibels, of rms microvolts of excess noise in a decade of frequency, to the dc voltage applied to a resistor.

NI = Noise index expressed in decibels (dB).

$$NI = 20 \left(\log \left[\frac{(10^6 E_{N(EX)})}{(V_{dc})} \right] \right)$$

$$NI = 20 \left(\log \left[\frac{(\text{excess noise in microvolts rms})}{(\text{applied dc voltage})} \right] \right)$$

NI = -20 to +10 dB carbon composition

NI = -25 to -10 dB carbon film

NI = -40 to -15 dB metal film

NI = -40 to -15 dB wire wound

Notes:

① Excess noise is noise in excess of thermal noise.

② Excess noise is 1/f noise while thermal noise has equal output at all frequencies. (white noise)

③ $(E_N)_{EX} = \sqrt{(E_N)_t^2 - (E_N)_{th}^2}$ (all voltages rms)



**Subscript Only
Zero and
Letter O**

O, o = Subscript symbol for output, open circuit, zero time, zero current, characteristic, etc.

o = Output in E_o , I_o , P_o , h_{ob} , h_{oe} , h_{oc}

o = Output in C_{ob} , g_{os} , P_{ob} , P_{oe} , Y_{oc} , Y_{os}

o = Output in C_{obo} and C_{oeo} (first o)

o = Open circuit in C_{obo} and C_{oeo} (last o)

o = Open circuit in C_{ibo} , C_{ieo}

O = Open circuit in BV_{CBO} , BV_{EBO} , LV_{CEO}

O = Open circuit in I_{CO} , I_{CBO} , I_{CEO} , I_{EBO}

O = Open circuit in V_{CBO} , V_{CEO} , V_{EBO}

O = Characteristic (impedance) in Z_O

O = Oscillation (frequency) in f_O

o = Resonant (frequency) in f_o (f_r is preferred)

o = Center (frequency of passband) in f_o and ω_o

o = Initial (at zero time) in E_o , etc.

O = Letter O in most printed material

0 = Zero in most printed material

\emptyset = The character used for many years to distinguish between zero and the letter O. Unfortunately, it has been used for both zero and the letter O. It also has been mistaken for the greek letter ϕ . The use of this character in formulas is not recommended.

Definitions**P****Definitions**

P = Symbol for power

P = The rate at which energy is utilized to produce work. The rate at which work is done. The rate at which electrical energy is transformed to another form of energy such as heat, light, radiation, sound, mechanical work, potential energy in any form or any combination of any of the forms of energy.

P = Electrical power expressed or measured in watts (W)

Power is also expressed in dBm, microwatts (μW), milliwatts (mW), kilowatts (kW), megawatts (MW), etc.

P_{peak} = Instantaneous peak power

P = Effective or average power

$P = E_{\text{dc}} \cdot I_{\text{dc}} = E_{\text{rms}} \cdot I_{\text{rms}}$ (pure resistances only)

$P \neq E_{\text{average}} \cdot I_{\text{average}}$

P_{sinewave} = Power produced by sinewave *voltage* and *current*, not the waveshape of the power. (Power waveshapes are rarely used except for rectangular waves where the waveshapes of power, voltage and current are identical.)

P_{ac} = P_{dc} in heating effect and all other transformations of electrical energy

P = Zero in all purely reactive circuits

P = Zero when the phase angle of the current with respect to the voltage equals $\pm 90^\circ$

Power, DC Circuits	P	Power, DC Circuits
$P_t = P_1 + P_2 \dots + P_n$ $P = E^2G$ $P = EI$ $P = E^2/R$ $P = I^2/G$ $P = I^2R$	General	
$P_t = P_1 + P_2 \dots + P_n$ $P_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n] I$ $P_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]^2 / (R_t)$ $P_t = E^2 / (R_1 + R_2 \dots + R_n)$ $P_t = I^2 (R_1 + R_2 \dots + R_n)$	Series Circuits	
$P_t = P_1 + P_2 \dots + P_n$ $P_t = E^2 (G_1 + G_2 \dots + G_n)$ $P_t = E (I_1 + I_2 \dots + I_n)$ $P_t = E^2 (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})$ $P_t = I_t^2 / (G_1 + G_2 \dots + G_n)$ $P_t = I_t^2 / (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})$	Parallel Circuits	
<i>Note:</i> $G = 1/R$ in all dc circuits		

**Power Ratios,
Misc. Formulas**

P

**Power Ratios,
Misc. Formulas**

$$P_{\text{peak}} = (E_R)_{\text{peak}} \cdot (I_{\text{peak}})$$

$$P_{\text{peak}} = (E_R)_{\text{peak}}^2 / R$$

$$P_{\text{peak}} = (I_{\text{peak}})^2 R \quad (\text{all series circuits})$$

$$P_{\text{peak}} = 2 P_{\text{average}} \quad (\text{sinewave})$$

$$P_{\text{peak}} = P_{\text{average}} \quad (\text{squarewave})$$

$$P_{\text{square}} = 2 P_{\text{sine}} \quad (\text{with same } E_{\text{peak}} \text{ or } I_{\text{peak}})$$

$$P = (CE^2)/(2t) \quad (\text{Power from a capacitor charge for time } t)$$

$$P = W/t \quad (W = \text{Work equivalent energy in joules or watt-seconds})$$

$$P = (LI^2)/(2t) \quad (\text{Power for time } t \text{ from energy stored in the field of an inductance})$$

P_{TH} = Thermal noise power (any value resistance)

$$P_{\text{TH}} = K_B T_K BW \quad (\text{Available } P_{\text{TH}} = P_{\text{TH}}/4)$$

K_B = Boltzmann's constant = $1.38 \cdot 10^{-23} \text{ J/}^\circ\text{K}$

T_K = Kelvin temperature, BW = Bandwidth

PWL = Power level in (acoustic) watts.

$$PWL = \overline{SPL} + [20(\log r)] + .5 \text{ dB} = \text{dB above } 10^{-12} \text{ watt}$$

(Freefield conditions) \overline{SPL} = Sound pressure level in dB above $20 \mu\text{N/m}^2$, r = distance in feet

Power from Dissipation or Q Factor	P	Terms	
$P = EI \cos(\tan^{-1} D^{-1})$		E I D	All Circuits
$P = EI \cos(\tan^{-1} Q)$		E I Q	
$P = [E^2 \cos(\tan^{-1} D^{-1})] / Z$		E Z D	
$P = [E^2 \cos(\tan^{-1} Q)] / Z$		E Z Q	
$P = I^2 Z \cos(\tan^{-1} D^{-1})$		I Z D	
$P = I^2 Z \cos(\tan^{-1} Q)$		I Z Q	
$P = [E \cos(\tan^{-1} D^{-1})]^2 / [D(\omega C)^{-1}]$		E C D	Pure Series Circuit Only
$P = Q(\omega L)^{-1} [E \cos(\tan^{-1} Q)]^2$		E L Q	
$P = I^2 D(\omega C)^{-1}$		I C D	
$P = (I^2 \omega L) / Q$		I L Q	
$P = E^2 D \omega C$		E C D	Pure Parallel Circuit Only
$P = E^2 / (Q \omega L)$		E L Q	
$P = [I \cos(\tan^{-1} D^{-1})]^2 / (\omega C D)$		I C D	
$P = \omega L Q [I \cos(\tan^{-1} Q)]^2$		I L Q	

Power, Series Circuits	P	Applicable Notes	Terms
$P_t = P_1 + P_2 \dots + P_n$		① ②	P
$P_t = I [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]$		① ②	$E_R I$
$P_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]^2 / R_t$		① ②	$E_R R$
$P_t = I^2 (R_1 + R_2 \dots + R_n)$		① ②	I R
$P = EI \text{ pf}$		①	E I pf
$P = EI \cos \theta_1$		① ②	$E I \theta_1$
$P = (E \text{ pf})^2 / R$		①	E R pf
$P = (E \cos \theta_Z)^2 / R$		① ②	$E R \theta_Z$
$P = (E^2 \text{ pf}) / Z$		①	E Z pf
$P = (E^2 \cos \theta_Z) / Z$		① ②	E Z θ_Z

P Notes:

- ① B_C = Capacitive susceptance, B_L = Inductive susceptance, C = Capacitance, D = Dissipation Factor, E = rms or dc Voltage, E_{peak} = Instantaneous peak voltage, G = Conductance, I = rms or direct current, I_{peak} = Instantaneous peak current, L = Inductance, pf = Power Factor, Q = Quality, Merit or Storage Factor, R = Resistance, t = Time, W = Work, X = Reactance, Y = Admittance, Z = Impedance, θ = Phase angle, ω = Angular velocity = $2\pi f$, \tan = tangent, \sin = sine, \cos = cosine

Power, Series Circuits	P	Applicable Notes	Terms
$P = I^2 Z \text{ pf}$		①	I Z pf
$P = I^2 Z \cos \theta_Z$		① ②	I Z θ_Z
$P = (EZ^{-1})^2 \sqrt{Z^2 - [(\omega L) - (\omega C)^{-1}]^2}$		① ③	E C L Z
$P = (EZ^{-1})^2 \sqrt{Z^2 - (X_L - X_C)^2}$		① ② ③	E X_C X_L Z
$P = \left (E \text{ pf})^2 [\tan(\cos^{-1} \text{ pf})] [(\omega L) - (\omega C)^{-1}]^{-1} \right $		① ③ ④ ⑤	E C L pf
$P = \left[(E \cos \theta_Z)^2 (\tan \theta_Z) \right] / [(\omega L) - (\omega C)^{-1}]$		① ② ③ ⑤	E C L θ_Z
$P = \left (E \text{ pf})^2 [\tan(\cos^{-1} \text{ pf})] (X_L - X_C)^{-1} \right $		① ② ③ ④ ⑤	E X_C X_L pf
$P = \left[(E \cos \theta_Z)^2 (\tan \theta_Z) \right] / (X_L - X_C)$		① ② ⑤	E X_C X_L θ_Z
$P = I^2 \sqrt{Z^2 - [(\omega L) - (\omega C)^{-1}]^2}$		① ③	I C L Z
$P = I^2 \sqrt{Z^2 - (X_L - X_C)^2}$		① ②	I X_C X_L Z
$P = \left [I^2 (X_L - X_C)] / (\tan \theta_Z) \right $		① ② ⑤	I X_C X_L θ_Z

Power, Parallel Circuits	P	Applicable Notes	Terms
$P_t = P_1 + P_2 \dots + P_n$		① ②	P
$P = E^2(G_1 + G_2 \dots + G_n)$		① ②	E G
$P = E^2(R_1^{-1} + R_2^{-1} \dots + R_n^{-1})$		① ② ③	E R
$P = (I_G)_t^2 / (G_1 + G_2 \dots + G_n)$		① ②	I_G G
$P = (I_R)_t^2 (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})^{-1}$		① ② ③	I_R R
$P = EI_t \text{ pf}$		① ②	E I_t pf
$P = EI_t \cos \theta_I$		① ②	E I_t θ_I
$P = E^2 Y \text{ pf}$		①	E Y pf
$P = E^2 Y \cos \theta_Y$		① ②	E Y θ_Y
$P = (E^2 \text{ pf})/Z$		①	E Z pf
$P = (E^2 \cos \theta_Z)/Z$		① ②	E Z θ_Z

P Notes:

- ② Subscripts C = capacitive, E = voltage, G = conductance, I = current, L = inductive, n = any number, R = resistive, t = total or equivalent, X = reactive, Y = admittance, Z = impedance
- ③ $x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $|x|$ = Absolute value or magnitude of x
- ④ \tan^{-1} = arc tangent
 \cos^{-1} = arc cosine

Power, Parallel Circuits	P	Applicable Notes	Terms
$P = (I_t^2 \text{ pf})/Y$		①	I_t Y pf
$P = (I_t^2 \cos \theta_Y)/Y$		① ②	I_t Y θ_Y
$P = I_t^2 Z \text{ pf}$		① ②	I_t Z pf
$P = I_t^2 Z \cos \theta_Z$		① ②	I_t Z θ_Z
$P = E^2 \sqrt{Y^2 - (B_L - B_C)^2}$		① ②	E B_C B_L Y
$P = E^2 \sqrt{Z^{-2} - [(\omega L)^{-1} - (\omega C)]^2}$		① ③	E CL Z
$P = E^2 \sqrt{Z^{-2} - (X_L^{-1} - X_C^{-1})^2}$		① ② ③	E X_C X_L Z
$P = \left \frac{E^2 (B_L - B_C)}{[\tan(\cos^{-1} \text{ pf})]} \right $		① ② ③ ④ ⊗	E B_C B_L pf
$P = \left \frac{E^2 (B_L - B_C)}{(\tan \theta_Y)} \right $		① ② ③ ⊗	E B_C B_L θ_Y
$P = \left E^2 [(\omega L)^{-1} - (\omega C)] [\tan(\cos^{-1} \text{ pf})]^{-1} \right $		① ② ③ ④ ⊗	E CL pf
$P = \left E^2 [(\omega L)^{-1} - (\omega C)] [\tan \theta_Z]^{-1} \right $		① ② ③ ⊗	E CL θ_Z

P Notes: ⊗ Division by zero, tangent of $\pm 90^\circ$ and purely reactive circuits are prohibited.

Power, Parallel Circuits	P	Applicable Notes	Terms
$P = \left \left[E^2 (X_L^{-1} - X_C^{-1}) \right] / \left[\tan(\cos^{-1} \text{ pf}) \right] \right $		① ② ③ ④ ⊗	E X _C X _L pf
$P = \left E^2 (X_L^{-1} - X_C^{-1}) (\tan \theta_Z)^{-1} \right $		① ② ③ ⊗	E X _C X _L θ _Z
$P = (I_t Y^{-1})^2 \sqrt{Y^2 - (B_L - B_C)^2}$		① ② ③	I B _C B _L Y
$P = (I_t Z)^2 \sqrt{Z^{-2} - [(\omega L)^{-1} - (\omega C)]^2}$		① ② ③	I C L Z
$P = (I_t Z)^2 \sqrt{Z^{-2} - (X_L^{-1} - X_C^{-1})^2}$		① ② ③	I X _C X _L Z
$P = \left \left[(I \text{ pf})^2 \tan(\cos^{-1} \text{ pf}) \right] / (B_L - B_C) \right $		① ② ③ ④ ⊗	I B _C B _L pf
$P = \left \left[(I \cos \theta_Y)^2 \tan \theta_Y \right] / (B_L - B_C) \right $		① ② ③ ⊗	I B _C B _L θ _Y
$P = \left \left[(I \text{ pf})^2 \tan(\cos^{-1} \text{ pf}) \right] / [(\omega L)^{-1} - (\omega C)] \right $		① ③ ④ ⊗	I C L pf
$P = \left \left[(I \cos \theta_Z)^2 \tan \theta_Z \right] / [(\omega L)^{-1} - (\omega C)] \right $		① ② ③ ⊗	I C L θ _Z
$P = \left \left[(I \text{ pf})^2 \tan(\cos^{-1} \text{ pf}) \right] / (X_L^{-1} - X_C^{-1}) \right $		① ② ③ ④ ⊗	I X _C X _L pf
$P = \left \left[(I \cos \theta_Z)^2 \tan \theta_Z \right] / (X_L^{-1} - X_C^{-1}) \right $		① ② ③ ⊗	I X _C X _L θ _Z

p PF pf

Pico,
Power Factor

p = Symbol for pico (pronounced peeko).

p = Prefix symbol meaning 10^{-12} unit. Replaces old $\mu\mu$ prefix.

Typical usage includes picofarad (pF), picosecond (ps), picoampere (pA), and picowatt (pW).

PF = Symbol for power factor.

pf = Symbol for power factor. (other symbols for power factor include: F_p , $\cos \theta$, PF, P.F. and p.f.)

pf = The ratio of actual power of an alternating current to apparent power. The ratio of power in watts to volt-amperes. The cosine of the phase angle of alternating current with respect to the voltage.

pf = Power factor expressed as a decimal or as a percentage.

pf \simeq The inverse of Q factor when $Q > 7$

pf = A measurement more often than a calculation.

pf = The cosine of the phase angle when the angle is positive or negative, when the phase angle is current with respect to voltage or voltage with respect to current and when the angle represents the phase of impedance or admittance.

pf = A decimal number between zero and one, or a percentage between 0 and 100.

pf = One in purely resistive circuits and zero in purely reactive circuits

pf = The ratio of resistance to impedance

Power Factor, Series Circuits	pf	Applicable Notes	Terms
$pf = \cos \theta$ ($\theta = \theta_E, \theta_I$ or θ_Z)		①	θ
$pf = R/Z$		①	R Z
$pf = \left(R^{-2} [(\omega L) - (\omega C)^{-1}]^2 + 1 \right)^{-\frac{1}{2}}$		① ②	C L R
$pf = \sqrt{1 - \left([(\omega L) - (\omega C)^{-1}] / Z \right)^2}$		① ②	C L Z
$pf = P/(EI)$		①	E I P
$pf = (RI)/E$		①	E I R
$pf = (PZ)/E^2$		①	E P Z
$pf = P/(I^2 Z)$		①	I P Z
$pf = \left([(X_L - X_C)/R]^2 + 1 \right)^{-\frac{1}{2}}$		① ②	R X_C X_L
$pf = \sqrt{1 - [(X_L - X_C)/Z]^2}$		①	X_C X_L Z

pf Notes:

- ① B_C = Capacitive Susceptance, B_L = Inductive Susceptance, C = Capacitance, E = rms Voltage, G = Conductance, I = rms Current, L = Inductance, P = Power, R = Resistance, R_p = Parallel Resistance, X_C = Capacitive Reactance, X_L = Inductive Reactance, Y = Admittance, Z = Impedance, θ = Phase Angle, ω = Angular Velocity, $\omega = 2\pi f$

Power Factor, Parallel Circuits	pf	Applicable Notes	Terms
pf = $\cos \theta$ ($\theta = \theta_E, \theta_I, \theta_Y$ or θ_Z)		①	θ
pf = G/Y		①	$G Y$
pf = Z/R_p		①	$R_p Z$
pf = $\left([(B_L - B_C)/G]^2 + 1 \right)^{-\frac{1}{2}}$		① ②	$B_C B_L G$
pf = $\sqrt{1 - [(B_L - B_C)/Y]^2}$		①	$B_C B_L Y$
pf = $(EG)/I$		①	$E I G$
pf = $P/(EI)$		①	$E I P$
pf = $E/(IR_p)$		①	$E I R_p$
pf = $(PZ)/E^2$		①	$E P Z$
pf = $\left([R_p(X_L^{-1} - X_C^{-1})]^2 + 1 \right)^{-\frac{1}{2}}$		① ②	$R_p X_C X_L$
pf = $\sqrt{1 - [Z(X_L^{-1} - X_C^{-1})]^2}$		①	$X_C X_L Z$

pf Notes:

② $x^{-1} = 1/x, x^{-2} = 1/x^2, x^{-\frac{1}{2}} = 1/\sqrt{x}, \cos = \text{cosine}$

Q

Q Factor, Quality Factor

Q = Symbol for Q Factor, Merit Factor, Storage Factor, Energy Factor, Magnification Factor and Quality Factor. (All names refer to the same factor. "Q" Factor is preferred)

Q = 1. The ratio of energy stored to the energy dissipated in inductors, coils, tuned circuits, and transformers. (Dissipation Factor which is the inverse of Q is commonly used for capacitors and dielectrics).

2. The tangent of the phase angle of alternating current with respect to the voltage in inductors.

3. In inductors at a given frequency, the ratio of reactance to the equivalent series resistance.

Q = A number from zero to infinity. (usually between 10 and 100)


Q = A factor used to calculate equivalent series or parallel resistance and a factor used to predict the voltage or current magnification of LC resonant circuits.

<p>Real or Equivalent Resistance in Series with Reactance</p> $Q = (\omega L_s) / R_s$ $Q = (X_L)_s / R_s$	<p>Real or Equivalent Resistance in Parallel with Reactance</p> $Q = R_p / (\omega L_p)$ $Q = R_p / (X_L)_p$	Inductors
$Q = 1/D_s$ $Q = 1/(\omega C_s R_s)$ $Q = (X_C)_s / R_s$	$Q = 1/D_p$ $Q = \omega C_p R_p$ $Q = R_p / (X_C)_p$	Capacitors


**Inductors or
Capacitors in
Series or Parallel**

Q


Q Factor

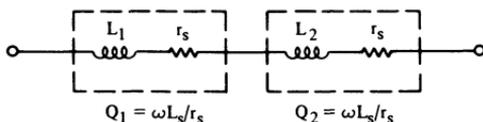

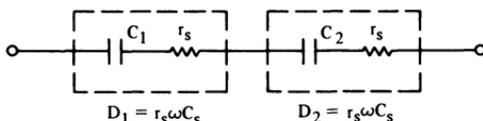
$$Q_t = (L_1 + L_2) / [(L_1/Q_1) + (L_2/Q_2)]$$


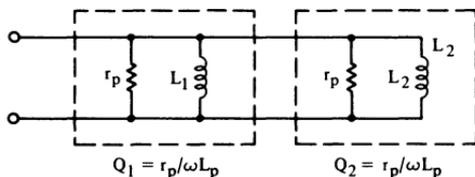
$$Q_t = (C_1 + C_2) / [(C_1 D_2) + (C_2 D_1)]$$


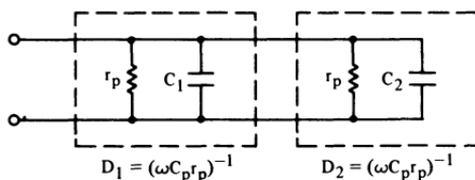
$$Q_t = (L_1^{-1} + L_2^{-1}) / [(L_1 Q_1)^{-1} + (L_2 Q_2)^{-1}]$$



$$Q_t = (C_1 + C_2) / [(C_1 D_1) + (C_2 D_2)]$$

Note: For series circuits C, D, L & Q must be C_s , D_s , L_s & Q_s . For parallel circuits C, D, L & Q must be C_p , D_p , L_p & Q_p . See Q Notes ③ & ④

**Series Resonant
Circuits**


Q

**Resonant Circuit
Q Factor**

$$Q = \infty$$

$$Z = 0, \quad BW = 0$$


$$f_r = (2\pi\sqrt{LC})^{-1}$$

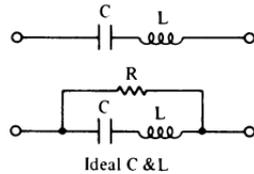

$$Q = (Q_s^{-1} + D_s)^{-1}$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}}$$

$$f_r = (2\pi\sqrt{LC})^{-1}$$

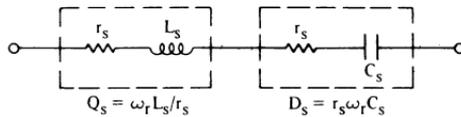


$$Q = L / (R\sqrt{LC})$$

$$Q = (2\pi f_r L) / R$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}}$$

$$f_r = (2\pi\sqrt{LC})^{-1}$$

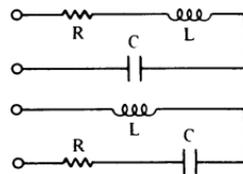


$$Q = \sqrt{LC} [(RC)^{-1} + (R/L)]$$

$$Q \approx \sqrt{LC} / (CR)$$

$$Q = (f_r)_{\text{DEF.1}} / (f_2 - f_1)_{-3\text{dB}}$$
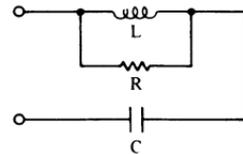
$$(f_r)_{\text{DEF.1}} = [(LC) - (L/R)^2]^{-\frac{1}{2}} / (2\pi)$$



Q Notes: ① BW = Bandwidth, C = Capacitance, D = Dissipation Factor, f_r = Frequency of Resonance, L = Inductance, R = Resistance, X = Reactance

**Series Resonant
Circuits**

Q


**Resonant Circuit
Q Factor**

$$Q = [(RC) + (L/R)] / \sqrt{LC}$$

$$Q \approx L / (R\sqrt{LC})$$

$$Q = (f_r)_{\text{DEF.1}} / (f_2 - f_1)_{-3\text{dB}}$$
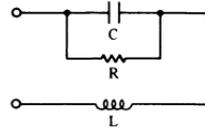
$$(f_r)_{\text{DEF.1}} = [(LC)^{-1} - (CR)^{-2}]^{1/2} / (2\pi)$$




$$Q = [Q_s^{-1} + D_s + (R\sqrt{L_s C_s} / L)]^{-1}$$

$$Q = L / [\sqrt{L_s C_s} (R + r_{L_s} + r_{C_s})]$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}}$$

$$f_r = (2\pi\sqrt{L_s C_s})^{-1}$$
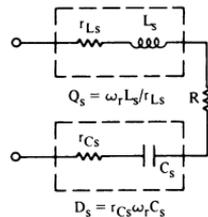
$$r_{L_s} = (\omega_r L_s) / Q_s, \quad r_{C_s} = D_s / \omega_r C_s$$




Note ③

$$Q = [\omega_r L_s / (R_{L_s} + R_{C_s})] \text{ Note ③}$$

$$Q \approx [2\pi f_r L (R_L^{-1} + R_C^{-1})]^{-1}$$

$$Q = (f_r)_{\text{DEF.1}} / (f_2 - f_1)_{-3\text{dB}}$$
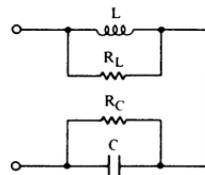
$$(f_r)_{\text{DEF.1}} = \sqrt{[(R_C^2 C)^{-1} - L^{-1}] / [(L/R_L^2) - C]} / (2\pi)$$



Q Notes:

- ① Cont. $\pi = 3.1416$, $\omega = \text{Angular Velocity } (2\pi f)$ $\omega_r = \text{Resonant Angular Velocity } (2\pi f_r)$
- ② $x^{-1} = 1/x$, $x^{1/2} = \sqrt{x}$, $x^{-1/2} = 1/\sqrt{x}$
- ③ D, Q, L and C do not have exactly the same value when capacitors and inductors are measured in the parallel mode. $L_s C_s$, $D_s Q_s = \text{Series mode.}$

**Parallel
Resonant Circuits**


Q

**Resonant Circuit
Q Factor**

$$Q = \infty$$

$$Z = \infty, \quad BW = 0$$

$$f_r = (2\pi\sqrt{LC})^{-1}$$

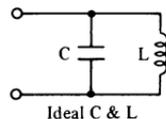


Note ④

$$Q = (Q_p^{-1} + D_p)^{-1} \quad \text{Note ⑤}$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}}$$

$$f_r = (2\pi\sqrt{L_p C_p})^{-1}$$

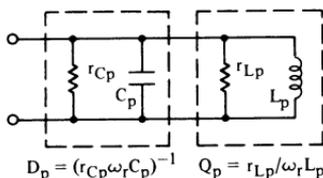


Note ⑥

$$Q = (R\sqrt{LC})/L$$

$$Q = R/(2\pi f_r L)$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}} = f_r / BW$$

$$f_r = (2\pi\sqrt{LC})^{-1}$$

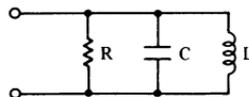


$$Q = \sqrt{(L/CR^2) - 1} \quad \text{exception} = \sqrt{-x}$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}} = f_r / BW$$

$$(f_r)_{\text{DEF.1}} = \sqrt{(LC)^{-1} - (R/L)^2} / (2\pi)$$

$$\text{exception} = \sqrt{-x}$$

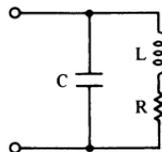

Q Notes:

- ④ D, Q, L and C do not have exactly the same value when measured in the series mode. D_p , Q_p , L_p and C_p = parallel mode.

**Parallel
Resonant Circuits**

Q


**Resonant Circuit
Q Factor**

$$Q = \sqrt{(L/CR^2) - 1}$$

$$Q = (f_r)_{\text{DEF.1}} / (f_2 - f_1)_{-3\text{dB}}$$

$$(f_r)_{\text{DEF.1}} = [(LC) - (CR)^2]^{-\frac{1}{2}} / (2\pi)$$


exception = $x^{-\frac{1}{2}}$

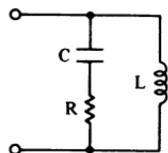

$$Q = \left[(L_p/C_p Q_p) + D_p + (L_p/R\sqrt{L_p C_p}) \right]^{-1} \quad \text{Note ⑤} \quad \text{Note ⑥}$$

$$Q = f_r / (f_2 - f_1)_{-3\text{dB}}$$

$$f_r = (2\pi\sqrt{L_p C_p})^{-1}$$

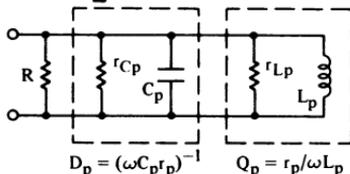


$$Q = [\omega_r L_p (R_{Lp}^{-1} + R_{Cp}^{-1})]^{-1} \quad \text{Note ⑨}$$

$$Q \approx \sqrt{L / [C(R_L + R_C)^2]}$$

$$(f_r)_{\text{DEF.1}} = \sqrt{[C^{-1} - (R_L^2/L)] / [L - (R_C^2 C)]} / (2\pi)$$

exception = $\sqrt{-x}$

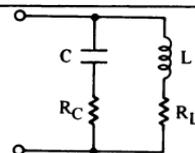

Q Notes:

- ⑤ C_p, D_p, L_p & Q_p = Parallel or equivalent parallel values. C_s, D_s, L_s & Q_s = Series or equivalent series values.
- ⑥ r_s = Equivalent series resistance derived from Q_s or D_s . r_p = Equivalent parallel resistance derived from Q_p or D_p .
- ⑦ Def. 1 = Resonant frequency definition 1. - See f_r . $(f_2 - f_1)_{-3\text{dB}} = 3 \text{ dB down bandwidth (half power)}$
- ⑧ L_s = Equivalent series inductance, R_{Ls} = Equivalent series resistance of inductor resistor. R_{Cs} = Equivalent series resistance of capacitor resistor.
- ⑨ L_p, R_{Cp} & R_{Lp} = Parallel equivalent of series quantities.

Q q

Electric Charge

Q = Symbol for quantity of electric charge

Q = Quantity of electric charge. The amount of excess electrons or the amount of holes (deficiency of electrons).

Q = Electric charge expressed in coulomb (C) units. (Many in electronics feel uncomfortable in using the symbol C for coulombs since the unit symbol C (coulombs) is seldom used and the capacitance symbol (C) is often used)

Q = Electric charge in units equal to $6.242 \cdot 10^{18}$ electrons

Q = The product of current and time in ampere · seconds

Q = CE

Q = It

Q = (2W)/E (W = work equivalent energy in joules or watt-

Q = $\sqrt{2CW}$ (seconds)

Charge of capacitor C, t seconds after application of voltage E to series RC circuit.

Q = $EC \left[1 - e^{-\frac{t}{RC}} \right]$ ($e = \ln$ base = 2.71828)

Q = Schematic Symbol for transistor. See – Active circuits

q = The electric charge of one electron or $1.6 \cdot 10^{-19}$ coulombs. (symbol e is also used for q)

Notes:

$$x^{(-y/z)} = (x^{-1})^{(y/z)} = \sqrt[z]{(x^{-1})^y}$$

(your scientific calculator will perform correctly with a negative exponent)

R = Symbol for resistance

R = That property which opposes the flow of electric current by the transformation of electrical energy into heat or other forms of energy. The total opposition to the flow of direct current at a given voltage. The non-reactive part of the total opposition to alternating current of a given voltage. The real part of impedance. The reciprocal of conductance in purely resistive or in dc circuits.

R = Resistance in units of ohms (Ω). (Ω = Greek letter capital omega) $k\Omega = 1000$ ohms, $M\Omega = 1,000,000$ ohms. $k\Omega$ is often contracted to K and $M\Omega$ is often contracted to M.

R = Parts list symbol for resistor.

R = $R/\angle 0^\circ$ in terms of polar impedance

R = $R + j0$ in terms of rectangular impedance

R Notes:

① B = Susceptance, C = Capacitance, D = Dissipation Factor, E = dc or rms voltage, f = Frequency, G = Conductance, I = rms or direct current, L = Inductance, P = Power, Q = Quality Factor, X = Reactance, Y = Admittance, Z = Impedance, Δ = Delta, θ = Phase Angle, π = Pi, ω = Angular Velocity, Ω = Ohm

② Subscripts:

C = capacitive, E = voltage, I = current, L = inductive, n = any number, p = parallel circuit, r = resonant, R = resistive, s = series circuit, t = total or equivalent, x = unknown, Y = admittance, Z = impedance 1, 2, 3 = first, second, third, A, B, C = first, second, third counterparts

Resistance, DC Circuits	R	Terms	
$R_t = R_1 + R_2 \dots + R_n$ $R_x = R_t - R_1$		R	Series Circuits
$R_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]/I$		E I	
$R_t = (E_R)_t^2/(P_1 + P_2 \dots + P_n)$ $R_t = [(E_R)_1 + (E_R)_2 \dots + (E_R)_n]^2/P_t$		E P	
$R_t = (P_1 + P_2 \dots + P_n)/I^2$		I P	
$R_t = (G_1 + G_2 \dots + G_n)^{-1}$		G	
$R_t = (R_1 R_2)/(R_1 + R_2)$ $R_t = (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})^{-1}$ $R_x = (R_1 R_t)/(R_1 - R_t)$ $R_x = (R_t^{-1} - R_1^{-1})^{-1}$		R	Parallel Circuits
$R_t = E/[(I_R)_1 + (I_R)_2 \dots + (I_R)_n]$		E I	
$R_t = E^2/(P_1 + P_2 \dots + P_n)$ $R_t = P_t/[(I_R)_1 + (I_R)_2 \dots + (I_R)_n]^2$		E P I P	

R Notes:

③ sin = sine, cos = cosine, tan = tangent

④ $x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$

**Equivalent
Resistance
from D and Q**

R_{EQUIV.}

**Equivalent
Resistance**

$R_s =$ Equiv. Series Resistance	$R_p =$ Equiv. Parallel Resistance	Terms
$R_s = D/(\omega C)$	$R_p = (\omega CD)^{-1}$	D C
$R_s = \omega LD$	$R_p = (\omega L)/D$	D L
$R_s = X_C D$	$R_p = X_C/D$	D X_C
$R_s = X_L D$	$R_p = X_L/D$	D X_L
$R_s = (\omega C Q)^{-1}$	$R_p = \omega C Q$	Q C
$R_s = (\omega L)/Q$	$R_p = Q/(\omega L)$	Q L
$R_s = X_C/Q$	$R_p = Q/X_C$	Q X_C
$R_s = X_L/Q$	$R_p = Q/X_L$	Q X_L
Series Resonant Circuits	Parallel Resonant Circuits	
$R_s = [D_C/(2\pi f_r C)] + [(2\pi f_r L)/Q_L]$	$R_p = \left([2\pi f_r C D_C] + [(2\pi f_r L)/Q_L] \right)^{-1}$	D Q C L
$R_s = [D_C X_C(@f_r)] + [(X_L(@f_r))/Q_L]$	$R_p = \left([D/X_C(@f_r)] + [(X_L(@f_r))/Q_L] \right)^{-1}$	D Q $X_C X_L$
Special Note: $f_r = (2\pi\sqrt{LC})^{-1}$		

Resistance, Series AC Circuits	R	Applicable Notes	Terms
$R_t = R_1 + R_2 \dots + R_n$ $R_x = R_t - R_1$		②	R
$R = \sqrt{Z^2 - (\omega C)^{-2}}$		① ④ ⑦	C Z
$R = \left [\tan \theta_Z (\omega C)]^{-1} \right $		① ② ③ ④ ⑤ ⑦	C θ_Z
$R = E_R / I$		① ②	E_R I
$R = E_R^2 / P$		① ②	E_R P
$R = P / I^2$		①	I P
$R = \sqrt{Z^2 - (\omega L)^2}$		① ⑦	L Z
$R = (\omega L) / (\tan \theta_Z)$		① ② ③ ⑦	L θ_Z
$R = \sqrt{Z^2 - X_C^2}$		① ②	X_C Z
$R = X_C / (\tan \theta_Z) $		① ② ③ ⑤	X_C θ_Z
$R = \sqrt{Z^2 - X_L^2}$		① ②	X_L Z
$R = X_L / (\tan \theta_Z)$		① ② ③	X_L θ_Z
$R = Z \cos \theta_Z$		① ② ③	Z θ_Z

R Notes:

⑤ $|x|$ = absolute value or magnitude of x

Resistance, Series AC Circuits	R	Applicable Notes	Terms
$R = \sqrt{Z^2 - [(\omega L) - (\omega C)^{-1}]^2}$		① ④ ⑦	C L Z
$R = \left [(\omega L) - (\omega C)^{-1}] / (\tan \theta_Z) \right $		① ② ③ ④ ⑥ ⑦ ⑧	C L θ_Z
$R = (E \cos \theta_I) / I$		① ② ③	E I θ_I
$R = (E_t \cos \theta_I)^2 / P$		① ② ③	E_t P θ_I
$R = \sqrt{Z^2 - (X_L - X_C)^2}$		① ②	X_C X_L Z
$R = (X_L - X_C) / (\tan \theta_Z) $		① ② ③ ⑤ ⑥ ⑧	X_C X_L θ_Z
Series to Parallel Conversion			
$R_p = Z / (\cos \theta_Z)$		① ②	Z θ_Z
$R_p = [(X_L - X_C)_s^2 / R_s] + R_s$		③	X_C X_L R

R Notes:

- ⑥ Phase angle may be θ_Z or θ_Y also $\theta_E - \theta_I$ or $\theta_I - \theta_E$
- ⑧ Division by zero at resonance prohibited ($\tan 0^\circ = 0$)
- ⑦ $\omega = 2\pi f$

Resistance, Parallel AC Circuits	R	Applicable Notes	Terms
$R = 1/G$ $R_t = (G_1 + G_2 \dots G_n)^{-1}$ $R_x = (G_t - G_1)^{-1}$		① ② ④	G
$R_t = (R_1 R_2)/(R_1 + R_2)$ $R_t = (R_1^{-1} + R_2^{-1})^{-1}$ $R_t = (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})^{-1}$ $R_x = (R_1 R_t)/(R_1 - R_t)$ $R_x = (R_t^{-1} - R_1^{-1})^{-1}$		① ② ④	R
$R = [Y^2 - B^2]^{-\frac{1}{2}}$		① ④	B Y
$R = (\tan \theta)/B $		① ③ ⑤	B θ
$R = [Y^2 - (\omega C)^2]^{-\frac{1}{2}}$		① ④ ⑦	C Y
$R = [Z^{-2} - (\omega C)^2]^{-\frac{1}{2}}$		① ④ ⑦	C Z
$R = (\tan \theta)/(\omega C) $		① ③ ⑤ ⑦	C θ
$R = E/I_R$		① ②	E I_R
$R = E^2/P$		①	E P
$R = P/I_R^2$		① ②	I_R P

Resistance, Parallel AC Circuits	R	Applicable Notes	Terms
$R = [Y^2 - (\omega L)^{-2}]^{-\frac{1}{2}}$		① ④ ⑦	L Y
$R = [Z^{-2} - (\omega L)^{-2}]^{-\frac{1}{2}}$		① ④ ⑦	L Z
$R = \omega L(\tan \theta) $		① ③ ⑤ ⑥ ⑦	L θ
$R = [Z^{-2} - X^{-2}]^{-\frac{1}{2}}$		① ④	X Z
$R = X(\tan \theta) $		① ③ ⑤ ⑥	X θ
$R = [Y \cos \theta_Y]^{-1}$		① ② ③ ④	Y θ_Y
$R = Z/(\cos \theta_Z)$		① ② ③ ⊗	Z θ_Z
$R = [Y^2 - (B_L - B_C)^2]^{-\frac{1}{2}}$		① ② ④	B _C B _L Y
$R = (\tan \theta)/(B_L - B_C) $		① ② ③ ⑤ ⊗	B _C B _L θ
$R = \left(Y^2 - [(\omega L)^{-1} - (\omega C)]^2 \right)^{-\frac{1}{2}}$		① ④ ⑦	C L Y
$R = \left(Z^{-2} - [(\omega L)^{-1} - (\omega C)]^2 \right)^{-\frac{1}{2}}$		① ④ ⑦	C L Z
$R = (\tan \theta)/[(\omega L)^{-1} - (\omega C)] $		① ③ ④ ⑤ ⑦ ⊗	C L θ

Resistance, Parallel AC Circuits	R	Applicable Notes	Terms
$R = EI_t(\cos \theta)$		① ② ③ ⑥	E I _t θ
$R = P/[I_t(\cos \theta)]$		① ② ③ ⑥	I _t P θ
$R = [Z^{-2} - (X_L^{-1} - X_C^{-1})^2]^{-\frac{1}{2}}$		① ② ④	X _C X _L Z
$R = (\tan \theta)/(X_L^{-1} - X_C^{-1}) $		① ② ③ ④ ⑤ ⑥ ⊗	X _C X _L θ
<hr/>			
Series Equivalent Resistance of a Parallel Circuit. [Parallel to Series Conversion (Transformation)]		Applicable Notes	Terms
$R_s = (\cos \theta_Y)/Y$		① ② ③	Y θ _Y
$R_s = Z \cos \theta_Z$		① ② ③	Z θ _Z
$R_s = G/[G^2 + (B_L - B_C)^2]$		① ②	B _C B _L G
$R_s = [R_p(X_L^{-1} - X_C^{-1})^2 + R_p^{-1}]^{-1}$		① ② ④	X _C X _L R


Series Circuits in Parallel

$$R_t = \left[(R_1 + R_2 \dots + R_n)_1^{-1} + (R_1 + R_2 \dots + R_n)_2^{-1} \dots + (R_1 + R_2 \dots + R_n)_n^{-1} \right]^{-1}$$


Parallel Circuits in Series

$$R_t = (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})_1^{-1} + (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})_2^{-1} \dots + (R_1^{-1} + R_2^{-1} \dots + R_n^{-1})_n^{-1}$$

Delta to Wye (Δ to Y) Transformation

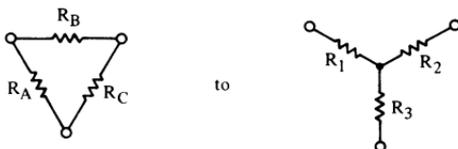

π section to T section Transformation

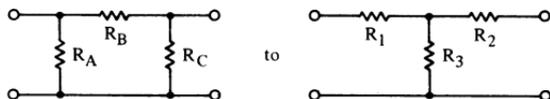

$$R_1 = (R_A R_B) / (R_A + R_B + R_C) \quad \text{Notes Applicable to this page } \textcircled{1} \textcircled{2} \textcircled{4}$$

$$R_2 = (R_B R_C) / (R_A + R_B + R_C)$$

$$R_3 = (R_A R_C) / (R_A + R_B + R_C)$$

$$R_A = \left[(R_1 R_2) + (R_2 R_3) + (R_1 R_3) \right] / R_2$$

$$R_B = \left[(R_1 R_2) + (R_2 R_3) + (R_1 R_3) \right] / R_3$$

$$R_C = \left[(R_1 R_2) + (R_2 R_3) + (R_1 R_3) \right] / R_1$$

Y to Δ
or
T to π
Transformation

Second

s S

Siemen

s = Symbol for second

s = Basic unit of time. 9 192 631 770 transitions between the two hyperfine levels of the ground state of the cesium-133 atom.

s = 10^{12} ps, 10^9 ns, 10^6 μ s and 10^3 ms

s = 1/3600 of an angular degree (decimals preferred)

s = Symbol for spacing

S = Symbol for siemens

S = Basic SI unit of conductance (G), susceptance (B) and admittance (Y) [The mho (Ω^{-1} or \mathcal{U}) predominates for this unit in the USA]

S = The reciprocal of resistance

S = $1/\Omega$ = mho

S = Abbreviation of signal (Sig is preferred).

S = Symbol for standing wave ratio.
(not recommended—use SWR or VSWR)

S = Symbol for cross-sectional area.
(the preferred symbol is A)

s = Subscript symbol for series and secondary

s = Subscript symbol for source and short-circuited

t

Time Definitions and Formulas

t = Symbol for time.

t = The duration of an event.

t = Time measured in seconds. (s or sec.) [time is expressed in picoseconds (ps), nanoseconds (ns), microseconds (μ s), milliseconds (ms), seconds (s), minutes (min.), hours (hr) etc]

t = $1/f$ Duration of one complete cycle of a periodic wave or of a periodic event.

t = $(CE)/I$ Time required to charge capacitance C to voltage E with current I.

t = Q/I Time required to accumulate charge Q in a capacitance with current I.

Time required to charge capacitance C to voltage e through resistance R from source voltage E.

$$t = -RC \left(\ln \left[1 - (e/E) \right] \right)$$

Time required to discharge capacitance C through resistance R from voltage E to voltage e.

$$t = RC \left[\ln(E/e) \right]$$

Time after application of voltage E to series inductance L and resistance R for current to rise from zero to current i.

$$t = -LR^{-1} \left(\ln \left[1 - (iRE^{-1}) \right] \right)$$

t *Notes:*

$$x^{-1} = 1/x, \ln(x) = \log_e(x)$$

t T

Temperature,
Telsa, Tera

t = Symbol for “customary” temperature (int’l).

T = Symbol for Kelvin temperature (int’l).

T = Symbol for temperature (USA common usage).

T_C = Symbol for temperature in degrees Celsius (°C).

T_F = Symbol for temperature in degrees Fahrenheit (°F).

T_K = Symbol for temperature in Kelvin (K).

$$T_C = (T_F - 32)/1.8$$

$$T_C = T_K - 273.15$$

$$T_F = 1.8T_C + 32$$

$$T_F = 1.8T_K - 459.67$$

$$T_K = T_C + 273.15$$

T_K = °C above absolute zero

Temperature determination of copper wire and copper wire windings by resistance measurement.

$$T_2 = [(R_2/R_1)(T_1 + 234.5)] - 234.5$$

R₁ = Resistance at known temperature T₁

R₂ = Resistance at unknown temperature T₂

T₁, T₂ = Temperature in °C

T = Symbol for telsa [SI unit of magnetic flux density (magnetic induction)]

T = Symbol for tera (unit prefix meaning 10¹² units)

T TC

**Time Constant,
Temperature
Coefficient**

T = Symbol for time constant. [other symbols include: t_C , Tc, TC, RC, script greek letter tau (τ) etc.]

T = 1. The time required for a capacitance to discharge through a resistance to 36.8% of the initial voltage or for the current to fall to 36.8% of the initial current.

2. The time required for a capacitance to charge through a resistance to 63.2% of the final voltage or for the current to fall to 36.8% of the initial current.

3. The time required for the voltage developed by cutoff of current through an inductor to fall to 36.8% of the maximum value.

4. The time required after application of voltage for the current through a series connected inductance and resistance to rise to 63.2% of the final value. [The exact values of 36.8% and 63.2% are $100e^{-1}$ and $100(1 - e^{-1})$]

$$T = RC \quad \text{also } (M\Omega) \cdot (\mu F)$$

$$T = L/R$$

TC = Symbol for temperature coefficient (other symbols include α)

TC = In circuit elements or materials, a factor used to determine the changes in characteristics with changes in its temperature.

TC = A factor in decimal, percentage or parts per million form per degree temperature change. (temperature coefficient is almost always in $^{\circ}C$)

Notes:

e = Base of natural logarithms (2.71828 ---), $e^{-1} = 1/e$. One part per million = .0001%.

U

**Mu Substitute,
Unit**

u = Typewritten substitute for greek letter mu (μ)
See— μ

u, U = Abbreviation of unit, ultra, etc.

V

Velocity

v = Symbol for velocity

v = Rate of motion in a given direction. A vector quantity having both magnitude (speed) and direction with respect to a reference.

v = Velocity measured in various linear units per second.

v = $f\lambda$ (f = frequency, λ = wavelength)

Velocity of sound in air

$v \simeq (1051 + 1.1T_F)$ ft/sec. (1136 @ 77°F)

$v \simeq (331.4 + .6T_C)$ meters/sec. (346.3 @ 25°C)

Velocity of sound in fresh water

$v = 1557 - [.245(74 - T_C)]$ meters/sec.

Velocity of electromagnetic waves in vacuum. (including light)

$v = 2.997\,925 \cdot 10^8$ m/s (use symbol c for light)

V

**Volt, Voltage,
Volume**

V = Symbol for volt (unit of electromotive force)

V = Symbol for electromotive force
(See—E for passive circuits. See also—V in active circuit sections)

V = The basic unit of electromotive force, potential or voltage.
The electric force required to develop a current of one ampere in a circuit with an impedance of one ohm.

V = Unit often used with multiplier prefixes

$$\mu\text{V} = 10^{-6} \text{ V} \quad \text{mV} = 10^{-3} \text{ V}$$

$$\text{kV} = 10^3 \text{ V} \quad \text{MV} = 10^6 \text{ V}$$

V = $\pm V_{\text{dc}}$ or V_{rms} (magnitude) (exceptions noted)

V_{BE} , V_{CC} , V_{CE} , etc.—See Active Circuits

V = Symbol for volume (cubic content)

V = The amount of space in three dimensions.

V = Volume measured in various units such as cubic inches (in^3), cubic feet (ft^3), cubic centimeters (cm^3), cubic meters (m^3), etc.

Volume required for Helmholtz resonator. (ported hollow sphere or box)

$$V = d[1948.7/f_r]^2 \quad (d \text{ in } x \text{ units, } V \text{ in } x^3 \text{ units})$$

d = diameter of port.

f_r = frequency of resonance in hertz

W

**Watt,
Work,
Energy**

W = Symbol for watt.

W = Basic unit of electric power. A unit of power equal to a current of one ampere through a resistance of one ohm. ($P = I^2R$)

W = Unit often used with multiplier prefixes

$$\mu W = 10^{-6} \text{ Watts} \quad mW = 10^{-3} \text{ Watts}$$

$$kW = 10^3 \text{ Watts} \quad MW = 10^6 \text{ Watts}$$

W = Symbol for work.

W = Symbol for energy. (Energy is potential work.) (The energy symbol E is rarely used in electronics thus avoiding confusion with emf symbol E.)

W = The product of power and time.

W = Work or energy in joule (J) units in electronics. (joules = watts · seconds) Other units include kilowatt hour (kWh), foot-pound (ft · lbf), erg (erg) etc.

Energy stored in a capacitor charge

$$W = .5CE^2$$

$$W = Q^2/(2C)$$

$$W = .5QE$$

W = $.5LI^2$ Energy stored in the field of an inductance.

X

Definitions

X = Symbol for reactance

X = That property of inductances and capacitances which opposes the flow of alternating current by storage of electrical energy. The imaginary part of impedance. The reciprocal of susceptance in purely parallel circuits. The non-resistive part of the total opposition to the flow of alternating current.

X = Reactance expressed in ohm (Ω) units.

X = $X_{\text{magnitude}}$

X_C = Magnitude of capacitive reactance

X_L = Magnitude of inductive reactance

$-X$ = Reactance identified as capacitive, not a real negative quantity.

$+X$ = Reactance identified as inductive, not a real positive quantity.

$-X = |-X| = X_C$

$+X = |+X| = X_L$

X = Complete description of reactance

$X_C = X_C / -90^\circ$ in terms of polar impedance

$X_L = X_L / +90^\circ$ in terms of polar impedance

$X_C = 0 - jX_C = 0 + (-X_C)j$ (rectangular impedance)

$X_L = 0 + jX_L = 0 + (+X_L)j$ (rectangular impedance)

Note that in $(-X_C)j$ and $(+X_L)j$, X_C and X_L have become real negative and positive quantities with the same signs that are assigned to the magnitude quantities.

Reactance, General and Misc.	X	Applicable Notes
$X_C = (\omega C)^{-1} = 1/(2\pi f C)$ $X_L = \omega L = 2\pi f L$ $X = R_s/D$ $X = R_s Q$ $X = Z \quad \text{when } R_s = 0$ $X_L - X_C = \pm X$ $ +X = X_L$ $ -X = X_C$ $X_L - X_C = 0 \text{ @ resonance}$		① ② ③ ⑤ Series Circuits
$X_C = B_C^{-1} = 1/B_C$ $X_L = B_L^{-1} = 1/B_L$ $X_C = (\omega C)^{-1} = 1/(2\pi f C)$ $X_L = \omega L = 2\pi f L$ $X = R_p D$ $X = Q/R_p$ $X_L^{-1} - X_C^{-1} = \pm X_p^{-1} = \pm B$ $ +X_p^{-1} = X_L^{-1} = B_L$ $ -X_p^{-1} = X_C^{-1} = B_C$ $[X_L^{-1} - X_C^{-1}]^{-1} = \infty \text{ @ resonance}$		① ② ③ ⑤ ④ Parallel Circuits

Reactance, Series Circuits	X	Applicable Notes	Terms
$(X_C)_t = \omega^{-1}(C_1^{-1} + C_2^{-1} \dots + C_n^{-1})$ $-X_t = \omega^{-1}(C_1^{-1} + C_2^{-1} \dots + C_n^{-1})$		① ② ③ ⑤	C
$(X_L)_t = \omega(L_1 + L_2 \dots + L_n)$ $+X_t = \omega(L_1 + L_2 \dots + L_n)$		① ② ③ ⑤	L
$(X_C)_t = (X_C)_1 + (X_C)_2 \dots + (X_C)_n$ $-X_t = (-X_1) + (-X_2) \dots + (-X_n)$		① ② ③ ⑤	X_C $-X$
$(X_L)_t = (X_L)_1 + (X_L)_2 \dots + (X_L)_n$ $+X_t = (+X_1) + (+X_2) \dots + (+X_n)$		① ② ③ ⑤	X_L $+X$
$\pm X = (\omega L) - (\omega C)^{-1}$		① ③ ⑤	C L
$ X = \sqrt{Z^2 - R^2}$		① ③	R Z
$\pm X = R [\tan(\pm\theta_Z)]$		① ② ④ ⑤	R θ_Z
$\pm X = X_L - X_C$		① ② ⑤	$X_C X_L$
$\pm X = Z [\sin(\pm\theta_Z)]$		① ② ④ ⑤	Z θ_Z

Reactance, Series Circuits	X	Applicable Notes	Terms
$ X = \sqrt{(E/I)^2 - (P/I^2)^2}$		① ③	E I P
$ X = \sqrt{(E/I)^2 - R^2}$		① ③	E I R
$\pm X = (E/I) [-\sin(\pm\theta_I)]$		① ② ④ ⑤	E I θ_I
$\pm X = P^{-1} (E \cos \theta)^2 [\tan(\pm\theta_Z)]$		① ② ③ ④ ⑤ ⊗	E P θ_Z
$ X = \sqrt{Z^2 - (P/I^2)^2}$		① ③	I P Z
$\pm X = (P/I^2) [-\tan(\pm\theta_I)]$		① ② ④ ⑤	I P θ_I
Series to Parallel Conversion			
$\pm X_p = Z [\sin(\pm\theta_Z)]^{-1}$		① ② ④ ③ ⑤	Z θ_Z
$\pm X_p = \pm X_s^{-1} (\pm X_s^2 + R_s^2)$		① ② ④ ③ ⑤	R _s $\pm X_s$

Reactance, Parallel Reactive Elements	X	Applicable Notes	Terms
$(X_C)_t = [(B_C)_1 + (B_C)_2 \cdots + (B_C)_n]^{-1}$		① ②	B_C
$(X_C)_t = [(-B_1) + (-B_2) \cdots + (-B_n)]^{-1}$		③	$-B$
$(X_L)_t = [(B_L)_1 + (B_L)_2 \cdots + (B_L)_n]^{-1}$		① ②	B_L
$(X_L)_t = [(+B_1) + (+B_2) \cdots + (+B_n)]^{-1}$		③	$+B$
$(X_C)_t = [\omega(C_1 + C_2 \cdots + C_n)]^{-1}$		① ② ③	C
$(X_L)_t = [\omega^{-1}(L_1^{-1} + L_2^{-1} \cdots + L_n^{-1})]^{-1}$		① ② ③	L
$(X_C)_t = [(X_C)_1^{-1} + (X_C)_2^{-1} \cdots + (X_C)_n^{-1}]^{-1}$		① ②	X_C
$(X_C)_t = [(-X_1)^{-1} + (-X_2)^{-1} \cdots + (-X_n)^{-1}]^{-1}$		③	$-X$
$(X_L)_t = [(X_L)_1^{-1} + (X_L)_2^{-1} \cdots + (X_L)_n^{-1}]^{-1}$		① ②	X_L
$(X_L)_t = [(+X_1)^{-1} + (+X_2)^{-1} \cdots + (+X_n)^{-1}]^{-1}$		③	$+X$
$\pm X = [B_L - B_C]^{-1}$		① ② ③ ⑤ ④	$B_C B_L$
$\pm X = [(\omega L)^{-1} - (\omega C)]^{-1}$		① ② ③ ⑤ ④	$C L$
$\pm X = [X_L^{-1} - X_C^{-1}]^{-1}$		① ② ③ ⑤ ④	$X_C X_L$

Reactance, Parallel Circuits	X	Applicable Notes	Terms
$ X = [Y^2 - G^2]^{-\frac{1}{2}}$		① ③	G Y
$\pm X = [-G \tan(\pm\theta_Y)]^{-1}$		① ② ③ ④ ⑤ ⑥	G θ_Y
$ X = [Z^{-2} - R^{-2}]^{-\frac{1}{2}}$		① ③	R Z
$\pm X = R[\tan(\pm\theta_Z)]^{-1}$		① ② ③ ④ ⑤ ⑥	R θ_Z
$\pm X = [-Y \sin(\pm\theta_Y)]^{-1}$		① ② ③ ④ ⑤ ⑥	Y θ_Y
$\pm X = [Z^{-1} \sin(\pm\theta_Z)]^{-1}$		① ② ③ ④ ⑤ ⑥	Z θ_Z
$ X = [(I/E)^2 - G^2]^{-\frac{1}{2}}$		① ③	E I G
$\pm X = E[I_L - I_C]^{-1}$		① ② ③ ⑤ ⑥	E I _C I _L
$ X = [(I/E)^2 - R^{-2}]^{-\frac{1}{2}}$		① ③	E I R
$\pm X = -E[I \sin(\pm\theta_I)]^{-1}$		① ② ③ ⑤ ⑥	E I θ_I

Reactance, Parallel Circuits	X	Applicable Notes	Terms
$ X = [Z^{-2} - (P/E^2)^2]^{-\frac{1}{2}}$		① ③	E P Z
$\pm X = (E^2/P) [\tan(\pm\theta_Z)]^{-1}$		① ② ③ ④ ⑤ ⑥	E P θ_Z
Parallel to Series Conversion			
$\pm X_s = Z [\sin(\pm\theta_Z)]$		① ② ③	Z θ_Z
$\pm X_s = [(\pm X_p/R_p^2) + (\pm X_p)^{-1}]^{-1}$		④ ⑤ ⑥	R _p $\pm X_p$

X Notes:

- ① General: B = Susceptance, C = Capacitance, D = Dissipation factor, E = Voltage, f = Frequency, G = Conductance, I = Current, L = Inductance, P = Power, Q = Q factor, R = Resistance, X = Reactance, Y = Admittance, Z = Impedance, θ = Phase angle, ω = Angular velocity, $\omega = 2\pi f$, $\omega = 6.283 \dots f$
- ② Subscripts:
c = Capacitive, E = Voltage, I = Current, L = Inductive, n = Any number, p = Parallel circuit, R = Resistive, s = Series circuit, t = Total or equiv., X = Reactive, Y = Admittance, Z = Impedance
- ③ Mathematics:
 $x^{-1} = 1/x$, $x^{-2} = 1/x^2$, $x^{\frac{1}{2}} = \sqrt{x}$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $|x|$ = Magnitude of x, ∞ = Infinite
- ④ \tan = tangent, \sin = sine, \cos = cosine, \tan^{-1} = arc tangent, \sin^{-1} = arc sine
- ⑤ Reminders:
 $\pm B$, $\pm X$, $\pm \theta$ – use the sign of the quantity.
 $|+B| = B_L$, $|-B| = B_C$, $|+X| = X_L$, $|-X| = X_C$.
 $+\theta_Z$ = Inductive circuit, $-\theta_Z$ = Capacitive circuit.
- ⑥ The reciprocal of zero may be manually converted to infinity.
 $\infty \cdot x = \infty$ when $x \neq 0$, $\infty/x = \infty$ when $x \neq \infty$
The reciprocal of infinity may be manually converted to zero.
 $0 \cdot x = 0$ when $x \neq \infty$, $0/x = 0$ when $x \neq 0$
- ⊗ Division by zero is prohibited.

Y

Admittance Definitions

Y = Symbol for admittance

Y = The total ease of alternating current flow at a given frequency and voltage. The reciprocal of impedance. A quantity which in rectangular form is as useful for parallel circuits as impedance is for series circuits. The resultant of conductance and susceptance in parallel. The resultant of reciprocal resistance and reciprocal reactance in parallel.

Y = Admittance expressed in siemens (S) or mho (Ω^{-1}) units.

$$Y = |Y| = Y_{\text{MAGNITUDE}}$$

θ_Y = Phase angle of admittance

$$Y_{\text{POLAR}} = Y / \pm \theta_Y = Z^{-1} / -(\pm \theta_Z)$$

$$Y_{\text{RECT}} = G - (\pm B)j = R_p^{-1} - (\pm X_p^{-1})j$$

- Y_{RECT} =
1. The rectangular form of admittance
 2. The complex number form of admittance
 3. The mathematical equivalent of conductance (G) and susceptance (B) in parallel
 4. The mathematical equivalent of reciprocal resistance (R^{-1}) and reciprocal reactance (X^{-1}) in parallel.

Y_{RECT} = An easy method of transforming a series circuit to a parallel equivalent circuit.

Y_{RECT} = Complex quantity used to solve problems involving complex parallel circuits.

Y_{RECT} = A quantity that is identical to rectangular assumed current when the assumed voltage is one.

Y Notes:**① General:**

B = Susceptance	C = Capacitance	D = Dissipation factor
E = rms Voltage	f = Frequency	G = Conductance
I = rms Current	j = Imaginary number	L = Inductance
P = Power	Q = Q factor	R = Resistance
X = Reactance	Y = Admittance	Z = Impedance
ϵ = Base of natural logarithms	π = Circum. to diam. ratio	
θ = Phase angle	ω = Angular Velocity	

② Subscripts:

C = capacitive	E = voltage	I = current
L = inductive	n = any number	p = parallel circuit
R = resistive	s = series circuit	t = total or equiv.
X = reactive	Y = admittance	Z = impedance

③ Constants:

$j = \sqrt{-1}$ = mathematical i = 90° multiplier	
$\epsilon = 2.718 \dots$	$\epsilon^{-1} = .36788 \dots$
$\pi = 3.1416$	$2\pi = 6.283 \dots$
$\omega = 2\pi f$	$\omega = 6.283 \dots f$

④ Algebra:

$x^{-1} = 1/x$	$x^{-2} = 1/x^2$	$x^{\frac{1}{2}} = \sqrt{x}$
$x^{-\frac{1}{2}} = 1/\sqrt{x}$	$ x $ = absolute value or magnitude of x	

⑤ Trigonometry:

sin = sine	cos = cosine	tan = tangent
\sin^{-1} = arc sine	\cos^{-1} = arc cosine	\tan^{-1} = arc tangent

⑥ Reminders:

$\pm \theta$ --- Use the sign of the angle

$\pm X, \pm I_X, \pm E_X, \pm B$ --- + identifies the quantity as inductive
 - identifies the quantity as capacitive

(As terms in formulas, these quantities must be used as real positive or negative quantities)

⑦ Cosine θ :

The cosine of either a positive or a negative angle is positive, therefore, $\cos \theta_Z = \cos \theta_Y = \cos \theta_E = \cos \theta_I$

Admittance, Series Circuits	Y	Applicable Notes	Terms
$Y = Z^{-1} = 1/Z$		① ④	Z
$Y = \left(R^2 + [(\omega L) - (\omega C)^{-1}]^2 \right)^{-\frac{1}{2}}$		① ③ ④	CL R
$Y = (\sin \theta) / [(\omega L) - (\omega C)^{-1}] $		① ③ ④ ⑤ ⑦ ⑧	CL θ
$Y = I/E$		①	E I
$Y = [R^2 + (X_L - X_C)^2]^{-\frac{1}{2}}$		① ② ④	R $X_C X_L$
$Y = (\cos \theta)/R$		① ⑤ ⑦	R θ
$Y = (\sin \theta)/(X_L - X_C) $		① ② ⑤ ⑦ ⑧	$X_C X_L \theta$
$Y = P/(E^2 \cos \theta)$		① ⑤ ⑦	E P θ
$Y = (I^2 \cos \theta)/P$		① ⑤ ⑦	I P θ

Y Notes:

- ④ The reciprocal of zero may be manually converted to infinity.
 $\infty \cdot x = \infty$ when $x \neq 0$, $\infty/x = \infty$ when $x \neq \infty$
 The reciprocal of infinity may be manually converted to zero.
 $0 \cdot x = 0$ when $x \neq \infty$, $0/x = 0$ when $x \neq 0$
- ⊗ Division by zero is prohibited. A zero divisor will occur at resonance and/or in purely reactive circuits.

Admittance, Parallel Circuits	Y	Applicable Notes	Terms
$Y = Z^{-1} = 1/Z$		① ④	Z
$Y = \sqrt{G^2 + (B_L - B_C)^2}$		① ②	$B_C B_L G$
$Y = (B_L - B_C)/(\sin \theta_Y) $		① ② ④ ③ ⑧	$B_C B_L \theta_Y$
$Y = \sqrt{R^{-2} + [(\omega L)^{-1} - (\omega C)]^2}$		① ③ ④	CL R
$Y = [(\omega L)^{-1} - (\omega C)]/(\sin \theta_Z) $		① ② ③ ④ ⑤ ⑧	CL θ_Z
$Y = I/E$		①	E I
$Y = G/(\cos \theta_Y) $		① ② ④	G θ_Y
$Y = \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}$		① ② ④	R $X_C X_L$
$Y = [R \cos \theta_Z]^{-1}$		① ② ④ ⑤	R θ_Z
$Y = P/(E^2 \cos \theta_Z)$		① ② ⑤	P E θ_Z
$Y = (I_t^2 \cos \theta_Z)/P$		① ② ⑤	$I_t P \theta_Z$

Y

Admittance and Phase, Series Circuits

Series Circuit Polar Admittance Formulas

$$\mathbf{Y}_{\text{POLAR}} = Y / \pm \theta_Y = Z^{-1} / -(\pm \theta_Z)$$

Polar Impedance is Preferred

Series Circuit Rectangular Admittance Formulas

Special Note: Rectangular admittance is intrinsically a parallel circuit quantity. The rectangular admittance of a series circuit is the mathematical equivalent of reciprocal resistance and reciprocal reactance in *parallel*.

$$\mathbf{Y}_{\text{RECT}} = G - (\pm B)j \quad \text{where} \quad |+B| = B_L, \quad |-B| = B_C$$

$$\mathbf{Y}_{\text{RECT}} = R_p^{-1} - (\pm X^{-1})j \quad \text{where} \quad |+X| = X_L, \quad |-X| = X_C$$

$$\mathbf{Y}_{\text{RECT}} = [Y \cos \theta_Y] - (Y \sin [-(\pm \theta_Y)])j$$

$$\mathbf{Y}_{\text{RECT}} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm \theta_Z)]j$$

$$G = R_p^{-1} = Y \cos \theta_Y = Z^{-1} \cos \theta_Z \quad \text{Note } \textcircled{a}$$

$$\pm B = B_L - B_C = X_L^{-1} - X_C^{-1}$$

$$\pm B = Y \sin [-(\pm \theta_Y)] = Z^{-1} \sin(\pm \theta_Z)$$

Note: Rectangular admittance is identical to rectangular current produced by a voltage of one except for the names of quantities. When $E = 1$, $I_{\text{POLAR}} = \mathbf{Y}_{\text{POLAR}}$, $I_{\text{RECT}} = \mathbf{Y}_{\text{RECT}}$, $I_R = G$, $I_{X_L} = B_L$, $I_{X_C} = B_C$, $\pm I_X = \pm B$.

Note: The use of $\mathbf{Y}_{\text{POLAR}}$ is not recommended unless used as a means of identification of a parallel quantity. Convert directly from $\mathbf{Z}_{\text{POLAR}}$ to \mathbf{Y}_{RECT}

See also $-Z$, θ , G and B

Admittance and Phase, Series Circuits	Y	Applicable Notes	Terms
$Y = \left(R^2 + [(\omega L) - (\omega C)^{-1}]^2 \right)^{-\frac{1}{2}}$ $\angle \pm \theta_Y = \tan^{-1} \left(- [(\omega L) - (\omega C)^{-1}] / R \right)$ $Y_{\text{RECT}} = G - (\pm B) j$ $G = [(\pm X_s^2 / R_s) + R_s]^{-1}$ $\pm B = [(R_s^2 / \pm X_s) + (\pm X_s)]^{-1}$ $\pm X_s = (\omega L_s) - (\omega C_s)^{-1}$	① ② ③ ④ ⑤ ⑥ ⑥	C L R	
$Y = [R^2 + (X_L - X_C)^2]^{-\frac{1}{2}}$ $\angle \pm \theta_Y = \tan^{-1} [-(X_L - X_C) / R]$ $Y_{\text{RECT}} = R_p^{-1} - (\pm X_p^{-1}) j$ $R_p^{-1} = R_s / [R_s^2 + (\pm X_s)^2]$ $\pm X_p^{-1} = \pm X_s / [(\pm X_s)^2 + R_s^2]$ $\pm X_s = X_L - X_C$	① ② ③ ④ ⑤ ⑥ ⑥	X _C X _L R	
$Y = Z^{-1}, \quad \angle \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = G - (\pm B) j$ $G = Z^{-1} \cos \theta_Z$ $\pm B = Z^{-1} \sin (\pm \theta_Z)$	① ② ③ ④ ⑤ ⑥	Z $\pm \theta_Z$	

**Admittance
and Phase,
Parallel Circuits**

Y

$$Y_{\text{POLAR}} = Y / \pm \theta_Y$$

$$Y_{\text{RECT}} = G - (\pm B) j$$

Note: $G = R_p^{-1}$, $\pm B = (X_L)_p^{-1} - (X_C)_p^{-1}$ ④		Applicable Notes	Terms
$Y = \sqrt{G^2 + (B_L - B_C)^2}$ $\pm \theta_Y = \tan^{-1} [-(B_L - B_C)/G]$ $Y_{\text{RECT}} = G - (B_L - B_C) j$		① ② ⑤ ⑥	G B _L B _C
$\pm \theta_Y = \sin^{-1} [-(B_L - B_C)/Y]$ $Y_{\text{RECT}} = \sqrt{Y^2 - (B_L - B_C)^2} - (B_L - B_C) j$		① ② ⑤ ⑥	Y B _L B _C
$Y = (B_L - B_C)/(\sin \theta_Y) $ $Y_{\text{RECT}} = \left(\frac{-(B_L - B_C)}{[\tan(\pm \theta_Y)]} \right) - (B_L - B_C) j$		① ② ⑤ ⑥ ⊗	θ_Y B _L B _C
$Y = \sqrt{R^{-2} + [(\omega L)^{-1} - (\omega C)]^2}$ $\pm \theta_Y = \tan^{-1} \left(R [(\omega L)^{-1} - (\omega C)] \right)$ $Y_{\text{RECT}} = R^{-1} - [(\omega L)^{-1} - (\omega C)] j$		① ② ③ ④ ⑤ ⑥	R L C
$Y = Z^{-1}$ $\pm \theta_Y = \sin^{-1} \left(-Z [(\omega L)^{-1} - (\omega C)] \right)$ $Y_{\text{RECT}} = \sqrt{Z^{-2} - [(\omega L)^{-1} - (\omega C)]^2} - [(\omega L)^{-1} - (\omega C)] j$		① ② ③ ④ ⑤ ⑥	Z L C

**Admittance
and Phase,
Parallel Circuits**

Y

$$Y_{\text{POLAR}} = Y / \pm \theta_Y$$

$$Y_{\text{RECT}} = G - (\pm B) j$$

Note: $G = R_p^{-1}$, $\pm B = (X_L)^{-1} - (X_C)^{-1}$ ④	Applicable Notes	Terms
$Y = \left [(\omega L)^{-1} - (\omega C)] / (\sin \theta_Y) \right $ $Y_{\text{RECT}} = \left(- [(\omega L)^{-1} - (\omega C)] / [\tan(\pm \theta_Y)] \right)$ $- [(\omega L)^{-1} - (\omega C)] j$	① ② ③ ④ ⑤ ⑥ ⑧	θ_Y CL
$Y = G / (\cos \theta_Y)$ $Y_{\text{RECT}} = G - [-G \tan(\pm \theta_Y)] j$	① ② ⑤ ⑥	θ_Y G
$Y = \sqrt{R^{-2} + (X_L^{-1} - X_C^{-1})^2}$ $\pm \theta_Y = \tan^{-1} [-R(X_L^{-1} - X_C^{-1})]$ $Y_{\text{RECT}} = R^{-1} - (X_L^{-1} - X_C^{-1}) j$	① ② ④ ⑤ ⑥	X_L X_C R
$Y = [R \cos \theta_Z]^{-1} \quad \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = R^{-1} - [R^{-1} \tan(\pm \theta_Z)] j$	① ② ④ ⑤ ⑥	θ_Z R
$Y = Z^{-1}$ $\pm \theta_Y = \sin^{-1} [-Z(X_L^{-1} - X_C^{-1})]$ $Y_{\text{RECT}} = \sqrt{Z^{-2} - (X_L^{-1} - X_C^{-1})^2} - (X_L^{-1} - X_C^{-1}) j$	① ② ④ ⑤ ⑥	Z X_L X_C

**Admittance
and Phase,
Parallel Circuits**

Y

$$Y_{\text{POLAR}} = Y / \pm \theta_Y$$

$$Y_{\text{RECT}} = G - (\pm B) j$$

Note: $G = R_p^{-1}$, $\pm B = (X_L)_p^{-1} - (X_C)_p^{-1}$ ④	Applicable Notes	Terms
$Y = (X_L^{-1} - X_C^{-1}) / (\sin \theta_Z) $ $Y_{\text{RECT}} = \left([X_L^{-1} - X_C^{-1}] / [\tan(\pm \theta_Z)] \right) - (X_L^{-1} - X_C^{-1}) j$	① ② ④ ⑤ ⑥ ⑧	θ_Z $X_C X_L$
$Y_{\text{RECT}} = [Y \cos \theta_Y] - [-Y \sin(\pm \theta_Y)] j$	① ② ⑤ ⑥	θ_Y Y
$Y = Z^{-1}, \quad \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm \theta_Z)] j$	① ② ④ ⑤ ⑥	Z θ_Z
$Y = I_t / E, \quad \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = [(I_t / E) \cos \theta_Z] - [(I_t / E) \sin(\pm \theta_Z)] j$	① ② ⑤ ⑥	θ_Z $E I$
$Y = P / (E^2 \cos \theta_Z), \quad \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = (P / E^2) - [(P / E^2) \tan(\pm \theta_Z)] j$	① ② ⑤ ⑥	θ_Z $E P$
$Y = (I_t^2 \cos \theta_Z) / P, \quad \pm \theta_Y = -(\pm \theta_Z)$ $Y_{\text{RECT}} = [(I_t \cos \theta_Z)^2 / P] - [Y \sin(\pm \theta_Z)] j$	① ② ⑤ ⑥	θ_Z $I_t P$



<p>Note: $\mathbf{Y_{RECT}} = G - (\pm B) j$ The sign of $(\pm B) j$ is real.</p>	<p>Terms</p>
<p>$(\mathbf{Y_{RECT}})_t = (\mathbf{Y_{RECT}})_1 + (\mathbf{Y_{RECT}})_2 \dots + (\mathbf{Y_{RECT}})_n$ $G_t = G_1 + G_2 \dots + G_n$ $\pm B_t = \pm B_1 \pm B_2 \dots \pm B_n$</p>	<p>$(\mathbf{Y_{RECT}})_1$ $(\mathbf{Y_{RECT}})_2$ $(\mathbf{Y_{RECT}})_n$</p>
<p>$\mathbf{Y_{RECT}}$ Procedure applies to any circuit in parallel with others.</p> <ol style="list-style-type: none"> Convert each series and each parallel circuit to polar impedance using applicable formulas. Convert each polar impedance to rectangular admittance from: $\mathbf{Y_{RECT}} = [\cos \theta_Z / Z] - [\sin(\pm \theta_Z) / Z] j$ The quantities inside the brackets represent G and $\pm B$. Maintain the sign of B inside brackets. Do not simplify to $\pm jB$. Algebraically sum all $\pm B$ quantities. Sum all G quantities. Convert to total polar impedance if desired from: $Z_t = [G_t^2 + (\pm B_t)^2]^{-\frac{1}{2}}$ $(\pm \theta_Z)_t = \tan^{-1} [(\pm B_t) / G_t]$ 	

**Conversions To
Rectangular
Admittance**

Y_{RECT}

Z_{POLAR} To Y_{RECT}

$$\mathbf{Z}_{\text{POLAR}} = Z/\pm\theta_Z, \quad \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$
$$\mathbf{Y}_{\text{RECT}} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm\theta_Z)] j$$

Z_{RECT} To Y_{RECT}

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j, \quad \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$
$$\mathbf{Y}_{\text{RECT}} = [R_s/(\pm X_s^2 + R_s^2)] - [\pm X_s/(\pm X_s^2 + R_s^2)] j$$

Series R and X To Y_{RECT}

$$R_s = \text{Series } R_t, \quad \pm X_s = \text{Series } (X_L - X_C)_t$$
$$\mathbf{Y}_{\text{RECT}} = [R_s/(\pm X_s^2 + R_s^2)] - [\pm X_s/(\pm X_s^2 + R_s^2)] j$$

Parallel R and X To Y_{RECT}

$$R_p = \text{Parallel } R_t, \quad \pm X_p = \text{Parallel } (X_L^{-1} - X_C^{-1})_t^{-1}$$
$$\mathbf{Y}_{\text{RECT}} = (R_p)_t^{-1} - (\pm X_p)_t^{-1} j \quad \text{Note } \textcircled{a}$$

Y_{POLAR} To Y_{RECT}

$$\mathbf{Y}_{\text{POLAR}} = Y/\pm\theta_Y, \quad \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$
$$\mathbf{Y}_{\text{RECT}} = [Y \cos \theta_Y] - [-Y \sin(\pm\theta_Y)] j$$

**Conversions
From
Rectangular
Admittance**

Y_{RECT}

Y_{RECT} To Z_{POLAR}

$$Y_{RECT} = G - (\pm B)j, \quad Z_{POLAR} = Z/\angle\theta_Z$$

$$Z_{POLAR} = [G^2 + (\pm B)^2]^{-\frac{1}{2}} / \angle \tan^{-1} [\pm B/G]$$

Y_{RECT} To Z_{RECT}

$$Y_{RECT} = G - (\pm B)j, \quad Z_{RECT} = R_s + (\pm X_s)j$$

$$Z_{RECT} = [G/(\pm B^2 + G^2)] + [\pm B/(\pm B^2 + G^2)]j$$

Y_{RECT} To Y_{POLAR}

$$Y_{RECT} = G - (\pm B)j, \quad Y_{POLAR} = Y/\angle\theta_Y$$

$$Y_{POLAR} = \sqrt{G^2 + (\pm B)^2} / \angle \tan^{-1} [-(\pm B/G)]$$

Y_{RECT} To Equiv. Series R and X

$$Y_{RECT} = G - (\pm B)j$$

$$R_s = G/(\pm B^2 + G^2), \quad \pm X_s = \pm B/(\pm B^2 + G^2)$$

$$|-X_s| = X_C, \quad |+X_s| = X_L$$

Y_{RECT} To Equiv. Parallel R and X

$$Y_{RECT} = G - (\pm B)j$$

$$R_p = G^{-1}, \quad \pm X_p = \pm B^{-1}$$

$$|-X_p| = X_C, \quad |+X_p| = X_C \quad \text{Note } \textcircled{a}$$

Y

ADMITTANCE Vector Algebra

Vector Algebra AC Ohms Law

$$\mathbf{E}_g = \mathbf{E}_g / 0^\circ \text{ or } \mathbf{I}_g = \mathbf{I}_g / 0^\circ \quad (1 = 1 / 0^\circ)$$

$$\mathbf{E} = \mathbf{I}_g / \mathbf{Y} = \mathbf{I}_g / \mathbf{Y} / 0^\circ - \theta_Y = -(\pm \theta_Y)$$

$$\mathbf{I} = \mathbf{E}_g \mathbf{Y} = \mathbf{E}_g \mathbf{Y} / 0^\circ + \theta_Y = \pm \theta_Y$$

$$\mathbf{Y} = 1 / \mathbf{Z} = 1 / \mathbf{Z} / 0^\circ - \theta_Z = -(\pm \theta_Z)$$

$$\mathbf{Y} = \mathbf{I} / \mathbf{E}_g = \mathbf{I} / \mathbf{E}_g / \theta_I - 0^\circ = \pm \theta_I$$

$$\mathbf{Y} = \mathbf{I}_g / \mathbf{E} = \mathbf{I}_g / \mathbf{E} / 0^\circ - \theta_E = -(\pm \theta_E)$$

$$\mathbf{Z} = 1 / \mathbf{Y} = 1 / \mathbf{Y} / 0^\circ - \theta_Y = -(\pm \theta_Y)$$

Addition and Subtraction of Rectangular Admittance

$$\mathbf{Y}_1 + \mathbf{Y}_2 = \mathbf{Y}_1(\text{RECT}) + \mathbf{Y}_2(\text{RECT})$$

$$= [\mathbf{G} - (\pm \mathbf{B})j]_1 + [\mathbf{G} - (\pm \mathbf{B})j]_2$$

$$= [\mathbf{G}_1 + \mathbf{G}_2] - [(\pm \mathbf{B}_1) + (\pm \mathbf{B}_2)]j$$

$$\mathbf{Y}_1 - \mathbf{Y}_2 = [\mathbf{G}_1 - \mathbf{G}_2] - [(\pm \mathbf{B}_1) - (\pm \mathbf{B}_2)]j$$

$$\mathbf{G}_t = (\mathbf{R}_p^{-1})_t$$




$$\pm \mathbf{B}_t = (\pm \mathbf{X}_p^{-1})_t$$

$$|-\mathbf{B}| = \mathbf{B}_C \quad |+\mathbf{B}| = \mathbf{B}_L$$

$$\mathbf{B}_C = (\mathbf{X}_C)_p^{-1} \quad \mathbf{B}_L = (\mathbf{X}_L)_p^{-1} \quad \text{Note } \textcircled{a}$$

See also—Z, Vector Algebra

See also—B, G, θ

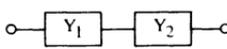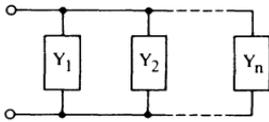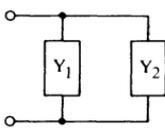ADMITTANCE Vector Algebra	Applicable Notes
<div style="text-align: center; font-size: 2em; font-weight: bold; margin-bottom: 10px;">Y</div> <div style="text-align: center; margin-bottom: 10px;">  </div> $Y_t = [Y_1^{-1} + Y_2^{-1} \dots + Y_n^{-1}]^{-1}$	Y_{VA} - ① - ②
<div style="text-align: center; margin-bottom: 10px;">  </div> $Y_2 = [Y_t^{-1} - Y_1^{-1}]^{-1}$	Y_{VA} - ① - ②
$Y_t = Y_1 + Y_2 \dots + Y_n$ <div style="text-align: center; margin-top: 10px;">  </div>	Y_{VA} - ① - ②
$Y_2 = Y_t - Y_1$ <div style="text-align: center; margin-top: 10px;">  </div>	Y_{VA} - ① - ②


Y_{VA} Notes:

- ① Admittance is a complex quantity requiring the mathematical operations of addition and subtraction to be performed in rectangular form. Rectangular form quantities may be multiplied like other binomials except that $j^2 = -1$. Reciprocals or other division by rectangular form quantities requires the divisor to be rationalized by multiplication of both the divisor and the dividend by the conjugate of the divisor. (The conjugate of $G - Bj$ is $G + Bj$). When using a calculator, it is easier to convert rectangular quantities to polar form for multiplication and division then reconvert to rectangular form for addition and subtraction.

ADMITTANCE
Vector Algebra

Y

Applicable
Notes

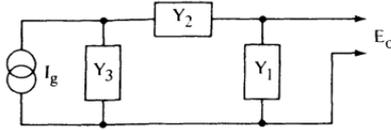


$$Y_i = Y_3 + (Y_2^{-1} + Y_1^{-1})^{-1}$$

$$Y_o = Y_1 + (Y_2^{-1} + Y_3^{-1})^{-1}$$

$$E_o = I_g [1 - (Y_3/Y_1)] / Y_1$$

Y_{VA}
- ①
- ②

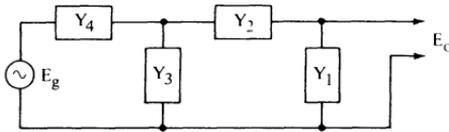

$$Y_i = Y_4^{-1} + [Y_3 + (Y_2^{-1} + Y_1^{-1})^{-1}]^{-1}$$

$$Y_o = Y_1 + [Y_2^{-1} + (Y_3 + Y_4)^{-1}]^{-1}$$

$$E_o = E_g [1 - (Y_1/Y_4)] / [(Y_1/Y_2) + 1]$$

Y_{VA}
- ①
- ②

Y_{VA} Notes:

- ② B_C or $-B$ = Capacitive Susceptance, B_L or $+B$ = Inductive Susceptance, E_g = Generator Voltage *, E_o = Output Voltage *, G = Conductance (Parallel Circuit Reciprocal Resistance), I_g = Generator Current *, I_o = Output Current *, R_p^{-1} = Parallel Circuit Reciprocal Resistance (Conductance), $\pm X_p^{-1}$ = Parallel Circuit Reciprocal Reactance (Susceptance), Y_i = Input Admittance *, Y_o = Output Admittance *, Z_i = Input Impedance *, Z_o = Output Impedance *, * = Vector (Phasor) characteristic.

Z

Impedance Definitions

Z = Symbol for impedance

Z = The total opposition to the flow of alternating current of a given frequency. A complex quantity having components of resistance and reactance. The ratio of applied alternating voltage to the alternating current flow through a circuit.

Z = Impedance expressed in ohm (Ω) units.

Z = $Z_{\text{MAGNITUDE}} = |Z|$

θ_Z = Phase angle of impedance

Z = Complete description of impedance which includes both magnitude and phase angle information.

Z_{POLAR} = Polar form of impedance = $Z/\pm\theta_Z$

Z_{POLAR} = The vectorial resultant of resistance (0°) and reactance ($\pm 90^\circ$).

Z_{RECT} = Rectangular form of impedance or the complex number form of impedance.

Z_{RECT} = The 0° (resistance) and $\pm 90^\circ$ (reactance) vectors in complex number form which have a resultant equal to polar impedance.

Z_{RECT} = The mathematical equivalent of resistance and reactance in series. (The series equivalent of a parallel circuit)

Z_{RECT} = $R \pm jX = R + (\pm X)j = R + (X_L - X_C)j$
where $|+X| = X_L$ and $|-X| = X_C$

$(\mathbf{Z}_{\text{RECT}})^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j = R_p^{-1} - (\pm X_p^{-1})j$

$(\mathbf{Z}_{\text{RECT}})^{-1}$ = A parallel equivalent circuit. See $-\mathbf{Y}_{\text{RECT}}$

Impedance, Series Circuits	Z	Applicable Notes	Terms
	$Z = \sqrt{R^2 + [(\omega L) - (\omega C)^{-1}]^2}$	① ④ ⑦	CL R
	$Z = [(\omega L) - (\omega C)^{-1}] / (\sin \theta_Z) $	① ② ③ ④ ⑦ ⑧	CL θ_Z
	$Z = E/I$	①	E I
	$Z = \sqrt{R^2 + (X_L - X_C)^2}$	① ③	R $X_C X_L$
	$Z = R / (\cos \theta_Z)$	① ② ③	R θ_Z
	$Z = (X_L - X_C) / (\sin \theta_Z) $	① ② ③ ⑧	$X_C X_L \theta_Z$
	$Z = \sqrt{E_R^2 + (E_L - E_C)^2} / I$	① ③	$E_R E_C E_L I$
	$Z = (E^2 \cos \theta_E) / P$	① ② ③	E P θ_E
	$Z = P / (I^2 \cos \theta_I)$	① ② ③	I P θ_I

Z Notes:

- ① B = Susceptance, C = Capacitance, E = rms Voltage, G = Conductance, I = rms Current, L = Inductance, P = Power, R = Resistance, X = Reactance, Y = Admittance, Z = Impedance, θ = Phase angle, ω = Angular velocity

Impedance, Parallel Circuits	Z	Applicable Notes	Terms
$Z = Y^{-1} = 1/Y$		① ④	Y
$Z = [G^2 + (B_L - B_C)^2]^{-\frac{1}{2}}$		① ③ ④	$B_C B_L G$
$Z = (\sin \theta_Y)/(B_L - B_C) $		① ② ③ ⑧	$B_C B_L \theta_Y$
$Z = (R^{-2} + [(\omega L)^{-1} - (\omega C)]^2)^{-\frac{1}{2}}$		① ④ ⑦	CL R
$Z = (\sin \theta_Z)/[(\omega L)^{-1} - (\omega C)] $		① ② ③ ④ ⑦ ⑧	CL θ_Z
$Z = E/I$		①	E I
$Z = (\cos \theta_Y)/G$		① ② ③	G θ_Y
$Z = [R^{-2} + (X_L^{-1} - X_C^{-1})^2]^{-\frac{1}{2}}$		① ③ ④	R $X_C X_L$
$Z = R \cos \theta_Z$		① ② ③	R θ_Z
$Z = (\sin \theta_Z)/(X_L^{-1} - X_C^{-1}) $		① ② ③ ④ ⑧	$X_C X_L \theta_Z$

Z Notes:

② cos = cosine, sin = sine, tan = tangent, \cos^{-1} = arc cosine, \sin^{-1} = arc sine, \tan^{-1} = arc tangent

Impedance and Phase, Single Elements	Z	Applicable Notes	Terms
$Z_{\text{POLAR}} = B_C^{-1} / \underline{-90^\circ} = -B^{-1} / \underline{-90^\circ}$ $Z_{\text{RECT}} = 0 + (-B^{-1})j$		① ③ ④ ⑤ ⑦	B_C or $-B$
$Z_{\text{POLAR}} = B_L^{-1} / \underline{+90^\circ} = +B^{-1} / \underline{+90^\circ}$ $Z_{\text{RECT}} = 0 + (+B^{-1})j$		① ③ ④ ⑤ ⑦	B_L or $+B$
$Z_{\text{POLAR}} = (\omega C)^{-1} / \underline{-90^\circ}$ $Z_{\text{RECT}} = 0 + (-\omega C)^{-1}j$		① ④ ⑦	C
$Z_{\text{POLAR}} = G^{-1} / \underline{0^\circ}$ $Z_{\text{RECT}} = G^{-1} + 0j$		① ④ ⑥ ⑦	G
$Z_{\text{POLAR}} = (\omega L) / \underline{+90^\circ}$ $Z_{\text{RECT}} = 0 + (+\omega L)j$		① ⑦	L
$Z_{\text{POLAR}} = R / \underline{0^\circ}$ $Z_{\text{RECT}} = R + 0j$		① ⑦	R
$Z_{\text{POLAR}} = X_C / \underline{-90^\circ} = -X / \underline{-90^\circ}$ $Z_{\text{RECT}} = 0 + (-X)j$		① ③ ⑦	X_C or $-X$
$Z_{\text{POLAR}} = X_L / \underline{+90^\circ} = +X / \underline{+90^\circ}$ $Z_{\text{RECT}} = 0 + (+X)j$		① ③ ⑦	X_L or $+X$

Z Notes:

- ③ Subscripts c = capacitive, E = voltage, I = current, L = inductive, n = any number, p = parallel circuit, s = series circuit, t = total or equivalent, Y = admittance, Z = impedance

Z/θ_Z Impedance, Series Circuits	Z POLAR	Applicable Notes	Terms
$Z = \sqrt{R^2 + [(\omega L) - (\omega C)^{-1}]^2}$ $\pm\theta_Z = \tan^{-1} \left([(\omega L) - (\omega C)^{-1}] / R \right)$		① ② ③ ④ ⑦ ⑧	CL R
$\pm\theta_Z = \sin^{-1} \left([(\omega L) - (\omega C)^{-1}] / Z \right)$		① ② ③ ④ ⑦ ⑧	CL Z
$Z = \left [(\omega L) - (\omega C)^{-1}] / (\sin \theta_Z) \right $		① ② ③ ④ ⑦ ⑧	CL θ_Z
$Z = \sqrt{R^2 + (X_L - X_C)^2}$ $\pm\theta_Z = \tan^{-1} [(X_L - X_C) / R]$		① ② ③ ⑧	R $X_C X_L$
$ \theta_Z = \tan^{-1} [\sqrt{Z^2 - R^2} / R]$		① ② ③ ④	R Z

Z Notes:

④ $x^{-1} = 1/x$, $x^{\frac{1}{2}} = \sqrt{x}$, $x^{-2} = 1/x^2$, $x^{-\frac{1}{2}} = 1/\sqrt{x}$, $|x| = x$ magnitude or the absolute value of x

⑤ Series resistance must equal zero.

⑥ Series reactance must equal zero.

⑦ $\omega = 2\pi f \approx 6.28f$ (f = frequency), $j = \sqrt{-1}$ = mathematical $i = 90^\circ$ multiplier = imaginary quantity = y axis quantity = reactive quantity

⑧ Reminders: $\pm\theta$ —Use the sign of the phase angle $\pm X$, $\pm B$ —treat the signs as real in all calculations except when converting to X_L , X_C , B_L or B_C .

The signs of $\pm X$ and $\pm B$ identify these reactive quantities as inductive or capacitive.

$|+X| = X_L$, $|-X| = X_C$, $|+B| = B_L$, $|-B| = B_C$

X_L , X_C , B_L and B_C are magnitudes, while $\pm X$ and $\pm B$ as used in formulas are “real” quantities.

Z/θ_Z Impedance, Series Circuits	Z POLAR	Applicable Notes	Terms
$Z = R/(\cos \theta_Z)$		① ② ③	R θ_Z
$\pm\theta_Z = \sin^{-1} [(X_L - X_C)/Z]$		① ② ③ ⑧	$X_C X_L Z$
$Z = (X_L - X_C)/(\sin \theta_Z) $		① ② ③ ⑧	$X_C X_L \theta_Z$
$Z = E/I$		① ③ ⑧ ⑨	E I θ_E
$\pm\theta_Z = \pm\theta_E$			
$Z = \sqrt{E_R^2 + (E_L - E_C)^2}/I$		① ② ③ ⑧	$E_C E_L E_R I$
$\pm\theta_Z = \tan^{-1} [(E_L - E_C)/E_R]$			
$Z = (E^2 \cos \theta_E)/P$		① ② ③ ⑧ ⑨	E P θ_E
$\pm\theta_Z = \pm\theta_E$			

Z Notes:

- ⑨ The phase angle of Z, Y, I and E ($\theta_Z, \theta_Y, \theta_I$ and θ_E) in a given circuit represent the same one and only one phase angle. $\pm\theta_Z = \pm\theta_E = -(\pm\theta_Y) = -(\pm\theta_I)$. The author does not recommend this use of θ_E and θ_I where each uses the other as the reference phase. The author uses the generator E_g or I_g as the reference. See also $-\theta$

Z/θ_Z Impedance, Parallel Circuits	Z POLAR	Applicable Notes	Terms
$Z = [G^2 + (B_L - B_C)^2]^{-\frac{1}{2}}$ $\pm\theta_Z = \tan^{-1} [(B_L - B_C)/G]$		① ② ③ ④ ⑧	$B_C B_L G$
$Z = Y^{-1}$ $\pm\theta_Z = \sin^{-1} [(B_L - B_C)/Y]$		① ② ③ ④ ⑧	$B_C B_L Y$
$Z = (\sin \theta_Y)/(B_L - B_C) $ $\pm\theta_Z = -(\pm\theta_Y)$		① ② ③ ④ ⑧ ⊗	$B_C B_L \theta_Y$
$Z = (R^{-2} + [(\omega L)^{-1} - (\omega C)]^2)^{-\frac{1}{2}}$ $\pm\theta_Z = \tan^{-1} (R [(\omega L)^{-1} - (\omega C)])$		① ② ③ ④ ⑦ ⑧	CL R
$\pm X_p = [(\omega L)^{-1} - (\omega C)]^{-1}$ $\pm\theta_Z = \sin^{-1} [Z/\pm X_p]$		① ② ③ ④ ⑦ ⑧ d	CL Z
$Z = (\sin \theta_Z)/[(\omega L)^{-1} - (\omega C)] $		① ② ③ ④ ⑦ ⊗	CL θ_Z
$Z = (\cos \theta_Y)/G$ $\pm\theta_Z = -(\pm\theta_Y)$		① ② ③ ⑧	G θ_Y

Z/θ_Z Impedance, Parallel Circuits	Z POLAR	Applicable Notes	Terms
$Z = R \cos \theta_Z$		① ② ③	R θ_Z
$Z = (\sin \theta_Z)/(X_L^{-1} - X_C^{-1}) $		① ② ③ ④ ⊗	$X_C X_L \theta_Z$
$Z = Y^{-1}$ $\pm \theta_Z = -(\pm \theta_Y)$		① ③ ④ ⑧	Y θ_Y
$Z = E/\sqrt{I_R^2 + (I_L - I_C)^2}$ $\pm \theta_Z = \tan^{-1} [(I_L - I_C)/I_R]$		① ② ③ ⑧ ⑨	E $I_R I_C I_L$
$Z = E/I$ $\pm \theta_Z = -(\pm \theta_I)$		① ③ ⑧ ⑨	E I θ_I

Z Notes:

- ④ Mathematics and calculators do not allow a division by zero or infinity. In formulas noted ③ however, the reciprocal of zero may be manually converted to infinity and the reciprocal of infinity may be manually converted to zero. The following additional manual operations may also be performed as required:

$$\begin{aligned}
 x \cdot \infty &= \infty \text{ when } x \neq 0, & x/\infty &= 0 \text{ when } x \neq \infty \\
 x \cdot 0 &= 0 \text{ when } x \neq \infty, & x/0 &= \infty \text{ when } x \neq 0 \\
 0^x &= 0 \text{ when } x \neq 0, & \infty^x &= \infty \text{ when } x \neq 0
 \end{aligned}$$

Calculators require the substitution of a very small number such as 10^{-30} for zero and of a very large number such as 10^{30} for infinity to perform these operations. All very small resultants must then be accepted as zero and all very large resultants must be accepted as infinity. Extreme care must be exercised to avoid accidental violation of the listed exceptions whenever more than one zero and/or infinity appear in the same formula. The arc tangent of infinity may be obtained from a calculator by also substituting a very large number for infinity.

- ⊗ Division by zero is prohibited. At circuit resonance, a zero divisor and a zero dividend will be presented. The division of zero by zero is always prohibited.

	Z
<p style="text-align: center;">Polar Impedances In Series</p> $Z_t = \left\{ \left([Z_1 \cos(\theta_{Z_1})] + [Z_2 \cos(\theta_{Z_2})] \cdots + [Z_n \cos(\theta_{Z_n})] \right)^2 \right. \\ \left. + \left([Z_1 \sin(\pm\theta_{Z_1})] + [Z_2 \sin(\pm\theta_{Z_2})] \cdots + [Z_n \sin(\pm\theta_{Z_n})] \right)^2 \right\}^{\frac{1}{2}}$ $\pm\theta_{Z_t} = \tan^{-1} \left[\frac{([Z_1 \sin(\pm\theta_{Z_1})] + [Z_2 \sin(\pm\theta_{Z_2})] \cdots + [Z_n \sin(\pm\theta_{Z_n})])}{([Z_1 \cos(\theta_{Z_1})] + [Z_2 \cos(\theta_{Z_2})] \cdots + [Z_n \cos(\theta_{Z_n})])} \right]$	Series Polar Impedances, Formula Method
<p style="text-align: center;">Unknown Series Impedance</p> $Z_x = \sqrt{([Z_t \cos(\theta_{Z_t})] - [Z_1 \cos(\theta_{Z_1})])^2 + ([Z_t \sin(\pm\theta_{Z_t})] - [Z_1 \sin(\pm\theta_{Z_1})])^2}$ $\pm\theta_{Z_x} = \tan^{-1} \left[\frac{([Z_t \sin(\pm\theta_{Z_t})] - [Z_1 \sin(\pm\theta_{Z_1})])}{([Z_t \cos(\theta_{Z_t})] - [Z_1 \cos(\theta_{Z_1})])} \right]$	

Polar Impedances in Parallel	Z	Parallel Polar Impedances, Formula Method
$Z_t = \left[\left([Z_1^{-1} \cos(\theta_{Z_1})] + [Z_2^{-1} \cos(\theta_{Z_2})] \cdots + [Z_n^{-1} \cos(\theta_{Z_n})] \right)^2 \right. \\ \left. + \left([Z_1^{-1} \sin(\pm\theta_{Z_1})] + [Z_2^{-1} \sin(\pm\theta_{Z_2})] \cdots + [Z_n^{-1} \sin(\pm\theta_{Z_n})] \right)^2 \right]^{-\frac{1}{2}}$ $\pm\theta_{Z_t} = \tan^{-1} \left[\frac{\left([Z_1^{-1} \sin(\pm\theta_{Z_1})] + [Z_2^{-1} \sin(\pm\theta_{Z_2})] \cdots + [Z_n^{-1} \sin(\pm\theta_{Z_n})] \right)}{\left([Z_1^{-1} \cos(\theta_{Z_1})] + [Z_2^{-1} \cos(\theta_{Z_2})] \cdots + [Z_n^{-1} \cos(\theta_{Z_n})] \right)} \right]$		
<p style="text-align: center;">Unknown Parallel Polar Impedance</p> $Z_x = \left[\left([Z_t^{-1} \cos(\theta_{Z_t})] - [Z_1^{-1} \cos(\theta_{Z_1})] \right)^2 + \left([Z_t^{-1} \sin(\pm\theta_{Z_t})] - [Z_1^{-1} \sin(\pm\theta_{Z_1})] \right)^2 \right]^{-\frac{1}{2}}$ $\pm\theta_{Z_x} = \tan^{-1} \left[\frac{\left([Z_t^{-1} \sin(\pm\theta_{Z_t})] - [Z_1^{-1} \sin(\pm\theta_{Z_1})] \right)}{\left([Z_t^{-1} \cos(\theta_{Z_t})] - [Z_1^{-1} \cos(\theta_{Z_1})] \right)} \right]$		

Z

Parallel Circuits In Series, Procedure Method

Procedure:

1. Convert each parallel circuit to polar form impedances using Z_{POLAR} , parallel circuit formulas.
2. Convert each polar impedance to equivalent series resistance and reactance from:

$$R_s = Z \cos \theta_Z \quad \pm X_s = Z \sin(\pm \theta_Z)$$

[If your calculator has the polar to rectangular conversion feature (P-R), enter Z_{POLAR} as the polar coordinates. The calculator x axis output is R_s and the calculator y axis output is $\pm X_s$]

3. Sum all R_s quantities and algebraically sum all $\pm X_s$ quantities.
[If your calculator has multiple memories, sum all R_s quantities into one memory and all $\pm X_s$ quantities into a second memory.]
4. Convert the total equivalent series resistance and the total equivalent series reactance to total polar impedance from:

$$Z_t = \sqrt{(R_s)_t^2 + (\pm X_s)_t^2}$$

$$(\pm \theta_Z)_t = \tan^{-1} [(\pm X_s)_t / (R_s)_t]$$

[If your calculator has the rectangular to polar conversion feature (R-P), enter $(R_s)_t$ as the x coordinate and $(\pm X_s)_t$ as the y coordinate. Calculator output will be polar impedance coordinates]

Z

Series Circuits In Parallel, Procedure Method

Procedure:

1. Convert each series circuit to polar form impedance using Z_{POLAR} , series circuit formulas.
2. Convert each polar impedance to equivalent parallel reciprocal resistance and equivalent parallel reciprocal reactance. [Note: parallel reciprocal resistance is also known as conductance (G) and parallel reciprocal reactance is also known as susceptance (B)]

$$R_p^{-1} = G = Z^{-1} \cos \theta_Z$$

$$\pm X_p^{-1} = \pm B = Z^{-1} \sin(\pm\theta_Z)$$

[If your calculator has the polar to rectangular conversion feature, enter Z^{-1} and $\pm\theta_Z$ as the polar coordinates. The calculator x coordinate output is R_p^{-1} or G and the calculator y coordinate output is $\pm X_p^{-1}$ or $\pm B$.]

3. Sum all R_p^{-1} (G) quantities and algebraically sum all $\pm X_p^{-1}$ ($\pm B$) quantities.

[If your calculator has multiple memories, sum all R_p^{-1} (G) quantities into one memory and sum all $\pm X_p^{-1}$ ($\pm B$) quantities into a second memory.]

4. Convert the total equivalent parallel reciprocal resistance [$(R_p^{-1})_t$ or G_t] and the total equivalent parallel reciprocal reactance [$(\pm X_p^{-1})_t$ or $\pm B_t$] to total polar impedance from:

$$Z_t = 1/\sqrt{G_t^2 + (\pm B_t)^2}$$

$$(\pm\theta_Z)_t = \tan^{-1}[\pm B_t/G_t]$$

[If your calculator has the rectangular to polar conversion feature (R-P), enter G_t as the x coordinate and $\pm B_t$ as the y coordinate. Calculator output will be $Z^{-1}(\pm\theta_Z)$. Convert the magnitude to Z with the 1/x key]

See also – Note ④

**Polar Impedance
Definitions and
Vector Algebra**

Z_{POLAR}

$$\mathbf{Z}_{\text{POLAR}} = Z / \pm\theta_Z$$

Z = Magnitude of impedance

$\pm\theta_Z$ = "Phase" angle of impedance

$\pm\theta_Z$ = The vectorial resultant angle when the magnitude of series resistance is placed at 0° , the magnitude of inductive reactance is placed at $+90^\circ$ and the magnitude of capacitive reactance is placed at -90° .

$\pm\theta_Z$ = That angle which has a tangent equal to the series reactance divided by the series resistance; the reactance having a positive sign if inductive and a negative sign if capacitive.

$\mathbf{Z}_{\text{POLAR}}$ = Impedance in a form where multiplication and division operations may be performed almost as easily as with ordinary numbers. (vector algebra)

$$(\mathbf{Z}_{\text{POLAR}})_1 \cdot (\mathbf{Z}_{\text{POLAR}})_2 = Z_1 Z_2 / (\pm\theta_Z)_1 + (\pm\theta_Z)_2$$

$$(\mathbf{Z}_{\text{POLAR}})_1 / (\mathbf{Z}_{\text{POLAR}})_2 = Z_1 / Z_2 / (\pm\theta_Z)_1 - (\pm\theta_Z)_2$$

$$\mathbf{E}_{\text{POLAR}} = \mathbf{I} (\mathbf{Z}_{\text{POLAR}}) = I Z / 0^\circ + (\pm\theta_Z)$$

$$\mathbf{I}_{\text{POLAR}} = \mathbf{E} / (\mathbf{Z}_{\text{POLAR}}) = E / Z / 0^\circ - (\pm\theta_Z)$$

$$\mathbf{Y}_{\text{POLAR}} = 1 / (\mathbf{Z}_{\text{POLAR}}) = 1 / Z / 0^\circ - (\pm\theta_Z)$$

$$\pm\theta_Z = \pm\theta_E = -(\pm\theta_I) = -(\pm\theta_Y)$$

$\mathbf{Z}_{\text{POLAR}}$ = The form used most often as the final resultant when simplifying complex circuits. It is equally "correct" however for the final resultant to be $\mathbf{Z}_{\text{RECT.}}$, $\mathbf{Y}_{\text{POLAR}}$ or $\mathbf{Y}_{\text{RECT.}}$. Both forms of \mathbf{Z} are series equivalent while both forms of \mathbf{Y} are parallel equivalent.

$$\mathbf{Z}_{\text{POLAR}} = \mathbf{Z}_{\text{RECT}} = [\mathbf{Y}_{\text{POLAR}}]^{-1} = [\mathbf{Y}_{\text{RECT}}]^{-1}$$

**Rectangular Impedance
Definitions, Sum
and Difference**

Z_{RECT}

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

R_s = Actual or equivalent total series resistance

$\pm X_s$ = Actual or equivalent net series reactance where:

$$|+X_s| = X_L \quad \text{and} \quad |-X_s| = X_C$$

$$\pm X_s = X_L - X_C$$

$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$ regardless of actual circuit configuration. The rectangular impedance of a parallel circuit represents the equivalent series circuit. (Note: Equivalent circuit values will vary with frequency.)

\mathbf{Z}_{RECT} = Impedance in a form where multiple impedances in series may be summed as easily as multiple resistances and multiple reactances in series. The series connected impedances may be any combination of individual series, parallel and unknown circuits.

$[\mathbf{Z}_{\text{RECT}}]_{\text{TOTAL}}$ = The sum of the resistive quantities and the algebraic sum of the reactive quantities.

\mathbf{Z}_{RECT} = The form necessary to perform any mathematical operation involving the addition or subtraction of impedances.

\mathbf{Z}_{RECT} = The form used by some for all mathematical operations and for the final resultant. (Not recommended. Use $\mathbf{Z}_{\text{POLAR}}$ for all multiplication and division and for the final resultant)

\mathbf{Z}_{RECT} may be converted (transformed) at any time to $\mathbf{Z}_{\text{POLAR}}$ or $[\mathbf{Z}_{\text{RECT}}]^{-1}$ using the appropriate formula.

$$([\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}})$$

$$\mathbf{Z}_{\text{RECT}} = \mathbf{Z}_{\text{POLAR}} = [\mathbf{Y}_{\text{POLAR}}]^{-1} = [\mathbf{Y}_{\text{RECT}}]^{-1}$$

Z_{RECT}

Rectangular Impedance Notes

1. This handbook contains no circuit elements to Z_{RECT} direct formulas. It is intended that all simple circuits should be converted to polar impedance and then converted as necessary to and from Z_{RECT} and $[Z_{RECT}]^{-1}$.
 2. The author apologizes to readers with good working knowledge of Y_{RECT} for the use of $[Z_{RECT}]^{-1}$, however Y_{RECT} is a necessary part of this section, $[Z_{RECT}]^{-1}$ fits the format better and many engineers as well as most technicians are very uncomfortable with Y_{RECT} .
 3. The use of $[Z_{POLAR}]^{-1}$ or Y_{POLAR} is not recommended. Do not confuse yourself or others by continually changing the signs of the angles. Convert directly from Z_{POLAR} to Y_{RECT} .
 4. Use the rectangular forms $R_s + (\pm X_s)j$ and $G - (\pm B)j$ as shown and do not simplify. The plus sign will identify the complex quantity as impedance or voltage and as a series equivalent quantity while the minus sign identifies the complex quantity as reciprocal impedance, admittance or current and also as a parallel equivalent quantity. Note also that in this form the sign of the reactive quantity within the parentheses is real and does not change during inversions. This maintains identification of the reactive quantity as inductive (+) or as capacitive (-) at all times.
 5. If any reader is uncomfortable with all rectangular quantities, direct conversion of series resistive and series reactive quantities to equivalent parallel reciprocal resistive and reciprocal reactive quantities is recommended. This conversion and its reverse allows the simplification of any series, parallel or series-parallel combination of impedances to a single impedance. This method is as fast as any other and there is less chance of error.
-

Reciprocal Rectangular Impedance Definitions, Sum and Difference $[Z_{RECT}]^{-1}$

$$[Z_{RECT}]^{-1} = [R_s + (\pm X_s)j]^{-1} = R_p^{-1} - (\pm X_p^{-1})j$$

The reciprocal of Z_{RECT} . (intrinsically a series or series equivalent quantity) is intrinsically a parallel or parallel equivalent quantity.

$$[Z_{RECT}]^{-1} = Y_{RECT} = \text{Rectangular admittance}$$

$$Y_{RECT} = G - (\pm B)j \quad \text{See also } -Y_{RECT}$$

G = Total parallel conductance or the equivalent parallel conductance

$\pm B$ = Total parallel susceptance or the equivalent parallel susceptance where:

$$|+B| = B_L, \quad |-B| = B_C$$

$$\pm B = B_L - B_C$$

$[Z_{RECT}]^{-1} = R_p^{-1} - (\pm X_p^{-1})j$ regardless of actual circuit configuration. The rectangular admittance of a series circuit represents the equivalent parallel circuit with the resistance and reactance in reciprocal form. (Note: Equiv. circuit values vary with freq.)

$[Z_{RECT}]^{-1}$ = Reciprocal impedance in a form where complex quantities in parallel may be simplified as easily as multiple resistances and multiple reactances in series. The complex quantities in parallel may represent any combination of individual series, parallel or unknown circuit configurations.

$[Z_{RECT}]_{TOTAL}^{-1}$ = The sum of the reciprocal resistances and the algebraic sum of the reciprocal reactances.

$[Z_{RECT}]^{-1}$ may be inverted back to rectangular or polar impedance at any time using the appropriate formula.

$$[Z_{RECT}]^{-1} = [Z_{POLAR}]^{-1} = Y_{RECT} = Y_{POLAR}$$

See also - Note @

Z_{RECT}

Rectangular Impedances In Series

$$[Z_{\text{RECT}}]_{\text{TOTAL}} = [Z_{\text{RECT}}]_1 + [Z_{\text{RECT}}]_2 \cdots + [Z_{\text{RECT}}]_n$$

Note: Rectangular impedance represents equivalent series resistance and reactance, however the actual circuit configuration may be series, parallel or unknown.

The first number in the rectangular impedance quantity is equivalent series resistance, the real part of impedance, the 0° component of impedance or the x axis coordinate of impedance.

The second number in the rectangular impedance quantity represents equivalent series reactance, the imaginary part of impedance, the $\pm 90^\circ$ component of impedance or the y axis coordinate of impedance.

When summing rectangular impedances, all resistive (R_s) components and all reactive ($\pm X_s$) components must be summed separately. The reactive components ($\pm X_s$) must also be summed algebraically. (Use the rectangular form $R_s + (\pm X_s)j$ not $R_s \pm jX_s$)

$$[Z_{\text{RECT}}]_1 = (R_s)_1 + (\pm X_s)_1 j$$

$$[Z_{\text{RECT}}]_2 = (R_s)_2 + (\pm X_s)_2 j$$

$$[Z_{\text{RECT}}]_n = (R_s)_n + (\pm X_s)_n j$$

$$[Z_{\text{RECT}}]_{\text{TOTAL}} = (R_s)_{\text{TOTAL}} + (\pm X_s)_{\text{TOTAL}} j$$

Note: $Z_{\text{POLAR}} = \sqrt{(R_s)_t^2 + (\pm X_s)_t^2} / \tan^{-1} [(\pm X_s)_t / (R_s)_t]$

$$Z_{\text{RECT}} = [Z \cos \theta_Z] + [Z \sin(\pm \theta_Z)] j$$

[Z_{RECT}]⁻¹

Reciprocal
Rectangular
Impedances
In Parallel

$$[\mathbf{Z}_{\text{RECT}}]_t^{-1} = [\mathbf{Z}_{\text{RECT}}]_1^{-1} + [\mathbf{Z}_{\text{RECT}}]_2^{-1} \cdots + [\mathbf{Z}_{\text{RECT}}]_n^{-1}$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}}$$

$$[\mathbf{Y}_{\text{RECT}}]_t = [\mathbf{Y}_{\text{RECT}}]_1 + [\mathbf{Y}_{\text{RECT}}]_2 \cdots + [\mathbf{Y}_{\text{RECT}}]_n$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = R_p^{-1} - (\pm X_p^{-1})j$$

$$\mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$G = R_p^{-1}, \quad \pm B = \pm X_p^{-1}$$

$$[\mathbf{Z}_{\text{RECT}}]_1^{-1} = (R_p^{-1})_1 \quad - (\pm X_p^{-1})_1 \quad j$$

$$[\mathbf{Z}_{\text{RECT}}]_2^{-1} = (R_p^{-1})_2 \quad - (\pm X_p^{-1})_2 \quad j$$

$$[\mathbf{Z}_{\text{RECT}}]_n^{-1} = (R_p^{-1})_n \quad - (\pm X_p^{-1})_n \quad j$$

$$[\mathbf{Z}_{\text{RECT}}]_{\text{TOTAL}}^{-1} = (R_p^{-1})_{\text{TOTAL}} - (\pm X_p^{-1})_{\text{TOTAL}} j$$

$$[\mathbf{Y}_{\text{RECT}}]_1 = G_1 \quad - (\pm B_1) \quad j$$

$$[\mathbf{Y}_{\text{RECT}}]_2 = G_2 \quad - (\pm B_2) \quad j$$

$$[\mathbf{Y}_{\text{RECT}}]_n = G_n \quad - (\pm B_n) \quad j$$

$$[\mathbf{Y}_{\text{RECT}}]_{\text{TOTAL}} = G_{\text{TOTAL}} - (\pm B)_{\text{TOTAL}} j$$

Note: $\mathbf{Z}_{\text{POLAR}} = [G_t^2 + (\pm B_t)^2]^{-\frac{1}{2}} / \tan^{-1} [\pm B_t / G_t]$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm \theta_Z)] j$$

See also – Note ④

Conversions From
Polar Impedance

Z_{POLAR}

Conversions

Z_{POLAR} To Z_{RECT}

$$Z_{RECT} = [Z \cos \theta_Z] + [Z \sin(\pm\theta_Z)] j$$

Z_{POLAR} To Y_{RECT} or [Z_{RECT}]⁻¹

$$Y_{RECT} = G - (\pm B)j = R_p^{-1} - (\pm X_p^{-1})j$$

$$Y_{RECT} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm\theta_Z)] j$$

$$[Z_{RECT}]^{-1} = Y_{RECT}$$

Z_{POLAR} To Y_{POLAR}

$$Y_{POLAR} = Z^{-1} / \angle(\pm\theta_Z)$$

Z_{POLAR} To Series R and X

$$R_s = Z \cos \theta_Z \quad \pm X_s = Z \sin(\pm\theta_Z)$$

$$|+X_s| = X_L \quad |-X_s| = X_C$$

Z_{POLAR} To Parallel R and X

$$R_p = Z / (\cos \theta_Z) \quad \pm X_p = Z / [\sin(\pm\theta_Z)]$$

$$|+X_p| = X_L \quad |-X_p| = X_C$$

See also – Note ④

Conversion To
Polar Impedance

Z_{POLAR}

Conversions

Equiv. Series R and X To Z_{POLAR}

$$Z = \sqrt{R_s^2 + (\pm X_s)^2}$$

$$\pm\theta_Z = \tan^{-1} [\pm X_s/R_s]$$

Equiv. Parallel R and X To Z_{POLAR}

$$Z = [R_p^{-2} + (\pm X_p)^{-2}]^{-\frac{1}{2}}$$

$$\pm\theta_Z = \tan^{-1} [R_p/\pm X_p]$$

Z_{RECT} To Z_{POLAR}

$$Z_{RECT} = R_s + (\pm X_s)j$$

$$Z = \sqrt{R_s^2 + (\pm X_s)^2}$$

$$\pm\theta_Z = \tan^{-1} [\pm X_s/R_s]$$

[Z_{RECT}]⁻¹ or Y_{RECT} To Z_{POLAR}

$$[Z_{RECT}]^{-1} = Y_{RECT} = G - (\pm B)j$$

$$= R_p^{-1} - (\pm X_p^{-1})j$$

$$Z = [G^2 + (\pm B)^2]^{-\frac{1}{2}}$$

$$\pm\theta_Z = \tan^{-1} [\pm B/G]$$

See also – Note ④

Conversions From
Rectangular
Impedance

Z_{RECT}

Conversions

Z_{RECT} To **Z**_{POLAR}

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

$$\mathbf{Z}_{\text{POLAR}} = \sqrt{R_s^2 + (\pm X_s)^2} / \tan^{-1} [\pm X_s/R_s]$$

Z_{RECT} To **Y**_{POLAR}

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

$$\mathbf{Y}_{\text{POLAR}} = [R_s^2 + (\pm X_s)^2]^{-\frac{1}{2}} / \tan^{-1} [-(\pm X_s/R_s)]$$

Z_{RECT} To **Y**_{RECT} or [**Z**_{RECT}]⁻¹

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

$$\mathbf{Y}_{\text{RECT}} = G - (\pm B)j = [\mathbf{Z}_{\text{RECT}}]^{-1} = R_p^{-1} - (\pm X_p^{-1})j$$

$$\mathbf{Y}_{\text{RECT}} = [R_s/(\pm X_s^2 + R_s^2)] - [\pm X_s/(\pm X_s^2 + R_s^2)]j$$

Z_{RECT} To Equiv. Parallel R and X

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

$$R_p = (\pm X_s^2 + R_s^2)/R_s$$

$$\pm X_p = (\pm X_s^2 + R_s^2)/\pm X_s$$

$$|+X_p| = X_L \quad |-X_p| = X_C$$

See also – Note ④

**Conversions To
Rectangular
Impedance**

Z_{RECT}

Conversions

Z_{POLAR} To Z_{RECT}

$$Z_{\text{POLAR}} = Z / \pm \theta_Z$$

$$Z_{\text{RECT}} = [Z \cos \theta_Z] + [Z \sin(\pm \theta_Z)] j$$

Y_{POLAR} To Z_{RECT}

$$Y_{\text{POLAR}} = Y / \pm \theta_Y$$

$$Z_{\text{RECT}} = [Y^{-1} \cos \theta_Y] + [-Y^{-1} \sin(\pm \theta_Y)] j$$

Y_{RECT} OR [Z_{RECT}]⁻¹ To Z_{RECT}

$$Y_{\text{RECT}} = G - (\pm B) j$$

$$Z_{\text{RECT}} = [G/(\pm B^2 + G^2)] + [\pm B/(\pm B^2 + G^2)] j$$

Series R and X To Z_{RECT}

$$Z_{\text{RECT}} = R_s + (\pm X_s) j$$

Parallel R and X To Z_{RECT}

$$Z_{\text{RECT}} = [(R_p/\pm X_p^2) + R_p^{-1}]^{-1} + [(\pm X_p/R_p^2) + (\pm X_p^{-1})]^{-1} j$$

G and B to Z_{RECT}

$$Z_{\text{RECT}} = [G/(\pm B^2 + G^2)] + [\pm B/(\pm B^2 + G^2)] j$$

See also – Note ④

Conversion From
Reciprocal
Rectangular
Impedance

$$[\mathbf{Z}_{\text{RECT}}]^{-1}$$

$[\mathbf{Z}_{\text{RECT}}]^{-1}$ or \mathbf{Y}_{RECT} To $\mathbf{Z}_{\text{POLAR}}$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$\mathbf{Z}_{\text{POLAR}} = [G^2 + (\pm B)^2]^{-\frac{1}{2}} / \tan^{-1} [\pm B/G]$$

$[\mathbf{Z}_{\text{RECT}}]^{-1}$ or \mathbf{Y}_{RECT} To \mathbf{Z}_{RECT}

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$\mathbf{Z}_{\text{RECT}} = [G/(\pm B^2 + G^2)] + [\pm B/(\pm B^2 + G^2)]j$$

$[\mathbf{Z}_{\text{RECT}}]^{-1}$ or \mathbf{Y}_{RECT} To $\mathbf{Y}_{\text{POLAR}}$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$\mathbf{Y}_{\text{POLAR}} = \sqrt{G^2 + (\pm B)^2} / \tan^{-1} [-(\pm B/G)]$$

$[\mathbf{Z}_{\text{RECT}}]^{-1}$ or \mathbf{Y}_{RECT} To Equiv. Series R and X

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$R_s = G/(\pm B^2 + G^2) \quad \pm X_s = \pm B/(\pm B^2 + G^2)$$

$[\mathbf{Z}_{\text{RECT}}]^{-1}$ or \mathbf{Y}_{RECT} To Equiv. Parallel R and X

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$R_p = G^{-1} \quad \pm X_p = \pm B^{-1}$$

See also – Note ③

**Conversions To
Reciprocal
Rectangular
Impedance**

$$[\mathbf{Z}_{\text{RECT}}]^{-1}$$

Z_{POLAR} To Y_{RECT} or [Z_{RECT}]⁻¹

$$\mathbf{Z}_{\text{POLAR}} = Z / \pm \theta_Z$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = [Z^{-1} \cos \theta_Z] - [Z^{-1} \sin(\pm \theta_Z)]j$$

Z_{RECT} To Y_{RECT} or [Z_{RECT}]⁻¹

$$\mathbf{Z}_{\text{RECT}} = R_s + (\pm X_s)j$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = [R_s / (\pm X_s^2 + R_s^2)] - [\pm X_s / (\pm X_s^2 + R_s^2)]j$$

Series R and X To Y_{RECT} or [Z_{RECT}]⁻¹

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = \mathbf{Y}_{\text{RECT}} = G - (\pm B)j$$

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = [R_s / (\pm X_s^2 + R_s^2)] - [\pm X_s / (\pm X_s^2 + R_s^2)]j$$

Parallel R and X To Y_{RECT} or [Z_{RECT}]⁻¹

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = R_p^{-1} - (\pm X_p^{-1})j$$

Y_{POLAR} To Y_{RECT} or [Z_{RECT}]⁻¹

$$[\mathbf{Z}_{\text{RECT}}]^{-1} = [Y \cos \theta_Y] - [-Y \sin(\pm \theta_Y)]j$$

See also – Note @

Z

Impedance, Vector Algebra Rules

Rules of Vector Algebra

$$\mathbf{Z}_1 \cdot \mathbf{Z}_2 = \mathbf{Z}_1 \mathbf{Z}_2 / (\pm\theta_{\mathbf{Z}})_1 + (\pm\theta_{\mathbf{Z}})_2$$

$$\mathbf{Z}_1 / \mathbf{Z}_2 = \mathbf{Z}_1 / \mathbf{Z}_2 / (\pm\theta_{\mathbf{Z}})_1 - (\pm\theta_{\mathbf{Z}})_2$$

$$(+1) \cdot \mathbf{Z} = \mathbf{Z} / 0^\circ + (\pm\theta_{\mathbf{Z}}) = \pm\theta_{\mathbf{Z}}$$

$$(+1) / \mathbf{Z} = 1 / \mathbf{Z} / 0^\circ - (\pm\theta_{\mathbf{Z}}) = -(\pm\theta_{\mathbf{Z}})$$

$$\mathbf{Z}_1 + \mathbf{Z}_2 = [\mathbf{Z}_{\text{RECT}}]_1 + [\mathbf{Z}_{\text{RECT}}]_2$$

$$\mathbf{Z}_1 + \mathbf{Z}_2 = [\mathbf{R}_s + (\pm X_s)j]_1 + [\mathbf{R}_s + (\pm X_s)j]_2$$

$$\mathbf{Z}_1 + \mathbf{Z}_2 = [(\mathbf{R}_s)_1 + (\mathbf{R}_s)_2] + [(\pm X_s)_1 + (\pm X_s)_2]j$$

$$\mathbf{Z}_1 - \mathbf{Z}_2 = [(\mathbf{R}_s)_1 - (\mathbf{R}_s)_2] + [(\pm X_s)_1 - (\pm X_s)_2]j$$

$$\mathbf{Z} + (+1) = [\mathbf{R}_s + 1] + [\pm X_s]j$$

$$\mathbf{Z} - (+1) = [\mathbf{R}_s - 1] + [\pm X_s]j$$

$$\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1} = [\mathbf{Z}_{\text{RECT}}]_1^{-1} + [\mathbf{Z}_{\text{RECT}}]_2^{-1}$$

$$\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1} = [\mathbf{Y}_{\text{RECT}}]_1 + [\mathbf{Y}_{\text{RECT}}]_2$$

$$\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1} = [\mathbf{G} - (\pm B)j]_1 + [\mathbf{G} - (\pm B)j]_2$$




$$\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1} = [\mathbf{G}_1 + \mathbf{G}_2] - [(\pm B)_1 + (\pm B)_2]j$$

$$\mathbf{Z}_1^{-1} - \mathbf{Z}_2^{-1} = [\mathbf{G}_1 - \mathbf{G}_2] - [(\pm B)_1 - (\pm B)_2]j$$

$$\mathbf{Z}^{-1} + (+1) = [\mathbf{G} + 1] - [\pm B]j$$




$$\mathbf{Z}^{-1} - (+1) = [\mathbf{G} - 1] - [\pm B]j$$

See—Z Conversion Formulas

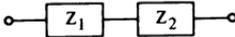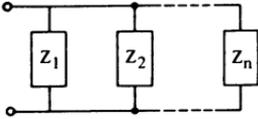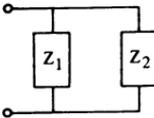IMPEDANCE Vector Algebra	Z	Applicable Notes
$\mathbf{Z}_t = \mathbf{Z}_1 + \mathbf{Z}_2 + \dots + \mathbf{Z}_n$		VA-1 VA-2 VA-3 VA-5
$\mathbf{Z}_2 = \mathbf{Z}_t - \mathbf{Z}_1$		VA-1 VA-2 VA-3 VA-5
$\mathbf{Z}_t = [\mathbf{Z}_1^{-1} + \mathbf{Z}_2^{-1} + \dots + \mathbf{Z}_n^{-1}]^{-1}$ $\mathbf{Y}_t = \mathbf{Y}_1 + \mathbf{Y}_2 + \dots + \mathbf{Y}_n$		VA-1 VA-2 VA-3 VA-4 VA-5
$\mathbf{Z}_2 = [\mathbf{Z}_t^{-1} - \mathbf{Z}_1^{-1}]^{-1}$ $\mathbf{Y}_2 = \mathbf{Y}_t - \mathbf{Y}_1$		VA-1 VA-2 VA-3 VA-4 VA-5

Z Notes:


VA-1 Impedance is a complex quantity requiring the mathematical operation of addition and subtraction to be performed in rectangular form while multiplication and division operations are usually performed in polar form by treating the phase angle as an exponent. Impedances in rectangular form may be multiplied like other binomials, division however requires the divisor to be rationalized by multiplying the divisor and the dividend by the conjugate of the divisor (the conjugate of $R_s + X_sj = R_s - X_sj$). To eliminate this lengthy calculation, it is recommended that all multiplication and division be performed in polar form.

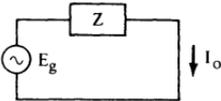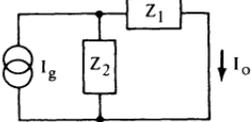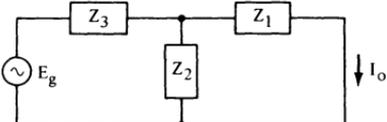Input IMPEDANCE Vector Algebra	Z_i etc.	Applicable Notes
$E_g = E_g / 0^\circ$ $Z_i = Z$ $I_o = E_g / Z$		VA-1 VA-2 VA-3 VA-5
$I_g = I_g / 0^\circ$ $Z_i = [Z_1^{-1} + Z_2^{-1}]^{-1}$ $E_g = I_g Z_i$ $I_o = (I_g Z_i) / Z_1$		VA-1 VA-2 VA-3 VA-4 VA-5
$E_g = E / 0^\circ$ $Z_i = Z_3 + [Z_2^{-1} + Z_1^{-1}]^{-1}$ $I_g = E_g / Z_i$ $I_o = E_g / (Z_i [(Z_1 / Z_2) + 1])$		VA-1 VA-2 VA-3 VA-4 VA-5
Z Notes:		
VA-2 E_g = Generator voltage I_g = Generator current Y_o = Output admittance Z_i = Input impedance Z_t = Total or Equivalent impedance	E_o = Output voltage I_o = Output current Y_t = Total admittance Z_o = Output impedance	

Input
IMPEDANCE
Vector
Algebra

Z_i etc.

Applicable
Notes

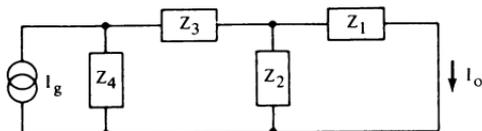


$$I_g = I_g \angle 0^\circ$$

$$Z_i = \left(Z_4^{-1} + [Z_3 + (Z_2^{-1} + Z_1^{-1})^{-1}]^{-1} \right)^{-1}$$

$$E_g = I_g Z_i$$

$$I_o = I_g \left[1 - (Z_i/Z_4) \right] / [(Z_1/Z_2) + 1]$$

VA-1
VA-2
VA-3
VA-4
VA-5

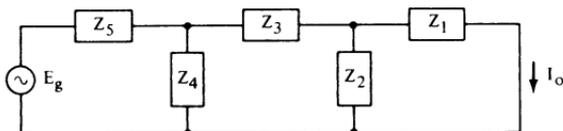

$$E_g = E \angle 0^\circ$$

$$Z_i = Z_5 + \left(Z_4^{-1} + [Z_3 + (Z_2^{-1} + Z_1^{-1})^{-1}]^{-1} \right)^{-1}$$

$$I_g = E_g/Z_i$$

$$I_o = I_g \left(1 - [(Z_i - Z_5)/Z_4] \right) / [(Z_1/Z_2) + 1]$$

VA-1
VA-2
VA-3
VA-4
VA-5

Z Notes:

VA-3 Impedances Z , Z_1 , Z_2 , Z_3 , Z_4 and Z_5 may represent any resistance, reactance, series circuit, parallel circuit, unknown circuit or any circuit regardless of complexity or configuration.

VA-4 $Z^{-1} = 1/Z = Y$, $Y^{-1} = 1/Y = Z$

VA-5 Z , Z_i , Z_o , Y , Y_o , I_o and E_o all will vary with frequency except purely resistive circuits.

IMPEDANCE
Vector
Algebra

Z_i Z_o etc.


Applicable
Notes

$$I_g = I_g \angle 0^\circ$$

$$Z_i = Z$$

$$Z_o = Z$$

$$E_o = I_g Z$$

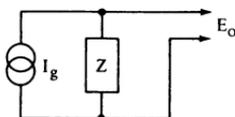

VA-1
VA-2
VA-3
VA-5


$$E_g = E_g \angle 0^\circ$$

$$Z_i = Z_1 + Z_2$$

$$Z_o = [Z_1^{-1} + Z_2^{-1}]^{-1}$$

$$Y_o = Y_1 + Y_2$$

$$E_o = (E_g Z_1) / Z_i$$

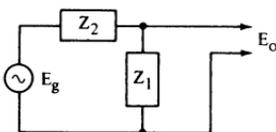

VA-1
VA-2
VA-3
VA-4
VA-5

$$I_g = I_g \angle 0^\circ$$


$$Z_i = [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1}$$

$$Z_o = [Z_1^{-1} + (Z_2 + Z_3)^{-1}]^{-1}$$

$$Y_o = Y_1 + (Y_2^{-1} + Y_3^{-1})^{-1}$$

$$E_g = I_g Z_i$$

$$E_o = I_g Z_1 [1 - (Z_i / Z_3)]$$

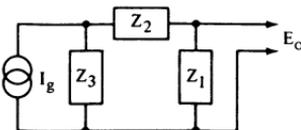


VA-1
VA-2
VA-3
VA-4
VA-5

IMPEDANCE
Vector
Algebra

Z_i Z_o etc.

Applicable
Notes

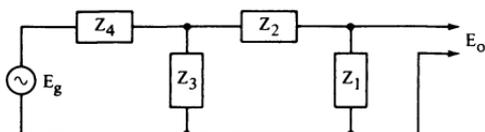

$$E_g = E_g \angle 0^\circ$$

$$Z_i = Z_4 + [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1}$$

$$Z_o = (Z_1^{-1} + [Z_2 + (Z_3^{-1} + Z_4^{-1})^{-1}]^{-1})^{-1}$$

$$Y_o = Y_1 + [Y_2^{-1} + (Y_3 + Y_4)^{-1}]^{-1}$$

$$I_g = E_g / Z_i$$

$$E_o = E_g [1 - (Z_4 / Z_i)] / [(Z_2 / Z_1) + 1]$$


VA-1

VA-2

VA-3

VA-4

VA-5

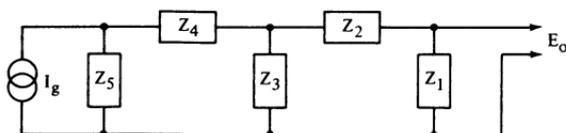

$$I_g = I_g \angle 0^\circ$$

$$E_g = I_g Z_i$$

$$Z_i = [Z_5^{-1} + (Z_4 + [Z_3^{-1} + (Z_2 + Z_1)^{-1}]^{-1})^{-1}]^{-1}$$

$$Z_o = [Z_1^{-1} + (Z_2 + [Z_3^{-1} + (Z_4 + Z_5)^{-1}]^{-1})^{-1}]^{-1}$$

$$Y_o = Y_1 + (Y_2^{-1} + [Y_3 + (Y_4^{-1} + Y_5^{-1})^{-1}]^{-1})^{-1}$$

$$E_o = [I_g (Z_i - Z_4)] / [(Z_2 / Z_1) + 1]$$

VA-1

VA-2

VA-3

VA-4

VA-5

Z

IMPEDANCE Δ to Y Conversion



Delta (Δ) to Wye (Y) or Reverse Conversion

Pi (π) section to Tee (T) section or reverse

Transformation

Δ or π section

Y or T section

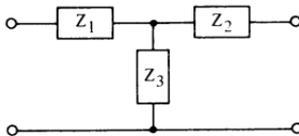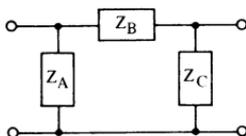

$$Z_1 = (Z_A Z_B) / [Z_A + Z_B + Z_C]$$

$$Z_2 = (Z_B Z_C) / [Z_A + Z_B + Z_C]$$

$$Z_3 = (Z_A Z_C) / [Z_A + Z_B + Z_C]$$

$$Z_A = [(Z_1 Z_2) + (Z_2 Z_3) + (Z_1 Z_3)] / Z_2$$

$$Z_B = [(Z_1 Z_2) + (Z_2 Z_3) + (Z_1 Z_3)] / Z_3$$

$$Z_C = [(Z_1 Z_2) + (Z_2 Z_3) + (Z_1 Z_3)] / Z_1$$

Page Notes:

1. Technically, delta and wye diagrams should be drawn with only three terminals.
 2. Convert all impedances and intermediate solutions to both polar and rectangular form. Perform all addition in rectangular form. Perform all multiplication and division in polar form.
-

PASSIVE CIRCUITS

SECTION 1.2 GREEK LETTERS

α to ω

Greek Alphabet

Spelling and Pronunciation	Small (Script)	Large (Capital)	Spelling and Pronunciation	Small (Script)	Large (Capital)
alpha (al'fa)	α	A	nu (nū)	ν	N
beta (bā'ta)	β	B	xi (zī)	ξ	Ξ
gamma (gam'a)	γ	Γ	omicron (om'i kron' ō'mi kron')	ο	Ο
delta (del'ta)	δ	Δ	pi (pī)	π	Π
epsilon (ep'sa lon')	ε	E	rho (rō)	ρ	Ρ
zeta (zā'ta)	ζ	Z	sigma (sig'ma)	σ s	Σ
eta (ā'ta)	η	H	tau (tou or taw) (ou as in out)	τ	T
theta (thā'ta)	θ	Θ	upsilon (up'sa lon')	υ	Υ
iota (i ō' ta)	ι	I	phi (fī or fē)	φ	Φ
kappa (kap'a)	κ	K	chi (kī)	χ	X
lambda (lam'da)	λ	Λ	psi (sī)	ψ	Ψ
mu (mū)	μ	M	omega (ō meg'a ō mē'ga)	ω	Ω

Note: For obvious reasons, capital Greek letters A B E Z H I K M N O P T X are not used as electronic symbols.

α to η

Greek
Letters

α = Symbol for many different passive circuit quantities but no standardization has been achieved. See also—Active Circuits

β = Symbol for many different passive circuit quantities but no standardization has been achieved. See also—Active Circuits

γ = Symbol seldom used in electronics. Used for conductivity (G) in other fields.

δ = Symbol for loss angle.

δ = Ninety degrees minus the absolute value of the phase angle.

$$\delta = 90^\circ - |\theta|$$

$$\delta = \tan^{-1} D$$

Note: The dissipation factor (D) of capacitors is specified by most USA manufacturers but the loss angle (δ) or the tangent of the loss angle ($\tan \delta$) is specified by most foreign manufacturers.

Δ = Symbol for increment or decrement. (Still used for vacuum tubes, but small signal parameters such as h_{fe} are used for semiconductors.)

ϵ = Symbol for the base of natural logarithms.

$$\epsilon = 2.718281828 \dots \quad \epsilon^{-1} = .3678794412 \dots$$

ζ = Seldom used and no standardization of meaning.

η = Efficiency. See also—Active Circuits

θ

Phase Angle Definitions

θ = Symbol for phase angle.

Note: Phi (ϕ) and other greek letters are also used as symbols for phase angle.

- θ = 1. The angular difference in phase between a quantity and a reference.
2. The phase angle of voltage, current, impedance or admittance with respect to a reference.
 3. The phase angle of voltage, current, impedance or admittance with respect to the phase angle of current, voltage, resistance or conductance.
 4. The phase angle of voltage or impedance with respect to the phase angle of total current or with respect to 0° .
 5. The phase angle of current or admittance with respect to the phase angle of total voltage or with respect to 0° .

θ = Phase angle measured and expressed in:

1. Decimal degrees
 $360^\circ =$ one cycle or one revolution
2. Degrees, minutes, seconds
 $1^\circ = 60'$ (minutes)
 $1' = 60''$ (seconds)
3. Radians
 2π radians = one cycle or one revolution
4. Grads
400 grads = one cycle or one revolution

$\theta = 0^\circ$ when voltage and current are in phase. 0° when circuit is or acts as a pure resistance or conductance.

$\theta = \pm 90^\circ$ when circuit is or acts as a pure reactance or susceptance.

$\theta = +90^\circ$ to -90° for all two terminal networks when θ is angle of total voltage, total current, total impedance or total admittance.

θ

Phase Angle Definitions

$+\theta$ = Leading phase angle. Counterclockwise rotation of a vector. Earlier in time than 0° .

$-\theta$ = Lagging phase angle. Clockwise rotation of a vector. Later in time than 0° .

$\theta_E = 1$. The difference in phase between the total voltage and the total current when the phase angle of the total current is placed at 0° .

2. The angular difference in phase between the total voltage and the current source. ($I_g = I_g \angle 0^\circ = +I_g$ unless noted)

θ_{E_O} = Output voltage phase with respect to the phase of the voltage or current input. (Voltage or current generator E_g or $I_g = 0^\circ$)

$\theta_I = 1$. The angular difference in phase between the total current and the total voltage when the phase angle of the total voltage is placed at 0° .

2. The angular difference in phase between the total current and the voltage source. ($E_g = E_g \angle 0^\circ = +E_g$ unless noted)

θ_{I_O} = Output current phase with respect to the phase of the voltage or current input. (Input phase = 0° unless noted)

Page Note: The phase angles of **E** and **I** may be confusing. To prevent confusion, always calculate polar impedance first and then assign zero degrees to the signal source. If the signal source is a voltage generator, $\theta_I = -\theta_Z$ and if the signal source is a current generator, $\theta_E = \theta_Z$. Use vector algebra to determine the phase angles of circuit voltages and/or currents. e.g., when a voltage source is connected to a series circuit, $\theta_I = -\theta_Z$, $\theta_{E_R} = \theta_I$, $\theta_{E_L} = \theta_I + 90^\circ$, $\theta_{E_C} = \theta_I - 90^\circ$, $\theta_{E_t} = 0^\circ$.

θ

Phase Angle Definitions

$\theta_Y = 1$. The angular difference between the admittance and the conductance of a circuit. (The angle of conductance $G = 0^\circ$)

2. The same angle as impedance except with opposite sign.

3. The same angle as the phase angle of the total current when the phase angle of total voltage is placed at 0° .

$\theta_Z = 1$. The angular difference between the impedance and the resistance of a circuit. (The angle of resistance $R = 0^\circ$)

2. The same angle as the admittance except with opposite sign.

3. The same angle as the phase angle of the total voltage when the phase angle of total current is placed at 0° .

$\pm\theta_E = -(\pm\theta_I)$ but both may not coexist.

$\pm\theta_I = -(\pm\theta_E)$ but both may not coexist.

$\pm\theta_Y = -(\pm\theta_Z)$ [$Y/\pm\theta_Y = Z^{-1}/-(\pm\theta_Z)$]

$\pm\theta_Z = -(\pm\theta_Y)$ [$Z/\pm\theta_Z = Y^{-1}/-(\pm\theta_Y)$]

$\pm\theta_E = -(\pm\theta_I) = -(\pm\theta_Y) = \pm\theta_Z$ in all two terminal networks where the phase angle of either the total voltage or the total current is placed at 0° . (It should be understood that reactance, a component of impedance, is the cause of the difference in phase between the voltage and the current, that $\theta_E, \theta_I, \theta_Y$ and θ_Z are the same one and only phase angle from different reference points, that only one may be used at any one time and that if Z or Y appears as a term in a formula the other term must be $E/0^\circ$ or $I/0^\circ$.)

θ

Phase Angle Definitions

$+\theta_E$ = Inductive circuit phase angle of voltage

$-\theta_E$ = Capacitive circuit phase angle of voltage

$+\theta_I$ = Capacitive circuit phase angle of current

$-\theta_I$ = Inductive circuit phase angle of current

$+\theta_Y$ = Capacitive circuit phase angle of admittance

$-\theta_Y$ = Inductive circuit phase angle of admittance

$+\theta_Z$ = Inductive circuit phase angle of impedance

$-\theta_Z$ = Capacitive circuit phase angle of impedance

$$\theta_{B_C} = +90^\circ$$

$$\theta_{B_L} = -90^\circ$$

$$\theta_{E_C} = -90^\circ$$

$$\theta_{E_L} = +90^\circ$$

$$\theta_{E_R} = 0^\circ$$

$$\theta_G = 0^\circ$$

$$\theta_{I_C} = +90^\circ$$

$$\theta_{I_L} = -90^\circ$$

$$\theta_{I_R} = 0^\circ$$

$$\theta_R = 0^\circ$$

$$\theta_{X_C} = -90^\circ$$

$$\theta_{X_L} = +90^\circ$$

$$1/\underline{0^\circ} = +1 = 1 + 0j$$

$$1/\underline{+90^\circ} = \sqrt{-1} = 0 + 1j$$

$$1/\underline{-90^\circ} = -\sqrt{-1} = 0 - 1j$$

$$1/\underline{\pm 180^\circ} = -1 = -1 + 0j$$

$$+270^\circ = -90^\circ, \quad -270^\circ = +90^\circ, \quad \pm 360^\circ = 0^\circ$$

Phase Angle, Series Circuits	θ	Terms
$ \theta_E = \theta_I = \theta_Y = \theta_Z = \tan^{-1} [D^{-1}]$		D_s
$ \theta_E = \theta_I = \theta_Y = \theta_Z = \tan^{-1} Q$		Q_s
$\pm\theta_E = \pm\theta_Z = \tan^{-1} [\pm E_X/E_R]$		$E_R \pm E_X$
$\pm\theta_E = \pm\theta_Z = \tan^{-1} [\pm X/R]$		$R \pm X$
$ \theta_E = \theta_I = \theta_Y = \theta_Z = \cos^{-1} [R/Z]$		$R Z$
$\pm\theta_E = \pm\theta_Z = \sin^{-1} [\pm X/Z]$		$\pm X Z$
$\pm\theta_E = \pm\theta_Z = \tan^{-1} [(E_L - E_C)/E_R]$		$E_R E_C E_L$
$\pm\theta_E = \pm\theta_Z = \tan^{-1} [(X_L - X_C)/R]$		$R X_C X_L$
$\pm\theta_E = \pm\theta_Z = \sin^{-1} [(X_L - X_C)/Z]$		$X_C X_L Z$
$(\pm\theta_Z)_t = \tan^{-1} [(\pm X_s)_t / (R_s)_t]$		$Z_1 / \pm\theta_1$ $Z_2 / \pm\theta_2$
$(\pm X_s)_t = [Z_1 \sin(\pm\theta_1)] + [Z_2 \sin(\pm\theta_2)]$		
$(R_s)_t = (Z_1 \cos \theta_1) + (Z_2 \cos \theta_2)$		

Phase Angle, Parallel Circuits	θ	Terms
	$ \theta_E = \theta_I = \theta_Y = \theta_Z = \tan^{-1} [D^{-1}]$	D_p
	$ \theta_E = \theta_I = \theta_Y = \theta_Z = \tan^{-1} Q$	Q_p
	$\pm\theta_Y = \pm\theta_I = \tan^{-1} [-(\pm B)/G]$	$\pm B \ G$
	$\pm\theta_Y = \pm\theta_I = \sin^{-1} [-(\pm B)/Y]$	$\pm B \ Y$
	$\pm\theta_I = \pm\theta_Y = \tan^{-1} [-(\pm I_X)/I_R]$	$\pm I_X \ I_R$
	$ \theta_E = \theta_I = \theta_Y = \theta_Z = \cos^{-1} [G/Y]$	$G \ Y$
	$\pm\theta_Z = \pm\theta_E = \tan^{-1} [R_p/\pm X_p]$	$R \ \pm X$
	$ \theta_E = \theta_I = \theta_Y = \theta_Z = \cos^{-1} [Z/R_p]$	$R \ Z$
	$\pm\theta_Z = \pm\theta_E = \sin^{-1} [Z/\pm X_p]$	$\pm X \ Z$

Page Notes: $|+B| = B_L = (X_L^{-1})_p$

$|-B| = B_C = (X_C^{-1})_p$

$|+X_p| = (X_L)_p = B_L^{-1}$

$|-X_p| = (X_C)_p = B_C^{-1}$

Phase Angle, Parallel Circuits	θ to κ	Terms
$\pm\theta_Y = \tan^{-1} [-(B_L - B_C)/G]$		$B_C B_L G$
$\pm\theta_Y = \sin^{-1} [-(B_L - B_C)/Y]$		$B_C B_L Y$
$\pm\theta_I = \tan^{-1} [-(I_L - I_C)/I_R]$		$I_C I_L I_R$
$\pm\theta_Z = \tan^{-1} [R(X_L^{-1} - X_C^{-1})]$		$R X_C X_L$
$\pm\theta_Z = \sin^{-1} [Z(X_L^{-1} - X_C^{-1})]$		$X_C X_L Z$
$(\pm\theta_Z)_t = \tan^{-1} [\pm B_t/G_t]$		$Z_2/\pm\theta_2$ $Z_1/\pm\theta_1$
$\pm B_t = [Z_1^{-1} \sin(\pm\theta_1)] + [Z_2^{-1} \sin(\pm\theta_2)]$		
$G_t = (Z_1^{-1} \cos \theta_1) + (Z_2^{-1} \cos \theta_2)$		
ι = Seldom as a symbol due to similarity to english letter i.		
κ = Seldom as a symbol due to similarity to english letter k.		



**Wavelength
Definitions &
Formulas**

λ = Symbol for wavelength.

$\lambda = 1$. In a periodic wave, the distance between points of corresponding phase of two consecutive cycles.

2. The length of one complete cycle of a periodic wave.

λ = Wavelength measured and expressed in various units of distance such as inches, feet, centimeters or meters.

$\lambda = v/f$ where v is the velocity of the wave in the medium through which it is traveling. f = frequency of wave.

Note: In physics, the symbol c is used for the velocity of light.

Wavelength of Sound in Air

$$\lambda \approx 1136/f \text{ feet @ } 25^\circ \text{ C}$$

$$\lambda \approx 346.3/f \text{ meters @ } 25^\circ \text{ C}$$

$$\lambda \approx (1051 + 1.1 T_F)/f \text{ feet @ std pressure}$$

$$\lambda \approx (331.3 + .6 T_C)/f \text{ meters @ std pressure}$$

Wavelength of Electromagnetic Waves

$$\lambda \approx (9.8 \cdot 10^8)/f \text{ feet}$$

$$\lambda \approx (3 \cdot 10^8)/f \text{ meters}$$

$$\lambda = (2.997\ 93 \cdot 10^8)/f \text{ meters (in vacuum)}$$

μ

**Micro,
Mu Factor,
Permeability**

μ = Symbol for micro.

μ = Prefix meaning 1/1,000,000. 10^{-6} multiplier prefix for most basic units. $\mu\text{V} = 10^{-6}$ Volts, $\mu\text{A} = 10^{-6}$ Amperes, $\mu\text{F} = 10^{-6}$ Farads, $\mu\text{H} = 10^{-6}$ Henries.

μ = Symbol for mu factor.

μ = Amplification factor (voltage) in vacuum tubes.

$\mu = \Delta E_p / \Delta E_g$ (with I_p constant)

$\mu = g_m r_p$ E_g = grid voltage, E_p = plate voltage
 g_m = mutual conductance (transconductance)
 r_p = dynamic plate resistance.

μ = Term not used with semiconductors.

See—Active Circuits A_v

μ = Symbol for magnetic permeability.

μ = The magnetic equivalent of electrical conductivity. The magnetic conductivity of a material compared to air or vacuum.

$\mu = B/H$

B = Flux density in gauss

H = Magnetizing force in oersteds

ω

Angular Velocity Definitions & Formulas



ω = Symbol for angular velocity or angular frequency.

ω = The rate at which an angle changes in radians per second. The angular change in a uniformly rotating system measured in radians per second. (2π radians = 360° , 2π radians per second = rps = r/s = Hz)

	Terms
$\omega = 2\pi f = 6.2831853 \dots f$	f
$\omega = B_C/C$	B_C C
$\omega = (B_L L)^{-1}$	BL L
$\omega = (X_C C)^{-1}$	C X_C
$\omega = X_L/L$	L X_L

Resonant Angular Velocity


$$\omega_r = \sqrt{(LC)^{-1}}$$

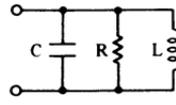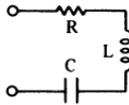

f_r Definition 1

$$\omega_r = [(LC) - (L/R)^2]^{-\frac{1}{2}}$$

(-x)^{-1/2} exception

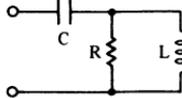

$$\omega_r \approx \sqrt{(LC)^{-1}}$$



ω_r

**Resonant
Angular
Velocity**

$$\omega_r = \sqrt{(LC)^{-1} - (CR)^{-2}} \quad \sqrt{-x} \text{ exception}$$

f_r definition 1

$$\omega_r \approx \sqrt{(LC)^{-1}}$$

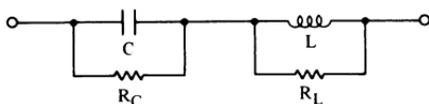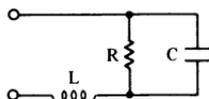

$$\omega_r = \sqrt{[(R_C^2 C)^{-1} - L^{-1}] / [(L/R_L^2) - C]} \quad \sqrt{-x} \text{ exception}$$


f_r definition 1

$$\omega_r \approx \sqrt{(LC)^{-1}}$$

$$\omega_r = \sqrt{(LC)^{-1} - (R/L)^2} \quad \sqrt{-x} \text{ exception}$$

f_r definition 1


$$\omega_r \approx \sqrt{(LC)^{-1}}$$

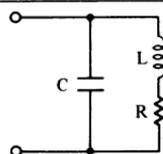

$$\omega_r = [(LC) - (CR)^2]^{-\frac{1}{2}} \quad (-x)^{-\frac{1}{2}} \text{ exception}$$

f_r definition 1


$$\omega_r \approx \sqrt{(LC)^{-1}}$$

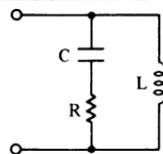

$$\omega_r = \sqrt{[C^{-1} - (R_L^2/L)] / [L - R_C^2 C]}$$

f_r definition 1 $\sqrt{-x}$ exception

$$\omega_r \approx \sqrt{(LC)^{-1}}$$

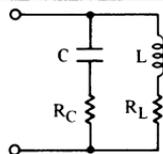

Ω

Ohm Definitions

Ω = Symbol for ohm.

- Ω = 1. The basic unit of resistance, reactance and impedance.
2. That resistance which will develop a current of one ampere from an applied potential of one volt.
 3. That reactance or impedance which will develop a steady state rms current of one ampere from an applied sinewave potential of one volt rms.
 4. The resistance of a uniform column of mercury 106.3 cm long weighing 14.4521 g at a temperature of 0°C.

Ω = Unit often used with multiplier prefixes.

$$\mu\Omega = 10^{-6} \text{ ohms}$$

$$\text{m}\Omega = 10^{-3} \text{ ohms}$$

$$\text{k}\Omega = 10^3 \text{ ohms}$$

$$\text{M}\Omega = 10^6 \text{ ohms}$$

$$\text{G}\Omega = 10^9 \text{ ohms}$$

$$\text{T}\Omega = 10^{12} \text{ ohms}$$

Note: $\text{k}\Omega$ is frequently contracted to K
 $\text{M}\Omega$ is frequently contracted to M
Megohm is frequently contracted to Meg

Ω = A real (positive or 0°) quantity when a unit of resistance.

Ω = A magnitude or a complex quantity when a unit of reactance or impedance.

SECTION TWO

TRANSISTORS

2.1 STATIC (DC) CONDITIONS

A to E

DC Transistor
Symbol
Definitions

$\bar{\alpha}$ – See $-h_{FB}$ or $\bar{\alpha}$

A_I = Static current amplification (seldom used)

A_V = Static voltage amplification (seldom used)

BV_{CBO} – See $-V_{(BR)CBO}$

BV_{CEO} – See $-V_{CEO(SUS)}$

BV_{CER} – See $-V_{CER(SUS)}$

BV_{CES} – See $-V_{CES(SUS)}$

BV_{CEV} – See $-V_{CEV(SUS)}$

BV_{CEX} – See $-V_{CEX(SUS)}$

BV_{EBO} – See $-V_{(BR)EBO}$

E – See $-V$ for dc transistor voltages

See also $-V$, Opamp

See also $-E$, Passive Circuits

E = The original symbol for the electric force originally known as electromotive force. This force is now known as voltage, potential or potential difference. The voltage symbol E has been superseded by V for dc transistor voltages and for all operational amplifier voltages.

$E_{S/b}$ – (second breakdown energy) See $-I_{S/b}$

Note: The term second breakdown energy ($E_{S/b}$) has never been appropriate for static transistor conditions since continuous power at any level converts to infinite energy.

h

Static (DC)
Hybrid
Parameters

h_{FB} = Seldom used common-base static forward-current transfer ratio.

$$h_{FB} = \text{DC alpha } (\bar{\alpha})$$

$$h_{FB} = I_C/I_E$$

$$h_{FB} = h_{FE}/(h_{FE} + 1)$$

h_{FE} = Common-emitter static forward-current transfer ratio at a specified collector current, collector voltage and junction temperature.

$$h_{FE} = \text{DC beta } (\bar{\beta})$$

$$h_{FE} = I_C/I_B$$

$$h_{FE} = (I_E/I_B) - 1$$

$$h_{FE} = [(I_E/I_C) - 1]^{-1}$$

$h_{FE(INV)}$ = Seldom used h_{FE} when collector and emitter leads are interchanged.

h_{IE} = Seldom used common-emitter static input resistance.

h Notes:

The DC counterparts of h_{fc} , h_{ib} , h_{ob} , h_{oc} , h_{oe} , h_{rb} , h_{rc} , and h_{re} are very seldom used.

h_{FE} usually has a different value than h_{fe} measured under the same conditions.

h_{IE} and h_{IB} will have a much higher value than their small signal counterparts measured under the same conditions.

|

**DC Transistor
Current
Definitions**

- I_B = DC base current.
- I_C = DC collector current. See—I Note ①
- I_E = DC emitter current.
- I_{BB} = Base supply current.
- I_{CC} = Collector supply current.
- I_{CO} — See— I_{CBO}
- I_{EE} = Emitter supply current.
- I_{EO} — See— I_{EBO}
- I_{CBO} = DC collector to base leakage current at a specified voltage and temperature with emitter open. ② ③
- I_{CEO} = DC collector to emitter leakage current at a specified voltage and temperature with base open. ② ③
- I_{CER} = DC collector to emitter leakage current at a specified voltage and temperature with a specified base to emitter resistance. See—I Notes ② ③
- I_{CES} = DC collector to emitter leakage current at a specified voltage and temperature with the base and emitter shorted. See—I Notes ② ③
- I_{CEV} = DC collector to emitter leakage current at a specified voltage and temperature with a specified base to emitter reverse bias voltage. See—I Notes ② ③
- I_{CEX} = DC collector to emitter leakage current at a specified voltage and temperature with a specified base to emitter circuit. See—I Notes ② ③
- I_{EBO} = DC base to emitter reverse bias leakage current at a specified voltage and temperature with open collector. See—I Notes ② ③
-

I I_{S/b}

DC Transistor
Currents,
Second Breakdown
Current

I_F = Forward bias dc current.

I_N = Noise current. See -I_N, Passive Circuits
See also -NF

I_O = DC output current. See also -Passive Circuits

I_R - See -I, Passive Circuits

I_{S/b} = Symbol for second breakdown current.

I_{S/b} = The collector current at which second breakdown occurs at a specified collector voltage, case or junction temperature and pulse duration.

Second breakdown occurs when the combination of voltage, current, temperature, time and a current con- striction within the transistor produces spot heating suf- ficient to thermally maintain or increase the collector current regardless of base bias. In the usual transistor circuit, if second breakdown has been allowed to occur, transistor failure will also occur due to excessive spot junction temperature.

Second breakdown is not the same as thermal failure where failure may be predicted from low voltage ther- mal resistance calculations. Second breakdown may occur at positive, zero, or negative base bias.

Circuit design should be such that the manufacturers second breakdown specifications are not exceeded under worst case conditions. Alternately, the second breakdown characteristics of transistors may be mea- sured with special non-destructive procedures.

Static (DC) Transistor Currents	I_B I_C I_E	Applicable Notes
$I_B = I_C/h_{FE}$		④
$I_B = I_E/(h_{FE} + 1)$		⑤
$I_B = V_{BE}/h_{IE}$		⑥
$I_B \approx [\log^{-1}(V_{BE}/.06)]/(10^{13}h_{FE})$		⑦
$I_C = h_{FE}I_B$		④
$I_C = I_E - I_B$		⑤
$I_C = (h_{FE}V_{BE})/h_{IE}$		⑥
$I_C \approx [\log^{-1}(V_{BE}/.06)](5 \cdot 10^{-16}h_{FE})$		⑦
$I_C \approx 10^{-13} [\log^{-1}(V_{BE}/.06)]$		
$I_E = I_C + I_B$		④
$I_E = (h_{FE} + 1)I_B$		⑤
$I_E = [V_{BE}(h_{FE} + 1)]/h_{IE}$		⑥
$I_E \approx (5 \cdot 10^{-16})(h_{FE} + 1) [\log^{-1}(V_{BE}/.06)]$		⑦

Notes:

- ① The subscript of I_C is a capital letter for DC. It is often difficult to distinguish between a capital and a lower case C subscript. I_c (lower case) is rms collector current and i_C (upper case) is instantaneous total collector current.

**Static (DC)
Transistor
Currents**


I_B I_C I_E

**Applicable
Notes**

$$I_C \approx 10^{-13} [\log^{-1} (V_{BB}/.06)]$$

$$I_B = I_C/h_{FE}$$

$$I_E = I_C + I_B$$

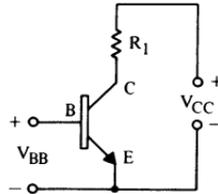

- ①
- ②
- ③
- ④
- ⑤
- ⑥


$$I_C = [h_{FE}(V_{BB} - V_{BE})]/R_2$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)]$$

$$V_{BE} \approx .6$$

$$I_B = I_C/h_{FE}$$

$$I_E = I_C + I_B$$

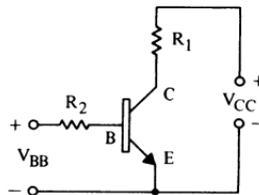

- ①
- ②
- ③
- ④
- ⑤
- ⑥
- ⑦


$$I_C = [h_{FE}(V_{CC} - V_{BE})]/R_2$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)]$$

$$V_{BE} \approx .6$$

$$I_B = I_C/h_{FE}$$

$$I_E = I_C + I_B$$

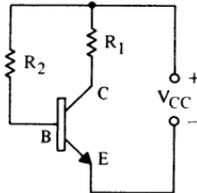

- ①
- ②
- ③
- ④
- ⑤
- ⑥
- ⑦

Notes:

- ② The standard specified temperature is 25°C
- ③ Transistor leakage currents have a temperature dependent component and a voltage dependent component.
- ④ h_{FE} , V_{BE} and h_{IE} are temperature, current and voltage dependent.
- ⑤ $\log x = \log_{10} x$, $\log^{-1} x = \text{antilog } x = 10^x$

Static (DC) Transistor Currents	I_B I_C I_E	Applicable Notes
$I_E = (V_{CC} - V_{BE}) / (R_1 + [R_3 / (h_{FE} + 1)])$ $V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$ $I_B = I_E / (h_{FE} + 1)$ $I_C = I_E - I_B$ $I_{CC} = I_E$		① ② ③ ④ ⑤ ⑥ ⑦
$I_E = (V_{CC} - V_{BE}) / (R_1 + R_5 + [R_3 / (h_{FE} + 1)])$ $V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$ $I_B = I_E / (h_{FE} + 1)$ $I_C = I_E - I_B$ $I_{CC} = I_E$		① ② ③ ④ ⑤ ⑥ ⑦
$I_C = [V_{CC} - (V_{BE} R_X)] / (R_1 + [(R_1 + R_3) / h_{FE}])$ $V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$ $R_X = [(R_1 + R_3) / R_4] + 1$ $I_B = I_C / h_{FE}$ $I_E = I_C + I_B$ $I_{CC} = I_E + (V_{BE} / R_4)$		① ② ③ ④ ⑤ ⑥ ⑦

Static (DC) Transistor Currents	I_B I_C I_E	Applicable Notes
$I_C = h_{FE} \left[\left(\frac{V_{CC} - V_{BE}}{R_2} \right) - \left[\frac{V_{BE}}{R_4} \right] \right]$ $V_{BE} \approx .06 \left[\log (10^{13} I_C) \right]$ $V_{BE} \approx .6$ $I_B = I_C / h_{FE}$ $I_E = I_C + I_B$		① ② ③ ④ ⑤ ⑥ ⑦
$I_C = \left[h_{FE} (V_{BB} - V_{BE}) \right] / \left(R_2 + \left[R_5 (h_{FE} + 1) \right] \right)$ $V_{BE} \approx .06 \left[\log (10^{13} I_C) \right]$ $V_{BE} \approx .6$ $I_B = I_C / h_{FE}$ $I_E = I_C + I_B$		① ② ③ ④ ⑤ ⑥ ⑦
$I_C = \left[h_{FE} (V_X - V_{BE}) \right] / \left(R_X + \left[R_5 (h_{FE} + 1) \right] \right)$ $V_{BE} \approx .06 \left[\log (10^{13} I_C) \right]$ $V_{BE} \approx .6$ $V_X = V_{CC} / \left[\left(R_2 / R_4 \right) + 1 \right]$ $R_X = \left(R_2^{-1} + R_4^{-1} \right)^{-1}$ $I_B = I_C / h_{FE}$ $I_E = I_C + I_B$		① ② ③ ④ ⑤ ⑥ ⑦

Static (DC)
Transistor
Currents

I_B I_C I_E

Applicable
Notes

$$I_C = \frac{[V_{CC} - (V_{BE} R_X)]}{(R_1 + R_6 + [(R_1 + R_3 + R_6)/h_{FE}])}$$


$$V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$$

$$R_X = [(R_1 + R_3 + R_6)/R_4] + 1$$

$$I_B = I_C/h_{FE}$$

$$I_E = I_C + I_B$$

$$I_{CC} = I_E + (V_{BE}/R_4)$$

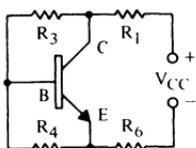

- ①
- ②
- ③
- ④
- ⑤
- ⑥
- ⑦

$$I_C = [V_{CC} - (V_{BE} R_{X1})] / [R_{X2} + (R_{X3}/h_{FE})]$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$$

$$R_{X1} = [(R_1 + R_3)/R_4] + 1$$


$$R_{X2} = R_1 + R_5 + [(R_1 R_5 + R_3 R_5)/R_4]$$

$$R_{X3} = R_{X2} + R_3$$

$$I_B = I_C/h_{FE}$$

$$I_E = I_C + I_B$$
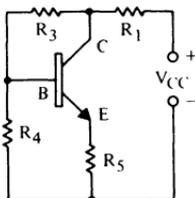
$$I_{CC} = I_E + [(I_E R_5 + V_{BE})/R_4]$$



- ①
- ②
- ③
- ④
- ⑤
- ⑥
- ⑦

I Notes:

- ⑥ "Exact formulas" apply to silicon, germanium, npn, pnp, small signal and power transistors. (Exact formulas are not really exact since h_{FE} will vary somewhat with collector current, collector voltage and temperature.)
- ⑦ The V_{BE} of silicon transistors varies with temperature at the rate of approximately -2.2 mV per $^{\circ}\text{C}$.

**Static (DC)
Transistor
Currents**

I_B I_C I_E

$$I_C = [V_{CC} - (V_{BE} R_{X1})] / [R_{X2} + (R_{X3} / h_{FE})]$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$$

$$R_{X1} = (R_1 G_4) + (R_3 G_4) + 1$$

$$R_{X2} = (R_1 R_5 G_4) + (R_3 R_5 G_4) + R_1 + R_5$$

$$R_{X3} = R_{X2} + R_3$$

$$R_1 = R_{1A} + R_{1B}$$


$$G_4 = 1/R_4$$

$$I_B = I_C / h_{FE}$$

$$I_E = I_C + I_B$$

$$I_{CC} = I_E + [(I_E R_5 + V_{BE}) / R_4]$$
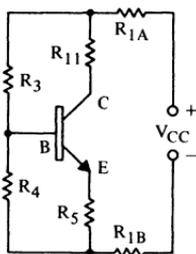
$$V_C = V_{CC} - (I_{CC} R_{1A}) - (I_C R_{11})$$



Page Notes:

1. R_{1A} , R_{1B} , G_4 , R_5 and/or R_{11} may equal zero.
2. R_4 must be manually converted to G_4 since conventional mathematics and calculators will not allow division by zero or infinity.
3. R_4 may equal infinity. When $R_4 = \infty$, $G_4 = 0$.
4. Reverse power supply polarity and emitter arrow for pnp transistors.
5. The effect of varying collector voltage upon collector current has been assumed to be negligible.

UNIVERSAL TRANSISTOR DC CURRENT FORMULA

L to r

Static (DC)
Definitions

LV_{CEO} – See– $V_{CEO(SUS)}$

LV_{CER} – See– $V_{CER(SUS)}$

LV_{CES} – See– $V_{CES(SUS)}$

LV_{CEV} – See– $V_{CEV(SUS)}$

LV_{CEX} – See– $V_{CEX(SUS)}$

n = Region of transistor where electrons are the majority carriers.

npn = Transistor type having two n regions and one p region.
(positive polarity V_{CC} and V_{BB})

p = Region of transistor where holes are the majority carriers.

pnp = Transistor type having two p regions and one n region.
(negative polarity V_{CC} and V_{BB})

P_C = Collector power dissipation

$$P_C = V_{CE}I_C$$

P_D = Device power dissipation. See– P_T

P_T = Total power dissipation of transistor.

$$P_T = (V_{CE}I_C) + (V_{BE}I_B)$$

r_B = T equivalent static internal series base resistance.

r_C = T equivalent static internal series collector resistance.

r_E = T equivalent static internal series emitter resistance.

$r_{CE(SAT)}$ = Collector to emitter saturation resistance.

R to T

DC or
Static
Definitions

- R_B = External series base resistance.
 R_C = External series collector resistance.
 R_E = External series emitter resistance.
 R_L = Load resistance.
 R_S = Source resistance.
 R_{BC} – See– R_{CB}
 R_{BE} = External base to emitter resistance.
 R_{CB} = External collector to base resistance.
 R_{CE} = External collector to emitter resistance.
 R_{EB} – See– R_{BE}
 R_{EC} – See– R_{CE}
 T_A = Ambient temperature.
 T_C = Case temperature. (T_C meaning “temperature in °C” is not used for semiconductors since temperature is given in °C unless noted.)
 T_J = Junction temperature.
 $T_J = T_A + (P_t R_{\theta JA})$
 $T_J = T_A + [P_t (R_{\theta SA} + R_{\theta CS} + R_{\theta JC})]$
 T_L = Lead temperature.
 T_S = (Heat) sink temperature.
 T_T = Tab temperature.
 T_{STG} = Storage temperature.
-

V

DC Transistor Voltage Symbol Definitions

- V_B = Base voltage.
- V_{BB} = Base supply voltage.
- V_{BC} – See $-V_{CB}$
- V_{BE} = Base to emitter forward bias voltage
- $V_{BE(ON)}$ = Base to emitter forward bias voltage with normal collector to base reverse bias voltage.
- $V_{BE(ON)} \approx (.06 [\log (10^{13} I_C)]) - [.0022 (T_J - 27)]$
- $V_{BE(SAT)}$ = Base to emitter forward bias voltage with collector in saturation. (typically, saturation occurs when the collector to base junction becomes forward biased)
- $V_{(BR)CBO}$ = Collector to base breakdown voltage with emitter open-circuited.
- $V_{(BR)CEO}$ – See $-V_{CEO(SUS)}$
- $V_{(BR)CER}$ – See $-V_{CER(SUS)}$
- $V_{(BR)CES}$ – See $-V_{CES(SUS)}$
- $V_{(BR)CEV}$ – See $-V_{CEV(SUS)}$
- $V_{(BR)CEX}$ – See $-V_{CEX(SUS)}$
- $V_{(BR)EBO}$ = Emitter to base breakdown voltage with collector open-circuited.
- V_C = Collector voltage.
- V_{CB} = Collector to base voltage.
- V_{CBO} = See $-V_{(BR)CBO}$
- V_{CC} = Collector supply voltage.
- V_{CE} = Collector to emitter voltage.
-

V

DC Transistor Voltage Symbol Definitions

V_{CEO} – See– $V_{CEO(SUS)}$

$V_{CEO(SUS)}$ = Collector to emitter sustaining voltage with base open.

V_{CER} – See– $V_{CER(SUS)}$

$V_{CER(SUS)}$ = Collector to emitter sustaining voltage with specified base to emitter resistance.

V_{CES} – See– $V_{CES(SUS)}$

$V_{CES(SUS)}$ = Collector to emitter sustaining voltage with base to emitter short-circuit.

V_{CEV} – See– $V_{CEV(SUS)}$

$V_{CEV(SUS)}$ = Collector to emitter sustaining voltage with specified base to emitter voltage.

V_{CEX} – See– $V_{CEX(SUS)}$

$V_{CEX(SUS)}$ = Collector to emitter sustaining voltage with specified base to emitter circuit.

V_E = Emitter voltage.

V_{EB} = Emitter to base reverse bias voltage.

V_{EBO} – See– $V_{(BR)EBO}$

V_{EE} = Emitter supply voltage.

V_{RT} = Reach through voltage (certain old transistors only).

Note:

Collector to emitter breakdown voltage of almost all present production transistors is measured at a current above the negative resistance region where the voltage is sustained over a wide range of current and is therefore called sustaining voltage.

DC Transistor Voltages

V_B V_C V_E


Applicable Notes

$V_E = 0$

$V_B = V_{BE} \approx .6$

$V_{BE} \approx .06 [\log (10^{13} I_C)]$

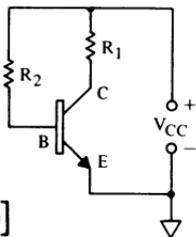$V_C = V_{CC} - [h_{FE}(V_{CC} - V_{BE})(R_1/R_2)]$



- I-①
- I-②
- I-③
- I-④
- I-⑤
- I-⑥
- I-⑦


$V_E = 0$

$V_B = V_{BE} \approx .6$

$V_{BE} \approx .06 [\log (10^{13} I_C)]$

$V_C \approx V_{CC} / ([h_{FE}(R_1/R_3)] + 1)$

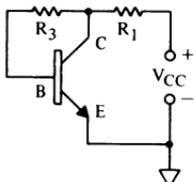$V_C = [(V_{CC} - V_{BE}) / ([h_{FE} + 1)(R_1/R_3)] + 1] + V_{BE}$



- I-①
- I-②
- I-③
- I-④
- I-⑤
- I-⑥
- I-⑦

$V_E = [V_{CC} - V_{BE}] / ([R_2 / [R_5(h_{FE} + 1))] + 1]$


$V_C = V_{CC} - R_1 h_{FE} ([V_{CC} - V_{BE}] / [R_2 + R_5(h_{FE} + 1)])$

$V_B = V_E + V_{BE}$

$V_{BE} \approx .06 [\log (10^{13} I_C)]$

$V_{BE} \approx .6$

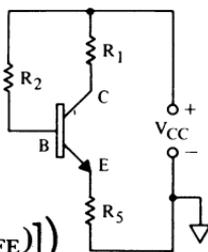$V_C \approx V_{CC} - ([R_1 V_{CC}] / [R_5 + (R_1/h_{FE})])$



- I-①
- I-②
- I-③
- I-④
- I-⑤
- I-⑥
- I-⑦

**DC Transistor
Voltages**

V_B V_C V_E

**Applicable
Notes**

$$V_C = V_{CC} - \left([R_1 h_{FE} (V_X - V_{BE})] / [R_X + R_5 (h_{FE} + 1)] \right)$$


$$V_E = [V_X - V_{BE}] / \left(R_X / [R_5 (h_{FE} + 1)] \right)$$

$$V_B = V_E + V_{BE} \approx V_E + .6$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$$

$$V_X = V_{CC} / \left[(R_2 / R_4) + 1 \right]$$

$$R_X = [R_2^{-1} + R_4^{-1}]^{-1}$$

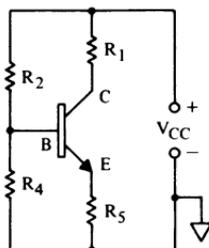

I-①
I-②
I-③
I-④
I-⑤
I-⑥
I-⑦

$$V_C = V_{CC} - (I_{CC} R_1)$$

$$V_E = I_E R_5$$

$$V_B = V_E + V_{BE} \approx V_E + .6$$

$$V_{BE} \approx .06 [\log (10^{13} I_C)] \approx .6$$

$$I_B = I_C / h_{FE}$$

$$I_E = [I_C (h_{FE} + 1)] / h_{FE} \approx I_C$$


$$I_{CC} = I_E + [(I_E R_5 + V_{BE}) / R_4]$$

$$I_C = [V_{CC} - (V_{BE} R_{X1})] / [R_{X2} + (R_{X3} / h_{FE})]$$

$$R_{X1} = [(R_1 + R_3) / R_4] + 1$$

$$R_{X2} = R_1 + R_5 + [(R_1 R_5 + R_3 R_5) / R_4]$$

$$R_{X3} = R_{X2} + R_3$$

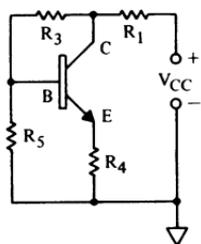

I-①
I-②
I-③
I-④
I-⑤
I-⑥
I-⑦

α to θ

Static (DC) Definitions & Formulas

α = Greek script letter alpha.

$\bar{\alpha}$ = Static (DC) alpha.

Note: Although “DC alpha” is still verbalized, the equivalent hybrid parameter symbol h_{FB} has almost completely superceded $\bar{\alpha}$ as the accepted written symbol. See— h_{FB}

$\bar{\alpha} = h_{FB}$

$\bar{\alpha}$ = Common base static forward current transfer ratio. See— h_{FB}

Note: $\bar{\alpha}$ and h_{FB} are seldom used with modern transistors since specifications are in the common emitter form h_{FE} .

$\bar{\alpha} = I_C/I_E = h_{FE}/(h_{FE} + 1)$

$\bar{\alpha} = (h_{FE}I_B)/I_E = I_C/[I_B(h_{FE} + 1)]$

β = Greek script letter beta.

$\bar{\beta}$ = Static (DC) beta.

Note: DC beta is often verbalized, but the equivalent hybrid parameter symbol h_{FE} is used on all specifications and most other written or printed usage. See— h_{FE}

$\bar{\beta} = h_{FE}$

$\bar{\beta}$ = Common emitter static forward current transfer ratio at specified I_C , V_{CE} and T_J . See— h_{FE}

$\bar{\beta} = I_C/I_B = (I_E/I_B) - 1 = [(I_E/I_C) - 1]^{-1}$

$\bar{\beta} = [\bar{\alpha}^{-1} - 1]^{-1} = [h_{FB}^{-1} - 1]^{-1}$

θ = Greek letter theta = Obsolete symbol for thermal resistance. See— R_θ

TRANSISTORS

SECTION 2.2

Small Signal

Conditions

***a* to C**

Small-Signal Low Frequency Definitions

a = Substitute symbol for α (not recommended)

A_i = Small-signal current amplification.
(small-signal current gain)

A_i = The ratio of output current to input current

$A_i = \alpha = h_{fb}$ when circuit is common base with output ac shorted.

$A_i = \beta = h_{fe}$ when circuit is common emitter with output ac shorted.

A_v = Small-signal voltage amplification.
(small-signal voltage gain)

A_v = The ratio of output voltage to input voltage

C_c = Collector to case capacitance.

$C_{b'c}$ = Collector to base feedback capacitance.

C_{cb} = Collector to base feedback capacitance.

C_{ob} — See— C_{obo}

C_{oe} — See— C_{oeo}

C_{ibo} = Common base open-circuit input capacitance.

C_{ieo} = Common emitter open-circuit input capacitance.




C_{obo} = Common base open-circuit output capacitance.

C_{oeo} = Common emitter open-circuit output capacitance.

Small-Signal Low-Frequency Common Base	A_i	Current Amplification	Applicable Notes
$A_i = i_o/i_g$ $A_i = i_c/i_e$ $A_i = \alpha$ (alpha) $A_i = h_{fb}$ $A_i = h_{fe}/(h_{fe} + 1)$ $A_i \approx 1$		① ③ ④ ⑤ ⑥	
$A_i = i_o/i_g$ $A_i = i_c/i_e$ $A_i \approx 1$ $A_i \approx [h_{fe}^{-1}(h_{oe}R_L + 1) + 1]^{-1}$ (accuracy typically > 4 digits)		① ③ ④ ⑤ ⑥	
$A_i = i_o/i_g$ $A_i = i_c/i_e$ $A_i \approx 1$ $A_i \approx [h_{fc}^{-1}(h_{oe}R_L + 1) + 1]^{-1}$		① ③ ④ ⑤ ⑥	

A Notes:

① $\text{---}\text{---}\text{---}$ is the graphic symbol for an alternating current generator (infinite impedance) or any very high impedance signal source.

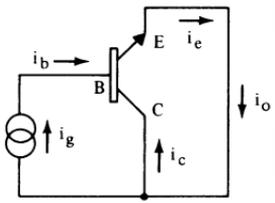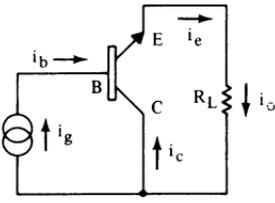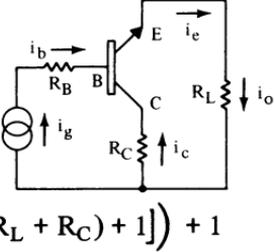Small-Signal Low Frequency Common Collector	A_i Current Amplification	Applicable Notes
$A_i = i_o/i_g = i_e/i_b$ $A_i = h_{fc}$ $A_i = h_{fe} + 1$		① ③ ④ ⑤ ⑥
$A_i = i_o/i_g = i_e/i_b$ $A_i \approx h_{fe}$ $A_i = [h_{fe} + 1] / [(h_{oe}R_L) + 1]$		① ③ ④ ⑤ ⑥
$A_i = i_o/i_g = i_e/i_b$ $A_i \approx h_{fe}$ $A_i \approx h_{fe} [h_{oe}(R_L + R_C) + 1]$ $A_i = ([h_{fe} - (h_{oe}R_L)] / [h_{oe}(R_L + R_C) + 1]) + 1$		① ③ ④ ⑤ ⑥

A Notes:

- ② $\text{---}\bigcirc\text{---}$ is the graphic symbol for an ac voltage generator (zero impedance) or any very low impedance signal source.
- ③ Formulas apply to silicon, germanium, npn and pnp bipolar transistors. Emitter arrows and the power supply polarity (if shown) must be reversed for pnp transistors.
- ④ Small-signal parameters will vary with temperature as well as with dc bias currents and voltages.
- ⑤ Small-signal parameters if specified by the manufacturer seldom have maximum or minimum limits and may vary widely. The relationships of parameters, however, will hold very closely to the formulas.

**Small-Signal
Low Frequency
Common Emitter**

A_i


**Current
Amplification**

**Applicable
Notes**

$$A_i = i_o/i_g = i_c/i_b$$

$$A_i = \beta \text{ (beta)}$$

$$A_i = h_{fe}$$

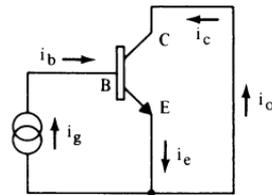


- ①
- ③
- ④
- ⑤
- ⑥

$$A_i = i_o/i_g = i_c/i_b$$

$$A_i \approx h_{fe}$$

$$A_i = h_{fe}/[h_{oe}R_L + 1]$$

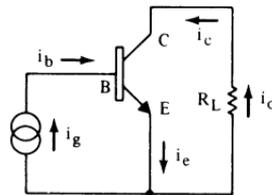


- ①
- ③
- ④
- ⑤
- ⑥

$$A_i = i_o/i_g = i_c/i_b$$

$$A_i \approx h_{fe}$$

$$A_i \approx h_{fe}/[h_{oe}(R_L + R_E) + 1]$$
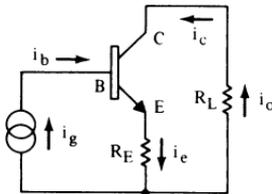
$$A_i = [h_{fe} - h_{oe}R_E]/[h_{oe}(R_L + R_E) + 1]$$




- ①
- ③
- ④
- ⑤
- ⑥

$$A_i = i_o/i_g$$

$$A_i = i_c/i_b$$

$$A_i \approx [(R_L/R_F) + h_{fe}^{-1}]^{-1}$$
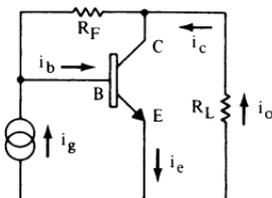
$$A_i \approx h_{fe} [R_L(R_F^{-1}h_{fe} + R_F^{-1} + h_{oe}) + 1]^{-1}$$



- ①
- ③
- ④
- ⑤
- ⑥

**Small-Signal
Low Frequency
Common Base**

A_V

**Voltage
Amplification**

**Applicable
Notes**


$$A_v = e_o/e_g = e_c/e_e$$

$$A_v \approx 37I_C R_L$$

$$A_v \approx (h_{fe} R_L)/h_{ie}$$

$$A_v \approx [h_{ie} h_{fe}^{-1} (R_L^{-1} + h_{oe}) - h_{re}]^{-1}$$
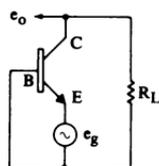
$$A_v = \frac{[h_{ie} h_{fe}^{-1} h_{oe} - h_{re} + 1]}{[h_{ie} h_{fe}^{-1} (R_L^{-1} + h_{oe}) - h_{re}]}$$



②
③
④
⑤
⑥


$$A_v = e_o/e_g$$

$$A_v = e_c/e_e$$

$$A_v \approx (h_{fe} R_L)/(h_{ie} + R_B)$$

$$A_v \approx [h_{fe}^{-1} (h_{ie} + R_B) (R_L^{-1} + h_{oe}) - h_{re}]^{-1}$$
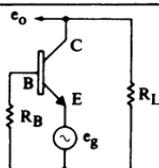
$$A_v = \frac{[(h_{ie} + R_B) h_{fe}^{-1} h_{oe} - h_{re} + 1]}{[h_{fe}^{-1} (h_{ie} + R_B) (R_L^{-1} + h_{oe}) - h_{re}]}$$




②
③
④
⑤
⑥

$$A_v = e_o/e_g$$

$$A_v \approx R_L/[R_E + h_{fe}^{-1} (h_{ie} + R_B)]$$
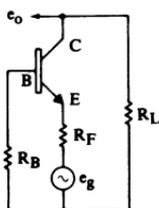
$$A_v \approx [h_{fe}^{-1} (h_{ie} + R_B + h_{fe} R_E) (R_L^{-1} + h_{oe}) - h_{re}]^{-1}$$



②
③
④
⑤
⑥

**Small-Signal
Low Frequency
Common Collector**

A_V

**Voltage
Amplification**


**Applicable
Notes**

$$A_v = e_o/e_g$$

$$A_v = e_e/e_b$$

$$A_v \approx 1$$
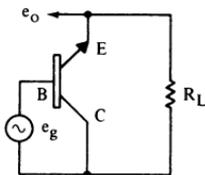
$$A_v = [h_{ie}(h_{oe} + R_L^{-1})(h_{fe} + 1)^{-1} - h_{re} + 1]^{-1}$$



②
③
④
⑤
⑥


$$A_v = e_o/e_g$$

$$A_v \approx 1$$

$$A_v \approx 1$$

when $R_g \ll (h_{fe}R_L)$
and $R_L \gg (h_{re}/h_{oe})$
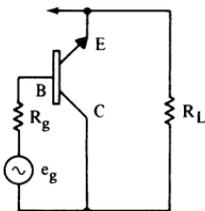
$$A_v = \left([(h_{ie} + R_g)(h_{oe} + R_L^{-1})(h_{fe} + 1)^{-1}] - h_{re} + 1 \right)^{-1}$$




②
③
④
⑤
⑥

$$A_v = e_o/e_g$$

$$A_v \approx 1$$

$$A_v = (\text{Common emitter } A_v) \cdot R_L(h_{fe}^{-1} + 1) R_{L2}^{-1}$$




See—Common emitter formulas

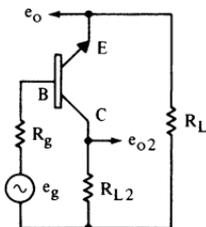

②
③
④
⑤
⑥

A Notes:

- ⑥ Most small-signal parameters are drastically different from the dc parameters due to the nonlinear nature of transistors. A diode or transistor junction which develops .6 volts from 1 mA forward current has a dc resistance of 600 ohms according to ohms law,

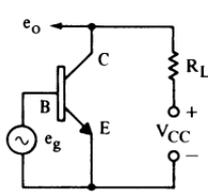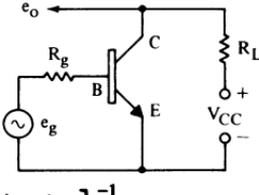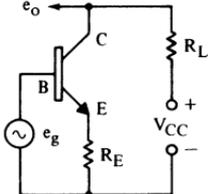Small-Signal Low Frequency Common Emitter	A_V Voltage Amplification	Applicable Notes
$A_V = e_o/e_g$ $A_V \approx 37I_C R_L$ $A_V \approx (h_{fe} R_L)/h_{ie}$ $A_V = [h_{ie} h_{fe}^{-1} (R_L^{-1} + h_{oe}) - h_{re}]^{-1}$		② ③ ④ ⑤ ⑥
$A_V = e_o/e_g$ $A_V \approx R_L [.027I_C^{-1} + R_g h_{fe}^{-1}]^{-1}$ $A_V \approx (h_{fe} R_L)/(h_{ie} + R_g)$ $A_V = [h_{fe}^{-1} (R_g + h_{ie})(R_L^{-1} + h_{oe}) - h_{re}]^{-1}$		② ③ ④ ⑤ ⑥
$A_V = e_o/e_g$ $A_V \approx R_L/R_E$ $A_V \approx (h_{fe} R_L)/[h_{ie} + (h_{fe} R_E)]$ $A_V = [h_{fe}^{-1} h_{ie} (R_L^{-1} + h'_{oe}) + R_E R_L^{-1} (h_{fe} + 1) + h_{fe}^{-1} h'_{oe} - h_{re}]^{-1}$ $h'_{oe} = (R_E + h_{oe}^{-1})^{-1}$		② ③ ④ ⑤ ⑥

A Notes:

- ⑥ Cont. but if a small ac signal is superimposed upon the dc and measured, the ac resistance will be found to be about 26 ohms. This small-signal resistance (r) is often verbally expressed as impedance (z), but admittance (y) is used at frequencies where internal capacitances are significant.

Small-Signal
Low Frequency
Common Emitter

A_V

Voltage
Amplification

Applicable
Notes

$$A_V = e_o/e_g$$

$$A_V \approx R_L [R_E(R_g h_{ie}^{-1} + 1)]^{-1}$$


$$A_V \approx h_{fe} R_L [h_{ie} + R_g + h_{fe} R_E]^{-1}$$

$$A_V = \left(h_{fe}^{-1} R_{BX} (R_L^{-1} + h'_{oe}) + h_{fe}^{-1} R_{EX} [R_L^{-1} (h_{fe} + 1) + h'_{oe}] \right)^{-1}$$

$$R_{BX} = R_g + [h_{ie} - h_{re} h_{oe}^{-1} (h_{fe} + 1)]$$

$$R_{EX} = R_E + h_{re} h_{oe}^{-1}$$

$$h'_{oe} = (h_{oe}^{-1} + R_E)^{-1}$$

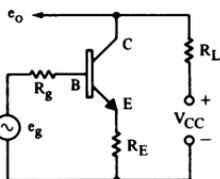


②
③
④
⑤
⑥

$$A_V = e_o/e_g$$

$$A_V \approx 38I_C (R_L^{-1} + R_F^{-1})^{-1}$$

$$A_V \approx h_{ie}^{-1} [h_{fe} (R_L^{-1} + R_F^{-1})^{-1}]$$
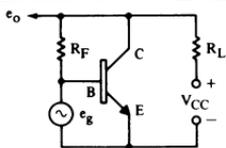
$$A_V = \left(h_{ie} h_{fe}^{-1} [R_L^{-1} + R_F^{-1} + h_{oe}] - h_{re} \right)^{-1}$$



②
③
④
⑤
⑥


$$A_V = e_o/e_g$$

$$A_V \approx R_F/R_g$$

$$A_V = A_{VX} \left([R_g R_F^{-1} (A_{VX} + 1)] + 1 \right)^{-1}$$

$$A_{VX} \approx 38I_C (R_L^{-1} + R_F^{-1})^{-1}$$
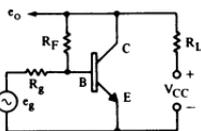
$$A_{VX} = \left(h_{ie} h_{fe}^{-1} [R_L^{-1} + R_F^{-1} + h_{oe}] - h_{re} \right)^{-1}$$




②
③
④
⑤
⑥

Small-Signal
Low Frequency
Common Emitter

A_V

Voltage
Amplification

Applicable
Notes

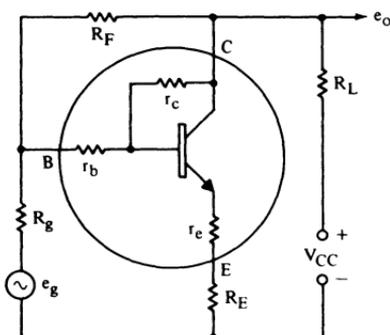

$$A_v = e_o/e_g$$

$$A_v = \left([R_{BX} h_{fe}^{-1} (R_L^{-1} + G_{CX})] + R_{EX} h_{fe}^{-1} [G_{CX} + R_L^{-1} (h_{fe} + 1)] \right)^{-1}$$

$$r_e = h_{re} h_{oe}^{-1}$$

$$r_c = h_{oe}^{-1} (h_{fe} + 1)$$

$$r_b = h_{ie} - [h_{re} h_{oe}^{-1} (h_{fe} + 1)]$$

$$R_{BX} = R_g + [(R_F r_b)(R_F + r_b + r_c)^{-1}]$$

$$R_{EX} = R_E + r_e + \frac{[(r_b + r_c)(R_F + r_b + r_c)^{-1}]}{(h_{fe} + 1)}$$

$$R_{CX} = (R_F r_c)(R_F + r_b + r_c)^{-1}$$

$$G_{CX} = \left([R_{CX} (h_{fe} + 1)^{-1}] + R_{EX} \right)^{-1}$$

②
③
④
⑤
⑥

e




Small-Signal Voltage Definitions

- e = Symbol for emitter. (small signal subscript)
- e = Small-signal voltage. (rms or instantaneous)
- e_b = Small-signal base voltage.
- e_c = Small-signal collector voltage.
- e_e = Small-signal emitter voltage.
- e_g = Generator voltage.
- e_i = Input voltage.
- e_N = Noise voltage (rms).
- e_N = Thermal noise voltage or equivalent input total transistor noise voltage.
- $e_{N(\sqrt{\text{Hz}})}$ = Noise voltage per root hertz.
($\text{BW} = 1 \text{ Hz}$ or $e_N/\sqrt{\text{BW}}$ for white noise)
- $e_{N(s)}$ = Transistor shot noise (white noise) voltage.
- $e_{N(\text{th})}$ = Thermal noise voltage. (white noise voltage of an ideal resistance at a specified temperature)
- $e_{N(\text{TR})}$ = Transistor noise voltage.
- $e_{N(1/f)}$ = $1/f$ noise voltage of a transistor. (Resistor $1/f$ noise is known as excess or current noise)
- e_o = Output voltage.
- e_p = Peak voltage.
- e_s — See— $e_{N(s)}$.
- e_t = Total or equivalent voltage.
- $e_{1/f}$ — See— $e_{N(1/f)}$.
-

e_b e_c	Small-Signal Voltages	Applicable Notes
$e_b = i_g h_{ie}$ $e_c = 0$		① ② ③ ④ ⑤
$e_b \approx i_g h_{ie}$ when $A_v < 50$ $e_b = i_g Z_i$ See $-Z_i$ $e_c \approx -h_{fe} i_g R_L$ $e_c = -A_v i_g Z_i$ See $-A_v, Z_i$		① ② ③ ④ ⑤
$e_b = e_g$ $e_c \approx -37 I_C e_g R_L$ when $A_v < 50$ $e_c = -e_g A_v$ See $-A_v$		② ③ ④ ⑤ ⑥
$e_b \approx e_g / [(R_S / h_{ie}) + 1]$ $e_b = e_g / [(R_S / Z_i) + 1]$ $e_c \approx -(e_g h_{fe} R_L) / (R_S + h_{ie}^{-1})$ when $A_v < 50$ $e_c = -(e_g A_i R_L) / (R_S + Z_i^{-1})$ See $-A_i, Z_i$		② ③ ④ ⑤

e Notes:

- ① $\text{---}\text{O}\text{---}$ is the graphic symbol for an alternating current generator. (an infinite impedance signal source)
- ② Transistors must be biased into an active region.
- ③ Approximations apply to high beta silicon small-signal transistors while exact formulas apply to all bipolar transistors.

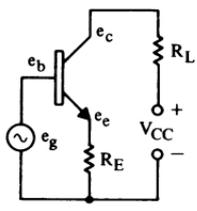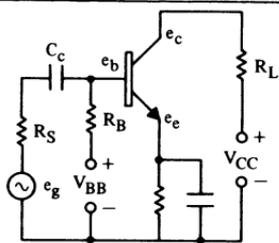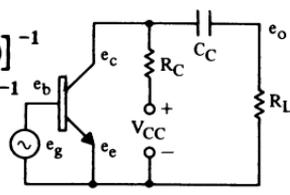e_b e_c e_e Small-Signal Voltages	Applicable Notes	
$e_b = e_g$ $e_c \simeq -(e_g R_L)/R_E$ when $R_E \gg (37I_C)^{-1}$ $e_c = -e_g A_v$ See $-A_v$ $e_e \simeq e_b$ when $R_E \gg (37I_C)^{-1}$		② ③ ④ ⑤ ⑥
$e_b \simeq e_g / [R_S(R_B^{-1} + h_{ie}^{-1}) + 1]$ $e_b = e_g / [R_S(R_B^{-1} + Z_i^{-1}) + 1]$ $e_c \simeq -37I_C e_b R_L$ $e_c = -e_b A_v$ See $-A_v, Z_i$ $e_e = 0$		② ③ ④ ⑤
$e_b = e_g$ $e_c \simeq -(e_g h_{fe}) [h_{ie}(R_C^{-1} + R_L^{-1})]^{-1}$ $e_c = -(e_g A_i) [Z_i(R_C^{-1} + R_L^{-1})]^{-1}$ $e_e = 0$ $e_o = e_c$ See $-A_i, Z_i$		② ③ ④ ⑤ ⑥

e Notes:

- ④ Formulas apply to pnp transistors as well as the npn transistors shown. Reverse emitter arrow and power supply polarity for pnp transistors.
- ⑤ Transistor parameters will vary with collector voltage and temperature as well as collector current.
- ⑥ The resistance of base bias resistors must be included in all calculations where the generator source resistance is of significance.

e_N

Noise Voltage

$$e_{N(\text{th})} = \sqrt{4K_B T_K R_S \overline{BW}} \quad \text{Thermal noise voltage}$$

$$(e_{N(\sqrt{\text{Hz}})})_{\text{th}} = \sqrt{4K_B T_K R_S} \quad \text{Thermal noise voltage per root hertz}$$

$$e_{N(s)} = I_e \sqrt{2q I_B \overline{BW}} \quad \text{Transistor shot noise (white noise)}$$

$$(e_{N(\sqrt{\text{Hz}})})_s = I_e \sqrt{2q I_B} \quad \text{Transistor shot noise per root hertz}$$

$$e_{N(1/f)} = \sqrt{(e_N)_{\text{TR}}^2 - (e_N)_s^2} \quad \text{Both same bandwidth}$$

$$(e_N)_{\text{TR}} = \sqrt{(e_N)_s^2 + (e_N)_{1/f}^2} \quad \text{Both same bandwidth}$$

Total Equivalent Input Noise Voltage

$$(e_N)_t = \left([R_S (i_N)_{\text{TR}}]^2 + (e_N)_{\text{TR}}^2 + (e_N)_{\text{th}}^2 \right)^{\frac{1}{2}}$$

(all same BW)

Wideband Total Noise Voltage Output

$$e_{N(\text{OUT})} = A_v \left([R_S (i_N)_{\text{TR}}]^2 + (e_N)_{\text{TR}}^2 + (e_N)_{\text{th}}^2 \right)^{\frac{1}{2}}$$

(all same BW)

Total Spot Noise Voltage Output

$$e_{N(\text{OUT})} = A_v \left([R_S (i_N)_{\text{TR}}]^2 + (e_N)_{\text{TR}}^2 + 4K_S T_K R_S \right)^{\frac{1}{2}}$$

all noise terms are for 1 Hz BW at same frequency

e_N Notes: K_B = Boltzmann constant ($1.38 \cdot 10^{-23}$ J/K); T_K = Kelvin temperature ($^{\circ}\text{C} + 273.15$); q = Charge of electron ($1.6 \cdot 10^{-19}$); \overline{BW} = Bandwidth, See—Opamp, $\overline{BW}_{\text{NOISE}}$; I_e = Internal transistor dynamic emitter resistance; $I_e \approx .027/I_C$; $(i_N)_{\text{TR}}$ = Transistor noise current equivalent input; A_v = stage voltage amplification; I_B, I_C = dc base and collector currents.

F to g_{me}

Small-Signal
Definitions

F – See–NF, See also–F, Passive Circuits

F_N – See–NF

f_c = Symbol for cutoff frequency. (The half power or 3 dB down frequency)

See– f_c , Opamps

f_T = Gain-bandwidth product. The frequency at which the common emitter small-signal forward current transfer ratio falls to unity.

(dc biased for large signal)

f_t = Same as f_T except biased for small-signal.

$f_{\alpha b}$ – See– f_{hfb}

$f_{\alpha e}$ – See– f_{hfe}

f_{hfb} = Common base small-signal forward current transfer ratio cutoff frequency with output ac shorted.

f_{hfe} = Common emitter small-signal forward current transfer ratio cutoff frequency with output ac shorted.

G_{pb} = Common base small-signal average power gain.

G_{pe} = Common emitter small-signal average power gain.

$G_{pe(\text{conv})}$ = Common emitter conversion gain.

g_{me} = Common emitter small-signal transconductance.

$$h_{fb} \quad h_{fc} \quad h_{fe}$$

Small-Signal
Forward
Current
Ratios

h_{fb} = Common base small-signal forward current transfer ratio with output ac shorted.

h_{fb} = Small signal alpha (α)

$$h_{fb} = i_c/i_e$$

$$h_{fb} = h_{fe}/(h_{fe} + 1)$$

h_{fc} = Common collector (emitter follower) small-signal forward current transfer ratio with output ac shorted.

$$h_{fc} = i_e/i_b$$

$$h_{fc} = h_{fe} + 1$$

h_{fe} = Common emitter small-signal forward current transfer ratio with output ac shorted.

h_{fe} = Small-signal beta (β).

$$h_{fe} = i_c/i_b$$

$$h_{fe} = \alpha/(1 - \alpha)$$

$$h_{fe} = h_{fb}/(1 - h_{fb})$$

$$h_{fe} = h_{fc} - 1$$

$$h_{fe} = h_{fb}h_{fc}$$

h_{fe} = Common emitter current gain when output is ac shorted.

$h_{fe} = (i_c h_{ie})/e_{be}$ when output is ac shorted.

h_{ib}	h_{ic}	h_{ie}	Small-Signal Input Impedance
----------	----------	----------	---

h_{ib} = Common base small-signal input impedance with output ac shorted.

$$h_{ib} = e_e/i_e$$

$$h_{ib} = h_{ie}/(h_{fe} + 1)$$

$$h_{ib} = r_e + [r_b/(h_{fe} + 1)]$$

$$h_{ib} \approx 1/(37I_C)$$

h_{ic} = Common collector (emitter follower) small-signal input impedance with output ac shorted.

$$h_{ic} = h_{ie} \quad (\text{since emitter is ac shorted})$$

h_{ie} = Common emitter small-signal input impedance with output ac shorted.

$$h_{ie} = e_b/i_b$$

$$h_{ie} = h_{ic}$$

$$h_{ie} = h_{ib}(h_{fe} + 1)$$

$$h_{ie} = r_b + r_e(h_{fe} + 1)$$

$$h_{ie} \approx h_{fe}/(37I_C)$$

$$h_{ie} \approx (26.7h_{fe})/(1000I_C)^{.78}$$

Approximations apply to small-signal silicon transistors.

h_{ob}	h_{oc}	h_{oe}	Small-Signal Output Admittance
----------	----------	----------	---

h_{ob} = Common base small-signal output admittance with input ac open-circuited.

$h_{ob} = i_c/e_c$ when emitter is ac open-circuited
(constant current emitter supply)

$h_{ob} = y_{ob}$ (y_{ob} is generally used at high frequencies)

$h_{ob} \approx h_{oe}/(h_{fe} + 1)$

$h_{ob} = r_c + r_b$

$h_{ob} = \left([h_{oe}^{-1}(h_{fe} + 1)] + [h_{ie} - h_{re}h_{oe}^{-1}(h_{fe} + 1)] \right)^{-1}$

h_{oc} = Common collector (emitter follower) small-signal output admittance with input ac open-circuited.

$h_{oc} = h_{oe}$ (since input is open-circuited)

h_{oe} = Common emitter small-signal output admittance with input ac open-circuited.

$h_{oe} = i_c/e_c$ when base is ac open-circuited
(constant current base supply)

$h_{oe} = y_{oe}$ (y_{oe} is generally used at high frequencies)

$h_{oe} = h_{oc}$

$h_{oe} = (h_{fe} + 1)/r_c$

$h_{oe} \approx 20 \mu\text{S} \quad (50 \text{ k}\Omega)^{-1}$ when $I_C \approx 1 \text{ mA}$, $V_{CE} > 5 \text{ V}$,
 $T \approx 25^\circ\text{C}$

h_{rb} h_{rc} h_{re} **Small-Signal Reverse Voltage Ratios**

h_{rb} = Common base small-signal reverse voltage transfer ratio with input ac open-circuited.

$h_{rb} = e_e/e_c$ when emitter is ac open-circuited
(constant current emitter supply)

$$h_{rb} = r_b/(r_b + r_c)$$

$$h_{rb} \approx [h_{ie}h_{oe}(h_{fe} + 1)^{-1}] - h_{re}$$

$$h_{rb} = \left[\left([h_{ie}h_{oe}(h_{fe} + 1)^{-1}] - h_{re} \right)^{-1} + 1 \right]^{-1}$$

h_{rc} = Common collector small-signal reverse voltage transfer ratio with input ac open-circuited.

$$h_{rc} = 1 - h_{re}$$

h_{re} = Common emitter small-signal reverse voltage transfer ratio with input ac open-circuited.

$h_{re} = e_b/e_c$ when base is ac open-circuited
(constant current base supply)

$$h_{re} = r_e h_{oe}$$

$$h_{re} = [r_e(h_{fe} + 1)]/r_c$$

$$h_{re} \approx 1.33 \cdot 10^{-6} h_{fe} \quad \text{when } I_C \approx 1 \text{ mA} \quad \text{and} \quad V_{CE} > 5 \text{ V}$$

Note: h_{re} is very V_{CE} sensitive at low voltage. h_{re} typically is very nonlinear over large variations of I_C .

I – See—I, Static (DC) Symbols
See also—I, Passive Circuits

i = Small-signal current.

i_b = Small-signal base current.

i_c = Small-signal collector current.

i_e = Small-signal emitter current.

i_g = Small-signal generator (source) current.

i_{in} = Small-signal input current

i_N = Noise current.

$i_{N(\text{TRANSISTOR})}$ = That portion of the input equivalent internal transistor noise which is proportional to the external resistance in shunt with the input (source resistance)

i_N Notes:

- ① $i_{N(\text{TRANSISTOR})}$ does not include the thermal noise or the excess noise currents of the effective external source resistance.
 - ② $i_{N(\text{TRANSISTOR})}$ may be included in the $e_{N(\text{TRANSISTOR})}$ (TOTAL) if a source resistance (R_S) has been specified.
 - ③ Much of the confusion regarding noise voltages and noise currents results from the difficulty in proper identification of the symbols for the various noise voltages and noise currents.
 - ④ See also— e_N , NF; See also— V_n , i_n , Opamps; See also— E_N , I_N , N_{th} , NI, Passive Circuits
-

i_o = Small-signal output current.

i_p = Small-signal peak current.

i_b i_c i_e	Small-Signal Transistor Currents	Applicable Notes
$i_b = i_g$ $i_c = i_g h_{fe}$ $i_e = i_g (h_{fe} + 1)$		① ② ③ ④ ⑤
$i_b = i_g$ $i_c \simeq i_g h_{fe}$ $i_c = i_g A_i$ See $-A_i$ $i_e \simeq i_g (h_{fe} + 1)$ $i_e = i_g (A_i + 1)$ See $-A_i$		① ② ③ ④ ⑤
$i_b \simeq e_g / h_{ie}$ $i_b = e_g / Z_i$ See $-Z_i$ $i_c \simeq (e_g h_{fe}) / h_{ie}$ $i_c = (e_g A_v) / R_L$ See $-A_v$ $i_e \simeq i_c$ $i_e = [e_g (A_v + 1)] / R_L$ See $-A_v$	 	② ③ ④ ⑤ ⑥

i Notes:

- ① $\text{---}\text{O}\text{---}$ is the graphic symbol for an infinite impedance alternating current generator. (any very high impedance source)
- ② Transistors must be biased into an active region.
- ③ Approximations apply to high beta small-signal silicon transistors. Exact formulas apply to all bipolar transistors.

i_b i_c i_e i_o	Small-Signal Currents	Applicable Notes
$i_b \simeq e_g / [(h_{fe} R_E) + h_{ie}]$ $i_b = e_g / Z_i \quad \text{See } -Z_i$ $i_c \simeq e_g / R_E$ <p style="text-align: center;">when $R_E \gg (37I_C)^{-1}$</p> $i_c = (e_g A_v) / R_L \quad \text{See } -A_v$ $i_e \simeq i_c \quad \text{when } h_{fe} > 100$ $i_e = [e_g (A_v + 1)] / R_L \quad \text{See } -A_v$		② ③ ④ ⑤ ⑥
$i_b \simeq e_g / (R_S + h_{ie})$ $i_b = e_g / (R_S + Z_i)$ $i_c \simeq (e_g h_{fe}) / (R_S + h_{ie})$ $i_c = (e_g A_i) / (R_S + Z_i) \quad \text{See } -A_i, Z_i$ $i_e \simeq i_c \quad \text{when } h_{fe} > 100$		② ③ ④ ⑤
$i_c \simeq e_g / R_E$ <p style="text-align: center;">when $R_E \gg (37I_C)^{-1}$</p> $i_o \simeq (e_g / R_E) [(R_L / R_C) + 1]^{-1}$ $i_o = i_c / [(R_L / R_C) + 1]$		② ③ ④ ⑤ ⑥

i Notes:

- ④ All formulas apply to pnp transistors as well as the npn transistors shown. Reverse emitter arrow and power supply polarity for pnp transistors.
- ⑤ Transistor parameters will vary with collector voltage and temperature as well as with collector current.
- ⑥ The resistance of base bias resistors must be included properly in all calculations where the signal source resistance is of significance.

NF

Noise Figure

NF = Symbol for noise figure (also known as noise factor)
(other symbols include F and F_N)

NF = 1. The ratio (usually in decibels) of the output signal-to-noise power to the input signal-to-noise power.

2. The ratio in decibels of the total output noise to that portion of the output noise generated thermally by the input termination resistance.

$$NF = 20 \left[\log \left(e_{ni} / e_{nR'} \right) \right]$$

$$NF = 20 \left(\log \left[e_{no} / (e_{nR'} A_v) \right] \right)$$

$$\text{where } e_{nR'} = e_{nR} / \left[(R_S / r_i) + 1 \right]$$

$$\text{and } e_{nR} = \sqrt{4K_B T_K \overline{BW}}$$

See also $-e_{N(\text{out})}$ and BW_{NOISE} , Opamp

NF Notes:

- ① A_v = Voltage amplification, \overline{BW} = Average bandwidth (rms bandwidth), e_{ni} = Input equivalent total noise voltage, e_{no} = Output noise voltage, e_{nR} = Thermal noise voltage of source resistance, K_B = Boltzmann constant ($1.38 \cdot 10^{-23}$ J/°K), r_i = Transistor input resistance, R_S = Source resistance (the total effective resistance presented to the transistor input), T_K = Kelvin temperature (°C + 273.15), log = Base 10 logarithm.
- ② The standard noise temperature (T_N) of the source resistance is 290 K (16.85°C) if unspecified.

See also $-e_N$ Notes

V V

Definitions

V = The unit symbol for volt.

See—V, Passive Circuits

V = The quantity symbol for voltage.

See—V, Static (dc) Parameters

See also—V, Opamp

Note: A definite trend exists towards the elimination of E and e as symbols for voltage. At present, E and e predominate in passive circuits, V and v predominate in operational amplifiers, V has superseded E in dc transistor parameters and e predominates for ac transistor parameters.

v = Symbol for small signal voltage.

See—e See also—V, Opamp

v_b — See— e_b

v_c — See— e_c

v_e — See— e_e

v_g — See— e_g

v_i — See— e_i

v_N — See— e_N (V_N —See—V, Opamp)




v_o — See— e_o

v_p — See— e_p

v_s — See— $e_{N(s)}$

v_t — See— e_t

$v_{1/f}$ — See— $e_{N(1/f)}$

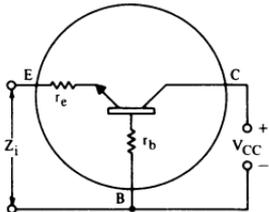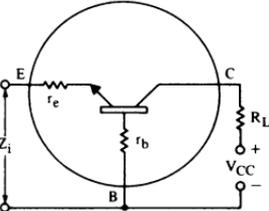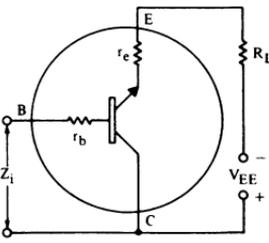Small Signal Low Frequency Common Base	Z_i	Input Impedance	Applicable Notes
$Z_i \approx 1/(37I_C)$ $Z_i = r_e + r_b(h_{fe} + 1)^{-1}$ $Z_i = h_{ib}$ $Z_i = h_{ie}/(h_{fe} + 1)$		③ ④ ⑤ ⑥ ⑨	
$Z_i \approx 1/(37I_C)$ (when $A_v < 50$) $Z_i \approx h_{ie}/(h_{fe} + 1)$ (when $A_v > 50$) $Z_i = (h_{oe}R_L + 1)/(h_{oe}R_L + 1 + h_{fe})$		③ ④ ⑤ ⑥ ⑧ ⑨	
Small Signal Low Frequency Common Collector	Z_i	Input Impedance	Applicable Notes
$Z_i \approx h_{fe}R_L$ $Z_i \approx h_{ie} + R_L(h_{fe} + 1)$ $Z_i = h_{ie} + [(h_{fe} + 1)/(h_{oe} + R_L^{-1})]$		③ ④ ⑤ ⑥ ⑧ ⑨	

Z NOTES

Z Notes:

- ① $\text{---}\text{---}\text{---}$ is the graphic symbol for an infinite impedance alternating current generator. (an ac current source) In practice, any very high impedance source of current may be substituted.
 - ② $\text{---}\text{---}$ is the graphic symbol for a zero impedance signal generator. (an ac voltage source) In practice, any very low impedance signal source may be substituted.
 - ③ Approximations apply to high beta, small signal, silicon transistors. Exact formulas apply to all bipolar transistors.
 - ④ Formulas apply to pnp as well as the npn transistors shown. Reverse emitter arrow and power supply polarity for pnp transistors.
 - ⑤ All internal dynamic resistances (r_b , r_c , r_e) vary with operating conditions. Primarily, r_e varies with emitter current while r_c varies primarily with temperature and collector voltage. Usually, r_b is assumed to be a non-varying resistance.
 - ⑥ All biasing resistors connected in shunt with an input are effectively in parallel with the input impedance. The equivalent resistance of all parallel quantities must be used in all calculations where the source resistance becomes significant. $Z_i' = (Z_{i(R)}^{-1} + R_1^{-1} + R_2^{-1})^{-1}$
 - ⑦ $x^{-1} = 1/x$
 - ⑧ In the usual circuit where the collector is capacitor coupled to a load, the series collector resistor and the load resistance are effectively in parallel and the net parallel resistance should be used in all ac calculations. $R_L = (R_1^{-1} + R_2^{-1})^{-1}$
 - ⑨ Base biasing is not shown but transistors must be biased into an active region.
 - ⑩ Collector bias and base bias circuits are not shown, however the transistors must be biased into an active region.
-

Small-Signal
Low Frequency
Common Emitter


Z_i

Input
Impedance

$$Z_i \approx h_{fe}/(37I_C)$$

$$Z_i = r_b + r_c(h_{fe} + 1)$$

$$Z_i = h_{ie}$$

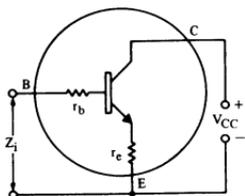

③
④
⑤
⑥
⑨


$$Z_i \approx h_{fe}/(37I_C)$$

(when $A_v < 50$)

$$Z_i \approx h_{ie}$$

(when $A_v < 50$)
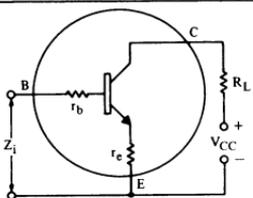
$$Z_i = h_{ie} + h_{re}h_{fe}h_{oe}^{-1} [(R_L h_{oe}^{-1} + 1)^{-1} - 1]$$



③
④
⑤
⑥
⑦
⑧
⑨

$$Z_i \approx h_{fe} [(37I_C)^{-1} + R_E]$$

(when $A_v < 50$)


$$Z_i \approx h_{ie} + h_{fe} R_E$$

$$Z_i = \frac{[(h_{fe} + 1)(R_E + r_e)]}{\left([h_{fe}^{-1}(r_c R_L^{-1} + 1) + 1]^{-1} + 1 \right)}$$

$$r_b = h_{ie} - h_{re}h_{oe}^{-1}(h_{fe} + 1)$$

$$r_c = h_{oe}^{-1}(h_{fe} + 1)$$

$$r_e = h_{re}h_{oe}^{-1}$$

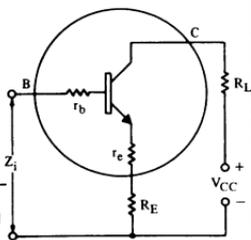

③
④
⑤
⑥
⑦
⑧
⑨

Small-Signal
Low Frequency
Common Base

Z_o

Output
Impedance


Applicable
Notes

$$Z_o \approx (h_{fe} + 1)/h_{oe}$$

$$Z_o = r_c + r_b$$

$$Z_o = 1/h_{ob}$$
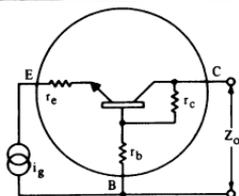
$$Z_o = \left([h_{oe}^{-1}(h_{fe} + 1)] + [h_{ie} - h_{re}h_{oe}^{-1}(h_{fe} + 1)] \right)^{-1}$$




①
③
④
⑤
⑥
⑦
⑩

$$Z_o \approx 200 \text{ k}\Omega$$

(when $I_C \approx 1 \text{ mA}$)

$$Z_o \approx h_{oe}^{-1} + h_{oe}^{-1}(50I_C h_{ie} h_{fe}^{-1} - 1)^{-1}$$
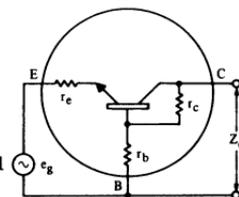
$$Z_o = h_{oe}^{-1} \left([(h_{ie} h_{oe} / h_{fe} h_{re}) - 1]^{-1} + 1 \right)$$




②
③
④
⑤
⑥
⑦
⑩

$$Z_o < R_B + (h_{fe}/h_{oe})$$

$$Z_o = h_{oe}^{-1} + h_{fe} h_{oe}^{-1} \left([(R_B + r_b)/(R_g + r_e)] + 1 \right)^{-1}$$

$$r_e = h_{re} h_{oe}^{-1}$$

$$r_b = h_{ie} - r_e(h_{fe} + 1)$$

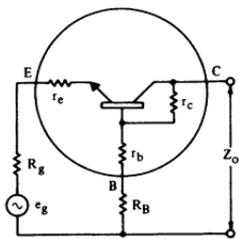

②
③
④
⑤
⑥
⑦
⑩

Small-Signal
Low Frequency
Common Collector

Z_o


Output
Impedance

Applicable
Notes

$Z_o \approx 50 \text{ k}\Omega$
(when $I_C \approx 1 \text{ mA}$, $V_{CE} > 5$)

$Z_o = 1/h_{oc}$

$Z_o = 1/h_{oe}$

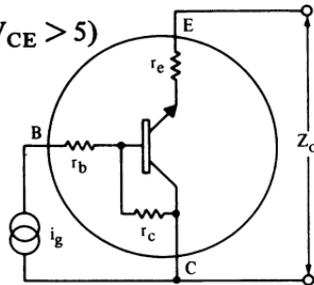


①
③
④
⑤
⑥
⑩

$Z_o \approx 1/(37I_C)$

$Z_o \approx h_{ie}/h_{fe}$

$Z_o = r_e + r_b(h_{fe} + 1)^{-1}$

$Z_o = h_{ie}/(h_{fe} + 1)$

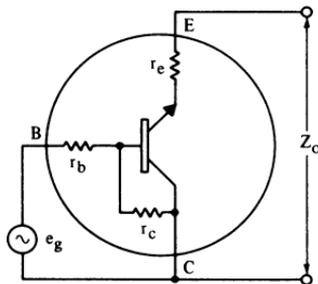


②
③
④
⑤
⑥
⑦
⑩

$Z_o \approx (37I_C)^{-1} + (R_g/h_{fe})$

$Z_o \approx (R_g + h_{ie})/h_{fe}$

$Z_o = r_e + [(R_g + r_b)/(h_{fe} + 1)]$

$Z_o = (h_{ie} + R_g)/(h_{fe} + 1)$

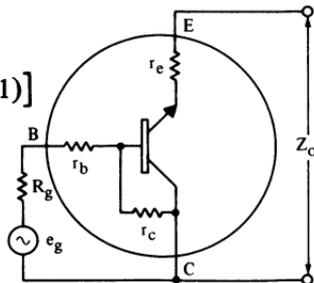

②
③
④
⑤
⑥
⑦
⑩

Small-Signal
Low Frequency
Common Emitter

Z_o

Output
Impedance

Applicable
Notes


$$Z_o \approx 50 \text{ k}\Omega$$

(when $I_C \approx 1 \text{ mA}$)

$$Z_o \approx r_c / (h_{fe} + 1)$$

$$Z_o = r_c (h_{fe} + 1)^{-1} + r_e$$

$$Z_o = 1/h_{oe}$$

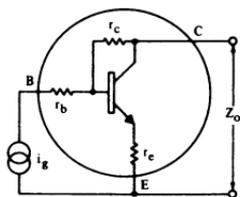


①
③
④
⑤
⑥
⑦
⑩

$$Z_o \approx 200 \text{ k}\Omega$$

(when $I_C \approx 1 \text{ mA}$)

$$Z_o \approx h_{oe}^{-1} + h_{oe}^{-1} (50 I_C h_{ie} h_{fe}^{-1} - 1)^{-1}$$
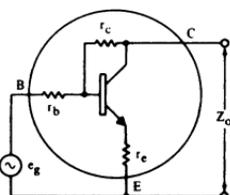
$$Z_o = h_{oe}^{-1} \left(\left[(h_{ie} h_{oe} / h_{fe} h_{re}) - 1 \right]^{-1} + 1 \right)$$




②
③
④
⑤
⑥
⑦
⑩

$$Z_o < R_g + (h_{fe} / h_{oe})$$

$$Z_o = (h_{oe}^{-1} + h_{fe} h_{oe}^{-1}) / \left(\left[(R_g + r_b) / (R_E + r_e) \right] + 1 \right)$$
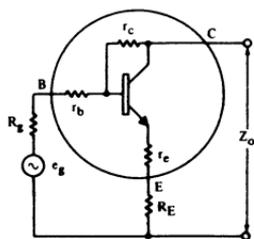
$$r_e = h_{re} h_{oe}^{-1}, \quad r_b = h_{ie} - r_e (h_{fe} + 1)$$



②
③
④
⑤
⑥
⑦
⑩

α β

Small-Signal Current Ratios

α = Greek script letter alpha.

α = Symbol for small signal common base forward current transfer ratio with output ac shorted.

Note: Although alpha predominates as the "oral symbol," the equivalent hybrid parameter h_{fb} has almost completely superseded α as the accepted written symbol. See— h_{fb}

$$\alpha = h_{fb}$$

$$\alpha = h_{fe}/(h_{fe} + 1) \quad \text{or} \quad (h_{fe}^{-1} + 1)^{-1}$$

$$\alpha = i_c/i_e \quad \text{when} \quad e_c \text{ and } e_b = 0$$

$$\alpha \simeq 1$$

$\alpha < 1$ exception—very early point contact transistors

β = Greek script letter beta.

β = Symbol for small signal common emitter forward current transfer ratio with output ac shorted.

Note: Although beta predominates as the "oral symbol," the equivalent hybrid parameter h_{fe} has almost completely superseded β as the accepted written symbol. See— h_{fe}

$$\beta = h_{fe}$$

$$\beta = i_c/i_b \quad \text{when} \quad e_c \text{ and } e_e = 0$$

$$\beta = (i_c h_{ie})/e_b \quad \text{when} \quad e_c \text{ and } e_e = 0$$

$$\beta = h_{fb}/(h_{fb} - 1) \quad \text{or} \quad (h_{fb}^{-1} - 1)^{-1}$$

$$\beta = (i_e/i_b) - 1 = [(i_e/i_c) - 1]^{-1}$$

SECTION THREE

OPERATIONAL AMPLIFIERS

3.1 DEFINITIONS

A

Opamp Symbol Definitions

- A – See— A_V
a – See— α (alpha)
 A_{CL} – See— A_{VCL}
 A_{DIFF} – See— A_{VD}
 $A_{(f_0)}$ – See— A_{V_0}
 A_I = Large signal current amplification (gain). Also dc current gain in direct coupled circuits.
 A_i = Small signal current amplification (gain).
 A_{IAC} = Alternating current amplification (gain).
 A_{IDC} = Direct current amplification (gain).
 A_m = Gain margin. The reciprocal of the open-loop voltage amplification at the lowest frequency at which the open-loop phase shift is such that the output is in phase with the inverting input. See also— θ_m
 A_o – See— A_{V_0}
 A_{OL} – See— A_{VOL}
 A_V = Large signal voltage amplification (gain). Also dc voltage gain in direct coupled circuits.
 A_v = Small signal voltage amplification (gain).
 A_{VAC} = AC voltage amplification (gain).
 A_{VD} = Large signal differential voltage amplification (gain).
 A_{VDC} = DC voltage amplification (gain).
 A_{VCL} = Large signal closed-loop voltage amplification. The large signal voltage gain of an opamp stage with inverse feedback. Applies also to dc voltage gain in direct coupled circuits. This symbol is used in place of A_V only when the meaning would otherwise be confusing. See also— A_V
-

A B

Opamp Symbol Definitions

- A_{vcl} = Small-signal closed-loop voltage amplification. The small-signal voltage gain of an operational amplifier stage with inverse feedback applied. See also— A_v
- A_{vo} = Midband voltage amplification. The voltage amplification at the midband or reference frequency (f_0)
- A_{vd} = Differential voltage amplification
- A_{vol} = Large-signal open-loop voltage amplification. The large-signal voltage gain of an operational amplifier before application of inverse feedback.
- A_{vol} = Small-signal open-loop voltage amplification. The small-signal voltage gain of an operational amplifier (opamp) before application of inverse feedback.
-
- B = See— BW , See also — B , Passive Circuits.
- B_1 = See — $BW_{(A_v=1)}$
- B_{OM} = Maximum output swing bandwidth.
- BW = Bandwidth
- $BW_{(-3\text{ dB})}$ = Half power or 3 dB down bandwidth
- $BW_{(-3\text{ dB})}$ = f_0/Q (bandpass filters)
- $BW_{(A_v=1)}$ = Unity gain bandwidth. The range of frequencies within which the open-loop voltage amplification is greater than unity. Unity gain bandwidth is also known as gain-bandwidth product but, is only approximately equal to actual gain-bandwidth product. (See— GBW , f_T). The unity-gain bandwidth is equal to the product of the small-signal closed-loop voltage amplification (A_{vcl}) and the closed-loop flat-response bandwidth only when the open-loop voltage gain is inversely proportional to frequency in the frequency range between the top bandpass frequency and the unity-gain frequency.
-

BW_{NOISE}

Noise
Bandwidth

BW_{NOISE} = Bandwidth used to compute noise output. (other symbols include: \bar{B} , B, BW, BW_n)

BW_{NOISE} = Noise bandwidth with zero noise contribution from frequencies above or below bandwidth limits

BW_{NOISE} = Noise bandwidth measured with filters having nearly rectangular response curves. (“cliff” or “brick wall” filters)

Effective Noise Bandwidth from zero to the 3 dB
Down Frequency using Butterworth Filters

$BW_{NOISE} = 1.57 BW_{-3dB}$ 6 dB per octave filter

$BW_{NOISE} = 1.11 BW_{-3dB}$ 12 dB per octave filter

$BW_{NOISE} = 1.05 BW_{-3dB}$ 18 dB per octave filter

$BW_{NOISE} = 1.025 BW_{-3dB}$ 24 dB per octave filter

$BW_{NOISE} = BW_{-3dB}$ ∞ dB per octave filter

Notes:

6 dB per octave = 20 dB per decade
(first order filter)

12 dB per octave = 40 dB per decade
(second order filter)

dB per decade = 3.333 (dB per octave)

dB per octave = .3 (dB per decade)

B C D

Opamp Symbol Definitions

$$BW_{(A_v = 1)} = [A_{vc1}] / [BW_{c1}]$$

BW_{c1} = Small signal flat response bandwidth.

$$BW_{c1} \simeq [BW_{(A_v = 1)}] / A_{vc1}$$

BW_{NOISE} – See preceding page

BW_p = Power bandwidth. See also—PBW

$$BW_p = SR / [\pi V_{opp}]$$

C_B = Bypass capacitor. Bootstrap capacitor.

C_C = Coupling capacitor.

C_I, C_i, C_{IN}, C_{in} = Input capacitance.

$CMRR$ = Common mode rejection ratio. The ratio of differential voltage gain to common mode voltage gain.

C_O, C_o, C_{out} = Output capacitance.

C_p = Parallel capacitance.

C_T, C_t = Total capacitance.

D – See—THD

d = Damping factor. (other symbols include α and δ) The reciprocal of the Q factor in most applications. A symbol used in high and low pass filter formulas where the 3 dB down definition of Q factor is not applicable. Note: Nearly everyone understands the meaning of Q factor regardless of the difficulty with an all encompassing definition. See—Q

$$d = 1/Q$$

D E

Opamp Symbol Definitions

dB = Decibel. A logarithmic ratio of power, voltage or current. See—dB editorial on preceding page. See also—dB, Passive Circuits

$$\text{dB} = 10 [\log (P_o/P_i)]$$

$$\text{dB} = 20 [\log (V_o/V_i)]$$

$$\text{dB} = 20 [\log (I_o/I_{in})]$$

dBf = Power in decibels referenced to one femtowatt. (fW = 10^{-15} W)

dBm = Power in decibels referenced to one milliwatt.

dB_{re} — See—dB_{REF}

dB_{REF} = Reference level in decibels.

dBV = 1. Voltage in decibels referenced to 1 volt rms.

2. Voltage ratio in decibels. (not recommended)

E — See—V See also—E, Passive Circuits

e — See—V See also—e, Transistors and e, Passive Circuits

e_g, e_i, e_{in} — See—V_g, V_i, V_s

E_N, E_n, e_N, e_n etc — See—V_n

— See also—e_N, NF, Transistors

— See also—E_N, NI, Passive Circuits

Note:

The transition from E to V as the quantity symbol for voltage is complete in this opamp section. The symbol E was used exclusively in the passive circuit section while the transistor section used V for dc voltages only. It is expected that eventually the symbol V will replace E for all electronic usage.

F G

Opamp Symbol Definitions

F = Noise factor. Noise factor is also known as noise figure (NF). F may represent the average or the spot noise factor. See—NF, Transistors

\bar{F} = Average noise factor.

f_1 — See—B1, $BW_{(A_v = 1)}$

$F(f)$ = Spot noise factor.

f_c = Cutoff frequency. The frequency at which the output falls to one-half power or 3 dB down from maximum.

f_{IN}, f_{in} = Input frequency

f_o = Reference, center, midband, resonant, oscillation or output frequency.

f_p = Frequency of pole. (poles and zeros)

f_r = Resonant frequency.

f_T, f_t = Unity gain frequency. The frequency at which the open-loop voltage gain falls to unity. Has exactly the same meaning as $BW_{(A_v = 1)}$ in all integrated circuit opamps. See— $BW_{(A_v = 1)}$

f_z = Frequency of zero. (poles and zeros)

G = Conductance See—G, Passive Circuits

GBW = Gain-bandwidth product. The product of the small signal voltage amplification (A_v) and the bandwidth (BW). See— $BW_{(A_v = 1)}$

$GBW \simeq$ or $= BW_{(A_v = 1)}$ or f_T

Depending upon the exact definition.

G H I

Opamp Symbol Definitions

G_m = Large-signal forward transconductance.

g_m = Small-signal forward transconductance.

G_p = Large-signal power gain.

G_p = Small-signal power gain.

G_v = Voltage gain. See also A_v

H_o = Passband gain.

I_+ = Positive dc supply current

I_- = Negative dc supply current

I_A = Amplifier dc supply current

I_{ABC} = Amplifier bias current.

I_B = Bias current

I_{CC} = Positive dc supply current

I_D = Device dc supply current

I_{D+} = Device positive dc supply current

I_{D-} = Device negative dc supply current.

I_{DG} = Non-inverting input grounded current.

I_{DO} = Non-inverting input open current.

I_{EE} = Device negative dc supply current.

I_g = Small-signal generator (source) current.

I_{IB} = Input bias current

I_{IN}, I_{in} = Input signal current

**Opamp
Symbol
Definitions**

I_{IO} = Input offset current. The difference between the bias currents into the two input terminals of an opamp with the output at zero volts.

$|I_{IO}|$ = The magnitude of input offset current. See also $-I_{IO}$

I_n = Device equivalent-input noise current. That component of device total equivalent-input noise which varies with the external source resistance and therefore is properly represented by an infinite impedance current source in parallel with the input terminals.

$$I_n = \sqrt{I_{ns}^2 + I_{nf}^2}$$

i_n - See $-I_n$

I_{nf} = Device equivalent-input 1/f noise current. That part of I_n which has a spectral density which is inversely proportional to frequency.

I_{nR} = Thermal (white) noise current of resistance See $-I_N$, Passive Circuits

I_{ns} = Device equivalent-input shot (white) noise current.

I_O = Large signal output current.

I_o = Small signal output current.

I_{O+} = Large signal positive swing output current.

I_{O-} = Large signal negative swing output current.

I_{OPP} = Peak to peak output current.

I_{OS} = Short-circuit output current. The maximum output current available from the device with the output shorted to ground or either supply.

I J K

Opamp Symbol Definitions

I_p	= Large signal peak current
I_p, I_{pk}, I_{peak}	= Small signal peak current
I_s	= 1. Source current. See— I_g, I_{in} 2. Shot noise current. See— I_{ns}
I_{SC}	— See I_{OS}
I_T, I_t, i_T	= Total current
I_{TH}	= Threshold current.
<hr/>	
J, j	— See— J, j , Passive Circuits
<hr/>	
K	= 1. Kelvin temperature. ($^{\circ}C + 273.15$) 2. Voltage gain See— A_v 3. Any constant.
k	= 1. Any constant 2. Boltzmann constant.
k_B	= Boltzmann constant. ($1.38 \cdot 10^{-23} J/^{\circ}K$)
k_{CMR}	= Common mode rejection ratio. See— $CMRR$
k_{SVR}	= Supply voltage rejection ratio. The absolute value of the ratio of change in supply voltage to the change in input offset voltage. The reciprocal of $PSRR$ or PSS . See also— $PSRR, PSS,$ k_{SVS}
k_{SVR}	= $ \Delta V_{CC}/\Delta V_{IO} $
k_{SVS}	= Supply voltage sensitivity. The absolute value of the ratio of change in input offset voltage to the change in supply voltages producing it. The reciprocal of k_{SVR} . See Also— $PSRR, PSS, k_{SVR}$
k_{SVS}	= $ \Delta V_{IO}/\Delta V_{CC} $

L M N

Opamp Symbol Definitions

- L = 1. Inductance. See—L, Passive Circuits
2. Level. Signal level in decibels with respect to a noted reference level.
-

mAdc = Direct current milliampere.

MAG = Maximum available (power) gain.

MUF = Maximum usable frequency.

mW/°C = Milliwatt per degree Celsius.

MΩ, M = Megohm

N = 1. Noise. See also— V_n , I_n .

2. Noise power. See— P_N , Passive Circuits

3. Number. A pure number or a ratio.

NF — See—F, See also—NF, Transistors

NI — See—NI, $E_{N(EX)}$, Passive Circuits.

N_p — See— P_N , Passive Circuits

N_{th} — See— P_N , Passive Circuits, See also— V_{nR}

nV/\sqrt{Hz} , $nV/(Hz)^{\frac{1}{2}}$, $nV/\sqrt{\sim} =$

Nanovolts per hertz or nanovolts per root hertz or nanovolts per root cycle. The spot noise voltage in nanovolts. The noise voltage in nanovolts for a bandwidth of one hertz at a specified frequency.

$nV/\sqrt{Hz} = (V_{n(nV)})/\sqrt{BW}$

only when the noise voltage has constant spectral density. (only when the noise voltage is white noise)

O P

Opamp Symbol Definitions

- os, OS = Overshoot
- P_C = 1. (Device) power consumption.
2. Collector power dissipation. See $-P_C$, Transistors
- P_D = 1. Device power dissipation
2. Power dissipation.
- PF, p.f. = Power factor. See—pf, Passive Circuits
- pF = Picofarad. (10^{-12} farad)
- P_i, P_{IN}, P_{in} = Input power.
- P_N = Noise power. See— P_N , Passive Circuits.
- P_o = Output power.
- PSRR = Power supply rejection ratio. The absolute value of the ratio of the change in input offset voltage to the change in power supply voltage producing it. This ratio is usually in $\mu V/V$ or in dB. When all are given in decibels and disregarding the sign of the decibel ratio, K_{SVR} , K_{SVS} , PSS, PSRR, VSRR, $|\Delta V_{CC}/\Delta V_{IO}|$ and $|\Delta V_{IO}/\Delta V_{CC}|$ are all equal. It is hoped that the industry will soon standardize on only one of these symbols.
- P_{SRR} = See—PSRR
- PSS = Power supply sensitivity. See—PSRR
- PSS \pm — See—PSS
- PSS+ = Positive power supply sensitivity. See—PSRR
- PSS- = Negative power supply sensitivity. See—PSRR
- P_T, P_t, P_{tot} = Total power.
-

Q R

Opamp Symbol Definitions

Q = Q factor. In simple bandpass filters, the ratio of the resonant frequency to the 3 dB down bandwidth. In highpass or lowpass filters where the 3 dB down definition is not applicable, the reciprocal of the damping factor (d). See also—Q, Passive Circuits.

Note: The Q factor is also known as the merit, quality, storage, magnification and energy factor. There is no known simple definition of Q which will encompass all of the applications. The general meaning of the term appears to be understood but the exact meaning, except in a few applications, is open to interpretation.

$$Q = 1/d$$

$$Q = f_o/BW_{(-3\text{ dB})}$$

$$Q = f_r/BW_{(-3\text{ dB})}$$

Q_L = Loaded Q factor.

Q_o = Q factor at center or reference frequency (f_o).

Q_u = Unloaded Q factor.

R = Resistance See—R, Passive Circuits

r = Small signal (dynamic) resistance. Any resistance of a semiconductor device which may be non-linear and therefore produce a different value between dc and small signal measurements.

R_F = Feedback Resistor

R_g = Generator resistance. See— R_S

R

Opamp Symbol Definitions

$R_I = 1$. Input resistor. (Not recommended)
2. Large signal input resistance. (Not recommended)

R_i = Small signal input resistance. See also— Z_i

r_i = Device small signal input resistance.

r_{id} = Device differential input resistance.

R_{IN} = Large signal input resistance.

R_{in} — See— R_i

r_{in} — See— r_i

R_L = Load resistance.

R_O = Large signal output resistance.

R_o = Small signal output resistance. See also— Z_o

r_o = Device small signal output resistance.

R_{OPT} = Optimum resistance. e.g. $R_{s(OPT)} = V_n/I_n$

R_{OUT}, R_{out} — See— R_O, R_o

R_P, R_p = Parallel resistance.

r_p = Dynamic plate resistance (vacuum tube) (anode resistance (r_a) is also used).

R_S = Source resistance.

R_s = Series resistance.

R_T, R_t = Total resistance.

R_{th} — See— R_θ , Transistors

R_θ — See— R_θ , Transistors

S T

Opamp Symbol Definitions

S = 1. Sensitivity.

2. Signal. See—sig

s = Laplace transform function.

S+ — See—PSS+

S- — See—PSS-

S± — See— k_{SVS} , PSRR, PSS

sig = Signal. Any electrical, visual, audible or other indication used to convey information.

S/N = Signal to noise ratio.

SR = Slew rate. The closed-loop average-time rate-of-change of output voltage for a step-signal input. A specification used to determine the maximum combination of frequency and peak-to-peak output signal without the distortion associated with rise and fall time.

SR = π PBW V_{OPP}

SR_($A_v = 1$) = Slew rate when closed-loop voltage amplification is unity.

T = 1. Temperature. ($^{\circ}$ C unless noted)

2. Time constant. See—T, Passive Circuits

3. Time. See—t

4. Loop gain. (A_{VOL}/A_{VCL})

t = 1. Time. Time or period in seconds

2. Temperature. See—T

T_A = Ambient temperature. The average temperature of the air in the immediate vicinity of the device.

TC = Temperature coefficient.

T_C = Case temperature.

T

Opamp Symbol Definitions

TC_{IIO} = Temperature coefficient of input offset current. The ratio of the change in input offset voltage to the change in free-air temperature when averaged over a specified temperature range.

$$TC_{IIO} = \left| \frac{[(I_{IO})_1 - (I_{IO})_2]}{[(T_A)_1 - (T_A)_2]} \right|$$

TC_{VIO} = Temperature coefficient of input offset voltage. The ratio of the change in input offset voltage to the change in free-air temperature when averaged over a specified temperature range.

$$TC_{VIO} = \left| \frac{[(V_{IO})_1 - (V_{IO})_2]}{[(T_A)_1 - (T_A)_2]} \right|$$

t_f = Fall time. The time required for the trailing edge of an output pulse to fall from 90% to 10% of the final voltage in response to a step function pulse at the input.

THD = Total harmonic distortion.

THD = $\sqrt{V_2^2 + V_3^2 + \dots + V_n^2} / V_1$ where V_1 is a sine-wave input signal (fundamental) and V_2 through V_n are the 2nd through nth harmonic respectively.

T_{high} = High temperature.

T_K = Kelvin temperature. ($^{\circ}C + 273.15$)

T_L = Lead temperature.

T_{low} = Low temperature.

t_{os} = Time of output short-circuit.

t_p, t_{pd} = Pulse duration

t_{PLH} — See— t_r

T U V

Opamp Symbol Definitions

t_r = Rise time. The time required for an output voltage step to rise from 10% to 90% of the final value.

t_{setlg} = Settling time. See— t_{tot}

T_{stg} = Storage temperature.

t_{THL} — See— t_f

t_{tot} = Total response time. (Settling time) The time between a step-function change of the input signal level and the instant at which the magnitude of the output signal reaches for the last time a specified level range.

U = Teletypewriter or computer printer substitute for Greek letter mu (μ).

u = Typewriter substitute for Greek letter mu (μ).

V = Symbol for the voltage quantity as well as for the volt unit.

V_A = DC or rms large signal voltage.

V_a = Small signal rms signal voltage.

v_A = Instantaneous large signal voltage.

v_a = Instantaneous small signal voltage.

+V = Any positive dc voltage.

-V = Any negative dc voltage.

V+ = Positive polarity power supply voltage.

V

Opamp Symbol Definition

- V_- = Negative polarity power supply voltage.
- V_{AC} – See– V_{AC} (V_{AC} or V_{ac} = unit-symbol)
- V_{AC} = Alternating current voltage.
- V_{BB} = Base power supply voltage or base bias voltage.
- V_{CC} = Collector supply voltage. (positive polarity in all present IC opamps)
- $+V_{CC}$ = Positive polarity collector supply voltage.
- V_{CM} = Common mode voltage.
- V_{DC} – See– V_{DC} (V_{DC} or V_{dc} = unit symbol)
- V_{DC} = Direct current voltage.
- V_{EE} = Emitter supply voltage. (negative polarity in all present IC opamps)
- $-V_{EE}$ = Negative polarity emitter supply voltage.
- V_g = Generator (signal) rms voltage.
- V_I = Input voltage range.
- V_i = Input (signal) rms voltage.
- v_i = Instantaneous input voltage.
- V_{IC} – See– V_{ICM}
- V_{ICM} = Common mode input voltage.
- V_{ICR} = Common mode input voltage range.
- V_{ID} = Differential input voltage.
-

V

Opamp Symbol Definitions

- V_{IDR} = Differential input voltage range.
- V_{IN} = Large signal input voltage.
- V_{in} = Small signal input voltage.
- V_{IO} = Input offset voltage. The dc voltage that must be applied between the input terminals to force the quiescent dc output to zero.
- $|V_{IO}|$ = The magnitude of V_{IO} . See $-V_{IO}$
- V_{IOR} = Input offset voltage adjustment range.
- V_{IR} = Input voltage range. See also $-V_I$
- V_n – See following page
- V_O = Large signal output voltage.
- V_o = Small signal output voltage.
- v_O = Instantaneous large signal output voltage.
- v_o = Instantaneous small signal output voltage.
- $V_{O(CM)}$ = Common mode output voltage.
- V_{OM} = Maximum output voltage.
- V_{OM+} , V_{OM+} = Maximum positive output voltage.
- V_{OM-} , V_{OM-} = Maximum negative output voltage.
- V_{OO} = Output offset voltage.
- V_{OOS} – See $-V_{OO}$
- V_{OPP} = Peak to peak output voltage.
- V_{OP-P} , $V_{O(p-p)}$ – See $-V_{OPP}$
-

V_n

Opamp Symbol Definitions

- V_n = 1. Any rms noise voltage
2. The equivalent-input rms noise voltage of that part of the device total noise which is independent of source resistance.

Notes:

1. The other parts of total equivalent-input noise voltage (V_{ni}) are the voltages developed by device noise current through the source resistance and that developed thermally by the source resistance.
2. Noise voltages vary with bandwidth. Wide band noise may be any bandwidth but is usually specified for a 10.7 kHz bandwidth. Narrow-band noise voltages are for a bandwidth of 1 Hz and usually are specified in nV. (nV/\sqrt{Hz})

$\overline{v_n^2}$ = The mean square noise voltage

V_{nf} = 1/f rms noise voltage

V_{ng} = Generator (noise generator) rms noise voltage

V_{ni} = The total equivalent input rms noise voltage

$V_{ni} = V_{no}/A_v$

$V_{ni} = \sqrt{BW(V_n^2 + I_n R_S + 4K_B T_K R_S)}$ See— BW_{NOISE}

V_{no} = The total output rms noise voltage

$V_{no} = A_v V_{ni}$

V_{nR} = Source resistance (R_S) rms thermal noise voltage.

V_{ns} = 1. Device rms shot noise voltage

2. See— V_{nR}

V_{nt} = 1. Any rms thermal noise voltage

2. See— V_{nR}

V_{nT} = Device total equivalent-input rms noise voltage including V_n and ($I_n R_S$)

V Z

Opamp Symbol Definitions

V_{OR} = Output voltage range.

V_{OUT} - See $-V_O'$

V_p, V_{pk}, V_{peak} = Peak voltage.

V_{p-p} = Peak to peak voltage.

V_{PS} = Power supply voltage.

V_Q = Quiescent voltage.

V_S = 1. Signal voltage
2. Source voltage
3. Supply voltage

$+V_S, V_{S+}$ = Positive polarity supply voltage.

$-V_S, V_{S-}$ = Negative polarity supply voltage.

Z_i = Small signal closed-loop input impedance.

z_i = Device small signal open-loop input impedance.

Z_{i+} = Small signal closed-loop non-inverting input impedance.

$Z_{i+} = (r_i A_{vol})/A_{vcl}$

Z_{i-} = Small signal closed-loop inverting input impedance.

$Z_{i-} \approx$ Series input resistor R.

$Z_{i-} = R + [R_F/(A_{vol} + 1)]$

z_{ic} = Device common mode input impedance. The parallel sum of the small signal open-loop impedance between each input terminal and ground.

Z to Ω

Opamp
Symbol
Definitions

z_{id} = Device differential input impedance.

Z_o = Small signal closed-loop output impedance.

$$Z_o = z_o / [(A_{VOL} / A_{VCL}) + 1]$$

z_o = Device small signal output impedance.

z_{od} = Differential output impedance. (opamps with differential output)

α – See–d etc.

α_{IIO} – See– TC_{IIO}

α_{VIO} – See– TC_{VIO}

$\Delta I_{IO} / \Delta T$ – See– TC_{IIO}

$\Delta V_{CC} / \Delta V_{IO}$ – See– k_{SVR} etc.

$\Delta V_{IO} / \Delta T$ – See– TC_{VIO}

$\Delta V_{IO} / \Delta V_{CC}$ – See– k_{SVS} etc.

δ – See–d etc.

θ_m = Phase margin. The absolute value of the open-loop phase shift between the output and the inverting input at the frequency at which the modulus of the open-loop amplification is unity.

ϕ_m – See– θ_m

ω_c = Cutoff (–3dB) angular velocity (angular frequency).

ω_o = Reference angular velocity (angular frequency).

ω_r = Resonant angular velocity (angular frequency).

OPERATIONAL AMPLIFIERS

SECTION 3.2
FORMULAS
AND
CIRCUITS

DC or Audio
Frequency


**AMPLIFIER
CURRENT
INPUT**

Large or Small
Signal

$$A_i = i_o/i_{in}$$

$$A_i = -R_F/R_L$$


$$e_o = -i_{in} R_F$$

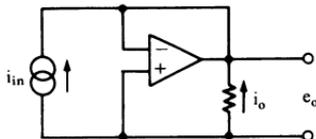

$$A_i = i_o/i_{in}$$

$$A_i = R_1/R_L$$


$$e_o = i_{in} R_1$$

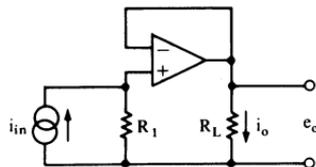

$$A_i = i_o/i_{in}$$

$$A_i = (R_1/R_L)(R_F/R_B + 1)$$

$$e_o = i_{in} R_1 (R_F/R_B + 1)$$

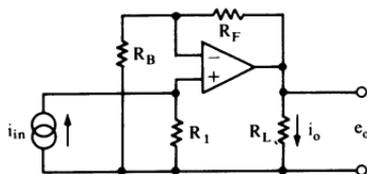


**NEGATIVE RESISTANCE
CURRENT AMPLIFIER**

When $R_1 R_B / R_F R_L - 1 > 0$:

$$A_i = 1 + (R_1 R_B / R_F R_L - 1)^{-1}$$

$$i_o = i_{in} + R_F / R_B R_1$$

$$e_o = R_L (i_{in} + R_F / R_B R_1)$$

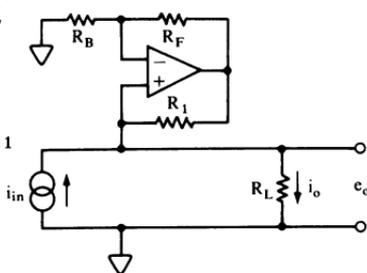


**Constant DC
Current**
**Variable R_L
and/or Voltage**

**AMPLIFIER
CURRENT
OUTPUT**

**Precision HV
Current Sources**

1/2 LM358
Opamp

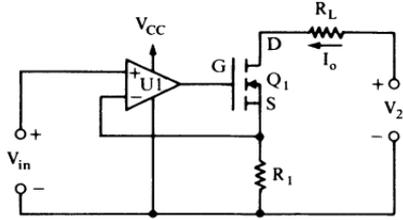

$$I_0 = V_{in}/R_1$$

$$P_{D(Q1)} = I_0 V_2 - I_0^2(R_L + R_1)$$

$$R_{L(MIN)} = V_2/I_0 - (P_{D(MAX)}/I_0^2) - R_1$$

$$V_{2(MAX)} = P_{D(MAX)}/[I_0 + I_0(R_L + R_1)]$$

$Q_1 = \text{VN2410M}$ for
 $V_2 \leq 200\text{V}$
and up to
 $P_D = .75\text{W}$
($P_D \leq 12\text{W}$
when
 $Q_1 = \text{VN2406D}$
with heatsink)

Example


Opamp = 1/2 LM358

$Q_1 = \text{MJE350 (Heatsink)}$

$Q_2 = \text{VN2410L}$

$V_2 = 150$

$I_0 = V_{in}/R_1$

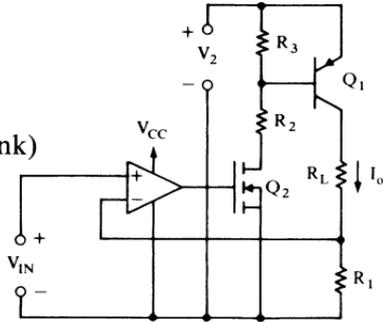

$$P_{D(Q1)} = I_0 V_2 - I_0^2(R_L + R_1)$$

$$R_{L(MIN)} = V_2/I_0 - (P_{D(MAX)}/I_0^2) - R_1$$

$$V_{2(MAX)} = P_{D(MAX)}/[I_0 + I_0(R_L + R_1)]$$

DC or Audio

Frequency


Large or Small
Signal

AMPLIFIER
CURRENT
OUTPUT

Bilateral
Current Source

$i_o = -1$ mA per volt
input with values shown

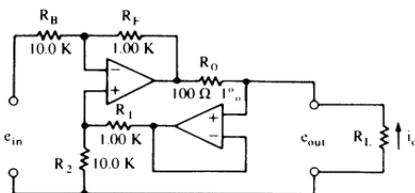Oscillation may occur
when $R_L > 27K$ (worst
case 1% tolerance
resistors)



$$Z_o = R_o / (1 - [(R_F/R_B + 1)/(R_1/R_2 + 1)])$$


(+ Z_o and - Z_o are both valid when $R_L < -Z_o$)

When $R_1 = R_F$ and $R_2 = R_B$:

$$i_o = -e_{in} R_F / R_o R_B, A_v = -R_L R_F / R_o R_B, Z_o = \infty$$

$i_o = -2$ mA per volt
input with values shown

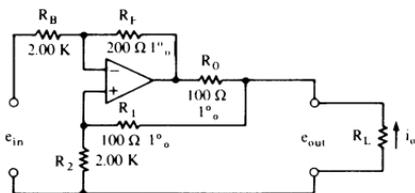Oscillation may occur
when $R_L > 13.9K$ (worst
case 1% tolerance
resistors)



$$Z_o = [R_o(R_1/R_2 + 1)] / [(R_o + R_1)/R_2] - R_F/R_B$$

(+ Z_o and - Z_o are both valid when $R_L < -Z_o$)

When $R_1 + R_o = R_F$ and $R_2 = R_B$:

$$i_o = -e_{in} R_F / R_o R_B, A_v = -R_L R_F / R_o R_B, Z_o = \infty$$

Recommended opamp = 1/2 NE5532 for up to 25 mA
peak output current

Low Frequency
Input Impedance


**AMPLIFIER
INPUT
IMPEDANCE**

Z_i

$$Z_i \approx R_B$$

$$Z_i = R_B + [R_F / (A_{VOL} + 1)]$$
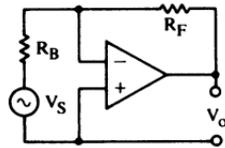
$$Z_i = R_B + [R_F / ([\log^{-1}(A_{VOL(dB)} / 20)] + 1)]$$




$$Z_i \approx [r_i A_{VOL}] / A_{VCL}$$

$$Z_i = \frac{r_i (A_{VOL} + 1)}{(R_F / R_B) + 1}$$

$$Z_i = r_i \left(\log^{-1} [(A_{VOL(dB)} - A_{VCL(dB)}) / 20] + 1 \right)$$

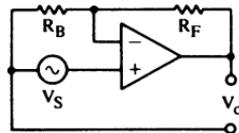
$$A_{VCL(dB)} = 20 \left(\log [(R_F / R_B) + 1] \right)$$



See Also—Amplifier, Voltage, Negative Resistance

AMPLIFIER OUTPUT IMPEDANCE

Z_o

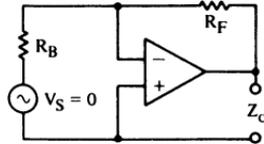


$$Z_o \simeq (r_o A_{VCL}) / A_{VOL}$$

$$Z_o = \frac{r_o}{(A_{VOL} / A_{VCL}) + 1}$$

$$Z_o \simeq (r_o R_F) / (R_B A_{VOL})$$

$$Z_o = \frac{r_o}{[(R_B A_{VOL}) / R_F] + 1}$$
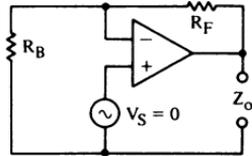
$$A_{VOL} = \log^{-1} [A_{VOL(dB)} / 20]$$



See Also—Amplifier, Current Output

DC or Audio
Frequency


**AMPLIFIER
VOLTAGE
DIFFERENTIAL**

Large or Small
Signal

BALANCED TO
UNBALANCED

$$A_V = -R_F/R_B$$


when $R_1 = R_B$ and $R_2 = R_F$

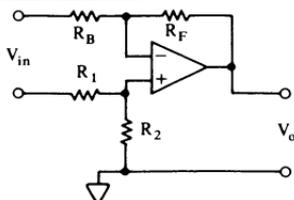

BALANCED TO
BALANCED

$$A_V = -2R_F/R_B$$

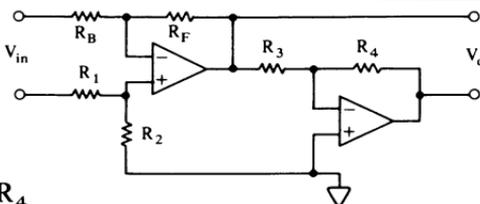when $R_1 = R_B$,
 $R_2 = R_F$ and $R_3 = R_4$




$$A_{V1} = -R_F/R_B$$

$$A_{V2} = 1 + [R_F(R_B^{-1} + R_X^{-1})]$$

$$V_0 = V_2 A_{V2} - V_1 A_{V1}$$

when V_1 and V_2 are same freq. & phase

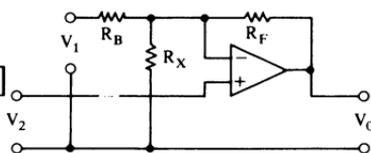

$$|V_0| = \sqrt{(V_1 A_{V1})^2 + (V_2 A_{V2})^2}$$


when V_1 and V_2 are
different frequencies and
 V_0, V_1 and $V_2 = V_{rms}$

TWO-PHASE LEVEL CONTROL

$A_V = 0$ at pot center

$A_V = -1$ at CW pot.

$A_V = +1$ at CCW pot.

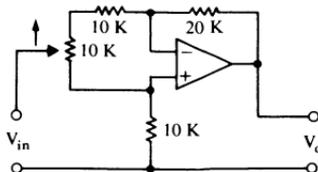


DC or Audio
Frequency

**AMPLIFIER
VOLTAGE
INVERTING**

Large or Small
Signal

$$A_V = -V_o/V_{in}$$
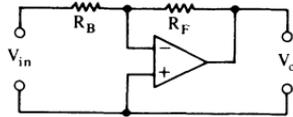
$$A_V = -R_F/R_B \quad \text{when } A_{VOL} \gg A_V$$




$$A_V = -\left[\frac{(R_B + R_B/A_{VOL})}{R_F} + A_{VOL}^{-1}\right]^{-1}$$

where $A_{VOL} = A_{VOL}$ at A_V freq.

$$A_V = -V_o/V_S$$

$$A_V = -R_F/(R_S + R_B)$$


when $A_{VOL} \gg A_V$

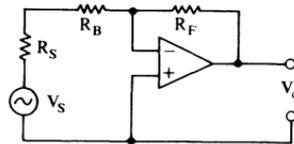

$$Z_{in} = R_B \quad \text{when } A_{VOL} \gg A_V$$

POSITIVE AND NEGATIVE FEEDBACK

(decreases input impedance)

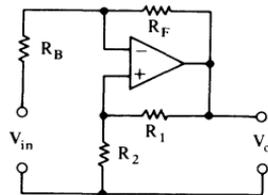


$$A_V = -V_o/V_{in}$$

$$A_V = -\left[1 + \frac{(R_1/R_2)}{\left[\frac{(R_1 R_B/R_F R_2)}{R_2} - 1\right]}\right]$$

when $(R_1 R_B/R_F R_2) - 1 > 0$

and $A_{VOL} \gg A_V$

$$A_V = -V_o/V_{in}$$

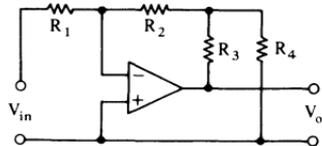


$$A_V = -\left[\frac{R_2 + R_3 + (R_2 R_3/R_4)}{R_1}\right] \quad \text{when } A_{VOL} \gg A_V$$

Negative
Impedance

**AMPLIFIER
VOLTAGE
NEGATIVE RESISTANCE**

Two-Way
Amplifier

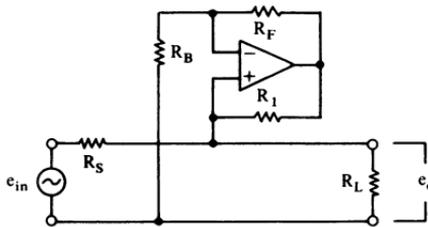

When $[R_1 R_B (R_S^{-1} + R_L^{-1}) / R_F] - 1 > 0$:

$$A_v = [1 + R_S (R_L^{-1} - R_F / R_B R_1)]^{-1}$$

$$Z_{in} = R_S + (R_L^{-1} - R_F / R_B R_1)^{-1}$$

$$Z_o = (R_L^{-1} + R_S^{-1} - R_F / R_B R_1)^{-1}$$


DC or Audio
Frequency

**AMPLIFIER
VOLTAGE
NON-INVERTING**

Large or Small
Signal

$$Z_{in} = R_{in}(1 + A_{VOL}/A_V)$$

$$Z_o = R_o/(1 + A_{VOL}/A_V)$$

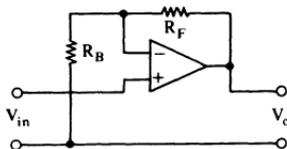

$$A_V = 1 + R_F/R_B \quad \text{when } A_{VOL} \gg A_V$$

$$A_V = 1 + \left(\left[(R_B + R_B/A_{VOL})/R_F \right] + A_{VOL}^{-1} \right)^{-1}$$


(A_{VOL} at A_V freq.)

INFINITE INPUT IMPEDANCE

$$Z_{in} \approx \infty \quad \text{when } R_1 \ll A_{VOL} R_{in}$$

$$Z_{in} = (A_{VOL} + 1)R_{in}$$
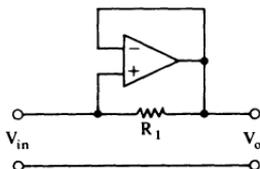
$$A_V = 1 \quad \text{when } f_{max} \ll \text{GBW}$$




NEGATIVE INPUT IMPEDANCE

When $(R_1 R_B / R_F R_2) - 1 > 0$
and $A_{VOL} \gg A_V$:

$$Z_{in} = R_2 - (R_1 R_B / R_F)$$

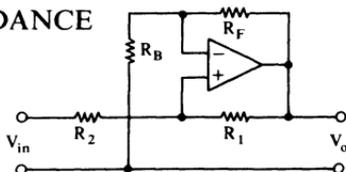
$$A_V = 1 + \left(\left[1 + (R_1 / R_2) \right] / \left[(R_1 R_B / R_F R_2) - 1 \right] \right)$$



$$A_V = V_o / V_{in}$$

$$A_V = 1 + \left[R_2 + R_3 + (R_2 R_3 / R_4) \right] / R_1$$

when $A_{VOL} \gg A_V$

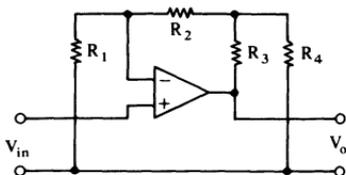


AMPLIFIER VOLTAGE SUMMING

Large or Small
Signal

$$A_{V1} = -R_F/R_1$$

$$A_{V2} = -R_F/R_2$$

$$A_{VN} = -R_F/R_N$$

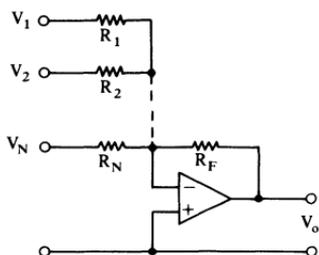

$$V_0 = \sqrt{(V_1 A_{V1})^2 + (V_2 A_{V2})^2 + \dots + (V_N A_{VN})^2}$$


where V_0, V_1, V_2 and $V_N = V_{rms}$

Minimum required peak to peak capability = $4\sqrt{2} V_{0rms(MAX)}$

Input to input isolation = $20 \log [(A_{VOL}/A_V) R_{in(OPAMP)}]$ dB
when inputs driven from current source

Input to input isolation $\approx \infty$ dB when inputs driven from opamp sources.

MIXER CIRCUIT

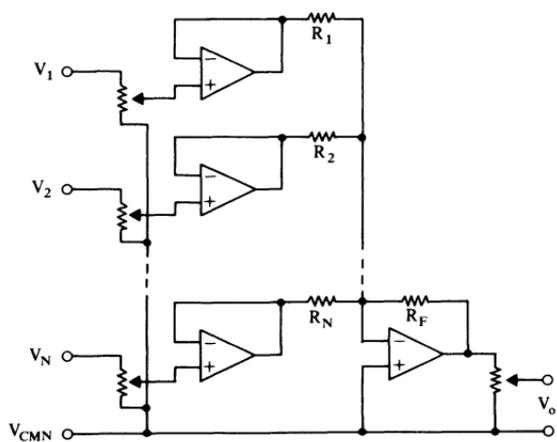

BANDWIDTH GENERAL


BW

$BW = BW_{-3\text{dB}} =$ Half-power or 3 dB down bandwidth unless otherwise specified (half power = -3.0103 dB).

AMPLIFIER BANDWIDTH

$$BW \simeq (B_1\sqrt{2})/(A_{vcl})$$

$$BW \simeq (R_B B_1\sqrt{2})/R_F$$

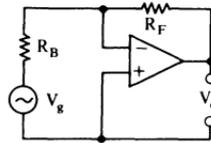

See Also—Opamp, Power bandwidth

BANDPASS FILTER BANDWIDTH

$$BW = f_{2(-3\text{dB})} - f_{1(-3\text{dB})}, f_0 = QBW, f_0 \approx f_1 + BW/2$$

$$BW = f_0/Q, f_1 = -BW/2 + \sqrt{BW^2/4 + f_0^2}, f_2 = f_1 + BW$$

$$f_1 \approx f_0 - BW/2, f_2 \approx f_0 + BW/2$$


BANDPASS FILTER

$$BW = (\pi CR_2)^{-1}$$

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

$$A_{VO} = R_2/2R_1$$


$$Q = \sqrt{R_2/4R_1}$$

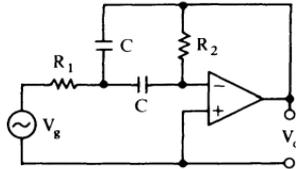


See Also—Filter, Bandpass

COMPARATOR WITH AND WITHOUT HYSTERESIS


INVERTING

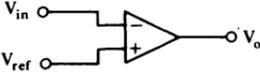


NON-INVERTING

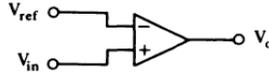

WITH HYSTERESIS

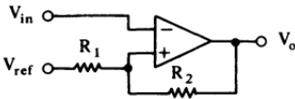


WITH HYSTERESIS

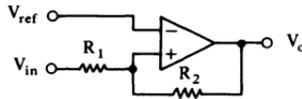

$$(V_{in})_{th} = V_{ref}/(R_1/R_2 + 1) \quad V_{ref} = (V_{in})_{th}(R_1/R_2 + 1)$$

Add diode in series with R_2 for unidirectional hysteresis

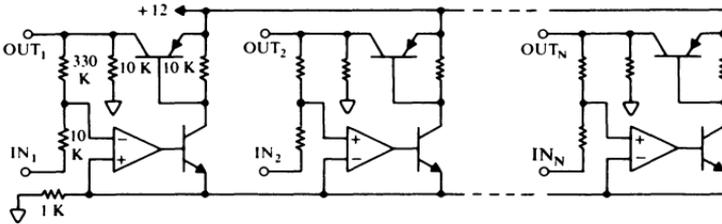**HIGHEST-INPUT-LEVEL ONE-OF-N CIRCUIT
(HIGHEST OF +.5 TO +10V_{dc} INPUTS HAS
ONLY OUTPUT)**




Opamps = 1/2 LM358 or 1/4 LM324

NPN transistors = 2N2222 etc, PNP transistors = 2N2907 etc


Hysteresis from 330K resistors minimizes hunting

DETECTOR PEAK


POSITIVE PEAK DETECTOR

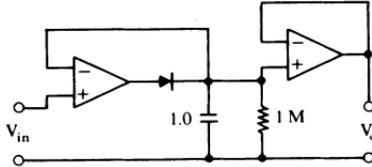

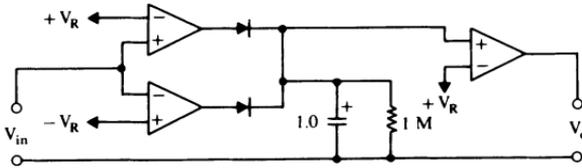DOUBLE ENDED LIMIT OR FULL-WAVE PEAK DETECTOR



FULL-WAVE PEAK DETECTOR

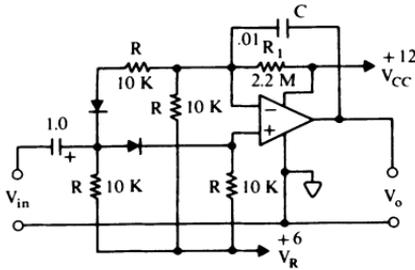

$V_{o(\text{MAX})}$ when $V_{in} \geq 1V_{p-p}$ sinewave
Sensitivity may be decreased by decreasing R_1


See Also—Comparator and Rectifier

INDUCTOR ACTIVE


$$L = C_1 R_1 (R_2 - R_1)$$

$$Q = 2\pi f_0 C_1 (R_2 - R_1)$$

$$R_S = R_1, \quad R_P = R_2$$

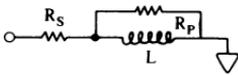


equivalent

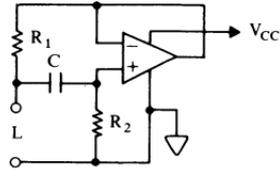

When $R_F = R_B$ and $R = R_1$:

$$L = R_1 RC$$

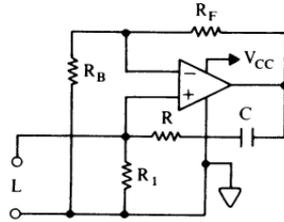$Q = \infty$ (Reduce the value of R_1 slightly if necessary to prevent oscillation)




When $C_1 = C_2$ and $R_2 = R_3$:

$L = R_1 R_2 C = 1\text{H}$ with values shown

$$Q = \infty$$

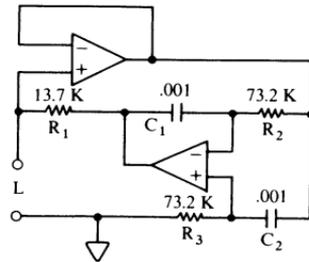
Due to component tolerances, oscillation may occur when connected to a high Q external circuit.




With only a high Q capacitor connected to the L input and R_3 tweaked to the edge of oscillation, circuit Q is very close to infinite.

**FILTER
ALLPASS
(PHASE SHIFTER)**

Unity Gain
All Frequencies

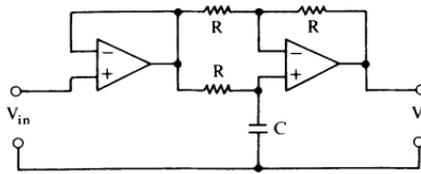


$$(\theta_e)_{out} + (\theta_e)_{in} = 2 \tan^{-1} (2\pi fRC)^{-1}, \quad |A_V| = 1$$

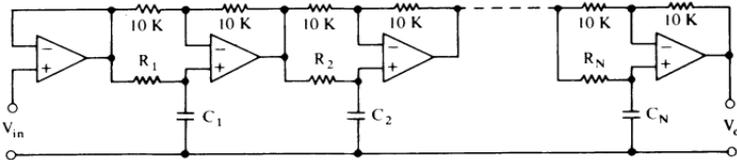

$$(\theta_e)_{out} = 2[\tan^{-1} (2\pi fR_1C_1)^{-1}] + 2[\tan^{-1} (2\pi fR_2C_2)^{-1}] \\ \dots + 2[\tan^{-1} (2\pi fR_NC_N)^{-1}]$$

BROADBAND, FOUR-PHASE-OUTPUT CIRCUIT

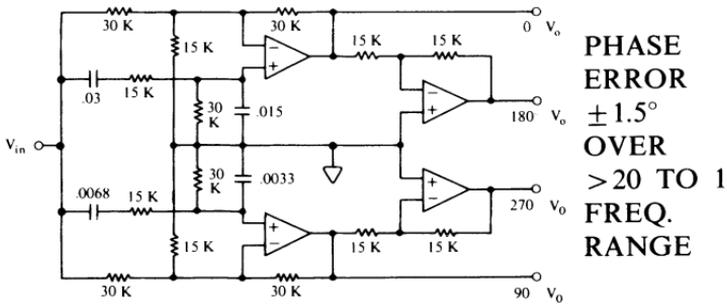


**PHASE
ERROR
 $\pm 1.5^\circ$
OVER
> 20 TO 1
FREQ.
RANGE**

Output phase is relative to other outputs; not to input

Second order

FILTER BANDPASS BIQUAD

Simplified
Formulas

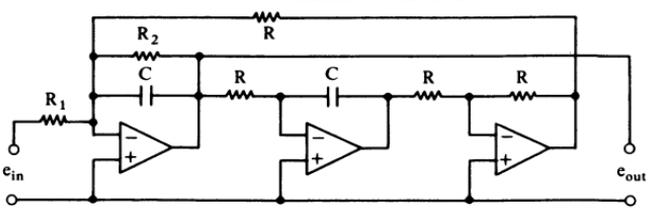


$$A_{VO} = R_2/R_1$$

$$f_0 = (2\pi RC)^{-1}$$

$$Q = R_2/R$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [R_2/(R_1 \sqrt{1 + Q^2 [(f/f_0) - (f_0/f)]^2})]$$

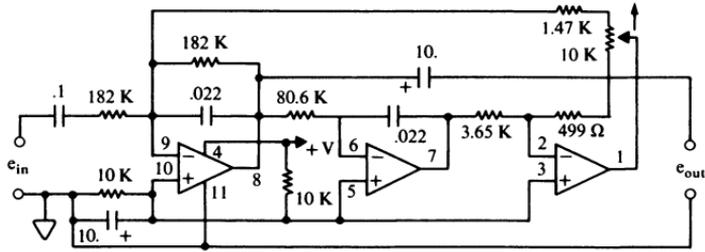VARIABLE FREQUENCY, CONSTANT BANDWIDTH BIQUAD BANDPASS FILTER



$A_{VO} = 1$ Opamp = 3/4 TL084 or equiv.

$f_0 = 100 \text{ to } 1000 \text{ Hz}$.022 μF caps are 5% low D
such as polystyrene or NPO

$BW_{-3dB} = 40 \text{ Hz}$

$Q = 25 \text{ at } 1000 \text{ Hz}$ 10K pot is 5% multiturn

Second Order

FILTER BANDPASS MULTIPLE FEEDBACK


General
Formulas

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

$$A_{VO} = R_2/2R_1, \quad R_2/R_1 = 2A_{VO}$$

$$Q = \sqrt{R_2/4R_1}$$


$$R_2/R_1 = 4Q^2$$

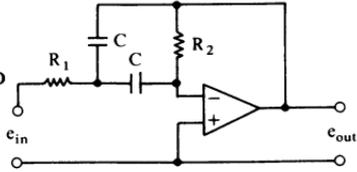

$$|e_{out}/e_{in}|_{dB} = 20 \log [R_2 / (2R_1 \sqrt{1 + Q^2 [(f/f_0) - (f_0/f)]^2})]$$

Without compensation, a Q of 10 is maximum for results within 5% of formula. At a Q of 5, an f_0 of 5 kHz is maximum for the same accuracy. When typical Mylar capacitors are used, a Q of 7.5 is maximum for 5% accuracy.

LOWER GAIN VERSION

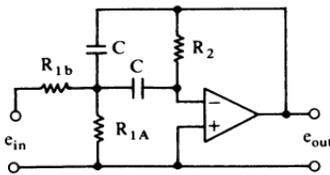

$$A_{VO} = R_2/2R_{1B}$$

$$f_0 = [2\pi C\sqrt{R_2/(R_{1A}^{-1} + R_{1B}^{-1})}]^{-1}$$


$$Q = \sqrt{R_2(R_{1A}^{-1} + R_{1B}^{-1})}/4$$

$$R_2 = 2Q/(2\pi f_0 C)$$

$$R_{1B} = R_2/2A_{VO}$$

$$R_{1A} = R_2/(4Q^2 - 2A_{VO})$$

HIGH GAIN, HIGH Z_{in}

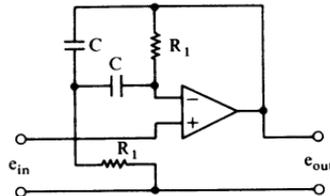

$$A_{VO} = (R_2/2R_1) + 1$$

$$|A_v|_{vlf} = |A_{vhf}| = 1$$

$$Q \approx \sqrt{R_2/4R_1}$$


$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

Second Order

**FILTER
BANDPASS
MULTIPLE FEEDBACK**

Variable
Frequency

CONSTANT Q

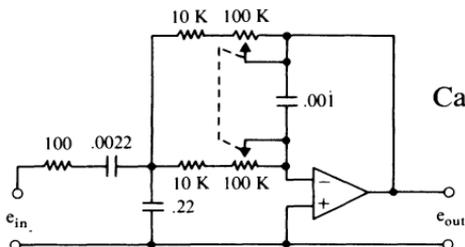

Opamp = 1/2 LF353


Capacitors = 5% Mylar

Tuning Range \approx 100 to 1000 Hz

$$Q = 7.4$$

$$A_{VO} = 1$$

CONSTANT BANDWIDTH

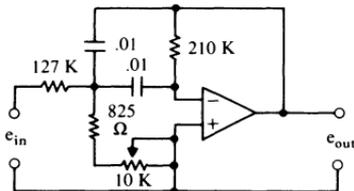

Opamp = 1/2 LF353

Capacitors = 5% Mylar

Tuning Range = > 400 to < 1000 Hz

$$BW_{-3\text{dB}} = 150 \text{ Hz at } 400 \text{ Hz } (Q = 2.7)$$

$$BW_{-3\text{dB}} = 150 \text{ Hz at } 1000 \text{ Hz } (Q = 6.7)$$

$$A_{VO} = 1$$

See Also—Filter, Bandpass, High f_0Q

Second
order


**FILTER
BANDPASS
MULTIPLE FEEDBACK TYPE II**

General and
High $f_0 Q$

$$f_0 = [2\pi R\sqrt{C_1 C_2}]^{-1}$$

$$A_{VO} = C_1/2C_2 = 2Q^2$$


$$Q = \sqrt{C_1/4C_2}$$

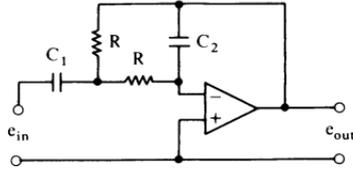

$$|e_{out}/e_{in}|_{dB} = 20 \log [2Q^2/\sqrt{1 + Q^2[(f/f_0) - (f_0/f)]^2}]$$

Type II MFB bandpass filters are capable of Qs of 50 or greater without compensation. Opamp GBW however, affects frequency. A GBW/ $f_0 Q$ of 30 develops $\approx -5\%$ frequency error. Uncompensated filters require capacitors with “Q”s of ≥ 100 circuit Q.

HIGH AUDIO FREQUENCY

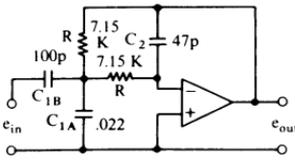

$$A_{VO} = C_{1B}/2C_2 \approx 1$$

$$f_0 = [2\pi R\sqrt{C_2(C_{1A} + C_{1B})}]^{-1}$$


$$Q = \sqrt{(C_{1A} + C_{1B})/4C_2}$$

$$= 10.8 \text{ (11)}$$

Opamp = 1/2 LF353 and
measured $f_0 = 20.4 \text{ kHz} = -7\%$

Capacitors = Polystyrene and
NPO ceramic

HIGH Q

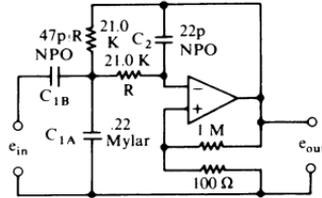

$$A_{VO} = 1.07 \text{ (1.0)}$$

$$f_0 = 3445 \text{ Hz (3000 Hz)}$$

$$Q = 50 \text{ (53.8)}$$


Opamp = 1/2 LF353

Positive feedback not
needed when .22 μF
capacitor is polystyrene
or polypropylene

Second Order

**FILTER
BANDPASS
STATE VARIABLE**

General
Formulas

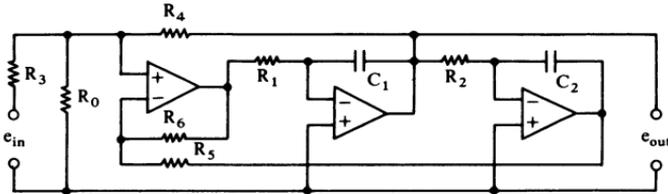

$$A_{VO} = H_{OBP} = R_4/R_3$$

$$f_0 = \sqrt{R_6/(R_5 4\pi^2 R_1 R_2 C_1 C_2)}$$

$$Q = [(1 + R_4/R_3 + R_4/R_0)\sqrt{(R_1 R_6 C_1)/(R_2 R_5 C_2)}] / (1 + R_6/R_5)$$

$$|e_{out}/e_{in}|_{dB} = 20 \log \left[R_4 / (R_3 \sqrt{1 + Q^2 [(f/f_0) - (f_0/f)]^2}) \right]$$

When $R_1 = R_2$, $C_1 = C_2$ and $R_5 = R_6$:

$$A_{VO} = H_{OBP} = R_4/R_3, f_0 = (2\pi R_1 C_1)^{-1}, R_1 = (2\pi f_0 C_1)^{-1}$$

$$Q = (1 + R_4/R_3 + R_4/R_0)/2, R_0 = R_4/(2Q - R_4/R_3 - 1)$$

Example

Let $A_{VO} = 1$, $f_0 = 1000$ Hz and $Q = 21$

Let $C_1 = C_2 = .01 \mu F$, $R_1 = R_2 = (2\pi f_0 C)^{-1} = 15.915$ K

$R_4 = R_3$, $R_5 = R_6$ —Let R_1, R_2, R_3, R_4, R_5 and $R_6 = 15.8$ K

$R_0 = R_4/(2Q - R_4/R_3 - 1) = 395 \Omega$ —Use 392Ω

Check using standard resistor values

$$A_{VO} = 1, f_0 = 1007 \text{ Hz}, Q = 21.2$$


See Also—Filter, Bandpass, High $f_0 Q$

Second Order

**FILTER
BANDPASS
STATE VARIABLE**

Variable
Frequency

CONSTANT Q

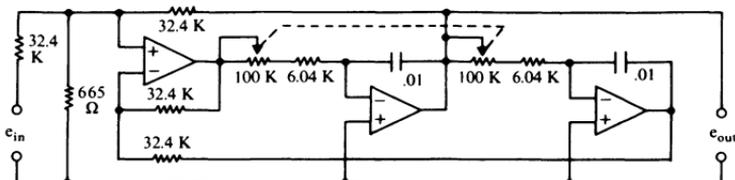


Tuning Range = 200 to 2000 Hz minimum

$A_{VO} = 1$, $Q = 25.4$, $(e_{out})_{p-p} = (V_S - 2.5)$ maximum

Opamps = 3/4 TL084, .01 μ F Caps = Polystyrene

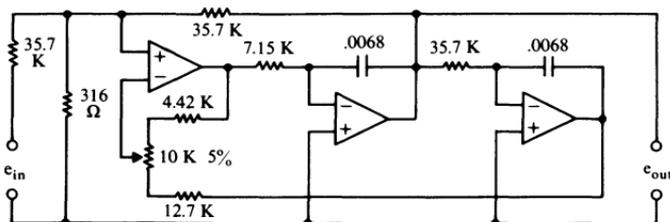SINGLE POT, MIN ΔQ , MAX $(e_{out})_{p-p}$



Tuning Range = 1000 to 2000 Hz minimum

$Q = 19.9$ at 1000 Hz to 25.7 at 2000 Hz

$A_{VO} = 1$, $(e_{out})_{p-p} = (V_S - 2.5)$ maximum

Opamps = 3/4 TL084, Capacitors = 5% Polystyrene


See Also—Filter, Bandpass, High f_0Q

Second Order

**FILTER
BANDPASS
STATE VARIABLE**

Variable
Frequency

CONSTANT BANDWIDTH

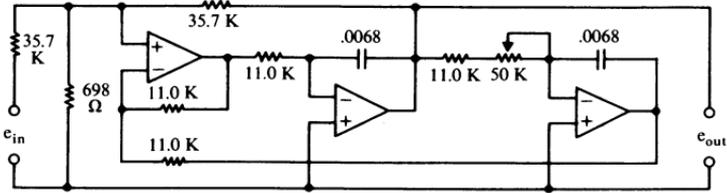


Tuning Range = 1000 to 2000 Hz minimum

BW = 80 at 1000 Hz ($Q = 12.5$), = 80 at 2000 Hz ($Q = 25$)

$A_{VO} = 1$, $(e_{out})_{p-p} = (V_S - 2.5)$ maximum

Opamps = 3/4 TL084, Capacitors = 5% Polystyrene

Q INVERSELY PROPORTIONAL TO FREQUENCY

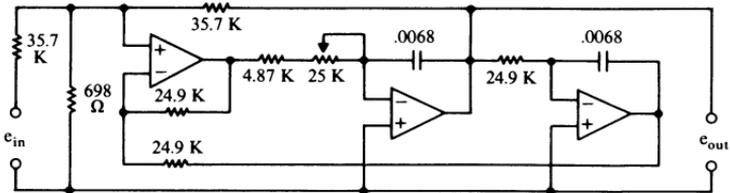

Tuning Range = 1000 to 2000 Hz minimum

$Q = 25$ at 1000 Hz to 12.5 at 2000 Hz

$A_{VO} = 1$, $(e_{out})_{p-p} = (V_S - 2.5)$ maximum

Opamps = 3/4 TL084, Capacitors = 5% Polystyrene

See Also—Filter, Bandpass, High f_0Q

FILTER BANDPASS, STATE VARIABLE HIGH f_0Q COMPENSATION

State variable filter formulas accurately describe operation with ideal components. When both the resonant frequency and the Q are low, the error caused by ordinary components is negligible (exception: electrolytic capacitors).

With ideal opamps, capacitors with a $Q(D^{-1})$ of 40 filter Q will cause a 5% formula error. A filter with a Q of 50 would therefore require capacitors with a Q of 2000 or greater (polystyrene or polypropylene) unless compensated.

With ideal capacitors, opamps having a gain-bandwidth product (GBW) or unity-gain bandwidth (B_1) of $150 f_0Q$ will also cause up to 5% formula error. A filter with an f_0 of 1000 Hz and a Q of 20 requires opamps with a B_1 of 3 MHz or greater for 5% maximum error unless compensated.

The effect of low capacitor Q is to decrease filter Q and gain however the effect of low opamp B_1 is to increase Q and gain, and to decrease f_0 . The effect of low opamp B_1 almost always dominates and compensation may be required.

Low opamp B_1 causes excess loop phase lag, therefore compensation consists of adding phase-lead components to eliminate or reduce this excess. The phase-lead required cannot be accurately obtained from opamp data books since GBW or B_1 and phase shift are given as typical with no minimum or maximum. High f_0Q filters therefore may require "tweaking" or adjustable compensation if very accurate results are required.



The most accurate method of compensation adjustment is to short-circuit the Q determining resistor R_0 and adjust compensation to the edge of oscillation. A less accurate but usually satisfactory method is adjustment of compensation to obtain calculated gain.

Compensation methods include very small capacitors in parallel with tuning resistors, very low value resistors in series with tuning capacitors and near 90° RC "positive" feedback. This last method allows the use of a wide range of RC values and provides the best overall accuracy.


Compensation need only be applied to one of the three state variable opamp stages and the third stage is the best choice. Third-stage compensation only is shown on the following page.

FILTER BANDPASS, STATE VARIABLE HIGH f_0Q COMPENSATION


STATE VARIABLE BANDPASS FILTER

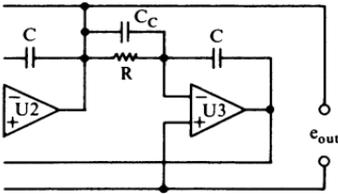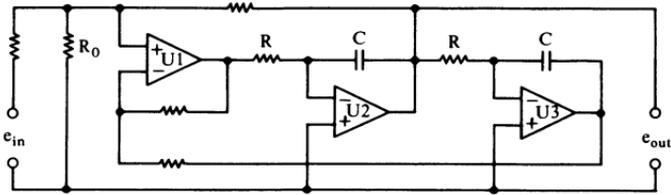

$$C_c \approx .8/(B_1 R)$$

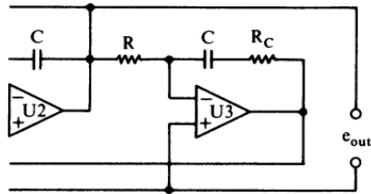

$$R_c \approx (6f_0 R)/B_1$$

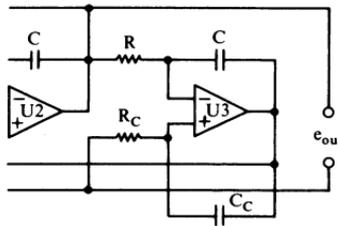


$$R_c C_c \approx .8/B_1$$

$$R_c \approx .8/(B_1 C_c)$$

$$C_c \approx .8/(B_1 R_c)$$

Variable Compensation

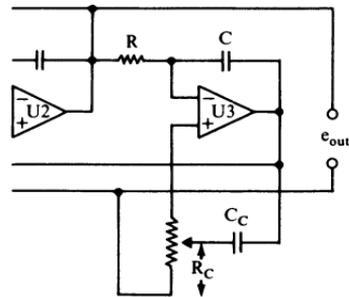


Short R_0 and tweak R_c or C_c to the edge of oscillation for best general formula accuracy. This also compensates for capacitor Q .

Second Order

**FILTER
BANDPASS
STATE VARIABLE TYPE II**

Simplified
Formulas

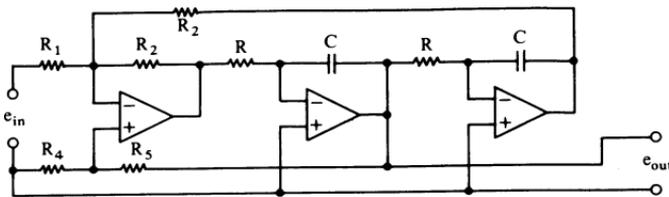

$$A_{VO} = H_{OBP} = QR_2/R_1 = (R_5/R_4 + 1)/(2R_1/R_2 + 1)$$

$$f_0 = (2\pi RC)^{-1}, \quad R = (2\pi f_0 C)^{-1}$$

$$Q = (R_5/R_4 + 1)/(R_2/R_1 + 2),$$


$$R_5/R_4 = Q(R_2/R_1 + 2) - 1$$

$$|e_{out}/e_{in}|_{dB} = 20 \log \left[QR_2 / \left(R_1 \sqrt{1 + Q^2 \left[(f/f_0) - (f_0/f) \right]^2} \right) \right]$$

When $R_1 = R_2$:

$$A_{VO} = Q, \quad Q = (R_5/R_4 + 1)/3, \quad R_5/R_4 = 3Q - 1,$$

$$f_0 = (2\pi RC)^{-1}$$

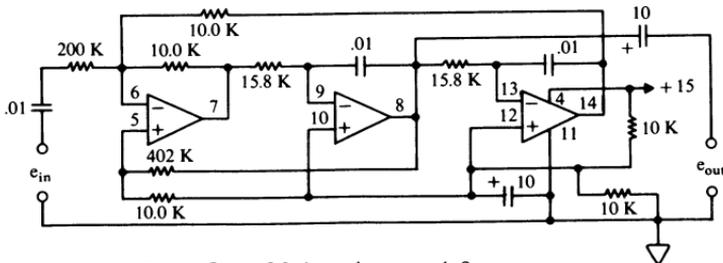

$$f_0 = 1007 \text{ Hz}, \quad Q = 20.1, \quad A_{VO} = 1.0$$

Opamps = 3/4 LF347, .01 μ F Caps = 5% Polystyrene


See Also—Filter, Bandpass, High f_0 Q

**Symmetrical
Two Pole BPF**

**FILTER
BANDPASS
UNIVERSAL**

**Fourth Order
General Formulas**

TYPE I

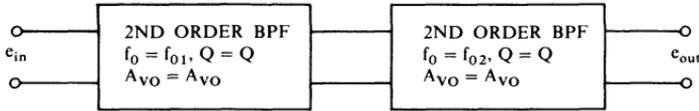


$$|e_o/e_{in}|_{dB} = 20 \log A_{VO}^2 -$$

$$20 \log \left(\frac{\sqrt{(1 + Q^2 [(f/f_{01}) - (f_{01}/f)]^2)}}{(1 + Q^2 [(f/f_{02}) - (f_{02}/f)]^2)} \right)$$

$$|A_{VC}|_{dB} = 20 \log [A_{VO}^2 (1 + Q^2 [\sqrt{f_{02}/f_{01}} - \sqrt{f_{01}/f_{02}}]^2)^{-1}]$$

A_{VC} = Voltage gain at passband center frequency

TYPE II

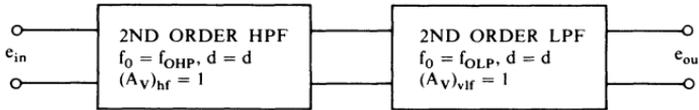

$$|e_o/e_{in}|_{dB} = -20 \log$$

$$\left(\frac{\sqrt{[(f_{OHP}/f)^4 + (f_{OHP}/f)^2(d^2 - 2) + 1]}}{[(f/f_{OLP})^4 + (f/f_{OLP})^2(d^2 - 2) + 1]} \right)$$

$$|A_{VC}|_{dB} = 20 \log [(f_{OLP}/f_{OHP}) / (f_{OLP}/f_{OHP} + f_{OHP}/f_{OLP} + d^2 - 2)]$$

when $f_{OLP} \geq f_{OHP}$ ($A_{VC} = A_V$ at PB center frequency)

The response of TYPE I and TYPE II filters are equal when:

$$f_{OHP} = f_{01}, \quad f_{OLP} = f_{02}, \quad d = 1/Q, \quad f_{OLP} \geq f_{OHP} \quad \text{and}$$


$$(A_{VO})_{TYPE I}^2 = Q^2 f_{02}/f_{01}.$$

Normalized for gain, TYPE I and TYPE II formulas may be used interchangeably.

Symmetrical
Two Pole BPF

FILTER
BANDPASS
UNIVERSAL


Fourth Order
General

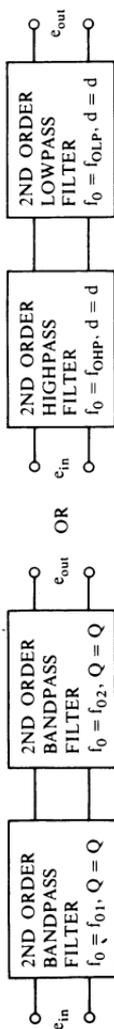

TYPE II ($f_{OLP} > f_{OHP}$)

TYPE I

	$BW_x = \frac{2 - 2^{-1}}{2 - 2^{-1}}$ TWO OCTAVE		$BW_x = \sqrt{2 - \sqrt{2^{-1}}}$ ONE OCTAVE		$BW_x = \frac{4\sqrt{2 - \sqrt{2^{-1}}}}{\sqrt{2 - \sqrt{2^{-1}}}}$ 1/2 OCTAVE		$BW_x = \frac{8\sqrt{2 - \sqrt{2^{-1}}}}{\sqrt{2 - \sqrt{2^{-1}}}}$ 1/4 OCTAVE	
	f_{02}/f_{01}	Q	f_{02}/f_{01}	Q	f_{02}/f_{01}	Q	f_{02}/f_{01}	Q
TYPE I								
TYPE II								
$BW_{-3dB}, \text{ MAX FLAT}$	3.100	1.098	1.6659	2.066	1.2812	4.094	1.1309	8.168
$BW_{-3dB}, \text{ 1 dB DIP}$	2.999	1.706	1.6830	3.242	1.2922	6.416	1.1362	12.799
$BW_{-3dB}, \text{ 2 dB DIP}$	3.044	2.063	1.7055	3.912	1.3017	7.736	1.1405	15.424
$BW_{-3dB}, \text{ 3 dB DIP}$	3.0973	2.407	1.7265	4.550	1.3103	8.9863	1.1443	17.915
$BW_{-2dB}, \text{ MAX FLAT}$	3.674	1.010	1.796	1.832	1.3276	3.594	1.1508	7.158
$BW_{-2dB}, \text{ 1 dB DIP}$	3.291	1.607	1.7617	2.998	1.3215	5.909	1.1489	11.779
$BW_{-2dB}, \text{ 2 dB DIP}$	3.288	1.961	1.7730	3.664	1.3272	7.214	1.1515	14.378
$BW_{-1dB}, \text{ MAX FLAT}$	4.981	.9035	2.0655	1.525	1.4167	2.947	1.1880	5.850
$BW_{-1dB}, \text{ 1 dB DIP}$	3.7656	1.4914	1.884	2.707	1.3660	5.295	1.1680	10.535

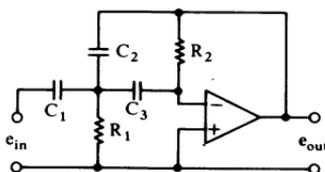

$$f_0 = [2\pi\sqrt{R_1 R_2 C_2 C_3}]^{-1}$$

$$|A_v| = C_1/C_2, \quad |A_{vfo}| = C_1/C_2 d$$

$$d = \sqrt{(R_1/R_2)[(C_1 + C_2 + C_3)^2/C_2 C_3]}$$

$$f_c = f_0/\sqrt{a + \sqrt{a^2 + 1}} \quad \text{where } a = 1 - (d^2/2)$$

$$f_{pk} = f_0/\sqrt{1 - (d^2/2)} \quad \text{when } d < \sqrt{2}$$

(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log [2C_1/(C_2 d \sqrt{4 - d^2})] \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log (C_1/[C_2 \sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}])$$

$$(\theta_e)_{out} - (\theta_e)_{in} = [\tan^{-1} (d/[(f/f_0) - (f_0/f)])] \pm 180^\circ$$

$$d = \sqrt{9R_1/R_2} \quad \text{when } C_1 = C_2 = C_3$$

$$d = (C_1/C_2 + 2)\sqrt{R_1/R_2} \quad \text{when } C_2 = C_3$$

$$R_2/R_1 = 9/d^2 \quad \text{when } C_1 = C_2 = C_3$$

$$R_2/R_1 = (C_1/C_2 + 2)^2/d^2 \quad \text{when } C_2 = C_3$$


$$C_1/C_2 = d\sqrt{R_2/R_1} - 2 \quad \text{when } C_2 = C_3$$

$$(\theta_e)_{out} - (\theta_e)_{in} = \pm 90^\circ \quad \text{when } f = f_0$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Unity Gain
Equal Capacitor

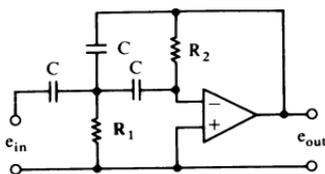

$$|A_{v\text{hf}}| = 1, \quad |A_{v\text{fo}}| = d^{-1}$$

$$f_0 = [2\pi C \sqrt{R_1 R_2}]^{-1}, \quad R_1 = d / (6\pi f_0 C)$$

$$d = \sqrt{9R_1 / R_2}, \quad R_2 = 9R_1 / d^2, \quad R_2 / R_1 = 3 / d^2$$

$$f_c = f_0 / \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c \sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{\text{pk}} = f_0 / \sqrt{1 - d^2/2}$$

when $d < \sqrt{2}$

(no peak when $d \geq \sqrt{2}$)

$$|A_{v\text{pk}}|_{\text{dB}} = 20 \log [2/d \sqrt{4 - d^2}] \quad \text{when } d < \sqrt{2}$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log [\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}]^{-1}$$

$$(\theta_e)_{\text{out}} - (\theta_e)_{\text{in}} = [\tan^{-1} (d / [(f/f_0) - (f_0/f)])] \pm 180^\circ$$

Choose f_c, d, C

$$f_0 = f_c \sqrt{a + \sqrt{a^2 + 1}}$$

($a = 1 - d^2/2$)

$$R_1 = d / (6\pi f_0 C)$$

$$R_2 = 9R_1 / d^2$$

Butterworth example

$$\text{Let } d = \sqrt{2}$$

$$\text{Let } f_c = 1000 \text{ Hz}$$

$$\text{Let } C = .01 \mu\text{F}$$

$$R_1 = 7.503 \text{ K—Use } 7.50 \text{ K}$$

$$R_2 = 33.76 \text{ K—Use } 34.0 \text{ K}$$

Check with practical values

$$d = \sqrt{9R_1 / R_2}$$

$$d = 1.409 (\approx \sqrt{2})$$

$$f_0 = [2\pi C \sqrt{R_1 R_2}]^{-1}$$

$$f_0 = 996.7 \text{ Hz}$$

$$f_c = f_0 / \sqrt{a + \sqrt{a^2 + 1}}$$


($a = 1 - d^2/2$)

$$f_c = 993.0 \text{ Hz}$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Gain \neq Unity
 $C_2 = C_3$ Formulas

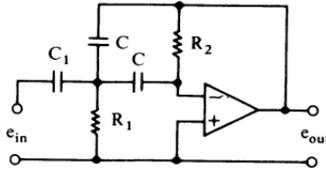

$$|A_V| = C_1/C, \quad |A_{Vf_0}| = C_1/Cd$$

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}, \quad R_1 = d/[(A_V + 2)(2\pi f_0 C)]$$

$$d = \sqrt{R_1/R_2} (C_1/C + 2), \quad R_2 = (A_V + 2)/(2\pi f_0 C d)$$

$$f_c = f_0/\sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c\sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0/\sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2}$$

(no peak when $d \geq \sqrt{2}$)

$$|A_{Vpk}|_{dB} = 20 \log (2C_1/[Cd\sqrt{4 - d^2/2}]) \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log (C_1/[C\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}])$$

$$(\theta_e)_{out} - (\theta_e)_{in} = [\tan^{-1} (d/[(f/f_0) - (f_0/f)])] \pm 180^\circ$$

Choose A_V, d, f_0, C

example, 1000 Hz Butterworth

$$C_1 = A_V C$$

Let $A_V = 10, d = \sqrt{2},$ and

$$C = .01 \mu F$$

$$R_1 = d/[(A_V + 2)(2\pi f_0 C)]$$

$$C_1 = .1 \mu F$$

$$R_2 = (A_V + 2)/(2\pi f_0 C d)$$

$$R_1 = 1.876 \text{ K—Use } 1.87 \text{ K}$$

$$R_2 = 135.0 \text{ K—Use } 133 \text{ K}$$

Check with practical values

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

$$f_0 = 1009 \text{ Hz}$$

$$d = [C_1/C_2 + 2]\sqrt{R_1/R_2}$$

$$d = 1.423 (\approx \sqrt{2})$$

$$f_c = f_0/\sqrt{a + \sqrt{a^2 + 1}},$$

$$f_c = 1015 \text{ Hz,}$$


$$A_V = C_1/C$$

$$A_V = 10$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Unity Gain
Equal Capacitor

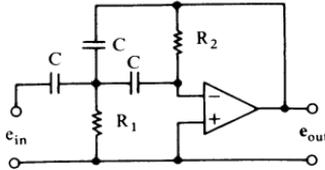

RESPONSE	d	R_2/R_1	f_c/f_0	R_1	R_2
Bessel (Best transient)	1.732	3.000	1.272	.7344a	2.203a
Butterworth (Flattest)	1.414	4.500	1.000	.4714a	2.121a
.1 dB Peak Chebyshev	1.303	5.300	.9276	.4029a	2.136a
.5 dB Peak Chebyshev	1.158	6.714	.8504	.3282a	2.204a
1 dB Peak Chebyshev	1.045	8.234	.8028	.2798a	2.304a
2 dB Peak Chebyshev	.8860	11.46	.7500	.2215a	2.539a
3 dB Peak Chebyshev	.7665	15.32	.7197	.1839a	2.817a

$$a = (2\pi f_c C)^{-1}$$

$$|A_v|_{\text{vhf}} = 1 = 0 \text{ dB}$$

$$|A_{\text{vpk}}|_{\text{dB}} = 20 \log [2/(d\sqrt{4-d^2})]$$

$$|A_{\text{vfo}}|_{\text{dB}} = 20 \log d^{-1}, \quad f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

$$|A_{\text{vfc}}| = \sqrt{1/2}$$

$$|A_{\text{vfc}}|_{\text{dB}} = 20 \log \sqrt{1/2} = -3.0103 \text{ dB}$$


$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log [\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}]^{-1}$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log [\sqrt{1 + (f_0/f)^4}]^{-1} \quad (\text{Butterworth})$$

Unity Gain
18 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Third Order
Butterworth

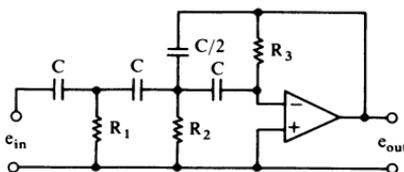

Butterworth Response

$$R_1 = .4074/(2\pi f_c C)$$

$$R_2 = .4742/(2\pi f_c C)$$

$$R_3 = 5.177/(2\pi f_c C)$$

$$f_c = f_0 = [2\pi C(R_1 R_2 R_3)^{\frac{1}{3}}]^{-1}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [\sqrt{(f_0/f)^6 + 1}]^{-1}$$

example

Let $f_c = 1000$ Hz

Let $C = .0068$ μ F

$C/2 = .0034$ μ F—use $.0033$ μ F

$R_1 = 9.535$ K—use 9.53 K

$R_2 = 11.10$ K—use 11.0 K

$R_3 = 121.2$ K—use 121 K


$f_c = 1004$ Hz

$A_v = .97 = -.26$ dB

Independent Gain
18 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Third Order
Equal Capacitor

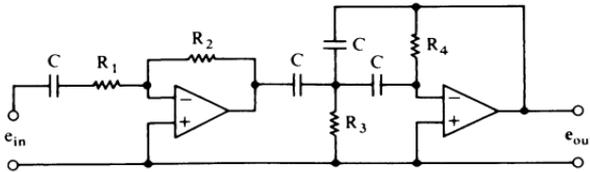

$$|A_V|_{\text{vhf}} = R_2/R_1$$

RESPONSE	R_1	R_3	R_4	f_b/f_c	ϵ
Bessel	1.323a	.6983a	3.001a	—	—
Butterworth	1.000a	.3333a	3.000a	—	—
.1 dB Dip Chebyshev	.6979a	.2656a	4.2985a	1.3890	.15262
.5 dB Dip Chebyshev	.5366a	.1789a	4.686a	1.1675	.34931
1 dB Dip Chebyshev	.4514a	.1505a	5.513a	1.0948	.50885
2 dB Dip Chebyshev	.3572a	.1191a	6.978a	1.0327	.76479
3 dB Dip Chebyshev	.2985a	.09951a	8.428a	1.0003	.99763

$$a = (2\pi f_c C)^{-1}$$

f_c = Cutoff, corner or half-power frequency

$$|A_V|_{fc} = R_2/(R_1\sqrt{2})$$

f_b = Rippleband-edge frequency. e.g. The lower 1 dB down frequency in a highpass 1 dB Chebyshev filter

$$f_{\text{dip}} = 2f_b, \quad |A_V|_{\text{dip}} = |A_V|_{fb} \quad (\text{Chebyshev})$$

$$|A_V|_{\text{pk}} = |A_V|_{\text{vhf}} = R_2/R_1, \quad f_{\text{pk}} = 1.155f_b \quad (\text{Chebyshev})$$


$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left[\frac{R_2}{R_1 \sqrt{1 + \epsilon^2 [4(f_b/f)^3 - 3(f_b/f)]^2}} \right] \quad (\text{Chebyshev})$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log (R_2/[R_1 \sqrt{(f_c/f)^6 + 1}]) \quad (\text{Butterworth})$$

Unity Gain
24 dB/Octave

**FILTER
HIGHPASS
MULTIPLE FEEDBACK**

Fourth Order
Equal Capacitor

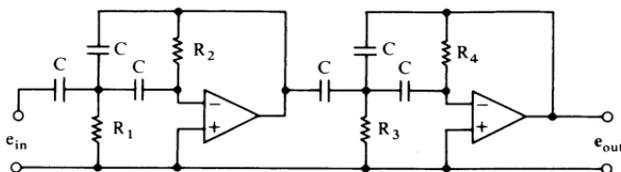

	R_1	R_2	R_3	R_4	f_b/f_c
Bessel	.9135a	2.240a	.6635a	3.875a	—
Butterworth	.6159a	1.624a	.2551a	3.920a	—
.1 dB Ripple Chebyshev	.3505a	1.208a	.1452a	6.226a	1.213
.5 dB Ripple Chebyshev	.2582a	1.155a	.1069a	8.322a	1.093
1 dB Ripple Chebyshev	.2133a	1.182a	.08834a	10.07a	1.053
2 dB Ripple Chebyshev	.1658a	1.289a	.06866a	13.04a	1.018
3 dB Ripple Chebyshev	.1371a	1.430a	.05677a	15.90a	1.00015

$$a = (2\pi f_c C)^{-1}$$

$$f_c = f_{-3.01 \text{ dB}} \quad (\text{Bessel and Butterworth})$$

$$f_c = \text{Frequency of } 3.01 \text{ dB down from } |A_{v_{pk}}| \quad (\text{Chebyshev})$$

f_b = Rippleband-edge frequency. The lowest frequency of $A_v = 0 \text{ dB}$. e.g. The lower ($A_{v_{pk}} - 1 \text{ dB}$) in a 1 dB highpass Chebyshev filter. (Chebyshev)

$|A_{v_{pk}}| = +1 \text{ dB}$ in a 1 dB filter, $+2 \text{ dB}$ in a 2 dB filter etc (Chebyshev)

$$|A_{v_{hf}}| = |A_v|_{\text{dip}} = |A_{vfb}| = 1 = 0 \text{ dB}$$


$$f_{pk} = 1.082f_b \text{ and } 2.612f_b, \quad f_{\text{dip}} = 1.414f_b$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log (\sqrt{1 + (f_c/f)^8})^{-1} \quad (\text{Butterworth})$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
SALLEN-KEY ①**

General
Formulas

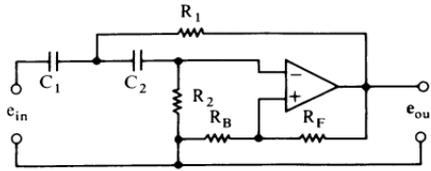

$$|A_{vhf}| = 1 + R_F/R_B, \quad |A_{vfo}| = (1 + R_F/R_B)/d$$

$$|A_{vpk}|_{dB} = 20 \log \left([2(1 + R_F/R_B)] / [d\sqrt{4 - d^2/2}] \right) \quad \text{when } d < \sqrt{2}$$

$$d = [(R_1/R_2)(C_1/C_2 + 1) - R_F/R_B] / \sqrt{(R_1/R_2)(C_1/C_2)}$$

$$f_c = f_0 / \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c \sqrt{a + \sqrt{a^2 + 1}} \quad \text{where } a = 1 - d^2/2$$

$$f_0 = [2\pi\sqrt{R_1 R_2 C_1 C_2}]^{-1}, \quad R_1 = [(2\pi f_0)^2 R_2 C_1 C_2]^{-1}$$

$$f_{pk} = f_0 / \sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2} \text{ (no peak when } d \geq \sqrt{2})$$

$$|e_{out}/e_{in}|_{dB} =$$

$$20 \log \left([1 + R_F/R_B] / \sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1} \right)$$

$$(\theta_{co} - \theta_{ci}) = \tan^{-1} \left(d / [(f/f_0) - (f_0/f)] \right)$$

$$(A_V)_{RQD} = (R_1/R_2)(C_1/C_2 + 1) + 1 - d\sqrt{(R_1/R_2)(C_1/C_2)}$$

$$(R_F/R_B) = (R_1/R_2)(C_1/C_2 + 1) - d\sqrt{(R_1/R_2)(C_1/C_2)}$$

$$(R_1/R_2) = [b + \sqrt{b^2 - 4ac}] / 2a$$

$$\text{where } a = C_1/C_2 + C_2/C_1 + 2, \quad c = (R_F/R_B)^2(C_2/C_1),$$

$$b = (2R_F/R_B)(C_2/C_1 + 1) + d^2$$

$$(C_1/C_2) = [b \pm \sqrt{b^2 - 4ac}] / 2a$$

$$\text{where } a = R_1/R_2,$$

$$b = 2R_F/R_B - 2R_1/R_2 + d^2,$$


$$c = R_1/R_2 + (R_F/R_B)^2(R_2/R_1) - 2R_F/R_B$$

Notes: ① Sallen-Key filters are also known as single feedback, voltage controlled voltage source and VCVS.

**Second Order
12 dB/Octave**

**FILTER
HIGHPASS
SALLEN-KEY**

**Equal Capacitor
Simplified Formulas**

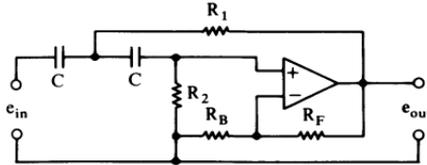

$$|A_{v\text{hf}}| = 1 + R_F/R_B, \quad |A_{v\text{fo}}| = (1 + R_F/R_B)/d$$

$$|A_{v\text{pk}}|_{\text{dB}} = 20 \log \left([2(1 + R_F/R_B)] / [d\sqrt{4 - d^2}] \right)$$

$$d = [2R_1/R_2 - R_F/R_B] / \sqrt{R_1/R_2} \quad \text{when } d < \sqrt{2}$$

$$f_c = f_0 / \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c \sqrt{a + \sqrt{a^2 + 1}}$$

$$\text{where } a = 1 - d^2/2$$

$$f_{\text{pk}} = f_0 / \sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2} \text{ (no peak when } d \geq \sqrt{2}\text{)}$$

$$(R_1/R_2) = [4R_F/R_B + d^2 + \sqrt{d^4 + 8d^2R_F/R_B}] / 8$$

$$R_2 = [\sqrt{(R_1/R_2)}(2\pi f_0 C)]^{-1}$$

$$(R_F/R_B) = 2R_1/R_2 - d\sqrt{R_1/R_2}, \quad (R_F/R_B) = A_v - 1$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left([1 + R_F/R_B] / \sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1} \right)$$

$$(\theta_{e_o} - \theta_{e_i}) = \tan^{-1} \left(d / [(f/f_0) - (f_0/f)] \right)$$

Example—Let $f_c = 800$ Hz, $A_v = 10$, $d = 1$ and $C = .01 \mu\text{F}$

$$(R_F/R_B) = A_v - 1 = 9$$

Let $R_F = 10.2$ K, $R_B = 1.13$ K, $R_F/R_B = 9.0265$

$$(R_1/R_2) = [4R_F/R_B + d^2 + \sqrt{d^4 + 8d^2R_F/R_B}] / 8 = 5.7078$$

$$f_0 = f_c \sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2)^2 + 1}} = 1018 \text{ Hz}$$

$$R_2 = [\sqrt{(R_1/R_2)}(2\pi f_0 C)]^{-1} = 6.55 \text{ K—use } 6.65 \text{ K}$$

$$R_1 = R_2(R_1/R_2) = 38.0 \text{ K—use } 38.3 \text{ K}$$

Check using chosen practical values


$$d = 1.038, \quad f_0 = 997.3 \text{ Hz}, \quad f_c = 798.0 \text{ Hz},$$

$$A_v = 10.03, \quad A_{v\text{pk}} = 21.15 \text{ dB}$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
SALLEN-KEY**

Unity Gain
Equal Capacitor

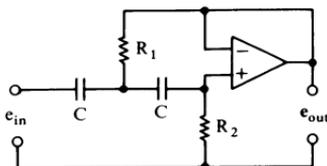

$$|A_{v_{hf}}| = 1, \quad |A_{v_{fo}}| = d^{-1}$$

$$|A_{v_{pk}}|_{dB} = 20 \log [2/d\sqrt{4-d^2}] \quad \text{when } d < \sqrt{2}$$

$$d = \sqrt{4R_1/R_2}, \quad d = 4\pi f_0 CR_1, \quad d = (\pi f_0 CR_2)^{-1}$$

$$f_c = f_0/\sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c\sqrt{a + \sqrt{a^2 + 1}}$$

$$\text{where } a = 1 - d^2/2$$

$$f_{pk} = f_0/\sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2} \quad (\text{no peak when } d \geq \sqrt{2})$$

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}, \quad f_0 = d/(4\pi R_1 C), \quad f_0 = (\pi R_2 C d)^{-1}$$

$$(R_1/R_2) = d^2/4, \quad R_1 = d/(4\pi f_0 C), \quad R_2 = (4\pi f_0 C d)^{-1}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}]^{-1}$$

$$(\theta_{eo} - \theta_{ei}) = \tan^{-1} (d/[(f/f_0) - (f_0/f)])$$

Example: Let $f_c = 1000$ Hz, $c = .01 \mu\text{F}$ and $d = \sqrt{2}$
(Butterworth)

$$f_0 = f_c\sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2) + 1}} = f_c = 1000 \text{ Hz}$$

$$R_1 = d/(4\pi f_0 C) = 11.25 \text{ K—use } 11.3 \text{ K}$$

$$R_2 = (\pi f_0 C d)^{-1} = 22.51 \text{ K—use } 22.6 \text{ K}$$

Check using chosen practical values

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1} = 995.9 \text{ Hz,}$$


$$d = \sqrt{4R_1/R_2} = 1.414 = \sqrt{2},$$

$$f_c = f_0 = 995.9 \text{ Hz,} \quad |A_{v_{fo}}| = d^{-1} = .7071 = -3.010 \text{ dB}$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
SALLEN-KEY**

Unity Gain
Equal Capacitor

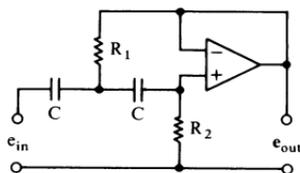

RESPONSE	d	f_c/f_0	R_2/R_1	R_1	R_2
Bessel	1.732	1.272	1.333	1.102a	1.469a
Butterworth	1.414	1.000	2.000	.7071a	1.414a
.1 dB Peak Chebyshev	1.303	.9276	2.355	.6043a	1.424a
.5 dB Peak Chebyshev	1.158	.8504	3.455	.4924a	1.469a
1 dB Peak Chebyshev	1.045	.8028	3.660	.4195a	1.536a
2 dB Peak Chebyshev	.8860	.7500	5.095	.3323a	1.693a
3 dB Peak Chebyshev	.7665	.7197	6.809	.2758a	1.878a

$$a = (2\pi f_c C)^{-1}$$

$$|A_{v_{hf}}| = 1, \quad |A_{v_{fo}}| = d^{-1}, \quad |A_{v_{fc}}| = 1/\sqrt{2}$$

$$|A_{v_{pk}}|_{dB} = 20 \log (2/[d\sqrt{4-d^2}]) \quad \text{when } d < \sqrt{2}$$

$$f_{pk} = f_0/\sqrt{1-d^2/2} = [2\pi C\sqrt{R_1 R_2}(1-d^2/2)]^{-1}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2-2) + 1}]^{-1}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [\sqrt{1+(f_0/f)^4}]^{-1} \quad \text{Butterworth only}$$


$$\text{Check: } f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}, \quad d = \sqrt{4R_1/R_2}$$

$$f_c = f_0/\sqrt{b + \sqrt{b^2 + 1}} \quad \text{where } b = 1 - 2R_1/R_2$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
SALLEN-KEY**

Free Gain
 $R_1 = R_2, C_1 = C_2$

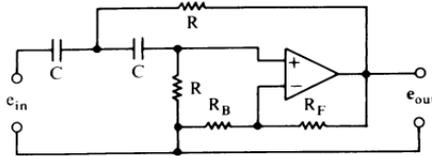

$$|A_{\text{vhf}}| = 1 + R_F/R_B, \quad |A_{\text{vfo}}| = (1 + R_F/R_B)/d$$

$$d = 2 - R_F/R_B, \quad (R_F/R_B) = 2 - d$$

$$f_c = f_0/\sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c\sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_0 = (2\pi RC)^{-1}, \quad R = (2\pi f_0 C)^{-1}$$

RESPONSE	d	R_F/R_B	A_{vhf}	A_{vpk}	R
Bessel	1.7321	.2679	1.268	2.06 dB max	$1.272/(2\pi f_c C)$
Butterworth	1.4141	.5858	1.586	4.0 dB max	$1.000/(2\pi f_c C)$
.1 dB Peak Chebyshev	1.3032	.6968	1.697	4.69 dB	$.9377/(2\pi f_c C)$
.5 dB Peak Chebyshev	1.1578	.8422	1.842	5.81 dB	$.8868/(2\pi f_c C)$
1 dB Peak Chebyshev	1.0455	.9545	1.955	6.82 dB	$.8624/(2\pi f_c C)$
2 dB Peak Chebyshev	.8860	1.114	2.114	8.50 dB	$.8446/(2\pi f_c C)$
3 dB Peak Chebyshev	.7665	1.234	2.234	9.98 dB	$.8409/(2\pi f_c C)$

$$|A_{\text{vpk}}|_{\text{dB}} = 20 \log \left([2(1 + R_F/R_B)]/[d\sqrt{4 - d^2/2}] \right)$$

when $d < \sqrt{2}$

$$f_{\text{pk}} = f_0/\sqrt{1 - d^2/2}, \quad |A_{\text{vfc}}|_{\text{dB}} = |A_{\text{vpk}}|_{\text{dB}} - 3.0103 \text{ dB}$$

when $d < \sqrt{2}$


$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left[(1 + R_F/R_B)/\sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1} \right]$$

$$(\theta_{e_o} - \theta_{e_i}) = \tan^{-1} \left(d/[(f/f_0) - (f_0/f)] \right)$$

Unity Gain
18 dB/Octave

**FILTER
HIGHPASS
SINGLE FEEDBACK**

Third Order
Equal Capacitor

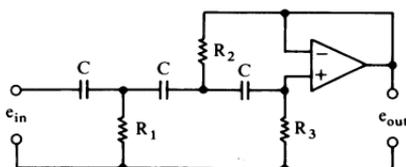

RESPONSE	R ₁	R ₂	R ₃	f _b /f _c	ε
Bessel	1.012a	.7027a	3.940a	—	—
Butterworth	.7184a	.2820a	4.941a	—	—
.1 dB Dip Chebyshev	.5479a	.1503a	7.435a	1.3890	.15262
.5 dB Dip Chebyshev	.4444a	.08905a	11.17a	1.1675	.34931
1 dB Dip Chebyshev	.3896a	.06180a	15.56a	1.0948	.50885
2 dB Dip Chebyshev	.3212a	.03595a	25.69a	1.0327	.76479
3 dB Dip Chebyshev	.2756a	.02303a	39.48a	1.0003	.99763

$$a = (2\pi f_c C)^{-1}$$

f_c = Cutoff, corner or half-power frequency = f_{-3.01 dB}

f_b = Rippleband-edge frequency e.g. The lower f_{-1 dB} in a 1 dB dip highpass Chebyshev filter

$$|A_v|_{\text{dip}} = |A_{vfb}|, \quad |A_{v\text{pk}}| = |A_{v\text{hf}}| = 1 \quad (\text{Chebyshev})$$

$$f_{\text{dip}} = 2f_b, \quad f_{\text{pk}} = 1.155f_b \quad (\text{Chebyshev})$$


$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left(\sqrt{1 + \epsilon^2 [4(f_b/f)^3 - 3(f_b/f)]^2} \right)^{-1} \quad (\text{Chebyshev})$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left[\sqrt{(f_c/f)^6 + 1} \right]^{-1} \quad (\text{Butterworth})$$

Gain = Two
18 dB/Octave

**FILTER
HIGHPASS
SINGLE FEEDBACK**

Third Order
Equal Resistor

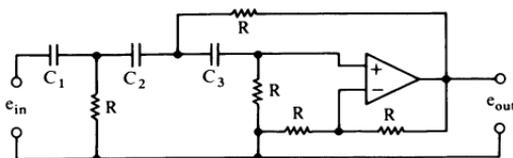

Butterworth Response

$$|A_{v_{hf}}| = 2, \quad |A_{v_{fc}}| = \sqrt{2}$$

$$C_1 = .6390/(2\pi f_c R)$$

$$C_2 = .6805/(2\pi f_c R)$$

$$C_3 = 2.300/(2\pi f_c R)$$

$$f_c = [2\pi R(C_1 C_2 C_3)^{\frac{1}{3}}]^{-1}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [2/\sqrt{(f_c/f)^6 + 1}]$$

1 dB Dip Chebyshev Response

$$|A_{v_{hf}}| = |A_{v_{pk}}| = 6 \text{ dB}, \quad |A_{v_{fb}}| = 5 \text{ dB}, \quad |A_{v_{fc}}| = 3 \text{ dB}$$

f_b = Rippleband Edge = Lower 1 dB down frequency

$$C_1 = .4395/(2\pi f_b R), \quad C_1 = .4014/(2\pi f_c R)$$

$$C_2 = .2744/(2\pi f_b R), \quad C_2 = .2506/(2\pi f_c R)$$

$$C_3 = 4.073/(2\pi f_b R), \quad C_3 = 3.720/(2\pi f_c R)$$

$$f_b = .7890/[2\pi R(C_1 C_2 C_3)^{\frac{1}{3}}]$$

$$f_c = .7206/[2\pi R(C_1 C_2 C_3)^{\frac{1}{3}}]$$

$$f_{-1 \text{ dB}} = 1.000f_b \text{ and } 2.000f_b$$

$$f_c = .9133f_b, \quad f_b = 1.095f_c$$


$$|e_{out}/e_{in}|_{dB} = 20 \log [2/\sqrt{1 + .25893[4(f_b/f)^3 - 3(f_b/f)]^2}]$$

Second Order
12 dB/Octave

**FILTER
HIGHPASS
STATE VARIABLE**

General and
Simplified Formulas

TYPE I STATE VARIABLE

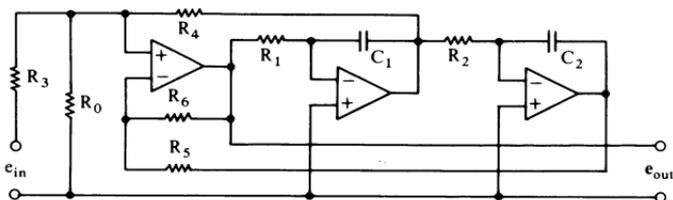

$$|A_{\text{vhf}}| = H_{\text{OHP}} = (1 + R_6/R_5)/(1 + R_3/R_0 + R_3/R_4)$$

$$d = (1 + R_6/R_5) / \left[(1 + R_4/R_3 + R_4/R_0) \sqrt{(R_1 R_6 C_1)/(R_2 R_5 C_2)} \right]$$


$$f_0 = \sqrt{R_6/(R_5 4\pi^2 R_1 R_2 C_1 C_2)}$$

When $R_1 = R_2$, $C_1 = C_2$ and $R_5 = R_6$:

$$|A_{\text{vhf}}| = H_{\text{OHP}} = R_4/R_3, \quad f_0 = (2\pi R_1 C_1)^{-1}, \quad R_1 = (2\pi f_0 C_1)^{-1}$$

$$d = 2/(1 + R_4/R_3 + R_4/R_0), \quad R_0 = R_4/(2/d - R_4/R_3 - 1)$$

TYPE II STATE VARIABLE

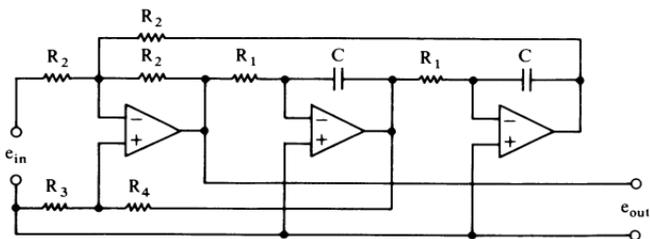

$$|A_{\text{vhf}}| = H_{\text{OHP}} = d^{-1} = (R_4/R_3 + 1)/3$$

$$d = 3/(R_4/R_3 + 1), \quad R_4 = R_3(3/d - 1)$$


$$f_0 = (2\pi R_1 C)^{-1}, \quad R_1 = (2\pi f_0 C)^{-1}$$

See Also—FILTER, UNIVERSAL, STATE VARIABLE

Second Order
12 dB/Octave

**FILTER
LOWPASS
BIQUAD**

General and
Simplified Formulas

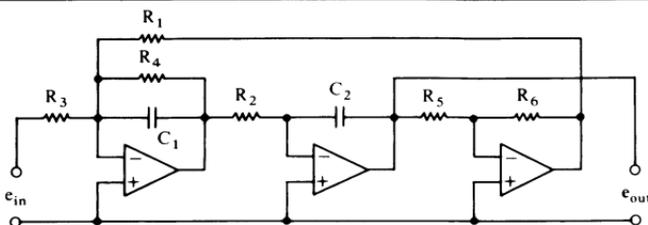

$$|A_v|_{vlf} = R_4/R_3$$

$$f_0 = \sqrt{R_6/(R_5 4\pi^2 R_1 R_2 C_1 C_2)}$$

$$d = (2\pi f_0 R_4 C_1)^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}} \quad \text{where } a = 1 - d^2/2$$

$$f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}} \quad \text{where } a = 1 - d^2/2$$

When $R_1 = R_2$, $C_1 = C_2$ and $R_5 = R_6$:

$$f_0 = (2\pi R_1 C_1)^{-1}, \quad R_1 = (2\pi f_0 C_1)^{-1}$$

example where $R_1 = R_2$, $C_1 = C_2$ and $R_5 = R_6$

Let $A_v = 1$, $f_c = 1000$ Hz, Bessel response ($d = 1.732$) and $C_1 = .01 \mu\text{F}$

$$f_0 = f_c / \sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2)^2 + 1}} = 1272 \text{ Hz}$$

$$R_1 = (2\pi f_0 C_1)^{-1} = 12.51 \text{ K—Use } 12.4 \text{ K}$$

$$R_2 = R_1/d = 7.16 \text{ K—Use } 7.15 \text{ K}, \quad R_3 = R_4/A_v = 7.15 \text{ K}$$

$$\text{Check: } f_0 = (2\pi R_1 C_1)^{-1} = 1283.5 \text{ Hz}$$

$$d = (2\pi f_0 R_4 C_1)^{-1} = 1.734$$

$$f_c = f_0 \sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2)^2 + 1}} = 1007 \text{ Hz}$$


$$A_v = 1$$

See Also—FILTER, UNIVERSAL, BIQUAD

Second Order
12 dB/Octave

**FILTER
LOWPASS
MULTIPLE FEEDBACK**

General
Formulas

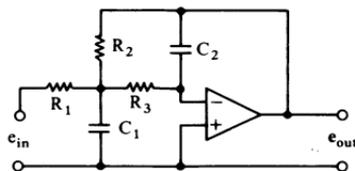

$$|A_{v|f}| = R_2/R_1, \quad |A_{v|fo}| = (R_2/R_1)/d$$

$$d = \sqrt{(R_2 R_3 C_2 / C_1)(R_1^{-1} + R_2^{-1} + R_3^{-1})^2}$$

$$f_0 = [2\pi\sqrt{R_2 R_3 C_1 C_2}]^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0 \sqrt{1 - d^2/2}$$

when $d < \sqrt{2}$

(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log(2R_2 / [R_1 d \sqrt{4 - d^2}]) \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log(R_2 / [R_1 \sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}])$$

$$(\theta_{eo} - \theta_{ei}) = [\tan^{-1}(d / [(f_0/f) - (f/f_0)])] \pm 180^\circ$$

Example and Design Formulas

Let $A_v = 10$, $f_0 = 1000$ Hz, $d = 1$ and $C_2 = .001 \mu\text{F}$

$C_1 \geq C_2 A_v (A_v^{-1} + 2)^2 / d^2$, $C_1 \geq 44.1 C_2$ —Let $C_1 = .047 \mu\text{F}$

$$R_2 = [b \pm \sqrt{b^2 - 4ac}] / 2a$$

where $a = C_1 C_2 (2\pi f_0)^2$, $b = 2\pi f_0 C_1 d$, $c = A_v + 1$

$R_2 = 99.68 \text{ K}$ —Let $R_2 = 100 \text{ K}$

$$R_1 = R_2 / A_v, \quad R_1 = 10.0 \text{ K}$$

$$R_3 = [(2\pi f_0)^2 R_2 C_1 C_2]^{-1}$$

$R_3 = 5.389 \text{ K}$ —Let $R_3 = 5.36 \text{ K}$

Check using chosen values


$$|A_{v|f}| = 10, \quad f_0 = 1003 \text{ Hz}, \quad d = 1.002, \quad f_c = 1275 \text{ Hz},$$

$$|A_{v|fo}| = 9.985$$

Second Order
12 dB/Octave

**FILTER
LOWPASS
MULTIPLE FEEDBACK**

Unity Gain
Std. Cap. Values

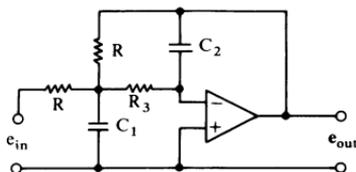

$$|A_{vif}| = R/R = 1, \quad |A_{vfo}| = d^{-1}$$

$$d = \sqrt{(RR_3C_2/C_1)(2/R + R_3^{-1})^2}, \quad f_0 = [2\pi\sqrt{RR_3C_1C_2}]^{-1}$$

$$f_c = f_0\sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c/\sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0\sqrt{1 - d^2/2}$$

when $d < \sqrt{2}$
(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log(2/[d\sqrt{4 - d^2}]) \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log[\sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}]^{-1}$$

$$(\theta_{eo} - \theta_{ei}) = [\tan^{-1}(d/[(f_0/f) - (f/f_0)])] \pm 180^\circ$$

Example and Design Formulas

Let $d = \sqrt{2}$ (Butterworth) and $f_c = 1000$ Hz,

$$f_0 = f_c \text{ when } d = \sqrt{2}$$

$C_2 \approx (1 \mu\text{F to } 10 \mu\text{F}) d/f_0$, $C_2 \approx .0014 \mu\text{F to } .014 \mu\text{F}$ —use

$$R_3 = \sqrt{[b \pm \sqrt{b^2 - 16}]/8/[2\pi f_0 \sqrt{C_1 C_2}]}$$

where $b = d^2 C_1 / C_2 - 4$

$R_3 = 16.54 \text{ K}$ —use 16.5 K

$$R = [(2\pi f_0)^2 R_3 C_1 C_2]^{-1}$$

$R = 14.81 \text{ K}$ —use 14.7 K


Check using chosen values

$$|A_{vif}| = 1, \quad f_0 = 1005 \text{ Hz}, \quad d = 1.416, \quad f_c = 1004 \text{ Hz}$$

Second Order
12 dB/Octave

**FILTER
LOWPASS
MULTIPLE FEEDBACK**

Unity Gain
Equal Resistor

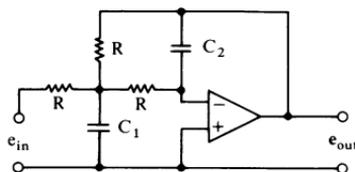

$$|A_{vlf}| = 1, \quad |A_{vfo}| = d^{-1}$$

$$d = \sqrt{9C_2/C_1}, \quad C_1 = 3/(2\pi f_0 R d), \quad C_2 = d/(6\pi f_0 R)$$

$$f_0 = [2\pi R \sqrt{C_1 C_2}]^{-1}, \quad C_1 = [C_2 (2\pi f_0 R)^2]^{-1},$$

$$C_2 = [C_1 (2\pi f_0 R)^2]^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}}$$

$$\text{where } a = 1 - d^2/2$$

$$f_{pk} = f_0 \sqrt{1 - d^2/2}$$

$$\text{when } d < \sqrt{2}$$

$$\text{(no peak when } d \geq \sqrt{2}\text{)}$$

$$|A_{vpk}|_{dB} = 20 \log \left(2 / [d \sqrt{4 - d^2}] \right) \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log \left[\sqrt{(f/f_0)^4 + (f/f_0)^2 (d^2 - 2) + 1} \right]^{-1}$$

$$(\theta_{eo} - \theta_{ei}) = \left[\tan^{-1} \left(d / [(f_0/f) - (f/f_0)] \right) \right] \pm 180^\circ$$

Design Formulas and Example

Let $d = \sqrt{2}$ (Butterworth) and $f_c = 1000$ Hz

Choose C_1, C_2 for $C_1/C_2 \approx 9/d^2$ ratio—use $C_1 = .015 \mu\text{F}$,

$C_2 = .0033 \mu\text{F}$

$f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}}$ where $a = 1 - d^2/2$, $f_0 = 1000$ Hz

$R = [2\pi f_0 \sqrt{C_1 C_2}]^{-1}$, $R = 22.6$ K—use 22.6 K

Check using chosen values


$f_0 = [2\pi R \sqrt{C_1 C_2}]^{-1} = 1001$ Hz, $d = \sqrt{9C_2/C_1} = 1.407$

$f_c = 1006$ Hz, $f_{pk} = 100.1$ Hz, $A_{vpk} = .0004$ dB

18 dB/Octave
Butterworth

**FILTER
LOWPASS
MULTIPLE FEEDBACK**

Third Order
Unity Gain

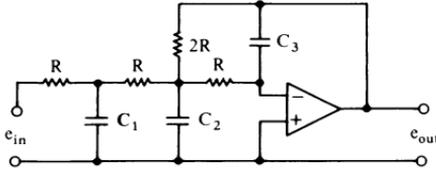

Butterworth Response

$$C_1 = 2.455/(2\pi f_c R)$$

$$C_2 = 2.109/(2\pi f_c R)$$

$$C_3 = .1931/(2\pi f_c R)$$

$$f_c = [2\pi R(C_1 C_2 C_3)^{\frac{1}{3}}]^{-1}$$

$$|A_V|_{vlf} = 1, \quad |A_V|_{vfo} = \sqrt{.5} = -3.01 \text{ dB}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log[\sqrt{(f/f_0)^6 + 1}]^{-1}$$

1000 Hz Example

$$R = 10 \text{ K}$$

$$C_1 = .039 \mu\text{F}$$

$$C_2 = .033 \mu\text{F}$$

$$C_3 = .003 \mu\text{F}$$


$$f_c = 1015 \text{ Hz}$$

$$|e_{out}/e_{in}| = -18 \text{ dB at } 2f_0 = -60 \text{ dB at } 10f_0$$

Independent Gain
18 dB/Octave

**FILTER
LOWPASS
MULTIPLE FEEDBACK**

Third Order
Std. Cap. Values

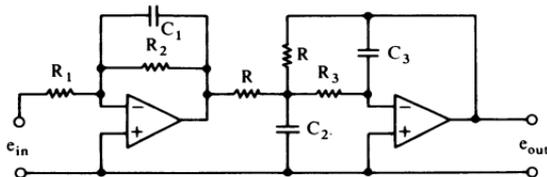

$$|A_V|_{vlf} = R_2/R_1$$

RESPONSE	R_2	R	R_3	C_3/C_2	f_b/f_c
Bessel	.7651a	1.364b	1.589b	.22	—
Butterworth	1.000a	2.764b	3.618b	.1	—
.1 dB Dip Chebyshev	1.433a	4.993b	3.362b	.068	.7199
.5 dB Dip Chebyshev	1.864a	5.032b	7.181b	.033	.8565
1 dB Dip Chebyshev	2.215a	5.783b	9.478b	.022	.9134
2 dB Dip Chebyshev	2.799a	7.630b	10.514b	.015	.9683
3 dB Dip Chebyshev	3.349a	7.505b	11.175b	.01	.9997

$a = (2\pi f_c C_1)^{-1}$ (C_1 may be chosen to be the same value as C_2)

$b = (2\pi f_c C_2)^{-1}$ (Choose C_2 to be .001, .01, .1 etc for std. value C_3)

f_c = Cutoff, corner, half-power or $R_2/R_1 - \sqrt{1/2}$ frequency

f_b = Rippleband-edge frequency e.g. The upper $R_2/R_1 - 1$ dB frequency in a 1 dB lowpass Chebyshev filter

$$|A_V|_{dip} = |A_{vfb}|, \quad |A_{vpk}| = |A_V|_{vlf} \quad (\text{Chebyshev})$$


$$f_{dip} = f_b/2, \quad f_{pk} = .8660f_b \quad (\text{Chebyshev})$$

$$|e_{out}/e_{in}|_{dB} = 20 \log(R_2/[R_1\sqrt{1 + (f/f_c)^6}]) \quad (\text{Butterworth})$$

Second Order
12 dB/Octave

**FILTER
LOWPASS
SALLEN-KEY ①**

General
Formulas

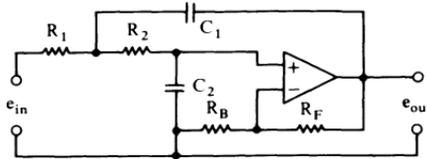

$$|A_{vlf}| = 1 + R_F/R_B, \quad |A_{vfo}| = (1 + R_F/R_B)/d,$$

$$|A_{vfc}| = (1 + R_F/R_B)/\sqrt{2}$$

$$d = [(C_2/C_1)(R_2/R_1 + 1) - R_F/R_B]/\sqrt{(C_2/C_1)(R_2/R_1)}$$

$$f_0 = [2\pi\sqrt{R_1 R_2 C_1 C_2}]^{-1}, \quad R_1 R_2 C_1 C_2 = [(2\pi f_0)^2]^{-1}$$

$$f_c = f_0\sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c/\sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0\sqrt{1 - d^2/2}, \quad f_0 = f_{pk}/\sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2}$$

$$|A_{vpk}|_{dB} = 20 \log [2(1 + R_F/R_B)/d\sqrt{4 - d^2}] \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB}$$

$$= 20 \log [(1 + R_F/R_B)/\sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}]$$

$$(\theta_{eo} - \theta_{ei}) = \tan^{-1} (d / [(f_0/f) - (f/f_0)])$$

$$(C_2/C_1) = [b + \sqrt{b^2 - 4ac}]/2a$$

$$\text{where } a = R_2/R_1 + R_1/R_2 + 2$$

$$b = (2R_F/R_B)(1 + R_1/R_2) + d^2$$

$$c = (R_F/R_B)^2(R_1/R_2)$$

$$(R_F/R_B) = (C_2/C_1)(R_2/R_1 + 1) - d\sqrt{(C_2/C_1)(R_2/R_1)}$$

$$(R_2/R_1) = [b + \sqrt{b^2 - 4ac}]/2a$$

$$\text{where } a = C_2/C_1, \quad b = 2R_F/R_B + d^2 - 2C_2/C_1$$


$$c = C_2/C_1 - 2R_F/R_B + (R_F/R_B)^2(C_1/C_2)$$

① Sallen-Key filters are also known as single feedback, voltage controlled voltage source and VCVS filters.

**Second Order
12 dB/Octave**

**FILTER
LOWPASS
SALLEN-KEY**

**Unity Gain
Std. Cap. Values**

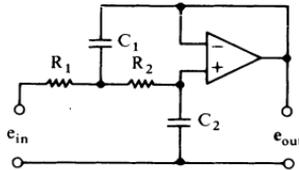

$$|A_{vlf}| = 1, \quad |A_{vfo}| = 1/d, \quad |A_{vfc}| = 1/\sqrt{2}$$

$$d = \sqrt{(C_2/C_1)(R_2/R_1 + R_1/R_2 + 2)}$$

$$f_0 = [2\pi\sqrt{R_1 R_2 C_1 C_2}]^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0 \sqrt{1 - d^2/2}$$

when $d < \sqrt{2}$
(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log[2/d\sqrt{4 - d^2}] \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log[\sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}]^{-1}$$

$$(\theta_{eo} - \theta_{ei}) = \tan^{-1}(d/[(f_0/f) - (f/f_0)])$$

Design Formulas and Example

Let $f_c = 1000$ Hz and $A_{vpk} = 1$ dB

$$d = \left(2 - \left[4 - (4/[\log^{-1}(A_{vpk})_{dB}/20]^2)\right]^{\frac{1}{2}}\right)^{\frac{1}{2}}, \quad d = 1.045$$

$$f_0 = f_c / \sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2)^2 + 1}}, \quad f_0 = 802.8$$
 Hz

$$C_2 \approx (4 \mu\text{F})(d/f_0), \quad C_2 \approx .0042 \mu\text{F—use } .0047 \mu\text{F}$$

$$C_1 \geq 4C_2/d^2, \quad C_1 \geq .0172\text{—use } .022 \mu\text{F}$$

$$(R_2/R_1) = b \pm \sqrt{b^2 - 1} \quad \text{where } b = d^2 C_1 / 2C_2 - 1,$$

$$(R_2/R_1) = 2.748$$

$$R_1 = [2\pi f_0 \sqrt{(R_2/R_1) C_1 C_2}]^{-1}, \quad R_1 = 11.76 \text{ K—use } 11.8 \text{ K}$$


$$R_2 = R_1 (R_2/R_1), \quad R_2 = 32.4 \text{ K—use } 32.4 \text{ K}$$

Check: $d = 1.045$, $f_0 = 800.5$ Hz, $f_c = 997.4$ Hz, $A_{vpk} = 1.0$ dB

Second Order
12 dB/Octave

**FILTER
LOWPASS
SALLEN-KEY**

Gain = Two
Equal Capacitor

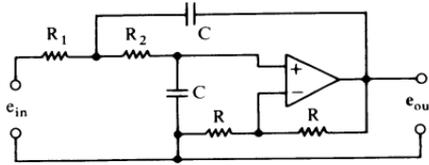

$$|A_{vif}| = 2, \quad |A_{vfo}| = 2/d, \quad |A_{vfc}| = 2/\sqrt{2}$$

$$d = \sqrt{R_2/R_1}, \quad R_2/R_1 = d^2$$

$$f_0 = [2\pi C \sqrt{R_1 R_2}]^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}} \quad \text{where } a = 1 - d^2/2$$

$$R_1 = [2\pi f_0 C d]^{-1}$$

$$R_2 = d/(2\pi f_0 C)$$

$$f_{pk} = f_0 \sqrt{1 - d^2/2} \quad \text{when } d < \sqrt{2}$$

(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log[4/d\sqrt{4 - d^2}] \quad \text{when } d < \sqrt{2}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log[2/\sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}]$$

$$(\theta_{eo} - \theta_{ei}) = \tan^{-1}(d/[(f_0/f) - (f/f_0)])$$

Design Formulas and Example

Let $f_c = 1000$ Hz, $d = 1.158$ (.5 dB peak) and $R = 10$ K

$$f_0 = f_c / \sqrt{(1 - d^2/2) + \sqrt{(1 - d^2/2)^2 + 1}}, \quad f_0 = 850.4$$
 Hz

$$C \approx (10 \mu\text{F})/f_0, \quad C \approx .012 \mu\text{F} \text{—use } .01 \mu\text{F}$$

$$R_1 = [2\pi f_0 C d]^{-1}, \quad R_1 = 16.2 \text{ K—use } 16.2 \text{ K}$$


$$R_2 = R_1 d^2, \quad R_2 = 21.7 \text{ K—use } 21.5 \text{ K}$$

Check: $f_0 = 852.8$ Hz, $f_c = 1003$ Hz, $d = 1.152$, $A_{vpk} = 6.54$ dB

Second Order
12 dB/Octave

**FILTER
LOWPASS
SALLEN-KEY**

Free Gain
Equal Capacitor

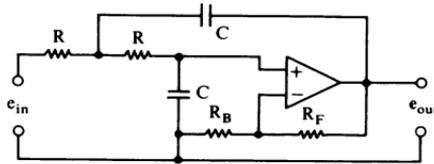

$$|A_{vlf}| = 1 + R_F/R_B, \quad |A_{vfo}| = (1 + R_F/R_B)/d,$$

$$|A_{vfc}| = (1 + R_F/R_B)/\sqrt{2}$$

$$d = 2 - R_F/R_B$$

$$f_0 = [2\pi RC]^{-1}$$

$$f_c = f_0 \sqrt{a + \sqrt{a^2 + 1}}, \quad f_0 = f_c / \sqrt{a + \sqrt{a^2 + 1}}$$

where $a = 1 - d^2/2$

$$f_{pk} = f_0 \sqrt{1 - d^2/2}$$

when $d < \sqrt{2}$
(no peak when $d \geq \sqrt{2}$)

$$|A_{vpk}|_{dB} = 20 \log [2(1 + R_F/R_B)/d\sqrt{4 - d^2}]$$

when $d < \sqrt{2}$


$$|e_{out}/e_{in}|_{dB} = 20 \log [(1 + R_F/R_B)/\sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}]$$

RESPONSE	A_v	R_F/R_B	d	f_c
Bessel (Best Delay)	1.268	.2679	1.732	.7861 f_0
Compromise	1.435	.4349	1.565	.8945 f_0
Butterworth (Flattest)	1.586	.5858	1.414	1.000 f_0
.1 dB Peak Chebyshev	1.697	.6968	1.303	1.078 f_0
.5 dB Peak Chebyshev	1.842	.8422	1.158	1.176 f_0
1 dB Peak Chebyshev	1.955	.9545	1.045	1.246 f_0
2 dB Peak Chebyshev	2.114	1.114	.8860	1.333 f_0
3 dB Peak Chebyshev	2.234	1.234	.7665	1.389 f_0

Unity Gain
18 dB/Octave

**FILTER
LOWPASS
SINGLE FEEDBACK**

Third Order
Equal Resistor

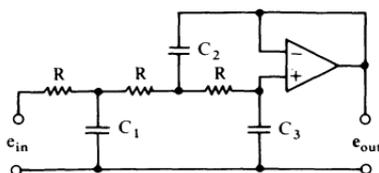

RESPONSE	C ₁	C ₂	C ₃	f _b /f _c	f _c /f _b	ε
Bessel	.9680a	1.423a	.2538a	—	—	—
Butterworth	1.392a	3.546a	.2024a	—	—	—
.1 dB Chebyshev	1.825a	6.653a	.1345a	.7199	1.3890	.15262
.5 dB Chebyshev	2.250a	11.23a	.08950a	.8565	1.1675	.34931
1 dB Chebyshev	2.567a	16.18a	.06428a	.9134	1.0948	.50885
2 db Chebyshev	3.113a	27.82a	.03892a	.9683	1.0327	.76479
3 dB Chebyshev	3.629a	43.42a	.02533a	.9997	1.0003	.99763

$$a = (2\pi f_c R)^{-1}$$

f_c = Cutoff, corner or half power frequency = f_{-3.01 dB}

f_b = Rippleband-edge frequency. e.g. The upper -1 dB frequency in a 1 dB Chebyshev lowpass filter

$$f_{\text{dip}} = f_b/2, \quad |A_v|_{\text{dip}} = |A_{v\text{rlb}}|, \quad |A_{v\text{pk}}| = 1 \quad (\text{Chebyshev})$$

$$f_{\text{pk}} = .8660f_b \quad (\text{Chebyshev})$$


$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left(\sqrt{1 + \epsilon^2 [4(f/f_b)^3 - 3(f/f_b)]^2} \right)^{-1} \quad (\text{Chebyshev})$$

$$|e_{\text{out}}/e_{\text{in}}|_{\text{dB}} = 20 \log \left[\sqrt{(f/f_c)^6 + 1} \right]^{-1} \quad (\text{Butterworth})$$

Gain = Two
18 dB/Octave

**FILTER
LOWPASS
SINGLE FEEDBACK**

Third Order
Equal Capacitor

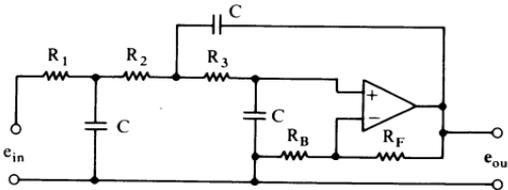

Butterworth Response

Example

$$R_F = R_B, \quad |A_V|_{vif} = 2, \quad |A_{vfc}| = \sqrt{2} \quad R_F = R_B = 10.0 \text{ K}$$

$$R_1 = 1.565 / (2\pi f_c C) \quad C = .01 \mu\text{F}$$

$$R_2 = 1.469 / (2\pi f_c C) \quad R_1 = 24.9 \text{ K}$$

$$R_3 = .4348 / (2\pi f_c C) \quad R_2 = 23.2 \text{ K}$$

$$f_c = [2\pi C(R_1 R_2 R_3)^{\frac{1}{3}}]^{-1} \quad R_3 = 6.98 \text{ K}$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [2 / \sqrt{(f/f_c)^6 + 1}] \quad f_c = 1000 \text{ Hz}$$

1 dB Dip Chebyshev Response, $R_F = R_B$

$$|A_V|_{vif} = |A_{vpk}| = 6 \text{ dB}, \quad |A_{vfc}| = 3 \text{ dB}, \quad |A_{vfb}| = 5 \text{ dB}$$

f_b = Rippleband Edge = Upper 1 dB down frequency

$$R_1 = 2.275 / (2\pi f_b C), \quad R_1 = 2.491 / (2\pi f_c C)$$

$$R_2 = 3.644 / (2\pi f_b C), \quad R_2 = 3.990 / (2\pi f_c C)$$

$$R_3 = .2455 / (2\pi f_b C), \quad R_3 = .2688 / (2\pi f_c C)$$

$$f_b = 1.267 / [2\pi C(R_1 R_2 R_3)^{\frac{1}{3}}], \quad f_c = 1.387 / [2\pi C(R_1 R_2 R_3)^{\frac{1}{3}}]$$

$$f_{+5dB} = 1.000f_b \text{ and } .5000f_b = .9134f_c \text{ and } .4567f_c$$


$$f_c = 1.095f_b, \quad f_b = .9134f_c$$

$$|e_{out}/e_{in}|_{dB} = 20 \log [2 / \sqrt{1 + .25893 [4(f/f_b)^3 - 3(f/f_b)]^2}]$$

Gain = Two
18 dB/Octave

**FILTER
LOWPASS
SINGLE FEEDBACK**

Third Order
Equal Capacitor

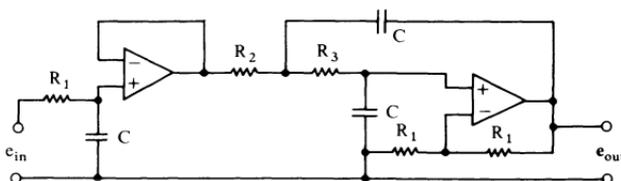

RESPONSE	R_1	R_2	R_3	f_b/f_c	ϵ
Bessel	.7561a	.4774a	.9996a	—	—
Butterworth	1.000a	1.000a	1.000a	—	—
.1 dB Dip Chebyshev	1.433a	1.433a	.7969a	.7199	.15262
.5 dB Dip Chebyshev	1.864a	1.864a	.6402a	.8565	.34931
1 dB Dip Chebyshev	2.215a	2.215a	.5442a	.9134	.50885
2 dB Dip Chebyshev	2.799a	2.799a	.4299a	.9683	.76479
3 dB Dip Chebyshev	3.349a	3.349a	.3560a	.9997	.99763

$$a = (2\pi f_c C)^{-1}$$

f_c = Cutoff, corner, half-power or 3.01 dB down frequency

f_b = Rippleband-edge frequency. e.g. The upper 1 dB down frequency in a lowpass 1 dB Chebyshev filter

$$|A_{V|dip}| = |A_{V|fb}|, \quad |A_{V|pk}| = |A_{V|vif}| = 2 \quad (\text{Chebyshev})$$

$$f_{dip} = f_b/2, \quad f_{pk} = .8660f_b \quad (\text{Chebyshev response})$$


$$|e_{out}/e_{in}|_{dB} = 20 \log\left(2/\sqrt{1 + \epsilon^2[4(f/f_b)^3 - 3(f/f_b)]^2}\right) \quad (\text{Chebyshev})$$

$$|e_{out}/e_{in}|_{dB} = 20 \log\left(2/\sqrt{1 + (f/f_c)^6}\right) \quad (\text{Butterworth})$$

Free Gain
24 dB/Octave

**FILTER
LOWPASS
SINGLE FEEDBACK**

Fourth Order
Equal Capacitor

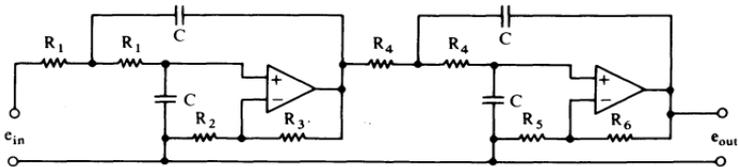

	R_1	R_3/R_2	R_4	R_6/R_5	$ A_{V _{vif}}$	f_b/f_c
Bessel	.6993a	.084	.6234a	.759	5.6 dB	—
Butterworth	1.000a	.154	1.000a	1.235	8.2 dB	—
.1 dB Chebyshev	1.537a	.384	1.052a	1.542	10.9 dB	.8243
.5 dB Chebyshev	1.831a	.582	1.060a	1.660	12.5 dB	.9148
1 dB Chebyshev	1.992a	.725	1.060a	1.719	13.4 dB	.9497
2 dB Chebyshev	2.164a	.924	1.057a	1.782	14.6 dB	.9820
3 dB Chebyshev	2.259a	1.07	1.052a	1.821	15.3 dB	.99985

$$a = (2\pi f_c C)^{-1}$$

f_c = Cutoff, corner, half-power or 3.01 dB down frequency

f_b = Rippleband-edge frequency. The highest frequency where gain equals $|A_{V|_{vif}}$ (Chebyshev)


$|A_{Vpk}| = |A_{V|_{vif}} + 1$ dB in a 1 dB filter, $|A_{V|_{vif}} + 2$ dB in a 2 dB filter etc. (Chebyshev)

$|A_{V|_{vif}} = |A_{V|_{dip}} = |A_{Vrb}|$ (Chebyshev)

$f_{pk} = .9242f_b$ and $.3828f_b$, $f_{dip} = .7071f_b$ (Chebyshev)

FILTER NOTCH ACTIVE INDUCTOR

High Q
Series Shunt

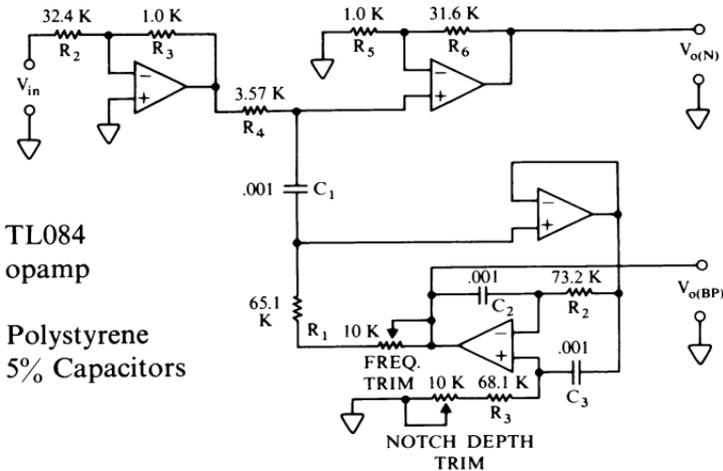

$A_{V(N)} \approx 1$ except near notch frequency

$|A_{V(O)BP}| \approx 1, |A_{V(O)N}| < -50 \text{ dB}$

$f_{0(N)} = f_{0(BP)} = 2175 \text{ Hz}$

$Q_{BP} \approx 21.5$

$BW_{BP} \approx 101 \text{ Hz}$

$BW_{N(-3 \text{ dB})} \approx 101 \text{ Hz}, BW_{N(-20 \text{ dB})} \approx 7 \text{ Hz},$

$BW_{N(-30 \text{ dB})} \approx 3 \text{ Hz}$

When $R_2 C_2 = R_3 C_3$:

$f_0 = [2\pi\sqrt{C_1 C_2 R_1 R_2}]^{-1}$


$Q = (2\pi f_0 R_4 C_1)^{-1}$

$A_{V(N)} = (R_3/R_2)(R_6/R_5 + 1)$ except near notch frequency

$L = R_1 R_2 C_2$

FILTER NOTCH ALLPASS

Unity Gain
Except Near f_N

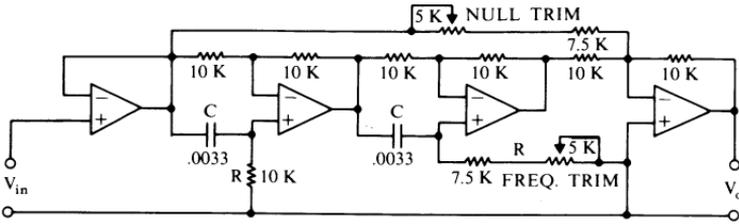


$$f_N = (2\pi RC)^{-1} \approx 5000 \text{ Hz}$$

$$(4 \tan^{-1} X_c/R = 180^\circ \text{ at } 5000 \text{ Hz})$$

$$|A_V|_{\text{NOTCH}} < -40 \text{ dB}, \quad BW_{N(-40 \text{ dB})} < 10 \text{ Hz},$$

$$BW_{N(-3 \text{ dB})} \approx 3000 \text{ Hz}$$

$$|V_o/V_{in}| = 1 \quad \text{except near } f_N$$

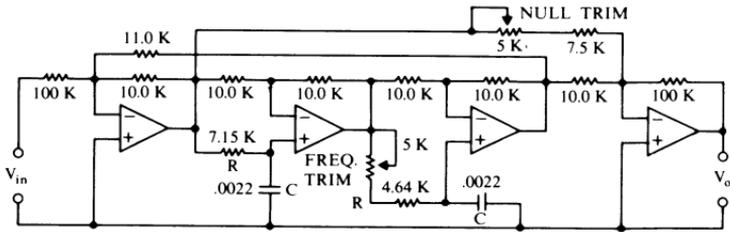

$$f_N = (2\pi RC)^{-1} \approx 10 \text{ kHz}$$

$$|A_V|_{\text{NOTCH}} < -40 \text{ dB}, \quad BW_{N(-40 \text{ dB})} < 5 \text{ Hz},$$

$$BW_{N(-3 \text{ dB})} \approx 1000 \text{ Hz}$$


$$|V_o/V_{in}| = 1 \quad \text{except near } f_N$$

FILTER NOTCH MULTIPLE FEEDBACK

Unity Gain
Except Near f_N

TL082
Opamp

5% Mylar
Capacitors

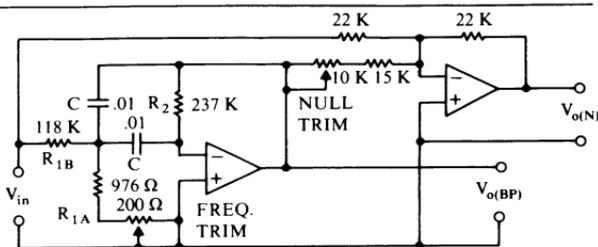

$$|A_{VO}|_N = -40 \text{ dB}, \quad BW_{N(-40 \text{ dB})} < 1 \text{ Hz}$$

$$BW_{N(-3 \text{ dB})} \approx 135 \text{ Hz}$$

$$|A_{VO}|_{BP} = R_2/2R_{1B}$$


$$f_{0(BP)} = f_{0(N)} = [2\pi C \sqrt{R_2/(R_{1A}^{-1} + R_{1B}^{-1})}]^{-1} = 1 \text{ kHz}$$

$$Q_{BP} = \sqrt{R_2/[4(R_{1A} + R_{1B})]} \approx 7.4$$

$$|V_o/V_{in}|_N = R_2/2R_{1B} = 1 \quad \text{except near } f_N$$

TL082
Opamp

5% NPO
Capacitors

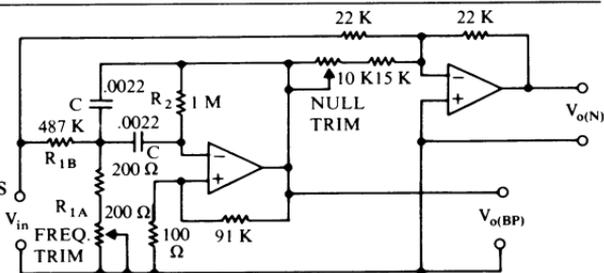

$$|A_V|_{\text{NOTCH}} < -40 \text{ dB}, \quad BW_{N(-40 \text{ dB})} < 1 \text{ Hz}$$

$$BW_{N(-3 \text{ dB})} \approx 140 \text{ Hz}$$

$$f_{0(N)} = f_{0(BP)} = [2\pi C \sqrt{R_2/(R_{1A}^{-1} + R_{1B}^{-1})}]^{-1} = 4 \text{ kHz}$$

$$Q_{BP} = \sqrt{R_2/[4(R_{1A} + R_{1B})]} \approx 28.9$$

$$|A_{VO}|_{BP} = R_2/2R_{1B} \approx 1$$


$$|V_o/V_{in}|_N = R_2/2R_{1B} \approx 1 \quad \text{except near } f_N$$

FILTER NOTCH STATE VARIABLE

Unity Gain
Except Near f_N

Opamps = 1, LF347

Capacitors = polystyrene

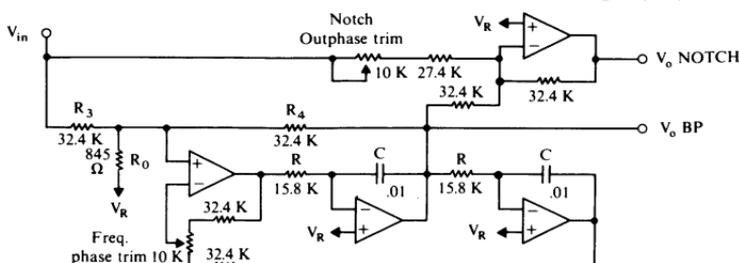

$$|A_V|_{\text{NOTCH}} < -40 \text{ dB}, \quad (BW_N)_{-40 \text{ dB}} < .5 \text{ Hz}$$

$$(BW_N)_{-3 \text{ dB}} \approx 50 \text{ Hz}$$


$$|A_{V0}|_{\text{BP}} = R_4/R_3 \approx 1, \quad f_{\text{BP}} = f_N = (2\pi RC)^{-1} = 1000 \text{ Hz}$$

$$Q_{\text{BP}} = (1 + R_4/R_3 + R_4/R_0)/2 \approx 20.2$$

$$|A_V|_N = 1 \quad \text{except near } f_N$$

Opamps = 1, LF347

Capacitors = 5% polystyrene

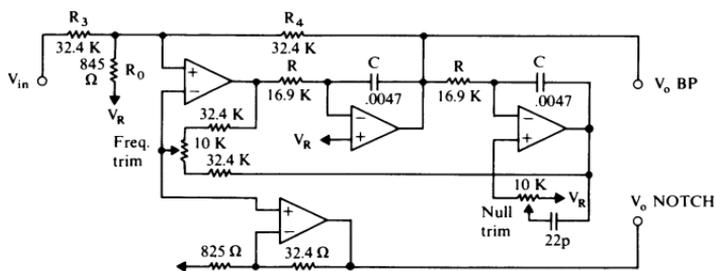

$$|A_{V0}|_{\text{NOTCH}} < -40 \text{ dB}, \quad \text{Notch BW}_{-40 \text{ dB}} < 1 \text{ Hz}$$


$$\text{Notch BW}_{-3 \text{ dB}} \approx 100 \text{ Hz}$$

$$|A_{V0}|_{\text{BP}} = R_4/R_3 \approx 1, \quad f_{\text{BP}} = f_N = (2\pi RC)^{-1} = 2000 \text{ Hz}$$

$$Q_{\text{BP}} = (1 + R_4/R_3 + R_4/R_0)/2 \approx 20.2$$

$$|A_V|_{\text{NOTCH}} = 1 \quad \text{except near } f_N$$

FILTER UNIVERSAL STATE VARIABLE

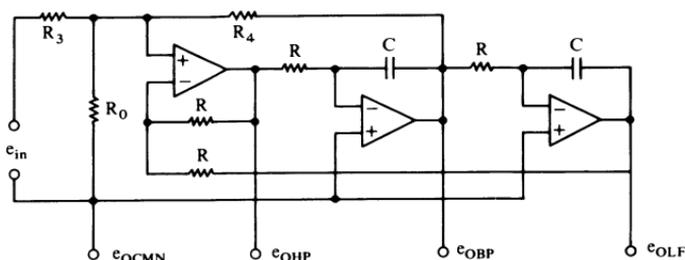

$$f_{\text{OHP}} = f_{\text{OBP}} = f_{\text{OLP}} = [2\pi RC]^{-1}$$

$$|A_{\text{vhf}}|_{\text{HP}} = |A_{\text{VO}}|_{\text{BP}} = |A_{\text{vlf}}|_{\text{LP}} = R_4/R_3$$

$$d_{\text{HP}} = Q_{\text{BP}}^{-1} = d_{\text{LP}} = 2/(1 + R_4/R_3 + R_4/R_0)$$

$$R_0 = R_4/(2/d - R_4/R_3 - 1)$$

$$|A_{\text{VO}}|_{\text{HP}} = |A_{\text{VO}}|_{\text{LP}} = R_4/R_3 d$$

$$|e_o/e_{\text{in}}|_{\text{HP}} = 20 \log$$

$$\left[R_4 / (R_3 \sqrt{(f_0/f)^4 + (f_0/f)^2(d^2 - 2) + 1}) \right] \text{ dB}$$

$$|e_o/e_{\text{in}}|_{\text{BP}} = 20 \log \left[R_4 / (R_3 \sqrt{1 + Q^2 [(f/f_0) - (f_0/f)]^2}) \right] \text{ dB}$$

$$|e_o/e_{\text{in}}|_{\text{LP}} = 20 \log$$

$$\left[R_4 / (R_3 \sqrt{(f/f_0)^4 + (f/f_0)^2(d^2 - 2) + 1}) \right] \text{ dB}$$

Example

Let $A_v = 1$, $f_0 = 1000 \text{ Hz}$ and $d = 1$


Let $C = .01 \mu\text{F}$, $R = [2\pi f_0 C]^{-1} = 15.9 \text{ K}$ —Use 15.8 K

Let $R_3 = 15.8 \text{ K}$, $R_4 = A_v R_3 = 15.8 \text{ K}$


$R_0 = R_4 / (2/d - R_4/R_3 - 1) = \infty$ —delete R_0

Check: $A_v = 1$, $f_0 = 1007 \text{ Hz}$, $d = 1$

LATCH (BISTABLE MULTIVIBRATOR)

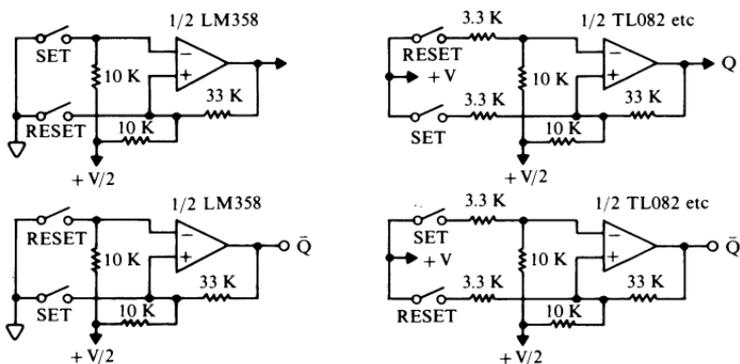

ONE OF N LATCH (LAST OPERATED ONLY)

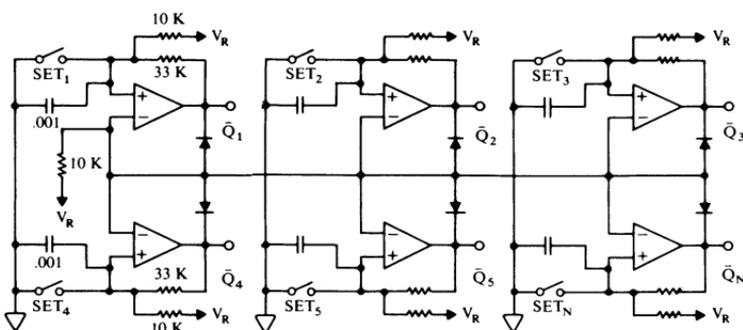

Opamps = 1/2 LM358 or 1/4 LM324,

Diodes = 1N914 or 1N4148

$V_R = +V/2$ (Capacitors unnecessary with clean wiring)

**MULTIVIBRATOR
ASTABLE
SEE—OSCILLATOR, SQUAREWAVE**

**MULTIVIBRATOR
BISTABLE
SEE—LATCH**

**MULTIVIBRATOR
MONOSTABLE
SEE—ONE-SHOT**


General Opamp Section Notes

1. $\text{---}\text{⊙}\text{---}$ is the graphic symbol for an infinite impedance alternating current generator (an ac current source). In practice, any very high impedance source of current.
2. $\text{---}\text{⊖}\text{---}$ is the graphic symbol for a zero impedance signal generator (an ac voltage source). In practice, any very low impedance and low resistance source of voltage.
3. A negative resultant for A_v or V_o indicates that a phase inversion has taken place (output 180° out of phase with the input).
4. 6 dB per octave equals 20 dB per decade, 12 dB per octave equals 40 dB per decade etc.
5. $|x|$ = the magnitude or the absolute value of x .
6. $\log x = \log_{10} x$, $\log^{-1} x = \text{antilog}_{10} x = 10^x$.
7. $x^{-1} = 1/x$, $x^{\frac{1}{2}} = \sqrt{x}$.
8. Source resistance, if significant, must be considered as an additional resistance in series with circuit input.
9. When supply voltage connections are not shown, a split supply is assumed with V_{CC} positive with respect to common (ground) and V_{EE} negative with respect to common (ground).

ONE-SHOT (MONOSTABLE MULTIVIBRATOR)

Opamp =
1/2 LM358

Diodes =
1N4148

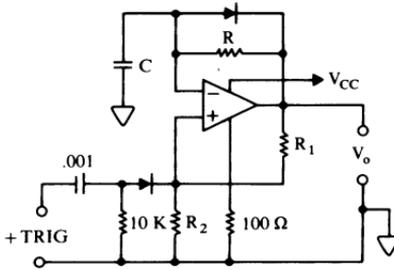


$$t_{on} = -RC(\ln[1 - (R_1/R_2 + 1)^{-1}])$$

$$t_{on} = RC \quad \text{when } R_2/R_1 = 1.72$$

Opamp =
1/2 LM358

Diodes =
1N4148

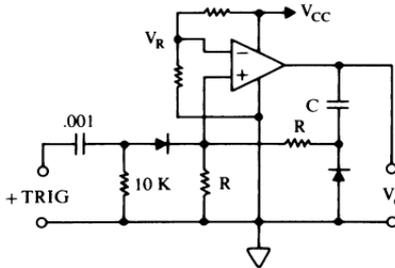


$$t_{on} = 2RC(\ln[V_{o(MAX)}/2V_R])$$

$$(V_{o(MAX)} \approx V_{CC} - 1.2 \text{ when } I_o \leq 1 \text{ mA})$$


$$t_{on} = 2RC \quad \text{when } V_R = .184V_{o(MAX)}$$

For use as a pulse stretcher or off-delay circuit, short the .001 μ F capacitor.

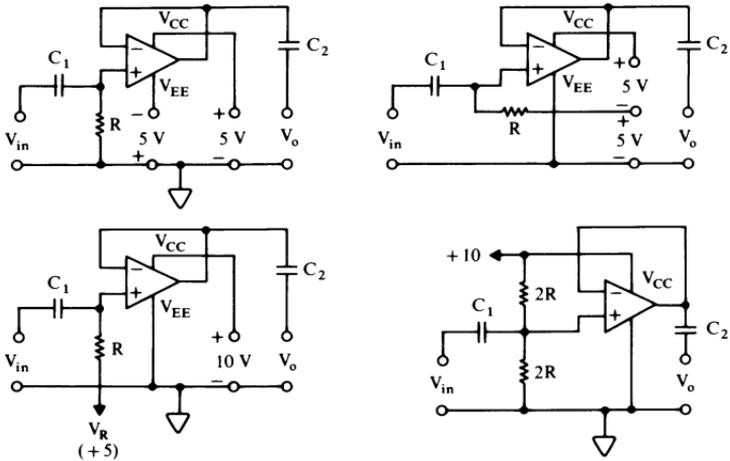OPAMP BIASING DUAL TO SINGLE SUPPLY CONVERSION



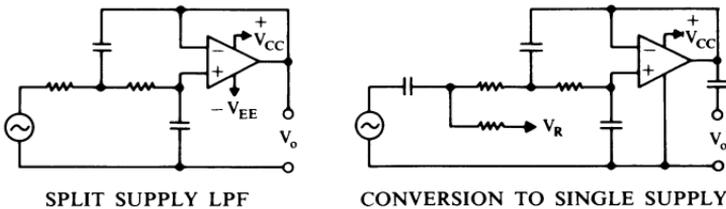
All of the above circuits have identical performance when the same “split supply” or “single supply” opamp is used.



All general purpose opamp inputs must have dc continuity to a dc voltage source, to ground or to an opamp output.

OPAMP BIASING SINGLE SUPPLY

$V_{O(DC)}$

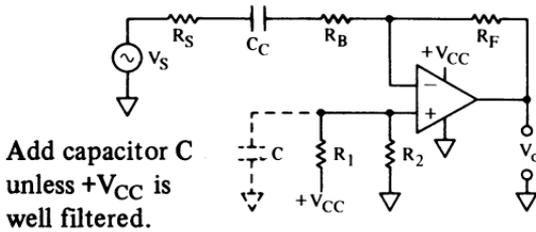


$$V_{O(DC)} = V_{CC}/2 \quad \text{when } R_1 = R_2$$

$$V_{O(DC)} = V_{CC}/[(R_1/R_2) + 1]$$

$$V_{O(AC)} = -A_V V_S$$

$$V_{O(AC)} = -(V_S R_F)/(R_B + R_S)$$

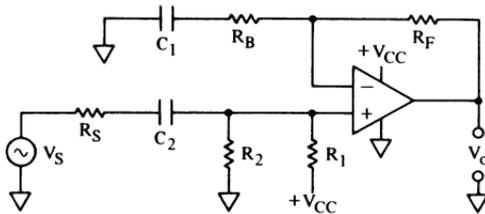

$$V_{O(DC)} = V_{CC}/2 \quad \text{when } R_1 = R_2$$

$$V_{O(DC)} = V_{CC}/[(R_1/R_2) + 1]$$


$$V_{O(AC)} \approx A_V V_S$$

$$V_{O(AC)} = V_S [(R_F/R_B) + 1] / [R_S (R_1^{-1} + R_2^{-1}) + 1]$$

Note: $+V_{CC}$ to R_1 must be well filtered. If R_S is low, such as the output impedance of another opamp stage, a large coupling capacitor (C_2) may provide proper filtering.

OPAMP BIASING SINGLE SUPPLY


$V_{O(DC)}$
 V_R, V_{REF}

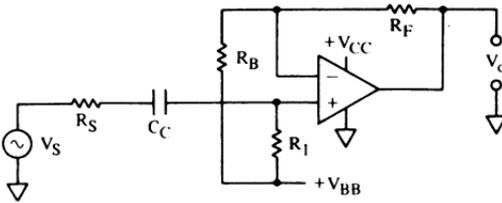

$$V_{O(DC)} = +V_{BB} \pm V_{OO} \quad \text{See } -V_{OO}$$

$$V_{O(AC)} = A_V V_S$$
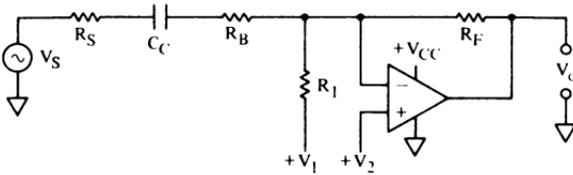
$$V_{O(AC)} = V_S [(R_F/R_B) + 1] / [(R_S/R_1) + 1]$$



$$V_{O(DC)} = (V_2 [(R_F/R_1) + 1]) - [V_1 (R_F/R_1) \pm V_{OO}]$$

$$V_{O(AC)} = A_V V_S$$

$$V_{O(AC)} = V_S [R_F / (R_B + R_S)]$$

Note: V_R is typically set to $V_{CC}/2$, but maximum output before clipping is obtained when $V_R \approx [(V_{CC} - 1.8)/2] + 1.2$ for standard opamps and when $V_R \approx [(V_{CC} - 1.8)/2] + .6$ for "single supply" opamps.

OPAMP NOISE VOLTAGE EQUIVALENT INPUT

V_{ni}

$$V_{ni} = V_{no}/A_v$$

V_{ni} = Total equivalent input rms noise voltage including:

1. Device equivalent input noise voltage (V_n)
2. The product of the device equivalent input noise current (I_n) and the sum of the effective source resistances at both inputs.
3. The thermal noise voltage (V_{nR}) of the effective source resistances at both inputs.


Note: All three noise voltages have components of $1/f$ noise as well as constant spectral density (white) noise. The device white noise component is shot noise and the white noise of resistance is thermal noise. The $1/f$ noise of resistances is excess noise or current noise. White noise voltage may be easily calculated from a spot noise voltage by multiplying by the square root of the noise bandwidth but $1/f$ noise or noise having a significant $1/f$ noise component must be averaged over the total bandwidth by the rms method. $1/f$ noise is usually neglected at frequencies above 1 kHz and is often assumed to have straight line response between the 100 Hz and 1 KHz spot noise measurement points.

$$V_{ni} = V_{no} \text{ when } A_v = 1$$

$$V_{ni} = \sqrt{BW[V_n^2 + I_n^2 R_S^2 + 4K_B T_K R_S]}$$

$$K_B = 1.38 \cdot 10^{-23}$$

$$T_K = ^\circ\text{C} + 273.15$$

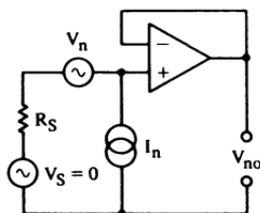

OPAMP NOISE VOLTAGE EQUIVALENT INPUT

V_{ni}

$$V_{ni} = V_{no}/A_v$$

$$V_{ni} = \sqrt{BW[V_1^2 + V_2^2 + V_3^2]}$$

where $V_1 = V_n$


$$V_2 = I_n R_X$$

$$R_X = [R_F^{-1} + (R_S + R_B)^{-1}]^{-1}$$

$$V_3 = \sqrt{4k_B T_K R_X}$$

k_B = Boltzmann constant ($1.38 \cdot 10^{-23} \text{ J}^\circ\text{K}$)

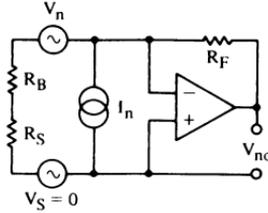T_K = Kelvin Temperature. ($^\circ\text{C} + 273.15$)



$$V_{ni} = V_{no}/A_v$$

$$V_{ni} = \sqrt{BW[V_1^2 + V_2^2 + V_3^2]}$$


where $V_1 = V_n, V_2 = I_n R_X$

$$R_X = R_S + (R_F^{-1} + R_B^{-1})^{-1}$$

$$V_3 = \sqrt{4k_B T_K R_X}$$


k_B = Boltzmann constant ($1.38 \cdot 10^{-23}$)

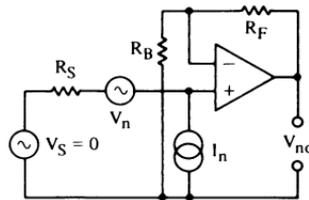T_K = Kelvin temperature. ($^\circ\text{C} + 273.15$)



OPAMP NOISE VOLTAGE OUTPUT

V_{no}

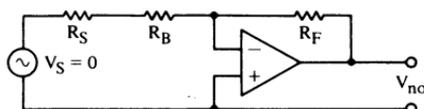

$$V_{no} = A_v \sqrt{BW} \cdot \sqrt{V_n^2 + (R_S + R_B)^2 (I_n^2 + 4kT_K R_F^{-1}) + 4k_B T_K (R_S + R_B)}$$

V_n = Equivalent input spot noise voltage of opamp at a given frequency. (usually given in nV/\sqrt{Hz} at 1 kHz)

I_n = Equivalent input spot noise current of opamp at a given frequency. (usually given in pA/\sqrt{Hz} at 1 kHz)

k_B = Boltzmann constant
 $k_B = 1.38 \cdot 10^{-23} \text{ J/}^\circ\text{K}$

T_K = Temperature in Kelvin
 $T_K = ^\circ\text{C} + 273.15$

A_v = Closed loop circuit voltage amplification (A_{vc1} or V_o/V_S)
 $A_v = R_F / (R_S + R_B)$

R_S = Source resistance

Notes:

Formula does not include opamp $1/f$ noise. (opamp $1/f$ noise usually is insignificant above 1 kHz)

Formula includes thermal noise of all external resistances, but does not include resistor excess noise (current noise or $1/f$ resistor noise)


Noise measurements require a bandwidth correction factor for all except rectangular response curves. See— BW_{NOISE} definition page 257

OPAMP NOISE VOLTAGE OUTPUT


V_{no}

Let $BW = 10 \text{ kHz}$

Let $T \approx 27^\circ\text{C}$

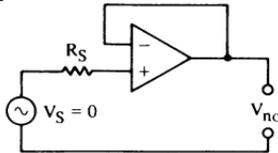
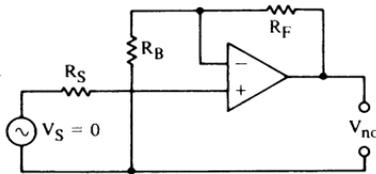
$$V_{no} = 100 \sqrt{V_n^2 + I_n^2 R_S^2 + 1.656 \cdot 10^{-20} R_S}$$



$$V_{no} = A_v \sqrt{BW} \sqrt{V_n^2 + I_n^2 (R_S + R_X)^2 + 4k_B T_K R_S}$$

V_n = Equivalent input spot noise voltage of opamp at a given frequency. (usually given in $\text{nV}/\sqrt{\text{Hz}}$ at 1 kHz)

I_n = Equivalent input spot noise current of opamp at a given frequency. (usually given in $\text{pA}/\sqrt{\text{Hz}}$ at 1 kHz)

T_K = Kelvin temperature ($^\circ\text{C} + 273.15$)

k_B = Boltzmann's constant ($1.38 \cdot 10^{-23}$)

$$R_X = R_F \parallel R_B = (R_F^{-1} + R_B^{-1})^{-1}$$


$$A_v = (R_F/R_B) + 1$$

See—Preceding page notes

**OPAMP
OUTPUT OFFSET
VOLTAGE**

V_{OO}

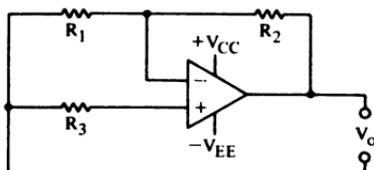**Output Offset Voltage
(input voltage(s) = 0)**



**Output from input offset voltage (V_{IO}) only
($I_{IO} = 0, I_{IB} = 0$)**

$$V_{OO} = V_{IO}(A_V + 1)$$

$$V_{OO} = V_{IO}[(R_2/R_1) + 1]$$

**Output from input offset current (I_{IO}) only
($V_{IO} = 0, R_3 = [R_1^{-1} + R_2^{-1}]^{-1}$)**

$$V_{OO} = I_{IO}R_3(A_V + 1)$$

$$V_{OO} = I_{IO}R_3[(R_2/R_1) + 1]$$

**Output from bias current (I_{IB}) only
($I_{IO} = 0, V_{IO} = 0$)**

$$V_{OO} = I_{IB}[R_3(A_V + 1) - R_2]$$



$$V_{OO} = I_{IB}[R_3(R_2/R_1 + 1) - R_2]$$

Total Output Offset Voltage

$$V_{OO} = [V_{IO}(A_V + 1)] + I_{IB}[R_3(A_V + 1) - R_2] \\ \pm [I_{IO}R_3(A_V + 1)]$$

**OPAMP
OUTPUT VOLTAGE
MAXIMUM PEAK TO PEAK**

$V_{OM(P-P)}$

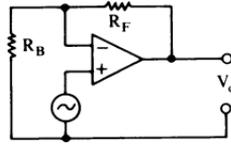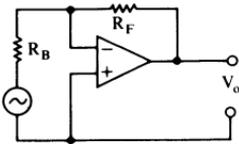

$$V_{OM(p-p)} = SR/(2\pi f)$$

when V_o is limited only by slew rate

$$V_{OM(p-p)} = \text{Total supply voltage minus } 1.8$$

when V_o is limited only by supply voltage and $R_L \geq 10 \text{ K}$. Symmetrical clipping at $V_{OM(p-p)}$ is obtained only when the output has been dc biased to the mid-point between $V_{OH(SAT)}$ and $V_{OL(SAT)}$. This mid-point voltage is not $V_{CC}/2$ in single supply circuits but $\approx [(V_{CC} - 1.8)/2] + 1.2\text{V}$ for "split supply" opamps and $\approx [(V_{CC} - 1.8)/2] + .6\text{V}$ for "single supply" opamps.



Note: A sinewave input signal is transferred into a triangular wave output signal by the effects of SR at outputs above SR limited $V_{OM(p-p)}$

Resistor R_F is effectively in parallel with the output load resistance R_L

OPAMP POWER BANDWIDTH

PBW

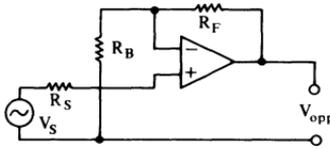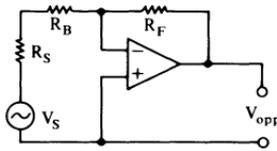PBW = In circuits where the low limit bandwidth is zero, the maximum frequency which may be used at a specified peak-to-peak output without the distortion (e.g. a sine wave becoming triangular) associated with slew rate (SR)



$$PBW = SR/(\pi V_{opp})$$


$$f_{(MAX)} = SR/(\pi V_{opp})$$

$$V_{opp(MAX)} = SR/(\pi f_{(MAX)})$$

$$SR_{(MIN)} = \pi f_{(MAX)} V_{opp(MAX)}$$

See Also – Opamp, SR
Opamp, V_{opp}

OSCILLATOR SINEWAVE BIQUAD

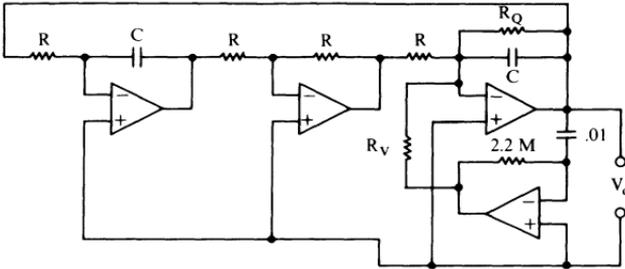


$$f_0 = [2\pi RC]^{-1}, \quad Q = R_Q(2\pi f_0 C)$$

$$V_{op-p} \approx 1.15(V_{CC} - 2)R_Q/R_V, \quad THD_{\%} \approx 100/Q$$

See Also—Filter, Bandpass, High Q

See Also—Filter, Bandpass, Biquad

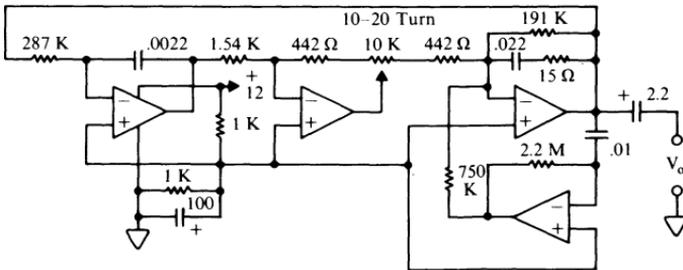VERY WIDE RANGE BIQUAD SINEWAVE OSCILLATOR



Min. Tuning Range = 300 to 4000 Hz

$$V_o \approx 3V_{p-p}$$

Quad Opamp IC
= LF347

.0022 and .022 Capacitors
= 5% NPO Ceramic


See Also—Filter, Bandpass, Biquad

OSCILLATOR SINEWAVE MISCELLANEOUS

WEIN BRIDGE OSCILLATOR

$$f_0 = [2\pi RC]^{-1} \approx 1000 \text{ Hz}$$

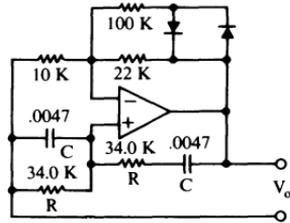
$$V_o \approx 2V_{p-p} \text{ (Very sensitive to tolerances)}$$




“LOWPASS VCVS” OSCILLATOR

$$f_0 = [2\pi R \sqrt{C_1 C_2}]^{-1} \approx 1000 \text{ Hz}$$
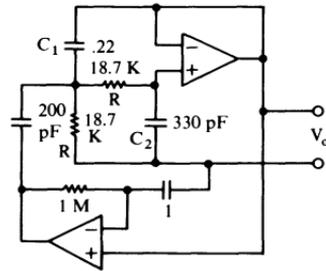
$$V_o \approx 3V_{p-p} \text{ when } V_s = 12$$


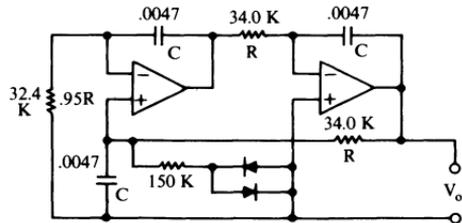
$$f_0 \approx [2\pi RC]^{-1} \\ \approx 1000 \text{ Hz}$$



$$V_o \approx 2V_{p-p} \text{ (Very sensitive to tolerances)}$$


OSCILLATOR SINEWAVE MULTIPLE FEEDBACK

Low
Distortion

Opamp = 1/2 LF353

Capacitors = 5% Mylar

Diodes = 1N4148

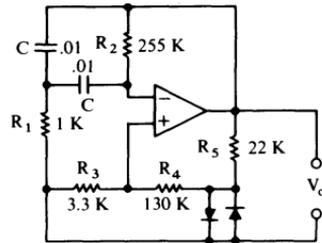

$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1}$$

$$V_{op-p} \approx [(R_2/2R_1) + 1]/(R_4/R_3 + 1)$$


$$\Delta V_{op-p} \approx -.04 \text{ dB}/^\circ\text{C}$$

$$(R_1/2R_2 + 1) > [1 + (R_4 + R_5)/R_3] \text{ for oscillation}$$

Opamp = LF353

Capacitors =
5% Polystyrene

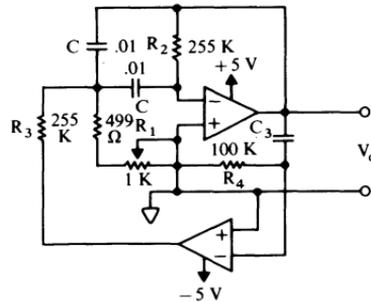R_4, C_3 unnecessary when:
 $(A_{VOL})_{dc} V_{IO} < 3$



$$f_0 = [2\pi C\sqrt{R_1 R_2}]^{-1} \approx 850 \text{ to } 1350 \text{ Hz}$$

$$V_{op-p} \approx (R_3/2R_2)[1.25(V_{SAT(HIGH)} - V_{SAT(LOW)})] \approx 4.4$$

$$A_{VOL} > 2R_2/R_3 \text{ for oscillation}$$

See Also—Filter, Bandpass, Multiple Feedback

OSCILLATOR SINEWAVE MULTIPHASE


THREE PHASE SINEWAVE OSCILLATOR

Opamps
= 3/4 TL084

Capacitors
= 5% Mylar

Diodes
= 1N4148

Power Supply = ± 5 V

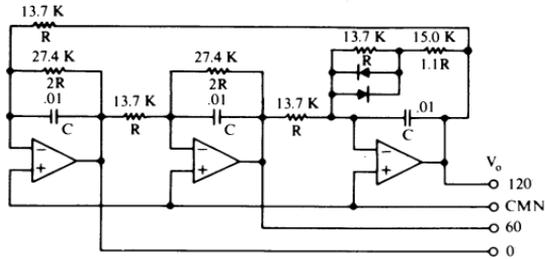

$$f_0 = \sqrt{3}/(4\pi RC) \approx 1000 \text{ Hz}$$

$$V_o \approx 3V_{p-p}$$


FOUR PHASE SINEWAVE OSCILLATOR

Opamp IC
= TL084

Capacitors
= 5% Mylar

Diodes
= 1N4148


Power Supply = ± 5 V

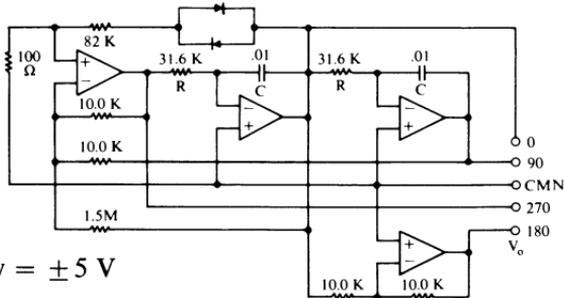

$$f_0 = [2\pi RC]^{-1} \approx 500 \text{ Hz}$$

$$V_o \approx 3V_{p-p}$$

OSCILLATOR SINEWAVE STATE VARIABLE

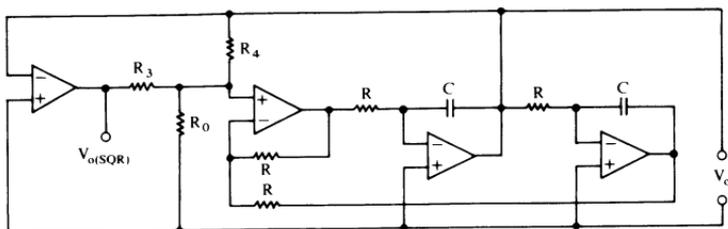


$$f_0 = [2\pi RC]^{-1}, \quad Q = (1 + R_4/R_3 + R_4/R_0)/2$$

$$V_{op-p} \approx 1.15V_{o(SQR)} R_4/R_3, \quad THD_{o/o} \approx 100/Q$$

$$V_{op-p(SQR)} \approx |V_{CC}| + |V_{EE}| - 2$$

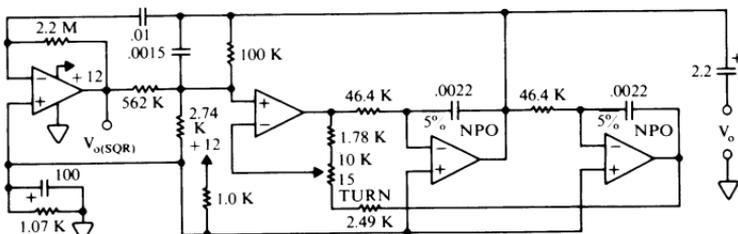WIDE RANGE STATE VARIABLE SINEWAVE OSCILLATOR




Min. Tuning Range = 600 to 3000 Hz

$$V_{op-p} \approx 2, \quad V_{op-p(SQR)} \approx 10$$

Quad Opamp IC = TL064

See Also—Filter, Bandpass, State Variable

OSCILLATOR PULSE

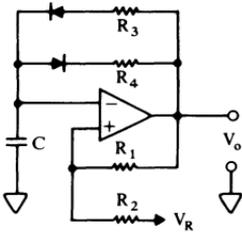


$$f_0 \approx 1000 \text{ Hz}$$

$$DF_H \approx 10\%$$

Opamp =
1/2 TL082

$$V_{op-p} \approx 10$$

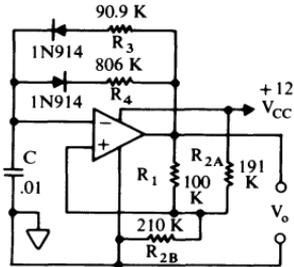

When $V_R = [(V_{SAT})_H + (V_{SAT})_L]/2$:

$$f_0 \approx \left(-C(R_3 + R_4) \left[\ln \left(1 - \left[\left(\frac{R_1}{2R_2} \right) + 1 \right]^{-1} \right) \right] \right)^{-1}$$

$$t_{VOH} \approx -CR_3 \left[\ln \left(1 - \left[\left(\frac{R_1}{2R_2} \right) + 1 \right]^{-1} \right) \right]$$


$$V_{op-p} = (V_{SAT})_H - (V_{SAT})_L \approx V_{CC} - 2$$

when R_3, R_4 and $R_L > 30 \text{ K}$

$$f_0 \approx 1000 \text{ Hz}$$

$$V_{op-p} \approx 10, \quad DF_H \approx 1\%$$

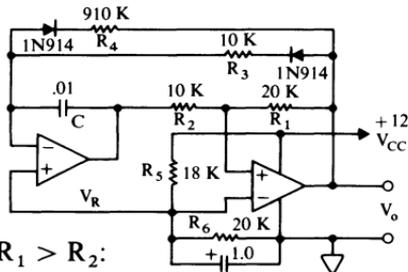Opamp = TL082 etc
(Transpose R_5 and R_6
when using LM358)



When V_R is mid-sat and $R_1 > R_2$:

$$f_0 \approx R_1 / [2R_2C(R_3 + R_4)]$$


$$t_{VOH} \approx (2R_2CR_3) / R_1$$

$$t_{VOL} \approx (2R_2CR_4) / R_1$$

$$V_{op-p} = (V_{SAT})_H - (V_{SAT})_L \approx V_{CC} - 2$$

when R_3, R_4 and $R_L > 30 \text{ K}$

OSCILLATOR SAWTOOTH

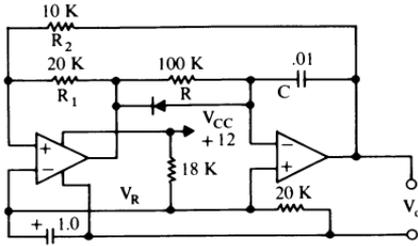


When $R_1 > R_2$ and $V_R = [(V_{SAT})_H + (V_{SAT})_L]/2$:

$$f_0 \approx (R_1/2R_2)/(RC)$$

$$V_{op-p} = (R_2/R_1)[(V_{SAT})_H - (V_{SAT})_L] \approx (R_2/R_1)(V_{CC} - 2)$$

VARIABLE RISE TIME SAWTOOTH OSCILLATOR

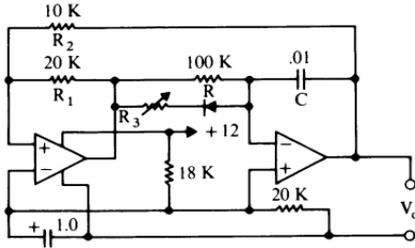


When $R_1 > R_2$ and $V_R = [(V_{SAT})_H + (V_{SAT})_L]/2$:

$$f_0 \approx R_1/[2R_2C(R + R_3)]$$

$$t_r \approx (R_2R_3C)/R_1$$

$$V_{op-p} = (R_2/R_1)[(V_{SAT})_H - (V_{SAT})_L] \approx (R_2/R_1)(V_{CC} - 2)$$


OSCILLATOR SQUAREWAVE

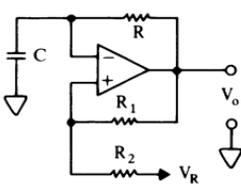

$$f_0 \approx 1000 \text{ Hz}$$

$$\text{Opamp} = 1/2 \text{ TL082}$$

$$V_{\text{op-p}} \approx 10$$

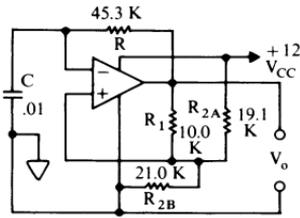

When V_R is centered between high and low saturation voltages, V_o is symmetrical (DF = 50%) and:

$$f_0 = \left(-2RC \left[\ln \left(1 - \left[\frac{R_1}{2R_2} + 1 \right]^{-1} \right) \right] \right)^{-1}$$

$$f_0 \approx (2.2RC)^{-1} \quad \text{when } R_1 = R_2$$


$$V_{\text{op-p}} = (V_{\text{SAT}})_H - (V_{\text{SAT}})_L, \quad \approx V_{\text{CC}} - 2 \quad \text{when } R_L > 10 \text{ K}$$

Tuning Range

30 to 1100 Hz min.

$$V_{\text{op-p}} \approx 10$$

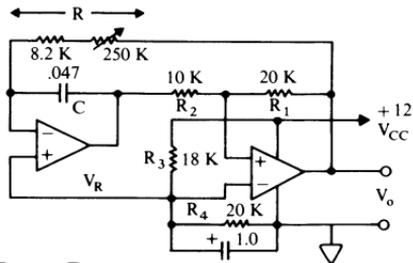Opamp = TL082 etc
(Transpose R_3 and R_4
when using LM358)



When V_R is mid-sat and $R_1 > R_2$:

$$f_0 = (R_1/4R_2)/(RC)$$

$$V_{\text{op-p}} \approx V_{\text{CC}} - 2 \quad \text{when } R_L > 10 \text{ K}$$


V_o is symmetrical when V_R is mid-sat

See Also—Oscillator, Sinewave, State Variable

OSCILLATOR TRIANGULAR WAVE

Tuning Range =
15 to 500 Hz min.

$V_{op-p} \approx 5$

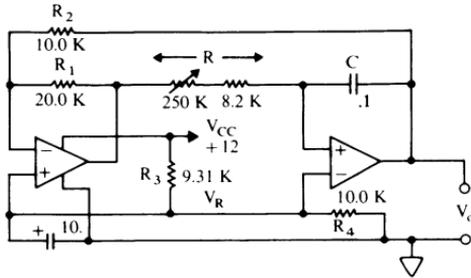

Opamp = TL82 etc
(Transpose R_3 and R_4 when
using "single supply" opamps)

When $R_1 > R_2$ and $V_R = [(V_{SAT})_H + (V_{SAT})_L]/2$:


$$f_0 = (R_1/4R_2)/(RC)$$

$$V_{op-p} = (R_2/R_1)[(V_{SAT})_H - (V_{SAT})_L], \approx (R_2/R_1)(V_{CC} - 2)$$

V_o is symmetrical when $V_R = [(V_{SAT})_H + (V_{SAT})_L]/2$

$$\approx V_{CC}/2 + .2 \approx V_{CC}/2 - .2$$

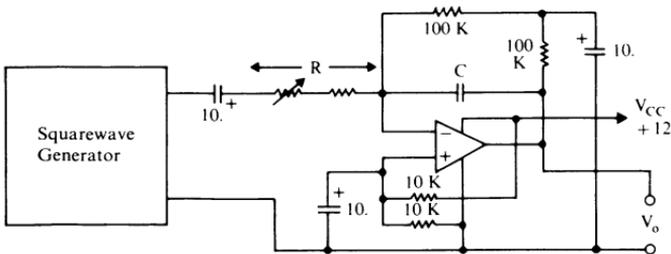
when "single supply" opamps are used. e.g. LM358



$$V_{op-p} = (V_{in})_{p-p}/(2fRC)$$

RECTIFIER PRECISION


POSITIVE V_o HALF WAVE

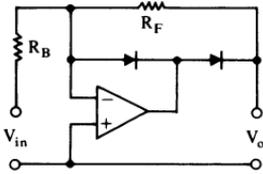

$$(V_o)_{pk} = (V_{in})_{p-p} R_F / 2R_B$$


$$(V_o)_{av} = (V_{in})_{+av} R_F / R_B$$

POSITIVE V_o FULL WAVE

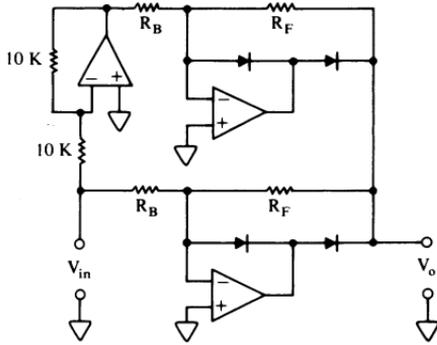

$$(V_o)_{pk} = (V_{in})_{p-p} R_F / 2R_B$$

FULL WAVE WITH INTEGRATOR

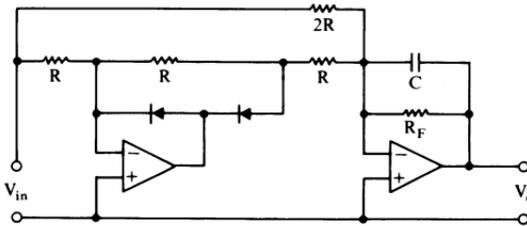

$$(V_o)_{dc} = (V_{in})_{av} R_F / 4R$$

$$t_r = RC$$

$$t_f = R_F C$$

APPENDIX A

RATIOS AVAILABLE FROM 5% COMPONENT VALUES

5% Component Values

**10	**33
11	36
*12	*39
13	43
**15	**47
16	51
*18	*56
20	62
**22	**68
24	75
*27	*82
30	91

** are also 10% and 20% values

* are also 10% values

Above values are available over the range of .1 ohm to 10 megohms in resistors.

5% capacitor values are not as available and demand a much greater premium than resistors and are not recommended. Resistor values may be changed to accept 20% value (not 20% tolerance) capacitors in almost all RC circuits. 10% tolerance capacitors and 5% tolerance resistors (7.5% overall) are recommended for most applications.

RATIOS 5% Component Value Ratios

Ratio	Values	Ratio	Values	Ratio	Values
9.38	150/16	8.24	750/91	6.96	390/56
9.23	120/13	8.23	510/62	6.94	430/62
9.23	360/39	8.20	82/10	6.92	270/39
9.22	470/51	8.18	180/22	6.91	470/68
9.17	110/12	8.18	270/33	6.88	110/16
9.17	220/24	8.15	220/27	6.83	82/12
9.17	330/36	8.13	130/16	6.83	560/82
9.15	430/47	8.00	120/15	6.82	75/11
9.15	750/82	8.00	160/20	6.82	150/22
9.12	620/68	8.00	240/30	6.81	620/91
9.11	510/56	7.69	100/13	6.80	68/10
9.10	91/10	7.69	300/39	6.80	510/75
9.09	100/11	7.68	430/56	6.67	100/15
9.09	200/22	7.67	330/43	6.67	120/18
9.09	300/33	7.66	360/47	6.67	160/24
9.07	390/43	7.65	390/51	6.67	180/27
9.07	680/75	7.58	91/12	6.67	200/30
9.03	560/62	7.58	470/62	6.67	220/33
9.01	820/91	7.56	620/82	6.67	240/36
9.00	180/20	7.50	75/10	6.50	130/20
9.00	270/30	7.50	120/16	6.47	330/51
8.89	160/18	7.50	150/20	6.43	360/56
8.89	240/27	7.50	180/24	6.38	300/47
8.67	130/15	7.50	270/36	6.32	430/68
8.46	110/13	7.50	510/68	6.31	82/13
8.46	330/39	7.47	560/75	6.29	390/62
8.43	430/51	7.47	680/91	6.28	270/43
8.39	470/56	7.45	82/11	6.27	470/75
8.37	360/43	7.41	200/27	6.25	75/12
8.33	100/12	7.33	110/15	6.25	100/16
8.33	150/18	7.33	220/30	6.25	150/24
8.33	200/24	7.27	160/22	6.22	510/82
8.33	300/36	7.27	240/33	6.20	62/10
8.30	390/47	7.22	130/18	6.18	68/11
8.29	680/82	7.06	360/51	6.15	240/39
8.27	91/11	7.02	330/47	6.15	560/91
8.27	620/75	7.00	91/13	6.11	110/18
8.24	560/68	6.98	300/43	6.11	220/36

RATIOS 5% Component Value Ratios

Ratio	Values	Ratio	Values	Ratio	Values
6.07	91/15	5.16	470/91	4.41	300/68
6.06	200/33	5.13	200/39	4.40	330/75
6.00	120/20	5.13	82/16	4.39	360/82
6.00	180/30	5.12	220/43	4.35	270/62
5.93	160/27	5.11	240/47	4.33	130/30
5.91	130/22	5.10	51/10	4.31	56/13
5.89	330/56	5.09	56/11	4.31	220/51
5.88	300/51	5.06	91/18	4.30	43/10
5.81	360/62	5.00	75/15	4.29	240/56
5.77	75/13	5.00	100/20	4.29	390/91
5.74	270/47	5.00	110/22	4.27	47/11
5.74	390/68	5.00	120/24	4.26	200/47
5.73	430/75	5.00	150/30	4.25	51/12
5.73	470/82	5.00	180/36	4.25	68/16
5.69	91/16	4.85	160/33	4.19	180/43
5.67	68/12	4.85	330/68	4.17	75/18
5.64	62/11	4.84	300/62	4.17	100/24
5.64	220/39	4.82	270/56	4.17	150/36
5.60	56/10	4.81	130/27	4.14	91/22
5.60	510/91	4.80	360/75	4.13	62/15
5.58	240/43	4.77	62/13	4.10	82/20
5.56	100/18	4.76	390/82	4.10	160/39
5.56	150/27	4.71	240/51	4.07	110/27
5.56	200/36	4.70	47/10	4.02	330/82
5.50	110/20	4.69	75/16	4.00	120/30
5.47	82/15	4.68	220/47	4.00	300/75
5.45	120/22	4.67	56/12	3.97	270/68
5.45	180/33	4.65	200/43	3.96	360/91
5.42	130/24	4.64	51/11	3.94	130/33
5.36	300/56	4.62	180/39	3.93	220/56
5.33	160/30	4.58	110/24	3.92	47/12
5.32	330/62	4.56	82/18	3.92	51/13
5.29	270/51	4.55	91/20	3.92	200/51
5.29	360/68	4.55	100/22	3.91	43/11
5.24	430/82	4.55	150/33	3.90	39/10
5.23	68/13	4.53	68/15	3.88	62/16
5.20	390/75	4.44	120/27	3.87	240/62
5.17	62/12	4.44	160/36	3.85	150/39

RATIOS 5% Component Value Ratios

Ratio	Values	Ratio	Values	Ratio	Values
3.83	180/47	3.29	270/82	2.80	56/20
3.79	91/24	3.27	36/11	2.79	120/43
3.78	68/18	3.25	39/12	2.78	75/27
3.75	75/20	3.24	220/68	2.78	100/36
3.73	56/15	3.23	200/62	2.77	36/13
3.73	82/22	3.21	180/56	2.77	130/47
3.72	160/43	3.20	240/75	2.76	91/33
3.70	100/27	3.19	150/47	2.75	33/12
3.67	110/30	3.18	51/16	2.73	30/11
3.66	300/82	3.14	160/51	2.73	82/30
3.64	120/33	3.13	47/15	2.70	27/10
3.63	330/91	3.13	75/24	2.69	43/16
3.62	47/13	3.11	56/18	2.68	150/56
3.61	130/36	3.10	62/20	2.68	220/82
3.60	36/10	3.09	68/22	2.67	200/75
3.60	270/75	3.08	120/39	2.65	180/68
3.58	43/12	3.06	110/36	2.64	240/91
3.57	200/56	3.04	82/27	2.61	47/18
3.55	39/11	3.03	91/30	2.60	39/15
3.55	220/62	3.03	100/33	2.58	62/24
3.53	180/51	3.02	130/43	2.58	160/62
3.53	240/68	3.00	30/10	2.56	100/39
3.50	56/16	3.00	33/11	2.56	110/43
3.49	150/43	3.00	36/12	2.55	51/20
3.44	62/18	3.00	39/13	2.55	56/22
3.42	82/24	2.97	270/91	2.55	120/47
3.41	75/22	2.94	47/16	2.55	130/51
3.40	51/15	2.94	150/51	2.54	33/13
3.40	68/20	2.94	200/68	2.53	91/36
3.40	160/47	2.93	220/75	2.52	68/27
3.37	91/27	2.93	240/82	2.50	30/12
3.33	100/30	2.90	180/62	2.50	75/30
3.33	110/33	2.87	43/15	2.48	82/33
3.33	120/36	2.86	160/56	2.45	27/11
3.33	130/39	2.83	51/18	2.44	39/16
3.31	43/13	2.83	68/24	2.44	200/82
3.30	33/10	2.82	62/22	2.42	150/62
3.30	300/91	2.82	110/39	2.42	220/91

RATIOS 5% Component Value Ratios

Ratio	Values	Ratio	Values	Ratio	Values
2.40	24/10	2.08	75/36	1.78	91/51
2.40	36/15	2.07	56/27	1.77	39/22
2.40	180/75	2.07	62/30	1.77	110/62
2.39	43/18	2.06	33/16	1.76	120/68
2.35	47/20	2.06	68/33	1.76	160/91
2.35	120/51	2.00	20/10	1.74	47/27
2.35	160/68	2.00	22/11	1.74	68/39
2.34	110/47	2.00	24/12	1.74	75/43
2.33	56/24	2.00	30/15	1.74	82/47
2.33	91/39	2.00	36/18	1.73	130/75
2.33	100/43	2.00	150/75	1.72	62/36
2.32	51/22	1.98	180/91	1.70	51/30
2.32	130/56	1.96	47/24	1.70	56/33
2.31	30/13	1.96	100/51	1.69	22/13
2.30	62/27	1.96	110/56	1.69	27/16
2.28	82/36	1.95	39/20	1.67	20/12
2.27	68/30	1.95	43/22	1.67	30/18
2.27	75/33	1.95	160/82	1.65	33/20
2.25	27/12	1.94	91/47	1.65	150/91
2.25	36/16	1.94	120/62	1.64	18/11
2.21	150/68	1.92	75/39	1.64	36/22
2.20	22/10	1.91	130/68	1.63	39/24
2.20	33/15	1.91	82/43	1.63	91/56
2.20	180/82	1.89	51/27	1.62	110/68
2.20	200/91	1.89	68/36	1.61	82/51
2.18	24/11	1.88	30/16	1.61	100/62
2.17	39/18	1.88	62/33	1.60	16/10
2.16	110/51	1.87	56/30	1.60	24/15
2.15	43/20	1.85	24/13	1.60	75/47
2.14	47/22	1.83	22/12	1.60	120/75
2.14	120/56	1.83	33/18	1.59	43/27
2.13	51/24	1.83	150/82	1.59	62/39
2.13	100/47	1.82	20/11	1.59	130/82
2.13	160/75	1.80	18/10	1.58	68/43
2.12	91/43	1.80	27/15	1.57	47/30
2.10	82/39	1.80	36/20	1.56	56/36
2.10	130/62	1.79	43/24	1.55	51/33
2.08	27/13	1.79	100/56	1.54	20/13

RATIOS 5% Component Value Ratios

Ratio	Values	Ratio	Values	Ratio	Values
1.50	15/10	1.32	62/47	1.11	62/56
1.50	18/12	1.32	82/62	1.11	91/82
1.50	24/16	1.32	120/91	1.10	11/10
1.50	27/18	1.31	47/36	1.10	22/20
1.50	30/20	1.31	51/39	1.10	33/30
1.50	33/22	1.30	13/10	1.10	43/39
1.50	36/24	1.30	39/30	1.10	56/51
1.47	22/15	1.30	43/33	1.10	68/62
1.47	75/51	1.30	56/43	1.10	75/68
1.47	91/62	1.25	15/12	1.10	100/91
1.47	100/68	1.25	20/16	1.09	12/11
1.47	110/75	1.25	30/24	1.09	24/22
1.46	82/56	1.23	16/13	1.09	36/33
1.46	120/82	1.23	27/22	1.09	47/43
1.45	16/11	1.22	22/18	1.09	51/47
1.45	68/47	1.22	33/27	1.09	82/75
1.44	39/27	1.22	62/51	1.08	13/12
1.44	56/39	1.22	100/82	1.08	39/36
1.44	62/43	1.21	47/39	1.07	16/15
1.43	43/30	1.21	68/56		
1.43	130/91	1.21	75/62	1.00	ALL
1.42	47/33	1.21	82/68		
1.42	51/36	1.21	91/75		
1.38	18/13	1.21	110/91		
1.38	22/16	1.20	12/10		
1.38	33/24	1.20	18/15		
1.36	15/11	1.20	24/20		
1.36	30/22	1.20	36/30		
1.35	27/20	1.19	43/36		
1.34	75/56	1.19	51/43		
1.34	91/68	1.19	56/47		
1.34	110/82	1.18	13/11		
1.33	16/12	1.18	39/33		
1.33	20/15	1.15	15/13		
1.33	24/18	1.13	18/16		
1.33	36/27	1.13	27/24		
1.33	68/51	1.11	20/18		
1.33	100/75	1.11	30/27		

This listing of all possible ratios between 10 and 1 may also be used for all other possible ratios by moving the proper decimal points.

APPENDIX B

STANDARD 1%, 0.5%, 0.25% AND 0.1% VALUES

1% VALUES

10.0	10.2	10.5	10.7	11.0	11.3	11.5	11.8	12.1	12.4	12.7	13.0
13.3	13.7	14.0	14.3	14.7	15.0	15.4	15.8	16.2	16.5	16.9	17.4
17.8	18.2	18.7	19.1	19.6	20.0	20.5	21.0	21.5	22.1	22.6	23.2
23.7	24.3	24.9	25.5	26.1	26.7	27.4	28.0	28.7	29.4	30.1	30.9
31.6	32.4	33.2	34.0	34.8	35.7	36.5	37.4	38.3	39.2	40.2	41.2
42.2	43.2	44.2	45.2	46.4	47.5	48.7	49.9	51.1	52.3	53.6	54.9
56.2	57.6	59.0	60.4	61.9	63.4	64.9	66.5	68.1	69.8	71.5	73.2
75.0	76.8	78.7	80.6	82.5	84.5	86.6	88.7	90.9	93.1	95.3	97.6

0.1%, 0.25% AND 0.5% VALUES

10.0	10.1	10.2	10.4	10.5	10.6	10.7	10.9	11.0	11.1	11.3	11.4
11.5	11.7	11.8	12.0	12.1	12.3	12.4	12.6	12.7	12.9	13.0	13.2
13.3	13.5	13.7	13.8	14.0	14.2	14.3	14.5	14.7	14.9	15.0	15.2
15.4	15.6	15.8	16.0	16.2	16.4	16.5	16.7	16.9	17.2	17.4	17.6
17.8	18.0	18.2	18.4	18.7	18.9	19.1	19.3	19.6	19.8	20.0	20.3
20.5	20.8	21.0	21.3	21.5	21.8	22.1	22.3	22.6	22.9	23.2	23.4
23.7	24.0	24.3	24.6	24.9	25.2	25.5	25.8	26.1	26.4	26.7	27.1
27.4	27.7	28.0	28.4	28.7	29.1	29.4	29.8	30.1	30.5	30.9	31.2
31.6	32.0	32.4	32.8	33.2	33.6	34.0	34.4	34.8	35.2	35.7	36.1
36.5	37.0	37.4	37.9	38.3	38.8	39.2	39.7	40.2	40.7	41.2	41.7
42.2	42.7	43.2	43.7	44.2	44.8	45.3	45.9	46.4	47.0	47.5	48.1
48.7	49.3	49.9	50.5	51.1	51.7	52.3	53.0	53.6	54.2	54.9	55.6
56.2	56.9	57.6	58.3	59.0	59.7	60.4	61.2	61.9	62.6	63.4	64.2
64.9	65.7	66.5	67.3	68.1	69.0	69.8	70.6	71.5	72.3	73.2	74.1
75.0	75.9	76.8	77.7	78.7	79.6	80.6	81.6	82.5	83.5	84.5	85.6
86.6	87.6	88.7	89.8	90.9	92.0	93.1	94.2	95.3	96.5	97.6	98.8

APPENDIX C

ELECTRONICS TERMS AND THEIR SYMBOLS

This is an alphabetical listing of passive, bipolar-transistor and operational-amplifier (opamp) linear-circuit electronics terms with their corresponding symbols. Included also, are selected electronic, magnetic, acoustic, electrical, mechanical, mathematical and physical terms with their corresponding symbol, abbreviation, sign or acronym.

An attempt has been made to include present common usage (USA), traditional and recognized standard symbols, however, the preferred symbol (listed last) is often the author's projection of present trend, personal preference or arbitrary selection and does not necessarily represent an accepted industry standard.

This listing is intended as a reference source of electronics symbols, but may also be used to locate formulas having unfamiliar resultant symbols. It should be noted, however, that several different symbols may be shown for a given term and that the last-listed symbol is not always the one used in the formula and definition sections, since the last-listed symbol may be the author's projection of present trend.

Textbooks and scientific journals conventionally use italic (slanted) type for quantity symbols, however, this handbook follows the example of almost all technical manuals where roman (upright) type is used for both quantity and unit symbols. Unit symbols are clearly indicated as such in this appendix.

Common electronics abbreviations should be written without periods and generally in lower case letters as listed, however, certain abbreviations are capitalized and certain others are capitalized when used as a noun.

An asterisk is used to indicate schematic letter symbols.

No attempt has been made to include terms or symbols associated with computing systems, control systems, digital systems, digital devices, non-linear circuits, non-linear devices, vacuum tubes or field effect transistors.

a		admittance	Y
about equal to	\approx	input	Y_{in}, Y_i
absolute temperature		magnitude	$ Y , Y$
(quantity)	T, T_K	output	Y_o
(unit)	K	vector	\vec{Y}, Y
absolute value (of x)	$ x $	admittance, transistor	
See also—magnitude		(hybrid parameters)	
absolute zero temperature		output	
	T_o	common base	h_{ob}
acceleration, angular	α	common collector	h_{oc}
acceleration, linear	a	common emitter	h_{oe}
acoustic		admittance, transistor,	
angular frequency	ω	(y parameters)	
angular velocity	ω	common base	
attenuation coefficient	α	forward transfer	Y_{fb}
damping coefficient	δ	input	Y_{ib}
frequency	f	output	Y_{ob}
impedance	Z_a	reverse transfer	Y_{re}
loudness level	L_N	common emitter	
mechanical impedance	Z_m	forward transfer	Y_{fe}
period	T	input	Y_{ie}
resonant frequency	f_r	output	Y_{oe}
reverberation time	T, T_{60}	reverse transfer	Y_{re}
sound power	P	alpha (Greek letter)	α
sound power level		alpha, transistor	
	PWL, L_P	small signal	α, h_{fb}
sound pressure	P	static (dc)	$\bar{\alpha}, h_{FB}$
sound pressure level		alpha cutoff frequency	$f_{\alpha b}$
	SPL, L_p	alternating current	AC, ac
sound velocity	c, v	ambient temperature	t_A, T_A
specific impedance	Z_s	American wire gage	AWG
wavelength	λ	ampere (unit)	A
		ampere-hour (unit)	$A \cdot h, Ah$

ampere-squared-seconds (unit)	$I^2 t$	angle, solid	Ω
ampere-turn (unit of magnetomotive force)	$A \cdot t, A, At$	angular frequency	ω
ampere per meter (unit of magnetic field strength)	$At/m, A/m$	angular velocity	ω
amplification (quantity)	A	antilogarithm (of x)	
amplification (unit)	dg, (numeric), dB	base 10	$lg^{-1}, 10^x, log^{-1}$
See also—gain		base e	e^x, e^x, ln^{-1}
amplification, dc or large signal		common	$lg^{-1}, 10^x, log^{-1}$
current	A_I	natural	e^x, e^x, ln^{-1}
power (gain)	G_p	antiresonant frequency	f_o, f_r
voltage	A_v	apparent power	
small signal		(quantity)	S, P_s, VA
current	A_i	(unit)	VA
power (gain)	G_p	approximately equal to	\approx
voltage	A_v	arc cosine	$arccos, cos^{-1}$
amplification factor (vacuum tube)	μ	hyperbolic	$arcosh, cosh^{-1}$
amplitude modulation	AM	arc cosecant	$arcsec, sec^{-1}$
angle, loss	δ	hyperbolic	$arsech, sech^{-1}$
angle, phase	ϕ, θ	arc cotangent	$arccot, cot^{-1}$
admittance	θ_Y	hyperbolic	$arcoth, coth^{-1}$
current	θ_I	arc secant	$arcsec, sec^{-1}$
impedance	θ_Z	hyperbolic	$arsech, sech^{-1}$
voltage	$\phi_E, \phi_V, \theta_E, \theta_V$	arc sine	$arcsin, sin^{-1}$
angle, phase margin	ϕ_m, θ_m	hyperbolic	$arsinh, sinh^{-1}$
angle, plane	ϕ, θ	arc tangent	$arctan, tan^{-1}$
		hyperbolic	$artanh, tanh^{-1}$
		area	A
		area, cross-sectional	S, A
		atmosphere	atm
		attenuation coefficient	α
		atto (unit prefix for 10^{-18})	a
		audio frequency	a-f
		automatic frequency control	AFC

automatic gain control	AGC	*base capacitor (transistor)	C_B
average current	I_{av}	base current (transistor) small signal	I_b
noise current	$i_N, \bar{i}_n, i_n, I_N, \bar{I}_n, I_n$	static (dc)	I_B
noise voltage	$E_N, \bar{E}_n, e_N, \bar{e}_n, \bar{V}_n, V_n$	base resistance (transistor) external	R_B
power (long term average)	\bar{P}, P_{av}	internal small signal	r_b
power (short term or one cycle average)	P	static (dc)	r_B
voltage	E_{av}, V_{av}	base spreading resistance (transistor)	$r_{bb'}, r_{bb}$
b		base supply voltage (transistor)	V_{BB}
bandwidth 3dB down	$(f_2 - f_1), B, B_3, BW, BW_{-3dB}$	base-to-emitter voltage (transistor) active	V_{BE} $V_{BE(ON)}$
half power	$(f_2 - f_1), B, B_3, BW, BW_{-3dB}$	saturated	$V_{BE(SAT)}$
noise	$B, BW, \bar{B}, B_n, \bar{B}_n, BW_n$	base voltage (transistor)	V_B
unity gain	$B_1, BW_{(A_v=1)}$	bel See—decibel	
*base (transistor)	B	beta (Greek letter)	β
base 10 logarithm	lg, \log_{10}, \log	beta, transistor small signal	β, h_{fe}
base of natural logarithms	ϵ, e, e	static (dc)	$\bar{\beta}, h_{FE}$
base ϵ logarithm	\log_{ϵ}, \ln	bias current, input (op amp)	I_{IB}
		Boltzmann constant	k, k_B
		*bootstrap capacitor	C_B
		breakdown, second (transistor) current	$I_{S/b}$
		energy	$E_{S/b}$

centimeter (unit)	cm	collector resistance	
cubic (unit)	cm ³	(transistor)	
square (unit)	cm ²	external	R _C
centimeter-gram-second		internal, T equiv.	r _c
(unit system)	cgs, CGS	collector supply voltage	
characteristic impedance	Z _O	(transistor, op amp)	V _{CC}
charge, electric	Q	collector voltage	
charge, elementary		(transistor)	
(charge of electron)	e, q	small signal	e _c , E _c , V _c
closed-loop voltage		static (dc)	V _C
amplification (op amp)		common base (transistor)	
	A _{VCL} , A _V	forward current	
coefficient,		transfer ratio	h _{fb}
attenuation	α	input impedance	h _{ib}
coupling	k	output admittance	h _{ob}
damping	δ	reverse voltage	
temperature	α, TC	transfer ratio	h _{rb}
*collector (transistor)	C	common collector (transistor)	
collector current (transistor)		forward current	
small signal	I _c	transfer ratio	h _{fc}
static (dc)	I _C	input impedance	h _{ic}
collector cutoff current		output admittance	h _{oc}
(transistor)		reverse voltage	
base open	I _{CEO}	transfer ratio	h _{rc}
base-to-emitter		common emitter (transistor)	
circuit	I _{CEX}	forward current ratio	
resistance	I _{CER}	small signal	h _{fe}
short	I _{CES}	static (dc)	h _{FE}
voltage	I _{CEV}	input impedance	h _{ie}
collector dissipation		output impedance	h _{oe}
(transistor)	P _C	reverse voltage	
collector efficiency		transfer ratio	h _{re}
(transistor)	η, η _C		

common emitter (transistor)		constant,	
voltage gain	G_{ve}	acceleration of free fall	g
broadband	G_{VE}	Boltzmann	k, k_B
common logarithm		dielectric	k, k_d
	\lg, \log_{10}, \log	gravitational	G
common mode (op amp)		Planck	h
input voltage	V_{ICM}	time	τ, T
range	V_{ICR}	See also—coefficient and	
rejection ratio	CMRR	factor	
voltage	V_{CM}	conversion gain	G_c
complex quantity		conversion	
(phasor quantity)		transconductance	
admittance	\vec{Y}, Y		g_c, g_{mc}
current	\vec{I}, I	cosecant	cosec
impedance	\vec{Z}, Z	hyperbolic	cosech
voltage	\vec{E}, \vec{V}, E, V	cosine	cos
conductance	G	hyperbolic	cosh
conductance, mutual	g_m	cotangent	cot
See also—transconductance		hyperbolic	coth
large signal	G_m	coulomb (unit)	Q
conductance, transistor		*coupling capacitor	C_C
(real part of y		coupling coefficient	k
parameters)		critical	k_c
common base		critical:	
forward transfer	g_{fb}	angular frequency	ω_c
input	g_{ib}	angular velocity	ω_c
output	g_{ob}	coupling coefficient	k_c
reverse transfer	g_{rb}	frequency	f_c
common emitter		wavelength	λ_c
forward transfer	g_{fe}	crossover	
input	g_{ie}	angular frequency	ω_c
output	g_{oe}	angular velocity	ω_c
reverse transfer	g_{re}		

crossover			current	
frequency	f_c		second breakdown	$I_{S/b}$
wavelength	λ_c		vector (phasor)	\vec{I}, I
cubic units			current, opamp	
centimeter	cm^3		bias	I_B
foot	cu ft, ft^3		device	
inch	cu in, in^3		negative supply	
meter	m^3		$I-, I_{D-}, I_{EE}$	
yard	cu yd, yd^3		non-inverting input	
current	I		grounded	I_{DG}
alternating	I_{AC}, I_{ac}, I		open	I_{DO}
average	I_{av}		positive supply	
capacitive	$+jI_X, I_C$		$I+, I_{D+}, I_{CC}$	
direct	I_{DC}, I_{dc}, I		input	
effective	I_{eff}, I_{rms}, I		bias	I_{IB}
generator	I_g		offset	I_{IO}
inductive	$-jI_X, I_L$		signal	I_{IN}, I_{in}
input	I_{in}, I_i		noise, equivalent input	
instantaneous	i		1/f	I_{nf}
lagging	$-jI_X$		device	I_n
leading	$+jI_X$		shot	I_{ns}
magnitude	I		noise, thermal noise of	
noise	i_N, I_N, i_n, I_n		input resistance	I_{nR}
output			output	
small signal	I_o		large-signal	I_O
large signal	I_O		maximum	I_{OM}
peak	I_{pk}, i_p, I_p		negative swing	I_{O-}
peak-to-peak	I_{p-p}		peak-to-peak	I_{OPP}
phasor	\vec{I}, I		positive swing	I_{O+}
polar form	I_{POLAR}		shorted	I_{OS}
rectangular form	I_{RECT}		small-signal	I_o
root-mean-square	I_{rms}, I			

current, transistor		decibel (ratio unit for power, voltage and current)	dB
base, small-signal	I_b	decibel level See—level	
base, static (dc)	I_B	decilog	dg
collector, small-signal	I_c	decimal point	.
collector, static (dc)	I_C	degree	°
emitter, small-signal	I_e	deka (unit prefix for 10)	da
emitter, static (dc)	I_E	(rare in USA)	
current, transistor		delay time	t_d
collector cutoff		delta (Greek letter)	
base-emitter		capital	Δ
circuit	I_{CEX}	script	δ
resistance	I_{CER}	depth	d
shorted	I_{CES}	device under test	DUT
voltage	I_{CEV}	diameter	d
current, transistor		inside	d_i, d_{in}, ID
emitter cutoff		outside	d_o, d_{out}, OD
collector open	I_{EBO}	dielectric constant	k, k_d
customary temperature	t	dissipation	
cutoff		collector (transistor)	P_C
angular frequency	ω_c	device	P_D
angular velocity	ω_c	power	P_D
frequency	f_c	total	P_t, P_T
wavelength	λ_c	dissipation factor	D
cycle, duty		distance	d
See—duty factor		distortion	
cycles per second cps, c/s, Hz		intermodulation	IM, IMD
See also—hertz		total harmonic	THD
d		direct current	DC, dc
damping coefficient	δ	double pole (switch)	
damping factor	α, δ, d	double throw	DPDT
deci (unit prefix for 10^{-1})	d	single throw	DPST
		drain See—FET literature	

duty cycle		emitter (transistor)	
See—duty factor		*capacitor	C_E
duty factor	F_D, D, DF, df	resistance, external	R_E
dynamic resistance	r	resistance, internal	
See—vacuum tube literature		small signal	r_e
See also—internal small-		static (dc)	r_E
signal resistance (transistor		*emitter resistor	R_E
and opamp)		energy	e, E, W
dyne (CGS unit)	dyn	second breakdown	$E_{S/b}$
e		epsilon (Greek letter)	ϵ, ϵ
effective		equal	=
bandwidth		approximately	\approx
B, BW, BW_{NOISE} ,		identically	\equiv
$BW_{eff}, \bar{B}, \bar{BW}, B_n, BW_n$		not	\neq, \neq
current (ac)		very nearly	\cong, \cong
I_{eff}, I_{rms}, I		equivalent (of x)	
power	P	$x_{equiv}, x_T, x_t, x =$	
radiated power	ERP	Note: The resultant of	
voltage (ac)		formulas is the equivalent	
$E_{eff}, E_{rms}, V_{rms}, E, V$		quantity.	
See also—equivalent		equivalent series	
and total		resistance	ESR
efficiency	η	erg (CGS unit)	erg
electric charge	Q	eta (Greek letter)	η
electromotive force		exa (unit prefix for 10^{18})	E
emf, E, V		excess noise voltage	
See also—voltage		$E_{EX}, E_{N(EX)}, V_{NR(EX)}$	
elementary charge		f	
(charge of electron)	e, q	factor	
*emitter (transistor)	E	damping	α, δ, d
breakdown voltage		dissipation	D
$BV_{EBO}, V_{(BR)EBO}$		energy See—quality	
		flare (flaring)	m

factor		flux density, magnetic	
magnification		(quantity)	B
See—quality		(unit)	G, T
merit See—quality		flux, total magnetic	
noise (transistor)		(quantity)	Φ, ϕ
(noise figure) F, NF, F_n		(unit)	Mx, Wb
power $\cos \theta, PF, pf, F_P$		foot (unit)	', ft
Q	Q	cubic (unit)	cu ft, ft ³
quality	Q	square (unit)	sq ft, ft ²
storage See—quality		force	
Fahrenheit temperature		electromotive emf, E, V	
(quantity) t, t ^{°F} , T _F		magnetizing See—	
(unit) °F		magnetic field	
fall time	t _f	strength	
farad (unit)	F	magnetomotive	
feedback		(quantity)	F, \mathcal{F}, F_m
* capacitor C _{FB} , C _F		(unit)	A · t, A, At
* resistor R _{FB} , R _F		mechanical	
transfer ratio β		(quantity)	F
femto (unit prefix for 10 ⁻¹⁵)	f	(unit)	kgf, lbf, N
field effect transistor	FET	forward current	
field strength, electric		(semiconductor)	I _F
(quantity) E		forward current	
(unit) V/m		transfer ratio	
field strength, magnetic		common base	h _{fb}
(quantity) H, H		common collector	h _{fc}
(unit) Oe, At/m, A/m		common emitter	
figure, noise (transistor)		small-signal	h _{fe}
(noise factor) F, NF, F_n		static (dc)	h _{FE}
flare (acoustic horn)		forward transfer	
cutoff frequency f _{FC}		admittance	
factor F _F , m		common base	Y _{fb}
		common emitter	Y _{fe}

frequency	f	frequency modulation	FM
angular	ω	function	F, f
carrier	f_c		
critical	f_c	g	
critical angular	ω_c	gain (amplification)	
crossover	f_c	current	
crossover angular	ω_c	large-signal	A_I
cutoff	f_c	small-signal	A_i
cutoff angular	ω_c	margin	ϕ_m, θ_m
deviation	f_d	voltage	
Doppler shift	f_D	large signal	A_V
extremely high	ehf	small signal	$G_V A_V$
flare cutoff	f_o, f_c, f_{FC}	transistor	G_{VE}
high	hf	broadband	G_{VE}
input	f_i, f_{in}	gain (power)	
intermediate	i-f	large signal	G_P
low	lf	small-signal	G_P
lowest satisfactory		transistor	
horn loading	f'	common base,	
maximum usable	MUF	large signal	G_{PB}
midband	f_o	common base	
modulation	f_m	small signal	G_{pb}
oscillation	f_{osc}, f_o	common emitter	
pulse repetition	f_p	large-signal	G_{PE}
reference	f_{ref}, f_o	common emitter	
resonant	f_o, f_r	small-signal	G_{pe}
resonant, angular	ω_o, ω_r	gain-bandwidth	
superhigh	shf	product	GBW
transition, transistor	f_T, f_t	opamp (unity gain	
ultra high	uhf	frequency)	
very high	vhf	$B_1, BW_{(A_V = 1)}$	
very low	vlf	transistor (transition	
		frequency)	f_t, f_T

gamma (Greek letter)	γ	high frequency	
gate See—FET literature		extremely (30–300 GHz)	
gauss (CGS unit)	G		ehf
generator current	i_g, I_g	super (3–30 GHz)	shf
generator voltage	e_g, E_g, V_g	ultra (300 MHz–3 GHz)	
giga (unit prefix for 10^9)	G		uhf
(pronounced jiga)		very (30–300 MHz)	vhf
gilbert (CGS unit)	Gb	horn, acoustic	
gram (CGS unit)	g	flare cutoff	
gravitational		frequency	f_o, f_c, f_{FC}
acceleration	g	flaring factor	F_F, m
acceleration,		lowest frequency for	
standard	g_n	satisfactory loading	f'
constant	G	horsepower (unit)	hp
greater than (x)	$>x$	hour (unit)	h
not	∇x	hour, ampere (unit)	
or equal to	$\geq x$		$A \cdot h, Ah$
grid See—vacuum tube literature		hybrid parameter (transistor)	
		forward current ratio	
		small signal	
	h	common base	h_{fb}
harmonic distortion,		common collector	h_{fc}
total	THD	common emitter	h_{fe}
heater See—vacuum tube literature		static (dc)	
		common emitter	h_{FE}
heatsink temperature	t_s, T_s	hybrid parameter	
hecto (unit prefix for 10^2)		(transistor)	
(rare USA)	h	input impedance	
height	h	common base	h_{ib}
henry (unit)	H	common collector	h_{ic}
hertz (unit)	Hz	common emitter	h_{ie}
high frequency (3–30 MHz)	hf		

inch (unit)	in	input capacitance	C_{in}, C_i
cubic (unit)	cu in, in^3	transistor	
square (unit)	sq in, in^2	common base	C_{ib}, C_{ibo}
increment	Δ	common emitter	
indefinite number	n		C_{ie}, C_{ieo}
index, noise	NI	input equivalent noise	
inductance	L	(opamp and transistor)	
mutual	M	current	i_n, I_n
parallel	L_p, L_p	total	e_{ni}, V_{ni}
primary	L_p	voltage	e_n, V_n
resonant	L_r	input frequency	f_i, f_{in}
secondary	L_s	input impedance	
series	L_s, L_s	opamp	z_{in}, z_i
induction, magnetic		common mode	z_{ic}
See—magnetic field		input impedance, transistor	
strength		common base	h_{ib}
inductive		common collector	h_{ic}
current	$-jI_X, +I_X, I_L$	common emitter	h_{ie}
reactance	$+X, X_L$	high frequency	z_{ie}
susceptance	$-jB, +B, B_L$	low frequency	r_{ie}
voltage		input offset current	
	$+E_X, +V_X, E_L, V_L$	(opamp)	I_{IO}
*inductor	L	input offset voltage	
*inductor, mutual	L_M	(opamp)	V_{IO}
infinity	∞	input power	P_{in}, P_i
infra-red	IR	input resistance	R_{in}, R_i
input admittance	Y_{in}, Y_i	opamp	R_i, r_i
transistor		differential	r_{id}
common base	y_{ib}	transistor	
common emitter	y_{ie}	common base	
			$R_{ib}, Re(h_{ib}), r_{ib}$
		common emitter	
			$R_{ie}, Re(h_{ie}), r_{ie}$

instantaneous current	i	kelvin temperature (thermodynamic temperature)	T, T _K
peak current	i _{pk} , i _p	kilo (unit prefix for 10 ³)	K, k
peak power	P _{pk} , P _{pk}	knot(unit)	kn
peak voltage	e _{pk} , e _p , v _{pk} , v _p		
power	P		l
voltage	e, v	lambda (Greek letter)	
*integrated circuit	IC	capital script	Λ λ
intermediate frequency	i-f	lead temperature	t _L , T _L
intermodulation	IM	leakage coefficient	σ
intermodulation distortion	IM, IMD	leakage current	I _L
internal resistance, opamp		transistor See—cutoff current	
input	R _i , r _i	leakage inductance	L' _s , l _s
output	R _o , r _o	primary	L' _p , l _p
internal resistance, transistor (T equivalent)		secondary	L' _s , l _s
base	r _b	length	ℓ
collector	r _c	less than (x)	<x
emitter	r _e	or equal to	≤x
intrinsic standoff ratio (unijunction transistor)	η	not	<x
inverse See—arc, negative reciprocal or reverse		level (in decibels)	
		current	
		ref. 1 pA	L _{I/pA}
		power	
		ref. 1 mW	dBm, L _{P/mW}
		ref. 1 fW	L _{P/fW}
joint army-navy specification	JAN	sound power	
joule (unit)	W · s, Ws, J	ref. 1 pW	PWL, L _{P/pW}
		sound pressure	
		ref. 20 μPa/m ²	
kelvin (unit)	K		SPL, L _{p/20 μPa}

level (in decibels)		magnetic flux	
voltage		(quantity)	Φ, ϕ
ref. 1V	dBV, $L_{V/V}$	(unit)	Mx, Wb
ref. $1V_{p-p}$	dBv, $L_{V/V_{p-p}}$	magnetic flux density	
light amplification by		(quantity)	B
stimulated emission of		(unit)	G, T
radiation	LASER, laser	(magnetic) permeability	
light dependent resistor	LDR	(quantity)	μ
light emitting diode	LED	(unit)	G/Oe, (numeric)
line (of magnetic flux) (unit)		(magnetic) reluctance	
See—Maxwell		(quantity)	R, \mathcal{R}
liter (unit)	l, ℓ , L	(unit)	A/Wb, At/Wb
load admittance	Y_L	magnetizing force	
load impedance	Z_L	See—magnetic	
load resistance	R_L	field strength	
*load resistor	R_L	magnetomotive force	
loaded Q	Q_L	(quantity)	\mathcal{F}, F, F_m
logarithm		(unit)	$A \cdot t, A, At$
base 10	lg, \log_{10}, \log	magnitude (of x)	$ x $
base e	\log_e, \ln	magnitude of	
common	lg, \log_{10}, \log	admittance	$ Y , Y$
natural	\log_e, \ln	capacitive reactance	X_C
loss angle	δ	capacitive susceptance	B_C
lot tolerance percent		current	$ I , I$
defective	LTPD	impedance	$ Z , Z$
low frequency	lf	inductive reactance	X_L
very	vlf	inductive susceptance	B_L
		input offset current	
m		(opamp)	$ I_{IO} , I_{IO}$
magnetic field strength		input offset voltage	
(quantity)	H, H	(opamp)	$ V_{IO} , V_{IO}$
(unit)		reactance	X
Gb/cm, Oe, At/m, A/m		susceptance	B

magnitude of voltage	$ E , V , E, V$	medium frequency (300 kHz–3 MHz)	mf
magnification factor (Q factor or quality factor)	Q	mega (unit prefix for 10^6)	M
margin, gain	A_m	merit factor	Q
margin, phase	ϕ_m, θ_m	See also—quality factor	
mark See—sign		meter (unit)	m
mass	m	cubic (unit)	m^3
maximum (device)		square (unit)	m^2
available gain	MAG	mho (unit)	mho, S, \mathcal{U}, Ω^{-1}
output current	I_{OM}	See also—seimens	
peak-to-peak	I_{OPP}	micro (unit prefix for 10^{-6})	μ
output swing bandwidth	B_{OM}	mile (unit)	mi
output voltage	V_{OM}	square (unit)	mi^2
usable frequency	MUF	mile per hour (unit)	mph, mi/h
maxwell (CGS unit)	Mx	milli (unit prefix for 10^{-3})	m
mean-time-between-failures	MTBF	milli-inch (unit)	mil
mean-time-to-failure	MTTF	mode, common rejection	CMR
mean-time-to-first-failure	MTTFF	rejection ratio	CMRR
mechanical		mouth area (acoustic horn)	S_M, A_M
efficiency	η	mu (Greek letter)	μ
energy	E, W	*mutual capacitor	C_M
force	F	mutual conductance (transconductance)	g_m
impedance	Z_m	transistor common emitter	g_{me}
power	P	large-signal	G_{me}, g_{ME}
pressure	p	mutual inductance	M
torque	T	*mutual inductor	L_M
work	W	mutual impedance	Z_M

n		noise, excess (quantity)	
nano (unit prefix for 10^{-9})	n	(unit)	$E_{EX}, E_{N(EX)}, V_{NR(EX)}$
naperian logarithm	\log_e, \ln		$\mu V/V_{dc}$
natural logarithm	\log_e, \ln	noise factor (quantity)	F, NF, F_n
natural resonant frequency	f_n	(unit)	dB
negative	-	noise figure	See—noise factor
negative quantity		noise index (quantity)	NI
See—specific quantity		(unit)	dB
“negative reactance”	-X, X_C	noise power	N, P_n
negative supply (opamp or npn transistor)		noise, resistance	See—thermal noise
current	I_{EE}	noise temperature	T_N
voltage	V_{EE}	noise, thermal	
neper (power ratio unit)	Np	current	$i_N, I_{n(th)}, I_{nR}$
net parallel susceptance		power	$N_{th}, P_{n(th)}, P_{nR}$
($B_L - B_C$), $\pm B$		voltage	$e_N, E_{n(th)}, V_{nR}$
net series reactance		noise voltage	
($X_L - X_C$), $\pm X$		average (broadband)	$e_n, \bar{e}_n, \bar{E}_n, \bar{V}_n$
neutralizing capacitor	C_N	spot (1 Hz BW)	$e_n, V_n, e_{n/\sqrt{Hz}}, V_{n/\sqrt{Hz}}$
newton (unit)	N	noise voltage, device	
*no connection	NC	equivalent input	
noise current		1/f	E_{nf}, e_{nf}, V_{nf}
average		average (broadband)	$e_n, V_n, \bar{E}_n, \bar{e}_n, \bar{V}_n$
(broadband)	\bar{i}_n, \bar{I}_n	shot	e_s, e_{ns}, V_{ns}
spot (1 Hz BW)	$i_n, I_n, I_{n/\sqrt{Hz}}$	spot (1 Hz BW)	$e_n, V_n, e_{n/\sqrt{Hz}}, V_{n/\sqrt{Hz}}$
noise current, device			
equivalent input			
average (broadband)	\bar{i}_n, \bar{I}_n		
spot (1 Hz BW)	$i_n, I_n, I_{n/\sqrt{Hz}}$		

noise voltage, device equivalent input total ($V_n, I_n R_S$ and V_{nR_S})	E_{ni}, e_{ni}, V_{ni}	operating temperature	t_{opr}, T_{OPR}
noise voltage output	E_{no}, e_{no}, V_{no}	operational amplifier	op amp, opamp
*non-polar (capacitor)	NP	operational transconductance amplifier	OTA
*normally closed (contact)	NC	optimum resistance	R_{opt}
*normally open (contact)	NO	oscillation frequency	f_{osc}, f_o
number	n, N	output admittance	Y_o
definite	N	output admittance, transistor	
imaginary	i, j	h parameters	
indefinite	n	common base	h_{ob}
pairs of poles	N_{pp}	common collector	h_{oc}
poles	N_p	common emitter	h_{oe}
primary turns	N_p	y parameters	
secondary turns	N_s	common base	y_{ob}
turns	N, N_t	common emitter	y_{oe}
turns ratio	$n, N_{p/s}$	output capacitance	C_{out}, C_o
o		output capacitance, transistor	C_{out}, C_o
oersted (CGS unit)	Oe	common base	C_{ob}
ohm (unit)	Ω	open circuit	C_{obo}
omega (Greek letter)		common emitter	C_{oe}
capital	Ω	open circuit	C_{oeo}
script	ω	output current	I_o
on-off ratio		output current (opamp)	
See—duty factor		maximum	I_{OM}
open loop voltage amplification (opamp)	A_{VOL}	peak-to-peak	I_{OPP}
		shorted output	I_{OS}
		output frequency	f_{out}, f_o

phasor quantities		potential See—voltage	
voltage	E, V	pound (unit)	lb
polar	E_{POLAR}	pound per square inch	psi
rectangular	E_{RECT}	power	P
phi (Greek letter)	ϕ	power amplifier	PA
pi (Greek letter)	π	power factor $\cos \theta$, PF, pf, F_P	
pico (unit prefix for 10^{-12})		power gain	G_P
(pronounced “peeko”)	p	transistor, large-signal	
Planck constant	h	common base	G_{PB}
plate See—vacuum tube		common emitter	G_{PE}
literature		transistor, small signal	
*plug (male connector)	P	common base	G_{pb}
polar		common emitter	G_{pe}
admittance	$Y/\theta_Y, Y_{POLAR}$	power, device	P_D
current	$I/\theta_I, I_{POLAR}$	power dissipation	P_D
impedance	$Z/\theta_Z, Z_{POLAR}$	power, effective radiated	ERP
voltage	$E/\theta_E, E_{POLAR}$	power input	P_{in}, P_i
	$V/\theta_V, V_{POLAR}$	power level (quantity)	
pole frequency		reference 1 fW	L_P/fW
(poles and zeros)	f_p	reference 1 mW	L_P/mW
positive	+	power level (unit)	
positive quantities		reference 1 fW	dBf
See—specific quantity		reference 1 mW	dBm
positive supply, opamp		power level, acoustic	
current	I_{D+}, I_{CC}	reference 1 pW	$PWL, L_P/pW$
voltage	V_{D+}, V_{CC}	power output	P_{out}, P_o
positive supply, transistor		power, radiated	P_R
npn		power ratio (unit)	dB
current	I_{CC}	power, signal	S, P_s
voltage	V_{CC}	power, total	P_T, P_t
pnp			
current	I_{EE}		
voltage	V_{EE}		

prefix, unit multiplier			q	
atto (10 ⁻¹⁸)	a	Q factor	Q	
centi (10 ⁻²)	c	quality assurance	QA	
deci (10 ⁻¹)	d	quality control	QC	
deka (10)	da	quality factor	Q	
exa (10 ¹⁸)	E	quantity of charge		
femto (10 ⁻¹⁵)	f	(quantity)	Q	
giga (10 ⁹)	G	(unit)	C	
(pronounced jiga)		quench frequency	f _q	
hecto (10 ²)	h	quiescent current	I _q	
kilo (10 ³)	k	quiescent voltage	E _q , V _q	
mega (10 ⁶)	M			
micro (10 ⁻⁶)	μ			
milli (10 ⁻³)	m	r		
nano (10 ⁻⁹)	n	radian (unit)	rad	
peta (10 ¹⁵)	P	radius	r	
pico (10 ⁻¹²)	P	radiated power	P _R	
(pronounced peeko)		effective	ERP	
tera (10 ¹²)	T	radiation efficiency	η, η _R	
primary		radiation resistance	R _R	
current	I _p	radio detection and		
impedance	Z _p	ranging	RADAR, radar	
voltage	E _p , V _p	radio frequency	rf, r-f	
printed circuit	PC	radio frequency choke	RFC	
printed circuit board	PCB	radio frequency interference	RFI	
printed wiring board	PWB	random noise		
programable unijunction		See—thermal noise		
transistor	PUT	rate, repetition		
psi (greek letter)	ψ	(frequency)	f	
public address (system)	PA	ratio (of x to y)	x/y, x:y	
pulse energy test	PET			

ratio (unit)		real part of transistor	
current, voltage		admittance	
or power (numeric), dB		common base	
other (numeric)		forward transfer	
ratio, power supply rejection		Re (y_{fb}), g_{fb}	
(opamp) PSRR		input Re (y_{ib}), g_{ib}	
ratio, transistor		output	
forward current transfer		Re (h_{ob}), Re (y_{ob}), g_{ob}	
small signal		reverse transfer	
common base h_{fb}		Re (y_{rb}), g_{rb}	
common collector h_{fc}		common emitter	
common emitter h_{fe}		forward transfer	
static (dc)		Re (y_{fe}), g_{fe}	
common emitter h_{FE}		input Re (y_{ie}), g_{ie}	
ratio, transistor		output	
reverse voltage transfer		Re (h_{oe}), Re (y_{oe}), g_{oe}	
common base h_{rb}		reverse transfer	
common collector h_{rc}		Re (y_{re}), g_{re}	
common emitter h_{re}		rectangular form	
ratio, turns $n, N_{p/s}$		admittance Y_{RECT}	
reactance X		current I_{RECT}	
capacitive $-X, X_C$		impedance Z_{RECT}	
inductive $+X, X_L$		voltage E_{RECT}, V_{RECT}	
parallel $\pm X_P, X_P$		reference re, ref	
series $\pm X_S, X_s$		angular frequency ω_o	
reactive		angular velocity ω_o	
current $\pm I_X, I_X$		current I_{ref}	
power P_q, var		frequency f_o	
voltage $\pm E_X, \pm V_X, E_X, V_X$		voltage E_{ref}, V_{ref}	
real part of (x) $Re(x)$		reluctance (magnetic) \mathcal{R}	
		reluctivity (magnetic) v, μ^{-1}	

repetition rate (frequency)	f	resonant	
resistance	R	angular frequency	ω_o, ω_r
device input	r_i	angular velocity	ω_o, ω_r
device output	r_o	capacitance	C_o, C_r
generator	R_g	frequency	f_o, f_r
input	R_{in}, R_i	inductance	L_o, L_r
output	R_{out}, R_o	wavelength	λ_o, λ_r
parallel	R_p, R_p	reverberation time	T_{RVB}, T, T_{60}
series	R_s, R_s	reverse current	I_R
source	R_s	reverse transfer	
resistance, opamp		admittance (transistor)	
input	R_i, r_i	common base	Y_{rb}
output	R_o, r_o	common emitter	Y_{re}
resistance, transistor		reverse voltage	V_R
input		reverse voltage, peak	PRV
common base		reverse voltage transfer	
$h_{ib}, Re(h_{ib}), r_{ib}$		ratio (transistor)	
common emitter		common base	h_{rb}
$h_{ie}, Re(h_{ie}), r_{ie}$		common collector	h_{rc}
output See also—	r_o	common emitter	h_{re}
output conductance		revolutions per	
resistance, transistor,		minute (unit)	r/min, rpm
saturation	$r_{CE(SAT)}$	second (unit)	rps, r/s
resistive current	I_R	rho (Greek letter)	ρ
resistive voltage	E_R, V_R	rise time	t_r
resistivity	ρ	root-mean-square	rms
*resistor	R		
* base (transistor)	R_B		s
* collector (transistor)	R_C	saturation	SAT
* emitter (transistor)	R_E	saturation resistance	
* feedback	R_F	(transistor)	$r_{ce(SAT)}$

scalar See—magnitude		sigma (Greek letter)	
screen See—vacuum tube literature		capital	Σ
second (angle unit)	"	script	s, σ
second (time unit)	s	signs and marks	
second breakdown (transistor)		absolute value	$ $
current	$I_{S/b}$	addition	+
energy	$E_{S/b}$	approaches	\doteq
secondary		ampersand	&
current	I_s	and	&
impedance	Z_s	angle	\angle
turns	N_s	apostrophe	'
voltage	E_s, V_s	asterisk	*
sectional area	S, A	at	@
sensitivity	S	because	\because
sensitivity, power supply (opamp)	PSS	braces	{ }
series		brackets	[]
aiding inductance	L_{SA}	breve	˘
capacitance	C_S, C_s	caret	^
impedance	Z_S, Z_s	cent	¢
inductance	L_S, L_s	circumflex	ˆ
opposing inductance	L_{SO}	colon	:
reactance	$X_S, \pm X_s, X_s$	comma	,
resistance	R_S, R_s	congruent	\cong
short-circuit output current (opamp)	I_{OS}	dagger	†
shot noise See—noise		decimal point	.
siemens (unit)	S	degree	°
See also—mho		difference	\sim
		directly proportional	\propto
		division	\div
		dollar	\$
		double dagger	‡
		em dash	—
		en dash	-

signs and marks		signs and marks	
equal to	=	number	#
approximately	≈	octothorp	#
congruently	≅	paragraph	¶
identically	≡	parallel	
not	≠	parentheses	()
nearly	≈	partial differential	∂
not	≠, ≠	percent	%
very nearly	≈, ≅	period	.
equivalent	≅	plus	+
exclamation mark	!	plus or minus	±, ±
factorial	!	positive	+
greater than	>	positive or negative	±, ±
not	≠	pound	#
or equal to	≥, ≥	prime	'
hyphen	-	double (second)	"
inch	"	triple (third)	'''
infinity	∞	proportion	::
integral	∫	proportional, directly	∝
less than	<	question mark	?
not	≠	quotation marks	"", ""
or equal to	≤, ≤	radical sign	√
macron	-	ratio	:
mean value	-	second	"
minute	'	sectional symbol	§
minus	-	semicolon	;
multiplication	×, ·	solidus	/
negative	-	subtraction	-
not		therefore	∴
equal to	≠, ≠	tilde	~
greater than	>	varies as	∝
identical	≡	viculum	-
less than	<	virgule	/
		signal	S, sig

signal generator		sound navigation and	
current	I_g	ranging	SONAR, sonar
impedance	Z_g	sound power	P
resistance	R_g	sound power level,	
voltage	E_g, V_g	ref. 1 pW	PWL, $L_{P/pW}$
signal, large		sound pressure	p
See—specific quantity		sound pressure level,	
signal level		ref. 20 $\mu\text{Pa}/\text{m}^2$	
See—level			SPL, $L_{p/20\mu\text{Pa}}$
signal power	P_s	source	
signal, small		current	I_S
See—specific quantity		impedance	Z_S
signal source		resistance	R_S
current	I_S	voltage	E_S, V_S
voltage	E_S, V_S	source (field effect transistor)	
signal-to-noise ratio	S/N	See—FET literature	
silicon controlled rectifier		spacing	s
	SCR	speed	
silicon controlled switch	SCS	See also—velocity	
silicon unilateral switch	SUS	light	c
sine	sin	sound	c, v
hyperbolic	sinh	spot noise	See—noise
sinewave power	P_{sine}	square units	
single pole (switch)		centimeter	cm^2
double throw	SPDT	foot	sq ft, ft^2
single throw	SPST	inch	sq in, in^2
single sideband	SSB	meter	m^2
sink temperature		mile	sq mi, mi^2
(heatsink)	t_s, T_s	yard	sq yd, yd^2
small-signal		square wave power	P_{sqw}
See-specific quantity		standing wave ratio	
*socket (receptacle or		power	SWR
female connector)	S	voltage	S, VSWR

static transistor parameter			
See—specific parameter			
storage factor			
See—quality factor			
sum	Σ		
summation	Σ		
super high frequency	shf		
supply voltage sensitivity			
(opamp)	PSS, k_{SVS}		
susceptance	B		
capacitive	B_C		
inductive	B_L		
susceptance, transistor			
(imaginary part of			
y parameters)			
common base			
forward transfer			
	$\pm j b_{fb}, \pm b_{fb}, b_{fb}$		
input	$\pm j b_{ib}, \pm b_{ib}, b_{ib}$		
output	$\pm j b_{ob}, \pm b_{ob}, b_{ob}$		
reverse transfer			
	$\pm j b_{rb}, \pm b_{rb}, b_{rb}$		
common emitter			
forward transfer			
	$\pm j b_{fe}, \pm b_{fe}, b_{fe}$		
input	$\pm j b_{ie}, \pm b_{ie}, b_{ie}$		
output	$\pm j b_{oe}, \pm b_{oe}, b_{oe}$		
reverse transfer			
	$\pm j b_{re}, \pm b_{re}, b_{re}$		
sustaining voltage			
See—voltage			
*switch	S, SW		
		t	
		tangent	tan
		hyperbolic	tanh
		tau (Greek letter)	τ
		television	TV
		temperature	
		ambient	t_A, T_A
		case	t_C, T_C
		Celsius	t_C, t, T_C, T
		centigrade	
		See—Celsius	
		coefficient	α, TC
		Fahrenheit	t, t_F, T_F
		junction	t_J, T_J
		Kelvin	T, T_K
		lead	t_L, T_L
		noise	T_n, T_N
		sink (heat)	t_S, T_S
		tab	t_T, T_T
		tera (unit prefix for 10^{12})	T
		tesla (magnetic unit)	T
		thermal conductance	G_θ
		thermal conductivity	λ
		thermal noise	
		See—noise	
		thermal resistance	θ, R_θ
		theta (Greek letter)	
		capital	Θ
		script	θ
		threshold current	I_{TH}
		throat area	
		(acoustic horn)	S_o, A_o
		time	t

time constant	τ, T	*transformer	T
time, delay	t_d	*transistor	Q, TR
time, fall	t_f	transistor parameters	
time of one cycle	T	See—specific parameter	
time,		transistor-under-test	TUT
periodic	T	transmission loss	
phase propagation	t_ϕ	(attenuation)	
pulse duration	t_p	(quantity)	α
rise	t_r	(unit)	(numeric), dB
reverberation	T_{RVB}, T, T_{60}	*tube, vacuum	V
storage	T_S, t_S, t_{STG}	turn(s)	n, N
total	t_{TOT}	ampere (magnetic unit)	
torque	T		$A \cdot t, A, At$
total (also meaning effective or equivalent)		primary	N_p
admittance	Y_T, Y_t	ratio	n, $N_{p/s}$
capacitance	C_T, C_t	secondary	N_s
conductance	G_T, G_t		u
current	I_T, I_t	ultra-high-frequency	uhf
dissipation	P_t, P_T	ultra-violet	UV
harmonic distortion	THD	unijunction (transistor)	UJT
impedance	Z_T, Z_t	unipolar transistor	
inductance	L_T, L_t	(field effect transistor)	
power	P_t, P_T		FET
resistance	R_T, R_t	unknown	
susceptance	B_T, B_t	capacitance	C_x
time	t_{TOT}	current	I_x
voltage	E_T, V_T, E_t, V_t	impedance	Z_x
transadmittance		inductance	L_x
See—admittance		resistance	R_x
transconductance	g_m	voltage	E_x, V_x
See also—mutual conductance		unloaded Q	Q_u

v		voltage (quantity)
*vacuum tube	V	average E_{av}, V_{av}
vacuum tube voltmeter	VTVM	capacitive E_C, V_C
variable frequency oscillator	VFO	dc E_{dc}, V_{dc}
vector See also—phasor		effective E_{rms}, V_{rms}, E, V
admittance	Y	gain (amplification) A_V, A_v
current	I	generator E_g, V_g
impedance	Z	inductive E_L, V_L
voltage	E, V	input E_{in}, V_{in}, E_i, V_i
velocity See also—speed		instantaneous e, v
(quantity)	v	peak e_p, v_p
(unit)	ft/s, m/s	level L_V
velocity of light		output E_o, V_o
See—speed		peak E_{pk}, V_{pk}, E_p, V_p
velocity of sound	c, v	peak-to-peak E_{p-p}, V_{p-p}
very high frequency (30–300 MHz)	vhf	polar $E/\theta_E, E_{POLAR}$
very low frequency (3–30 kHz)	vlf	$V/\theta_V, V_{POLAR}$
very nearly equal to	\cong	power supply E_{PS}, V_{PS}
video cassette recorder	VCR	primary E_p, V_p
volt (unit)	V	rectangular E_{RECT}, V_{RECT}
ac VAC, V AC, V ac		resistive E_R, V_R
average V av		root-mean-square E_{rms}, V_{rms}, E, V
dc VDC, V DC, V dc		source E_S, V_S
peak V_{pk}		voltage controlled oscillator VCO
peak-to-peak V_{p-p}		voltage controlled resistor VCR
root-mean-square V_{rms}		voltage controlled voltage source VCVS
voltage (quantity)		
ac E_{ac}, V_{ac}		
amplification A_V, A_v		

voltage, transistor (general)		voltage, transistor breakdown	
base	V_B	base-emitter resistance	
base supply	V_{BB}	$BV_{CER}, V_{CER(SUS)}$	
base-to-emitter	V_{BE}	base-emitter short	
active	$V_{BE(ON)}$	$BV_{CES}, V_{CES(SUS)}$	
saturated	$V_{BE(SAT)}$	base open	
collector	V_C	$BV_{CEO}, V_{CEO(SUS)}$	
collector supply	V_{CC}	emitter-to-base	
collector-to-base	V_{CB}	collector open	
emitter open	V_{CBO}	$BV_{EBO}, V_{(BR)EBO}$	
collector-to-emitter	V_{CE}	voltage, transistor, sustaining	$LV, V_{(SUS)}$
base-emitter circuit	V_{CEX}	collector-to-emitter	
resistance	V_{CER}	base-emitter resistance	
short	V_{CES}	$LV_{CER}, V_{CER(SUS)}$	
voltage	V_{CEV}	base-emitter short	
base open	V_{CEO}	$LV_{CES}, V_{CES(SUS)}$	
emitter	V_E	base-emitter voltage	
emitter supply	V_{EE}	$LV_{CEV}, V_{CEV(SUS)}$	
emitter-to-base	V_{EB}	base open	
open collector	V_{EBO}	$LV_{CEO}, V_{CEO(SUS)}$	
voltage, transistor, breakdown		voltage, working	WV
collector-to-base		voltampere	
emitter open		(apparent power)	
$BV_{CBO}, V_{(BR)CBO}$		(quantity)	S, P_s, VA
collector-to-emitter		(unit)	VA
base-emitter circuit		volt-ohm meter	VOM
$BV_{CEX}, V_{CEX(SUS)}$		volume (cubic content)	V
		volume unit (similar to dBm)	vu, VU

	w	wirewound (resistor)	WW
watt (unit)	W	work	
watthour (unit)	W · h, Wh	(quantity)	W
wattsecond (unit)	W · s, Ws	(unit)	KWh, W · s, J
(joule)	J	working voltage	WV
wavelength	λ	wye connection	Y
weber (magnetic unit)	Wb		
weight	W	x y z	
See also—mass		xi (Greek letter)	
white noise See—noise		capital	Ξ
width (breadth)	b	script	ξ
wire gage (gauge)		zener (semiconductor)	
American	AWG	current	I_Z
British standard	SWG	impedance	Z_Z
steel	Stl WG	voltage	V_Z
		zeta (Greek letter)	ζ

The concise, easy-to-use, pocket guide to today's passive and active analog circuit technology.

HANDBOOK OF ELECTRONICS FORMULAS, SYMBOLS, AND DEFINITIONS

Second Edition

By John R. Brand

Get instant access to thousands of electronics formulas, symbols, and definitions that relate to modern passive and active analog circuit technology—all in this convenient guide. Designed so that you can find information quickly and without using an index, the *Handbook* is extensive enough to serve as a desktop resource—yet small enough for you to take on the job or carry in your briefcase.

Clearly rendered with schematic illustrations, the *Handbook* fully covers transistors, in both static and small signal conditions. An entirely new section on operational amplifiers (Op Amps) is organized by type, rather than alphabetically, to speed you to information even faster. Eighty new diagrams and equation pairs represent a wide range of popular filter configurations.

You'll find detailed coverage of passive circuits, including series, parallel, and complex circuit formulas—along with additional information on impedance, admittance, susceptance, bandwidth, inductance, Q factor, and much more.

The new edition of this popular resource will be welcomed by engineers, technicians, commercial operators, students, hobbyists, and everyone concerned with electronics formulas, terms, and symbols.

About the Author:

John R. Brand has worked for over 30 years as a working manager in engineering departments in major companies. He has served as Director of Research and Development and as Director of Engineering, and has been issued 23 U.S. patents.